

EE 2720, Spr. 2012

Homework # 3 solution

EE 2720, Homework # 3 solutions (1)

Problem 1: The right side of (T11') is

$$(X+Y) \cdot (X'+Z) = X \cdot Z + X' \cdot Y \quad (1)$$

The left side of ~~(T11')~~ (T11') is

$$\begin{aligned} (X+Y) \cdot (X'+Z) \cdot (Y+Z) &= (X \cdot Z + X' \cdot Y) \cdot (Y+Z) \\ &= X \cdot Z \cdot Y + X \cdot Z \cdot Z + X' \cdot Y \cdot Y + X' \cdot Y \cdot Z \\ &= X \cdot Y \cdot Z + X \cdot Z + X' \cdot Y + X' \cdot Y \cdot Z \\ &= X \cdot Z + X' \cdot Y + X \cdot Y \cdot Z + X' \cdot Y \cdot Z \\ &= X \cdot Z + X' \cdot Y + Y \cdot Z \cdot (X+X') \\ &= X \cdot Z + X' \cdot Y + Y \cdot Z \cdot 1 = X \cdot Z + X' \cdot Y + \underbrace{Y \cdot Z} \end{aligned}$$

↑  
consensus  
term and  
can be elimi-  
nated accor-  
ding to (T11)

$$= X \cdot Z + X' \cdot Y \quad (2)$$

Because both right and left side of (T11') reduced to the same expression (which is  $X \cdot Z + X' \cdot Y$ ), theorem (T11') is valid.

EE 2720, HW # 3 solutions cont (2)

Problem 2: I will first provide the canonical sum and then the canonical product for each logic function.


$$(a) F = \sum_{x,y} (1,2) = X' \cdot Y + X \cdot Y' = \prod_{x,y} (0,3) \\ = (X+Y) \cdot (X'+Y')$$

$$(b) \prod_{A,B} (0,1,2) = \text{minterm } 3 = A \cdot B \\ = \prod_{A,B} (0,1,2) = (A+B) \cdot (A+B') \cdot (A'+B)$$

$$(c) F = \sum_{A,B,C} (3,4,6,7) = A' \cdot B \cdot C' + A \cdot B' \cdot C' \\ + A \cdot B \cdot C' + A \cdot B \cdot C = \prod_{A,B,C} (0,1,3,5) \\ = (A+B+C) \cdot (A+B+C') \cdot (A+B'+C') \cdot (A'+B+C')$$

$$(d) F = \prod_{M,N,P} (0,1,3,6,7) = \sum_{M,N,P} (2,4,5) \\ = M' \cdot N \cdot P' + M \cdot N' \cdot P' + M \cdot N' \cdot P$$

$$\text{XXXXXXXXXX} = \prod_{M,N,P} (0,1,3,6,7) \\ = (M+N+P) \cdot (M+N+P') \cdot (M+N'+P') \cdot \\ (M'+N'+P) \cdot (M'+N'+P')$$

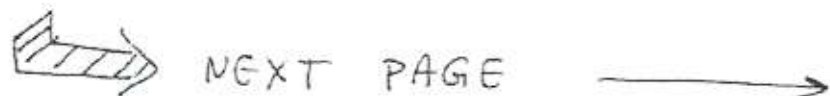 NEXT PAGE  $\longrightarrow$

EE 2720, HW # 3 solutions cont. (3)

Problem 2 cont: (e)  $F = X + Y' \cdot z'$

$$= X \cdot (\underbrace{Y+Y'}_{\perp}) \cdot (\underbrace{z+z'}_{\perp}) + Y' \cdot z' \cdot (\underbrace{X+X'}_{\perp})$$
$$= X \cdot (Y \cdot z + Y \cdot z' + Y' \cdot z + Y' \cdot z') + Y' \cdot z' \cdot X + Y' \cdot z' \cdot X'$$
$$= \underset{\perp}{X} \cdot \underset{\perp}{Y} \cdot \underset{\perp}{z} + \underset{\perp}{X} \cdot \underset{\perp}{Y} \cdot \underset{0}{z'} + \underset{\perp}{X} \cdot \underset{0}{Y'} \cdot \underset{\perp}{z} + \underset{\perp}{X} \cdot \underset{0}{Y'} \cdot \underset{0}{z'}$$
$$+ \cancel{\underset{\perp}{X} \cdot \underset{0}{Y'} \cdot \underset{0}{z'}} + \underset{0}{X'} \cdot \underset{0}{Y'} \cdot \underset{0}{z'}$$
$$= \Sigma_{X,Y,z} (0, 4, 5, 6, 7) = \Pi_{X,Y,z} (\perp, 3, 3)$$
$$= (X+Y+z') \cdot (X+Y'+z) \cdot (X+Y'+z')$$

(f)  $F = A' \cdot B + B' \cdot C + A$

$$= A' \cdot B \cdot (\underbrace{C+C'}_{\perp}) + B' \cdot C \cdot (\underbrace{A+A'}_{\perp})$$
$$+ A \cdot (\underbrace{B+B'}_{\perp}) \cdot (\underbrace{C+C'}_{\perp})$$

 NEXT PAGE  $\rightarrow$

EE 2720, HW#3 solutions cont. (4)

Problem 2(f) cont.:

$$= A' \cdot B \cdot C + A' \cdot B \cdot C' + A \cdot B' \cdot C + A' \cdot B' \cdot C$$

$$+ A \cdot (B \cdot C + B \cdot C' + B' \cdot C + B' \cdot C')$$

$$= A' \cdot B \cdot C + A' \cdot B \cdot C' + A \cdot B' \cdot C + A' \cdot B' \cdot C$$

$$+ A \cdot B \cdot C + A \cdot B \cdot C' + A \cdot B' \cdot C + A \cdot B' \cdot C'$$

$$= \sum_{A,B,C} (1, 2, 3, 4, 5, 6, 7) = \text{maxterm } 0 = A+B+C$$


~~Handwritten scribbles and crossed-out text covering the bottom half of the page.~~

$$\begin{aligned}
 \text{Problem 3: } F &= (a'+b) \cdot (a+bc') \cdot (b'+c) \\
 &= (a'+b + \underbrace{c \cdot c'}_0) \cdot (a+bc' + \underbrace{b \cdot b'}_0) \cdot (b'+c + \underbrace{a \cdot a'}_0) \\
 &= (a'+b+c) \cdot (a'+b+c') \cdot (a+bc'+b) \cdot (a+bc'+b') \\
 &\quad (b'+c+a) \cdot (b'+c+a') \\
 &= \begin{pmatrix} a'+b+c \\ 1 & 0 & 0 \end{pmatrix} \cdot \begin{pmatrix} a'+b+c' \\ 1 & 0 & 1 \end{pmatrix} \cdot \begin{pmatrix} a+bc'+b \\ 0 & 0 & 1 \end{pmatrix} \cdot \begin{pmatrix} a+bc'+b' \\ 0 & 1 & 1 \end{pmatrix} \\
 &\quad \begin{pmatrix} a+b'+c \\ 0 & 1 & 0 \end{pmatrix} \cdot \begin{pmatrix} a'+b'+c \\ 1 & 1 & 0 \end{pmatrix} \\
 &= \Pi_{a,b,c} (1, 2, 3, 4, 5, 6).
 \end{aligned}$$

Problem 4: (a) Algebraic approach:

$$\begin{aligned}
 F &= a' \cdot b + c \cdot d' + e \\
 &= \left[ (a' \cdot b + c \cdot d' + e)' \right]' \\
 &= \left[ (a' \cdot b)' \cdot (c \cdot d')' \cdot e' \right]' \quad (1)
 \end{aligned}$$

From (1) we get the following figure

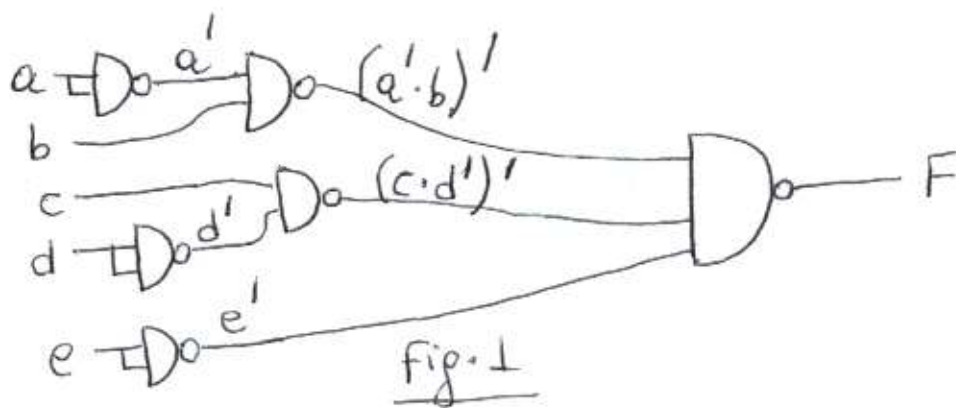


(b) Graphical approach: I first provide a


logic circuit showing an AND-OR realization of F

(Figure on next page)

Prob. 4 cont

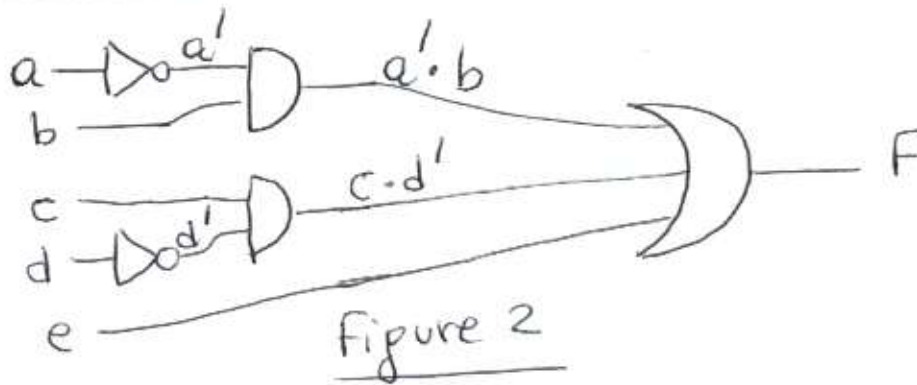

From the above fig. 2 one gets

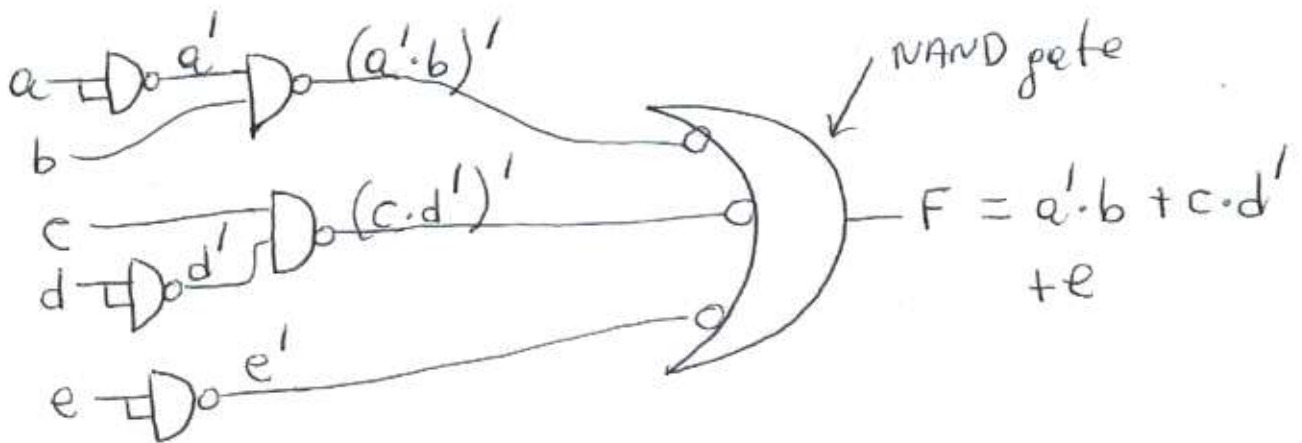




Problem 5: (a) Algebraic approach

$$\begin{aligned}
 F &= (a'+b) \cdot (c+d') \cdot e \\
 &= \left[ \left[ (a'+b) \cdot (c+d') \cdot e \right]' \right]' \\
 &= \left[ (a'+b)' + (c+d')' + e' \right]' \quad (2)
 \end{aligned}$$


From (2) we get the following figure

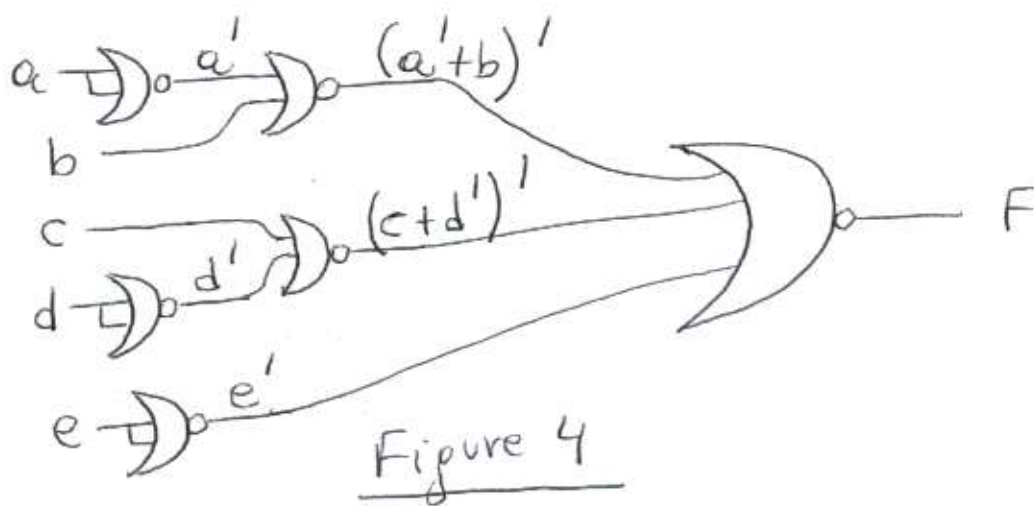


(b) Graphical approach: I first provide

a logic circuit showing an OR-AND realization of  $F$ . This is shown on the next page.

Prob. 5 cont.

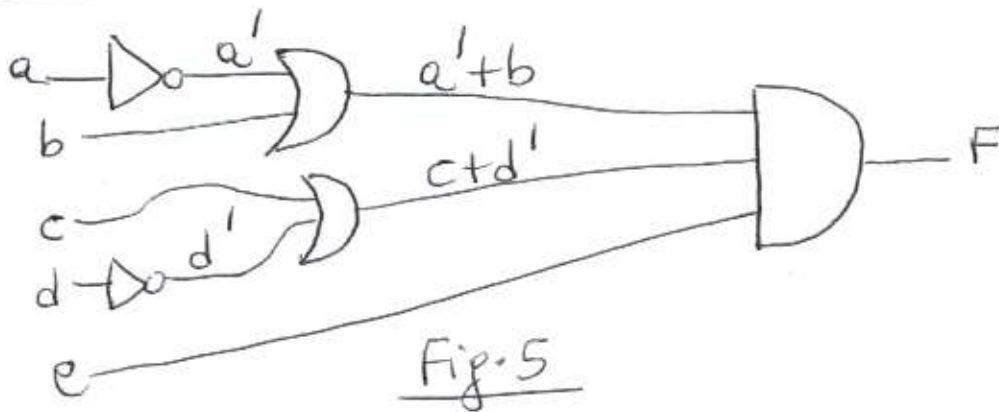

From the above Figure 5 one gets

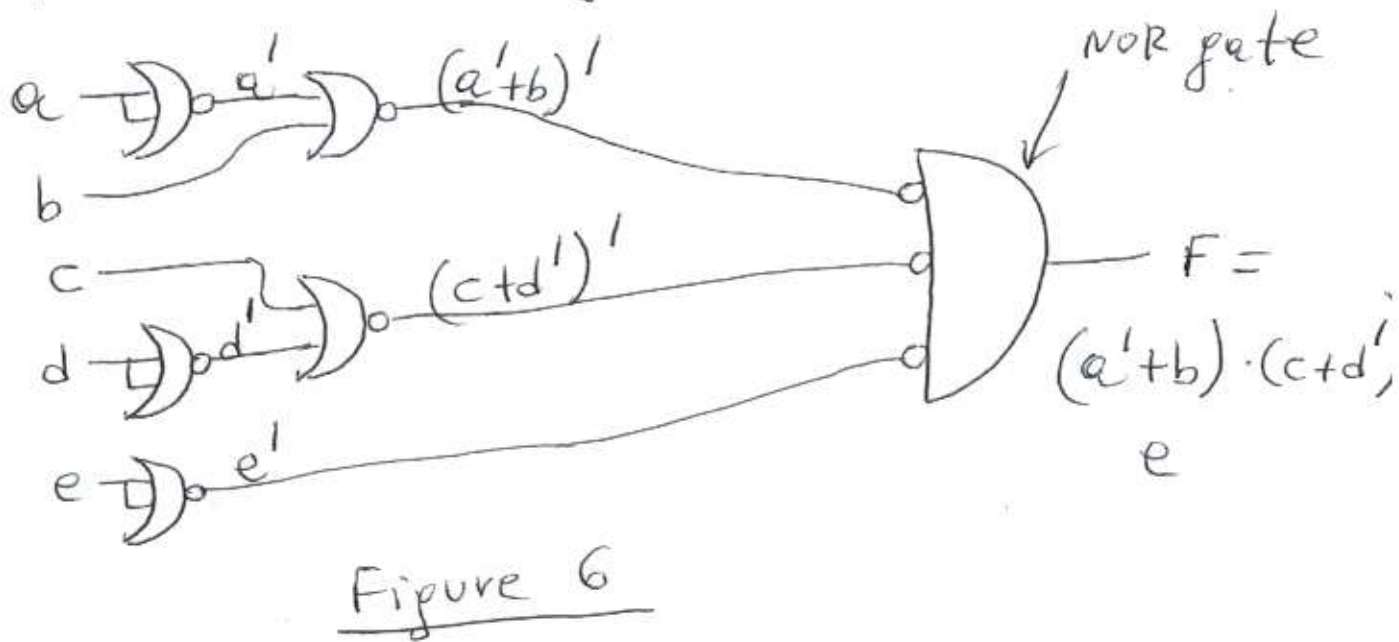

Problem 6:

(a) Proof of (5) or proof of  $X \oplus 0 = X$

- Case  $X=0$ :  $0 \oplus 0 = 0$
- Case  $X=1$ :  $1 \oplus 0 = 1$

(b) Proof of (6) or proof of  $X \oplus 1 = X'$

- Case  $X=0$ :  $0 \oplus 1 = 1$
- Case  $X=1$ :  $1 \oplus 1 = 0$

(c) Proof of (7) or proof of  $X \oplus X = 0$

- Case  $X=0$ :  $0 \oplus 0 = 0$
- Case  $X=1$ :  $1 \oplus 1 = 0$


(d) Proof of (8) or proof of  $X \oplus X' = 1$

- Case  $X=0$ :  $0 \oplus 1 = 1$
- Case  $X=1$ :  $1 \oplus 0 = 1$

Note: The above eqs. (5) - (8) can also be proven algebraically. How?

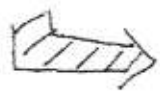(e) Proof of (11) or proof of

$$X \cdot (Y \oplus Z) = X \cdot Y \oplus X \cdot Z$$



NEXT PAGE →

EE 2720, HW #3 solutions cont.

11

Problem 6 (c) cont.:

The right side of (11) is:

$$\begin{aligned} X \cdot Y \oplus X \cdot Z &= X \cdot Y \cdot (X \cdot Z)' + (X \cdot Y)' \cdot X \cdot Z \\ &= X \cdot Y \cdot (X' + Z') + (X' + Y') \cdot X \cdot Z \\ &= \cancel{X \cdot Y \cdot X'} + X \cdot Y \cdot Z' + \cancel{X' \cdot X \cdot Z} + Y' \cdot X \cdot Z \\ &= X \cdot Y \cdot Z' + X \cdot Y' \cdot Z = X \cdot (Y \cdot Z' + Y' \cdot Z) \\ &= X \cdot (Y \oplus Z) = \text{left side of (11)} \Rightarrow \text{proven.} \end{aligned}$$