

EE 2720, Spr. 2012

Homework #4

Due Monday March 26, 2012, in class

Problem 1: Design a circuit to convert a number represented in Excess-3 code to BCD. You must use Karnaugh maps in this problem. Provide a circuit diagram as well.

Problem 2: Design a combinational logic circuit with three inputs A, B, C and three outputs X, Y, Z. When the binary inputs are 0, 1, 2 or 3, the binary output is two greater than the binary input. When the binary input is 4, 5, 6, or 7, the binary output is 2 less than the input. You must use Karnaugh maps in this problem.

Problem 3: A full adder (FA) is a circuit that adds three binary digits X, Y, C_{in} , producing a sum and a carry, S and C_{out} . The sum S is 1 if one or three of X, Y, C_{in} are 1. The carry C_{out} is 1, if two out of three, or all three of X, Y, C_{in} are 1. Design a full adder circuit using AND, OR and NOT gates; (I want an AND-OR realization). Show all your work, truth table, Karnaugh maps, logic equations and logic diagrams. (Here you learned something new that I was going to do in class!!)

Problem 4: A half adder (HA) is a circuit that adds two binary digits X, Y , producing a sum and a carry S and C_{out} . The sum S is 1 if one of X or Y are 1. The carry C_{out} is 1 if both X and Y are 1. Design a half adder circuit using AND, OR and NOT gates; (I want an AND-OR realization). Show all your work, truth table, Karnaugh maps,

HW# 4 cont.

Problem 4 cont: logic equations and logic diagrams
 (again here you learned something new that I
 was going to do in class!!) *don't do this.*

Problem 5: Using Karnaugh maps, find a simplified sum-of-products expression for the logic function $F = \sum_{w,x,y,z}(1, 2, 4, 7, 8, 11, 13, 14)$.

Problem 6: Using Karnaugh maps, find a simplified sum-of-products expression for each of the following logic functions:

- (a) $F = \sum_{x,y,z}(1, 3, 5, 6, 7)$
- (b) $F = \sum_{w,x,y,z}(1, 4, 5, 6, 7, 9, 14, 15)$
- (c) $F = \prod_{w,x,y}(0, 1, 3, 4, 5)$
- (d) $F = \sum_{w,x,y,z}(0, 2, 5, 7, 8, 10, 13, 15)$
- (e) $F = \prod_{A,B,C,D}(1, 7, 9, 13, 15)$.

Problem 7: Using Karnaugh maps, find a simplified product-of-sums expression for each logic function of problem 6 above. Combine 0's here.

Problem 8: Using Karnaugh maps, find a simplified sum-of-products expression for each of the following logic functions:

Problem 9 cont:

- (a) $F = \sum_{w,x,y,z} (0,1,3,5,14) + d(8,15)$
- (b) $F = \sum_{w,x,y,z} (0,1,2,8,11) + d(3,9,15)$
- (c) $F = \sum_{A,B,C,D} (1,5,9,14,15) + d(11)$
- (d) $F = \sum_{A,B,C,D} (1,5,6,7,9,13) + d(4,15)$

Problem 10: Using karnaugh maps, find a simplified product-of-sums expression for each logic function of problem 9 above.

Problem 11: Derive a simplified product-of-sums expression for the prime BCD-digit detector described in handout # 16. In this problem, you must, of course provide a Karnaugh map.

Note: Enjoy this homework. It is lots of fun!! It is about karnaugh maps mainly, which is the most important subject in EE 2720. So enjoy it!!

~~Alex~~

Alex!!