

EE 2723 ~~EE 2723~~ Spring 2012


Homework # 7 and solution of HW # 7

Not to be returned; (it will not be  
graded)

Homework # 7 and solution of HW# 7

Problem: Write an explicit structural Verilog description to implement  $x = (a \oplus b) + c$ . Here  $\oplus$  denotes EXCLUSIVE-OR operation and  $+$  denotes OR operation. You are not allowed to instantiate one Exclusive-OR gate. Use AND, OR, NOT gates instead. Your module should be complete including module name, port list, declaration of inputs and outputs, declaration of wires and proper gate instantiation.

② Write an implicit structural Verilog description to implement  $x = (a \oplus b) + c$ .

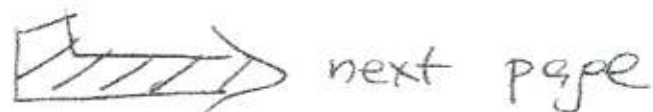 next page

HW#7 and solution of HW#7 cont.

Solution: (a)  $x = (a \oplus b) + c = a' \cdot b + a \cdot b' + c$

```

module alex(x, a, b, c);
  input a, b, c;
  output x;
  wire na, nb, na_b, a_nb;
  not n1(na, a);
  not n2(nb, b);
  and a1(na_b, na, b);
  and a2(a_nb, a, nb);
  or o1(x, na_b, a_nb, c);
endmodule

```

```

(b) module george(x, a, b, c);
  input a, b, c;
  output x;
  assign x = (a ^ b) | c;
endmodule

```