

EE 3755

Verilog Handout # 5

```

/// LSU EE 3755 -- Fall 2001 -- Computer Organization
///
/// Verilog Notes 5 -- Integer Addition and Subtraction

/// Contents
///
/// Representation of Integers in Computers
/// Binary Addition and Subtraction
/// Construction of ALUs
/// Carry Look Ahead Adders
/// Flat Carry Look-Ahead Adder
/// Two-Level Carry Look-Ahead Adder
/// Real-World Integer Adders (Under Construction)

/// References
///
/// :P: Palnitkar, "Verilog HDL"
/// :Q: Qualis, "Verilog HDL Quick Reference Card Revision 1.0"
/// :H: Hyde, "Handbook on Verilog HDL"
/// :LRM: IEEE, Verilog Language Reference Manual (Hawaii Section Numbering)
/// :PH: Patterson & Hennessy, "Computer Organization & Design"

```

```

/////////////////////////////////////////////////////////////////
/// Representation of Integers in Computers

```

```

/// :PH: 4.1, 4.2

```

```

/// Difference between real-world and computer integers:
///
/// Real-world integers don't have a maximum or minimum.
/// Computer integers do because they are represented by a fixed
/// number of bits. (With a few exceptions.)
///
/// Keep this in mind for overflow and negative numbers.

```

```

/// Two's Complement Representation
///
/// Since the use of two's complement is nearly universal, "signed integer"
/// is usually understood to mean "two's complement signed integer."
///
/// Let  $i$  be a positive integer. The  $n$ -bit two's complement representation/
/// of  $-i$  is obtained by:
///
/// Start with the  $n$ -bit binary representation of  $i$ .
/// Invert the bits in  $i$ .
/// Add 1.
///
/// In Verilog or C:  $\text{minus } i = \sim i + 1$ ;
///

```

```

/// Two's Complement Sign Bit
///
/// A two's complement representation is negative if and only if the
/// most-significant bit is 1.
///
/// Not surprisingly, the MSB is called the /sign bit/.

```

```

/// Example: Find 4-bit representation of -5.
///
/// Start: +5 = 0101
/// Invert: 1010
/// Add 1: 1011
/// So -5 = 1011

```

```

/// Range of Representation:
///
/// (Smallest and largest representable numbers.)

```

```

//
// Unsigned n-bit range:
//   Minimum: 0
//   Maximum: (2^n)-1   Two-to-the-n minus 1.
//   Example: 4-bit: Minimum 0, maximum 15.
//
// Signed 2's complement n-bit range:
//   Minimum: -2^{n-1}
//   Maximum: 2^{n-1}-1
//   Example: 4-bit: Minimum -8, maximum 7.

// Remember These 4-bit Signed Numbers:
//   0: 0000
//  -1: 1111
//  -2: 1110
//  -7: 1001
//  -8: 1000

////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
/// Binary Addition and Subtraction

// :PH: 4.3 and classroom lectures.
//
// If necessary, review binary addition.
// Notes here discuss overflow.

/// Overflow Definition
//
// Describes an arithmetic operation in which the result cannot
// be represented. The result might be too large or too small.

/// Overflow in Unsigned Addition
//
// There is overflow in unsigned addition of two n-bit numbers
// if there is a carry out (from the MSB).

// Example:
//
// Addition of 4-bit unsigned representations of 10 and 7:
//
// 1010
// +0111
// ----
// 10001
// C
//
// The digit over the "C" is the carry out. Since it is 1 the
// addition overflowed.

/// Overflow Detection
//
// There has been overflow in the addition of two n-bit two's complement
// numbers when the sign of the two operands are the same and the sign
// of the sum is different.
//
// This implies that there can not be overflow when the signs of the
// two operands are different.
//
// A carry out does not necessarily indicate overflow.

// :Example:
//
// 6: 0110   Sign of first operand: 0 (positive)
// -2: 1110  Sign of second operand: 1 (negative)
// ----
// 4: 10100  Sign of sum: 0 (positive), sum correct

```

```

//      CS
//
// The digit over the C is the carry out. Since this is signed
// addition, ignore it.
//
// The sign of the two operands are different, so overflow is not possible.

// :Example:
//
// 6: 0110 Sign of first operand: 0 (positive)
// 2: 0010 Sign of second operand: 0 (positive)
//     ----
// -8: 01000 Sign of sum: 1 (negative), addition overflowed so sum wrong.
//      CS
//
// The digit over the C is the carry out. In this case there is no
// carry out, which is irrelevant since carry out is ignored.
//
// The sign of the two operands are the same, 0, and is different than
// the sign of the sum, 1, so there is overflow.

// :Example:
//
// -6: 1010 Sign of first operand: 1 (negative)
// -2: 1110 Sign of second operand: 1 (negative)
//     ----
// -8: 11000 Sign of sum: 1 (negative), no overflow, sum correct.
//      CS
//
// The digit over the C is the carry out.
//
// The sign of the two operands are the same, 1, and is the same as
// the sign of the sum, 1, so there is no overflow.

```

```

////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
/// Construction of ALUs

```

```
// :PH: 4.5
```

```
// /ALU/: The primary device in a computer for performing integer
// arithmetic and logical operations. [There may be other /functional units/
// that perform additional integer and also floating-point operations.]

// Goal: Design ALU that can share as much hardware as possible.
//
// First ALU below does not share much hardware.
// In the second ALU below adder is shared for addition, subtraction, and
// less than.

```

```
/// First ALU
```

```
//
// Operations: and (0), or (1), add (2)
// Numbers refer to "op" (operation) input.

// Step 1:
// Define a slice module that can perform any of the operations
// (and, or, add) on two one-bit inputs and a carry.
//
// Step 2:
// Connect the slices to construct the entire ALU.

```

```
// :Example:
```

```
//
// Slice for first alu. See :PH: Figure 4.14

```

```

module alu_slice(result,cout,a,b,cin,op);
    input a, b, cin;
    input [1:0] op;
    output      result, cout;

    parameter    op_and = 0;
    parameter    op_or  = 1;
    parameter    op_add  = 2;

    bfa_implicit bfa(sum,cout,a,b,cin);

    assign result =
        op == op_and ? a & b :
        op == op_or  ? a | b :
        op == op_add ? sum : 0;

endmodule

// :Example:
//
// ALU using slice above.  See :PH: Figure 4.15.

module alu(result,a,b,cin,op);
    input [31:0] a, b;
    input      cin;
    input [1:0] op;
    output [31:0] result;

    wire [31:0] cout;

    alu_slice slice0(result[0],cout[0],a[0],b[0],1'b0,op);
    alu_slice slice1(result[1],cout[1],a[1],b[1],cout[0],op);
    alu_slice slice2(result[2],cout[2],a[2],b[2],cout[1],op);
    alu_slice slice3(result[3],cout[3],a[3],b[3],cout[2],op);
    alu_slice slice4(result[4],cout[4],a[4],b[4],cout[3],op);
    alu_slice slice5(result[5],cout[5],a[5],b[5],cout[4],op);
    alu_slice slice6(result[6],cout[6],a[6],b[6],cout[5],op);
    alu_slice slice7(result[7],cout[7],a[7],b[7],cout[6],op);
    alu_slice slice8(result[8],cout[8],a[8],b[8],cout[7],op);
    alu_slice slice9(result[9],cout[9],a[9],b[9],cout[8],op);
    alu_slice slice10(result[10],cout[10],a[10],b[10],cout[9],op);
    alu_slice slice11(result[11],cout[11],a[11],b[11],cout[10],op);
    alu_slice slice12(result[12],cout[12],a[12],b[12],cout[11],op);
    alu_slice slice13(result[13],cout[13],a[13],b[13],cout[12],op);
    alu_slice slice14(result[14],cout[14],a[14],b[14],cout[13],op);
    alu_slice slice15(result[15],cout[15],a[15],b[15],cout[14],op);
    alu_slice slice16(result[16],cout[16],a[16],b[16],cout[15],op);
    alu_slice slice17(result[17],cout[17],a[17],b[17],cout[16],op);
    alu_slice slice18(result[18],cout[18],a[18],b[18],cout[17],op);
    alu_slice slice19(result[19],cout[19],a[19],b[19],cout[18],op);
    alu_slice slice20(result[20],cout[20],a[20],b[20],cout[19],op);
    alu_slice slice21(result[21],cout[21],a[21],b[21],cout[20],op);
    alu_slice slice22(result[22],cout[22],a[22],b[22],cout[21],op);
    alu_slice slice23(result[23],cout[23],a[23],b[23],cout[22],op);
    alu_slice slice24(result[24],cout[24],a[24],b[24],cout[23],op);
    alu_slice slice25(result[25],cout[25],a[25],b[25],cout[24],op);
    alu_slice slice26(result[26],cout[26],a[26],b[26],cout[25],op);
    alu_slice slice27(result[27],cout[27],a[27],b[27],cout[26],op);
    alu_slice slice28(result[28],cout[28],a[28],b[28],cout[27],op);
    alu_slice slice29(result[29],cout[29],a[29],b[29],cout[28],op);
    alu_slice slice30(result[30],cout[30],a[30],b[30],cout[29],op);
    alu_slice slice31(result[31],cout[31],a[31],b[31],cout[30],op);

endmodule

```

```

// Second ALU
//
// This ALU can perform additional operations: subtract and less than.
// Both subtract and less than use the adder's hardware.

```

```

// :Example:
//
// Slice for second ALU. See :PH: Figure 4-17. Input less is
// generated by MSB slice, alu_slice2MSB for bit zero and 0 for all
// the others.

```

```

module alu_slice2(result,cout,a,b,cin,op,binvert,less);
  input a, b, cin, binvert, less;
  input [1:0] op;
  output      result, cout;

  parameter  sop_and = 0;
  parameter  sop_or  = 1;
  parameter  sop_add = 2;
  parameter  sop_slt = 3;

  wire       b2 = binvert ? ~b : b;
  wire       sum;

  bfa_implicit bfa(sum,cout,a,b2,cin);

  assign result =
    op == sop_and ? a & b :
    op == sop_or  ? a | b :
    op == sop_add ? sum :
    less; // else, op == sop_slt

endmodule

```

Fig 4.17 πάνω

```

// :Example:
//
// Bit slice for bit 31. This also generates a set and overflow
// output.

```

```

module alu_slice2MSB(result,set,overflow,a,b,cin,op,binvert,less);
  input a, b, cin, binvert, less;
  input set, overflow;
  input [1:0] op;
  output      result;

  parameter  sop_and = 0;
  parameter  sop_or  = 1;
  parameter  sop_add = 2;
  parameter  sop_slt = 3;

  wire       b2 = binvert ? ~b : b;
  wire       sum;

  assign overflow =
    op != sop_add ? 1'b0 :
    a != b2       ? 1'b0 :
    a == sum      ? 1'b0 : 1'b1;

  assign set = a != b2 ? sum : a;

  bfa_implicit bfa(sum,cout,a,b2,cin);

  assign result =
    op == sop_and ? a & b :
    op == sop_or  ? a | b :
    op == sop_add ? sum :

```

Fig 4.17 κάτω

```

        less; // else, op == sop_slt
    endmodule

// :Example:
//
// Second ALU. The same module is used for bits 0-30, bit 31
// is computed by a special module that also determines overflow
// and whether a < b.

module alu2(result,overflow,a,b,alu_op);
    input [31:0] a, b;
    input [2:0] alu_op;
    output [31:0] result;
    output      overflow;

    wire [31:0] cout;

    parameter op_and = 0;
    parameter op_or  = 1;
    parameter op_slt = 2;
    parameter op_add = 3;
    parameter op_sub = 4;

    parameter sop_and = 0;
    parameter sop_or  = 1;
    parameter sop_add = 2;
    parameter sop_slt = 3;

    wire [1:0] op =
        alu_op == op_and ? sop_and :
        alu_op == op_or  ? sop_or  :
        alu_op == op_slt ? sop_slt :
        alu_op == op_add ? sop_add :
        alu_op == op_sub ? sop_add : 0;

    wire      binvert = alu_op == op_sub || alu_op == op_slt;

    wire      set; // MSB of sum.

    alu_slice2 slice0(result[0],cout[0],a[0],b[0],binvert,op,binvert,set);
    alu_slice2 slice1(result[1],cout[1],a[1],b[1],cout[0],op,binvert,1'b0);
    alu_slice2 slice2(result[2],cout[2],a[2],b[2],cout[1],op,binvert,1'b0);
    alu_slice2 slice3(result[3],cout[3],a[3],b[3],cout[2],op,binvert,1'b0);
    alu_slice2 slice4(result[4],cout[4],a[4],b[4],cout[3],op,binvert,1'b0);
    alu_slice2 slice5(result[5],cout[5],a[5],b[5],cout[4],op,binvert,1'b0);
    alu_slice2 slice6(result[6],cout[6],a[6],b[6],cout[5],op,binvert,1'b0);
    alu_slice2 slice7(result[7],cout[7],a[7],b[7],cout[6],op,binvert,1'b0);
    alu_slice2 slice8(result[8],cout[8],a[8],b[8],cout[7],op,binvert,1'b0);
    alu_slice2 slice9(result[9],cout[9],a[9],b[9],cout[8],op,binvert,1'b0);
    alu_slice2 slice10(result[10],cout[10],a[10],b[10],cout[9],op,binvert,1'b0);
    alu_slice2 slice11(result[11],cout[11],a[11],b[11],cout[10],op,binvert,1'b0);
    alu_slice2 slice12(result[12],cout[12],a[12],b[12],cout[11],op,binvert,1'b0);
    alu_slice2 slice13(result[13],cout[13],a[13],b[13],cout[12],op,binvert,1'b0);
    alu_slice2 slice14(result[14],cout[14],a[14],b[14],cout[13],op,binvert,1'b0);
    alu_slice2 slice15(result[15],cout[15],a[15],b[15],cout[14],op,binvert,1'b0);
    alu_slice2 slice16(result[16],cout[16],a[16],b[16],cout[15],op,binvert,1'b0);
    alu_slice2 slice17(result[17],cout[17],a[17],b[17],cout[16],op,binvert,1'b0);
    alu_slice2 slice18(result[18],cout[18],a[18],b[18],cout[17],op,binvert,1'b0);
    alu_slice2 slice19(result[19],cout[19],a[19],b[19],cout[18],op,binvert,1'b0);
    alu_slice2 slice20(result[20],cout[20],a[20],b[20],cout[19],op,binvert,1'b0);
    alu_slice2 slice21(result[21],cout[21],a[21],b[21],cout[20],op,binvert,1'b0);
    alu_slice2 slice22(result[22],cout[22],a[22],b[22],cout[21],op,binvert,1'b0);
    alu_slice2 slice23(result[23],cout[23],a[23],b[23],cout[22],op,binvert,1'b0);
    alu_slice2 slice24(result[24],cout[24],a[24],b[24],cout[23],op,binvert,1'b0);
    alu_slice2 slice25(result[25],cout[25],a[25],b[25],cout[24],op,binvert,1'b0);
    alu_slice2 slice26(result[26],cout[26],a[26],b[26],cout[25],op,binvert,1'b0);

```

} ALU

} slice of ALU

```

alu_slice2 slice27(result[27],cout[27],a[27],b[27],cout[26],op,binvert,1'b0);
alu_slice2 slice28(result[28],cout[28],a[28],b[28],cout[27],op,binvert,1'b0);
alu_slice2 slice29(result[29],cout[29],a[29],b[29],cout[28],op,binvert,1'b0);
alu_slice2 slice30(result[30],cout[30],a[30],b[30],cout[29],op,binvert,1'b0);
alu_slice2MSB slice31(result[31],set,overflow,a[31],b[31],
                    cout[30],op,binvert,1'b0);

```

```
endmodule
```

```
// :Example:
```

```
//
```

```
// Testbench for second ALU. Material for this testbench not covered.
```

```
module test_alu();
```

```

    wire [31:0] result;
    wire        overflow;
    reg [31:0]  a, b;
    reg [2:0]   alu_op;

```

```
    alu2 alu(result,overflow,a,b,alu_op);
```

```
    integer    i, shadow_result, shadow_overflow, as, bs;
```

```
    initial begin
```

```
        alu_op = alu.op_sub;
```

```
        for(i=0; i<10000; i=i+1) begin
```

```

            as = $random;
            a = as;
            bs = $random;
            b = bs;

```

```
            alu_op = ( $random & 32'h7fffffff ) % 5;
```

```
            case( alu_op )
```

```
                alu.op_and:
```

```
                begin
```

```
                    shadow_result = as & bs;
                    shadow_overflow = 0;
                end
```

```
                alu.op_or:
```

```
                begin
```

```
                    shadow_result = as | bs;
                    shadow_overflow = 0;
                end
```

```
                alu.op_add:
```

```
                begin
```

```
                    shadow_result = as + bs;
                    shadow_overflow = as > 0 && bs > 0 && shadow_result < 0
                                        || as < 0 && bs < 0 && shadow_result > 0;
                end
```

```
                alu.op_sub:
```

```
                begin
```

```
                    shadow_result = as - bs;
                    shadow_overflow = as > 0 && bs < 0 && shadow_result < 0
                                        || as < 0 && bs > 0 && shadow_result > 0;
                end
```

```
                alu.op_slt:
```

```
                begin
```

```
                    shadow_result = as < bs;
                    shadow_overflow = 0;
                end
```

```
            end
```

```
        endcase
```



```

#1;

if( shadow_result != result ) begin
    $display("Wrong result op %d, %x op %x = %x != %x",
            alu_op, a, b, shadow_result, result);
    $stop;
end
if( shadow_overflow != overflow ) begin
    $display("Wrong overflow op %d, %x op %x; %d != %d",
            alu_op, a, b, shadow_overflow, overflow);
    $stop;
end
end
end
$display("Done with test.");
end

endmodule

////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
/// Carry Look Ahead Adders

// :PH: 4.5 (In middle of section 4.5.)

/// Motivation
//
// Ripple adders take to long;
// Delay of n-bit adder is 2n+1 gate delays.
// Modern processors need 1-cycle 64-bit adders,
// that's 129 gate delays in one cycle. A ripple adder is too slow.

/// Carry Look-Ahead Adder Properties
//
// More expensive but much faster.
// Cost varies by configuration.
//
// Flat (One-level) Carry Look-Ahead Adder
// Delay is six gate delays, regardless of size. (Counting xor as 3 gates.)
// Cost is proportional to square of number of bits.
// Requires large fan-in gates, which may not be practical.
//
// Multiple Level Carry Look-Ahead Adders. (Second level of abstraction.)
// Delay typically proportional to square root number of bits or lower.
// Cost lower than flat CLA.
// Designed to fit technology constraints and capabilities (fan-in, etc.)

////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
/// Flat Carry Look-Ahead Adder

// :PH: 4.5 (In middle of section 4.5.)

/// Flat Carry Look-Ahead Adder Structure
//
// At each slice (pair of input bits and output bit) create a
// /generate/ and /propagate/ signal to be used by more-significant
// bits.
//
// At each slice use generate and propagate signals of less-significant
// bits to produce a sign bit.
//
// See examples below.

// :Example:
//
// A slice for a CLA. Like a BFA, its inputs are one bit
// of each operand, a and b, and a carry in, cin. Its outputs

```

```

// are one bit of the sum and, instead of a cout, a generate
// and propagate signal.

module cla_slice(sum,g,p,a,b,cin);
  input a, b;
  input cin; // Determined using other generate and propagates.
  output sum;
  output g; // Generate
  output p; // Propagate

  /// Generate
  //
  // If a and b are 1 a carry will be generated here.
  //
  assign g = a & b;

  /// Propagate
  //
  // If a or b are 1 a carry in to this digit position will
  // "propagate through" to a carry out. (There is no actual
  // carry out signal.)
  //
  assign p = a | b;

  /// Sum
  //
  // This is the usual formula for the sum.
  //
  assign sum =
    ~a & ~b & cin |
    ~a & b & ~cin |
    a & ~b & ~cin |
    a & b & cin;

endmodule

// :Example:
//
// A 5-bit CIA using five cla slices. The generate and propagate
// signals are used to produce the carry in signals.

module cla_5(sum,a,b);
  input [4:0] a, b;
  output [5:0] sum;

  wire [4:0] g, p, carry;

  /// Logic for Carry In Signals
  //
  // General idea: for there to be a carry at bit x either:
  // either the carry is generated at bit x-1
  // or the carry is generated at bit x-2 and prop. through x-1
  // or the carry is generated at bit x-3 and prop. through x-1 and x-1
  // ...
  // or the carry is generated at bit 0 and prop. through 1 and ... and x-1

  assign carry[0] = 1'b0;

  assign carry[1] = g[0];

  assign carry[2] = g[0] & p[1]
    | g[1];

  assign carry[3] = g[0] & p[1] & p[2]
    | g[1] & p[2]
    | g[2];

```

```

assign    carry[4] = g[0] & p[1] & p[2] & p[3]
           | g[1] & p[2] & p[3]
           | g[2] & p[3]
           | g[3];

assign sum[5] = g[0] & p[1] & p[2] & p[3] & p[4]
           | g[1] & p[2] & p[3] & p[4]
           | g[2] & p[3] & p[4]
           | g[3] & p[4]
           | g[4];

cla_slice s0(sum[0],g[0],p[0],a[0],b[0],carry[0]);
cla_slice s1(sum[1],g[1],p[1],a[1],b[1],carry[1]);
cla_slice s2(sum[2],g[2],p[2],a[2],b[2],carry[2]);
cla_slice s3(sum[3],g[3],p[3],a[3],b[3],carry[3]);
cla_slice s4(sum[4],g[4],p[4],a[4],b[4],carry[4]);

endmodule

// :Example:
//
// Testbench for CLA. The testbench includes material not covered
// in the course.

module testcla();

    wire [5:0] sum;
    reg [5:0] shadow_sum;
    reg [4:0] a, b;
    integer i;

    cla_5 c(sum, a, b);

    initial begin

        for(i=0; i<1024; i=i+1) begin

            a = i[4:0];
            b = i[9:5];
            shadow_sum = a + b;
            #1;
            if( sum != shadow_sum ) begin
                $display("Wrong sum: %h + %h = %h != %h\n",
                    a, b, shadow_sum, sum);
                $stop;
            end
        end

        $display("Tests completed.");

    end

endmodule

////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
// Two-Level Carry Look-Ahead Adder

// :PH: 4.5 (In middle of section 4.5.) Also see Figure 4.24

// Goal: Avoid large fan-ins of flat CLA.
//
// Idea:
//   Divide adder into multiple adder blocks.
//   Each adder block is itself a CLA.
//   Adder block produces "super" generate and propagate signals.
//   Use these to generate cin for adder blocks.

```

```

// Below a 12-bit two-level CLA is constructed using three 4-bit adder
// blocks.
//
// For comparison, these are followed by a flat 12-bit CLA, a 12-bit
// ripple adder, and a testbench.

```

```

// :Example:

```

```

//
// A four-bit adder block. This uses the same cla_slice as the
// earlier CLA.

```

```

module cla_4_block(sum,gout,pout,a,b,cin);
  input [3:0] a, b;
  input      cin;
  output [3:0] sum;
  output      gout, pout;

  wire [3:0] carry, p, g;

  assign carry[0] = cin;

  assign carry[1] = cin & p[0]
    | g[0];

  assign carry[2] = cin & p[0] & p[1]
    | g[0] & p[1]
    | g[1];

  assign carry[3] = cin & p[0] & p[1] & p[2]
    | g[0] & p[1] & p[2]
    | g[1] & p[2]
    | g[2];

  assign gout = g[0] & p[1] & p[2] & p[3]
    | g[1] & p[2] & p[3]
    | g[2] & p[3]
    | g[3];

  assign pout = p[0] & p[1] & p[2] & p[3];

  cla_slice s0(sum[0],g[0],p[0],a[0],b[0],carry[0]);
  cla_slice s1(sum[1],g[1],p[1],a[1],b[1],carry[1]);
  cla_slice s2(sum[2],g[2],p[2],a[2],b[2],carry[2]);
  cla_slice s3(sum[3],g[3],p[3],a[3],b[3],carry[3]);

```

```

endmodule

```

```

// :Example:

```

```

//
// The 12-bit two-level CLA.

```

```

module cla_12_two_level(sum,a,b);
  input [11:0] a, b;
  output [12:0] sum;

  wire [2:0] P, G, carry;

  assign      carry[0] = 1'b0;

  assign      carry[1] = G[0];

  assign      carry[2] = G[0] & P[1]
    | G[1];

  assign      sum[12] = G[0] & P[1] & P[2]

```

```

        | G[1] & P[2]
        | G[2];

    cla_4_block ad0(sum[3:0], G[0], P[0], a[3:0], b[3:0], carry[0]);
    cla_4_block ad1(sum[7:4], G[1], P[1], a[7:4], b[7:4], carry[1]);
    cla_4_block ad2(sum[11:8], G[2], P[2], a[11:8], b[11:8], carry[2]);

endmodule

// :Example:
//
// A 12-bit flat CLA. For comparison with the two-level adder.

module cla_12_flat(sum,a,b);
    input [11:0] a, b;
    output [12:0] sum;

    wire [11:0] g, p, carry;

    assign carry[0] = 1'b0;

    assign carry[1] = 1'b0;

    assign carry[2] = g[0] & p[1]
        | g[1];

    assign carry[3] = g[0] & p[1] & p[2]
        | g[1] & p[2]
        | g[2];

    assign carry[4] = g[0] & p[1] & p[2] & p[3]
        | g[1] & p[2] & p[3]
        | g[2] & p[3]
        | g[3];

    assign carry[5] = g[0] & p[1] & p[2] & p[3] & p[4]
        | g[1] & p[2] & p[3] & p[4]
        | g[2] & p[3] & p[4]
        | g[3] & p[4]
        | g[4];

    assign carry[6] = g[0] & p[1] & p[2] & p[3] & p[4] & p[5]
        | g[1] & p[2] & p[3] & p[4] & p[5]
        | g[2] & p[3] & p[4] & p[5]
        | g[3] & p[4] & p[5]
        | g[4] & p[5]
        | g[5];

    assign carry[7] = g[0] & p[1] & p[2] & p[3] & p[4] & p[5] & p[6]
        | g[1] & p[2] & p[3] & p[4] & p[5] & p[6]
        | g[2] & p[3] & p[4] & p[5] & p[6]
        | g[3] & p[4] & p[5] & p[6]
        | g[4] & p[5] & p[6]
        | g[5] & p[6]
        | g[6];

    assign carry[8] = g[0] & p[1] & p[2] & p[3] & p[4] & p[5] & p[6] & p[7]
        | g[1] & p[2] & p[3] & p[4] & p[5] & p[6] & p[7]
        | g[2] & p[3] & p[4] & p[5] & p[6] & p[7]
        | g[3] & p[4] & p[5] & p[6] & p[7]
        | g[4] & p[5] & p[6] & p[7]
        | g[5] & p[6] & p[7]
        | g[6] & p[7]
        | g[7];

    assign carry[9] = g[0] & p[1] & p[2] & p[3] & p[4] & p[5] & p[6] & p[7] & p[8]
        | g[1] & p[2] & p[3] & p[4] & p[5] & p[6] & p[7] & p[8]

```

```

| g[2] & p[3] & p[4] & p[5] & p[6] & p[7] & p[8]
| g[3] & p[4] & p[5] & p[6] & p[7] & p[8]
| g[4] & p[5] & p[6] & p[7] & p[8]
| g[5] & p[6] & p[7] & p[8]
| g[6] & p[7] & p[8]
| g[7] & p[8]
| g[8];

assign carry[10] = g[0] & p[1] & p[2] & p[3] & p[4] & p[5] & p[6] & p[7] & p[8] &
| g[1] & p[2] & p[3] & p[4] & p[5] & p[6] & p[7] & p[8] & p[9]
| g[2] & p[3] & p[4] & p[5] & p[6] & p[7] & p[8] & p[9]
| g[3] & p[4] & p[5] & p[6] & p[7] & p[8] & p[9]
| g[4] & p[5] & p[6] & p[7] & p[8] & p[9]
| g[5] & p[6] & p[7] & p[8] & p[9]
| g[6] & p[7] & p[8] & p[9]
| g[7] & p[8] & p[9]
| g[8] & p[9]
| g[9];

assign carry[11] = g[0] & p[1] & p[2] & p[3] & p[4] & p[5] & p[6] & p[7] & p[8] &
| g[1] & p[2] & p[3] & p[4] & p[5] & p[6] & p[7] & p[8] & p[9] & p[10]
| g[2] & p[3] & p[4] & p[5] & p[6] & p[7] & p[8] & p[9] & p[10]
| g[3] & p[4] & p[5] & p[6] & p[7] & p[8] & p[9] & p[10]
| g[4] & p[5] & p[6] & p[7] & p[8] & p[9] & p[10]
| g[5] & p[6] & p[7] & p[8] & p[9] & p[10]
| g[6] & p[7] & p[8] & p[9] & p[10]
| g[7] & p[8] & p[9] & p[10]
| g[8] & p[9] & p[10]
| g[9] & p[10]
| g[10];

assign sum[12] = g[0] & p[1] & p[2] & p[3] & p[4] & p[5] & p[6] & p[7] & p[8] & p
| g[1] & p[2] & p[3] & p[4] & p[5] & p[6] & p[7] & p[8] & p[9] & p[10] & p
| g[2] & p[3] & p[4] & p[5] & p[6] & p[7] & p[8] & p[9] & p[10] & p[11]
| g[3] & p[4] & p[5] & p[6] & p[7] & p[8] & p[9] & p[10] & p[11]
| g[4] & p[5] & p[6] & p[7] & p[8] & p[9] & p[10] & p[11]
| g[5] & p[6] & p[7] & p[8] & p[9] & p[10] & p[11]
| g[6] & p[7] & p[8] & p[9] & p[10] & p[11]
| g[7] & p[8] & p[9] & p[10] & p[11]
| g[8] & p[9] & p[10] & p[11]
| g[9] & p[10] & p[11]
| g[10] & p[11]
| g[11];

cla_slice s0(sum[0],g[0],p[0],a[0],b[0],carry[0]);
cla_slice s1(sum[1],g[1],p[1],a[1],b[1],carry[1]);
cla_slice s2(sum[2],g[2],p[2],a[2],b[2],carry[2]);
cla_slice s3(sum[3],g[3],p[3],a[3],b[3],carry[3]);
cla_slice s4(sum[4],g[4],p[4],a[4],b[4],carry[4]);
cla_slice s5(sum[5],g[5],p[5],a[5],b[5],carry[5]);
cla_slice s6(sum[6],g[6],p[6],a[6],b[6],carry[6]);
cla_slice s7(sum[7],g[7],p[7],a[7],b[7],carry[7]);
cla_slice s8(sum[8],g[8],p[8],a[8],b[8],carry[8]);
cla_slice s9(sum[9],g[9],p[9],a[9],b[9],carry[9]);
cla_slice s10(sum[10],g[10],p[10],a[10],b[10],carry[10]);
cla_slice s11(sum[11],g[11],p[11],a[11],b[11],carry[11]);

endmodule

// :Example:
//
// A BFA, for use in 12-bit ripple adder.

module bfa_implicit(sum,cout,a,b,cin);
input a,b,cin;
output sum,cout;

```

```

assign sum =
    ~a & ~b & cin |
    ~a & b & ~cin |
    a & ~b & ~cin |
    a & b & cin;

assign cout = a & b | b & cin | a & cin;

endmodule

// :Example:
//
// Twelve-bit ripple adder, for comparison.

module ripple_12(sum,a,b);
    input [11:0] a, b;
    output [12:0] sum;

    wire [11:0] carry;

    bfa_implicit bfa0(sum[0],carry[0],a[0],b[0],1'b0);
    bfa_implicit bfa1(sum[1],carry[1],a[1],b[1],carry[0]);
    bfa_implicit bfa2(sum[2],carry[2],a[2],b[2],carry[1]);
    bfa_implicit bfa3(sum[3],carry[3],a[3],b[3],carry[2]);
    bfa_implicit bfa4(sum[4],carry[4],a[4],b[4],carry[3]);
    bfa_implicit bfa5(sum[5],carry[5],a[5],b[5],carry[4]);
    bfa_implicit bfa6(sum[6],carry[6],a[6],b[6],carry[5]);
    bfa_implicit bfa7(sum[7],carry[7],a[7],b[7],carry[6]);
    bfa_implicit bfa8(sum[8],carry[8],a[8],b[8],carry[7]);
    bfa_implicit bfa9(sum[9],carry[9],a[9],b[9],carry[8]);
    bfa_implicit bfa10(sum[10],carry[10],a[10],b[10],carry[9]);
    bfa_implicit bfa11(sum[11],sum[12],a[11],b[11],carry[10]);

endmodule

// :Example:
//
// Testbench. Runs all three adders. Material for testbench not covered.

module testcla2();
    wire [12:0] sum_r, sum_2, sum_f;
    reg [12:0] shadow_sum;
    reg [11:0] a, b;
    integer i;

    cla_12_flat c1(sum_f,a,b);
    cla_12_two_level c2(sum_2,a,b);
    ripple_12 c3(sum_r,a,b);

    initial begin

        for(i=0; i<4194304; i=i+1) begin

            a = i[11:0];
            b = i[21:12];
            shadow_sum = a + b;
            #1;
            if( sum_2 != shadow_sum || sum_2 != sum_r || sum_2 != sum_f ) begin
                $display("Wrong sum: %h + %h = %h != %h or %h or %h\n",
                    a, b, shadow_sum, sum_2, sum_r);
                $stop;
            end
        end

        $display("Tests completed.");
    end
end

```

end

endmodule

////////////////////////////////////
/// Real-World Integer Adders

// Under construction.