

EE 3755

Spring 2003

Homework #4

Not to be returned; (it will  
not be graded).

①

HW#4


① Consider the "first example computer" presented in class; (see appropriate handouts). Suppose that the controller operates using a clock with period 10 nanoseconds.

- (a) How much time is required for fetching, decoding and executing one 32-bit arithmetic instruction with indirect addressing mode?
- (b) How much time is required for fetching, decoding and executing a couple of two-address 16-bit instructions located next to each other in the same memory word?

Note: Ignore step 0. Start from step 1.

- ② Show in block diagram form the design of a combinational right-shifter that can shift to the right a 64-bit input word  $A$  by any shift amount varying between 0 and 63 bits. Inputs to your combinational shifter are the 64-bit word  $A$  and a 6-bit word  $D$  indicating the shift amount.

②

③ . Design a circuit that will accept as input the signal coming from an asynchronous push button having a long duration (40 clock periods for example) and will create as an output a synchronous signal of duration 5 clock periods.

④ Consider the following two binary unsigned numbers:  $A = a_5 a_4 a_3 a_2 a_1 a_0$  and  $B = b_3 b_2 b_1 b_0$  where  $a_5$  and  $b_3$  are the most significant bits of  $A$  and  $B$  while  $a_0$  and  $b_0$  their least significant bits. Consider the multiplication  $P = A \times B$ .

① Show the matrix of summands

② Draw the diagram of a 6-by-4 unsigned array multiplier.

③ If the propagation delay through a 2-input AND gate is  $D_{AND}$  and the propagation delay through a full adder is  $D_{FA}$ , compute the propagation delay through the 6-by-4 unsigned array multiplier.