

Class Notes

for EE 3755

Part I I

Prepared by: Alexander Skavrentzos

- The number of elements in a vector is called dimension of the vector

For example, a 32-bit register A has dimension 32.

- Naming the elements of a vector

Let A be a 32-bit vector

Then $A = A[0], A[1], A[2], \dots, A[31]$

The above naming scheme is called

0-origin indexing

or

0-origin counting ~~etc~~ scheme.

- $A[5:10] = A[5], A[6], A[7], A[8], A[9], A[10]$

② a

- Matrices (2-dimensional arrays of operands)

Below you see the components of a k -row by n -column matrix (or a matrix of dimension k -by- n)

$$M\langle 0 \rangle[0] \quad M\langle 0 \rangle[1] \quad M\langle 0 \rangle[2] \quad \dots \quad M\langle 0 \rangle[n-1]$$

$$M\langle 1 \rangle[0] \quad M\langle 1 \rangle[1] \quad M\langle 1 \rangle[2] \quad \dots \quad M\langle 1 \rangle[n-1]$$

$$M\langle 2 \rangle[0] \quad M\langle 2 \rangle[1] \quad M\langle 2 \rangle[2] \quad \dots \quad M\langle 2 \rangle[n-1]$$

⋮

⋮

$$M\langle k-1 \rangle[0] \quad M\langle k-1 \rangle[1] \quad M\langle k-1 \rangle[2] \quad \dots \quad M\langle k-1 \rangle[n-1]$$

-
- $M\langle i \rangle[j]$ = component of row i and column j of matrix M

- $M\langle i:j \rangle$ = matrix consisting of rows i through j (included) of matrix M .

- $M[m:q]$ = matrix consisting of columns m through q (included) of matrix M .

Boolean Operators

③a

NOT denoted by $\bar{\quad}$; AND denoted by \wedge ;
OR denoted by \vee ; ~~Ex-OR~~ Exclusive OR (EX-OR)
denoted by \oplus


- The operators \wedge \vee \oplus apply between vectors or matrices of the same dimension except in case of vectors (matrices) and a scalar.
- The operator NOT applies componentwise on the elements of a vector or a matrix

Example: Consider two n -bit vectors

$$A = A[0], A[1], A[2], \dots, A[n-1]$$



$$B = B[0], B[1], B[2], \dots, B[n-1]$$

 Then $\bar{A} = \bar{A}[0], \bar{A}[1], \dots, \bar{A}[n-1]$




 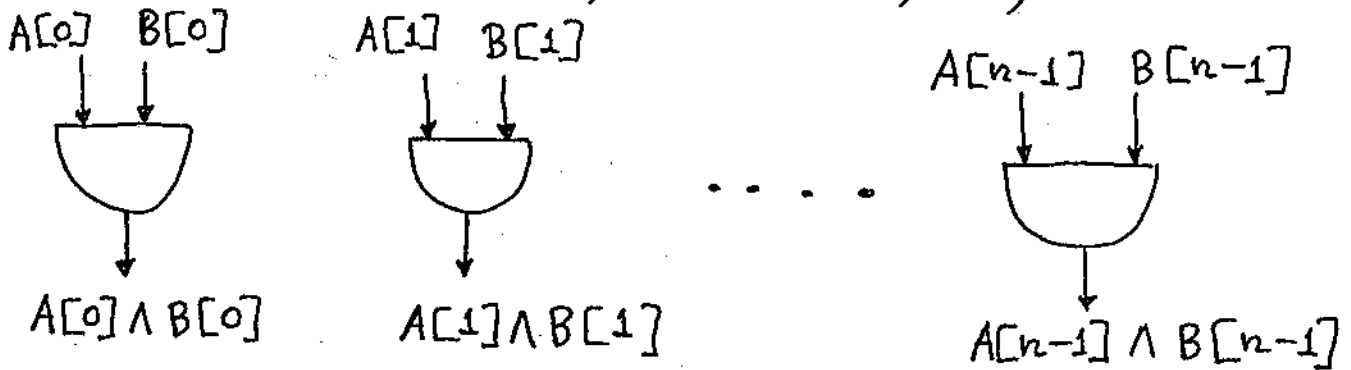(4) a

$$A \wedge B = (A[0] \wedge B[0], A[1] \wedge B[1], \dots, A[n-1] \wedge B[n-1])$$


 
$$A \vee B = (A[0] \vee B[0], A[1] \vee B[1], \dots, A[n-1] \vee B[n-1])$$






• The situation is similar with the EX-OR

Let b be a scalar and A be a vector of dimension n or $A = A[0], A[1], \dots, A[n-1]$. ⑤a

Then
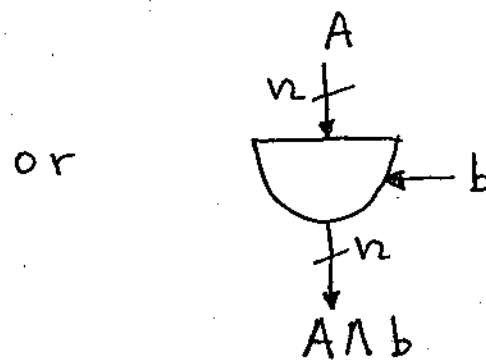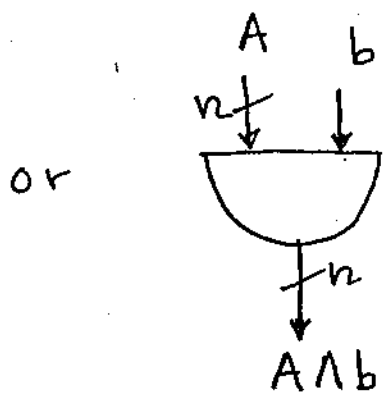 
$$A \wedge b = (A[0] \wedge b, A[1] \wedge b, A[2] \wedge b, \dots, A[n-1] \wedge b)$$



The situation is similar with $A \vee b$ and $A \oplus b$.

$$A[10:12] \wedge B[12:14] =$$

$$= A[10] \wedge B[12], A[11] \wedge B[13], A[12] \wedge B[14].$$

⑥a

• Catenate operation

The catenate operation is denoted by $,$ (comma). Let X and Y be the vectors

$$X = X[0], X[1], \dots, X[n_1 - 1]$$

$$Y = Y[0], Y[1], \dots, Y[n_2 - 1].$$

Then

$$X, Y = X[0], X[1], \dots, X[n_1 - 1], Y[0], Y[1], \dots, Y[n_2 - 1].$$

Example: Consider a 4-bit vector A and an 8-bit vector B . Then

$$A[2:3], B[2:4], B[6:7] =$$

$$= A[2], A[3], B[2], B[3], B[4], B[6], B[7].$$

• Row catenate (it applies on matrices)

The notation for row catenation is $!$

Let M and N be matrices. Then

$M!N$ = a new matrix with the rows of M above the rows of N .

Example: $M = \begin{bmatrix} 0 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix}$; $N = \begin{bmatrix} 1 & 1 & 1 \\ 1 & 0 & 1 \end{bmatrix}$. ⑦a

Then

$$M \wedge N = \begin{bmatrix} 0 & 0 & 1 \\ 1 & 1 & 0 \\ 1 & 1 & 1 \\ 1 & 0 & 1 \end{bmatrix}$$

• Reduction for vectors

Let X be a vector of dimension n
 $X = X[0], X[1], X[2], \dots, X[n-1]$.

Reduction by means of operation \odot
 applied on vector $X =$

$$= \odot / X = X[0] \odot X[1] \odot X[2] \odot \dots \odot X[n-1]$$

where \odot is $\vee \wedge \oplus$

Example: $X = X[0], X[1], X[2], X[3]$.

Then

$$\wedge / X = X[0] \wedge X[1] \wedge X[2] \wedge X[3]$$

The situation is similar with the operators $\vee \oplus$.

⑧a

Reduction applied on matrices

Let M be a matrix

- Row reduction by means of \odot applied on M
 $= \odot/M =$ horizontal vector where each component of the vector is the result of reducing a row by means of operation \odot
- Column reduction by means of \odot applied on M
 $= \odot//M =$ horizontal vector where each component is the result of reducing a column by means of the operation \odot

Again \odot can be $\vee \wedge \oplus$

Example: Let N be $N = \begin{bmatrix} 1 & 0 & 1 \\ 1 & 1 & 1 \\ 0 & 1 & 1 \\ 1 & 1 & 1 \end{bmatrix}$

Then $\wedge/N = (0, 1, 0, 1)$

$\oplus//N = (1, 1, 0)$

$\vee/(\oplus//N) = \vee/(1, 1, 0) = 1 \vee 1 \vee 0 = 1$

9a

• Binary encode

The notation for binary encoding is T

$nT_p = n$ -bit vector representation of value p .

For example


$$3T_0 = 0, 0, 0$$

$$4T_{10} = 1, 0, 1, 0$$

$$5T_{15} = 0, 1, 1, 1, 1$$

$$7T_{32} = 0, 1, 0, 0, 0, 0, 0$$

 
$$\overline{4T_0} = \overline{0, 0, 0, 0} = 1, 1, 1, 1$$




D Flip Flop (FF)

Register transfers are clocked which means that they are synchronized by a system master clock.

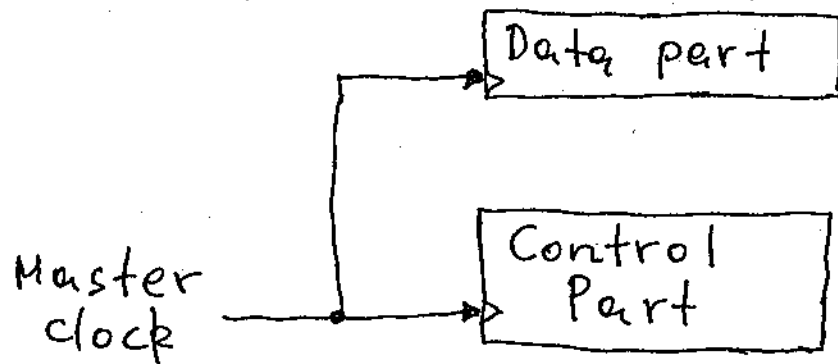We assume that the control section as well as the data section of a digital system are synchronized by the system master clock




(2) b

 


Changes of states of flip flops (FFs) can happen at the leading edge of a clock pulse



or at the trailing edge of a clock pulse

 

 We will assume trailing-edge-triggered systems; (this means trailing-edge triggered flip-flops will be assumed).





Whatever is the D input it will be stored in Q right after




trailing edge of the clock.



③b

 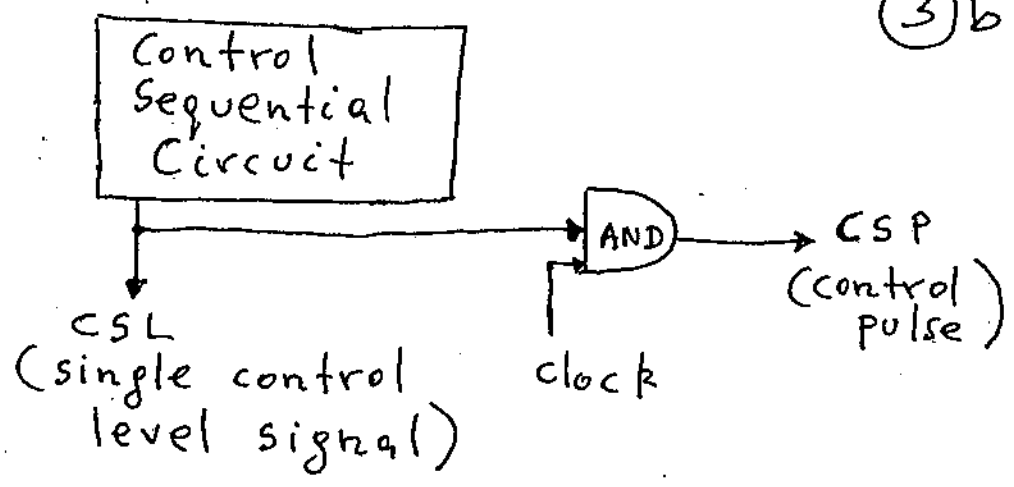

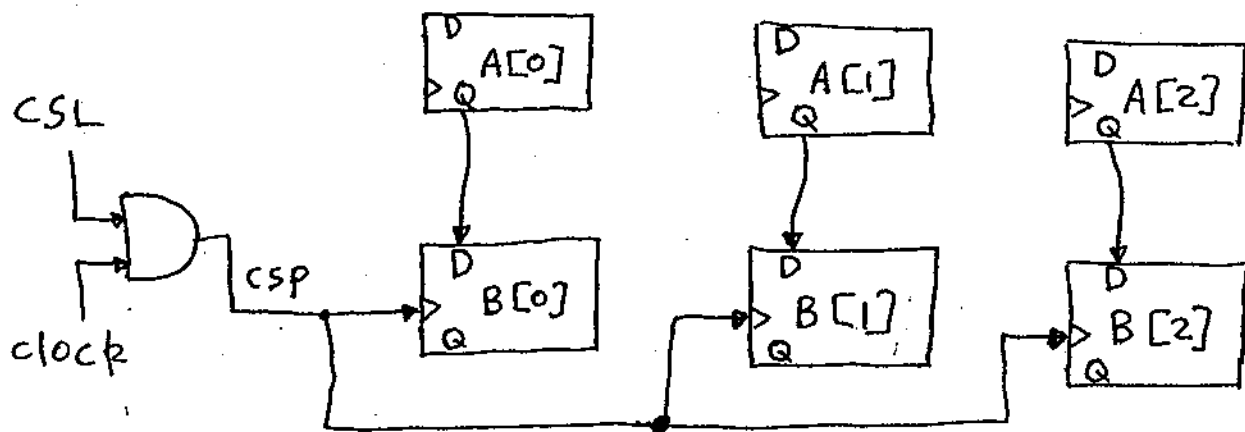- A and B are 3-bit registers. (4) b
 Do $B \leftarrow A$ if $CSL = 1$. Show in logic block diagram form the above transaction.



or

  

old data in B new data in B

(5) b

- A B C D are 3-bit registers:

Do

$D \leftarrow A$ if $CSL1 = 1$

$D \leftarrow B$ if $CSL2 = 1$

$D \leftarrow C$ if $CSL3 = 1$.


Question: Is there any restriction regarding the control signals $CSL1$, $CSL2$, $CSL3$?

Answer: At most one of $CSL1$, $CSL2$, $CSL3$ can be 1.

- Show in block diagram form the above transactions.

⑦ b

 
The bit level diagram of the previous page is now shown in a more compact way



(8) b


- The general problem:
- Connect n sources (origin vectors) to m destinations.
- Two approaches can be followed:

(a) Using dedicated data paths

 

$n \times m$
dedicated
data paths

(b) Using a single BUS

 

Only one
source
 S_i can
be connec-
ted to the
BUS at any
time

** We will compare the cost/speed of the two above approaches.

(9) b

Example of approach (a); (dedicated data paths).

A; B; C are b -bit source (origin) registers.
D; E are b -bit destination registers.

Do

$D \leftarrow A$ if $CSL1 = 1$

$D \leftarrow B$ if $CSL2 = 1$

$D \leftarrow C$ if $CSL3 = 1$

$E \leftarrow A$ if $CSL4 = 1$


$E \leftarrow B$ if $CSL5 = 1$

$E \leftarrow C$ if $CSL6 = 1$.

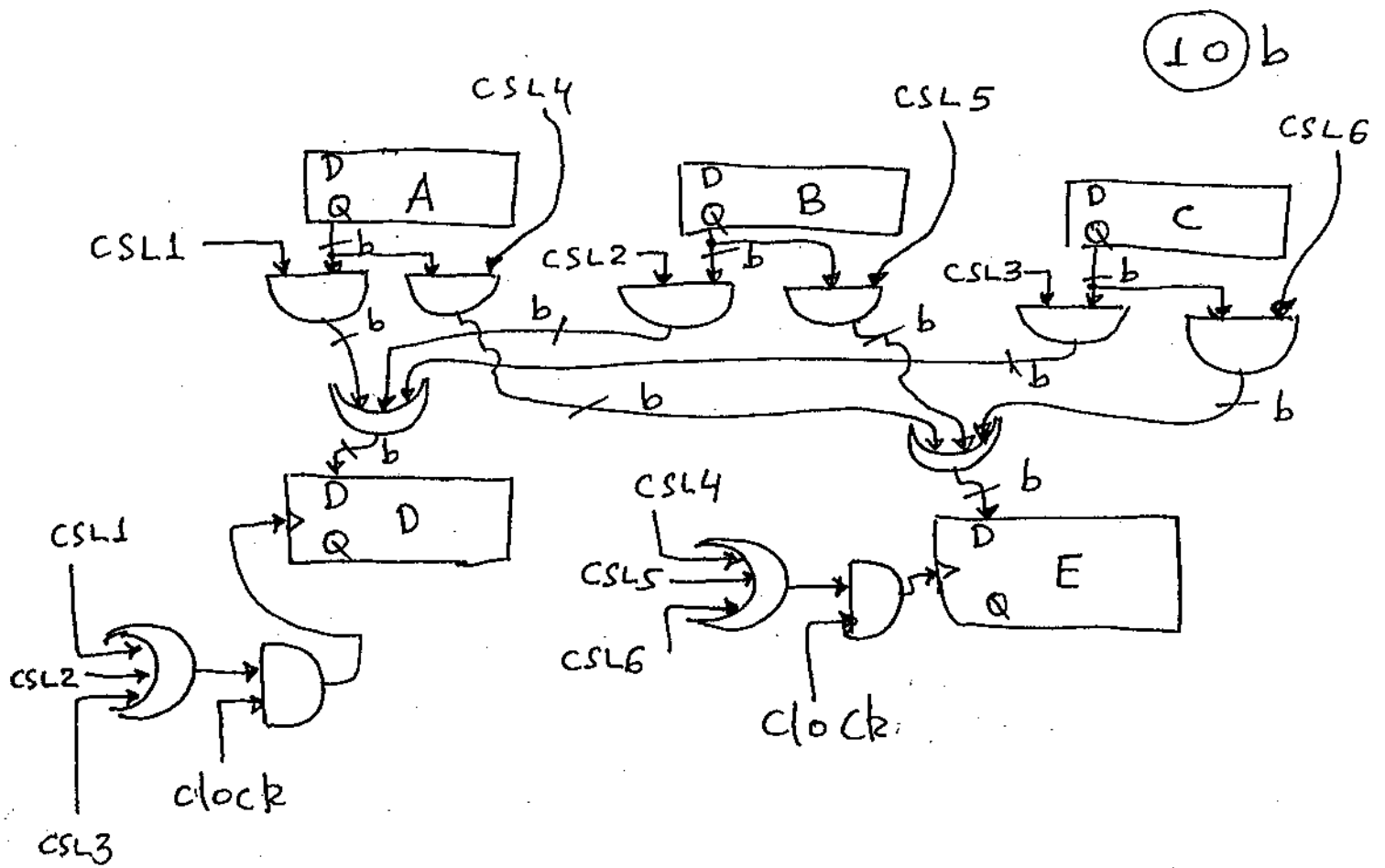Question: Is there any restriction regarding the control signals $CSL1$, $CSL2$, ..., $CSL6$?

Answer: At most one of $CSL1$, $CSL2$, $CSL3$ can be 1. Also, at most one of $CSL4$, $CSL5$, $CSL6$ can be 1.

- Show in logic block diagram form the above transactions.



Here the cost for connecting A; B;

C to D; E is

6 groups (or banks) of AND gates
 +) 2 groups (or banks) of OR gates

8 groups of AND/OR gates
 or 8x6 bit-level AND/OR gates.

(11)b

In general: If we have n sources (origin vectors) and m destinations, the cost of connecting any source to any destination using the dedicated data path approach is

+). $\left. \begin{array}{l} n \times m \text{ groups (banks) of AND gates} \\ m \text{ groups (banks) of OR gates} \end{array} \right\}$

$n \times m + m = m(n+1)$ groups of AND/OR gates
or


Cost dedicated = $m(n+1) \cdot b$ bct level AND/OR gates (1)

where b = number of bcts per source or destination.

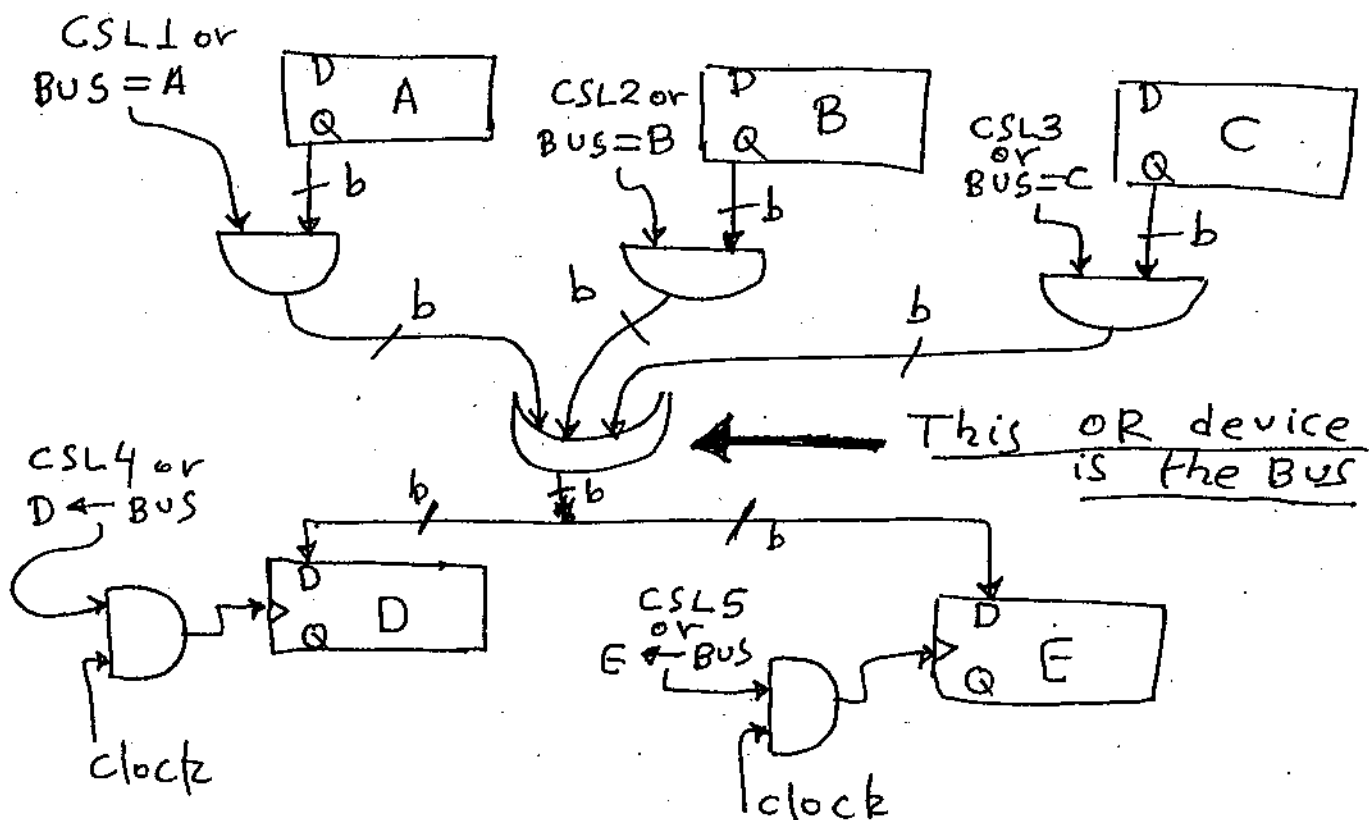Example of approach (b) (single $12b$ BUS).

A; B; C are b -bit source (origin) registers. D; E are b -bit destination registers.

- Show in logic block diagram form how any transfer from any source to any destination can be mechanized using a single BUS.




**** Note :** Only one of CSL1, CSL2, CSL3 can be true at any time.

 
(13) b

Timing diagram:

Suppose $D \leftarrow A$ needs to be accomplished.



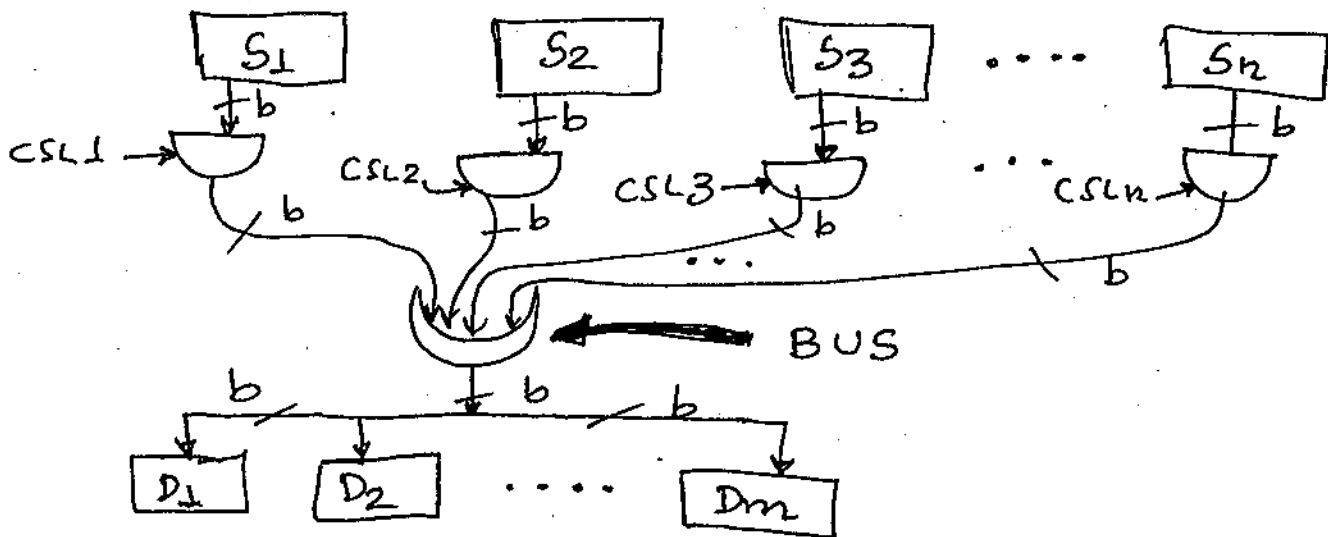In general: n sources (origin vectors);
 m destinations;
 b bits per source/destination



(14).b

The cost of connecting any source to any destination using the BUS approach is

f) n groups of AND gates
1 group of OR gates; (the BUS)

$n+1$ groups of AND/OR gates


or

$$\text{Cost}_{\text{BUS-connct.}} = (n+1) \cdot b \text{ bit level AND/OR gates} \quad (2)$$


* Compare costs of (1), (2).

Tradeoff: cost vs. speed.

Notations for BUS connections

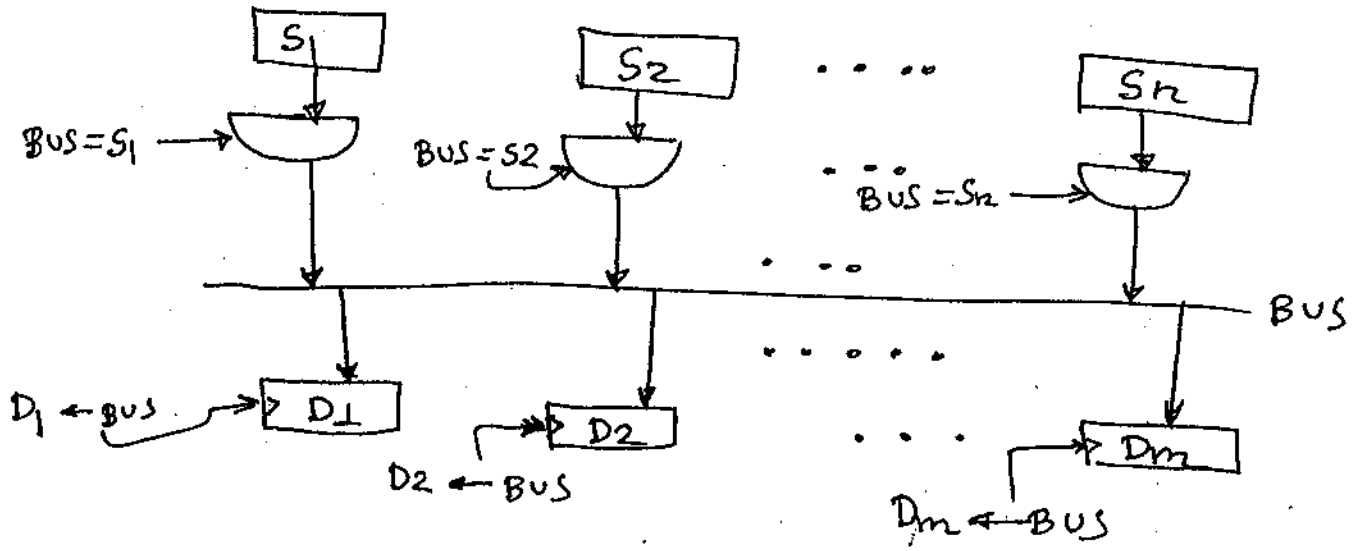


OR

 

(16) b


• Another approach for constructing long BUSES (buses used to connect digital systems being far away from each other) is by using tristate elements.

• Tristate element

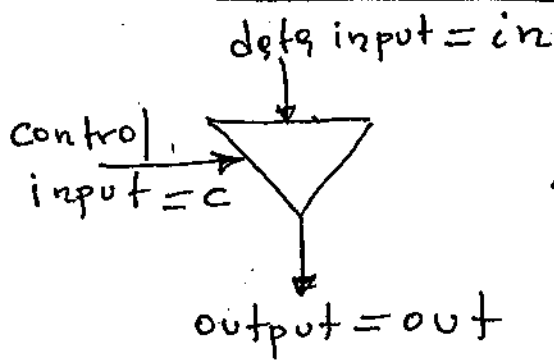


if $c=0 \Rightarrow$ out/ i_n isolated; (open switch).
if $c=1 \Rightarrow$ out = i_n ; (closed switch).

OR

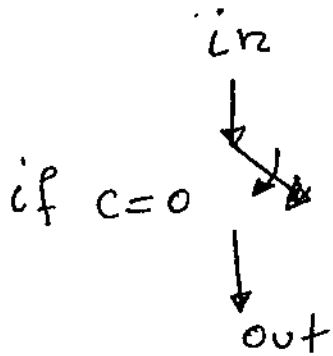


(high impedance).

 

(17).b

• Tristate BUSES

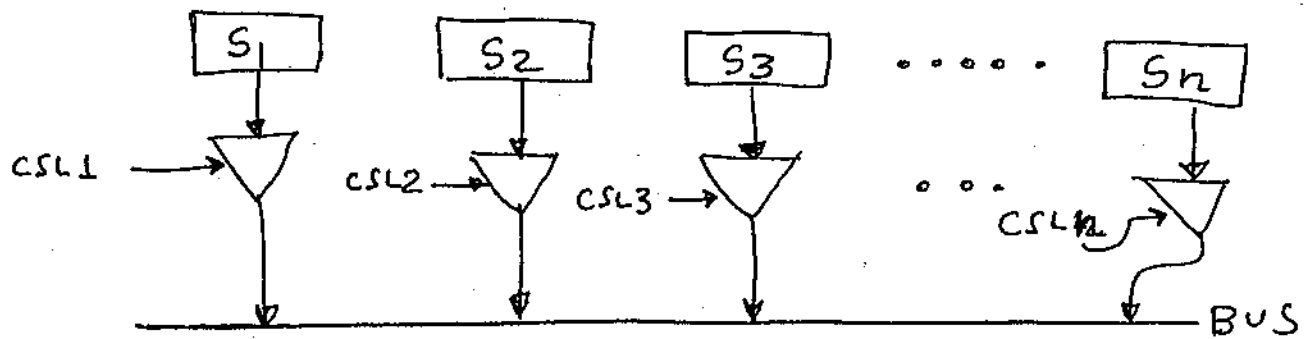

*: At most one of $CSL_1, CSL_2, \dots, CSL_n$ can be 1.

** : Tristate elements can get in four different states; high impedance; zero; one; unknown.

