
 



CH 5

 

Multiplexor




ALU

 


D-FF
(Register)




Program Counter
(Register)

 

Memory

 


Register file

 

Incrementor


#Program Counter

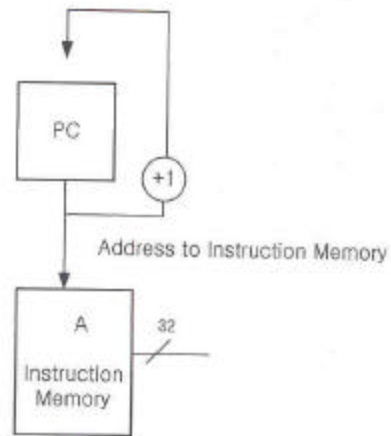


Why just increment 1?

“Because of Alignment”

“Every instruction is 4 bytes long”.

 


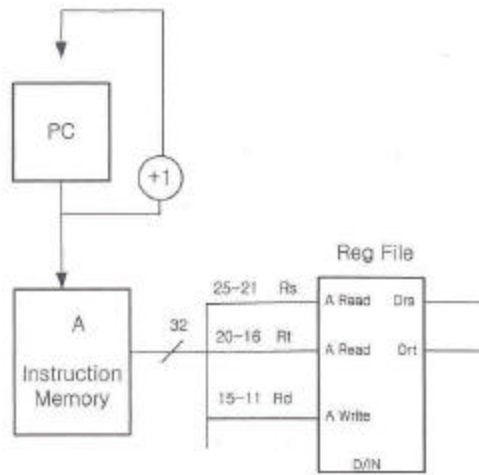


Instruction

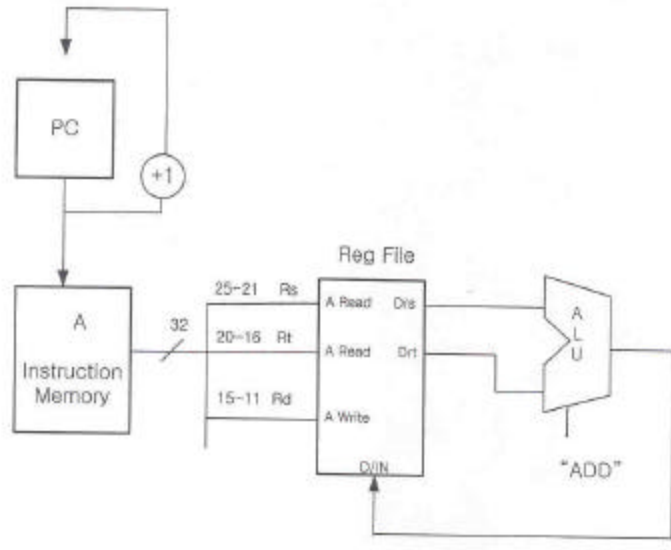How to Implement ADD Instruction to work?






ADD R1, R2, R3

 


ADD Rd, Rs Rt

 Where the "ADD" control signal for ALU comes?
 "From the instruction field "5-0" [function field]
 and OPCode(31-26)"



OP FUN ALUOP

0	20	ADD
---	----	-----

 


SUB R4, R5, R6

OP	RS	RT	RD	SA	FUN
0	5	6	4	0	22
31	26 25	21 20	16 15	11 10	6 5
					0


	OP	FUN	ALUOP
ADD R1, R2, Rs	0	20	ADD
SUB R4, R5, R6	0	22	SUB

Can the above H/W perform ADDi Instructions?"

What do we need?

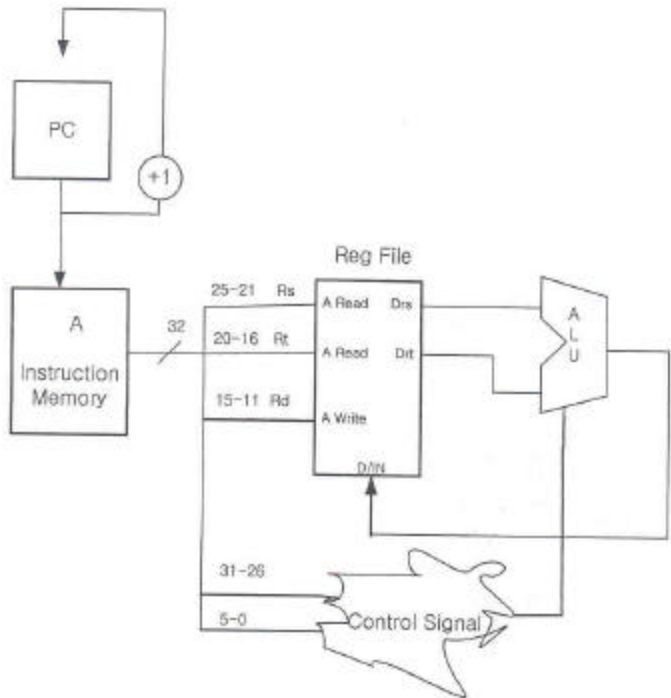


ADDi R7, R8, 5

 

I format

ADDi rt,rs, imm

 
We need to get the immediate data, and "RT" field becomes acting like destination field at "R" format.



Where the "CNT" signal come?
 "From the OPCode field (31-26)


	OP	FUN	ALUOP
ADD R1, R2, Rs	0	20	ADD
SUB R4, R5, R6	0	22	SUB
ADDi R7, R8, 5	8	X	ADD

25-21 Rs 20-16 Rt

 

(Probably not work due to fan-out)




 


“Can the above H/W perform OR Instruction?”

“Do we need more H/W?”

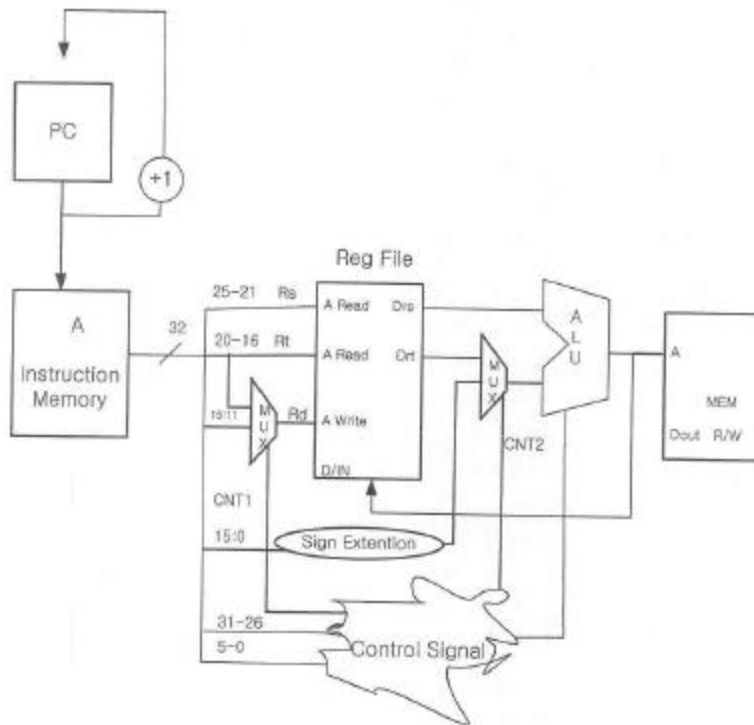So far we don't have any instructions to access memory and we don't have data memory unit yet.




LW R7, 8(R9) ; LW rt, address

 

How to implement this? And what will be ALU operation?

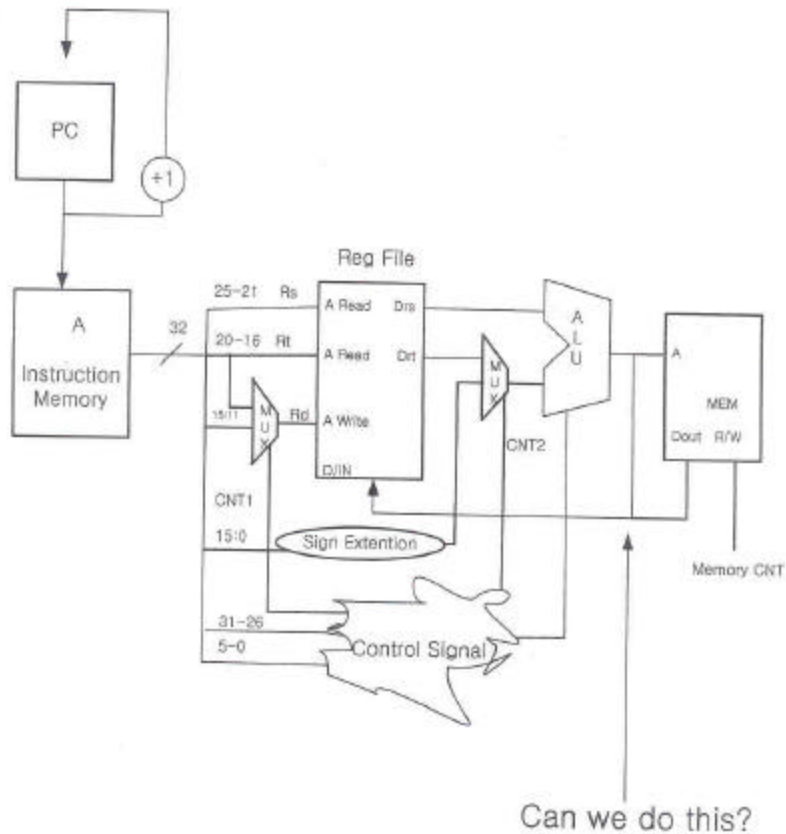
One way to do this is using the ALU to compute memory address and put the output of ALU (computed memory address; $(R9+8)$) to the address of memory and put the data from the memory register file (R7).



Memory output should go back to register file and ALU output should go back to register file.

But this time ALU output is memory address and
Dout is data. This is a collision.

How can we solve this? => Multiplexor

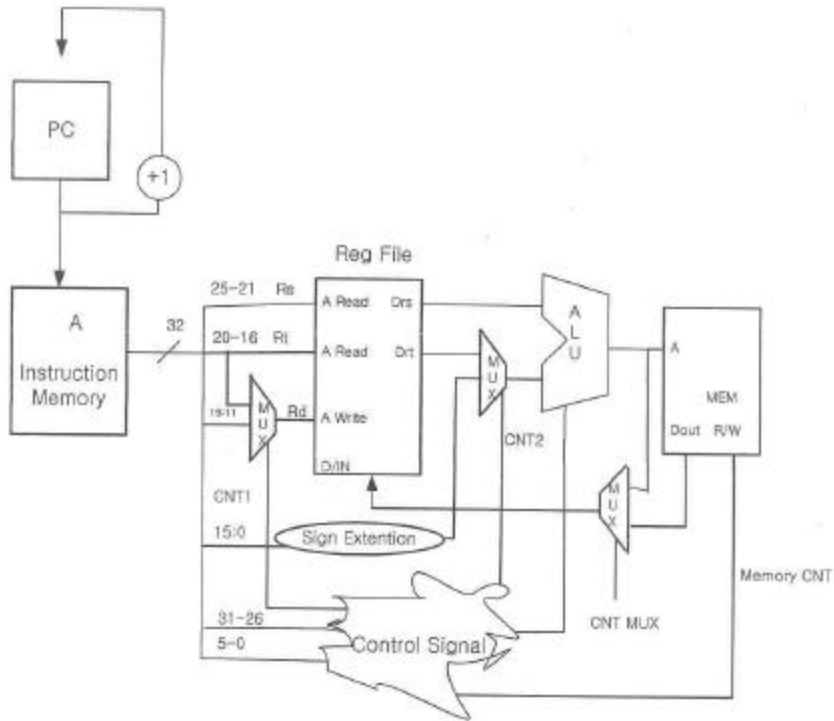

Where the CNTMUX come?

=> If "LW" instruction, then the mux should select
input from memory.


=> So, from Control Signal.

LB is loading only one byte and LW is loading 4 bytes. So we have to think about either modifying memory unit (Memory Module) to get one byte data at a time (LW, we assume the memory unit giving us 4 bytes data).


So Let's assume the memory unit giving us 4 bytes data, then we have to truncate extra 3 bytes data, and we have to think about memory address.

If we assume we could access arbitrary memory address, then we need logic to do that.

LB R1 2(R3) LB rt, address

 


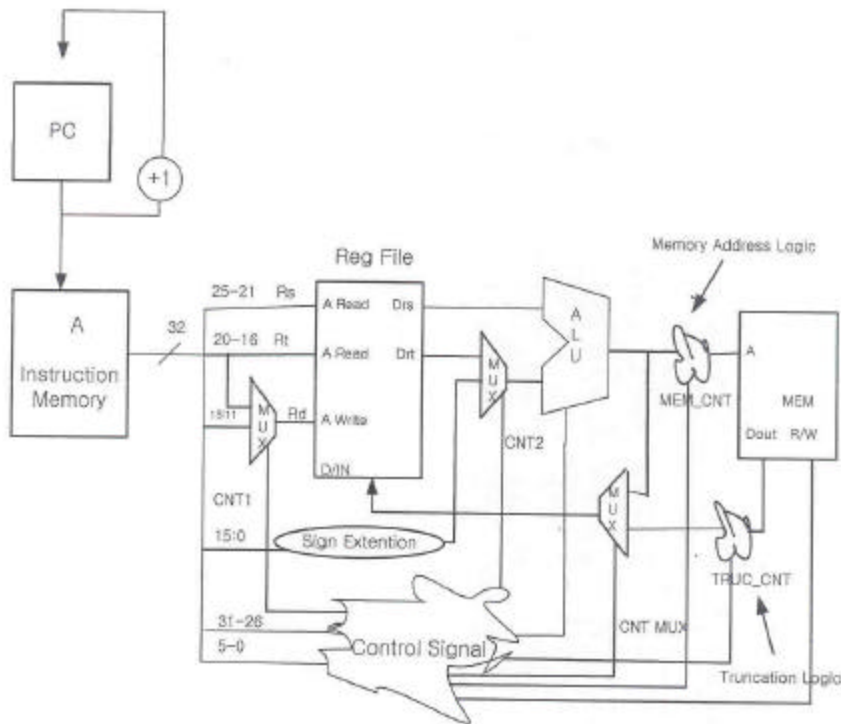We need logic to truncate extra 3 bytes data and memory address logic to access arbitrary address (Alignment problem).



So when we perform "LBU", truncation logic will give us byte data with 20^{24} zeroes padded to upper part. So we could make TRUC_CNT and MEM_CNT from Control Signal. It(LBU) can be done with above H/W. But think about "SB". Can "SB" be done with above approach?

TRUNCATE LOGIC

 

MUX-select (from Control Signal)

- if LB=> select 24 bits zeroes
- if LW=> select 24 bits from memory


But because of alignment problem and accessing arbitrary address the logic will be complicated.

Address =>	0	0	0	0	1	
	0	0	0	1	2	
	0	0	0	2	3	
	0	0	0	3	4	


<= data

The above logic is working when accessing "0000" but what about accessing "0001"?


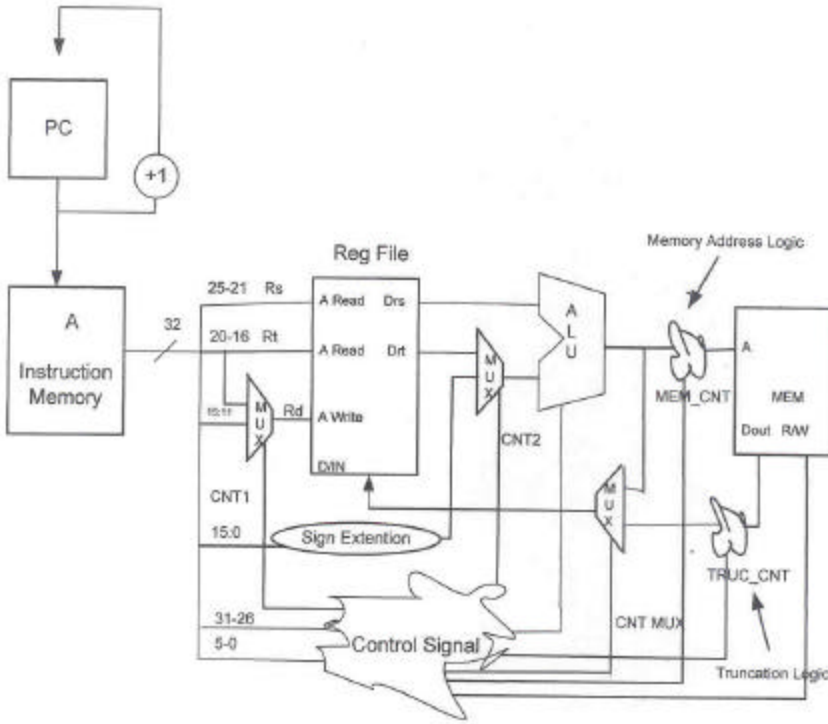
The problem of SB is we are saving only one byte out of 4 bytes. So we have to think about how to save data to the memory.
 For SW, if we assume can save 4 bytes by giving an address, SW will be easily implemented.



SW R10, 11(R12)

 

SW rt, address

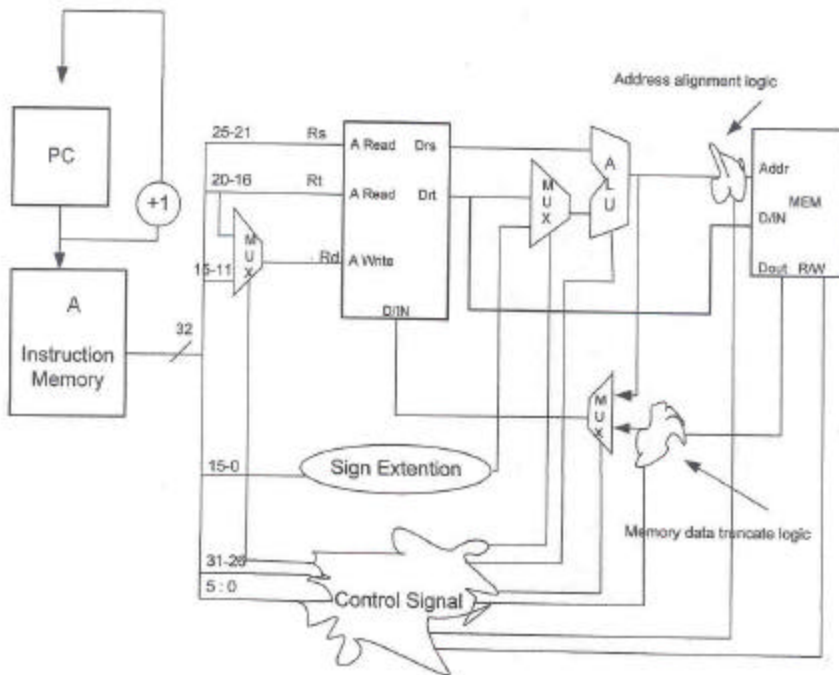 

- Can "SB" be done with above "HW"?
- Can we remove the new datapath?
- Can we just by pass through ALU?

66-a

When we cover Verilog, we implement ALU unit.

It can perform "ADD", "SUBTRACTION", "SLT", "AND", "OR", "ByPassA" and "ByPassB".

So, we could bypass Drt value through ALU, we can remove the new datapath.

BUT, The Answer is NO.

No., ALU is performing Address calculation (RS + offset).

So, we can not bypass this time.

Then we need the new datapath.

67

Again, even we can perform SW, doing "SB" is not OK.

For "LB", we could use "LW" and then truncate some bits (24 bits). But for "SB" case, we can not do that.


One way of doing that is "LW" and modifying byte information and using "SW".

But this brings extra "LW".

- So, we may assume that we could store byte and for SW instruction, we assume we could store 4 bytes.


Then we need control circuit between Drt and Din.

SB rt, address
 SB R10, 11(R12)

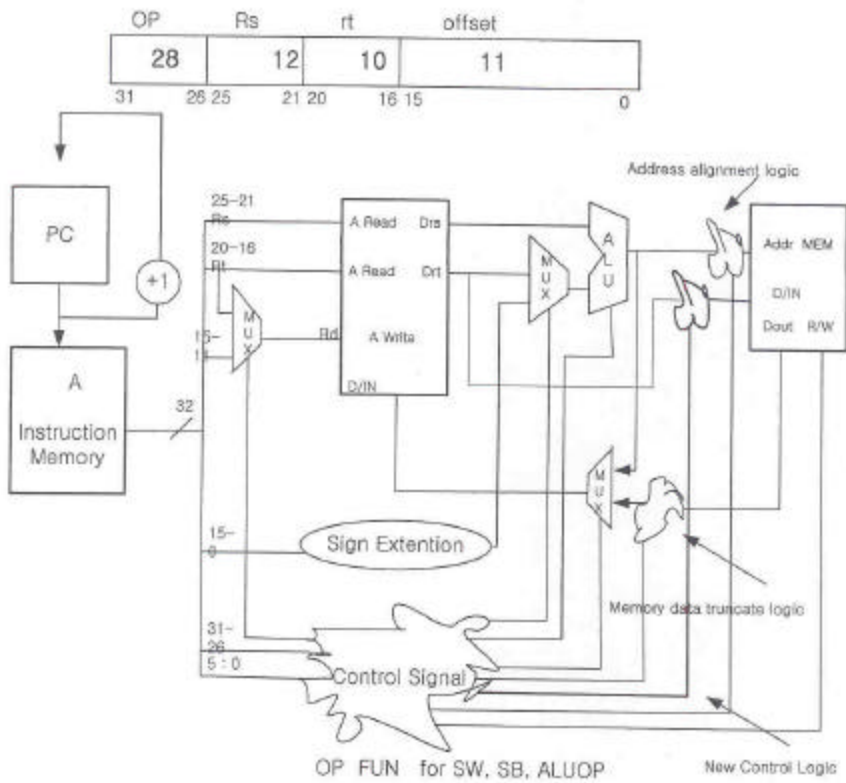

	OP	FUN	for SW, SB, ALUOP
ADD R1, R2, R3	0	20	ADD
SUB R4, R5, R6	0	22	SUB
ADDI R7, R8, 5	8	X	ADD
OR R9, R10, R11	0	25	OR
LW R7, 8(R9)	23	X	ADD
LB R1, 2(R3)	20	X	ADD
SW R10, 11(R12)	2b	X	ADD
SB R10, 11(R12)	28	X	ADD

Slt R1, R2, R3
 Slt rd, rs, rt


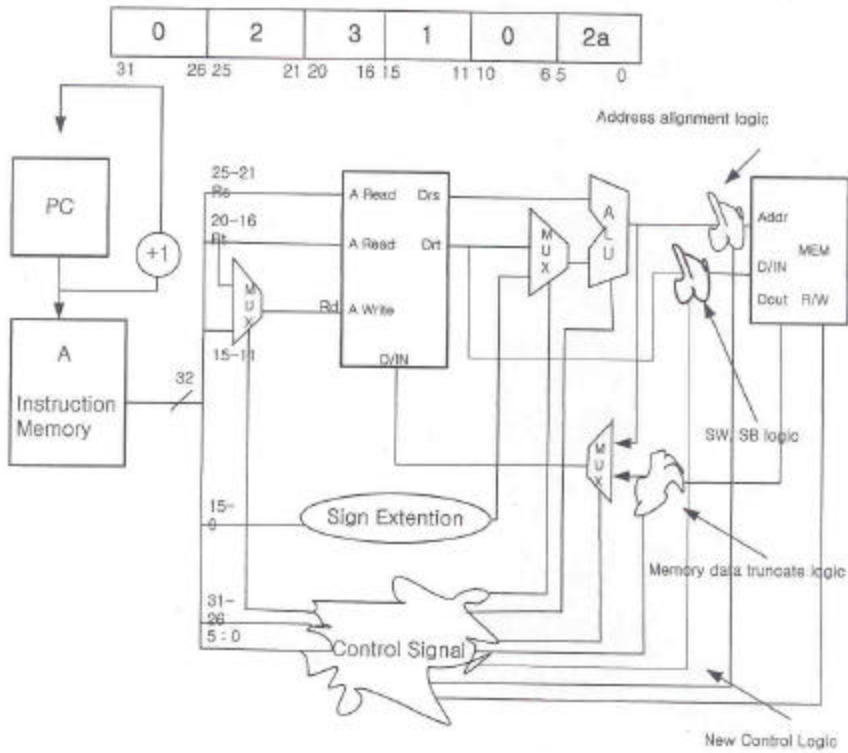


Do we need extra datapath to perform Slt?

Do we need extra HW to perform Slt?

Can the above H/W perform "SLTI"?

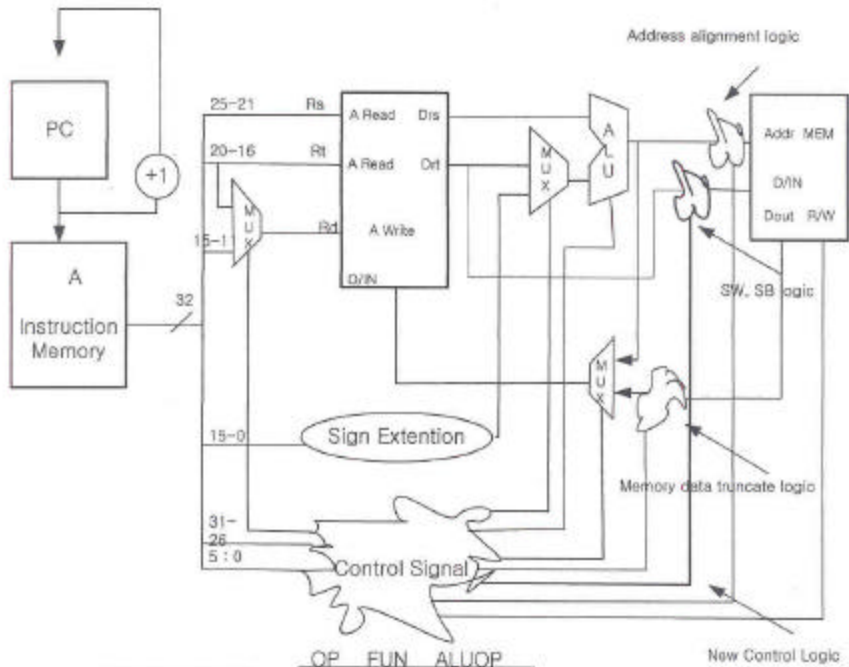 Slti R4, R5, 6
 Slti ~~rs~~ ^{rt} rs, imm




	OP	FUN	ALUOP
ADD R1, R2, R3	0	20	ADD
SUB R4, R5, R6	0	22	SUB
ADDi R7, R8, 5	8	X	ADD
OR R9, R10, R11	0	25	OR
LW R7, 8(R9)	23	X	ADD
LB R1, 2(R3)	20	X	ADD
SW R10, 11(R12)	2b	X	ADD
SB R10, 11(R12)	28	X	ADD
SLT R1, R2, R3	0	2a	SUB SLT

0x1000: BEQ R10, R11, 12

What will be the target address?
How to compute the target address?

BEQ rs, rt, label

 


What kind of action do we need?

- a) compute the target address
- b) check the branch condition (rs=rt)

Action a) needs Addition

Action b) needs Addition [Subtraction]

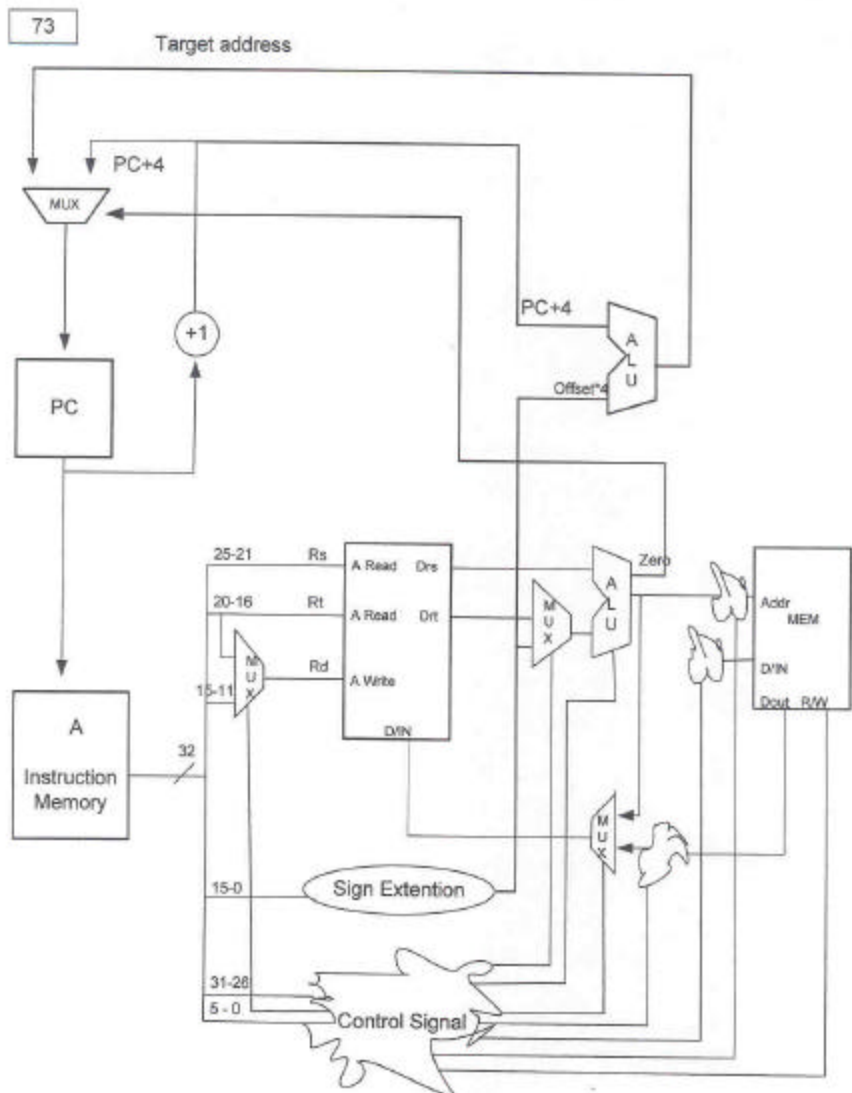



Target Address Computation logic: Added
 Branch condition logic : Added
 Multiplexor for PC+4 and Target address : Added

What's wrong with this?(What if an instruction performs subtraction and the result is zero; what will be the next address?
??

	OP	FUN	ALUOP
ADD R1, R2, R3	0	20	ADD
SUB R4, R5, R6	0	22	SUB
ADDi R7, R8, 5	8	X	ADD
OR R9, R10, R11	0	25	OR
LW R7, 8(R9)	23	X	ADD
LB R1, 2(R3)	20	X	ADD
SW R10, 11(R12)	2b	X	ADD
SB R10, 11(R12)	28	X	ADD
SLT R1, R2, R3	0	2a	SUB SLT
SLTi R4, R5, 6	a	X	SUB SLT
BEQ R10, R11, 12	4	X	SUB


Can the previous page H/W perform "BNE"?

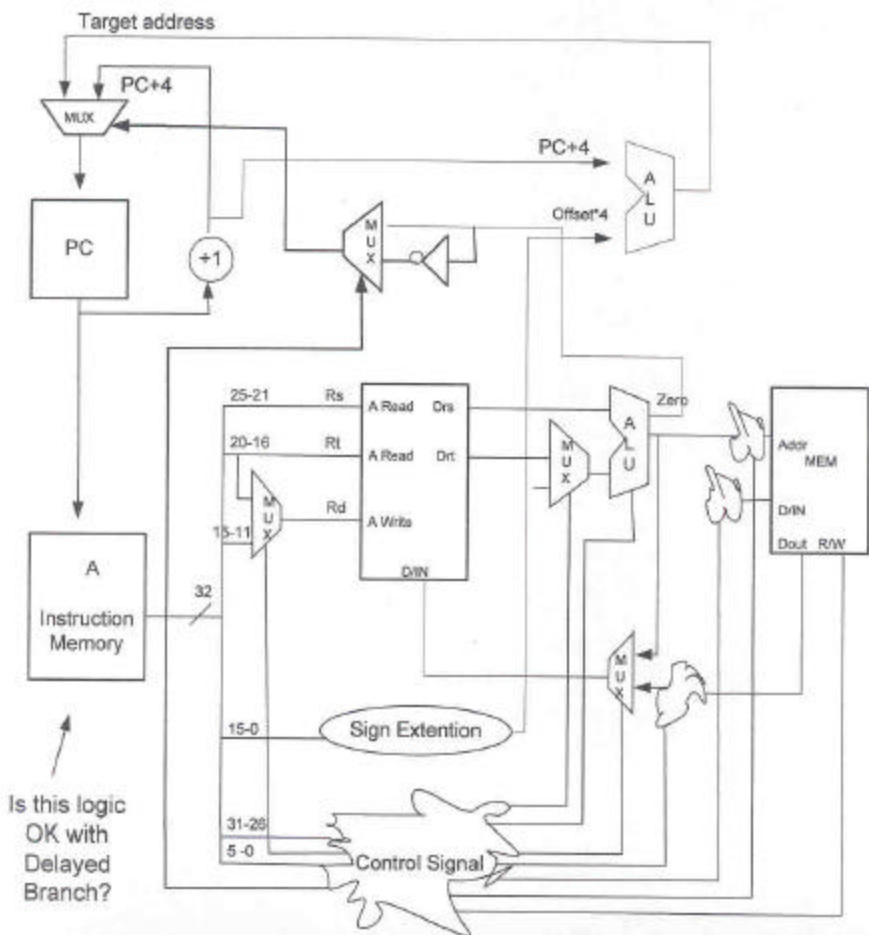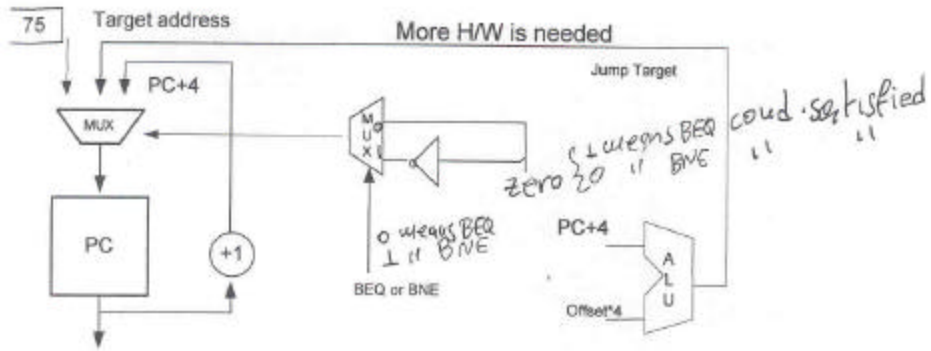- a) computing target address
- b) computing branch condition




75-a

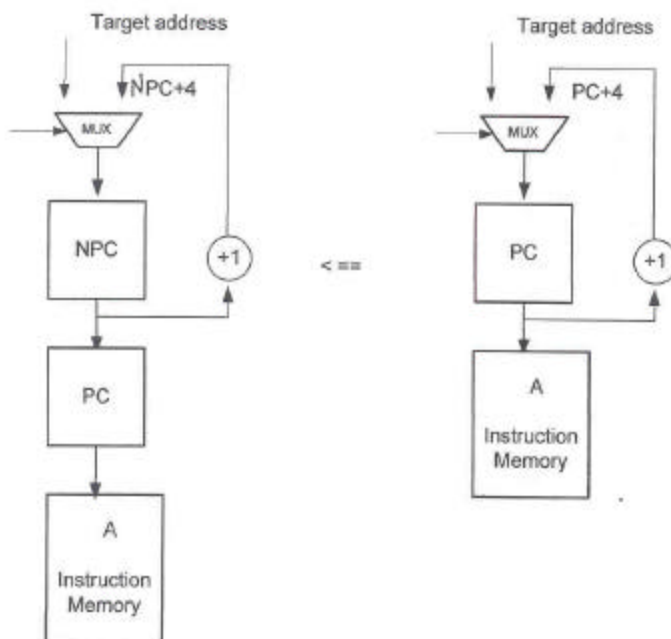
If branch condition is true, the next instruction to be executed is the branch target, instead of PC+4.
So, we need to change the H/W



BNE R10, R11, 12
 BNE Rs, Rt, label

 

JUMP
 j target j ox2000

 

How to compute the target address?


a) Address computation logic is needed.

Target address computation

{ pc [31:28], target, 00 }

$$10000000 + 2000 * 4$$

$$= 10008000 \text{ target address}$$

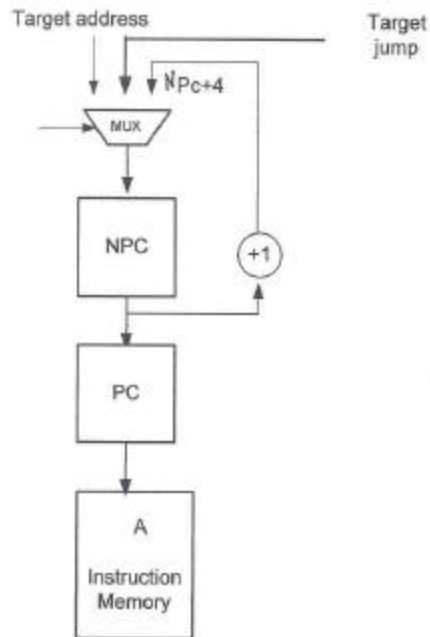

77-a

Target address computation

{ pc [31:28], target, 00 }

$$10000000 + 2000 * 4$$

= 10008000 target address

0x10000000 jr 0x2000

0001 0000 0000 0000 0000 0000 0000 0000 (pc)

take 0001 (pc[31:28]) 4bits


take 00 0000 0000 0010 0000 0000 0000 (target) 26bits.

0001 00 0000 0000 0010 0000 0000 0000 00(padding 2 zeros)

0001 00 0000 0000 0010 0000 0000 0000 00

0001 0000 0000 0000 1000 0000 0000 0000 (rearrange)

0X 1 0 0 0 8 0 0 0 (target address)

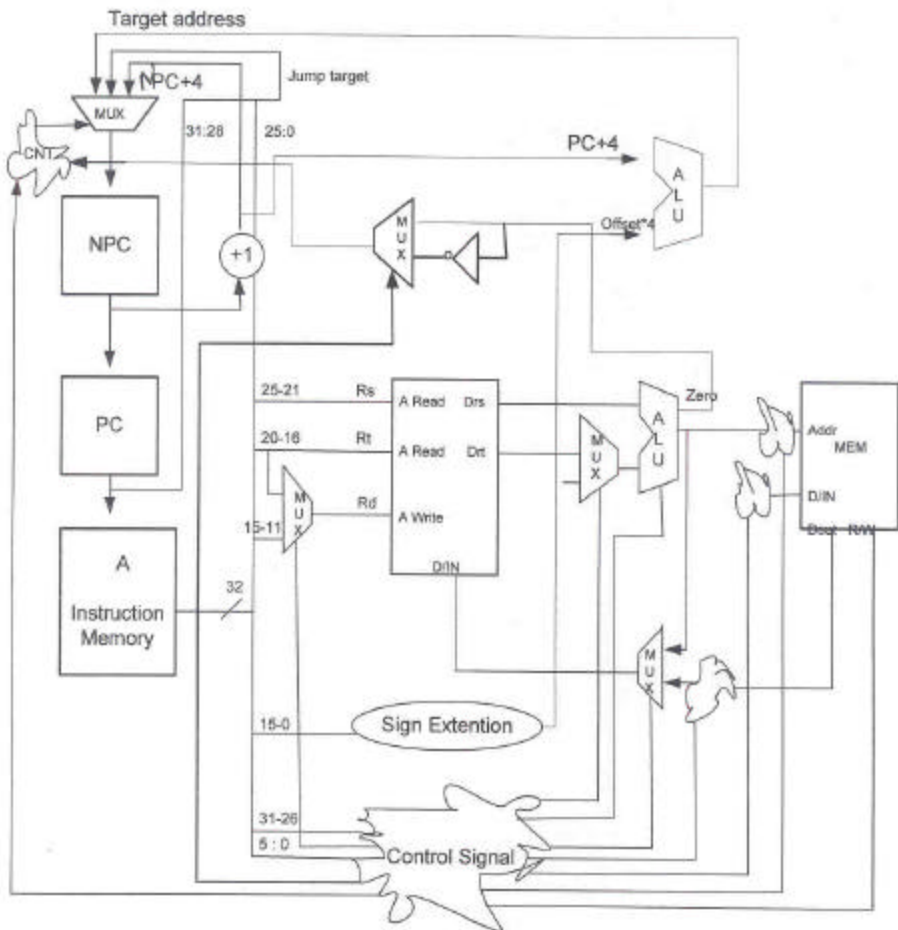


JUMP
 "Can the above H/W perform jr R10?"



Jr R10;
jr Rs




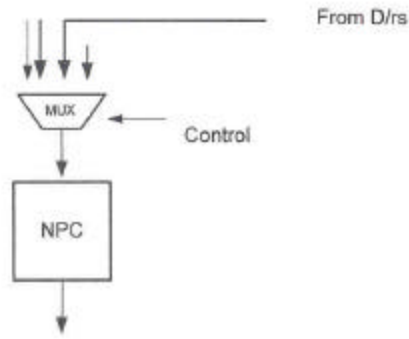Target address is in R10.
So we need a datapath from D/rs to NPC.



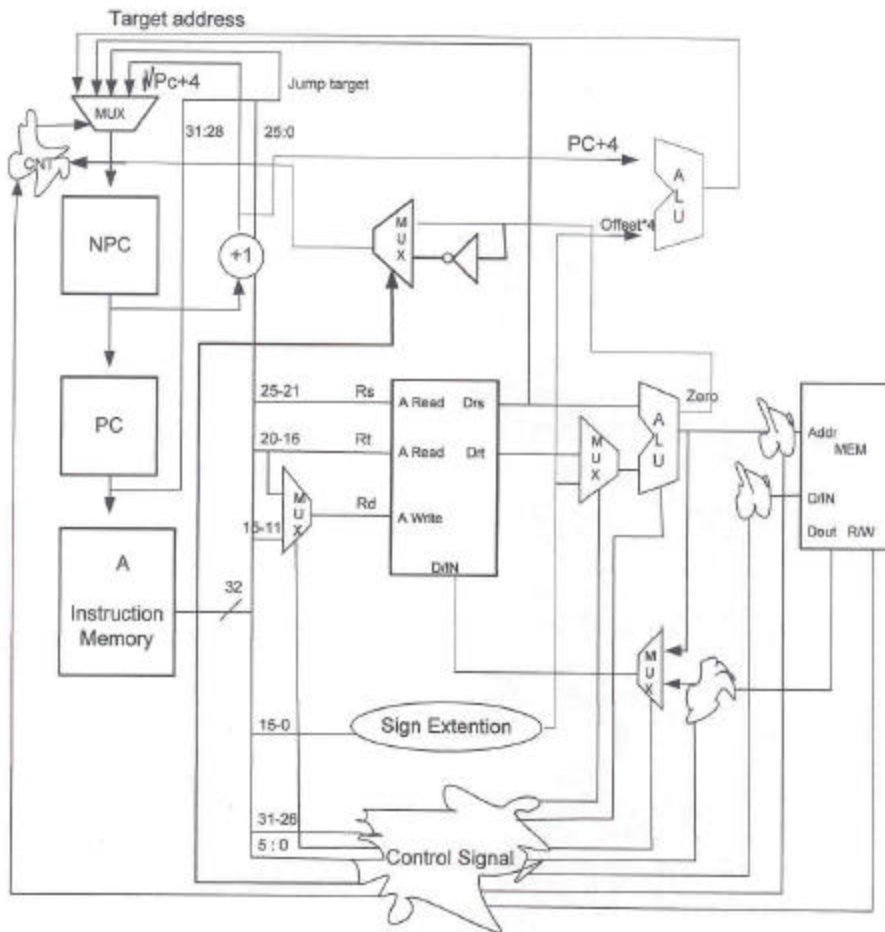The "Control" comes from
bit 31-26 and bit 5-0





“Jr Rs”


If we want to perform jal, what do we need more?

	OP	FUN	ALUOP
ADD R1, R2, R3	0	20	ADD
SUB R4, R5, R6	0	22	SUB
ADDi R7, R8, 5	8	X	ADD
OR R9, R10, R11	0	25	OR
LW R7, 8(R9)	23	X	ADD
LB R1, 2(R3)	20	X	ADD
SW R10, 11(R12)	2b	X	ADD
SB R10, 11(R12)	28	X	ADD
SLT R1, R2, R3	0	2a	SLT
SLTi R4, R5, 6	a	X	SLT
BEQ R10, R11, 12	4	X	SUB
BNE	5	X	SUB
J 2000	2	X	X
JR R10	0	8	X


For Jal instruction, everything is the same as j instruction, except, we have to save

~~PC~~ to "R31".
~~PC+8 or NPCT4 to R31~~ \rightarrow PC+8 or NPCT4 to ~~R31~~ R31

Jal ox2000

 


 So we need data path to D/In from NPC and datapath to Awrite to point ra (r31)



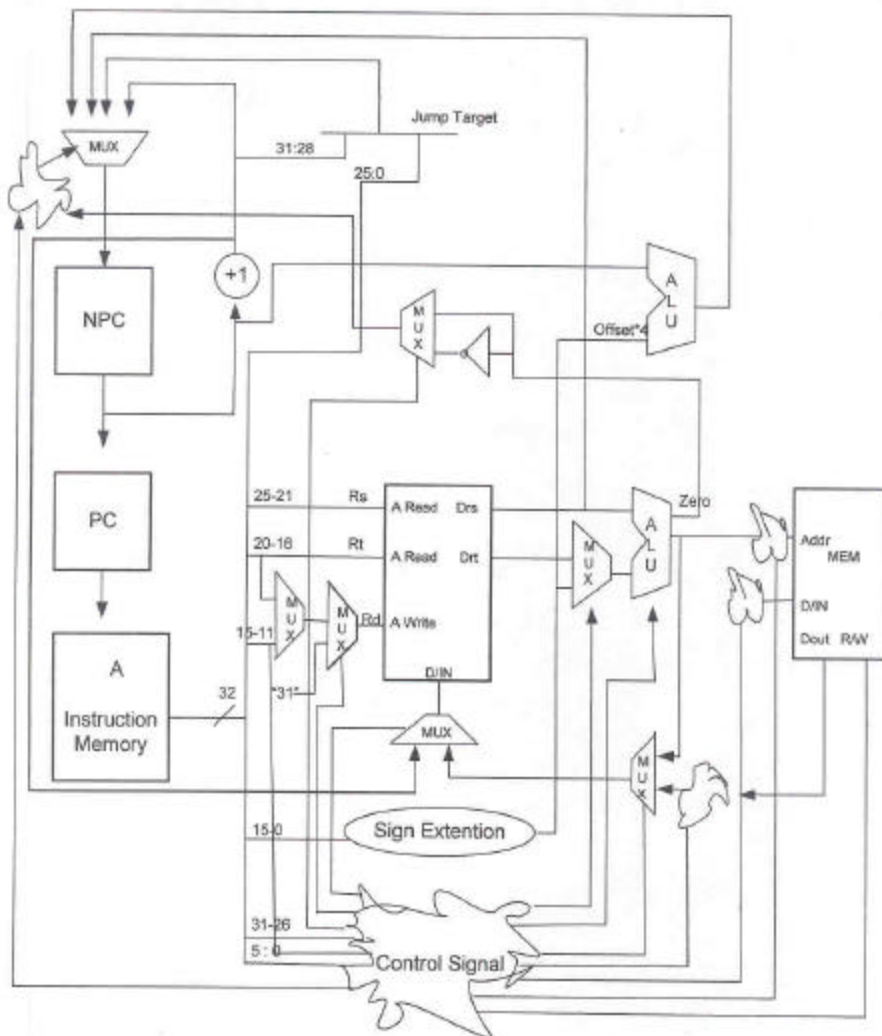This way, we could save PC+8 to ra.
The control and CNT signals can be coming from Control logic.






“jal ox2000”
“Added HW for saving R31”


84

 “Jalr Rs, Rd” Instruction.
Everything is same to jr rs instruction,
except we have to save the return
address to “rd”.



Jalr R10, R11

Do we need new datapath? *No*
No

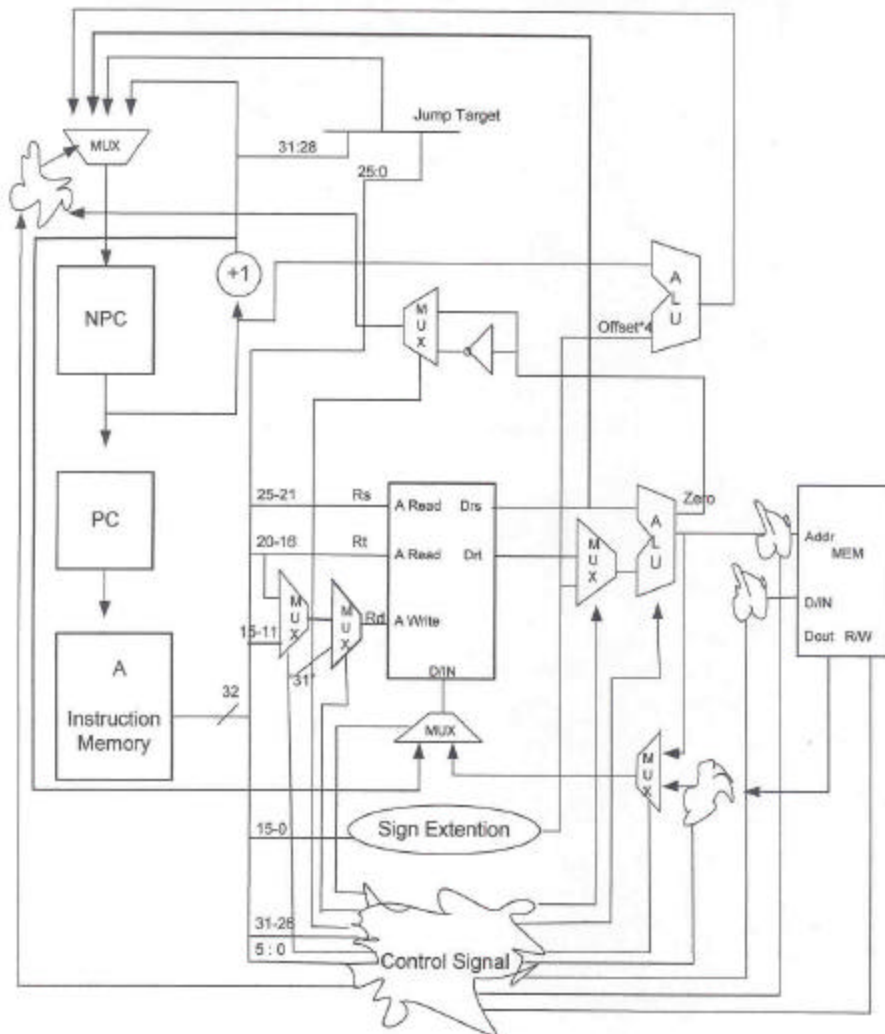

`jalr R10, R11`
 We don't need new datapath