

/// LSU EE 3755 -- Computer Organization

//

/// Verilog Notes 2 -- Expressions

/// Contents

// Continuous Assignment

// Operators: Bitwise Logical

// Vectors, Bit Selects, and Part Select

// Sized Numbers and Constants (Parameters)

// Operators: Bitwise with Vectors

// Operators: Arithmetic

// Operators: Logical AND, etc

/// References

// :P: Palnitkar, "Verilog HDL"

// :Q: Qualis, "Verilog HDL Quick Reference Card Revision 1.0"

// :PH: Patterson & Hennessy, "Computer Organization & Design"

||||||||||||||||||||||||||||||||||||||||

/// Continuous Assignment

```
// :P: 6.1

// Continuous assignment specifies a value for a wire using an
// expression.

//
//

// Continuous assignments can be made using the /assign/ keyword and in a
// wire [or other net] declaration.

// :Keyword: assign

//
// :Sample: assign a = b;
//
// Here "b" is the expression.

// The left hand side of an assignment always should be a wire[net].
// :Example:

//
// A simple use of the assign keyword. Output x is given
// the value of "a". Whenever "a" changes "x" also changes.
// Don't forget that: Whenever "a" changes "x" also changes.

//
// The module below passes the signal through unchanged.

module really_simple(x,a);
    input a;
```

```
output x;  
  
assign x = a;  
  
endmodule  
  
  
// :Example:  
  
//  
  
// The module below is functionally equivalent to the one above.  
  
  
module really_simple_with_a_gate(x,a);  
  
    input a,;  
  
    output x;  
  
  
    and a1(x,a);  
  
  
endmodule  
  
  
// :Example:  
  
//  
  
// The module below also passes a signal through the module unchanged,  
// but this time it goes through an extra wire, w. Whenever "a"  
//
```

```
// changes, w will change and that will change x.
```

```
module something_similar(x,a);
```

```
    input a;
```

```
    output x;
```

```
    wire w;
```

```
    assign w = a;
```

```
    assign x = w;
```

```
endmodule
```

```
// :Example:
```

```
//
```

```
// The module below is like the one above except that
```

```
// continuous assignment to w is done in the wire declaration
```

```
// rather than with a separate assign statement.
```

```
module something_else_similar(x,a);
```

```
    input a;
```

```
    output x;
```

```
wire w = a;  
assign x = w;  
  
endmodule
```

```
//////////
```

```
/// Operators: Bitwise Logical
```

```
// :P: 6.3,6.4
```

```
// :P: 6.4.5
```

```
// Operators for performing bitwise logical operations.
```

```
//
```

```
// (The meaning of bitwise and logical will be explained in the Vector
```

```
// section below.)
```

```
//
```

```
//
```

```
// Operators:
```

```
// & bitwise and
```

```
// | bitwise or
```

```
// ~bitwise not
```

```
// ^ bitwise exclusive or
```

```
// :Example:  
//  
// A module implementing: x = ab + c;  
  
module my_abc_module(x,a,b,c);  
    input a, b, c;  
    output x;  
  
    assign x = a & b | c;  
  
endmodule
```

```
// :Example:  
//  
// The module below is functionally equivalent but less readable than  
// the one above.
```

```
module my_abc_module_gates(x,a,b,c);  
    input a, b, c;  
    output x;  
  
    wire ab;
```

```
and a1(ab,a,b);
```

```
or o1(x,ab,c);
```

```
endmodule
```

```
// :Example:
```

```
//
```

```
// Simple uses of the &, |, and ~ operators along with truth tables.
```

```
module operator_demo(x1,x2,x3,x4,a,b);
```

```
    input a, b;
```

```
    output x1, x2, x3, x4;
```

```
// Bitwise AND. (There is also a logical AND, discussed later.)
```

```
//
```

```
    assign x1 = a & b;
```

```
//
```

```
// a b | a & b
```

```
// *****
```

```
// 0 0 | 0
```

```
// 0 1 | 0
```

```
// 1 0 | 0
```

// 1 1 | 1

// Bitwise OR. (There is also a logical OR, discussed later.)

//

assign x2 = a | b;

//

// a b | a|b

// \*\*\*\*\*

// 0 0 | 0

// 0 1 | 1

// 1 0 | 1

// 1 1 | 1

// Bitwise XOR.

//

assign x3 = a ^ b;

//

// a b | a^b

// \*\*\*\*\*

// 0 0 | 0

// 0 1 | 1

// 1 0 | 1

// 1 1 | 0

```
// Bitwise NOT;  
//  
assign x4 = ~a;  
//  
// a | ~a  
// 0 | 1  
// 1 | 0
```

```
endmodule
```

```
// :Example:  
//  
// A binary-full adder using operators. Some consider this more  
// readable than the earlier version. Note how spaces and returns  
// (whitespace) are used to make the assignment to sum readable.
```

```
module bfa_implicit(sum,cout,a,b,cin);
```

```
    input a,b,cin;
```

```
    output sum,cout;
```

```
    assign sum =
```

```
        ~a & ~b &in |
```

```
~a & b & ~cin |  
a & ~b & ~cin |  
a & b & cin;  
  
assign cout = a & b | b & cin | a & cin;  
  
endmodule
```

```
//////////
```

```
/// Vectors, Bit Selects, and Part Select
```

```
// :P: 3.2.4
```

```
/// Vectors
```

```
//
```

```
// So far only 1-bit wires have been shown.
```

```
//
```

```
// A /vector/ is a wire [or reg] that is more than one bit.
```

```
//
```

```
// The size and the bit numbering are specified in the declaration.
```

```
// (See examples.)
```

```
// :Sample: wire [10:0] a;
```

```
// :Sample: output [10:0] b;  
//  
// Declares wire a and output b with least-significant bit 0 and  
// most-significant bit 10 (for a total of 11 bits).
```

### /// Bit and Part Selects

```
//  
// A bit select is used to extract a single bit from a wire [or reg].  
// :Sample: assign x = a[1]; // Extract bit 1.  
//  
// A part select is used to extract several consecutive bits from a  
// wire [or reg].  
// :Sample: assign y = a[5:3]; // Set y to 3 bits of a, bits 5 to 3.
```

### // :Example:

```
// This example does not use vectors. The author, who knew nothing  
// about vectors, wanted a 4-bit input "a" and a 4-bit output x,  
// plus a one-bit output msb.
```

```
module without_vectors(msb,x3,x2,x1,x0,a3,a2,a1,a0);  
output msb;
```

```
output x3, x2, x1, x0;  
input a3, a2, a1, a0;
```

```
assign msb = a3;  
assign x3 = a3;  
assign x2 = a2;  
assign x1 = a1;  
assign x0 = a0;
```

```
endmodule
```

```
// :Example:
```

```
//  
// This is the way the module above should be done. Here input "a"  
// and output "x" are declared as 4-bit vectors. A bit select  
// is used in the assignment to msb.
```

```
module with_vectors(msb,x,a);  
    output msb;  
    // Declare x as a 4-bit input, bit 3 is the most-significant bit (MSB).  
    output [3:0] x;  
    input [3:0] a;
```

```
assign msb = a[3]; // Extract bit 3 from a, which is the MSB.  
assign x = a;  
  
endmodule
```

```
// :Example:  
  
//  
// This module does the same thing as the one above. It is written  
// differently: 0 is used to indicate the MSB (rather than 3). Some  
// prefer that the MSB be the highest-numbered bit, some like it to be  
// the lowest-numbered bit.
```

```
module more_vectors(msb,x,a);  
    output msb;  
    output [0:3] x; // Here MSB is 0 and LSB is 3.  
    input [0:3] a;
```

```
    assign msb = a[0];  
    assign x = a;
```

```
endmodule
```

```
// :Example:  
//  
// Here the vector declaration is used in a wire, rather than  
// a port (input or output).
```

```
module and_more_vectors(x,a);
```

```
    input [15:0] a;
```

```
    output [15:0] x;
```

```
    wire [15:0] w;
```

```
    assign     w = a;
```

```
    assign     x = w;
```

```
endmodule
```

```
///////////
```

```
/// Sized Numbers and Constants (Parameters)
```

```
// :P: 3.1.4, 3.2.8
```

```
/// Sized Numbers
```

```
//
```

```
// In Verilog numbers can be written with a specific size and using  
// one of four radices (bases).
```

```
// The number consists of a size (in bits) followed by an apostrophe,  
// followed by a b,o,d, or h (for binary, octal, decimal,  
// hexadecimal), followed by the number.
```

```
//
```

```
// :Sample: 16'd5
```

```
//
```

```
// The number five using 16 bits written in decimal.
```

```
//
```

```
// :Sample: 16'b101
```

```
//
```

```
// The number five represented using 16 bits written in binary.
```

```
/// Constants
```

```
//
```

```
// Constants are specified using the /parameter/ keyword.
```

```
//
```

```
// :Sample: parameter limit = 5;
```

```
//
```

```
// This specifies a parameter named limit with a value of 5.
```

```
// Identifier limit can be used in expressions but cannot be
```

```
// assigned. For more information see parameter_examples module
```

```
// below.
```

```
// :Keyword:
```

```
// parameter
```

```
// :Example:
```

```
//
```

```
// The number one and the number ten are specified in a variety of  
// ways. Note the size of the wires and that each wire is assigned  
// multiple times. (In this class, one should not assign the same wire  
// multiple times. [Elsewhere, it might be done if the wire is a bus  
// and is driven by tri-state devices.])
```

```
module fixed(one,ten);
```

```
    output [7:0] one;
```

```
    output [15:0] ten;
```

```
// All assignments below do the same thing.
```

```
//
```

```
// Use the one that's easiest to read.
```

```
//
```

```
assign one = 1; // No size specified.
```

```
assign one = 8'b1; // One specified in binary.
```

```
assign one = 8'b00000001; // One specified in binary.  
assign one = 4'b1; // Sloppy, but works: Specified wrong size.  
assign one = 8'd1; // One specified in decimal.  
assign one = 8'h1; // One specified in hexadecimal;
```

```
// All assignments below do the same thing.
```

```
//
```

```
// Use the one that's easiest to read.
```

```
//
```

```
assign ten = 10;  
assign ten = 16'b1010;  
assign ten = 16'b000000000000001010;  
assign ten = 16'd10;  
assign ten = 16'ha;  
assign ten = 16'h000a;
```

```
endmodule
```

```
// :Example:
```

```
//
```

```
// A sized number is used to specify the carry in of one of the bfa's  
// in a two-bit ripple adder. It's important to use a sized number  
// (rather than a regular number) for connections to modules.
```

```
module ripple_2(sum,cout,a,b);  
    input [1:0] a, b;  
    output [1:0] sum;  
    output     cout;  
  
    wire     c0;  
  
    bfa_implicit bfa0(sum[0],c0,a[0],b[0],1'b0);  
    bfa_implicit bfa1(sum[1],cout,a[1],b[1],c0);  
  
endmodule
```

```
// :Example:  
//  
// A module illustrating the use of parameters (as constants).
```

```
module parameter_examples(an_input);  
    input [7:0] an_input;
```

```
    parameter one = 1;
```

```
// Parameters can be sized numbers.
```

```
parameter two = 10'd2;  
  
// The value of seconds_per_day is computed once, at analysis  
// (usually compile) time.  
parameter seconds_per_day = 60 * 60 * 24;  
  
parameter width = 12;  
parameter height = 21;  
  
// The value of area is computed once, at analysis  
// (usually compile) time.  
parameter area = width * height;  
  
// The line below is an error because "an_input" is not a constant.  
parameter double_input = an_input * two;  
  
endmodule
```

```
||||||||||||||||||||||||||||||||||||||||||||
```

```
/// Operators: Bitwise with Vectors
```

```
// The same references as the earlier bitwise logical section.
```

```
//
```

```
// :P: 6.3,6.4
```

```
// :P: 6.4.5
```

```
// Operators &, |, ~, ^ are called /bitwise/ because when  
// the operands are vectors the operation is done on each  
// bit of the vector.
```

```
// :Example:
```

```
//
```

```
// An appropriate use of a bitwise operator, followed by  
// code that does the same thing the hard way.
```

```
module and_again(x1,a,b);
```

```
    input [2:0] a, b; // Both a and b are 3 bits.
```

```
    output [2:0] x1;
```

```
// An appropriate use.
```

```
//
```

```
// Bitwise AND, but this time operands are 3-bit vectors.
```

```
//
```

```
assign x1 = a & b; // ANDs three pairs of bits.
```

```
// The same thing the hard way:
```

```
//  
assign x1[0] = a[0] & b[0];  
assign x1[1] = a[1] & b[1];  
assign x1[2] = a[2] & b[2];  
  
//  
// Examples:  
  
//  
// a  b  | a & b  
// 000 000 | 000  
// 000 001 | 000  
// 010 111 | 010  
// 100 110 | 100  
  
endmodule  
  
///////////  
/// Operators: Arithmetic  
  
// :P: 6.4.1  
  
//  
  
// The arithmetic operators are:
```

```
// + (addition), - (subtraction), * (multiplication), / (division),
// and % (remainder).
```

```
// They operate on wires and data types to be covered later.
```

```
// :Example:
```

```
//
```

```
// A simple demonstration of arithmetic operators.
```

```
module arith_op(sum,diff,prod,quot,rem,a,b);
```

```
    input [15:0] a, b;
```

```
    output [15:0] sum, diff, prod, quot, rem;
```

```
// For these operators vectors are interpreted as integers.
```

```
// Addition
```

```
    assign sum = a + b;
```

```
// Subtraction
```

```
    assign diff = a - b;
```

```
// Multiplication
```

```
    assign prod = a * b;
```

```
// Division  
assign quot = a / b;  
  
// Remainder (Modulo)  
assign rem = a % b;  
  
//  
// Examples:  
//  
// a  b  | a % b  
// 3  5  | 3  
// 5  3  | 2  
// 7  7  | 0  
  
endmodule  
  
// :Example:  
//  
// The input to the module below is a complex number (specified  
// with a real and imaginary part); the output is the square  
// of that number.
```

```
module complex_square(sr,si,ar,ai);  
    input [31:0] ar, ai;  
    output [31:0] sr, si;  
  
    assign     sr = ar * ar - ai * ai;  
    assign     si = 2 * ar * ai;  
  
// Notes on code above:  
//  
// Multiplication has higher precedence than subtraction and so  
// subtraction done last.  
//  
// A constant is used in the si expression.  
  
endmodule
```

```
///////////
```

```
/// Operators: Logical AND, etc
```

```
// :P: 6.4.2
```

```
// There is a logical AND operator, &&, that is different than  
// the bitwise AND, &.
```

```
// Likewise there is a logical OR, ||, and a logical NOT, !.
```

```
// See the example.
```

```
// :Example:
```

```
//
```

```
// Illustration of logical operators, and how they are different than  
// the bitwise operators.
```

```
module and_again_again(x1,x2,x3,x4,a,b);
```

```
    input [2:0] a, b; // Both a and b are 3 bits.
```

```
    output [2:0] x1;
```

```
    output x2, x3, x4;
```

```
// Bitwise AND, but this time operands are 3-bit vectors.
```

```
//
```

```
assign x1 = a & b; // ANDs three pairs of bits.
```

```
//
```

```
// The same thing the hard way:
```

```
//
```

```
assign x1[0] = a[0] & b[0];
```

```
assign x1[1] = a[1] & b[1];
```

```
assign x1[2] = a[2] & b[2];
```

```
//  
// Examples:  
//  
// a b | a & b  
// """"  
// 000 000 | 000  
// 000 001 | 000  
// 010 111 | 010  
// 100 110 | 100  
  
// Logical AND. (Not to be confused with bitwise AND!)  
//  
assign x2 = a && b;  
//  
// Here both a and b are 3 bits, but x2 is a single bit.  
// Wire a is treated as logical true if any bit is 1;  
// it is treated as logical false if all bits are 0.  
//  
// Therefore x2 is set to 1 if a and b are true and to zero  
// if a or b is false.  
//  
// Examples:  
//  
// a b | a && b
```

```
// *****
// 000 000 | 0
// 000 001 | 0
// 010 101 | 1
// 100 110 | 1

// Logical OR. (Not to be confused with bitwise OR.)
//
assign x3 = a || b;
//
// Operands are treated as logical values as described for &&.
//
// Wire x3 is set to 1 if a or b is true and to zero
// if a and b are false.
//
// Examples:
//
// a  b  | a || b
// *****
// 000 000 | 0
// 000 001 | 1
// 010 101 | 1
// 100 110 | 1
```

```
// Logical NOT.  
//  
assign x4 = !a;  
//  
// Wire x4 is set to zero if any bit in a is 1,  
// x4 is set to one if all bits in a are zero.  
  
endmodule
```