

Class Notes

for EE 7715

Part I

Instructor: Alex Skarvantzos


# The Carry Lookahead Adder (1) a

Consider two  $n$ -bit binary numbers

$$A = (A_{n-1} A_{n-2} \dots A_1 A_0)_2$$

$$B = (B_{n-1} B_{n-2} \dots B_1 B_0)_2$$

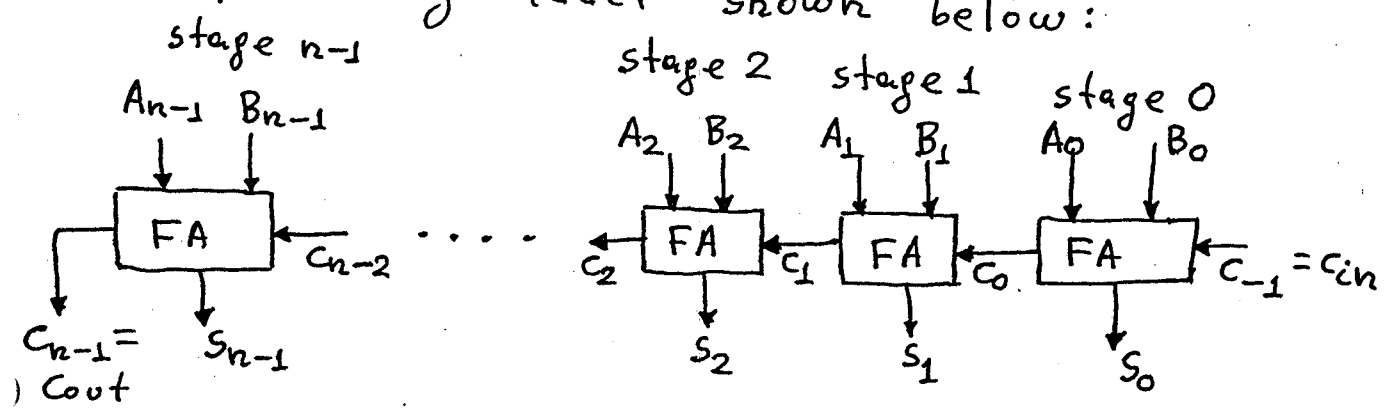One simple design of a binary adder is the ripple carry adder shown below:




The ripple carry adder shown above is a slow design. Its propagation delay is  $n \times D_{FA}$  where  $D_{FA}$  is the propagation delay through a Full Adder (FA).

A faster design of a binary adder is the carry lookahead adder presented next. The following notations will be used in this handout:

- denotes AND operation
- + denotes OR operation
- ⊕ denotes Exclusive-OR operation

 1) Consider the stage  $i$  of the addition of two  $n$ -bit numbers (2) a



The truth table and logic equations of the Full Adder (FA) are shown below:

$A_i$	$B_i$	$C_{i-1}$	$C_i$	$S_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$C_i = A_i \cdot B_i + C_{i-1} \cdot (A_i \oplus B_i)$$

$$S_i = A_i \oplus B_i \oplus C_{i-1}$$

The above truth table can be rewritten as shown below

$A_i$	$B_i$	$C_i$
0	0	0
0	1	$C_{i-1}$
1	0	$C_{i-1}$
1	1	1

Define the functions  $G_i$  and  $P_i$  as follows: (3) a

$$\begin{aligned} G_i &= A_i \cdot B_i \\ P_i &= A_i \oplus B_i \end{aligned} \quad (1)$$

The function  $G_i$  is called "carry generate" function and reflects the condition where a carry out is generated at the  $i$ th stage. The function  $P_i$  is called "carry propagate" function. This function  $P_i$  is true when the  $i$ th stage will propagate the incoming carry  $c_{i-1}$  to the next higher stage.

Using the expressions of  $G_i$ ,  $P_i$  of equation (1), the logic equations for  $c_i$  and  $s_i$  of the previous page become

$$c_i = G_i + c_{i-1} \cdot P_i \quad (2)$$

$$s_i = P_i \oplus c_{i-1} \quad (3)$$

Repeatedly applying the recursive equat. (2) one gets the following set of carry equations in terms of the  $G_i$ 's, the  $P_i$ 's and the initial carry input  $c_{-1}$ :

$$c_0 = G_0 + c_{-1} \cdot P_0$$

$$c_1 = G_1 + c_0 \cdot P_1 = G_1 + G_0 \cdot P_1 + c_{-1} \cdot P_0 \cdot P_1$$

$$c_2 = G_2 + c_1 \cdot P_2 = G_2 + G_1 \cdot P_2 + G_0 \cdot P_1 \cdot P_2 + c_{-1} \cdot P_0 \cdot P_1 \cdot P_2$$

$$c_3 = G_3 + c_2 \cdot P_3 = G_3 + G_2 \cdot P_3 + G_1 \cdot P_2 \cdot P_3 + G_0 \cdot P_1 \cdot P_2 \cdot P_3$$

$$+ c_{-1} \cdot P_0 \cdot P_1 \cdot P_2 \cdot P_3$$

⋮  
⋮  
⋮  
⋮  
⋮

$$c_{n-1} = G_{n-1} + G_{n-2} \cdot P_{n-1} + G_{n-3} \cdot P_{n-2} \cdot P_{n-1} + \dots + G_0 \cdot P_1 \cdot P_2 \dots \cdot P_{n-1}$$

$$+ c_{-1} \cdot P_0 \cdot P_1 \cdot P_2 \dots \cdot P_{n-1}$$

(4)

(4) a

The previous derivations form the basis <sup>(5) a</sup> for the design of the carry lookahead (CLA) adder. The block diagram below shows a carry lookahead (CLA) adder.

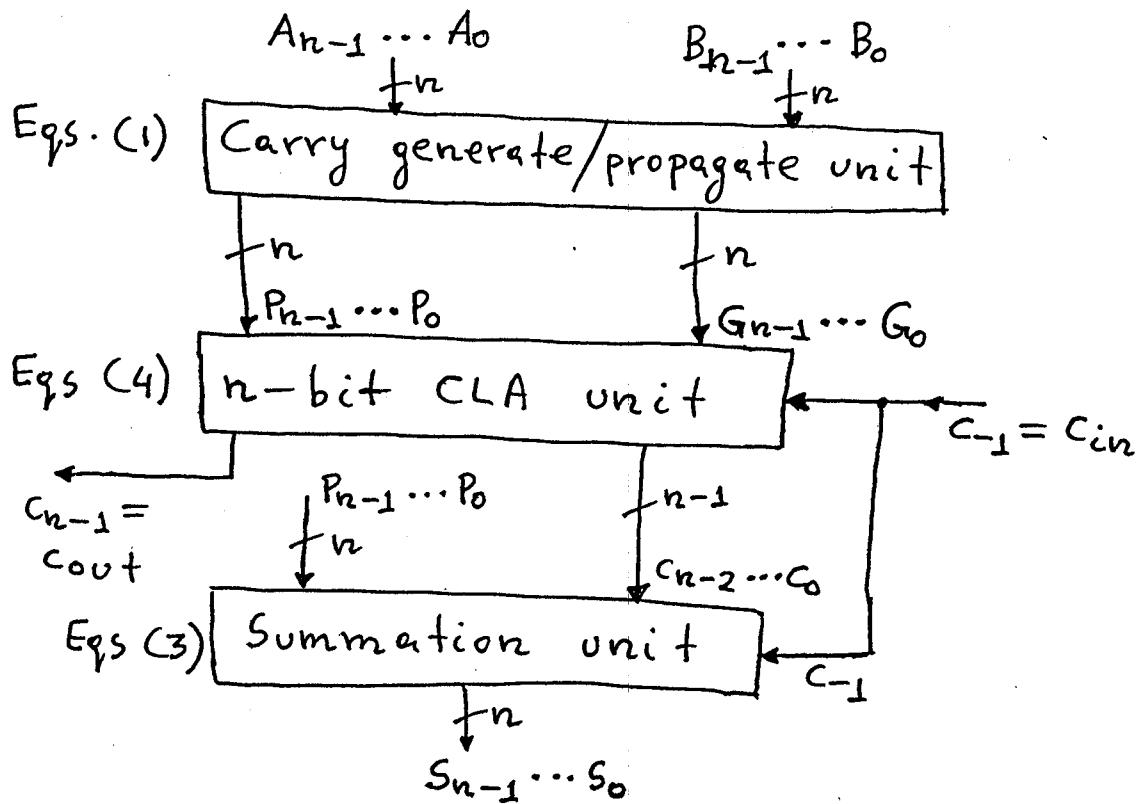


Fig 1: The block diagram of a CLA adder.

If

$D_1$  = propagation delay through the carry generate/propagate unit;

$D_2$  = propagation delay through the CLA unit;

$D_3$  = propagation delay through the summation unit

then the propagation delay through the above CLA adder is  $D_1 + D_2 + D_3$ .

6a  
There is a major problem when the  $n$ -bit CLA unit of figure 1 relies on implementing the set of equations (4). The problem is that as  $n$  becomes large, the number of inputs to the high-order gates in the CLA logic also becomes large. From equations (4), it can be seen that  $C_{n-1}$  (the carry out) relies on AND/OR logic, with the largest AND and OR gates requiring  $n+1$  inputs. For large values of  $n$ , current technologies might not supply logic gates with such a large number of inputs.


The above problem can be solved by partitioning the adder into blocks. The situation is clarified by the presentation offered below.

- Block generate/block propagate

Consider, for example, a 16-bit addition decomposed into four 4-bit blocks as shown below.

↳ go to next page

⑦ a

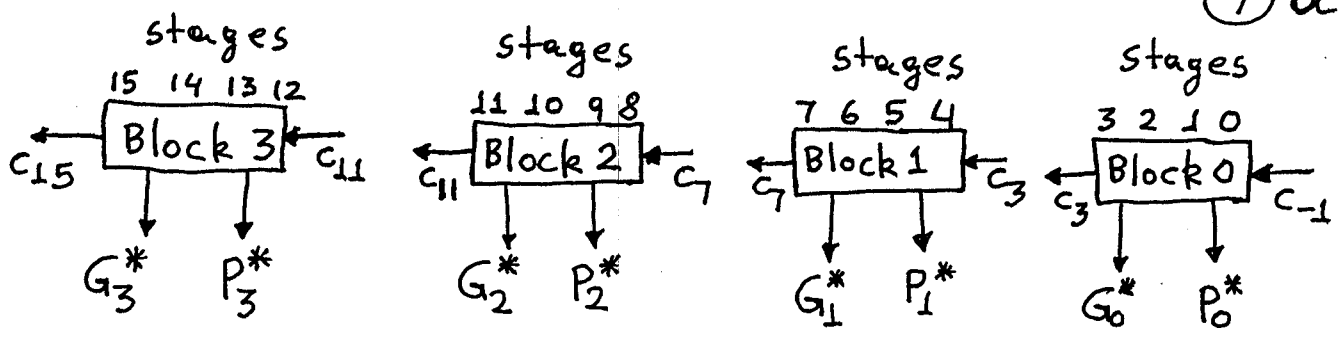

The above figure does not reflect any implementation but just shows the decomposition of the 16-bit addition into four blocks.

The new functions  $G_0^*$ ,  $G_1^*$ ,  $G_2^*$ ,  $G_3^*$  are the "block generate" functions of blocks 0, 1, 2, 3 respectively. The functions  $P_0^*$ ,  $P_1^*$ ,  $P_2^*$ ,  $P_3^*$  are the "block propagate" functions of blocks 0, 1, 2, 3.

- The function  $G_i^*$  is true when the carry out of the  $i$ th block is generated within the  $i$ th block itself.
- The function  $P_i^*$  is true when the carry in to the  $i$ th block is propagated through the entire  $i$ th block.

Expressions for  $G_0^*$ ,  $P_0^*$ ,  $G_1^*$ ,  $P_1^*$  follow:

$$G_0^* = G_3 + G_2 \cdot P_3 + G_1 \cdot P_2 \cdot P_3 + G_0 \cdot P_1 \cdot P_2 \cdot P_3$$

$$P_0^* = P_0 \cdot P_1 \cdot P_2 \cdot P_3$$



$$G_4^* = G_7 + G_6 \cdot P_7 + G_5 \cdot P_6 \cdot P_7 + G_4 \cdot P_5 \cdot P_6 \cdot P_7$$

(8) a

$$P_1^* = P_4 \cdot P_5 \cdot P_6 \cdot P_7$$

Similar expressions hold true for  $G_2^*$ ,  $P_2^*$ ,  $G_3^*$ ,  $P_3^*$ .

Important Observation: As seen from the above expressions, the block generates  $G_i^*$ 's and block propagates  $P_i^*$ 's are functions of only the bit-level generate and propagate functions but do not depend on any carry-in.

Expressions for the carry outputs  $C_3$ ,  $C_7$ ,  $C_{11}$ ,  $C_{15}$  follow. The carry outputs are expressed as functions of the block generate and propagate functions as well as  $C_{-1}$  (the carry-in).

$$C_3 = G_0^* + C_{-1} \cdot P_0^*$$

$$C_7 = G_1^* + G_0^* \cdot P_1^* + C_{-1} \cdot P_0^* \cdot P_1^*$$

$$C_{11} = G_2^* + G_1^* \cdot P_2^* + G_0^* \cdot P_1^* \cdot P_2^* + C_{-1} \cdot P_0^* \cdot P_1^* \cdot P_2^*$$

$$C_{15} = G_3^* + G_2^* \cdot P_3^* + G_1^* \cdot P_2^* \cdot P_3^* + G_0^* \cdot P_1^* \cdot P_2^* \cdot P_3^* + C_{-1} \cdot P_0^* \cdot P_1^* \cdot P_2^* \cdot P_3^*$$

The previous discussions form the basis for the two-level carry lookahead (CLA) adder. A 32-bit two-level CLA adder is shown by figure 2 on the next page.

9a

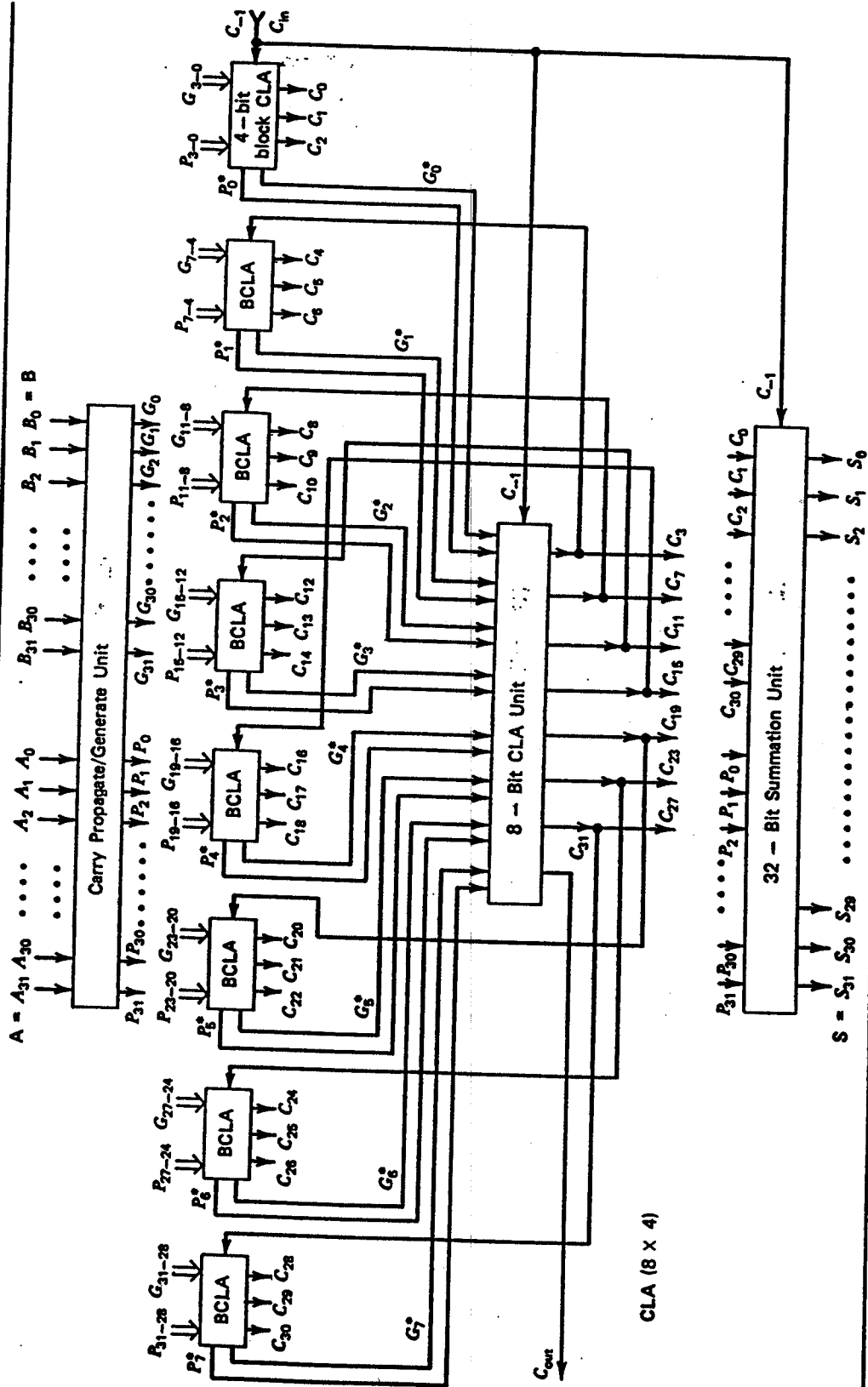


Figure 2 Two-level carry lookahead adder with 32-bit word length arranged in an 8-by-4 configuration.

## Explanation of figure 2

(10) a

Let  $D_1, D_2, D_3, D_4$  be:

$D_1$  = worst case propagation delay through the carry generate/propagate unit.

$D_2$  = worst case propagation delay through a 4-bit BCLA unit.

$D_3$  = worst case propagation delay through the 8-bit CLA unit.

$D_4$  = worst case propagation delay through the summation unit.

- The inputs  $A = A_{31} \dots A_0$ ,  $B = B_{31} \dots B_0$  and  $c_{-1} = c_{in}$  are available at time 0 (zero).
- The bit-level generates and propagates  $G_0, \dots, G_{31}$ ,  $P_0, \dots, P_{31}$  are available at time  $D_1$ .
- The block generates and block propagates  $G_0^*$ ,  $\dots, G_7^*$ ,  $P_0^*, \dots, P_7^*$  are available at time  $D_1 + D_2$ . Also, the correct  $c_0, c_1, c_2$  are available at time  $D_1 + D_2$ .
- The carry outputs  $c_3, c_7, c_{11}, c_{15}, c_{19}, c_{23}, c_{27}, c_{31} = c_{out}$  are available at time  $D_1 + D_2 + D_3$ .

• The correct  $c_4, c_5, c_6, c_8, c_9, c_{10}, c_{12}, c_{13}, c_{14}, c_{16}, c_{17}, c_{18}, c_{20}, c_{21}, c_{22}, c_{24}, c_{25}, c_{26}, c_{28}, c_{29}, c_{30}$  are available at time  $D_1 + D_2 + D_3 + D_2$ . (11) a

• The correct summation bits  $s_0, s_1, \dots, s_{31}$  are available at time  $D_1 + D_2 + D_3 + D_2 + D_4$ .

Thus, the worst case propagation delay through the entire 32-bit CLA adder of figure 2 is  $D_1 + 2D_2 + D_3 + D_4$ .

Question 1: Write the equations by which the carry generate/propagate unit computes  $G_{10}$  and  $P_7$ .

Answer:  $G_{10} = A_{10} \cdot B_{10}$  ;  $P_7 = A_7 \oplus B_7$ .

Question 2: Write the equations by which the appropriate BCLA unit computes  $P_3^*$  and  $G_3^*$ .

Answer:  $P_3^* = P_{12} \cdot P_{13} \cdot P_{14} \cdot P_{15}$

$G_3^* = G_{15} + G_{14} \cdot P_{15} + G_{13} \cdot P_{14} \cdot P_{15} + G_{12} \cdot P_{13} \cdot P_{14} \cdot P_{15}$

Question 3: Write the equation by which the 8-bit CLA unit computes  $c_{15}$  (12) a

Answer:

$$c_{15} = G_3^* + G_2^* \cdot P_3^* + G_1^* \cdot P_2^* \cdot P_3^* + G_0^* \cdot P_1^* \cdot P_2^* \cdot P_3^* + c_{-1} \cdot P_0^* \cdot P_1^* \cdot P_2^* \cdot P_3^*$$

Question 4: Write the equation by which the appropriate BCLA unit computes  $c_{22}$ .

Answer:





$$c_{22} = G_{22} + G_{21} \cdot P_{22} + G_{20} \cdot P_{21} \cdot P_{22} + c_{19} \cdot P_{20} \cdot P_{21} \cdot P_{22}$$

Question 5: Write the equation by which the summation unit computes  $s_{12}$ .




Answer:  $s_{12} = P_{12} \oplus c_{11}$

Minimum delay CSA trees

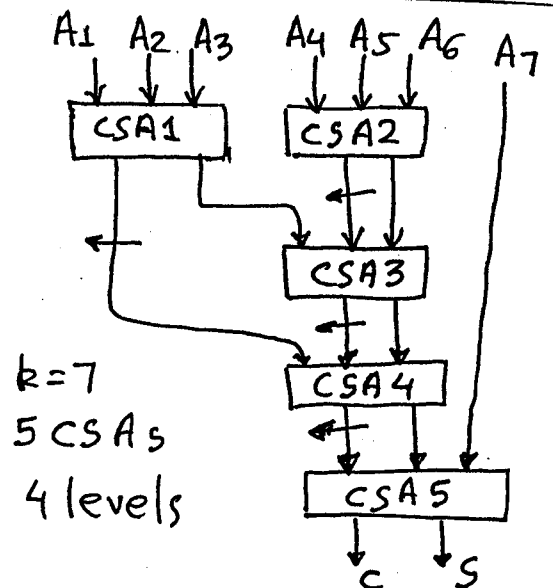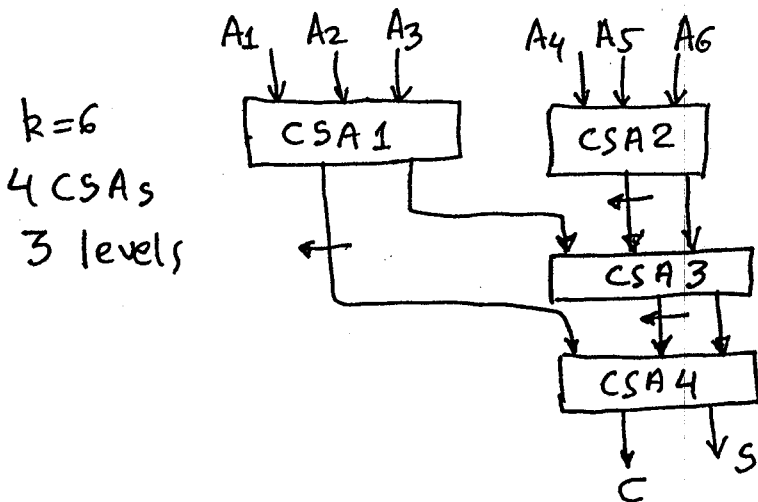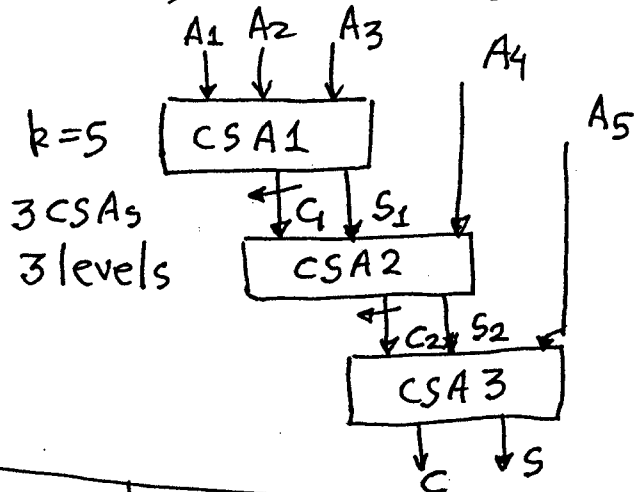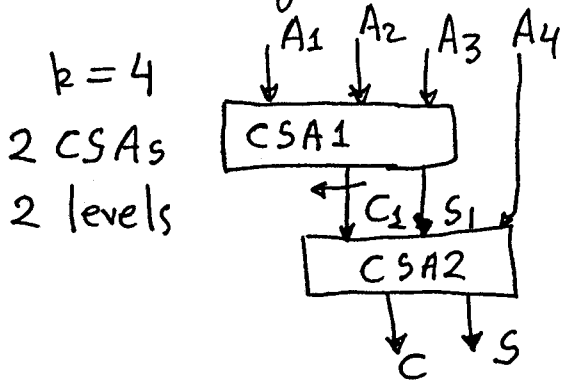The figures below show several minimum delay CSA trees for adding  $k$  numbers and reducing them down to two; (S vector, C vector)




② b

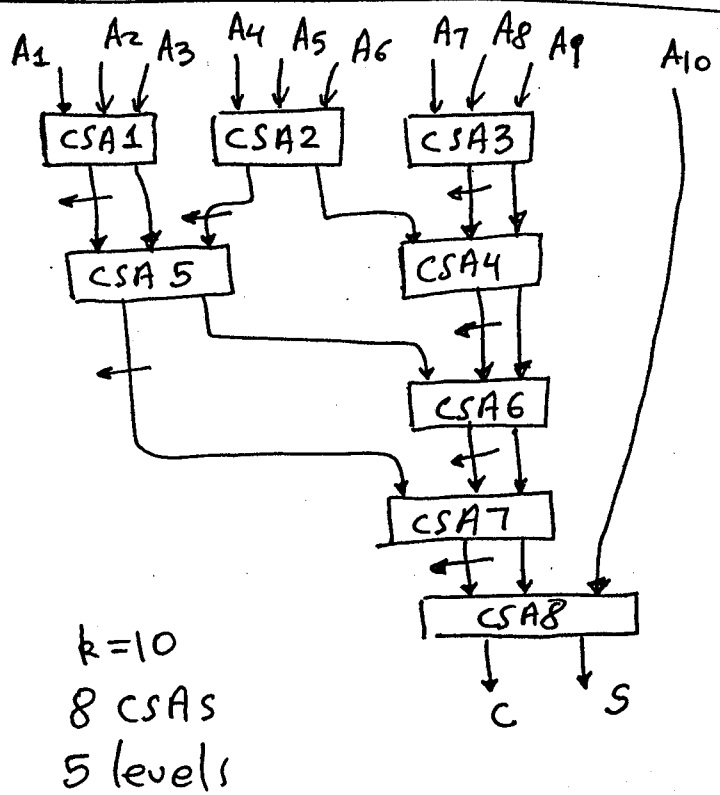 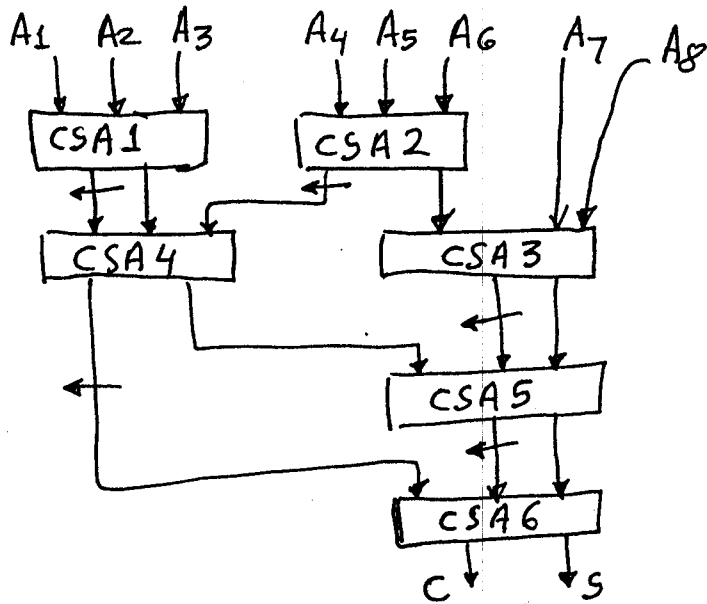


①

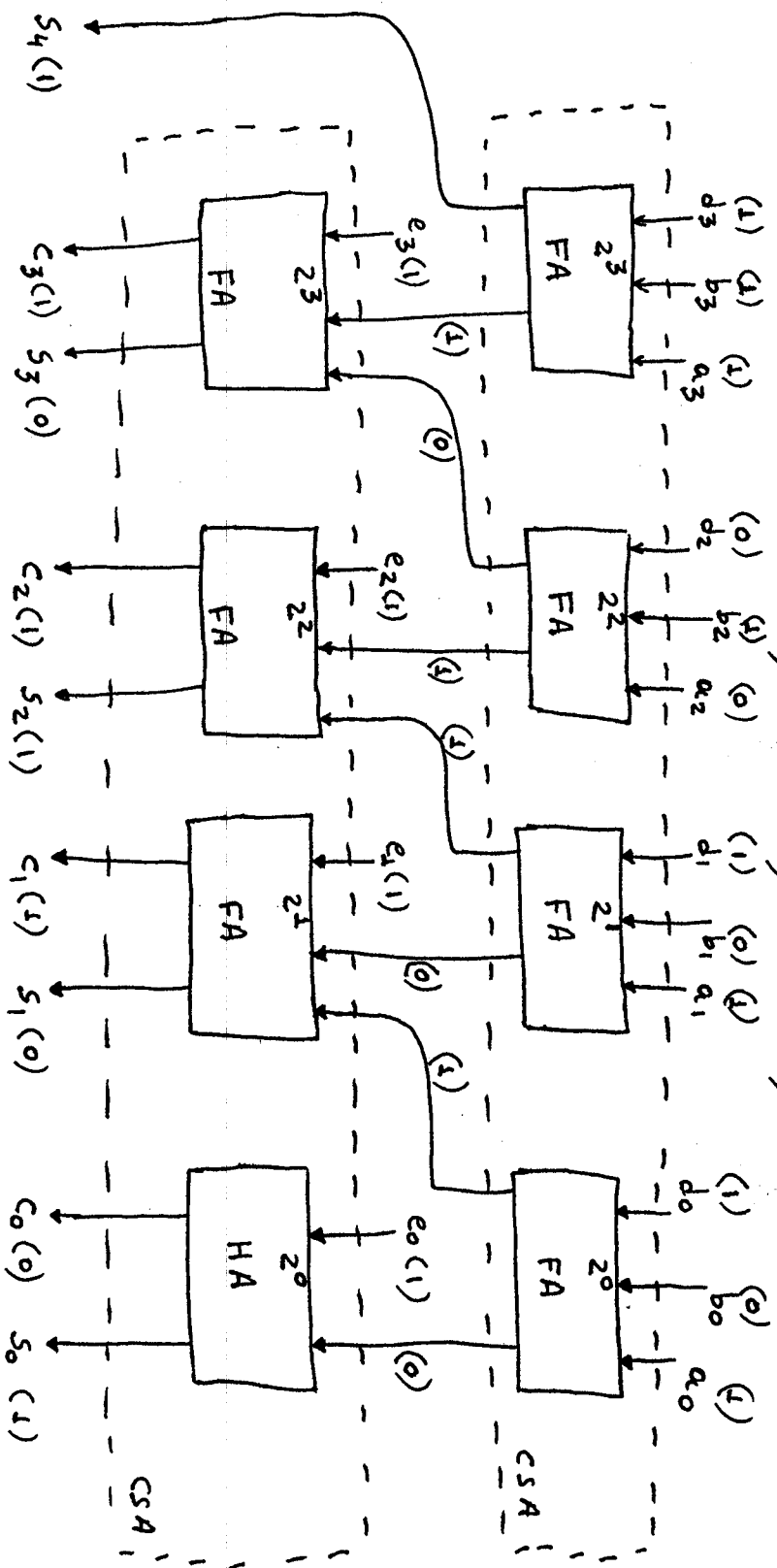Using a CSA tree and a CPA add four 4-bit numbers  $A = (a_3 a_2 a_1 a_0)_2$ ;  $B = (b_3 b_2 b_1 b_0)_2$ ;  $D = (d_3 d_2 d_1 d_0)_2$ ;  $E = (e_3 e_2 e_1 e_0)_2$ . On your design show the numerical example with  $A = 1011$ ;  $B = 1100$ ;  $D = 1011$ ;  $E = 1111$ . (Show detailed design).



 
\* \* Numbers in parentheses reflect the numerical example.





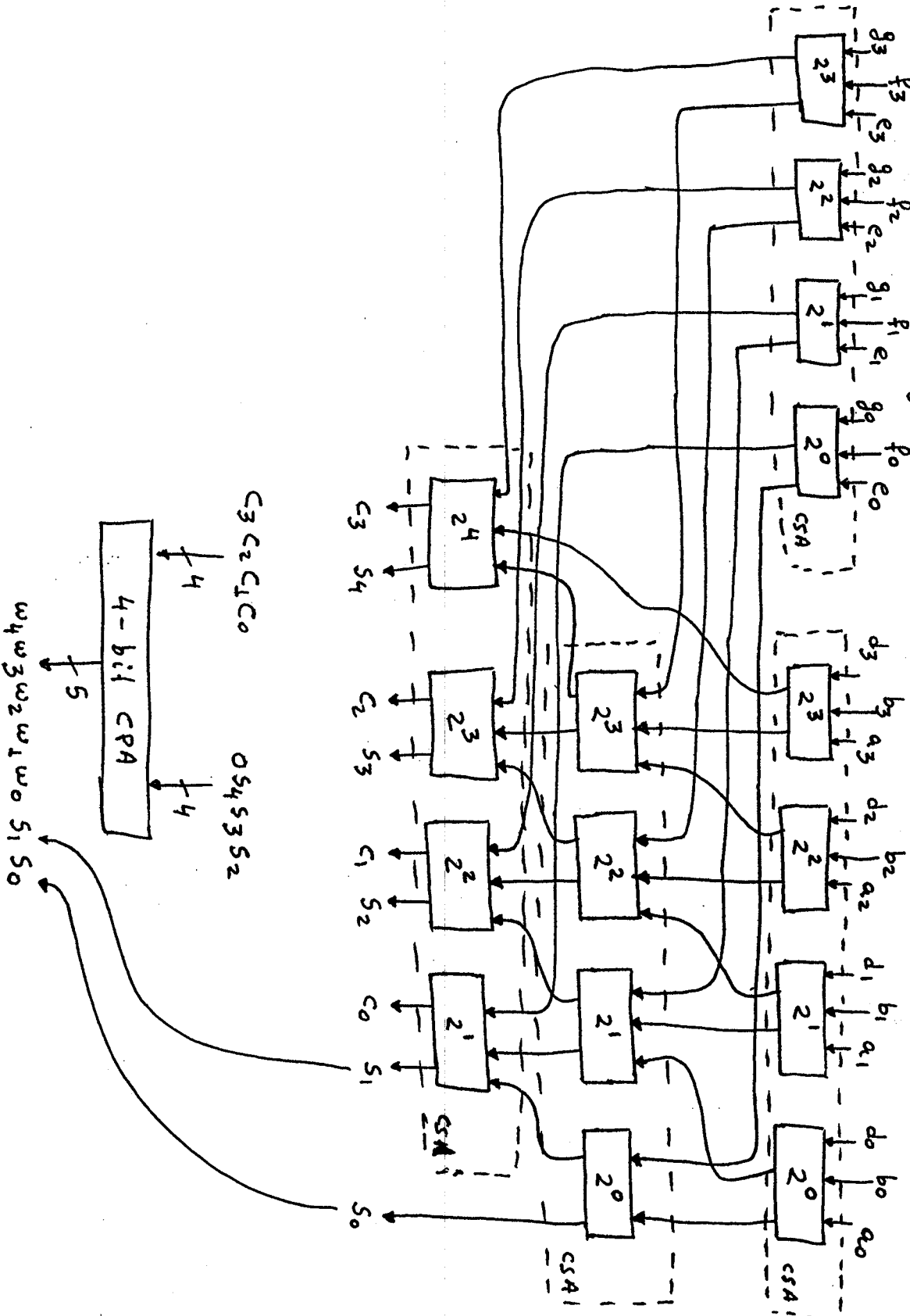(2)

Using a CSA tree and a CPA add six 4-bit numbers  $A = (a_3 a_2 a_1 a_0)_2$ ;  
 $B = (b_3 b_2 b_1 b_0)_2$ ;  $D = (d_3 d_2 d_1 d_0)_2$ ;  $E = (e_3 e_2 e_1 e_0)_2$ ;  $F = (f_3 f_2 f_1 f_0)_2$ ;  $G = (g_3 g_2 g_1 g_0)_2$ .  
 Show detailed design for your CSA tree.



(3) c

Using a CSA tree and a CPA add nine 4-bit numbers A; B; D; E; F; G; H; I; J. Show detailed design for your CSA tree.

