

## Very Simple (VS) MIPS Implementation


Goal is to share as much hardware as possible.

Goal is to be simple.

Good for illustrating datapath and control hardware.

With relatively minor changes VS MIPS can be made into a practical design.

## Very Simple Implementation

 


*Datapath* components in black.

*Control* signals in blue.

Control signals set by control logic.


**Warning:** This implementation impractically slow.

## Control for add Instruction

 


State	SubSt	xma	omem	eir	xalu1	xalu2	oalu	xrwr	xrws	enpc	epc	Next
IF		pc	rd32	1								ID
ID	add				rsv	rtv	add	rd	alu			NI
NI					npc	4	add			1	1	IF

## Control for sub Instruction

 


	State	SubSt	xma	omem	eir	xalu1	xalu2	oalu	xrwr	xrws	enpc	epc	Next
IF			pc	rd32	1								ID
ID	sub					rsv	rtv	sub	rd	alu			NI
NI						npc	4	add			1	1	IF

## Control for addi Instruction

 

	State	SubSt	xma	omem	eir	xalu1	xalu2	oalu	xrwr	xrws	enpc	epc	Next
IF			pc	rd32	1								ID
ID	addi					rsv	simm	add	rt	alu			NI
NI						npc	4	add			1	1	IF

## Control for `lw` Instruction

 


State	SubSt	xma	omem	eir	xalu1	xalu2	oalu	xrwr	xrws	enpc	epc	Next
IF		pc	rd32	1								ID
ID	lw	alu	rd32		rsv	simm	add	rt	md			NI
NI					npc	4	add			1	1	IF

The `lw` instruction reveals a weakness in this design...

... `ID` takes much longer for `lw` than for `add` and other instructions...

... forcing the clock frequency to be slower than it has to be. (Nevermind for now.)


## Control for 1b Instruction

 

State	SubSt	xma	omem	eir	xalu1	xalu2	oalu	xrwr	xrws	enpc	epc	Next
IF		pc	rd32	1								ID
ID	1b	alu	rd8s		rsv	simm	add	rt	md			NI
NI					npc	4	add			1	1	IF


The work of sign-extending or padding the loaded value is done by the memory port.

## Control for sb Instruction

 

State	SubSt	xma	omem	eir	xalu1	xalu2	oalu	xrwr	xrws	enpc	epc	Next
IF		pc	rd32	1								ID
ID	sb	alu	wr8s		rsv	simm	add					NI
NI					npc	4	add			1	1	IF

## Control for beq Instruction

 

	State	SubSt	xma	omem	eir	xalu1	xalu2	oalu	xrwr	xrws	enpc	epc	Next
IF			pc	rd32	1								ID
ID	beq					rsv	rtv	seq					NI or BT
BT	beq					npc	bimm	add			1	1	IF
NI						npc	4	add			1	1	IF

## Control Logic Design

Lets collect the control signals we've decided so far:

State	SubSt	xma	omem	eir	xalu1	xalu2	oalu	xrwr	xrws	enpc	epc	Next
IF		pc	rd32	1								ID
BT					npc	bimm	add			1	1	IF
NI					npc	4	add			1	1	IF
ID	add				rsv	rtv	add	rd	alu			NI
ID	sub				rsv	rtv	sub	rd	alu			NI
ID	addi				rsv	simm	add	rt	alu			NI
ID	lw	alu	rd32		rsv	simm	add	rt	md			NI
ID	lb	alu	rd8s		rsv	simm	add	rt	md			NI
ID	sb	alu	wr8s		rsv	simm	add					NI
ID	beq				rsv	rtv	seq					NI

Notice that **IF**, **BT**, and **NI** states were all identical ...

... but **ID** varies depending on the instruction.

## Control Logic Design

### The State Register

We'll need a register to hold the current state.

Since there are four states we can use a two-bit register.

Possible state encoding:  $\text{IF} = 0$ ,  $\text{ID} = 1$ , ... .

In diagrams we will use names, such as  $\text{IF}$ , instead of encoded values, such as  $0$ .


### Next-State Logic

There will be combinational logic to determine the next state.

Next state is computed in terms of...

... *current state, opcode*, and for branches the *ALU output*.

# Control Logic for State

 

Note: **Magic Cloud** checks for a taken branch.

Logic for the `enpc` signal.

State	SubSt	xma	omem	eir	xalu1	xalu2	oalu	xrwr	xrws	enpc	epc	Next
IF		pc	rd32	1								ID
BT					npc	bimm	add			1	1	IF
NI					npc	4	add			1	1	IF
ID	add				rsv	rtv	add	rd	alu			NI
ID	sub				rsv	rtv	sub	rd	alu			NI
ID	addi				rsv	simm	add	rt	alu			NI
ID	lw	alu	rd32		rsv	simm	add	rt	md			NI
ID	lb	alu	rd8s		rsv	simm	add	rt	md			NI
ID	sb	alu	wr8s		rsv	simm	add					NI
ID	beq				rsv	rtv	seq					NI

Notice that `enpc` is **1** in **BT** and **NI** and **0** in the other states.

So we need logic with an output of 1 for those two states.

An easy way to do that is a mux, we'll rely on the synthesis program to streamline the logic.

## Some Control Logic

