

Name \_\_\_\_\_

Digital Logic I  
EE 2720-2  
Midterm Examination 10<sub>2</sub>  
9 November 2011, 14:40–15:30 CST

Exam Rules

Use only a pencil or pen. No calculators of any kind are allowed. Texting is out of the question.

Problem 1 \_\_\_\_\_ (22 pts)

Problem 2 \_\_\_\_\_ (22 pts)

Problem 3 \_\_\_\_\_ (22 pts)

Problem 4 \_\_\_\_\_ (12 pts)

Problem 5 \_\_\_\_\_ (12 pts)

Problem 6 \_\_\_\_\_ (10 pts)

Alias \_\_\_\_\_

Exam Total \_\_\_\_\_ (100 pts)

*Good Luck!*

Problem 1: (22 pts) The problems below are based on the following Boolean function:

$$(a + bc + b'c')(abc')'$$

(a) Draw a logic diagram (using AND, OR, and NOT gates) corresponding to the Boolean function. (Do **not** simplify the expression.)

Logic diagram.

(b) Write the Boolean function in minterm canonical form. (Show a Boolean expression, not just a list of minterm numbers.) *Hint: For most people directly constructing a truth table would be easier than algebraic manipulation.*

Expression in minterm canonical form.

(c) Write the Boolean function in maxterm canonical form.

Expression in maxterm canonical form.

(d) Draw a Karnaugh map for the expression. (Just draw the Karnaugh map, don't use it to simplify the expression.)

Karnaugh map, including variables and row and column numbers.

Problem 2: (22 pts) Consider the Karnaugh map below.

$xy \backslash$	$zw$		
		1	
		1	1
		1	1
		1	1

(a) Write in the row and column numbers.

Row and column numbers.

(b) List all of the prime implicants both on the Karnaugh map above, and as a list below.

Prime implicants circled on Karnaugh map.

List prime implicant expressions below.

(c) In the list of prime implicants above, write an “E” next to each *essential* prime implicant.

Write an “E” next to essential prime implicants.

(d) Provide an example of an implicant that’s neither a prime implicant, nor a minterm. Circle this implicant and show the corresponding Boolean expression.

Circle implicant that’s not just a minterm but not prime either.

Show an expression for the implicant.

(e) Based on the Karnaugh map show a minimum-cost expression for this logic function.

Minimum-cost expression.

Problem 3: (22 pts) Consider the Boolean function below:

$$ab' + b'c + a'bc'$$

(a) Use a  $3 \times 8$  decoder plus whatever logic gates are needed to implement this function.

Implement using  $3 \times 8$  decoder and gates.

(b) Use an 8-input multiplexer to implement this function.

Implement using an 8-input multiplexer.

(c) Use a multiplexer and additional logic, including possibly exclusive-or gates, to implement this function by performing a Shannon expansion with respect to  $a$  (use  $a$  as the multiplexer control input). *Hint: it might be easier to eyeball a truth table than to do this by algebraic manipulation.*

Implement using a multiplexer based on  $a$ .

Problem 4: (12 pts) Show how to implement the 8-input multiplexers described below. In each case the three select input bits should be labeled  $s_2$ ,  $s_1$ ,  $s_0$ , with  $s_0$  being least significant. Label the data inputs 0 to 7.

(a) Implement an 8-input multiplexer using two 4-input multiplexers and a 2-input multiplexer.

Eight-input mux using two 4-input multiplexers.

(b) Implement an 8-input multiplexer using four 2-input multiplexers and one 4-input multiplexer.

Eight-input mux using four 2-input multiplexers and a 4-input mux.

Problem 5: (12 pts) Implement the devices as described below.

(a) Show the logic gates needed to implement a  $2 \times 4$  decoder, include an enable input.

Logic diagram for a  $2 \times 4$  decoder, just use gates.

Include logic for enable input.

(b) Show how to implement an 8-input multiplexer using a decoder and logic gates.

Logic diagram for an 8-input multiplexer using gates and a decoder.

Problem 6: (10 pts) Answer each question below.

(a) Consider five seats, numbered 0 to 4, arranged in a circle and described by Boolean variables  $i_0$  to  $i_4$ . Boolean variable  $i_0$  is true if seat 0 is occupied and  $i_0$  is false if the seat is not occupied (no one is sitting in the seat), likewise for  $i_1$ ,  $i_2$ ,  $i_3$ , and  $i_4$ .

Write a Boolean expression that's true if at least two people are sitting next to each other and at least one seat is not occupied. (Note: Just write one Boolean expression.) *Hint: This can easily be solved without a truth table.*

Boolean expression.

(b) The statement below is not true. Explain why and correct it.

*“By implementing a sum-of-products expression using only NAND gates (in place of AND and OR gates) we expose additional opportunities for simplification.”*

Statement is incorrect because ...

The real reason for using NAND gates is ...