

FE Review Course Outline

1. Electrostatics
 - a. Charge
 - b. Voltage
 - c. Current
 - d. Resistance
2. Circuit Analysis Basics
 - a. Resistor simplification
 - i. Parallel
 - ii. Series
 - b. Source Equivalents
 - i. Thevenin
 - ii. Norton
 - c. Node Analysis
 - d. Loop Analysis
3. Transient Circuits
 - a. RC Circuits
 - b. RL Circuits
4. AC Circuits
 - i. RMS
 - ii. Phasor Transforms
 - iii. AC impedance
 - iv. AC Steady State analysis
5. Power
 - a. DC Power
 - i. Power supplied
 - ii. Power Absorbed
 - b. AC Power
 - i. Complex power
 - ii. power factor
6. Transformers
 - a. Current and Voltage in an Ideal transformers
 - b. Impedance seen at the input of an ideal transformer
7. Operational Amplifiers (OP-AMPS)
 - a. Ideal OP-AMPS
 - b. solving OP-AMP Circuits
8. Resonant Circuits
 - a. Series Resonance
 - b. Parallel Resonance
 - c. Quality Factor
 - d. Bandwidth

What you need to know:

1. Electrostatics

a. Charge

- i. Units: Coulombs (C), 1 C is defined as the charge of 6.24×10^{16} electrons. The charge of an electron is 1.6×10^{-19} C.
- ii. The force of one charge on another charge: $\vec{F}_{12} = \frac{Q_1 Q_2}{4\pi\epsilon r^2} \vec{a}_{12}$;

Where:

- 1. Q_i = the i point charge
- 2. \vec{F}_{12} = the force on charge 2 due to charge 1
- 3. r = the distance between the two charges
- 4. \vec{a}_{12} = a unit vector directed from 1 to 2
- 5. ϵ = the permittivity of the medium (how capable is the medium in which the charges exist of allowing these forces to exist)


b. Voltage – The potential difference between two points, is the work done per unit charge required to move the charge between two points.

c. Current – Rate of charge passing across a surface:

$$I = i(t) = \frac{dQ}{dt}$$

d. Resistance – Measure of the ability of charge to move from one point to another for a given potential difference (voltage).

$$R = \frac{\rho L}{A}$$

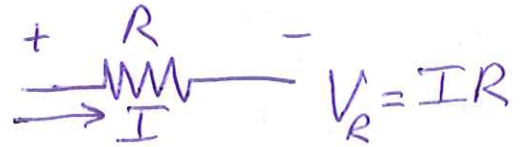


e. Ohm's Law $V=IR$ or $v(t) = i(t)R$


2. Circuit Analysis

a. Resistor Simplification

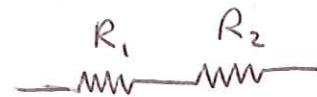i. Two resistors in series: $R_{TOT} = R_1 + R_2$



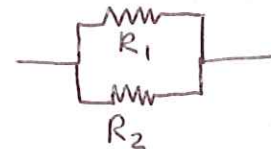ii. Two resistors in parallel: $R_{TOT} = \frac{R_1 R_2}{R_1 + R_2}$



b. Node Analysis – Using Kirchoff's Current Law (KCL): ($\sum I = 0$) at any node.

And: $I_{AB} = \frac{V_A - V_B}{R_{AB}}$

Write a system of equations to solve for unknown node voltages.


c. Loop Analysis – Using Kirchoff's Voltage Law (KVL): ($\sum V = 0$) around any closed path.

Write a system of equations to solve for the unknown currents in each branch.

d. Source equivalents – At any port a linear circuit can be simplified into an ideal source and a resistance

i. Thevenin Equivalent Circuit – circuit is simplified into a series combination of an ideal voltage source and a resistance.

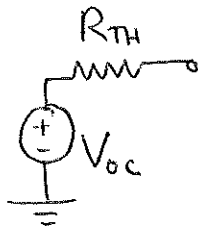
- 1. Find the open circuit voltage (V_{oc}) at the port of interest



2. Find the equivalent resistance (R_{TH}) at the port of interest
Or Find the short circuit current (I_{sc}) at the port of interest

$$R_{TH} = \frac{V_{oc}}{I_{sc}}$$

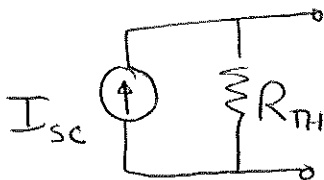- ii. Norton Equivalent Circuit – circuit is simplified into a parallel combination of an ideal current source and a resistance



1. Find the short circuit current (I_{sc}) at the port of interest
2. Find the equivalent resistance (R_{TH}) at the port of interest
Or Find the open circuit voltage (V_{oc}) at the port if interest

$$R_{TH} = \frac{V_{oc}}{I_{sc}}$$

3. Transient Circuits – Circuits that contain capacitors and/or inductors as well as resistors. Voltages or Current sources are switched on or off at $t = 0$. Response is analyzed

- a. Capacitors: $C = \frac{\epsilon A}{d}$; capacitance for a parallel plate capacitor



$$i(t) = C \frac{dv_c(t)}{dt}$$


open ckt to DC

- b. Inductors: $L = \frac{N\phi}{i(t)}$;

L SHORT TO DC

inductance for a coil with N turns and magnetic flux ϕ enclosed in the coil

$$v(t) = L \frac{di_L(t)}{dt}$$

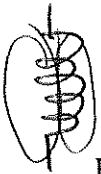

Requires solving first order (C or L only) or second order (L and C) differential eqns.

4. AC Circuits – Steady state analysis of circuits with (periodic) sinusoidal voltage and current sources.

$$\omega = 2\pi f$$

- a. Capacitors replaced with frequency dependent impedance $Z_C = \frac{1}{j\omega C}$
- b. Inductors replaced with frequency dependent impedance $Z_L = j\omega L$
- c. Circuit Analysis is simplified from DIFFEQ's to (complex) algebraic techniques used in resistive circuit analysis

5. Power

- a. DC (Resistive) Circuits

- i. Real power P supplied by a source; $P = VI$
- ii. Power absorbed by a resistor; $P = \frac{V^2}{R} = I^2 R$
- iii. Circuits with multiple sources may have some sources ABSORBING power. (Battery charging)

- b. AC (Complex) Circuits

Complex power; $S = P + jQ$

$$\begin{aligned} \text{Real Power } P &= \left(\frac{1}{2}\right) V_{max} I_{max} \cos\theta \\ &= V_{rms} I_{rms} \cos\theta \end{aligned}$$


$$\text{Complex Power } Q = \left(\frac{1}{2}\right) V_{max} I_{max} \sin\theta$$

θ is the angle measured from V to I.

6. Transformers: Two coils in proximity sharing magnetic flux.

$n = \frac{N_1}{N_2}$; the ratio of the number of turns in the two coils

$$n = \frac{|V_1|}{|V_2|} = \frac{|I_2|}{|I_1|}$$

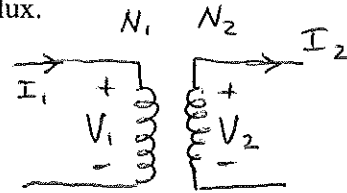


Beware of the Dots!

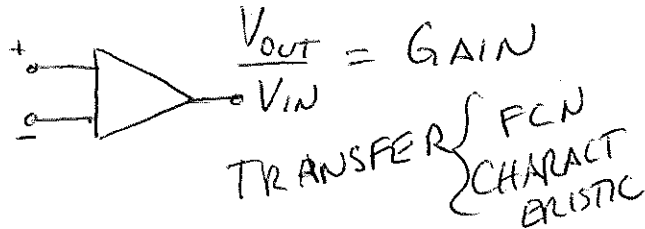7. Operational Amplifiers

For Ideal Op-Amps:

- No current flows into the input terminals
- The input terminals have the same voltage



8. Resonant Circuits – Parallel and Series LC circuits have a bandpass frequency response. This response is located at a center frequency (ω_o) and has a bandwidth (BW)


Resonant Frequency:	$\omega_o = \frac{1}{\sqrt{LC}}$	$\omega_o = \frac{1}{\sqrt{LC}}$
Impedance at Resonance:	$Z = R$	
Series Resonance:	$Q = \frac{\omega_o L}{R} = \frac{1}{\omega_o RC}$	
$Z_L + Z_C = 0$	$BW = \frac{\omega_o}{Q}$	
Parallel Resonance:	$Q = \omega_o RC = \frac{R}{\omega_o L}$	
$\omega = Z_L Z_C$	Quality Factor	

V_L as a fun of ω

V_L @ DC

$$V_L = I Z_L$$

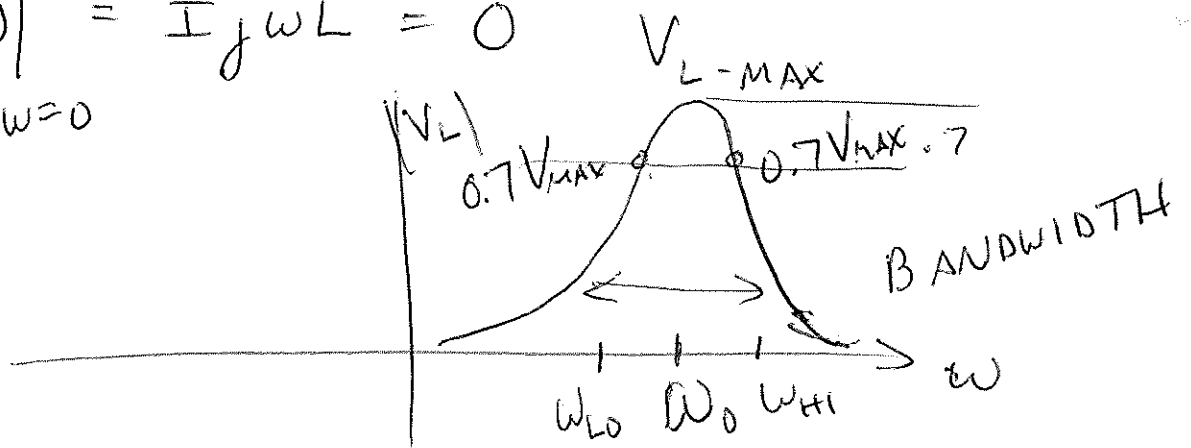
$$V_L(\omega) = I j \omega L = 0 \quad \omega = 0$$



SIMPLIFYING RESISTIVE CIRCUITS.


- RESISTOR SIMPLIFICATION
- THEVENIN EQUIVALENT CIRCUITS
- NORTON EQUIVALENT CIRCUITS.

RESISTORS IN SERIES

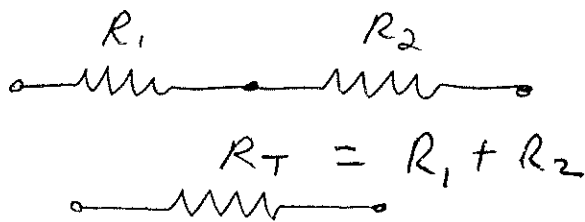

$$R = R_1 + R_2$$



RESISTORS IN PARALLEL

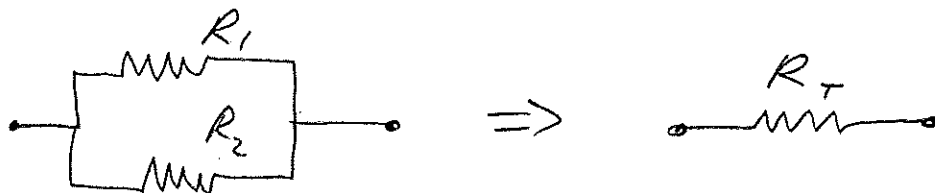

$$R_T = \frac{(R_1)(R_2)}{R_1 + R_2}$$


THEVENIN EQUIVALENT CIRCUIT

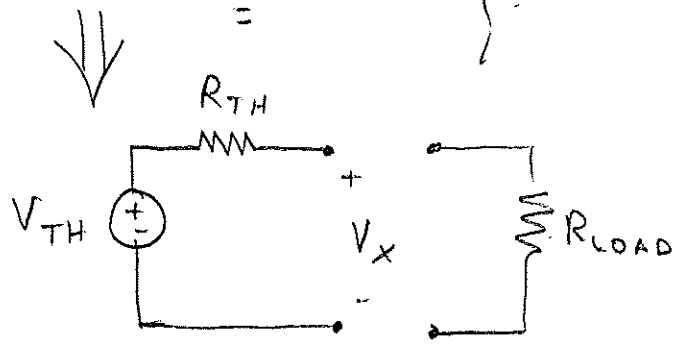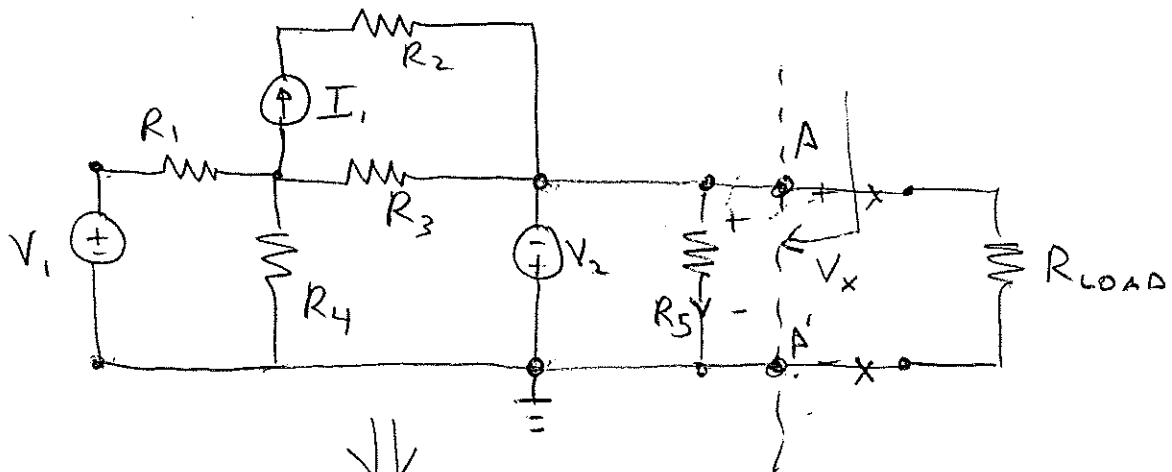ANY RESISTIVE CIRCUIT, NO MATTER HOW COMPLEX, CAN BE REDUCED TO A SERIES VOLTAGE AND RESISTANCE, AT ANY TERMINAL IN THAT CIRCUIT.





OR

NORTON EQUIVALENT.

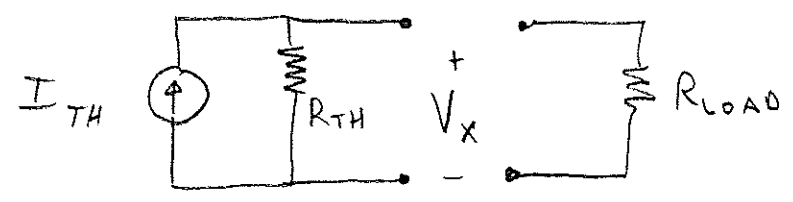
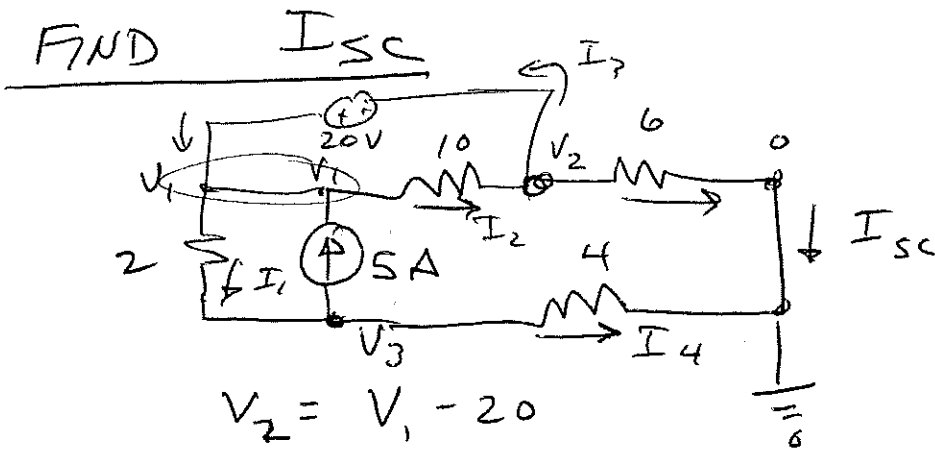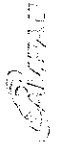
$$V_x = I_{TH} \left(\frac{R_{TH} R_L}{R_{TH} + R_L} \right)$$



$$I_{sc} = \frac{V_2}{6} = \frac{V_1 - 20}{6}$$

KCL $\text{Node } V_1$


$$I_1 + I_2 = I_3 + 5A$$

$$\frac{V_1 - V_3}{2} + \frac{V_1 - V_2}{10} =$$

KCL $\text{Node } V_2$


$$I_2 = I_3 + I_{sc}$$

$$R_{TH} = \frac{V_{oc}}{I_{sc}}$$

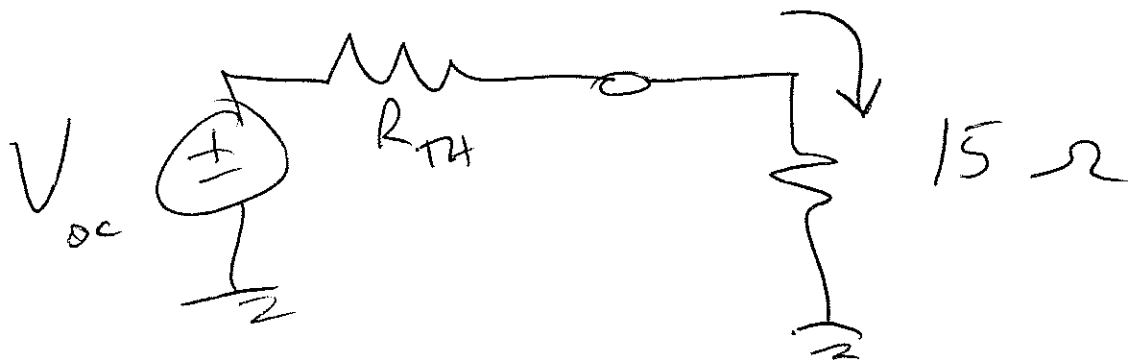


20001 BUSINESS
20002 SHEETS
20003 SHEETS
20004 SHEETS

20005 SHEETS

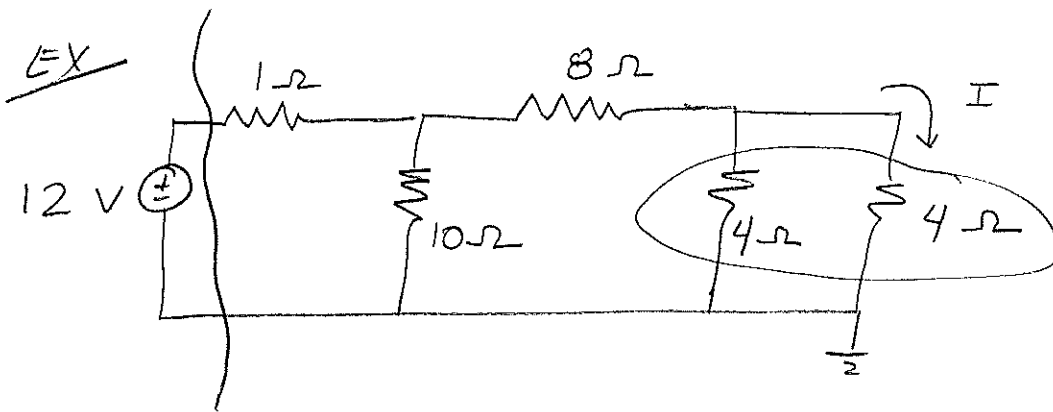




FIND I IN THIS CKT.

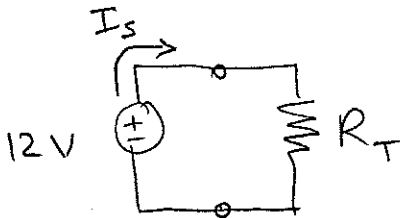CAN USE LOOP EQUATIONS OR RESISTIVE SIMPLIFICATION





CURRENT FROM SOURCE I_s
DELIVERED TO RESISTIVE CIRCUIT.
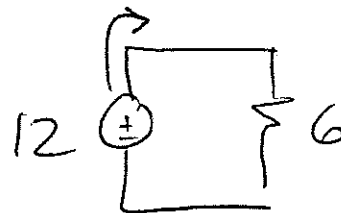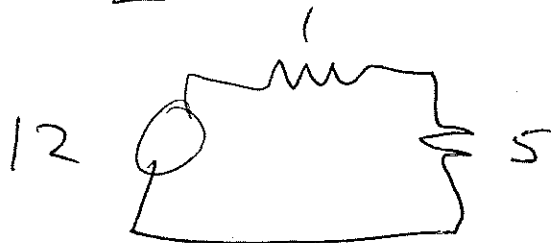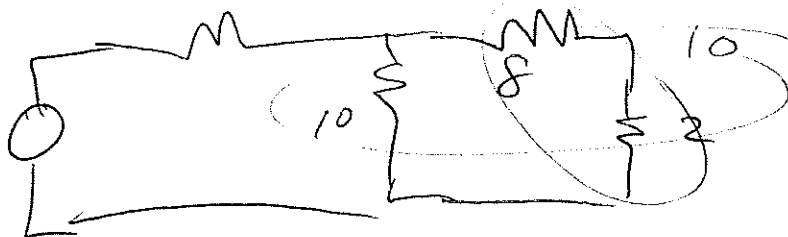
$$4\Omega // 4\Omega = \frac{16}{8} = 2\Omega$$



$$V = IR$$


$$I = 2A$$

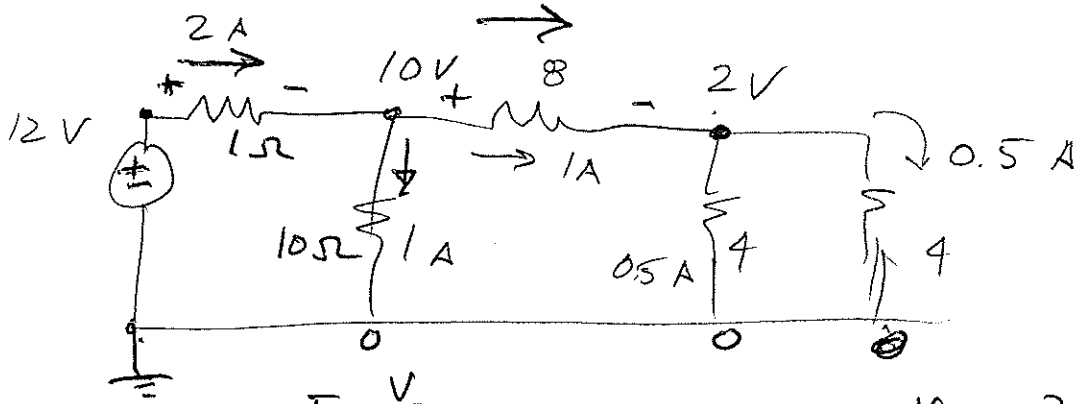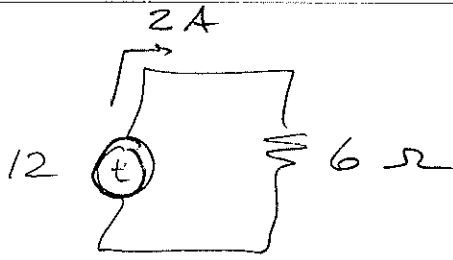

$$I = \frac{V}{R}$$

$$I = \frac{V}{R} = \frac{2}{4} = \frac{1}{2} \text{ A}$$

FIND V_{oc}

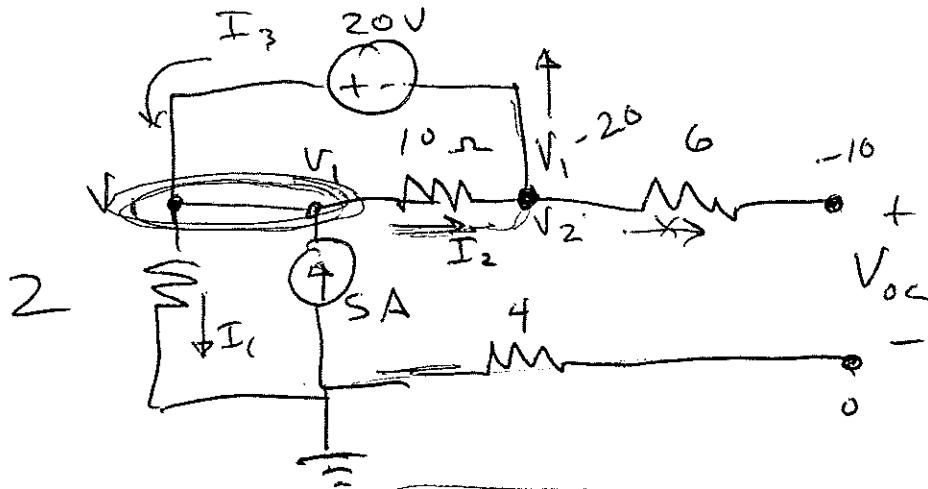

KCL @ V_1

$$\cancel{I_2 + I_1 = 5 + I_3}$$

$$\frac{V_1 - (V_1 - 20)}{10} + \frac{V_1 - 0}{2} = 5 + I_2$$

$$\frac{V_1}{2} = 5$$



$$V_1 = 10$$

$$V_2 = -10$$

$$V_{oc} = 10$$




FINDING T.E.C

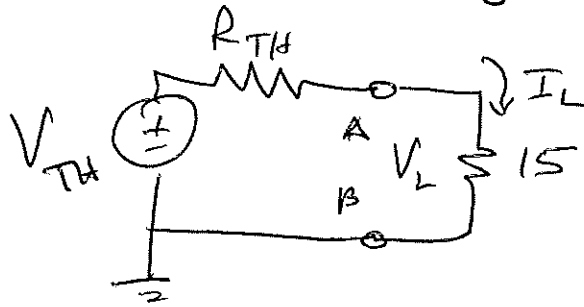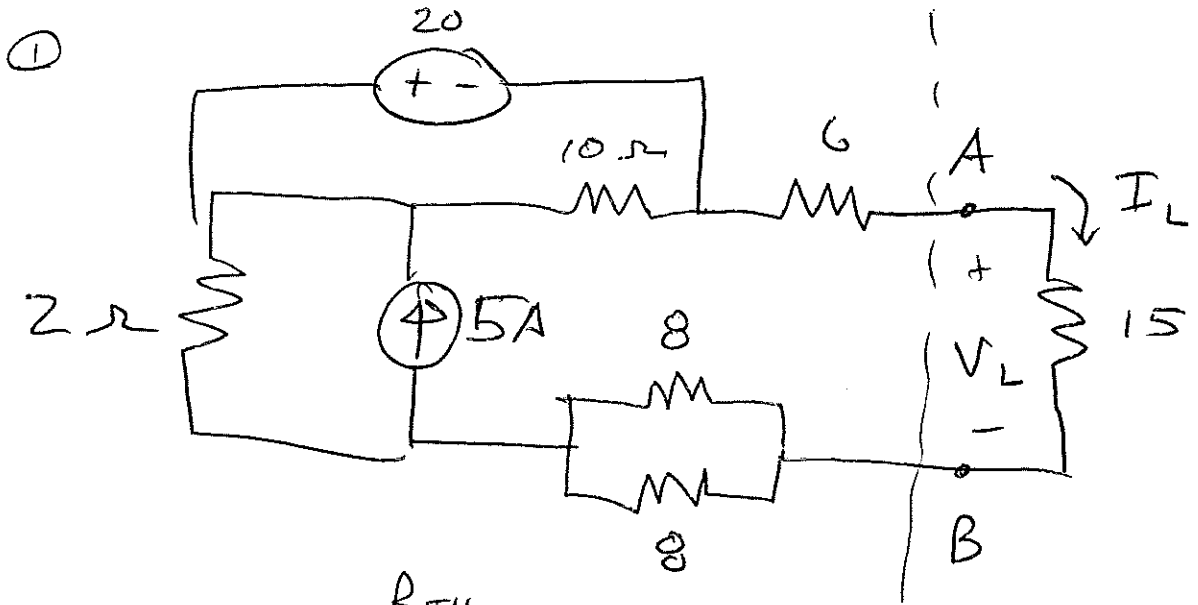

$$I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

$$V_L = 15 I_L$$

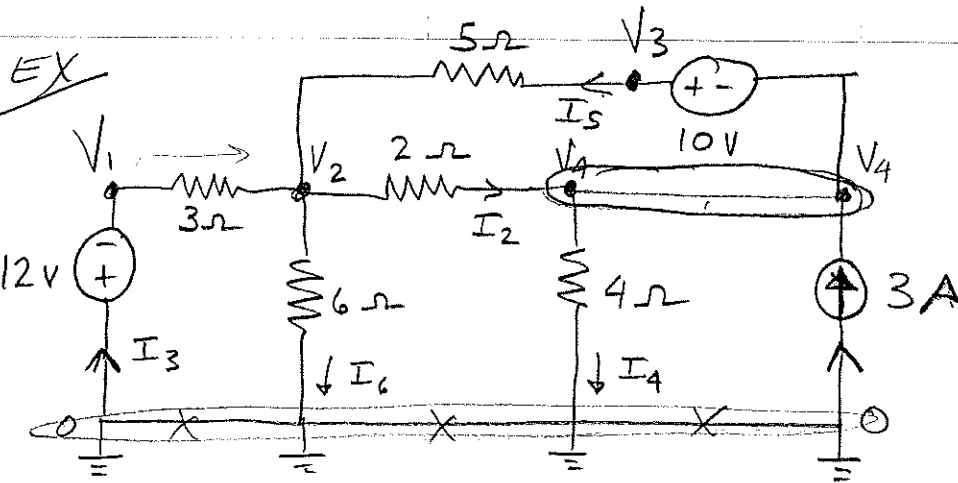

FIND ALL BRANCH CURRENTS AND NODE VOLTAGES.

STEP 1) LABEL ALL BRANCHES AND NODES

BRANCH CURRENTS I_3, I_6, I_4, I_5, I_2

FIND VOLTAGES AT ALL NODES
THEN USE OHM'S LAW

$$I_2 = \frac{V_2 - V_4}{2\Omega}$$

$$I_6 = \frac{V_2 - 0}{6}$$

$$V_1 = -12\text{ V}$$

$$V_3 = 10 + V_4$$

KCL @ NODE 2

$$I_3 + I_5 = I_6 + I_2$$

$$\sum I = 0$$

$$I_3 = \frac{V_1 - V_2}{3}$$

$$I_5 = \frac{V_3 - V_2}{5}$$

$$\frac{V_1 - V_2}{3} + \frac{V_3 - V_2}{5} = \frac{V_2}{6} + \frac{V_2 - V_4}{2}$$


KCL @ NODE 4

$$I_2 + 3 = I_4 + I_5$$

$$I_4 = \frac{V_4 - 0}{4}$$


4 EQN. 4 UNKNOWN CAN BE SOLVED SIMULTANEOUSLY

FIRST ORDER TRANSIENT CIRCUITS

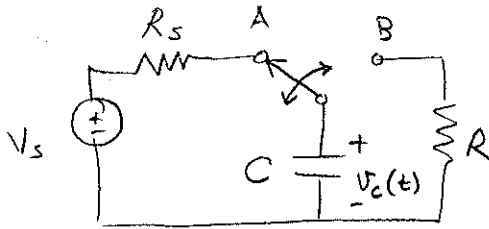

- VOLTAGE DOES NOT CHANGE INSTANTANEOUSLY ACROSS CAP
- CAP IS O.C. TO DC CURRENT AS $t \rightarrow \infty$


POSITION A (FOR A LONG TIME)

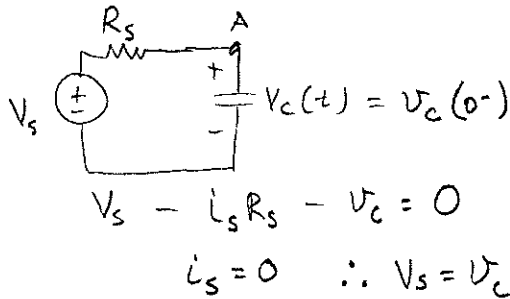

$$V_s - I_s R_s - V_c = 0$$

$$I_s = 0 \quad \therefore V_s = V_c$$

POSITION B

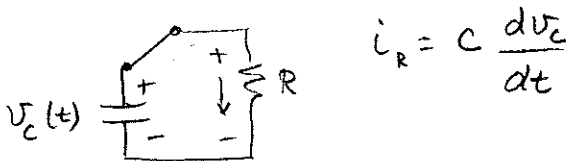

$$i_R = C \frac{dV_c}{dt}$$

$$V_c + C \frac{dV_c}{dt} R = 0$$

$$V_c + RC \frac{dV_c}{dt} = 0$$


$$\frac{dV_c(t)}{dt} + \frac{1}{RC} V_c(t) = 0$$

$$V_c(t) = k_2 e^{-\frac{t}{RC}}$$


$$V_c(0^+) = V_c(0^-) = k_2 e^{-\frac{0}{RC}} = k_2$$

$$k_2 = V_s$$


$$V_c(t) = V_s e^{-\frac{t}{RC}}$$

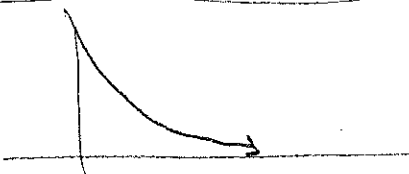

POSITION B

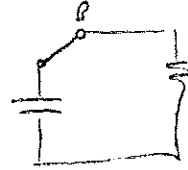

$$i_c = 0 \quad V_c(0) = 0$$

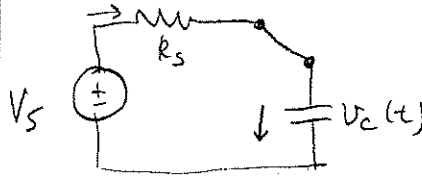

$$i_R = \frac{V_s - V_c(t)}{R} = C \frac{dV_c}{dt} = i_c$$

$$\frac{dV_c(t)}{dt} + \frac{1}{RC} V_c(t) = \frac{V_s}{RC}$$

$$V_c(t) = k_1 + k_2 e^{-\frac{t}{RC}}$$

$$k_2 \left(-\frac{1}{RC}\right) e^{-\frac{t}{RC}} + \frac{k_1}{RC} + \frac{k_2}{RC} e^{-\frac{t}{RC}} = \frac{V_s}{RC}$$

$$\frac{k_1}{RC} = \frac{V_s}{RC} \quad \boxed{V_s = k_1}$$

$$-\frac{k_2}{RC} e^{-\frac{t}{RC}} = -\frac{k_2}{RC} e^{-\frac{t}{RC}}$$

$$\boxed{\tau = RC}$$

$$V_c(t) = V_s + k_2 e^{-\frac{t}{RC}}$$

$$V_c(0^-) = 0 = V_s + k_2$$

$$\boxed{k_2 = -V_s}$$

$$V_c(t) = V_s - V_s e^{-\frac{t}{RC}}$$

$$\frac{dx(t)}{dt} + ax(t) = f(t)$$

IF $x_p(t)$ IS A SOLN, AND $x_c(t)$ IS A SOLN

TO THE HOMOGENEOUS EQN:

$$\frac{dx(t)}{dt} + ax(t) = 0$$

THEN

$$x(t) = x_p(t) + x_c(t)$$

LET $f(t) = A$ constant

$$\frac{dx_p(t)}{dt} + ax_p(t) = A$$

$$x_p(t) = K_1$$

$$\frac{dx_c(t)}{dt} + ax_c(t) = 0$$

$$x_c(t) = K_2 e^{-at}$$

$$x_p(t) = K_1 = \frac{A}{a}$$

$$x(t) = K_1 + K_2 e^{-at}$$


$$v(t) = k_1 + k_2 e^{-\left(\frac{1}{RC}\right)t}$$

$$v(0^-) = v(0^+) = \boxed{V_s = k_1 + k_2}$$

$$v(t) = k_2 e^{-\left(\frac{1}{RC}\right)t}$$

$$\frac{dv_c(t)}{dt} + \frac{v_c(t)}{RC} = 0$$

$$v_c(t) = k_2 e^{-\frac{t}{RC}}$$

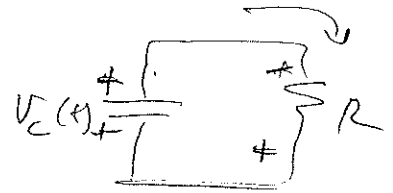

$$v_c(t) + i_R R = 0$$

$$i_R = C \frac{dv_c}{dt}$$

$$v_c + RC \frac{dv_c}{dt} = 0$$

$$\frac{dv_c}{dt} + \frac{1}{RC} v_c = 0$$

$$v_c = k_2 e^{-\frac{1}{RC}t}$$

$$\frac{k_2}{RC} e^{-\frac{1}{RC}t} - \frac{k_2}{RC} e^{-\frac{1}{RC}t} = 0$$

USING LAPLACE TRANSFORMS

$$V_C(t) + CR \frac{dV_C}{dt} = 0$$

$$V(0^-) = V_s$$

$$V(s) + CR(sV(s) - V(0^-)) = 0$$

$$V(s)(1 + CRs) - CRV(0^-) = 0$$

$$V(s) = \frac{CR V_s}{1 + CRs} = \frac{V_s}{\frac{1}{RC} + s}$$

$$V(t) = V_s e^{-\frac{1}{RC}t}$$

$$\frac{1}{s+a} \leftrightarrow e^{-at}$$

$$\frac{dV_C(t)}{dt} + \frac{1}{RC} V_C(t) = \frac{V_s}{RC}$$

$$sV(s) + \frac{V(s)}{RC} = \frac{V_s}{sRC}$$

$$V(s) \left(s + \frac{1}{RC} \right) = \frac{V_s}{RC} = \frac{k_1}{s} + \frac{k_2}{s + \frac{1}{RC}}$$

$$\frac{V_s}{RC} \bigg|_{s=0} = k_1 = V_s$$





$$\frac{V_s}{RC} \bigg|_{s=-\frac{1}{RC}} = k_2 = -V_s$$

$$V(t) = V_s - V_s e^{-\frac{t}{RC}}$$

AC SS CRT ANALYSIS INIT. COND = 0

AC CKT ANALYSIS

$$v(t) = A \cos(\omega t + \theta)$$

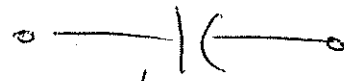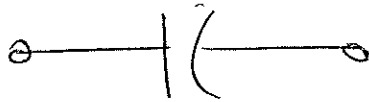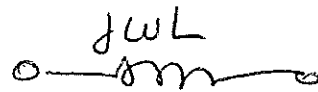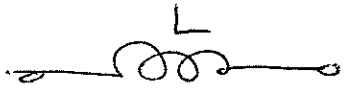

$$\frac{1}{j\omega C} = \frac{-j}{\omega C}$$

AC CIRCUIT ANALYSIS - STEADY STATE ANALYSIS


CONVERT TO PHASOR DOMAIN

$$v(t) = A \cos(\omega t + \theta) = \operatorname{Re} [A e^{j(\omega t + \theta)}]$$

ALSO WRITTEN AS A PHASOR $\mathbf{V} = A \angle \theta$

CONVERT COMPONENTS

<u>TIME DOMAIN</u>	<u>PHASOR</u>
R	R
L	$j\omega L$
C	$\frac{1}{j\omega C}$

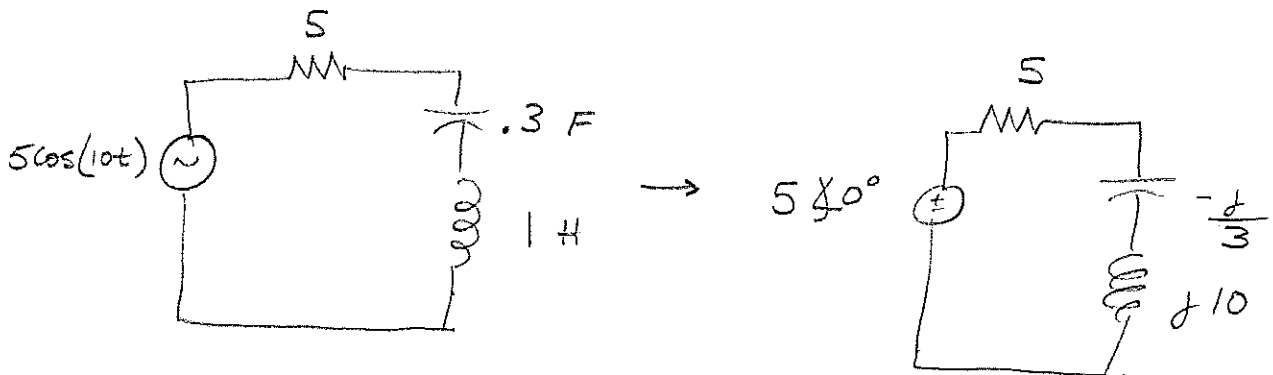

$$I = \frac{5 \angle 0^\circ}{5 - \frac{j}{3} + j10}$$

$$I = \frac{5 \angle 0^\circ}{5 + j(10 - \frac{1}{3})}$$

$$I = \frac{5 \angle 0^\circ}{5 + j9.67} = \frac{5 \angle 0^\circ}{10.89 \angle 62.6^\circ} = 0.459 \angle -62.6^\circ$$

$$i(t) = 0.459 \cos(10t - 62.6^\circ)$$

SUMMARY OF COMPLEX NUMBERS

$$x + jy = r e^{j\theta}$$

$$r = \sqrt{x^2 + y^2}$$

$$\theta = \tan^{-1} \frac{y}{x}$$

$$x = r \cos \theta$$

$$y = r \sin \theta$$

$$\frac{1}{e^{j\theta}} = e^{-j\theta}$$

$$\text{or } \frac{1}{5 \angle 30^\circ} = 0.2 \angle -30^\circ$$

AC RMS

RMS \rightarrow DC EQUIVALENT OF
AN AC SIGNAL

$$V_{RMS} = \left[\frac{1}{T} \int_0^T v^2(t) dt \right]^{1/2}$$

FOR SINUSOID

$$V_{RMS} = \frac{V_p}{\sqrt{2}}$$

TIME $v(t) = V_p \sin(\omega t - \theta_v)$

PHASOR $\vec{V} = \frac{V_p}{\sqrt{2}} \angle \theta_v$

8. A.C. Circuits

Whenever a voltage and current change in a circuit, inductance and capacitance must be accounted for. If the voltage is of the form $v = V_{max} \cos(\omega t + \theta)$ it must be converted to the effective or RMS value.

$$V_{RMS} = \left[\frac{1}{\text{period}} \int_0^{\text{period}} v^2 dt \right]^{\frac{1}{2}} \text{ for a sine wave } V_{RMS} = \frac{V_{max} e^{j\theta}}{\sqrt{2}} = \frac{V_{max}}{\sqrt{2}} \angle \theta$$

$$\omega = 2\pi \text{ (frequency in HZ)}$$

$$\omega = \frac{2\pi}{T} \text{ where } T = \text{period in seconds}$$

ω is in radians per second

$$e^{j\theta} = \cos\theta + j\sin\theta$$

where $j = \sqrt{-1}$ and represents the y axis

The essential facts in A.C. circuits are:

R	L	C
$v_R = i_R R$	$v_L = L \frac{di}{dt}$	$v_C = \frac{1}{C} \int i_C dt$
$i_R = \frac{V_R}{R}$	$i_L = \frac{1}{L} \int v_L dt$	$i_C = C \frac{dv_C}{dt}$
	i_L does not change instantaneously	v_C does not change instantaneously

R
 L
 C

When the voltage and currents are converted to RMS values.

$V_R = I_R R$	$V_L = I_L (jX_L)$	$V_C = I_C (-jX_C)$
	$= I_L X_L \angle 90^\circ = I_L X_L e^{j90}$	$= I_C X_C \angle -90^\circ = I_C X_C e^{-j90}$
	where $X_L = \omega L$	$X_C = \frac{1}{\omega C}$
	I_L is at 0°	I_C is at 0°
$I_R = \frac{V_R}{R}$	$I_L = \frac{V_L \angle 0}{jX_L} = \frac{V_L}{X_L} \angle 90$	$I_C = \frac{V_C \angle 0}{-jX_C} = \frac{V_C}{X_C} \angle 90$
Current is in phase with voltage	I_L lags V_L by 90	I_C leads V_C by 90


Impedance in $\Omega =$ Resistance in $\Omega \pm j$ Reactance in ohms

$$Z \angle \theta = R + jx = R + j(X_L - X_C)$$

$$Z \angle \theta = Z \cos\theta + jZ \sin\theta$$

$$\text{so } R = Z \cos\theta \quad X = Z \sin\theta$$

Solve for L, C, I_s , I_R , I_L , I_c

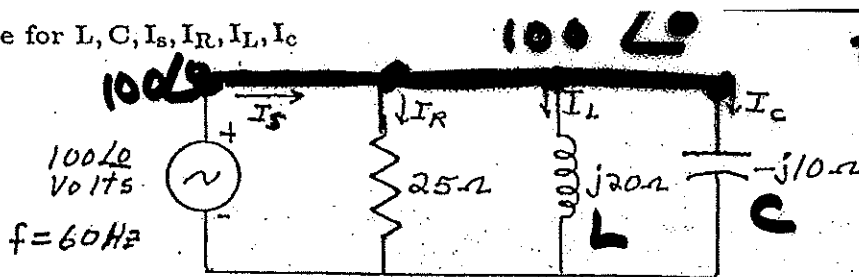

$$Z_L = j\omega L$$

$$\tan^{-1} \frac{20}{0}$$

$$Z_L = j20 = 20 \angle 90$$

$$V_L = I_L Z_L$$

$$V_C = I_C Z_C$$

$$Z_C = -j10$$

$$= 10 \angle -90$$

$$I_R = \frac{100 \angle 0}{25} = 4 \angle 0 = 4 \text{ AMPS}$$

$$i(t) = 4\sqrt{2} \cos \omega t$$

$$I_L = \frac{100 \angle 0}{20 \angle 90} = 5 \angle -90$$

$$i_L(t) = 5\sqrt{2} \cos(\omega t - 90)$$

$$\omega t - 90$$


$$I_C = \frac{100 \angle 0}{10 \angle -90} = 10 \angle 90$$

$$i_C(t) = 10\sqrt{2} \cos(\omega t + 90)$$



DC POWER

$$P = VI$$

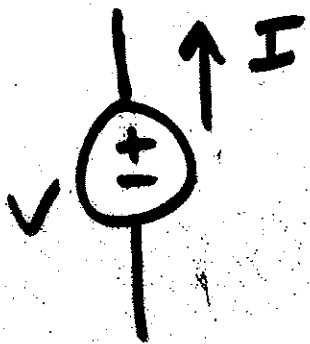
RESISTOR $P_{\text{abs}} = \frac{V^2}{R} = I^2 R$



DELIVERING

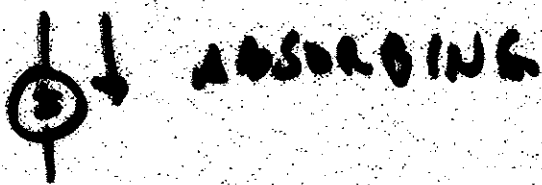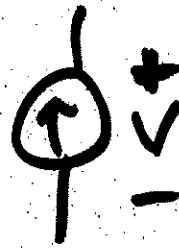

ABSORBING

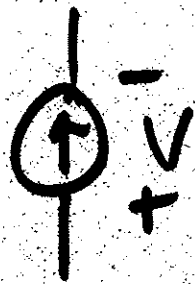

COMPLEX

$$S = P + jQ = VI^*$$

$$S = |S| \angle \theta_s = (|V| \angle \theta_v) (|I| \angle -\theta_i)$$

$$S = |V| |I| \angle \theta_v - \theta_i$$

Power factor = pf

$$\cos(\theta_v - \theta_i)$$

What is the power in the components of the series circuit

What you need to know:

1. In A.C. circuits power is complex so that:

Apparent or complex power in Volt amperes = Power in watts $\pm j$ Reactive power in VARS (volt amperes reactive)

$$S \angle \theta = P + jQ = s \cos \theta + js \sin \theta$$

2. Resistance is the only thing that dissipates power in watts.

3. VARS can come only from reactance.

4. Inductance causes $+j$ VARS

5. Capacitance causes $-j$ VARS

6. The power equations are:

$$\begin{aligned} \text{For } R \quad |P| &= VI \cos \theta \quad P = |I_R|^2 R = \frac{|V_R|^2}{R} \text{ watts} \\ \text{For } X_L \quad |Q_L| &= VI \sin \theta \quad jQ_L = |I_L|^2 (jX_L) = \frac{|V_L|^2}{jX_L} \text{ VARS} \\ \text{For } X_c \quad |Q_c| &= VI \sin \theta \quad -jQ_c = |I_c|^2 (-jX_c) = \frac{|V_c|^2}{(-jX_c)} \text{ VARS} \end{aligned}$$

Note: The * means take the conjugate of the quantity (change the sign of the j term).

$VA = VI^*$ where V is at 0 degrees

Solution:

1. $P = |I_R|^2 R = 14.14^2(10) = 2000$ watts

2. $jQ_L = |I_L|^2 jX_L = 14.14^2(j30) = j6000$ VARS


3. $jQ_L = |I_c|^2 (-jX_c) = 14.14^2(-j40) = -j8000$ VARS

4. The generator is supplying $2000 + j6000 - j8000$ volt amperes = $2000 - j2000 = 2828 \angle -45$ VA

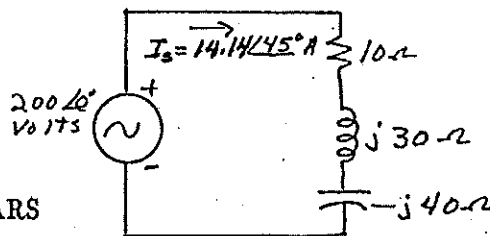5. We get the same result by using

$$V_s I_s^* = (200)(14.14 \angle +45)^* = (200)(14.14 \angle -45) = 2828 \angle -45 \text{ Volt amperes}$$

$$= P - jQ = 2828 \cos 45 - j2828 \sin 45 = 2000 - j2000$$



COMPLEX POWER

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

INSTANTANEOUS POWER $p(t) = v(t) i(t) = I_m V_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$

$$p(t) = \frac{V_m I_m}{2} \left[\underset{\substack{\uparrow \\ \text{TIME IND.}}}{\cos(\theta_v - \theta_i)} + \cos(2\omega t + \theta_v + \theta_i) \right]$$

\uparrow TIME DEP.

AVERAGE POWER

$$P_{AV} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) = \frac{V_m \angle \theta_v}{\sqrt{2}} \frac{I_m \angle \theta_i}{\sqrt{2}}$$


$$pf \equiv \text{power factor} = \cos(\theta_v - \theta_i) = V_{rms} I_{rms} (pf)$$

DIFFERENCE IN PHASE ANGLE OF V and I SINUSOIDAL R.M.S.

$$V_{rms} I_{rms} \equiv \text{APPARENT POWER}$$

$$-1 \leq \cos(\theta_v - \theta_i) \leq 1 \quad \begin{array}{l} 0 < pf < 1 \quad \text{lagging pf} \\ -1 < pf < 0 \quad \text{leading pf} \end{array}$$

EX

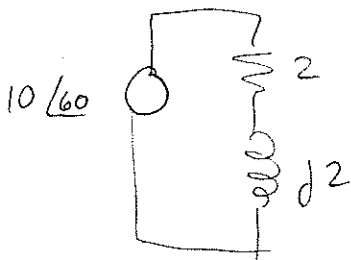

FIND P_{ave} , pf

$$V = 10 \angle 60$$

$$I = \frac{10 \angle 60}{2 + j2} = 3.53 \angle 15^\circ$$


$$P_{ave} = \frac{10 (3.53)}{2} \cos(60 - 15) = 12.48 \text{ Watts}$$

$$pf = \cos(45^\circ) = .707 \text{ lagging (INDUCTIVE LOAD)}$$

Ex INDUSTRIAL LOAD USES 88 kW @ $pf = .707$ lag.
FROM 480 Vrms LINE

a) FIND POWER NEEDED FROM Power Co.

b) if $pf = 0.90$

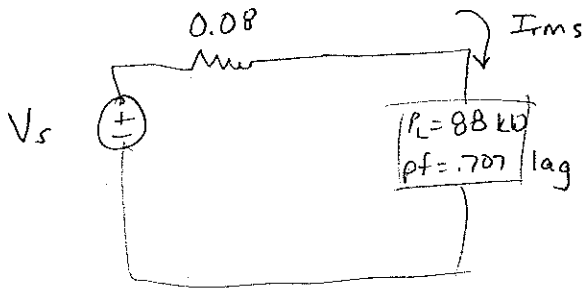

$$P_L = 88 \text{ kW} = I_{rms} V_{rms} (pf)$$

$$88 \text{ kW} = I_{rms} (480) (.707)$$

$$I_{rms} = 259.3 \text{ A}$$

$$P_S = I_{rms}^2 (R) + 88 \text{ kW}$$


$$P_S = 93.38 \text{ kW}$$

b) $pf = 0.90$

$$I_{rms} = 203.7 \text{ A}$$

$$P_S = 91.32 \text{ kW}$$

COMPLEX POWER.

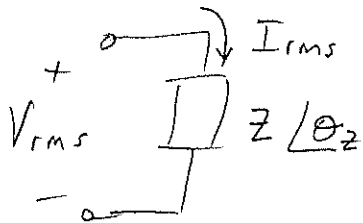

$$S = V_{rms} I_{rms}^* = V_{rms} I_{rms} \angle \theta_v - \theta_i$$

$$= V_{rms} I_{rms} \cos(\theta_v - \theta_i) + j V_{rms} I_{rms} \sin(\theta_v - \theta_i)$$


real power

reactive
quadrature.

$$S = P + jQ$$

$$P = \text{Re}(S) = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

IDEAL TRANSFORMERS

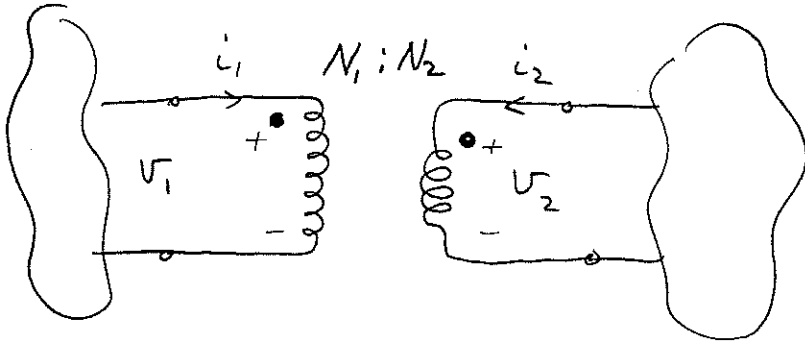


$$\frac{v_1}{v_2} = \frac{N_1}{N_2} \quad \frac{i_1}{i_2} = -\frac{N_2}{N_1}$$

$$v_1 i_1 + v_2 i_2 = 0$$

NO POWER LOST IN AN
IDEAL XFORMER


$$n = \frac{N_2}{N_1} \quad \text{:= turns ratio}$$
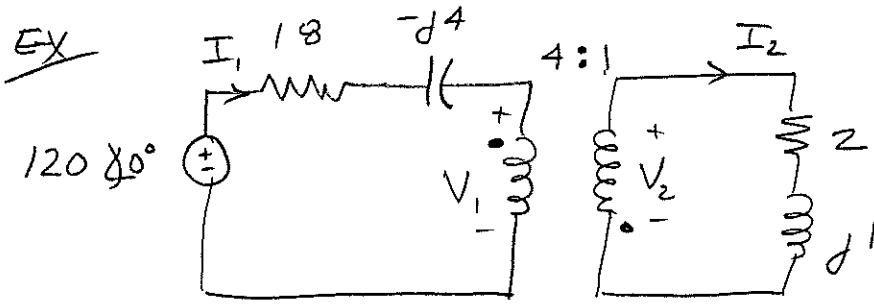
$$V_1 = \frac{V_2}{n} \quad I_1 = n I_2 \quad Z_1 = \frac{Z_L}{n^2}$$



$$V_1 = \frac{-V_2}{n} \quad I_1 = -n I_2 \quad n = \frac{1}{4}$$

$$Z_1 = \frac{Z_L}{n^2} = 4^2 Z_L$$

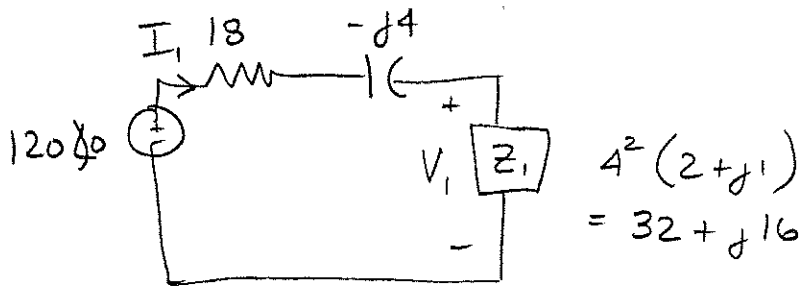



$$I_1 = \frac{120 \angle 0^\circ}{18 - j4 + 32 + j16} = 2.33 \angle -13.5^\circ$$

$$V_1 = I_1 Z_1 = (2.33 \angle -13.5^\circ)(32 + j16) = 83.49 \angle 13.07^\circ$$

$$V_2 = -V_1 n = \frac{1}{4} 83.49 \angle 13.07^\circ = 20.87 \angle 193.07^\circ$$

$$I_2 = -\frac{I_1}{n} = 4 (2.33 \angle 13.5^\circ) = 9.33 \angle 166.50^\circ$$

SERIES
Resonance Ckts

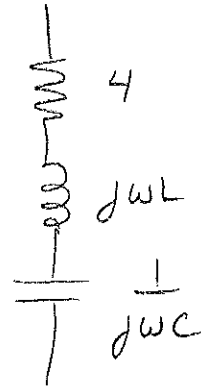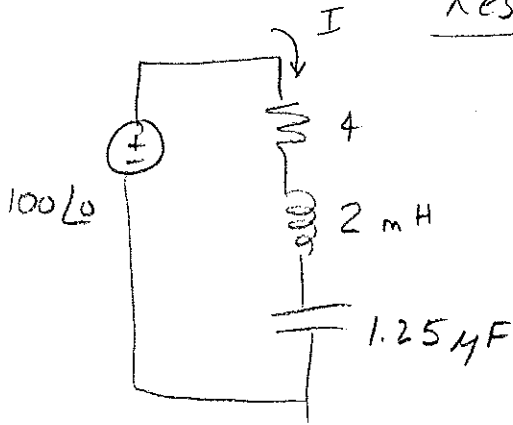

$$Z_T = R + j\omega L - j \frac{1}{\omega C}$$

$$= R + j \left(\omega L - \frac{1}{\omega C} \right)$$

① $\omega L = \frac{1}{\omega C}$

$$\omega_0^2 = \frac{1}{LC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$


$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$\Rightarrow Z_T = R$$

$|Z_T|$ IS MINIMUM

I IS MAXIMUM


$|V_L| = |V_C|$ BUT ARE 180° OUT OF PHASE

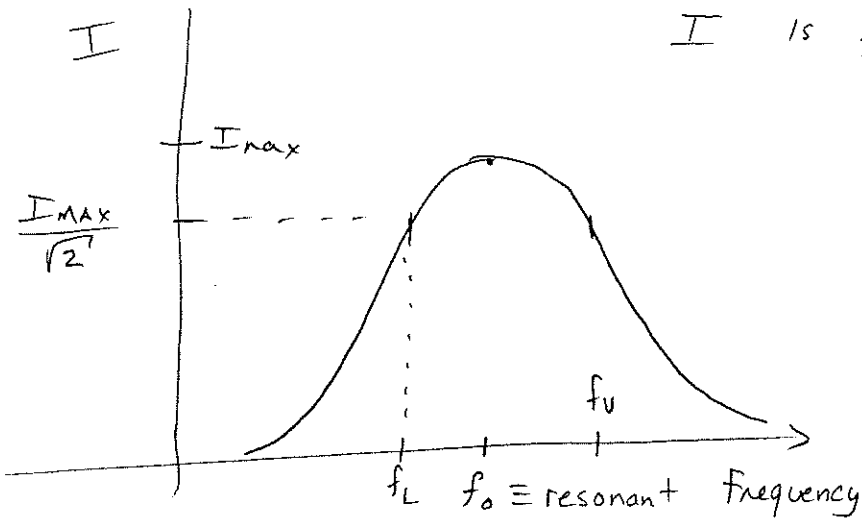

$$Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 C R} \quad \text{Quality factor}$$

$$BW = \frac{\omega_0}{Q} \quad \text{BANDWIDTH} = f_U - f_L$$

EX

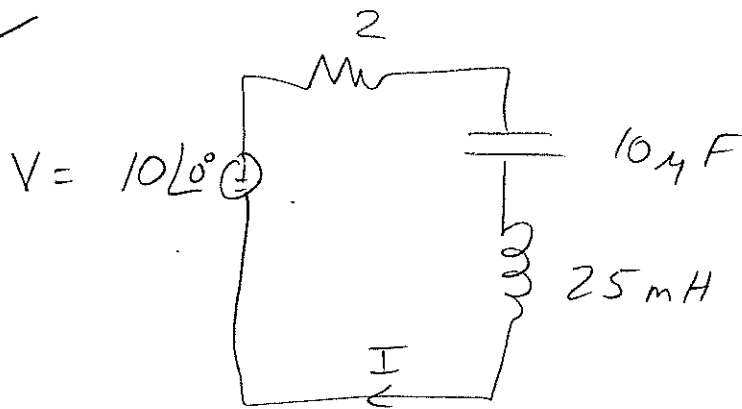

FIND ω_0, Q
 V_C, V_L
 I
@ ω_0

$$Z_T = R + j\omega L - \frac{1}{j\omega C}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 2000$$

$$\text{@ } \omega_0 \quad I = \frac{V}{R} \quad \text{B/c } j\omega L - \frac{1}{j\omega C} = 0$$
$$= 5 \angle 0^\circ$$

$$V_R = I(2) = 10 \angle 0^\circ$$

$$V_L = j\omega L I = 250 \angle 90^\circ$$


$$V_C = \frac{1}{j\omega C} (I) = 250 \angle -90^\circ$$

$$Q = \frac{\omega_0 L}{R} = 25$$

NOTICE: $|V_L| = \omega_0 L |I| = \frac{\omega_0 L}{R} |V_S| = Q |V_S|$

$$|V_C| = \frac{1}{\omega_0 C} |I| = \frac{1}{\omega_0 C R} |V_S| = Q |V_S|$$

EX

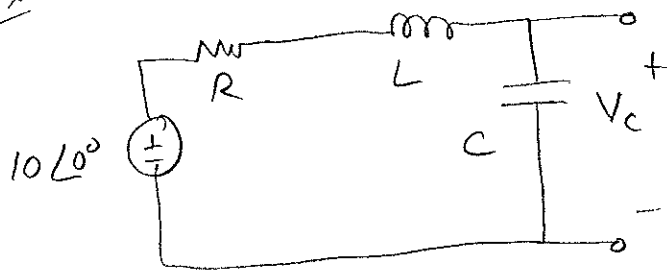

Ckt MUST HAVE:

$$f_0 = 1000 \text{ Hz}$$

$$L = 0.02 \text{ H}$$

$$R = 0.63$$

CHOOSE C FIND V_c @ resonance.
 Q

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$C = 1.27 \mu\text{F}$$

$$\omega_0 = 6275 \text{ rad/s}$$

$$Q = \frac{\omega_0 L}{R} = \frac{2\pi(1000)(0.02 \text{ H})}{0.63} = 200$$

AT Resonance:

$$j\omega L - \frac{1}{j\omega C} = 0$$

$$Z_T = R$$

$$I = \frac{10\angle 0^\circ}{0.63} = 15.87 \angle 0^\circ$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{2\pi f C}$$


$$V_c = I Z_C = 15.87 \angle 0^\circ \left(\frac{1}{2\pi(1000)(1.27 \mu\text{F})} \right) \angle -90^\circ$$

$$= 15.87 \angle 0^\circ (125.3 \angle -90^\circ)$$

$$V_c = \frac{V_s}{R} \left(\frac{1}{2\pi f C} \right) = 2000$$

$$\left(\frac{1}{2\pi f C} \right)$$

Parallel Resonance

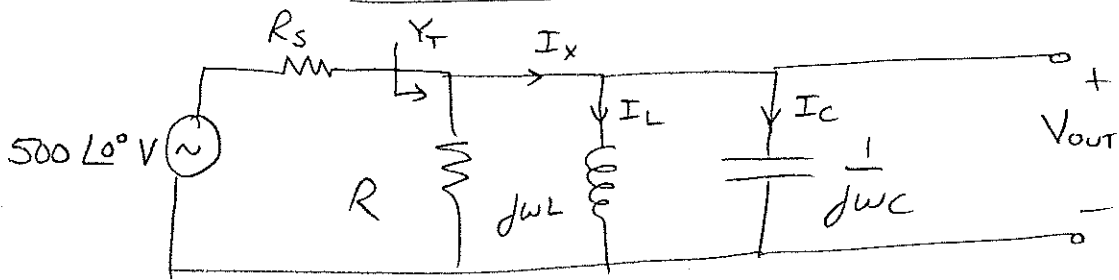

$$Y_T = \frac{1}{R} + \frac{1}{j\omega L} + j\omega C$$

$$Y_T = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)$$

$$@ \omega C = \frac{1}{\omega L}$$


$$\omega_0^2 = \frac{1}{LC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi LC}$$

$\Rightarrow Y_T$ IS MINIMUM
 Z_T IS MAXIMUM
 V_{OUT} IS MAXIMUM


$|I_L| = |I_C|$ BUT ARE 180°
 OUT OF PHASE
 $\therefore I_x = 0$

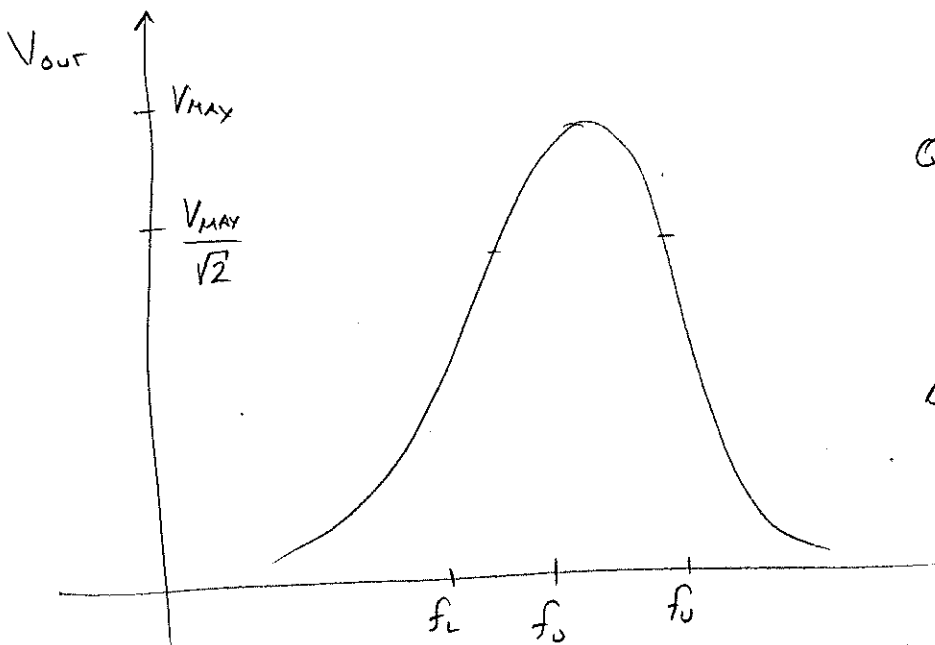

$$Q = \frac{R}{\omega_0 L} = \omega_0 RC$$

$$BW = \frac{\omega_0}{Q}$$

$$BW = f_h - f_l$$

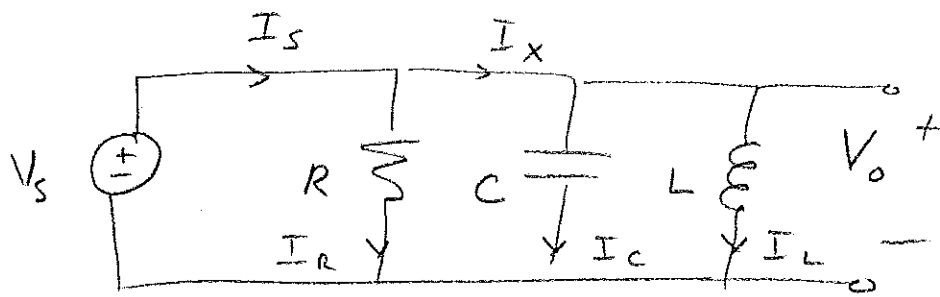

$$V_s = 120 \angle 0^\circ \quad R = 100 \quad C = 600 \mu\text{F} \quad L = 120 \text{ mH}$$

FIND ALL I , V_o @ Resonance

$$\omega_0 = \frac{1}{\sqrt{LC}} = 117.85 \text{ rad/s}$$

$$Y_C = j\omega_0 C = j70.7 \times 10^{-3}$$

$$Y_L = \frac{1}{j\omega_0 L} = -j70.7 \times 10^{-3}$$

$$I_R = \frac{V_s}{R} = \frac{120 \angle 0^\circ}{100} = 1.2 \angle 0^\circ$$

$$I_C = V_s Y_C = 8.49 \angle 90^\circ$$

$$I_L = V_s Y_L = 8.49 \angle -90^\circ$$


$$I_s = I_R + I_C + I_L = 1.2 \angle 0^\circ = I_s$$

$$V_o = V_s \quad (\text{OF COURSE})$$

OP-AMPS


- ① ONLY USE NODE ANALYSIS
- ② "+" AND "-" SIGNS ARE ARBITRARY
- ③ NO CURRENT FLOWS INTO AN OP-AMP
- ④ THERE IS 0 VOLTS BETWEEN INPUT TERMINALS

OP AMPS - IDEAL

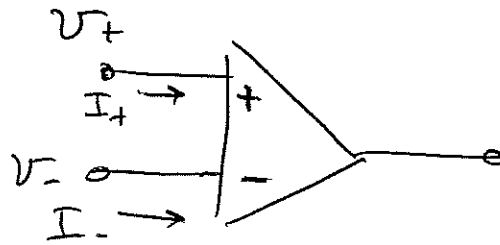

No CURRENT FLOWS INTO OP-AMP $I_+ = I_- = 0$
 VOLTAGES AT V_+ AND V_- ARE SAME.

VIRTUAL SHORT

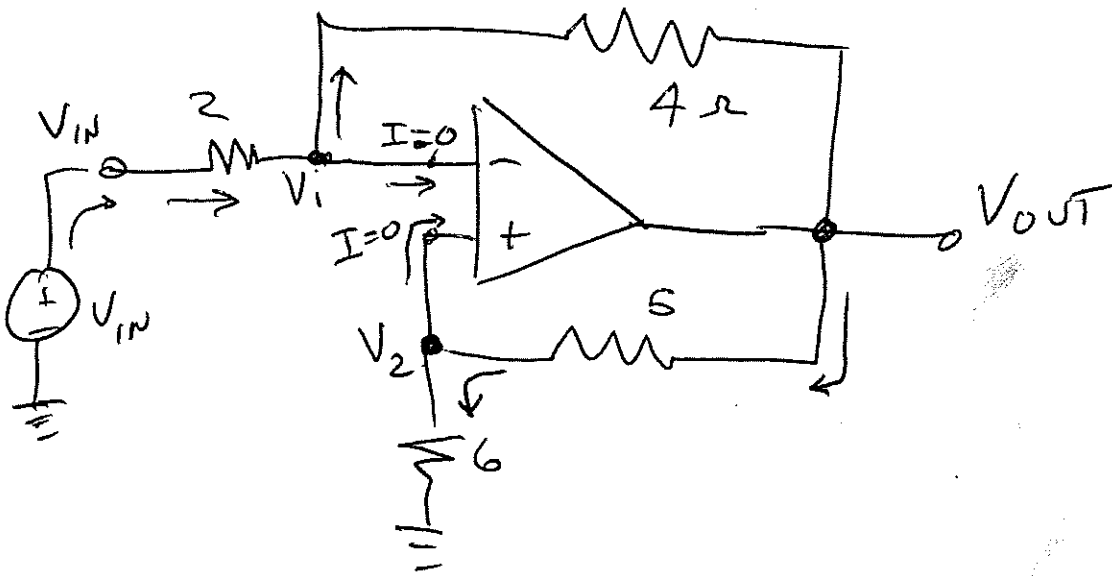


$$V_1 = V_2$$

@ NODE 1 $\frac{V_{IN} - V_1}{2} = \frac{V_1 - V_{OUT}}{4}$ $V_1 = f(V_{IN}, V_{OUT})$

@ NODE 2 $\frac{V_{OUT} - V_2}{5} = \frac{V_2}{6}$

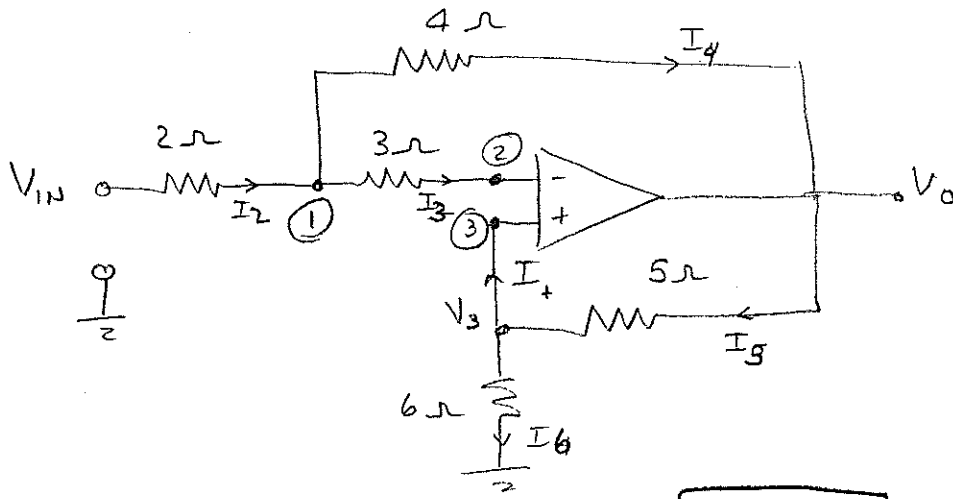$\frac{V_{OUT}}{V_{IN}} \Rightarrow$ GAIN TRANSFER CHARACTERISTIC.



FIND $\frac{V_o}{V_{IN}}$:

USING IDEAL PROPERTIES :

$$I_3 = 0 \quad I_2 = I_4$$

$$I_+ = 0 \quad I_5 = I_6$$

$$V_3 = V_1$$

$$V_3 = V_o \left(\frac{6}{5+6} \right) = V_1$$

NODE 3 :

$$I_5 = I_6$$

$$\frac{V_o - V_3}{5} = \frac{V_3 - 0}{6}$$

$$6V_o - 6V_3 = 5V_3$$

$$6V_o = 11V_3$$

$$V_3 = \frac{6}{11} V_o$$

ALSO BY
VOLTAGE
DIVISION

NODE 1 :

$$\frac{V_{IN} - V_1}{2} = \frac{V_1 - V_o}{4} \rightarrow \frac{V_{IN} - \frac{6}{11} V_o}{2} = \frac{\frac{6}{11} V_o - V_o}{4}$$

$$2V_{IN} - \frac{12}{11} V_o = \frac{-5}{11} V_o$$

$$2V_{IN} = \frac{7}{11} V_o$$

$$\frac{V_o}{V_{IN}} = \frac{22}{7}$$