

Problem 1: The homework Verilog file, `hw05.v`, contains something similar to the streamlined multiplier presented in class, `mult_seq_stream`, and even more streamlined versions of the multiplier, `mult_seq_stream_2`, and `mult_seq_stream_3`. These modules are reproduced at the end of this assignment. For an HTML version visit <http://www.ece.lsu.edu/koppel/v/2015/hw05.v.html>. See the 2014 midterm exam for similar problems.

(a) Show the hardware that will be synthesized for each module for the default parameters. Show the module after optimization.

(b) Estimate the clock frequency of each module based on the following assumptions:

Latch delay: 10 units. Multiplexor latency: 2 units. Latency of a n -bit adder: $5\lceil \lg n \rceil$ units.
Latency of an n -input gate: $\lceil \lg n \rceil$ units.

(c) Why would module `mult_seq_stream_3` provide a result in less time than the other two, even assuming that the clock frequency for all the modules was the same?

```

module mult_seq_stream #( int wid = 16 )
( output logic [2*wid-1:0] prod,
  input logic [wid-1:0] plier,
  input logic [wid-1:0] cand,
  input clk);

localparam int wlog = $clog2(wid);

logic [wlog-1:0] pos;
logic [2*wid-1:0] accum;

always @(*( posedge clk ) begin

  logic [wid:0] pp;

  if ( pos == 0 ) begin

    prod = accum;
    accum = cand;
    pos = wid - 1;

  end else begin

    pos--;

  end

  // Note: the multiplicand is in the lower bits of the accumulator.
  //
  pp = accum[0] ? { 1'b0, plier } : 0;

  // Add on the partial product and shift the accumulator.
  //
  accum = { { 1'b0, accum[2*wid-1:wid] } + pp, accum[wid-1:1] };

end

endmodule

```

```

module mult_seq_stream_2 #( int wid = 16 )
( output logic [2*wid-1:0] prod,
  input logic [wid-1:0] plier,
  input logic [wid-1:0] cand,
  input clk);

localparam int wlog = $clog2(wid);

logic [wlog-1:0] pos;
logic [2*wid-1:0] accum;

always @(*( posedge clk ) begin

  if ( pos == 0 ) begin

    prod = accum;
    accum = { 1'b0, cand[0] ? plier : wid'(0), cand[wid-1:1] };
    pos = wid - 1;

  end else begin

    logic [wid:0] pp;

    // Note: the multiplicand is in the lower bits of the accumulator.
    //
    pp = accum[0] ? plier : 0;

    // Add on the partial product and shift the accumulator.
    //
    accum = { { 1'b0, accum[2*wid-1:wid] } + pp, accum[wid-1:1] };

    pos--;

  end

end

endmodule

```

```

module mult_seq_stream_3 #( int wid = 16 )
( output logic [2*wid-1:0] prod,
  input logic [wid-1:0] plier,
  input logic [wid-1:0] cand,
  input clk);

localparam int wlog = $clog2(wid);

logic [wlog-1:0] pos;
logic [2*wid-1:0] accum;

always @(*( posedge clk ) begin

  if ( pos == 0 ) begin

    accum = { 1'b0, cand[0] ? plier : wid'(0), cand[wid-1:1] };
    pos = wid - 1;

  end else begin

    logic [wid:0] pp;

    // Note: the multiplicand is in the lower bits of the accumulator.
    //
    pp = accum[0] ? plier : 0;

    // Add on the partial product and shift the accumulator.
    //
    accum = { { 1'b0, accum[2*wid-1:wid] } + pp, accum[wid-1:1] };

    if ( pos == 1 ) prod = accum;

    pos--;

  end

end

endmodule

```