

# Simple Cost and Performance Model

## Simple Model Goals

Choose between design alternatives.

Characterize a particular design approach.

## Simple Model Non-Goals

Approximate the post synthesis cost and performance.

## The Cost Model

### *Base Costs*

2-input AND gate: 1 unit.

2-input OR gate: 1 unit.

NOT gate: 0 units. (Zero cost.)

### Derived Costs

Based on equivalent circuit using gates above.

Cost of  $n$ -input OR gate:  $n - 1$  units.

Cost of  $n$ -input AND gate:  $n - 1$  units.


Cost of a 2-input XOR gate is 3 units.

## Simple Examples:


A 2-input AND gate: cost is 1 unit.

A 10-input OR gate: cost is 9 units.

A 1-input OR gate: free.

 

: cost is  $1 + 1 = 2$  units.

 

: cost is  $3 + 3 + 1 = 7$  units.

## The Performance Model

### *Base Delays*

2-input AND gate: 1 unit.

2-input OR gate: 1 unit.

NOT gate: 0 units.

### Derived Delays


Based on equivalent circuit using gates above.

Delay of a 2-input XOR gate is 2 units.

Delay of  $n$ -input OR gate:  $\lceil \lg n \rceil$  units.

Delay of  $n$ -input AND gate:  $\lceil \lg n \rceil$  units.

## Multiplexors

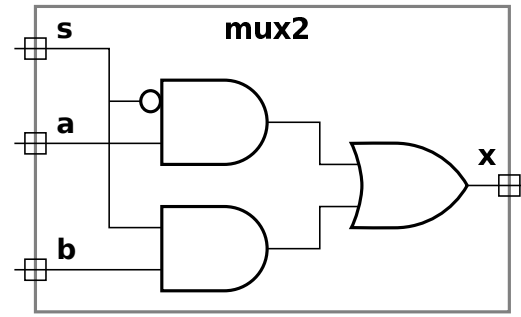

*A 2-input, 1-bit mux:*

Cost, 3 units; delay, 2 units.

*A 2-input,  $w$ -bit mux:*

This is equivalent to  $w$  copies of the mux above.

Cost,  $3w$  units; **delay, 2 units.**

## Multiplexors

*An  $n$ -input,  $w$ -bit mux,  
unoptimized decoder implementation:*

Note: The number of select bits is  $\lceil \lg n \rceil$ .


Cost Computation:

Decoder AND gates (first column):  $n(\lceil \lg n \rceil - 1)$ .

Selection AND gates (second column):  $wn$ .

OR gate:  $w(n - 1)$ .

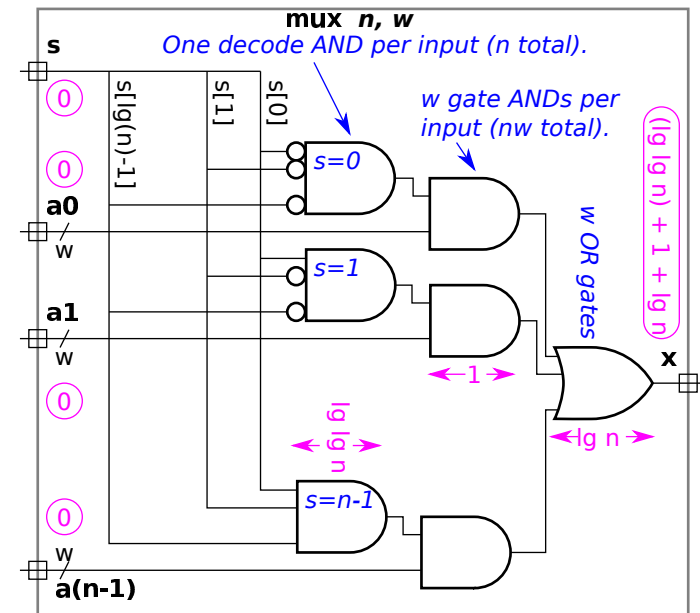Total cost:  $n(\lceil \lg n \rceil - 1) + 2wn - w$ .



## Delay Computation


Decoder AND gate (first column):  $\lceil \lg(\lceil \lg n \rceil - 1) \rceil$ .

Selection AND gates (second column): 1.

OR gate:  $\lceil \lg n \rceil$ .

Total delay:  $\lceil \lg(\lceil \lg n \rceil - 1) \rceil + 1 + \lceil \lg n \rceil$ .

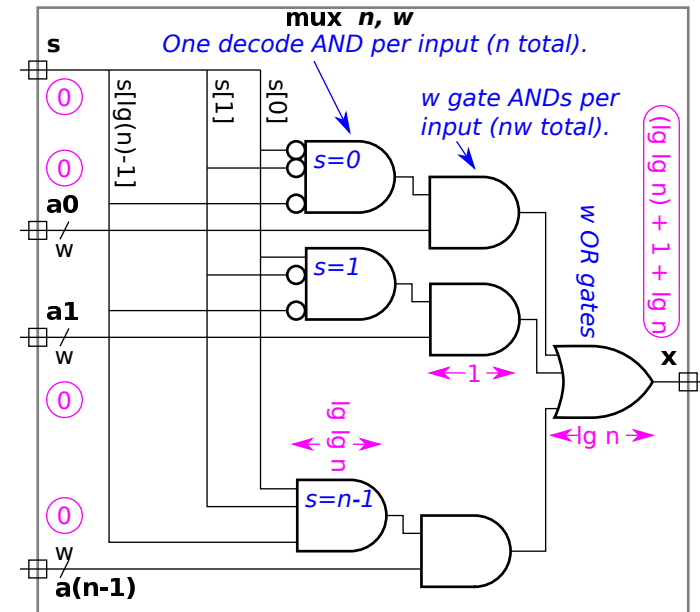Approximate delay:  $1 + \lceil \lg n \rceil$ .



## An $n$ -input, $w$ -bit mux, tree implementation:

Constructed from 2-input multiplexors.

Illustration is for  $n = 8$ .

The path from the selected input ...  
... is through  $\lceil \lg n \rceil$  2-input muxen ...  
... through 3 for illustrated size,  $n = 8$ .


The number of muxen connected to select bit  $i$  ...  
... is  $n/2^{i+1}$  for  $0 \leq i < \lceil \lg n \rceil$  ...  
... for illustrated size 2 muxen connect to bit 1.

### Cost Computation

Total number of 2-input muxen ...  
...  $\sum_{i=0}^{\lg n - 1} n/2^{i+1} = n - 1$  ...  
... for illustrated mux, 7 2-input muxen.

Total cost:  $3w(n - 1)$ .

Total Delay:  $2\lceil \lg n \rceil$ .

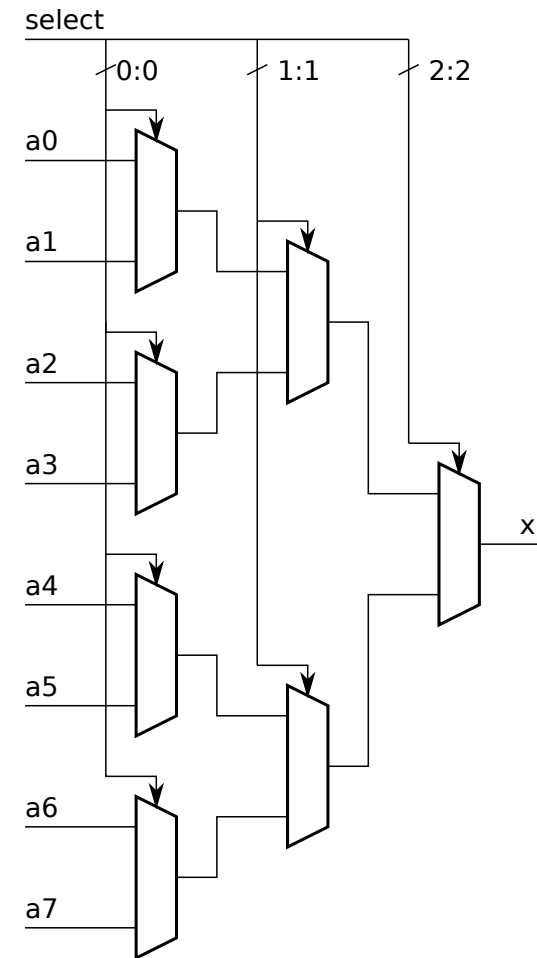



## Equality Comparison ( $a == b$ )

Output is 1 iff  $w$ -bit inputs are equal.

Assume  $w$  is a power of 2.


Cost Computation

XOR Gates:  $3w$ .

Reduction tree of AND gates:

$$\sum_{i=1}^{\lg w} w/2^i = w - 1.$$

Total Cost:  $4w - 1 \approx 4w$ .

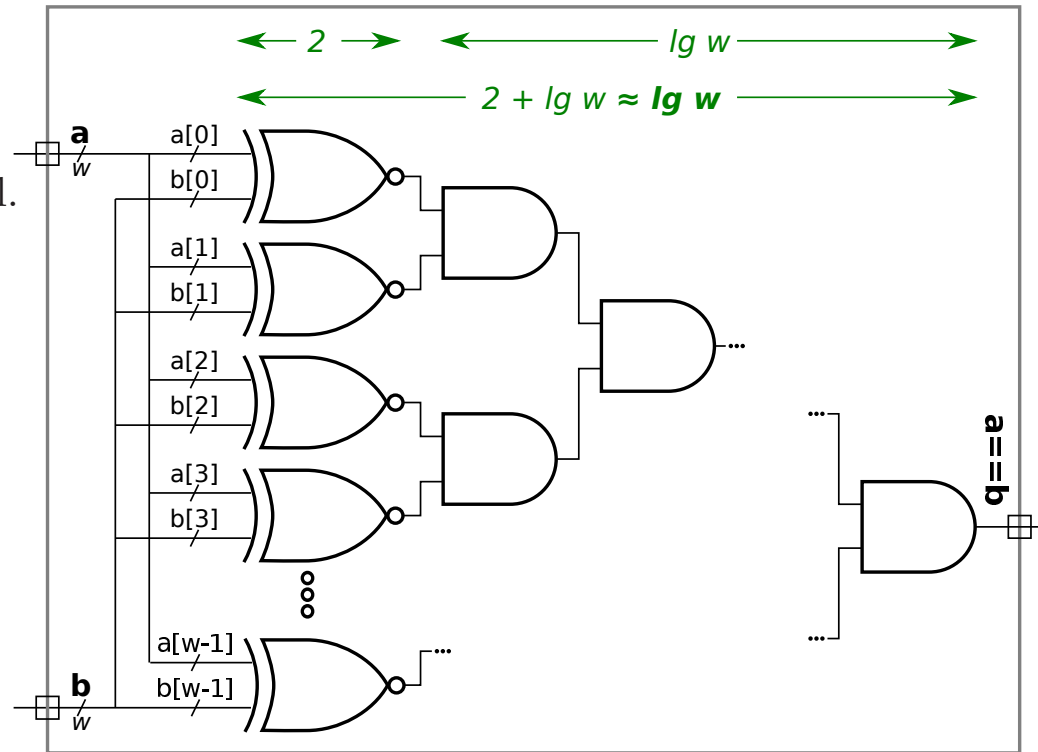

Delay Computation

XOR Gates: 2.

Reduction Tree:  $\lg w$ .


Total Delay:  $2 + \lg w \approx \lg w$ .

## Binary Full Adder Implementations

Fast BFA
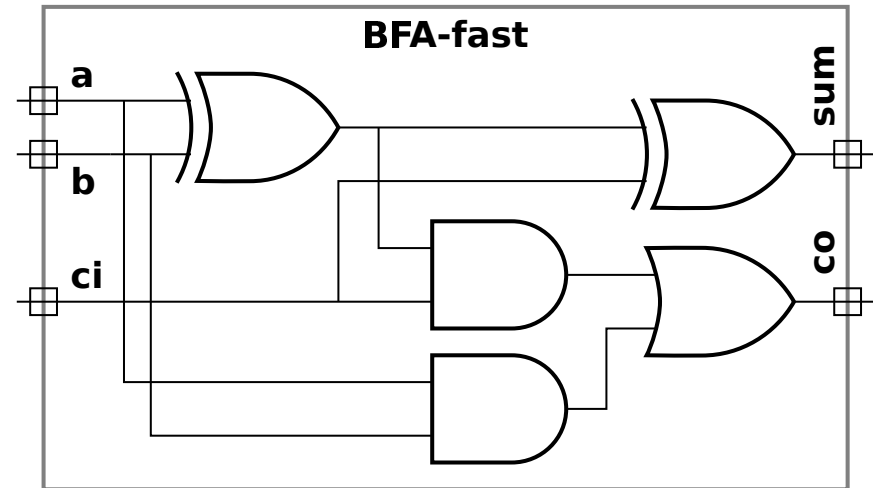
## Cost Computation

Two XOR, 3 AND:  $2 \times 3 + 3 = 9$  units.



## Fast BFA

Delay: Any input to any output.

See **Path I** and...

... **purple** labels in diagram.


Delay: 4 units.

Delay: **ci** to **co**.

This delay is useful when **a** and **b** arrive earlier than **ci**.


See **Path II** and **green** labels in diagram.

Delay: 2 units.

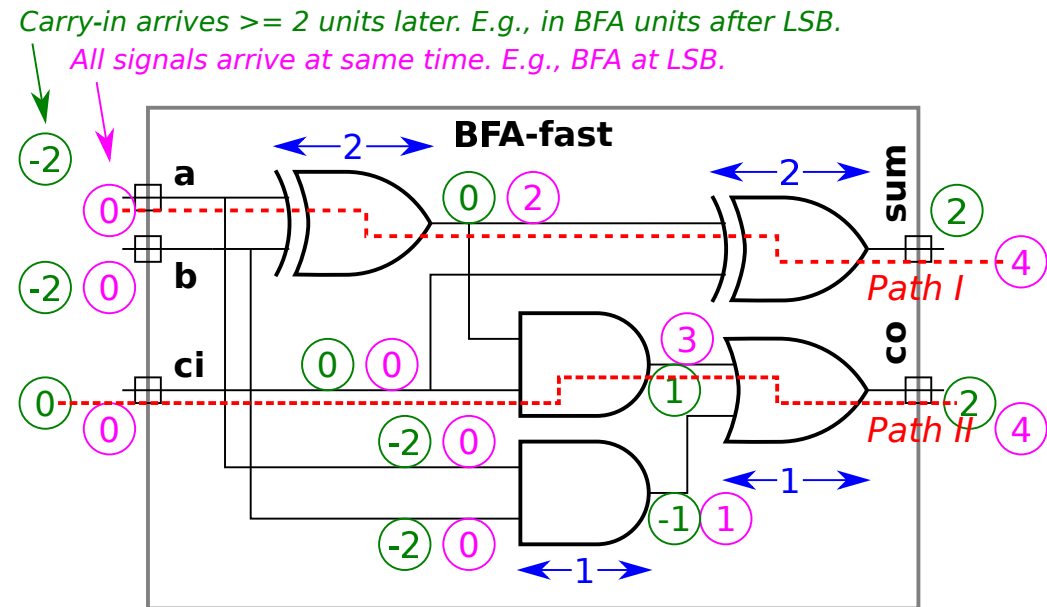

## *w*-Bit Ripple Adder

Implementation using Fast BFA

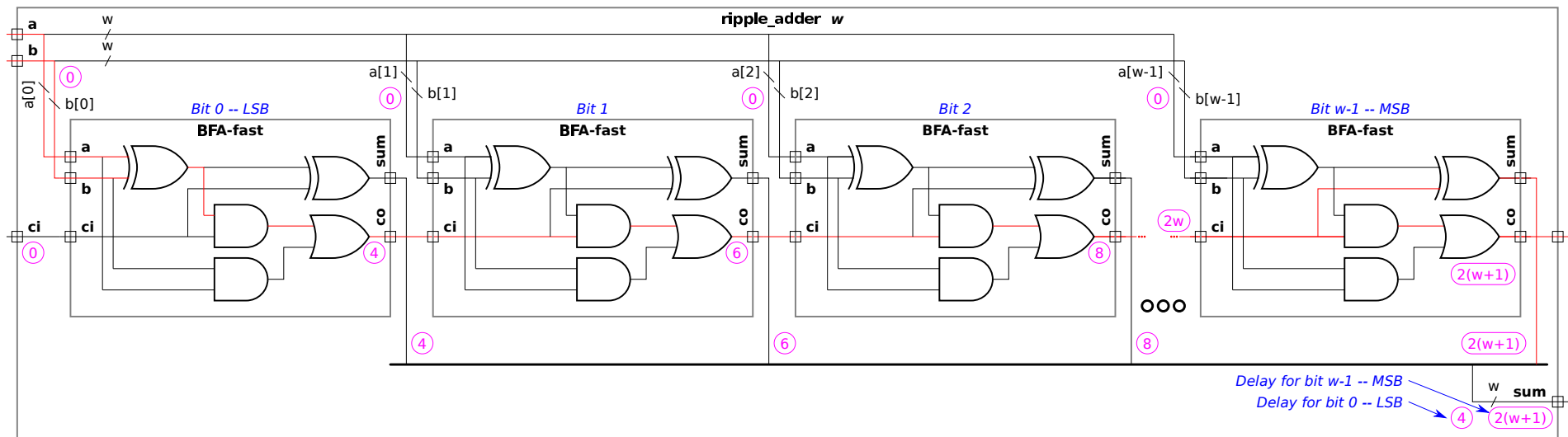

Cost Computation: Cost of  $w$  BFAs:  $9w$  units.

Delay Computation

See **critical path (in red)** in diagram.

Delay:  $2(w + 1) \approx 2w$ .

## *Integer Magnitude Comparison*

For comparisons like  $a < b$ .

Implementation:

Compute  $a - b$  and check whether result negative.

If carry out of MSB is 0 then  $a - b < 0$  and so  $a < b$  is true.

Omit sum hardware in BFA, and replace remaining XOR with an OR.

Cost Computation

Each modified BFA now costs 4 units.

Total cost:  $4w$  units.

Delay Computation

Delay is 3 for first bit, 2 for remaining bits.

Total delay:  $2w + 1 \approx 2w$ .

## *Cascaded Ripple Units*

For computations using ripple units...

... such as  $a + b + e$ , and  $(a + b) < e$ , etc.

### Cost Computation

Cost is sum of costs of each ripple unit.

For example,  $a + b + c$  is two ripple adders, cost is  $18w$  ...

...  $(a + b) < e$  is a ripple adder plus a magnitude comparison:  $9w + 4w = 13w$ .

## Cascaded Ripple Units

Delay Computation:

Consider  $(a + b) + e$ .

Naïve analysis: wait for  $a + b$  to finish, then start  $+e$ .

But, LSB of  $a + b$  available after only 4 cycles ...

... bit  $i$  is available after  $4 + 2i$  cycles ...

... so the  $+e$  computation can start after 4 cycles.

Delay for two ripple units is  $4 + 2(w + 1)$ .

Delay for  $n$  ripple units is  $4(n - 1) + 2(w + 1)$ .

## Cost and Performance with Constant Inputs

### *Constant Inputs*


Signal values which never change.

Cost and delay are radically different when an input never changes.

In Verilog, this might be an elaboration-time constant ...  
... or other expressions that never change.


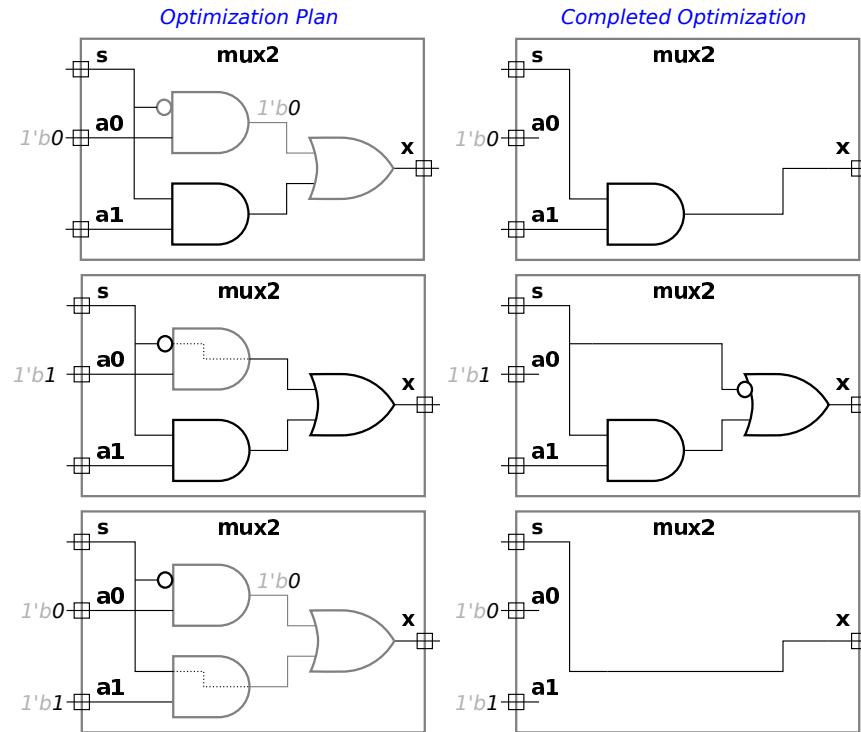
## Multiplexor Constant-Input Optimizations



Sample mux optimizations:

Costs: From top to bottom costs are: 1 unit, two units, zero units.

Delays: From top to bottom delays are: 1 unit, two units, zero units.