

EE 2720, Spr. 05
Homework #5

Due Wednesday April 6 at 9:30 am
in my office; (Room EE 245).

EE 2720, HW # 5

Note: Please staple your homework. ①

Problem 1: Consider the logic function F where F is $F = A' \cdot B \cdot C + D \cdot E' + G$. Realize F using only NAND gates using the graphical approach (bubbles etc.). Show a figure.

Problem 2: Consider the logic function F where F is $F = (A' + B + C) \cdot (D + E') \cdot G$. Realize F using only NOR gates using the graphical approach (bubbles etc.). Show a figure.

Problem 3: Consider the logic function F where $F = A' \cdot B \cdot C + D \cdot E' + G$.

Ⓐ Realize F using NOT, AND and OR gates. This is of course going to be an AND-OR realization. Call this realization, realization # 1.

Ⓑ Realize F using only NAND gates. Do not use the graphical approach this time. Use an algebraic approach this time. Call this realization, realization # 2.

Ⓒ Realize F using only OR and NAND gates. Call this realization, realization # 3.

- ① Realize F using only NOR and OR gates. Call this realization, realization # 4.
- ② Transform realization # 3 into realization # 4 using the graphical approach (bubbles etc.).
- ③ Transform realization # 4 into realization # 3 using the graphical approach (bubbles etc.).

Note: You must show figures here in problem 3.

Problem 4: Consider the logic function F

where F is $F = (A' + B + C) \cdot (D + E') \cdot G$.

- ① Realize F using NOT, OR and AND gates. This is of course going to be an OR-AND realization. Call this realization, realization # 1.
- ② Realize F using only NOR gates. Do not use the graphical approach this time. Use an algebraic approach instead. Call this realization, realization # 2.

- (c) Realize F using only AND and NOR gates. Call this realization, realization # 3.
- (d) Realize F using only NAND and AND gates. Call this realization, realization # 4.
- (e) Transform realization # 3 into realization # 4 using the graphical approach (bubbles etc.).
- (f) Transform realization # 4 into realization # 3 using the graphical approach (bubbles etc.).

Note: You must show figures here in problem 4 of course.

Problem 5: Consider the logic circuit of figure 1 on next page. It is an AND-OR logic circuit. Transform the circuit of Fig. 1 into an equivalent OR-AND logic circuit by using the graphical approach (bubbles etc.). Show a figure

↳ Next page

Problem 5 cont:

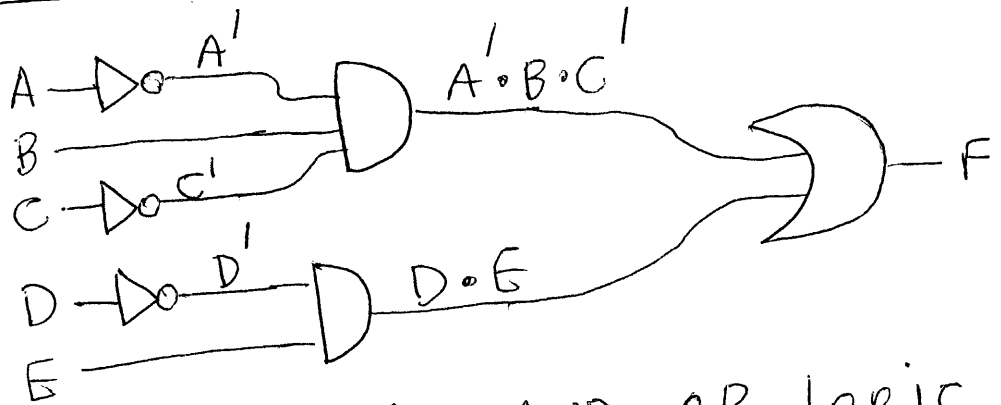


Figure 1: An AND-OR logic circuit

Problem 6: Consider the logic circuit of figure 2 below. It is an OR-AND logic circuit. Transform the circuit of figure 2 into an equivalent AND-OR logic circuit by using the graphical approach (bubbles etc). Show a figure.

 


Figure 2: An OR-AND logic circuit.

Problem 7: Prove equations (5), (6), (7), (8) and (11) on page 8 of handout #11; (they relate to the XOR operator). You are not allowed to use a truth table when proving eq. (11).