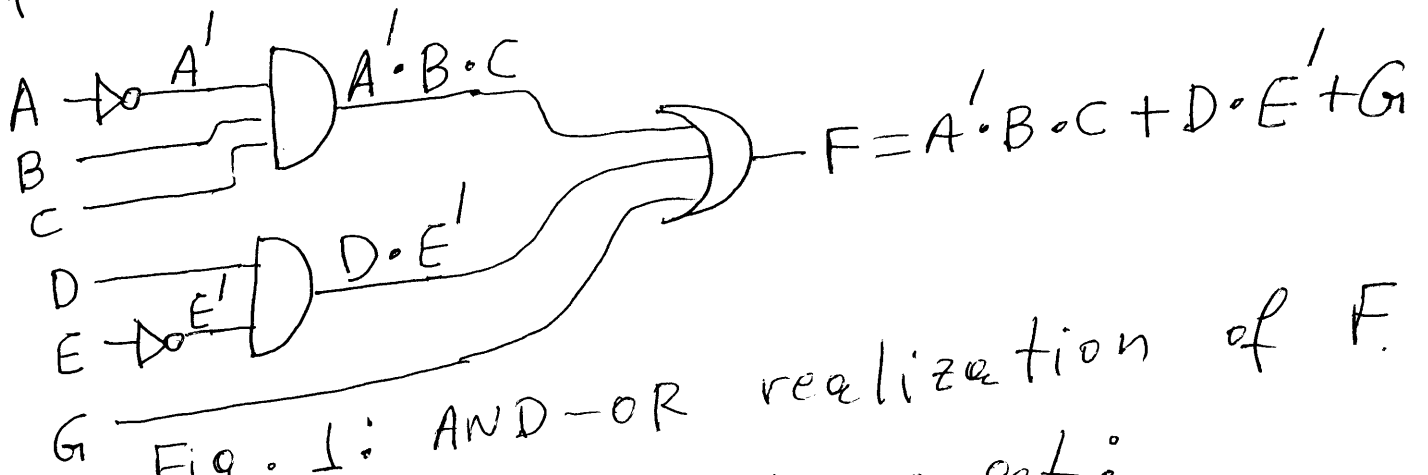


EE 2720, Spr 05  
Solutions of Homework # 5

Problem 1: I first provide a logic <sup>(1)</sup> circuit showing an AND-OR realization of  $F$ . This is shown in fig. 1 below:



From the above fig. 1 we get:

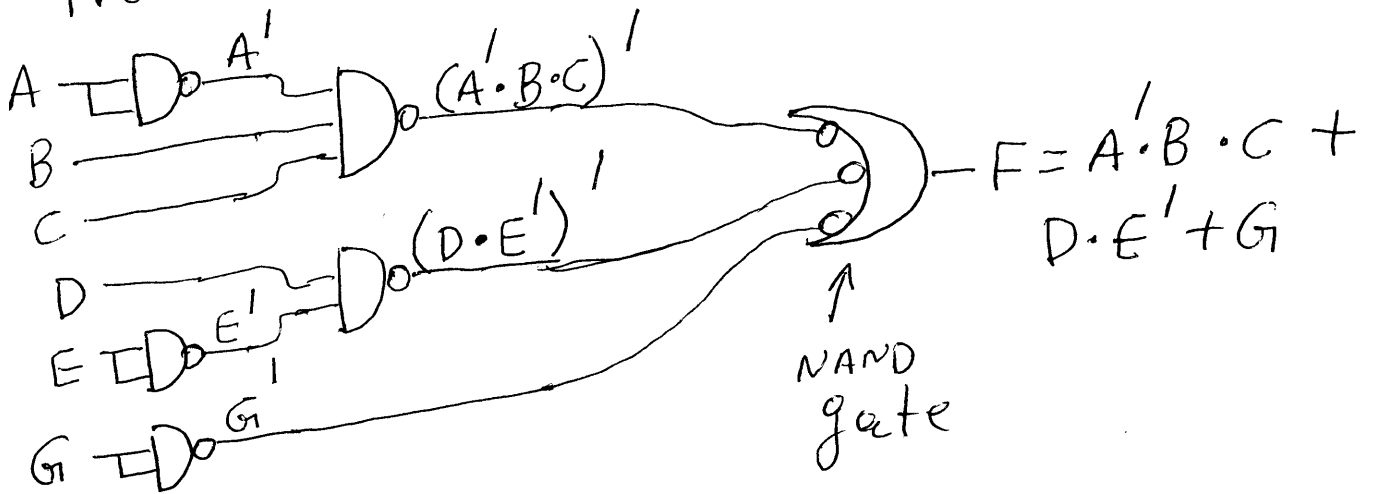


Fig. 2: Realization of  $F$  using only NAND gates.

Problem 2: I first provide a logic circuit showing an OR-AND realization of  $F$ . This is shown in figure 1 below:

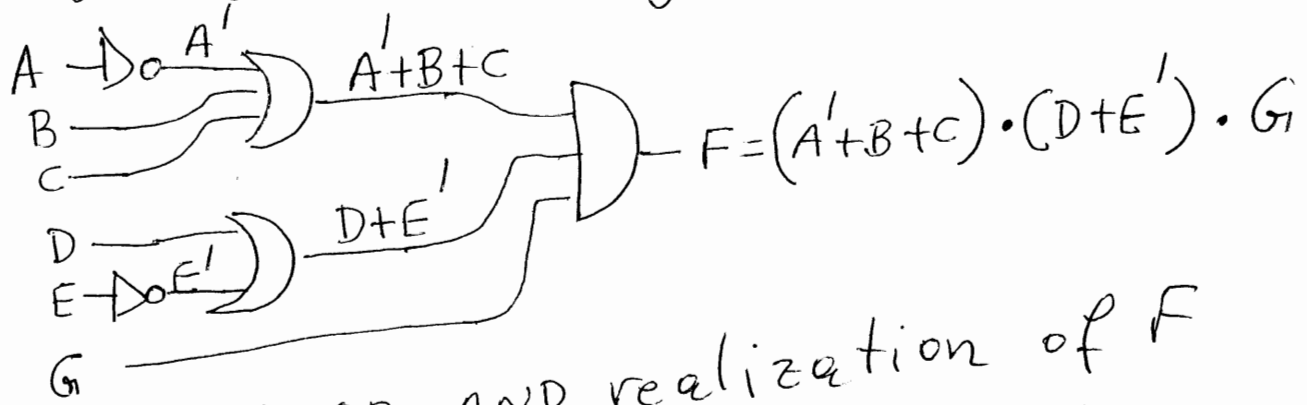


Fig. 1: OR-AND realization of  $F$   
 From the above fig. 1 we get:

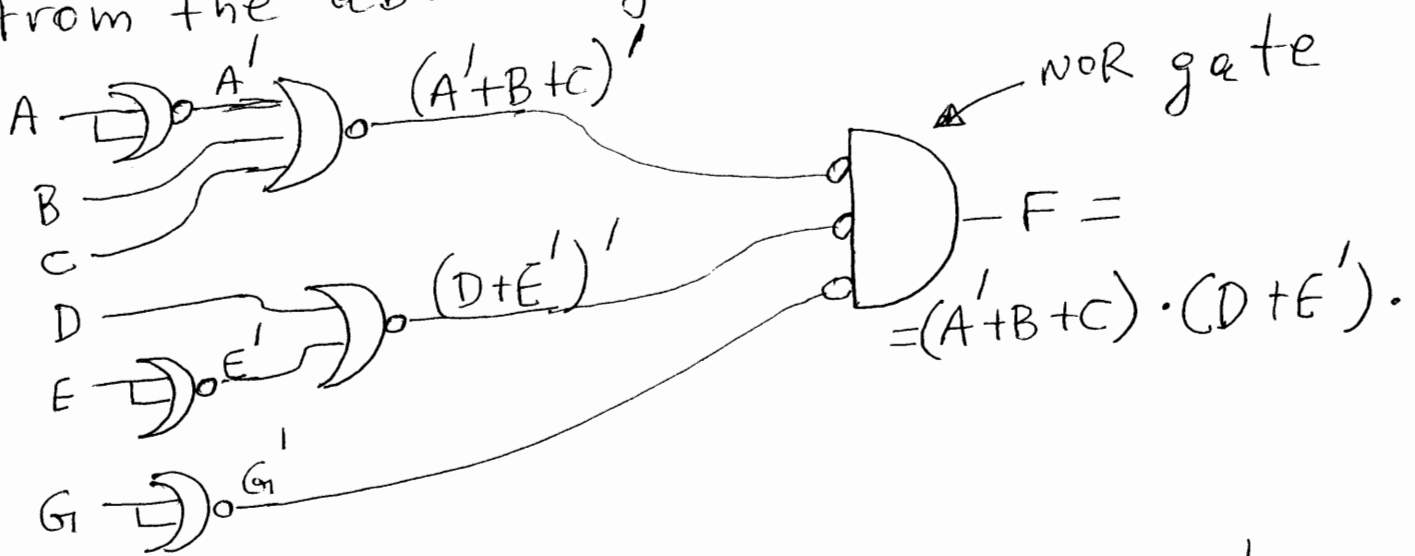


Fig. 2: Realization of  $F$  using only NOR gates

Problem 3:

$$F = A' \cdot B \cdot C + D \cdot E' + G \quad (1)$$

$$= \left[ (A' \cdot B \cdot C + D \cdot E' + G)' \right]'$$

$$= \left[ (A' \cdot B \cdot C)' \cdot (D \cdot E')' \cdot G' \right]' \quad (2)$$

$$\left[ (A+B'+G') \cdot (D'+E) \cdot G' \right]' \quad (3)$$

$$= (A+B'+G')' + (D'+E)' + G \quad (4)$$

The above equations (1), (2), (3), (4) will give us realizations # 1, 2, 3, 4 respectively shown in figures 1, 2, 3, 4 respectively.

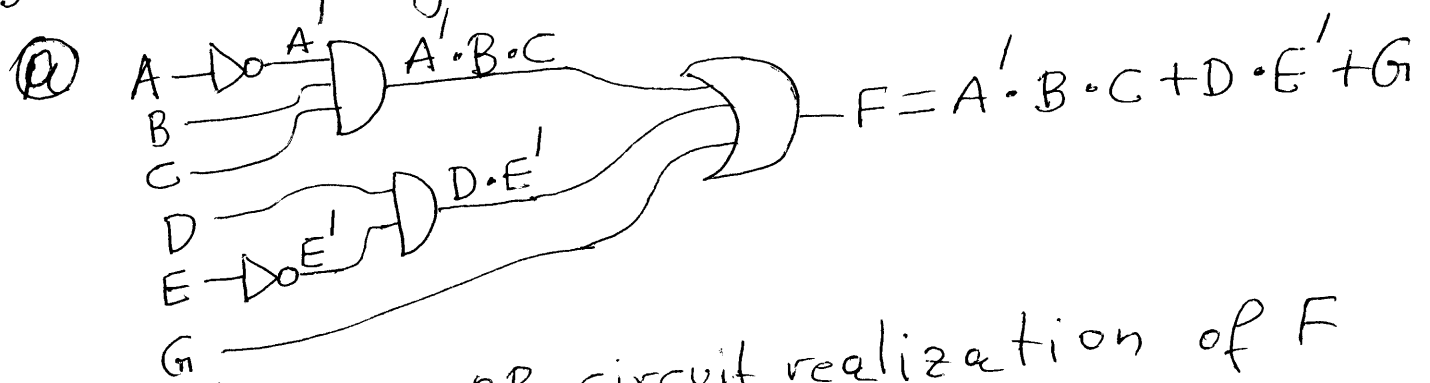


Fig. 1 AND-OR circuit realization of F

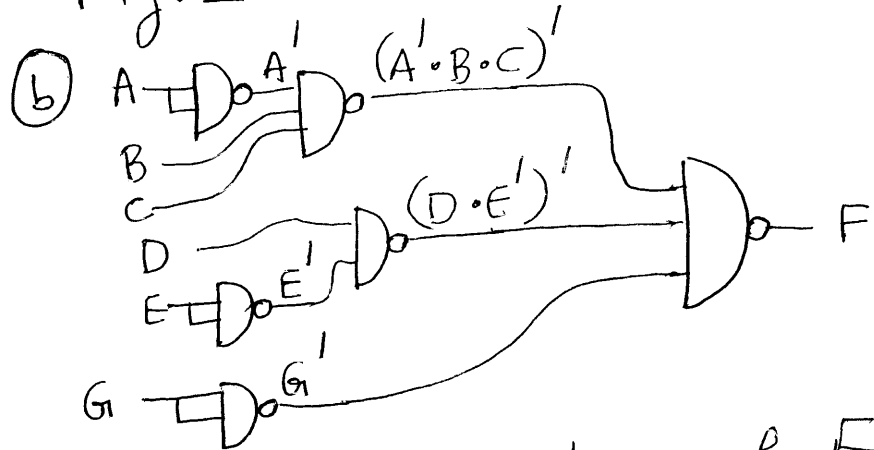


Fig. 2: Realization of F using only NAND gates

### Problem 3 cont.

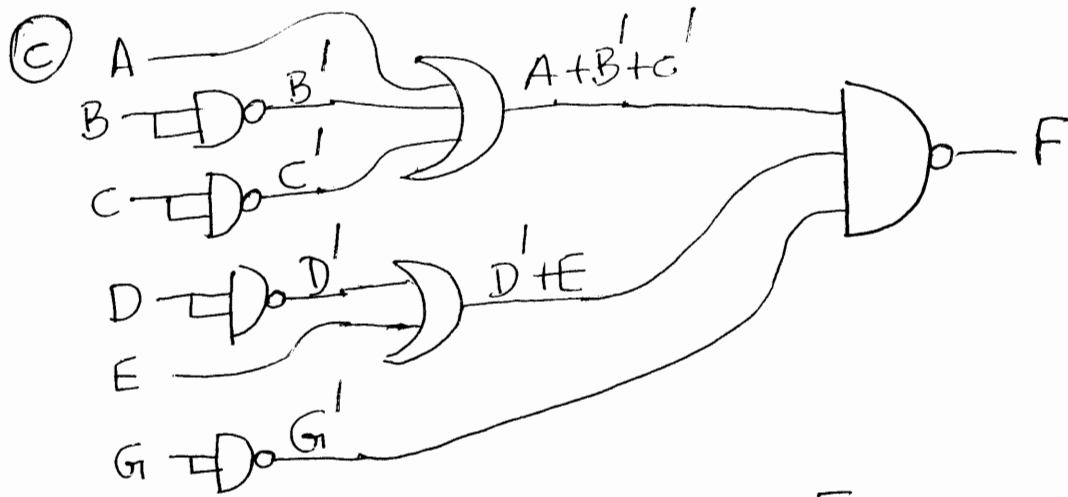


Fig. 3: Realization of  $F$  using only OR and NAND gates.

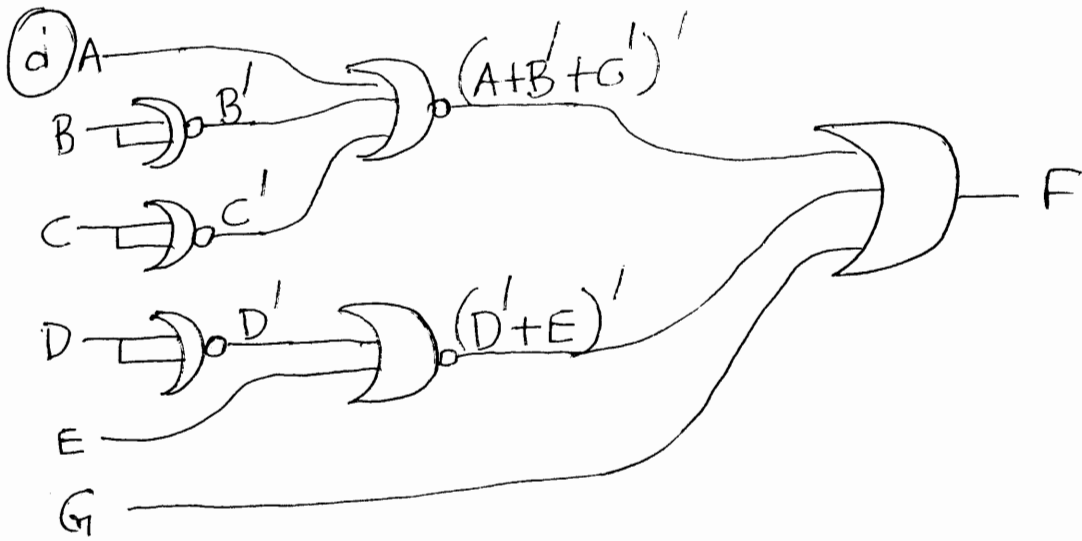


Fig. 4: Realization of  $F$  using only NOR and OR gates.

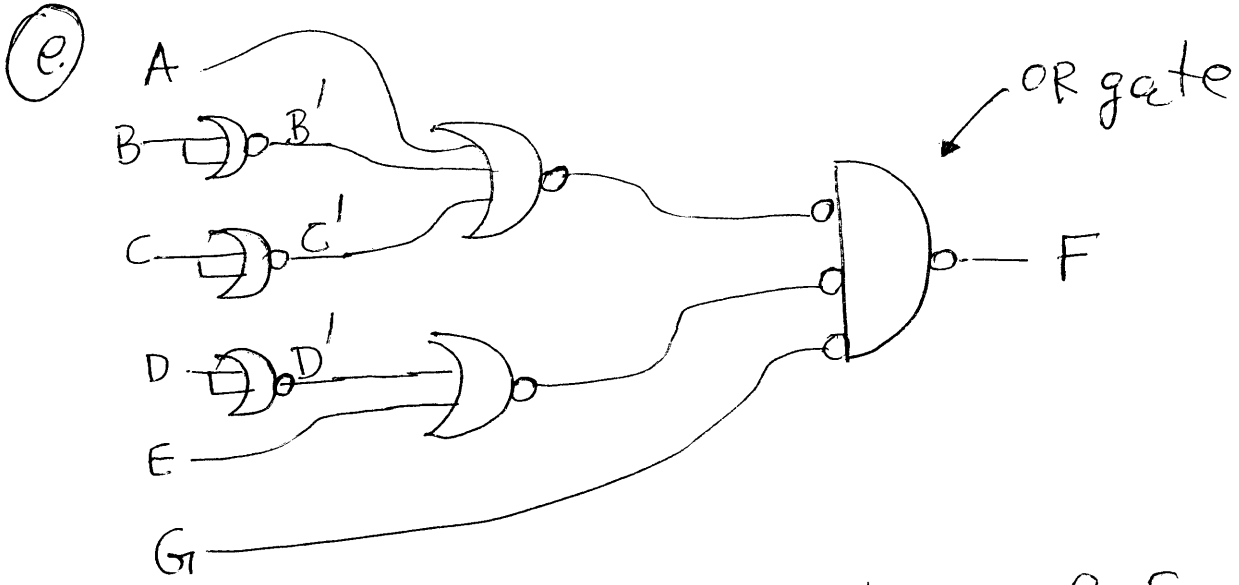


Fig. 5: Another realization of F using only NOR and OR gates.

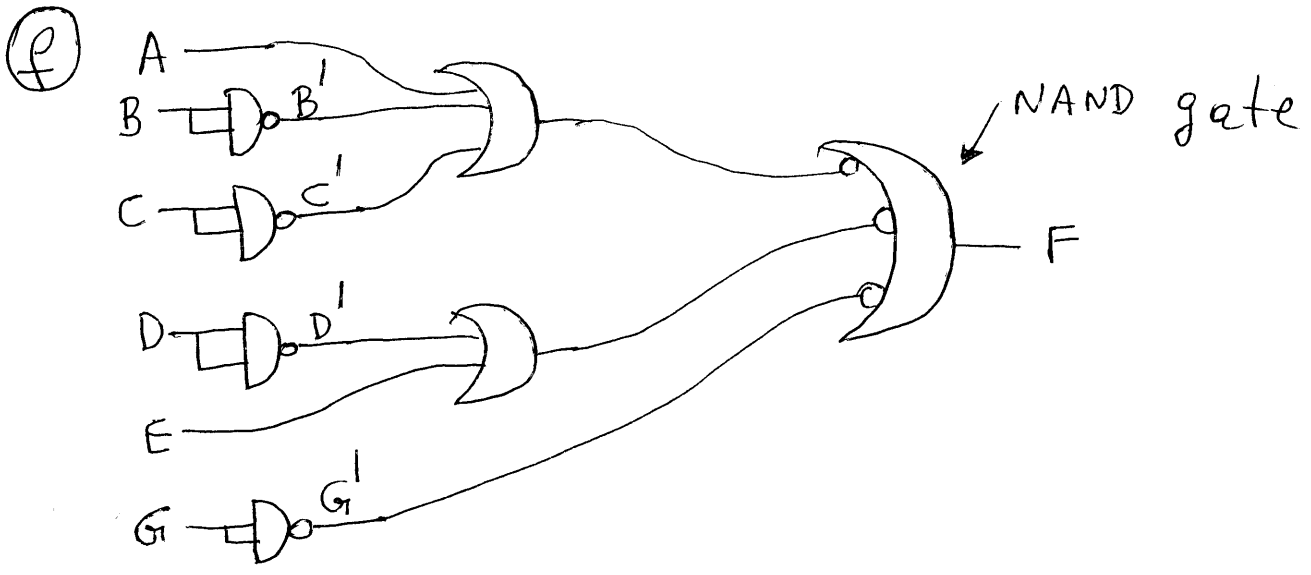


Fig. 6: Another realization of F using only NAND and OR gates.

Problem 4:

$$F = (A' + B + C) \cdot (D + E') \cdot G \quad (1)$$

$$= \left[ \left[ (A' + B + C) \cdot (D + E') \cdot G \right]' \right]'$$

$$= \left[ (A' + B + C)' + (D + E')' + G' \right]' \quad (2)$$

$$= (A \cdot B' \cdot C' + D' \cdot E + G')' \quad (3)$$

$$= (A \cdot B' \cdot C')' \cdot (D' \cdot E)' \cdot G \quad (4)$$

Equations (1), (2), (3), (4) above will give us realizations # 1, 2, 3, 4 respectively, shown in figures 1, 2, 3, 4 respectively.

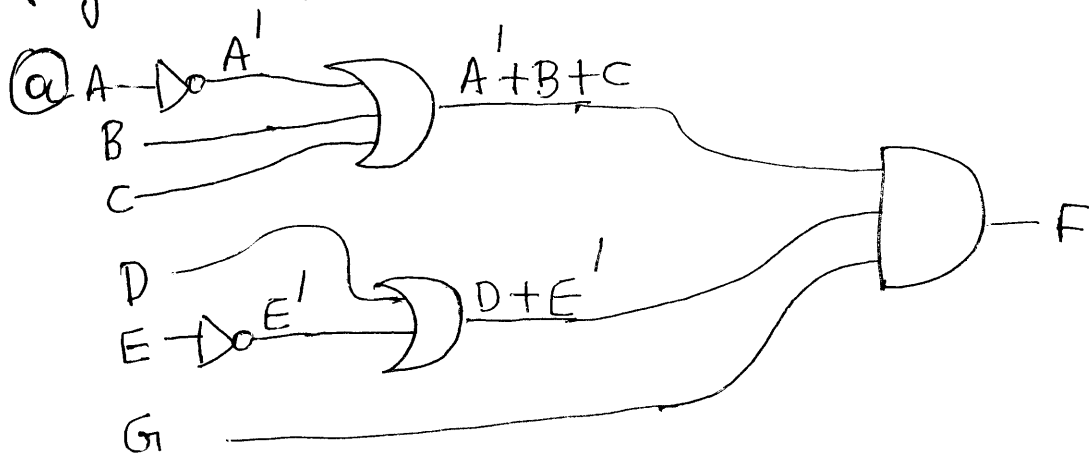


Fig. 1: OR-AND realization of F

Problem 4 cont.

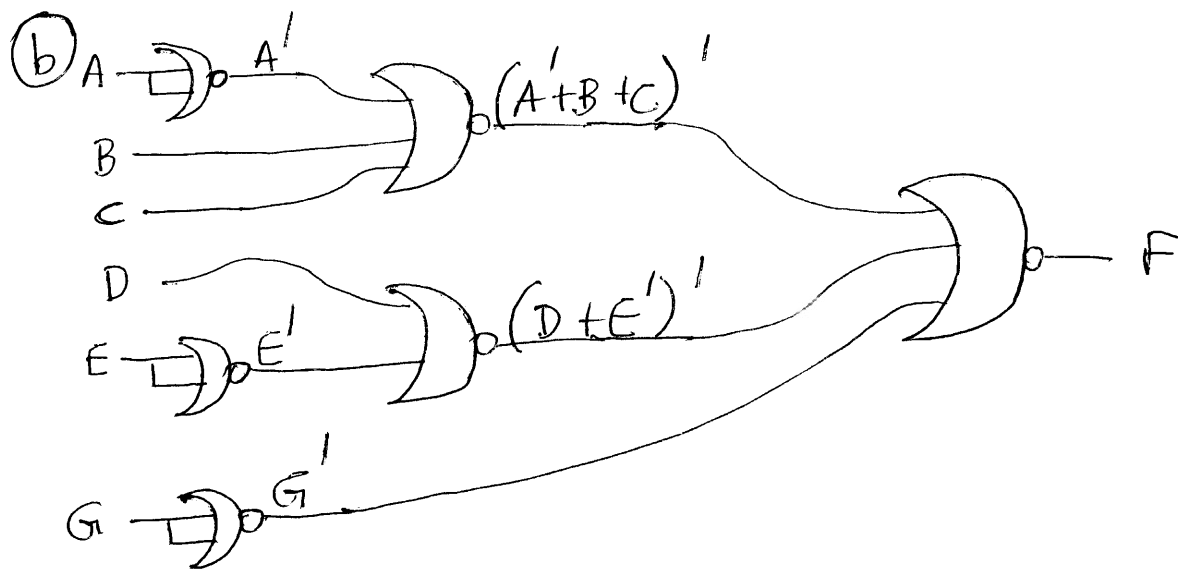


Fig. 2: Realization of F using only NOR gates.

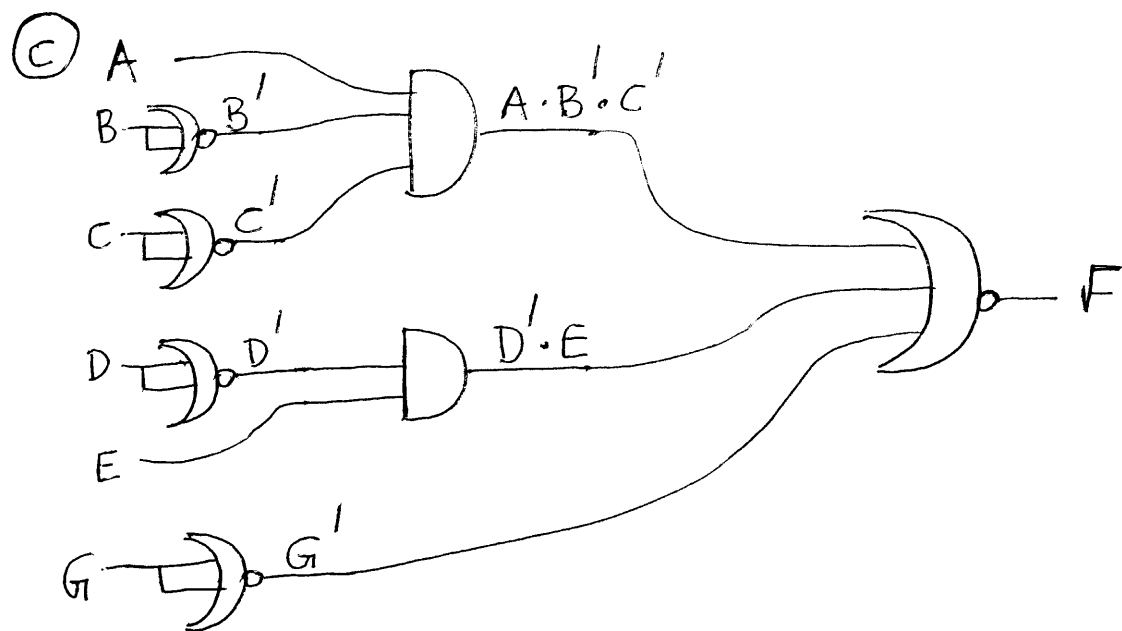


Fig. 3: Realization of F using only AND and NOR gates

Problem 4 cont.

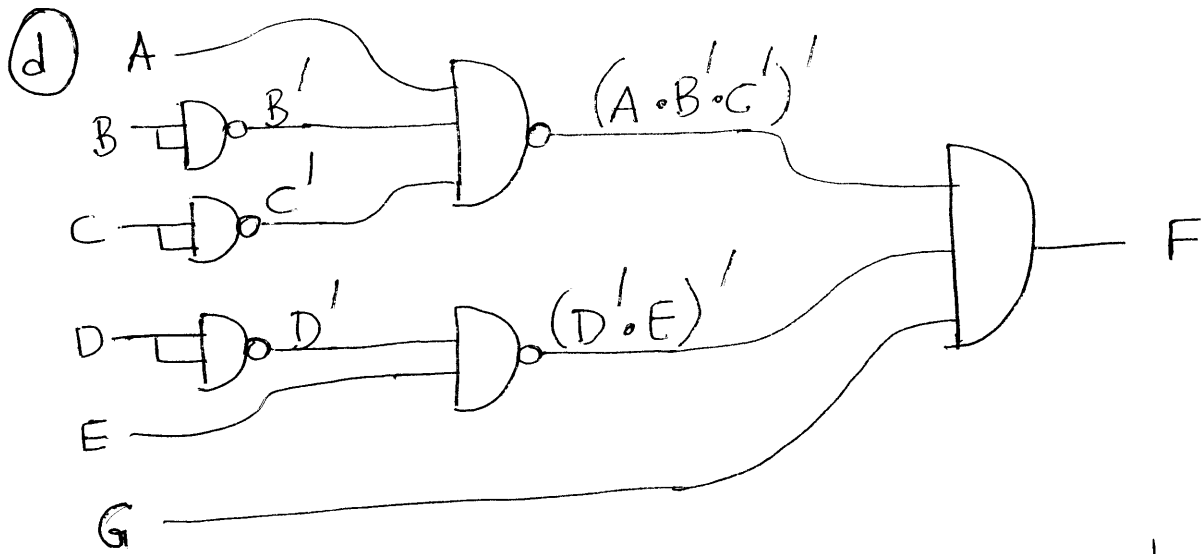


Fig. 4: Realization of F using only NAND and AND gates.

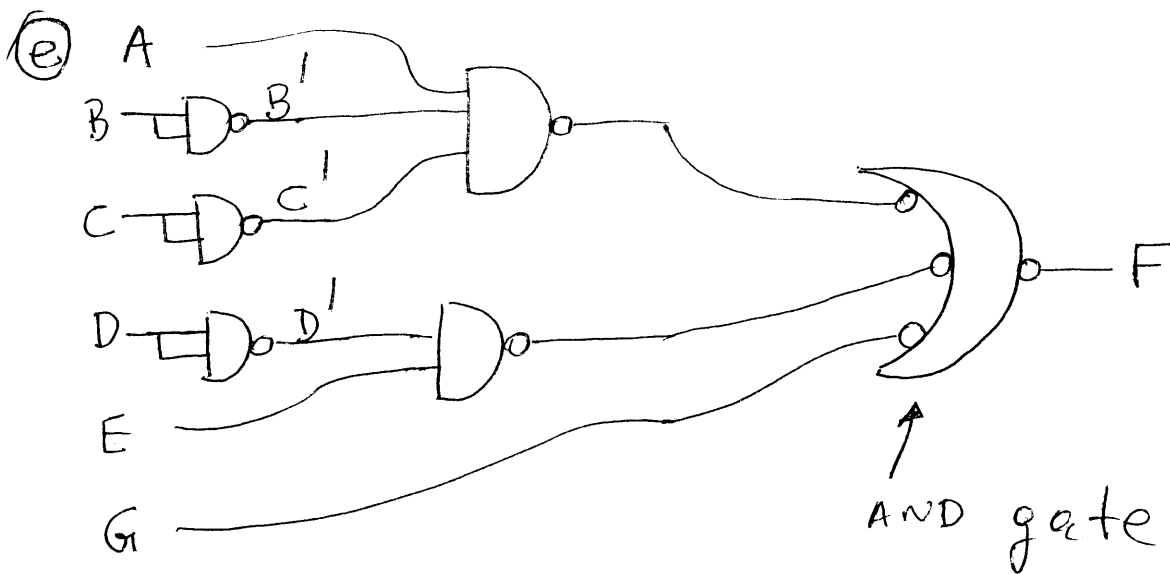


Fig. 5: Another realization of F using only NAND and AND gates.

Problem 4 cont.

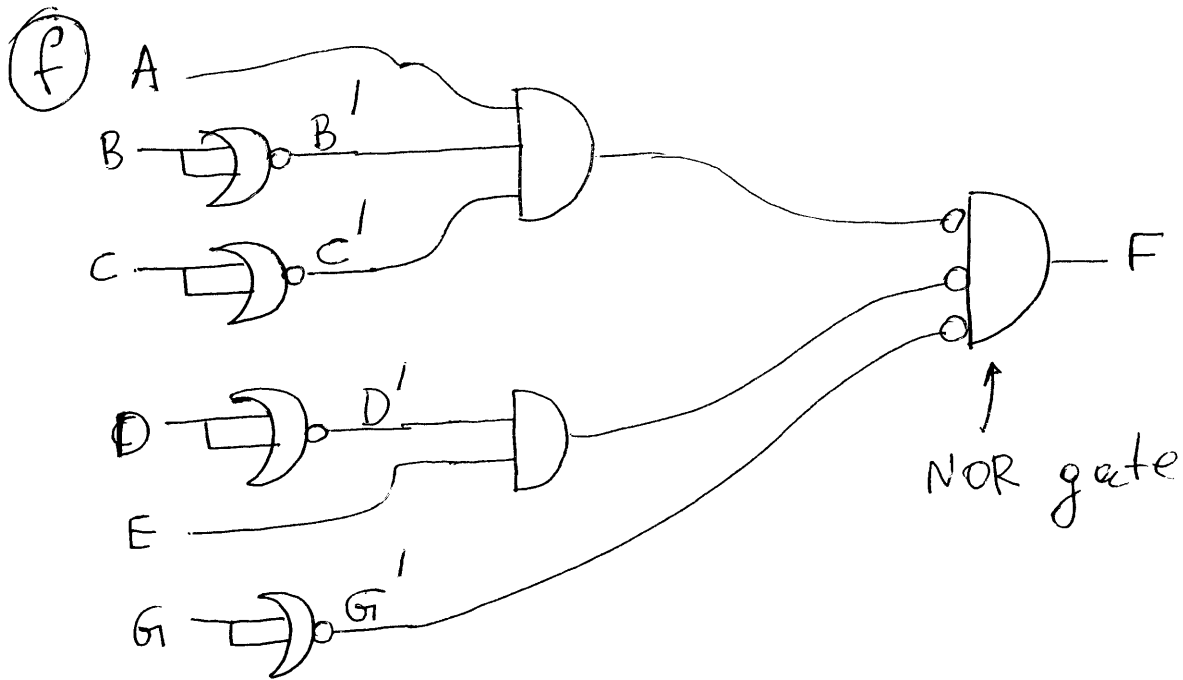


Fig. 6: Another realization of F using only AND and NOR gates.

Problem 5:

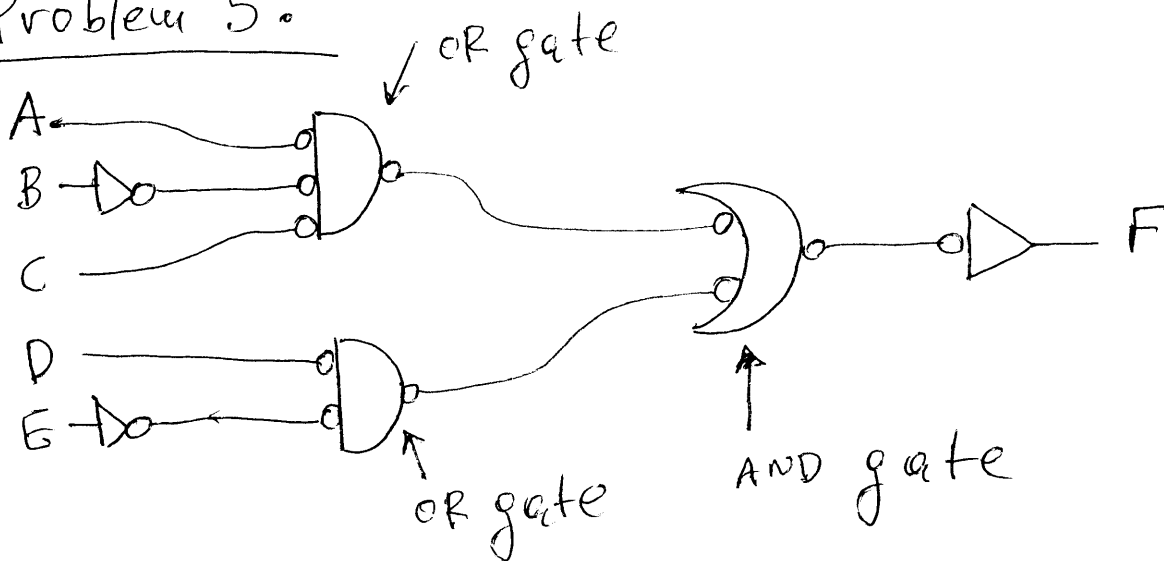


Fig 1a: The equivalent OR-AND logic circuit for F.

### Problem 6:

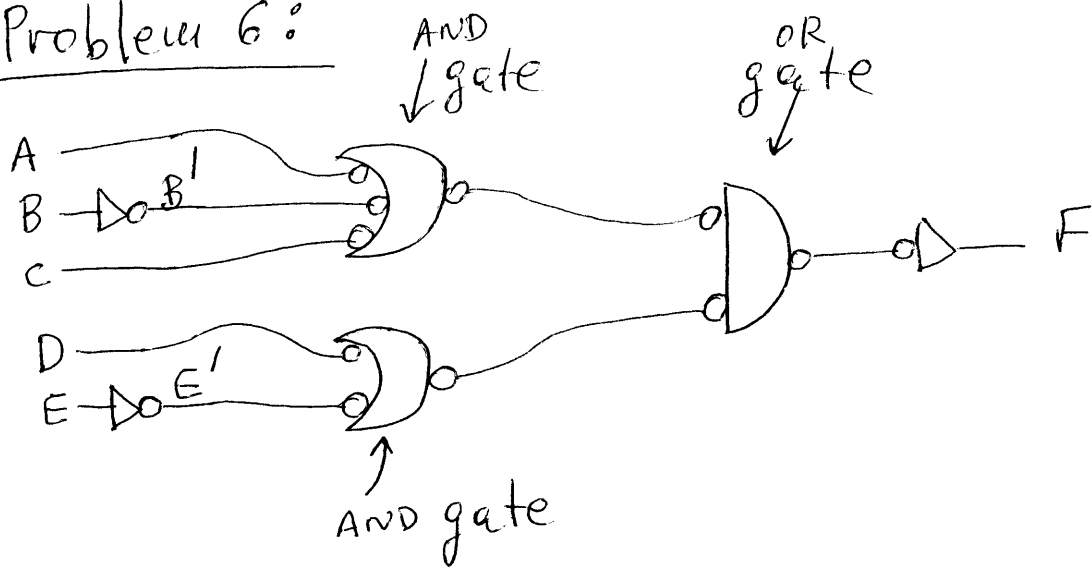


Fig 2a: The equivalent AND-OR logic circuit for F.

### Problem 7:

(a) Proof of (5) or proof of  $X \oplus 0 = X$

- Case  $X=0$  :  $0 \oplus 0 = 0$
- Case  $X=1$  :  $1 \oplus 0 = 1$

(b) Proof of (6) or proof of  $X \oplus 1 = X'$

- Case  $X=0$  :  $0 \oplus 1 = 1$
- Case  $X=1$  :  $1 \oplus 1 = 0$

(c) Proof of (7) or proof of  $X \oplus X = 0$

- Case  $X=0$  :  $0 \oplus 0 = 0$
- Case  $X=1$  :  $1 \oplus 1 = 0$

(d) Proof of (8) or proof of  $X \oplus X' = 1$

- Case  $X=0$  :  $0 \oplus 1 = 1$
- Case  $X=1$  :  $1 \oplus 0 = 1$

## Problem 7 cont.

(11)

Note: Eqs. (5), (6), (7), (8) can also be proved by using eq. (1) on top of page 5 of handout # 11.

(e) Proof of (11) or proof of

$$X \cdot (Y \oplus Z) = X \cdot Y \oplus X \cdot Z$$

The right handside of (11) is

$$X \cdot Y \oplus X \cdot Z = X \cdot Y \cdot (X \cdot Z)' + (X \cdot Y)' \cdot X \cdot Z =$$

$$= X \cdot Y \cdot (X' + Z') + (X' + Y') \cdot X \cdot Z =$$

$$= \cancel{X \cdot Y \cdot X'} + X \cdot Y \cdot Z' + \cancel{X' \cdot X \cdot Z} + Y' \cdot X \cdot Z =$$

$$= X \cdot Y \cdot Z' + X \cdot Y' \cdot Z = X \cdot (Y \cdot Z' + Y' \cdot Z)$$

$$= X \cdot (Y \oplus Z). \text{ But we have now reached}$$

the left side of (11) so the proof is completed.