

2720, Spring 06

Homework # 6 solutions

Homework # 6 Solutions

①

Problem 1: Let the inputs of the circuit be  $E_3, E_2, E_1, E_0$  representing the Excess-3 number. Let the outputs of the circuit be  $B_3, B_2, B_1, B_0$  representing the BCD number. Below I show the truth table.

$E_3$	$E_2$	$E_1$	$E_0$	$B_3$	$B_2$	$B_1$	$B_0$
0	0	0	0	d	d	d	d
0	0	0	1	d	d	d	d
0	0	1	0	d	d	d	d
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	1
0	1	0	1	0	0	1	0
0	1	1	0	0	0	1	1
0	1	1	1	0	1	0	0
1	0	0	0	0	1	0	1
1	0	0	1	0	1	1	0
1	0	1	0	0	1	1	1
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	1
1	1	0	1	d	d	d	d
1	1	1	0	d	d	d	d
1	1	1	1	d	d	d	d

} d means don't care

} d means don't care

From the above truth table, one can easily get the Karnaugh maps for the outputs  $B_3, B_2, B_1, B_0$ . These Karnaugh maps are shown on the next page.

Problem 1 cont:

		$E_1 E_0$			
		00	01	11	10
$E_3 E_2$	00	d	d		d
	01				
	11	1	d	1	d
	10			1	

From the Karnaugh map of fig. 1 we get the following expression for  $B_3$ :

$$B_3 = E_3 \cdot E_2 + E_3 \cdot E_1 \cdot E_0 \quad (1)$$

Fig. 1: Karnaugh map for output  $B_3$ .

		$E_1 E_0$			
		00	01	11	10
$E_3 E_2$	00	d	d		d
	01			1	
	11		d	1	d
	10	1	1		1

From the Karnaugh map of fig. 2 we get the following expression for  $B_2$ :

$$B_2 = E_2' \cdot E_1' + E_3 \cdot E_2' \cdot E_0' + E_2 \cdot E_1 \cdot E_0 \quad (2)$$

Fig. 2: Karnaugh map for output  $B_2$ .

		$E_1 E_0$			
		00	01	11	10
$E_3 E_2$	00	d	1		d
	01		1		1
	11		d	d	d
	10		1		1

From the Karnaugh map of fig. 3 we get the following expression for  $B_1$ :

$$B_1 = E_1' \cdot E_0 + E_1 \cdot E_0' = E_1 \oplus E_0 \quad (3)$$

Fig. 3: Karnaugh map for output  $B_1$ .

Problem 1 cont:

$E_1 E_0$		00	01	11	10
		$d$	$d$		$d$
$E_3 E_2$	00	$d$			$d$
	01	1			1
	11	1	$d$	$d$	$d$
	10	1			1

$E_0'$

From the Karnaugh map of Fig. 4 we get the following expression for  $B_0$ :

$$B_0 = E_0' \quad (4)$$

Fig. 4: Karnaugh map for output  $B_0$

From equations (1), (2), (3), (4) we get the following circuit shown in figure 5 below; (this is one possible realization).

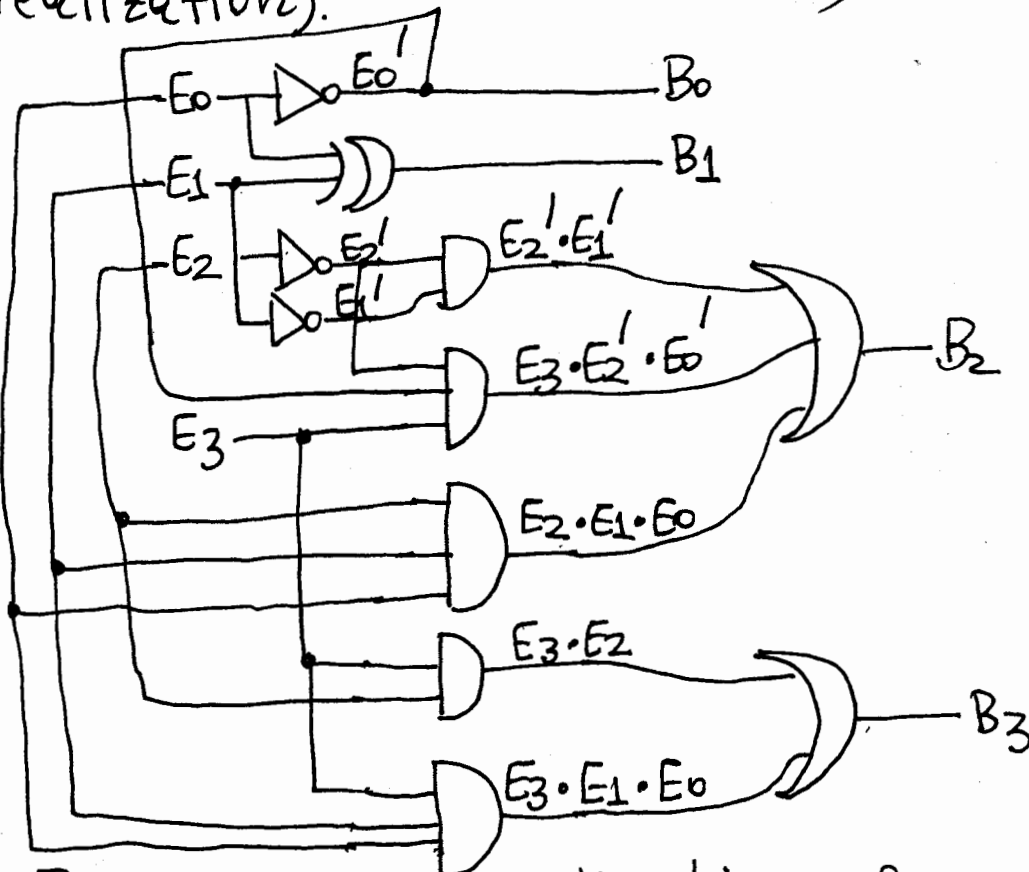


Fig. 5: Circuit realization of the Excess-3 to BCD converter.

HW#6 Solutions cont.

Problem 2: The inputs here are A, B, C and the outputs are X, Y, Z. Below I show the truth table.

A	B	C	X	Y	Z
0	0	0	0	1	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	0	1	1
1	1	0	1	0	0
1	1	1	1	0	1

From the truth table, one can easily get the Karnaugh maps for the outputs X, Y, Z. These Karnaugh maps are shown below:

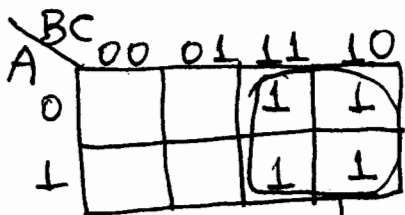


Fig. 1: Karnaugh map for output X

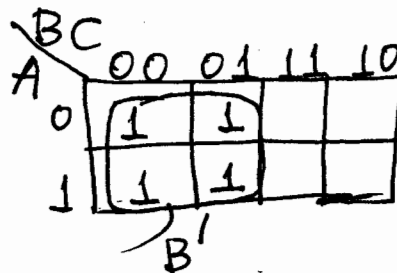


Fig. 2: Karnaugh map for output Y


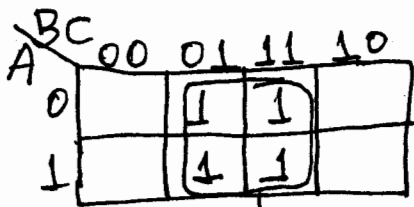


Fig. 3: Karnaugh map for output Z

From the Karnaugh maps of figures 1, 2, 3 we get the following expressions for X, Y, Z:

$$\begin{aligned}
 X &= B \quad (1) \\
 Y &= B' \quad (2) \\
 Z &= C \quad (3)
 \end{aligned}$$

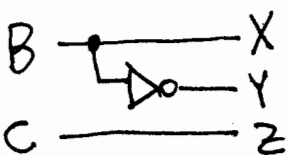From equations (1), (2), (3) above we get the following circuit:



Note: As seen, the circuit is very simple; it relies only on one inverter.

Fig. 4: Circuit realization for problem 2

Problem 3: Below I show the truth table.

X	Y	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

From the truth table, one can easily get the karnaugh maps for the outputs S, Cout. These karnaugh maps are shown below:

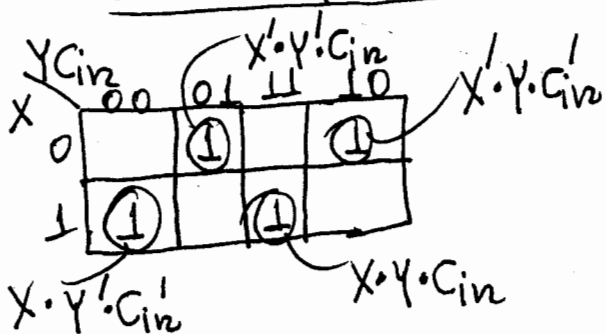


Fig. 1: Karnaugh map for output S

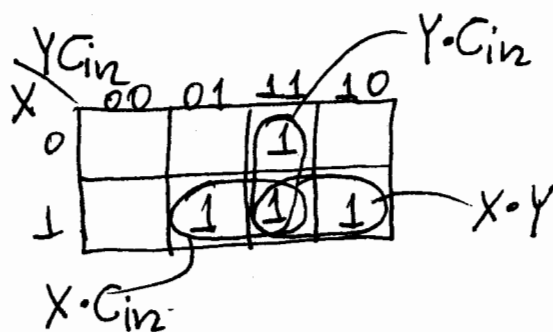



Fig. 2: Karnaugh map for output Cout.

From the karnaugh maps of figures 1 & 2 above, we get the following expressions for S and Cout:

$$S = X'Y'Cin + X'Y.Cin + X.Y'Cin + X.Y.Cin \quad (1)$$

$$Cout = X.Y + X.Cin + Y.Cin \quad (2)$$

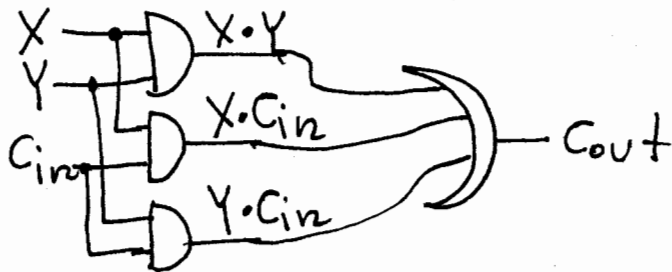From equations (1), (2) above we get the following AND-OR realization for the full adder:



The rest of the figure showing the output S is on the next page.

EE 2720  
 HW #6 solutions cont.

Problem 3 cont:

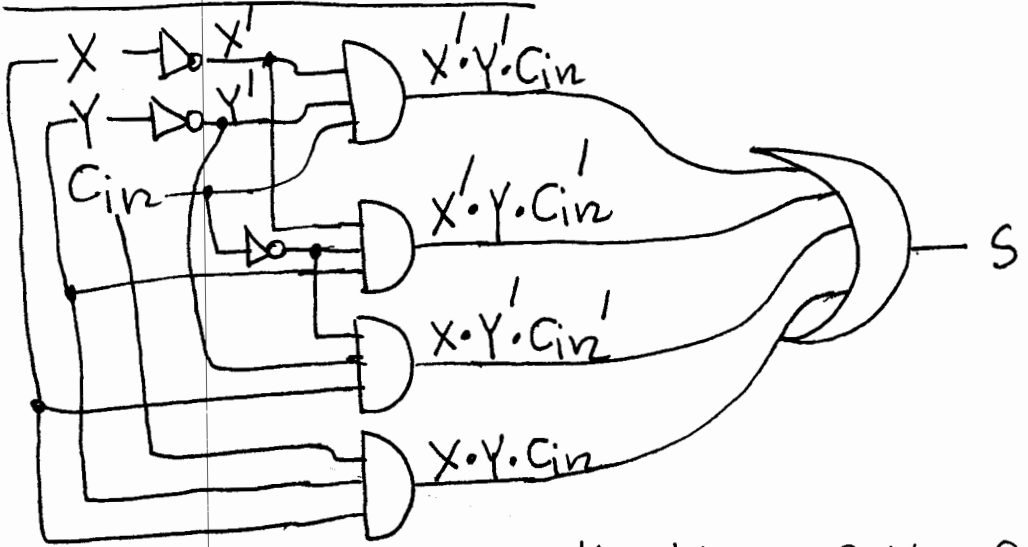


Fig. 3: AND-OR realization of the full adder.

Note: The expression of  $S$  provided in equation (1) cannot be simplified at all. It is a canonical sum actually;  $S = \sum x_i y_i C_{in} (1, 2, 4, 7)$ . As seen from the Karnaugh map of Fig. 1, we cannot combine any cells containing 1's. (The same is true for cells containing 0's). Question: Can you provide another expression for  $S$ ?

Problem 4: Below I show the truth table

X	Y	S	Cout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

→ From the truth table, one can easily get the Karnaugh maps for the outputs  $S$ ,  $Cout$  shown below:

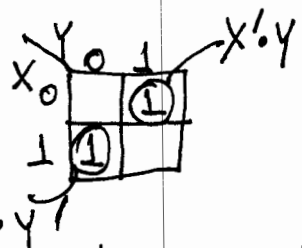


Fig. 1: Karnaugh map for output  $S$

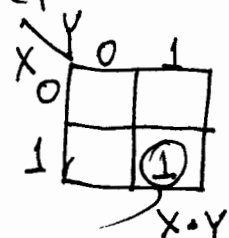


Fig. 2: Karnaugh map for output  $Cout$

→ From the Karnaugh maps of figures 1, 2 we get the expressions:  
 $S = X' \cdot Y + X \cdot Y'$  (1)  
 $Cout = X \cdot Y$  (2)

HW # 6 Solutions cont.

Problem 4 cont: From equations (1), (2) of previous page we get the following AND-OR realization for the half adder:

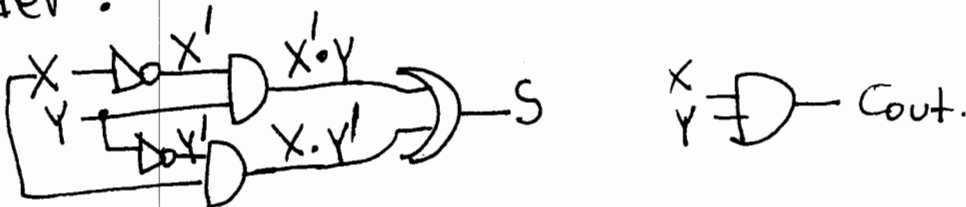


Fig. 3: AND-OR realization of the half adder.

Note: The expression of  $S$  provided by eq. (1) cannot be simplified at all. It is a canonical sum. As seen from the Karnaugh map of fig. 1, we cannot combine the two cells containing 1's; (they are not adjacent).

Note: This problem is so simple (trivial actually) that you don't need a truth table or Karnaugh map.

Problem 6:

wx \ yz	00	01	11	10
00		1		1
01	1		1	
11		1		1
10	1		1	

→ This function  $F$  can't be simplified at all. As seen from the Karnaugh map we can't combine any cells. So  $F$  is the given original expression which is a canonical sum, or  $F$  is

$F = \sum_{w,x,y,z} (1, 3, 4, 7, 8, 11, 13, 14)$ . I hope you can now write an algebraic expression for  $F$ , but even if you give me this as an answer, it is OK.

Problem 7: The Karnaugh maps and the respective simplified sum-of-products expressions are shown on the next page.

Problem 7 cont:

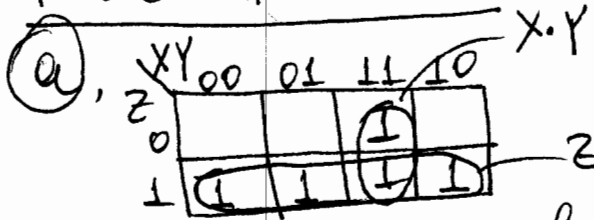


Fig. 1: Karnaugh map for  $F = \sum_{x,y,z} (1,3,5,6,7)$

From the Karnaugh map of Fig. 1 we get the following simplified sum-of-product expression for F:  
 $F = z + x \cdot y$  (1); (this is the minimal sum by the way)

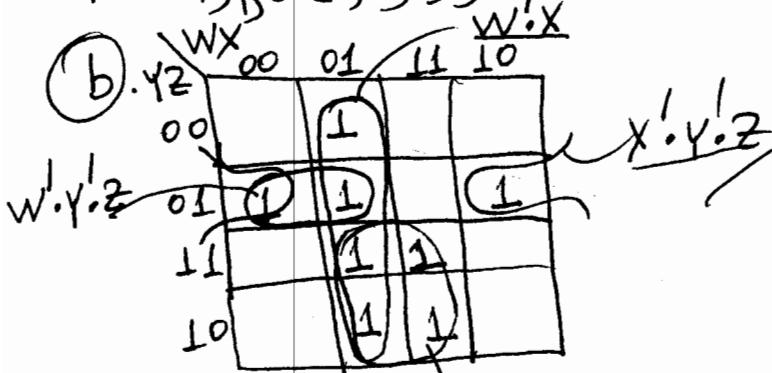


Fig. 2: Karnaugh map for  $F = \sum_{w,x,y,z} (1,4,5,6,7,9,14,15)$

From the Karnaugh map of Fig. 2 we get the following simplified sum-of-products expression for F:  
 $F = w' \cdot x + x' \cdot y' \cdot z + x \cdot y + w' \cdot y' \cdot z$  (2)

(this is not the minimal sum. Can you find the minimal sum?).

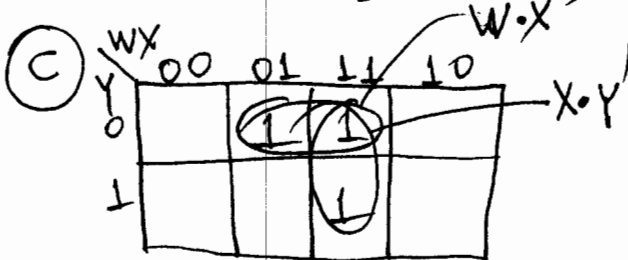


Fig. 3: Karnaugh map for  $F = \prod_{w,x,y} (0,1,3,4,5)$

$F = \prod_{w,x,y} (0,1,3,4,5) = \sum_{w,x,y} (2,6,7)$

From the Karnaugh map of Fig. 3 we get the following simplified sum-of-products expression for F:  
 $F = w \cdot x + x \cdot y'$  (3); (this is the minimal sum by the way).

Go to next page →

Problem 7 cont:

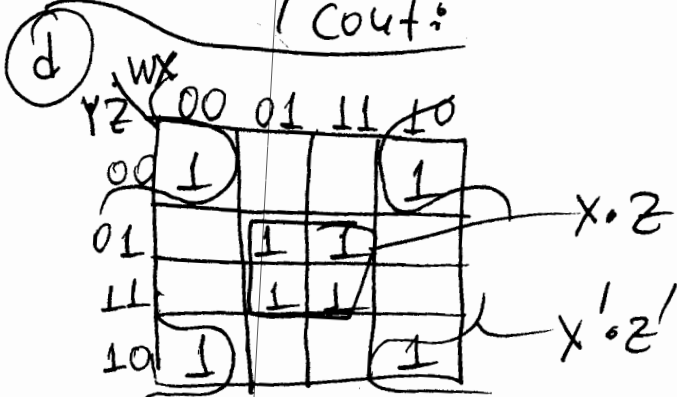


Fig. 4: karnaugh map for  $F = \sum w, x, y, z (0, 3, 5, 7, 8, 10, 13, 15)$

From the karnaugh map of fig. 4, we get the following simplified sum-of-products expression for F:  
 $F = x \cdot z + x' \cdot z'$  (this is the minimal sum by the way)

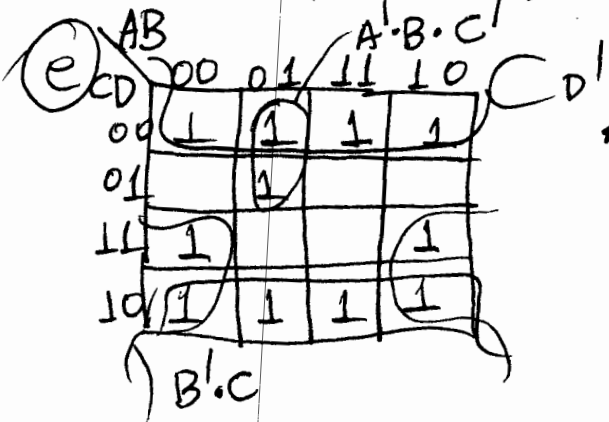


Fig. 5: karnaugh map for  $F = \prod A, B, C, D (1, 3, 9, 13, 15)$

$F = \prod A, B, C, D (1, 3, 9, 13, 15) = \sum A, B, C, D (0, 2, 3, 4, 5, 6, 8, 10, 11, 12, 14)$

From the karnaugh map of fig. 5, we get the following simplified sum-of-products expression for F:  
 $F = D' + B' \cdot C + A \cdot B \cdot C'$  (this is the minimal sum).

Problem 8:

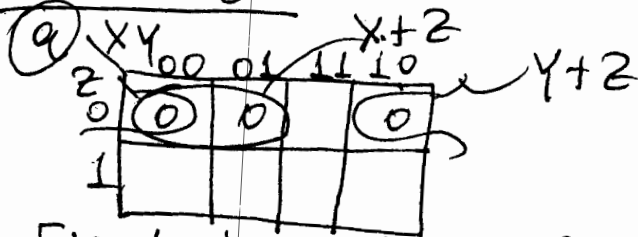


Fig. 1: karnaugh map for  $F = \sum x, y, z (1, 3, 5, 6, 7)$

From the karnaugh map of fig. 1, we get the following simplified product-of-sums expression for F:

$F = (x+z) \cdot (y+z)$  (this is the minimal product by the way).

Problem 8 cont:

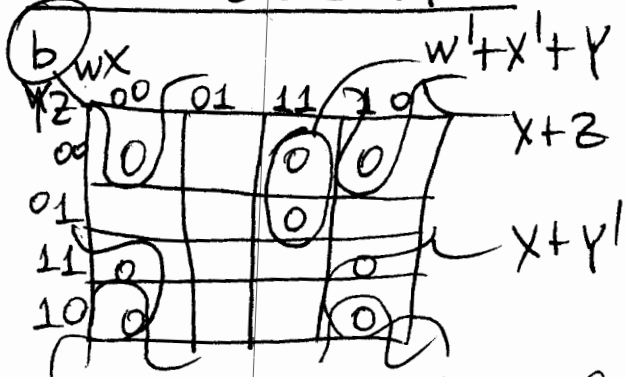


Fig. 2: Karnaugh map for  $F = \sum_{w,x,y,z} (1, 4, 5, 6, 7, 9, 14, 15)$

From the Karnaugh map of Fig. 2, we get the following simplified product-of-sums expression for  $F$ :  
 $F = (x + z) \cdot (x + y') \cdot (w' + x' + y)$   
 (this is the minimal product by the way).

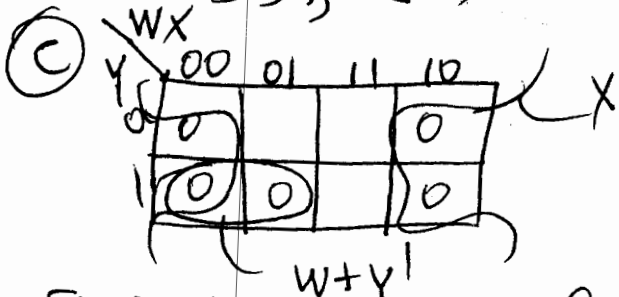


Fig. 3: Karnaugh map for  $F = \prod_{w,x,y} (0, 1, 3, 4, 5)$

From the Karnaugh map of Fig. 3, we get the following simplified product-of-sums expression for  $F$ :  
 $F = x \cdot (w + y')$   
 (this is the minimal product)

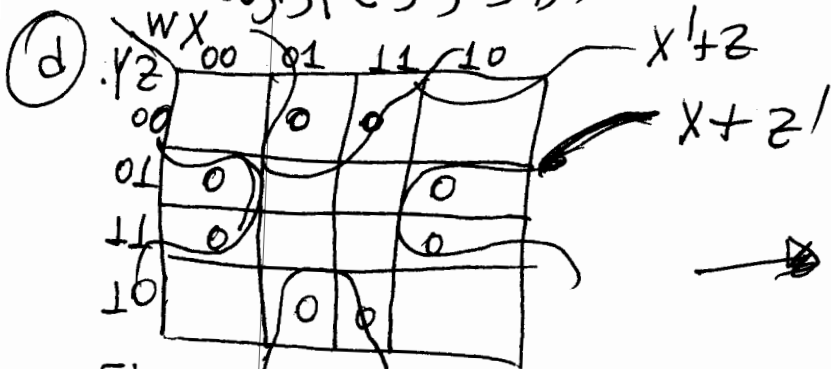


Fig. 4: Karnaugh map for  $F = \sum_{w,x,y,z} (0, 2, 5, 7, 8, 10, 13, 15)$

From the Karnaugh map of Fig. 4, we get the following simplified product-of-sums expression for  $F$ :  
 $F = (x' + z) \cdot (x + z')$   
 (this is the minimal product by the way).

Problem 8 cont:

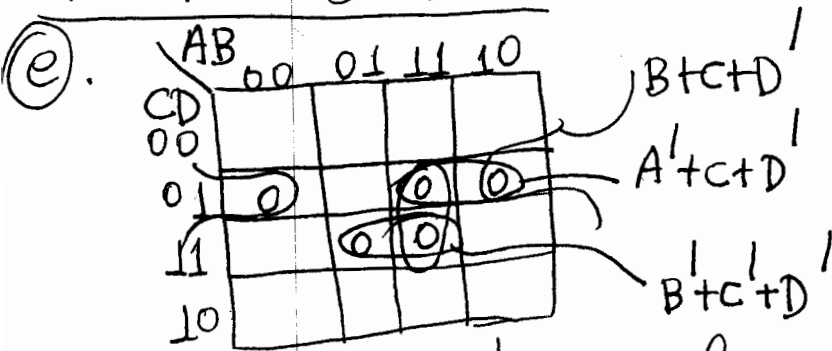


Fig. 5: Karnaugh map for  $F = \prod_{A,B,C,D} (1, 7, 9, 13, 15)$

From the Karnaugh map of fig. 5, we get the following simplified product-of-sums expression for F:  $F = (B+C+D') \cdot (B'+C'+D') \cdot (A'+C+D')$  (5); (this is a minimal product). You can also get another minimal product. Can you get it?

Problem 9:

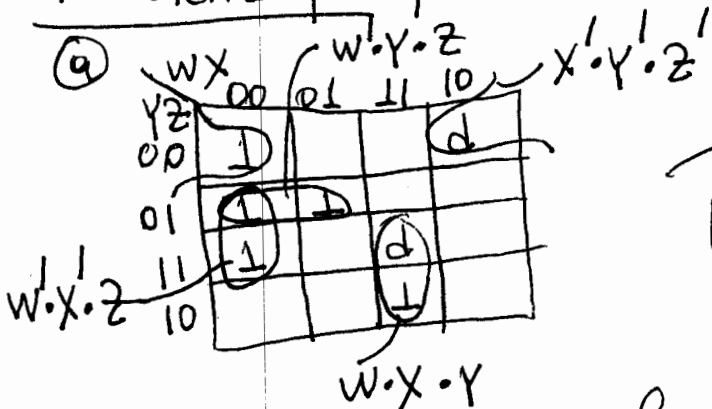


Fig. 1: Karnaugh map for  $F = \sum_{w,x,y,z} (0, 1, 3, 5, 14) + d(8, 15)$

From the Karnaugh map of fig. 1, we get the following simplified sum-of-products expression for F:  $F = w' \cdot y' \cdot z + w' \cdot x' \cdot z + w \cdot x \cdot y + x' \cdot y' \cdot z'$  (1); (this is a minimal sum). You can also get one more minimal sum.


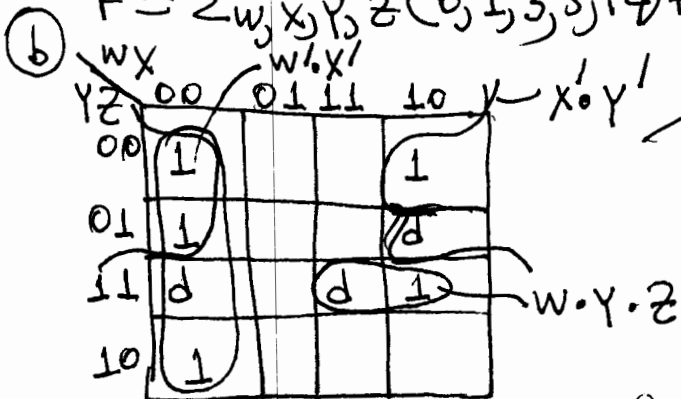


Fig. 2: Karnaugh map for  $F = \sum_{w,x,y,z} (0, 1, 2, 8, 11) + d(3, 9, 15)$


From the Karnaugh map of fig. 2 we get the following:  $F = w' \cdot x' + x' \cdot y' + w \cdot y \cdot z$  (2); (this is a minimal sum). You can get two more minimal sums. Can you get them?

Problem 9 cont:

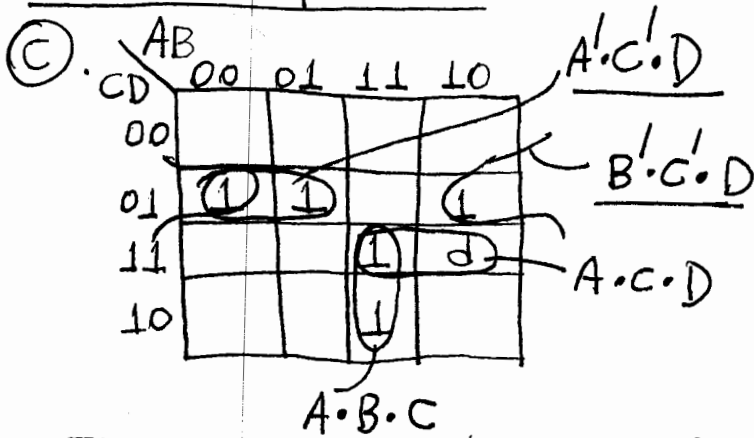

From the Karnaugh map of Fig. 3, we get the following:  
 $F = A \cdot B \cdot C + A \cdot C \cdot D + B \cdot C \cdot D + A \cdot C \cdot D + A \cdot C \cdot D + A \cdot C \cdot D$  (3);  
 (the above is not a minimal sum. Can you find a minimal sum?)


Fig. 3: Karnaugh map for  $F = \sum_{A,B,C,D} (1,5,9,14,15) + d(4)$

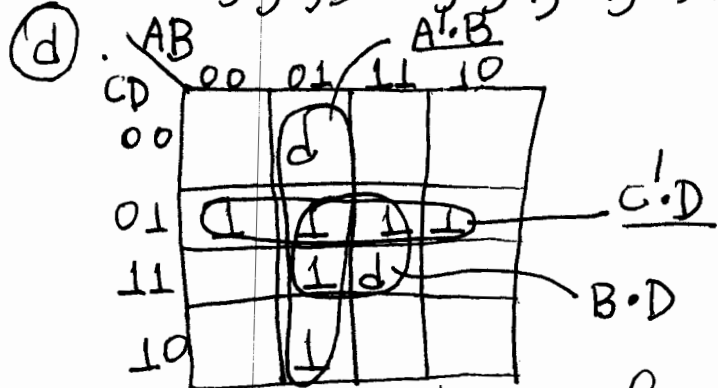

From the Karnaugh map of Fig. 4, we get the following:  
 $F = A \cdot B + C \cdot D + B \cdot D$  (4);  
 (the above is not a minimal sum. Can you find a minimal sum?)

Fig. 4: Karnaugh map for  $F = \sum_{A,B,C,D} (1,5,6,7,9,13) + d(4,15)$

Problem 10:

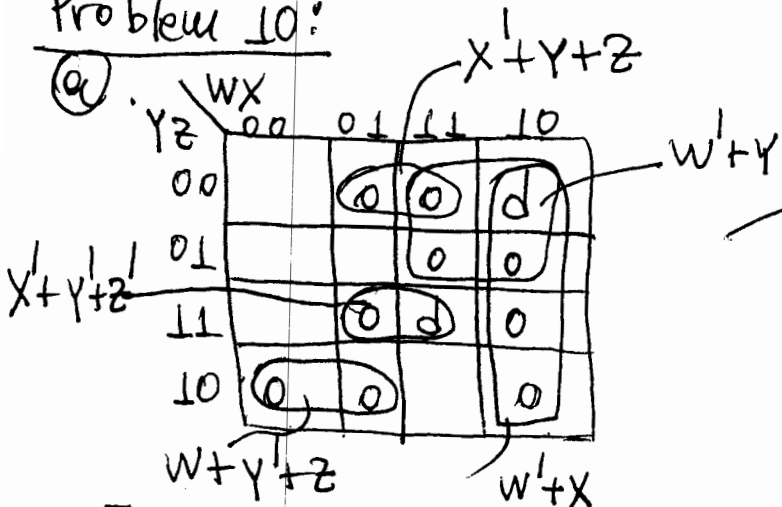

From the Karnaugh map of Fig. 1, we get the following:  
 $F = (X + Y + Z) \cdot (W + Y) \cdot (W + X) \cdot (W + Y + Z) \cdot (X + Y + Z)$  (1);  
 (the above is not a minimal product)

Fig. 1: Karnaugh map for  $F = \sum_{W,X,Y,Z} (0,1,3,5,14) + d(8,15)$

Problem 10 cont:

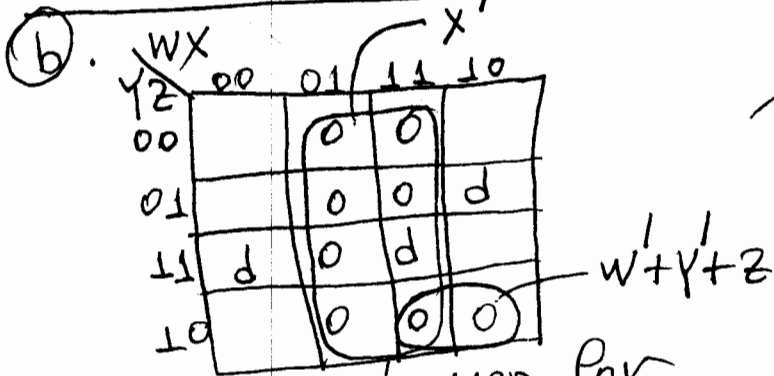


Fig. 2: Karnaugh map for  $F = \sum_{w,x,y,z} (0,1,3,8,11) + d(3,9,15)$

From the Karnaugh map of Fig. 2, we get the following:  
 $F = x' \cdot (w' + y' + z)$ ; (this expression is a minimal product).

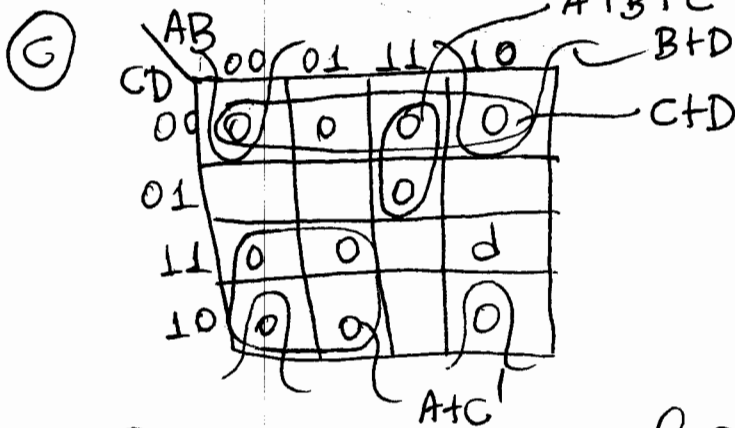


Fig. 3: Karnaugh map for  $F = \sum_{A,B,C,D} (1,5,9,14,15) + d(11)$

From the Karnaugh map of Fig. 3, we get the following:  
 $F = (A' + B' + C) \cdot (B + D) \cdot (C + D)$ .  
 $(A + C)$ ; (this is a minimal product).

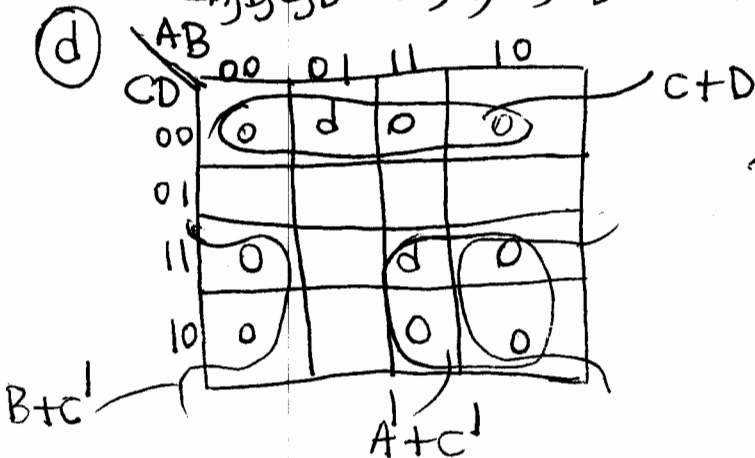


Fig. 4: Karnaugh map for  $F = \sum_{A,B,C,D} (1,5,6,7,9,13) + d(4,15)$

From the Karnaugh map of Fig. 4, we get the following:  
 $F = (C + D) \cdot (A + C') \cdot (B + C')$ ; (the above expression is a minimal product).  
 You can get two more minimal products. Can you get them?

## Problem 11:

$a_3 a_2$	00	01	11	10
$a_1 a_0$	00	0	d	0
01			d	0
11			d	d
10		0	d	d

$a_1 + a_0$  (circled in top row)  
 $a_3'$  (circled in bottom row)  
 $a_2' + a_0$  (circled in bottom-left cell)

From the Karnaugh map of Fig. 1 we get the following:

$$F = a_3' \cdot (a_2' + a_0) \cdot (a_1 + a_0)$$

(1); (the above is a minimal product)

Fig. 1: Karnaugh map for the prime BCD-digit detector showing 0's and d's.

Note: This HW was a little bit time consuming but I think it was lots of fun!! So I hope you enjoyed it!! The next HW, (if we have one) is not going to be test time consuming. We will definitely have one more HW, but I might not grade it. However, like always, I will post the solutions of it.