

EE 2720, Spring 05

~~Solutions of Homework #7~~

Solutions of Test #2

EE 2720, Spring 05, Test 2 Solutions (1)

Problem 1: $X \cdot Y + X' \cdot Z + Y \cdot Z =$
 $X \cdot Y + X' \cdot Z + 1 \cdot YZ = X \cdot Y + X' \cdot Z + (X + X') \cdot Y \cdot Z =$
 $= X \cdot Y + X' \cdot Z + X \cdot Y \cdot Z + X' \cdot Y \cdot Z =$
 $= \underbrace{X \cdot Y + X \cdot Y \cdot Z} + \underbrace{X' \cdot Z + X' \cdot Z \cdot Y} =$
 $= X \cdot Y \cdot (1 + Z) + X' \cdot Z \cdot (1 + Y) =$
 $= X \cdot Y \cdot 1 + X' \cdot Z \cdot 1 = X \cdot Y + X' \cdot Z \Rightarrow \text{proven}$

Problem 2: Apply theorem of eq. (2) first to get:

$$(A+B+C') \cdot (A'+B'+D) \cdot (A'+C+D') \cdot (A+C'+D) =$$
$$= (A+C'+B) \cdot (A+C'+D) \cdot (A'+B'+D) \cdot (A'+C+D') =$$
$$= (A+C'+B \cdot D) \cdot [A'+(CB'+D) \cdot (C+D')] =$$
$$= (A+C'+B \cdot D) \cdot [A'+(CD+B') \cdot (CD'+C)]$$

Now apply theorem of eq. (3) on

$(CD+B') \cdot (CD'+C)$ to get:

$$(A+C'+B \cdot D) \cdot (A'+D \cdot C+D' \cdot B')$$

); (apply theorem of eq (3) again).
); (now apply theorem of eq (1))

$$= A \cdot (D \cdot C + D' \cdot B') + A' (C' + B \cdot D)$$

↳ next page →

EE 2720, Spring 05, Test 2 solutions (2)

Problem 2 cont:

$$= A \cdot D \cdot C + A \cdot D' \cdot B' + A' \cdot C' + A' \cdot B \cdot D.$$

If we were to multiply out using only theorems of eq. (1), we would generate $3 \times 3 \times 3 \times 3 = 81$ product terms and would have to eliminate 77 of them!! (too much work and not easy). Here I only got 4 terms

Problem 3:

$$F = X + X' \cdot Y + Y \cdot Z'$$

$$= X \cdot \underbrace{(Y + Y')} \cdot \underbrace{(Z + Z')} + X' \cdot Y \cdot \underbrace{(Z + Z')} + Y \cdot Z' \cdot \underbrace{(X + X')}$$

$$= X \cdot (Y \cdot Z + Y \cdot Z' + Y' \cdot Z + Y' \cdot Z') + X' \cdot Y \cdot Z + X' \cdot Y \cdot Z' + X \cdot Y \cdot Z' + X \cdot Y \cdot Z' =$$

$$= X \cdot Y \cdot Z + X \cdot Y \cdot Z' + X \cdot Y' \cdot Z + X \cdot Y' \cdot Z'$$

$$+ X' \cdot Y \cdot Z + X' \cdot Y \cdot Z' + \cancel{X \cdot Y \cdot Z'} + \cancel{X' \cdot Y \cdot Z}$$

$$= \underset{1}{X} \cdot \underset{1}{Y} \cdot \underset{1}{Z} + \underset{1}{X} \cdot \underset{1}{Y} \cdot \underset{0}{Z'} + \underset{1}{X} \cdot \underset{0}{Y'} \cdot \underset{1}{Z} + \underset{1}{X} \cdot \underset{0}{Y'} \cdot \underset{0}{Z'} + \underset{0}{X'} \cdot \underset{1}{Y} \cdot \underset{1}{Z}$$

$$+ \underset{0}{X'} \cdot \underset{1}{Y} \cdot \underset{0}{Z'} = \sum_{X,Y,Z} (2, 3, 4, 5, 6, 7)$$

Problem 4: $F = (X' + Y) \cdot (X + Z')$

$$= (X' + Y + \underbrace{Z \cdot Z'}_0) \cdot (X + Z' + \underbrace{Y \cdot Y'}_0) \cdot (Y' + Z + \underbrace{X \cdot X'}_0)$$

$$= (X' + Y + Z) \cdot (X' + Y + Z') \cdot (X + Z' + Y) \cdot (X + Z' + Y')$$

$$(Y' + Z + X) \cdot (Y' + Z + X') =$$

$$= (X' + Y + Z) \cdot (X' + Y + Z') \cdot (X + Y + Z') \cdot (X + Y' + Z')$$

$$\cdot (X + Y' + Z) \cdot (X' + Y' + Z) = \prod_{x,y,z} (1, 2, 3, 4, 5, 6)$$

$\begin{matrix} \text{1} & \text{0} & \text{0} & \text{1} & \text{0} & \text{1} & \text{0} & \text{0} & \text{1} & \text{0} & \text{1} & \text{1} & \text{0} \\ \text{0} & \text{1} & \text{0} & \text{1} & \text{1} & \text{0} & & & & & & & \end{matrix}$

Problem 5: (a) Using the graphical approach:
 I will first provide a figure showing an OR-AND realization of F from where I will get the figure that shows the realization using only NOR gates

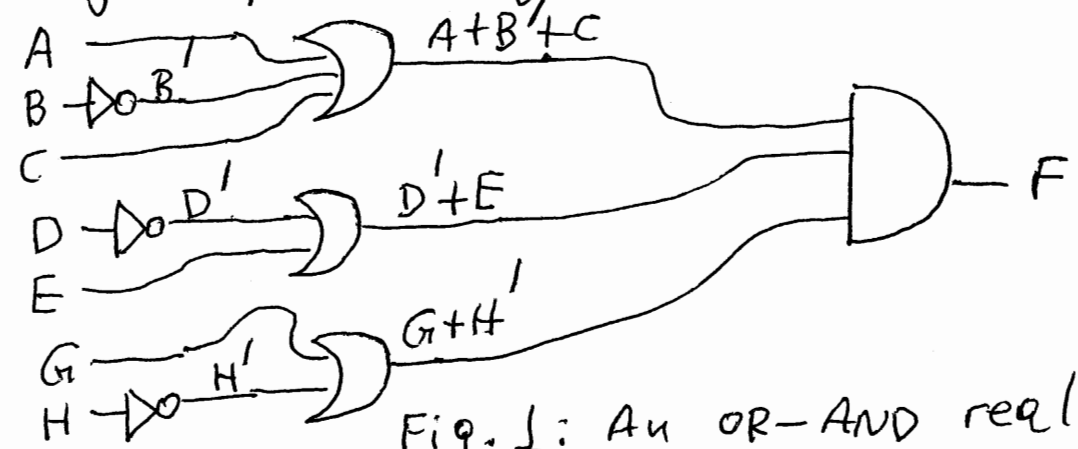


Fig. 1: An OR-AND realization of F

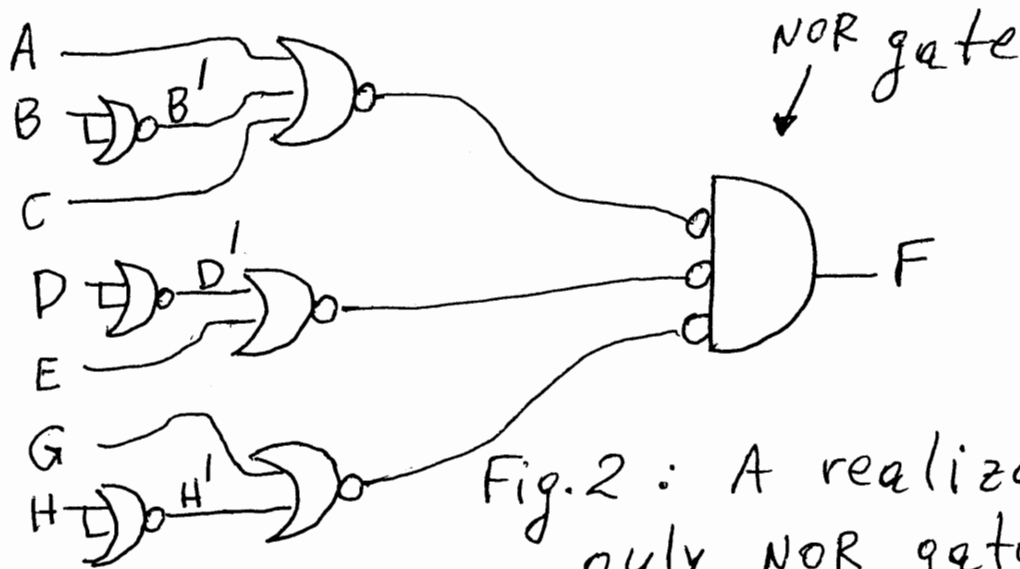


Fig. 2: A realization of F using only NOR gates.

(b) Using the algebraic approach: we have:

$$\begin{aligned}
 F &= (A+B'+C) \cdot (CD'+E) \cdot (G+H') \\
 &= \left[\left[(A+B'+C) \cdot (CD'+E) \cdot (G+H') \right]' \right]' \\
 &= \left[(A+B'+C)' + (CD'+E)' + (G+H')' \right]' \quad (1)
 \end{aligned}$$

From the above eq. (1) we get the following realization shown below.


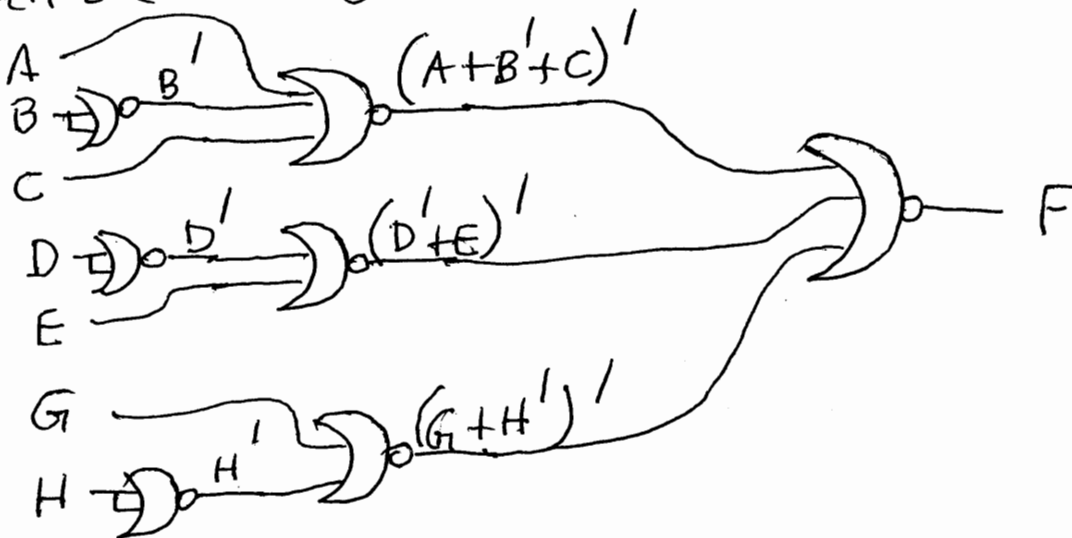


Fig 3: Realization of F using only NOR gates.


Problem 6:

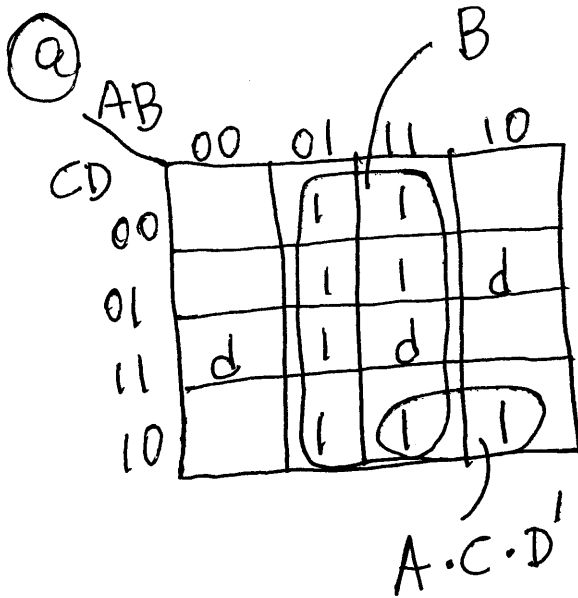

From this Karnaugh map we get the following simplified sum-of-products expression for

F:

$$F = B + A \cdot C \cdot D'$$

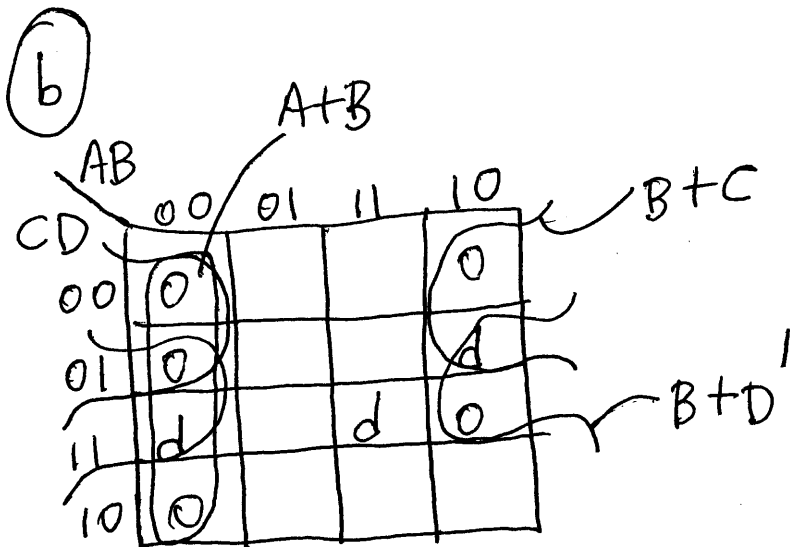

From this Karnaugh map we get the following simplified product-of-sums expression for F:

$$F = (A+B) \cdot (B+C) \cdot (B+D')$$

Note: Points $\rightarrow (16+20+16+16+16+16)$ pts = 100 pts