

EE 2720, Fall 2010

Homework #4 solution

EE 2720  
 Homework # 4 Solutions

(1)

Problem 1: Let the inputs of the circuit be  $E_3, E_2, E_1, E_0$  representing the Excess-3 number. Let the outputs of the circuit be  $B_3, B_2, B_1, B_0$  representing the BCD number. Below I show the truth table.

$E_3$	$E_2$	$E_1$	$E_0$	$B_3$	$B_2$	$B_1$	$B_0$
0	0	0	0	d	d	d	d
0	0	0	1	d	d	d	d
0	0	1	0	d	d	d	d
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	1
0	1	0	1	0	0	1	0
0	1	1	0	0	0	1	1
0	1	1	1	0	1	0	0
1	0	0	0	0	1	0	1
1	0	0	1	0	1	1	0
1	0	1	0	0	1	1	1
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	1
1	1	0	1	d	d	d	d
1	1	1	0	d	d	d	d
1	1	1	1	d	d	d	d

} d means don't care

} d means don't care

From the above truth table, one can easily get the Karnaugh maps for the outputs  $B_3, B_2, B_1, B_0$ . These Karnaugh maps are shown on the next page.

Problem 1 cont:

	$E_1 E_0$	00	01	11	10
$E_3 E_2$	00	d	d		d
	01				
	11	1	d	d	d
	10			1	

From the Karnaugh map of fig. 1 we get the following expression for  $B_3$ :

$$B_3 = E_3 \cdot E_2 + E_3 \cdot E_1 \cdot E_0 \quad (1)$$

Fig. 1: Karnaugh map for output  $B_3$ .

	$E_1 E_0$	00	01	11	10
$E_3 E_2$	00	d	d		d
	01			1	
	11		d	d	d
	10	1	1		1

From the Karnaugh map of fig. 2 we get the following expression for  $B_2$ :

$$B_2 = E_2' \cdot E_1' + E_3 \cdot E_2' \cdot E_0' + E_2 \cdot E_1 \cdot E_0 \quad (2)$$

Fig. 2: Karnaugh map for output  $B_2$ .

	$E_1 E_0$	00	01	11	10
$E_3 E_2$	00	d	d		d
	01		1		1
	11		d	d	d
	10		1		1

From the Karnaugh map of fig. 3 we get the following expression for  $B_1$ :

$$B_1 = E_1' \cdot E_0 + E_1 \cdot E_0' = E_1 \oplus E_0 \quad (3)$$

Fig. 3: Karnaugh map for output  $B_1$ .

Problem 1 cont:

	$E_1 E_0$	00	01	11	10
$E_3 E_2$	00	d	d		d
	01	1			1
	11	1	d	d	d
	10	1			1
		$E_0'$			

From the Karnaugh map of Fig. 4 we get the following expression for  $B_0$ :  
 $B_0 = E_0'$  (4).

Fig. 4: Karnaugh map for output  $B_0$

From equations (1), (2), (3), (4) we get the following circuit shown in figure 5 below; (this is one possible realization).

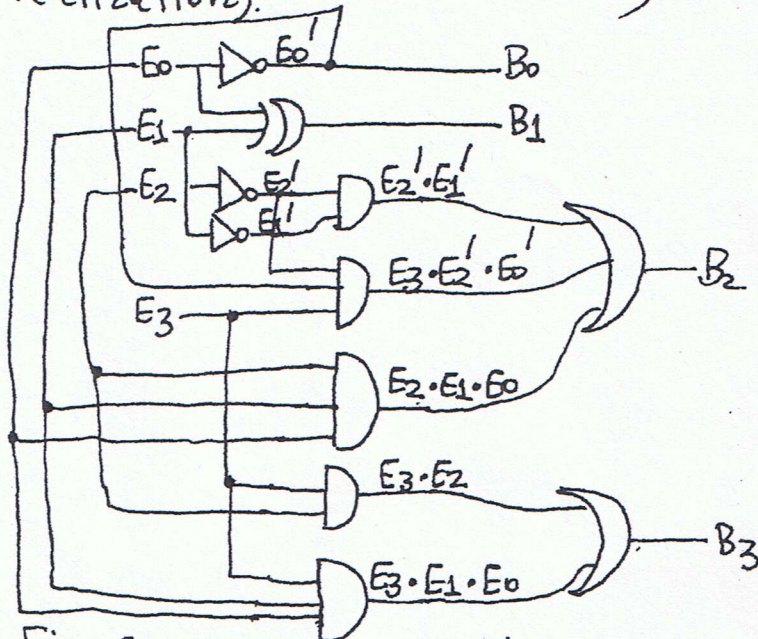


Fig. 5: Circuit realization of the Excess-3 to BCD converter.

HW#4 Solutions cont.

Problem 2: The inputs here are A, B, C and the outputs are X, Y, Z. Below I show the truth table.

ABC	X	Y	Z
000	0	1	0
001	0	1	1
010	1	0	0
011	1	0	1
100	0	1	0
101	0	1	1
110	1	0	0
111	1	0	1

From the truth table, one can easily get the Karnaugh maps for the outputs X, Y, Z. These Karnaugh maps are shown below:

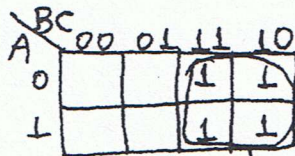


Fig. 1: Karnaugh map for output X

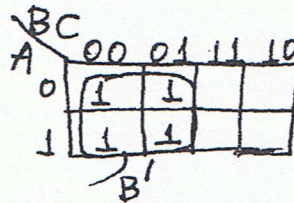


Fig. 2: Karnaugh map for output Y

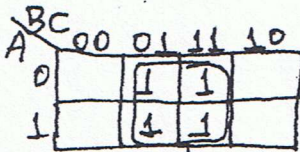


Fig. 3: Karnaugh map for output Z

From the Karnaugh maps of figures 1, 2, 3 we get the following expressions for X, Y, Z:

$$X = B \quad (1)$$

$$Y = B' \quad (2)$$

$$Z = C \quad (3)$$

From equations (1), (2), (3) above we get the following circuit:

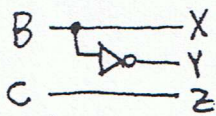


Fig. 4: Circuit realization for problem 2

Note: As seen, the circuit is very simple; it relies only on one inverter.

Problem 3: Below I show the truth table.

X	Y	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

→ From the truth table, one can easily get the karnaugh maps for the outputs S, Cout. These karnaugh maps are shown below:

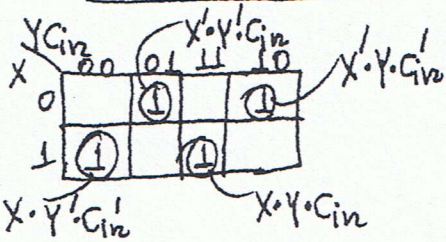


Fig. 1: Karnaugh map for output S

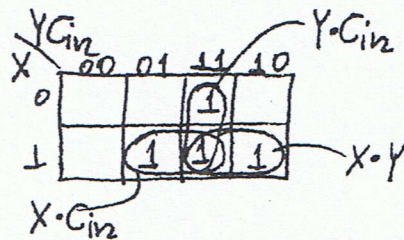



Fig. 2: Karnaugh map for output Cout.

From the karnaugh maps of figures 1 & 2 above, we get the following expressions for S and Cout:

$$S = X'Y' Cin + X'Y Cin + X Y' Cin + X Y Cin \quad (1)$$

$$Cout = X Y + X Cin + Y Cin \quad (2)$$

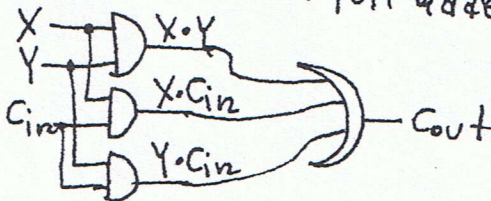From equations (1), (2) above we get the following AND-OR realization for the full adder:



The rest of the figure showing the output S is on the next page.

Problem 3 cont:

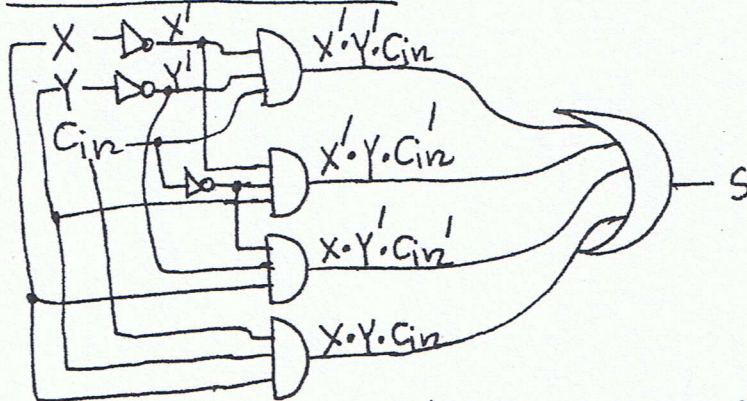




Fig. 3: AND-OR realization of the full adder.

Note: The expression of  $S$  provided in equation (1) cannot be simplified at all. It is a canonical sum actually:  $S = \sum x_i y_i c_{in} (1, 2, 4, 7)$ . As seen from the Karnaugh map of Fig. 1, we cannot combine any cells containing 1s. (The same is true for cells containing 0s). Question: Can you provide another expression for  $S$ ?

Problem 4: Below I show the truth table

X	Y	S	Cout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

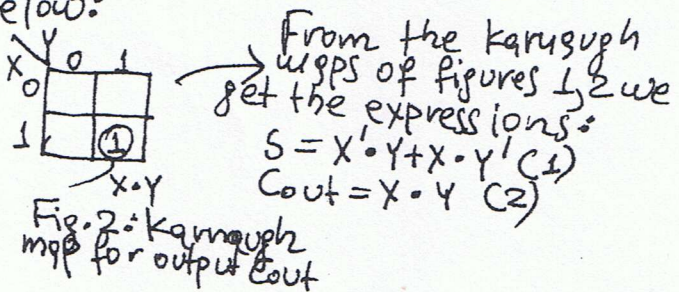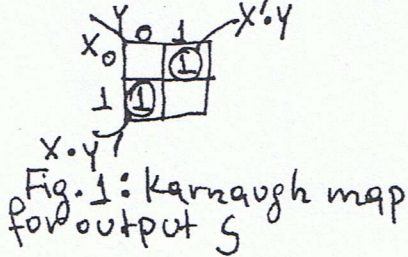→ From the truth table, one can easily get the Karnaugh maps for the outputs  $S$ ,  $Cout$  shown below:



→ From the Karnaugh maps of figures 1, 2 we get the expressions:  
 $S = X'Y + X.Y' (1)$   
 $Cout = X.Y (2)$

## HW # 4 Solutions cont.

Problem 4 cont: From equations (1), (2) of previous page we get the following AND-OR realization for the half adder:

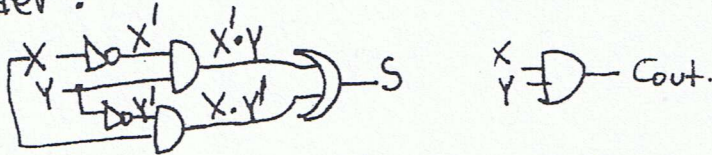


Fig. 3: AND-OR realization of the half adder.

Note: The expression of  $S$  provided by eq. (1) cannot be simplified at all. It is a canonical sum. As seen from the Karnaugh map of fig. 1, we cannot combine the two cells containing 1s; (they are not adjacent).

Note: This problem is so simple (trivial actually) that you don't need a truth table or Karnaugh map.

Problem 6:

wxyz	00	01	11	10
00		1		1
01	1		1	
11		1		1
10	1		1	

This function  $F$  can't be simplified at all. As seen from the Karnaugh map we can't combine any cells. So  $F$  is the given original expression which is a canonical sum, or  $F$  is

$F = \sum_{wxyz} (1, 3, 7, 8, 11, 13, 14)$ . I hope you can now write an algebraic expression for  $F$ , but even if you give me this as an answer, it is ok.

Problem 7: The Karnaugh maps and the respective simplified sum-of-products expressions are shown on the next page.

Problem 7 cont:

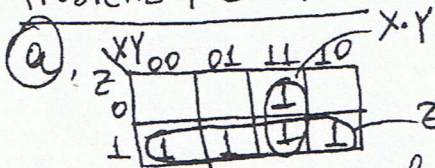


Fig. 1: Karnaugh map for  $F = \sum_{x,y,z} (1,3,5,6,7)$

From the Karnaugh map of Fig. 1 we get the following simplified sum-of-product expression for F:  
 $F = Z + X \cdot Y$  (1) ; (this is the minimal sum by the way)

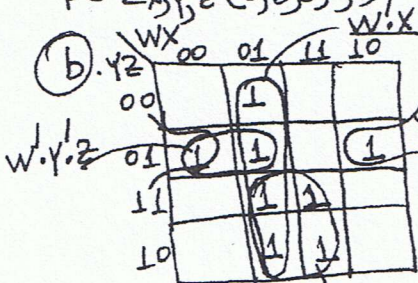


Fig. 2: Karnaugh map for  $F = \sum_{w,x,y,z} (1,4,5,6,7,9,14,15)$

From the Karnaugh map of Fig. 2 we get the following simplified sum-of-products expression for F:  
 $F = W \cdot X + X' \cdot Y' \cdot Z + X \cdot Y + W' \cdot Y' \cdot Z$  (2)

(this is not the minimal sum. Can you find the minimal sum?).

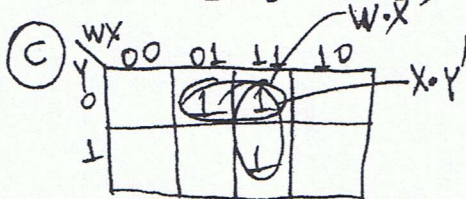


Fig. 3: Karnaugh map for  $F = \prod_{w,x,y} (0,1,3,4,5)$

$$F = \prod_{w,x,y} (0,1,3,4,5) = \sum_{w,x,y} (2,6,7)$$

From the Karnaugh map of Fig. 3 we get the following simplified sum-of-products expression for F:  
 $F = W \cdot X + X \cdot Y'$  (3) ; (this is the minimal sum by the way).

↳ Go to next page →

Problem 7 cont:

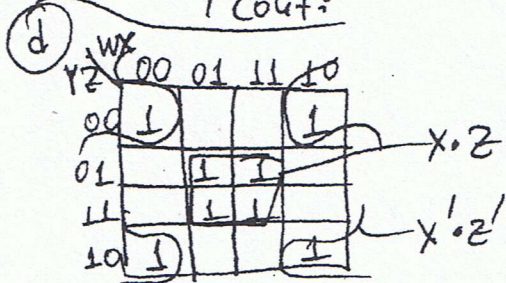


Fig. 4: karnaugh map for  $F = \sum_{w,x,y,z} (0, 3, 5, 7, 8, 10, 13, 15)$

From the karnaugh map of Fig. 4, we get the following simplified sum-of-products expression for F:  
 $F = x \cdot z + x' \cdot z'$  (4); (this is the minimal sum by the way)

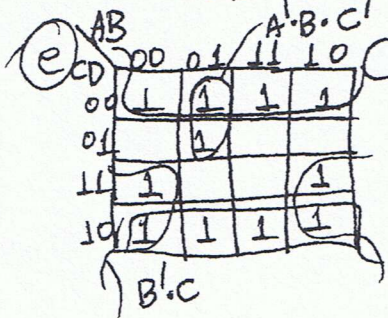


Fig. 5: karnaugh map for  $F = \prod_{A,B,C,D} (1, 3, 9, 13, 15)$

$F = \prod_{A,B,C,D} (1, 3, 9, 13, 15) = \sum_{A,B,C,D} (0, 2, 3, 4, 5, 6, 8, 10, 11, 14, 15)$

From the karnaugh map of Fig. 5, we get the following simplified sum-of-products expression for F:  
 $F = D + B \cdot C + A' \cdot B \cdot C'$  (5); (this is the minimal sum).

Problem 8:

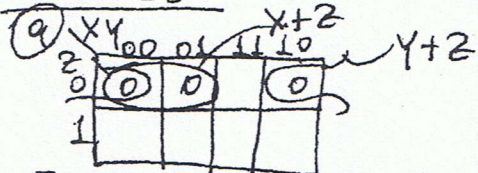


Fig. 1: karnaugh map for  $F = \sum_{x,y,z} (1, 3, 5, 6, 7)$

From the karnaugh map of Fig. 1, we get the following simplified product-of-sums expression for F

$F = (x+z) \cdot (y+z)$  (1); (this is the minimal product by the way).

Problem 8 cont:

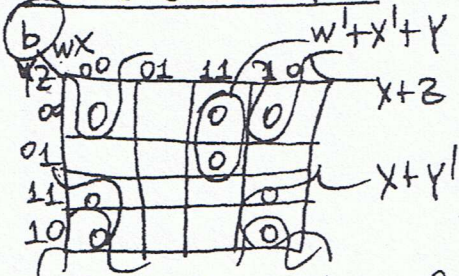


Fig. 2: Karnaugh map for  $F = \sum_{w,x,y,z} (4, 5, 6, 7, 9, 14, 15)$

From the Karnaugh map of Fig. 2, we get the following simplified product-of-sums expression for F:

$$F = (x+z) \cdot (x+y') \cdot (w'+x'+y)$$

(this is the minimal product by the way).

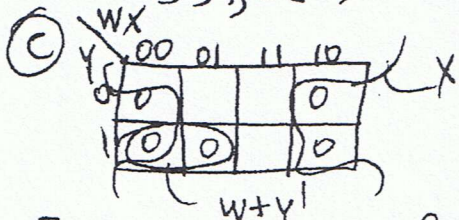


Fig. 3: Karnaugh map for  $F = \prod_{w,x,y} (0, 3, 4, 5)$

From the Karnaugh map of Fig. 3, we get the following simplified product-of-sums expression for F:

$$F = x \cdot (w+y')$$

(this is the minimal product)

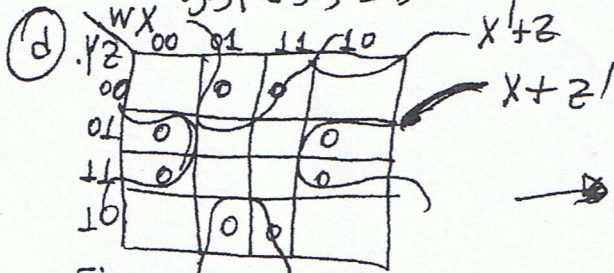


Fig. 4: Karnaugh map for  $F = \sum_{w,x,y,z} (0, 3, 5, 7, 8, 10, 13, 15)$

From the Karnaugh map of Fig. 4, we get the following simplified product-of-sums expression for F:

$$F = (x'+z) \cdot (x+z')$$

(this is the minimal product by the way).

Problem 8 cont:

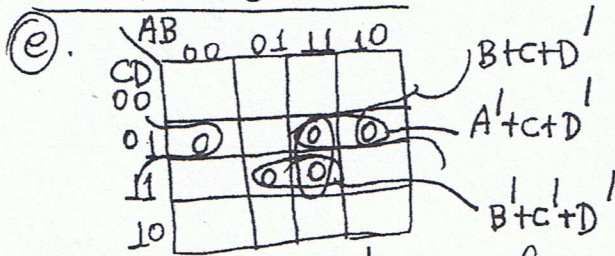


Fig. 5: Karnaugh map for  $F = \prod_{A,B,C,D} (1,7,9,13,15)$

From the Karnaugh map of fig. 5, we get the following simplified product-of-sums expression for F:  $F = (Btcd') \cdot (B'tcd') \cdot (A'tcd')$  (5); (this is a minimal product). You can also get another minimal product. Can you get it?

Problem 9:

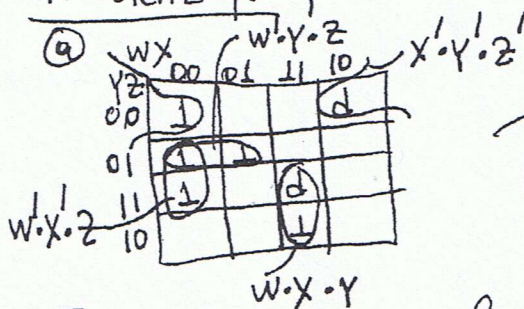


Fig. 1: Karnaugh map for  $F = \sum_{w,x,y,z} (1,3,5,14) + d(8,15)$

From the Karnaugh map of fig. 1, we get the following simplified sum-of-products expression for F:  $F = w'y'z + w'x'z + w'x'y + x'y'z'$  (4); (this is a minimal sum). You can also get one more minimal sum.

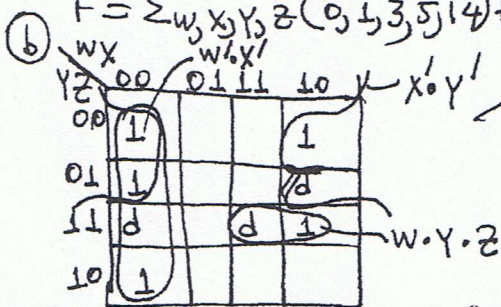


Fig. 2: Karnaugh map for  $F = \sum_{w,x,y,z} (0,1,2,8,11) + d(3,9,15)$

From the Karnaugh map of fig. 2 we get the following:  $F = w'x' + x'y' + w'y'z$  (2). (this is a minimal sum). You can get two more minimal sums. Can you get them?

Problem 9 cont:

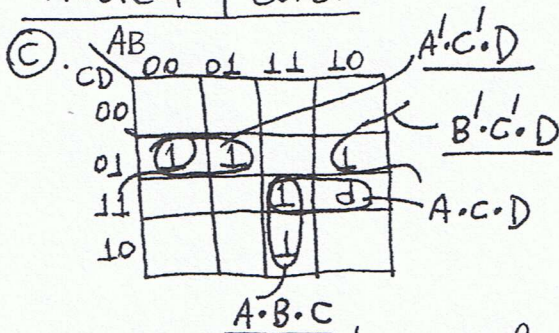


Fig. 3: Karnaugh map for  $F = \sum_{A,B,C,D} (1,5,9,14,15) + d(4,11)$

From the Karnaugh map of Fig. 3, we get the following:

$$F = A \cdot B \cdot C + A \cdot C \cdot D + B \cdot C \cdot D + A \cdot C \cdot D \quad (3)$$

(the above is not a minimal sum. Can you find a minimal sum?)

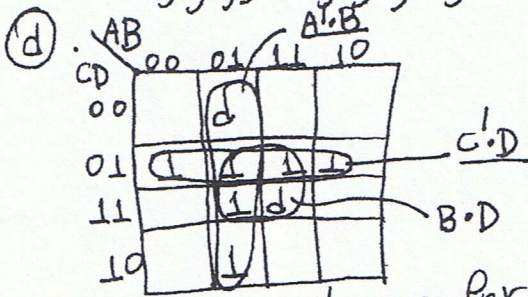


Fig. 4: Karnaugh map for  $F = \sum_{A,B,C,D} (1,5,6,7,9,13) + d(4,15)$

From the Karnaugh map of Fig. 4, we get the following:

$$F = A \cdot B + c \cdot D + B \cdot D \quad (4)$$

(the above is not a minimal sum. Can you find a minimal sum?)

Problem 10:

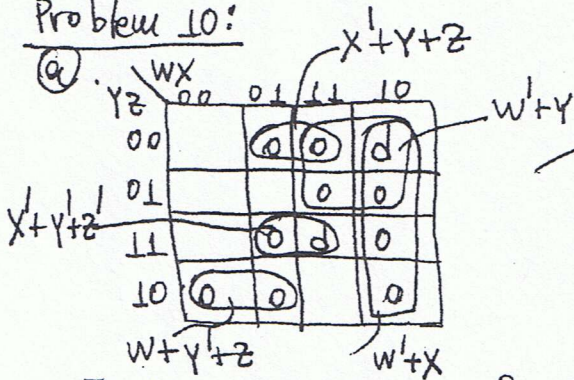



Fig. 1: Karnaugh map for  $F = \sum_{w,x,y,z} (0,1,3,5,14) + d(8,15)$

From the Karnaugh map of Fig. 1, we get the following:

$$F = (x+y+z) \cdot (w+y) \cdot (w+x) \cdot (w+y+z) \cdot (x+y+z) \quad (1)$$


(the above is not a minimal product)

Problem 10 cont:

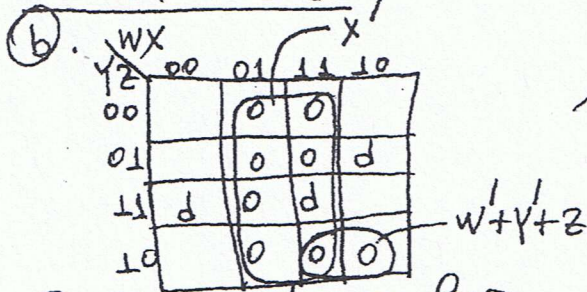


From the karnaugh map of fig. 2, we get the following  $F = x' \cdot (w'+y'+z)$  (2); this expression is a minimal product.

Fig. 2: karnaugh map for  $F = \sum_{w,x,y,z} (0,1,2,3,4) + d(3,9,15)$

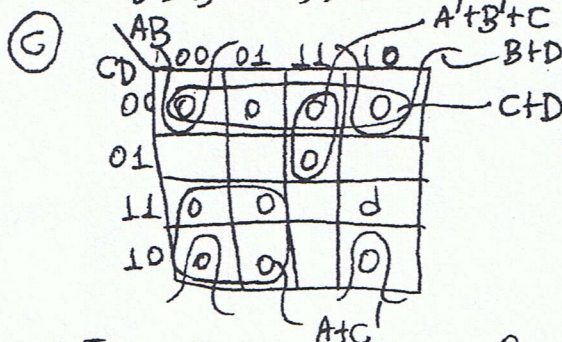

From the karnaugh map of fig. 3, we get the following:  $F = (A'+B'+C) \cdot (B+D) \cdot (C+D) \cdot (A+C)$  (3); this is a minimal product.

Fig. 3: karnaugh map for  $F = \sum_{A,B,C,D} (1,5,9,14,15) + d(11)$

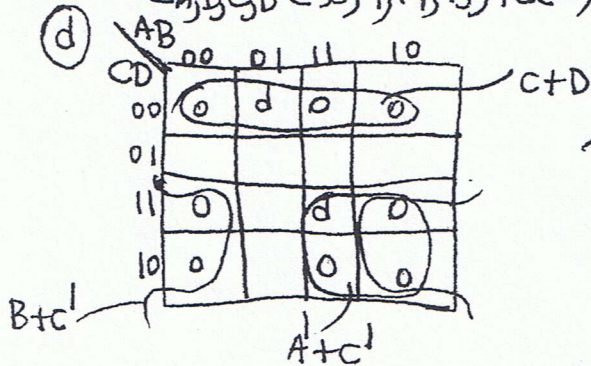

From the karnaugh map of fig. 4, we get the following:  $F = (C+D) \cdot (A+C') \cdot (B+C')$  (4); (the above expression is a minimal product).

Fig. 4: karnaugh map for  $F = \sum_{A,B,C,D} (1,5,7,9,13) + d(4,15)$

You can get two more minimal products. Can you get them?

