

EE 2720, Fall 2010


Homework # 7 and solution of HW # 7

Not to be returned; Cit will not be graded).

Homework # 7 and solution of HW# 7

Problem: Write an explicit structural Verilog description to implement $x = (a \oplus b) + c$. Here \oplus denotes EXCLUSIVE-OR operation and $+$ denotes OR operation. You are not allowed to instantiate one Exclusive-OR gate. Use AND, OR, NOT gates instead. Your module should be complete including module name, port list, declaration of inputs and outputs, declaration of wires and proper gate instantiation.

(b) Write an implicit structural Verilog description to implement $x = (a \oplus b) + c$.

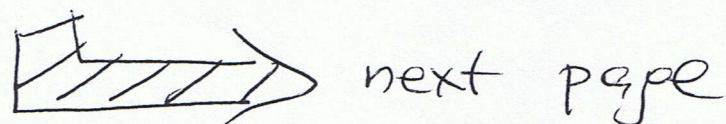 next page

HW#7 and solution of HW#7 cont.

Solution: (a) $x = (a \oplus b) + c = a' \cdot b + a \cdot b' + c$

```

module alex(x, a, b, c);
input a, b, c;
output x;
wire na, nb, na_b, a_nb;
not n1(na, a);
not n2(nb, b);
and a1(na_b, na, b);
and a2(a_nb, a, nb);
or o1(x, na_b, a_nb, c);
endmodule

```

```

(b) module george(x, a, b, c);
input a, b, c;
output x;
assign x = (a ^ b) | c;
endmodule

```