

EE 2720, Spr. 2011
Homework #5 solution


Note: Here in this homework I will denote minterm i by $\underline{m_i}$ and max-term i by $\underline{M_i}$.

Problem 1:

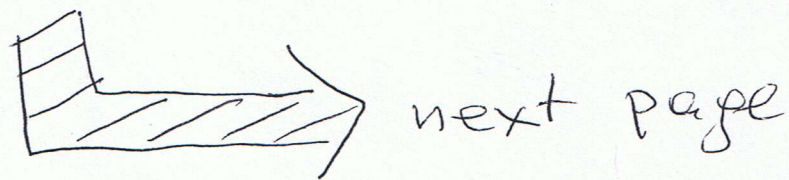
(a) we have

$$\begin{aligned}
 F &= \sum_{A,B,C,D} (1, 3, 5, 7, 8, 10, 12, 13, 14, 15) \\
 &= m_1 + m_3 + m_5 + m_7 + m_8 + m_{10} + m_{12} + m_{13} + m_{14} + m_{15} \\
 &= (m_1' \cdot m_3' \cdot m_5' \cdot m_7' \cdot m_8' \cdot m_{10}' \cdot m_{12}' \cdot m_{13}' \cdot m_{14}' \cdot m_{15}')' \\
 &= (M_1 \cdot M_3 \cdot M_5 \cdot M_7 \cdot M_8 \cdot M_{10} \cdot M_{12} \cdot M_{13} \cdot M_{14} \cdot M_{15})'
 \end{aligned}$$

From the above we get the figure shown on the next page



Pr. 1 (a) cont.:

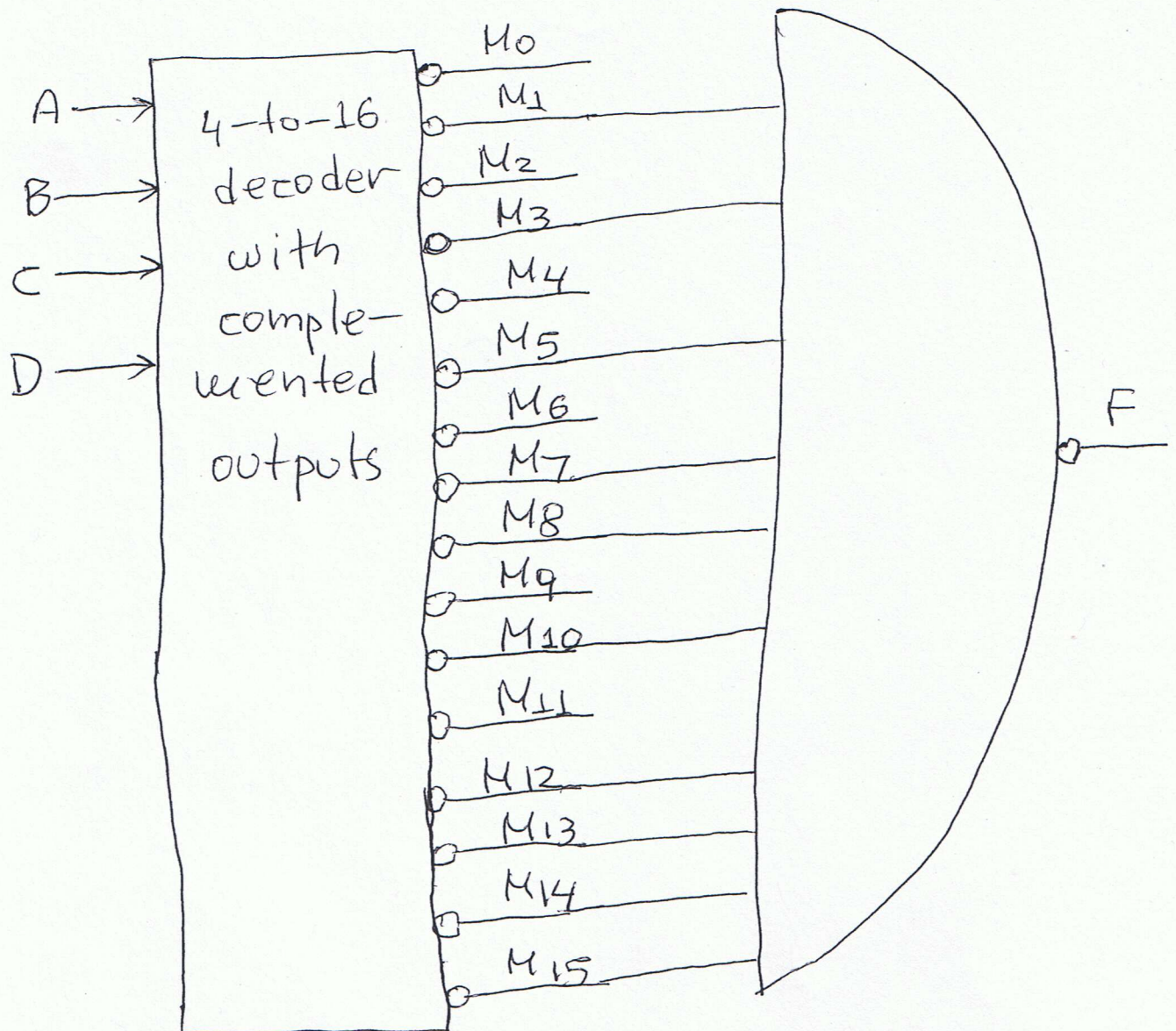


(b) We have

$$F = \sum_{A,B,C,D} (1, 3, 5, 7, 8, 10, 12, 13, 14, 15)$$

$= \prod_{A,B,C,D} (0, 2, 4, 6, 9, 11)$. From this we get the figure shown on the next page

next page


Pr. 1 (b) cont.:

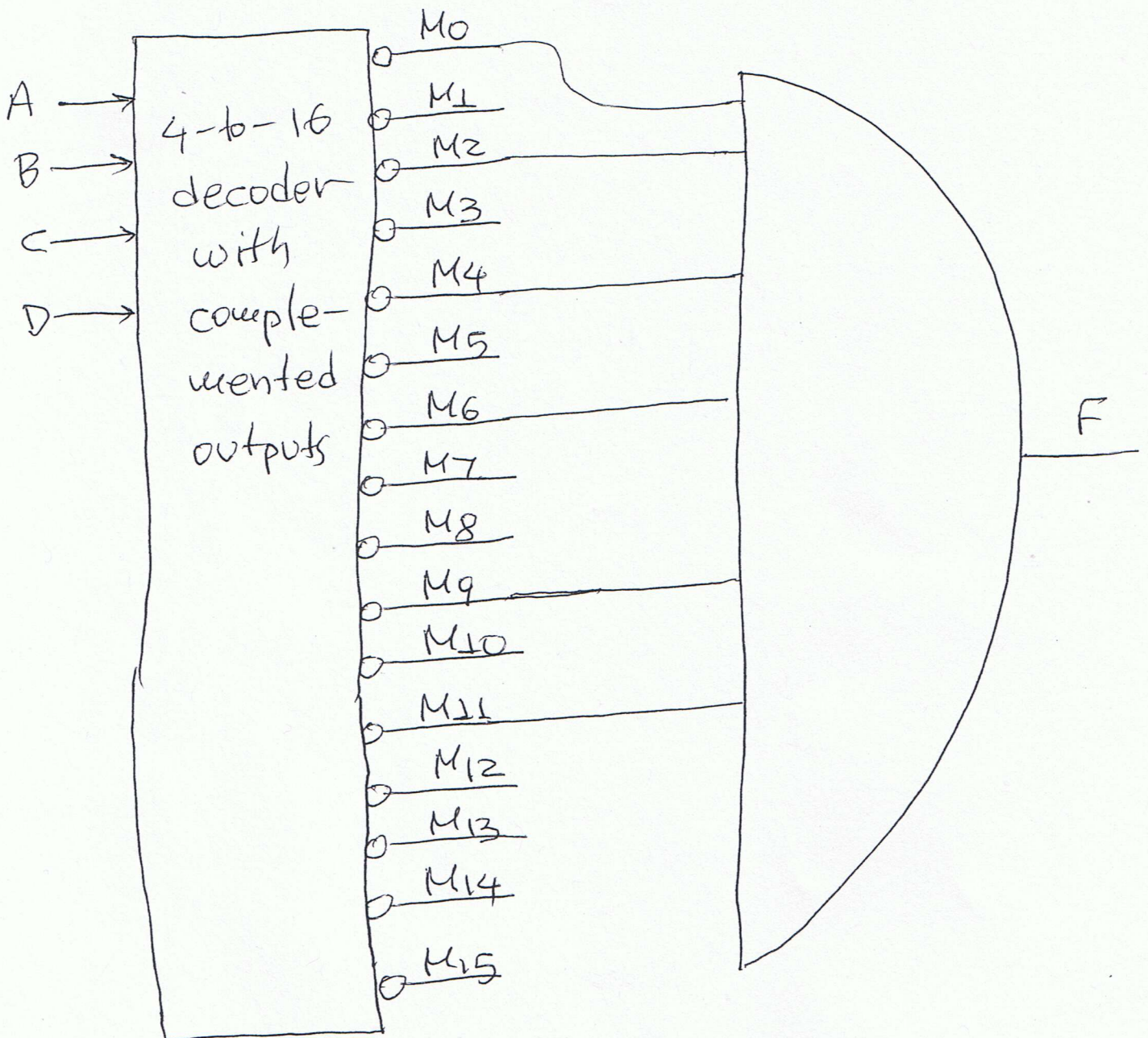

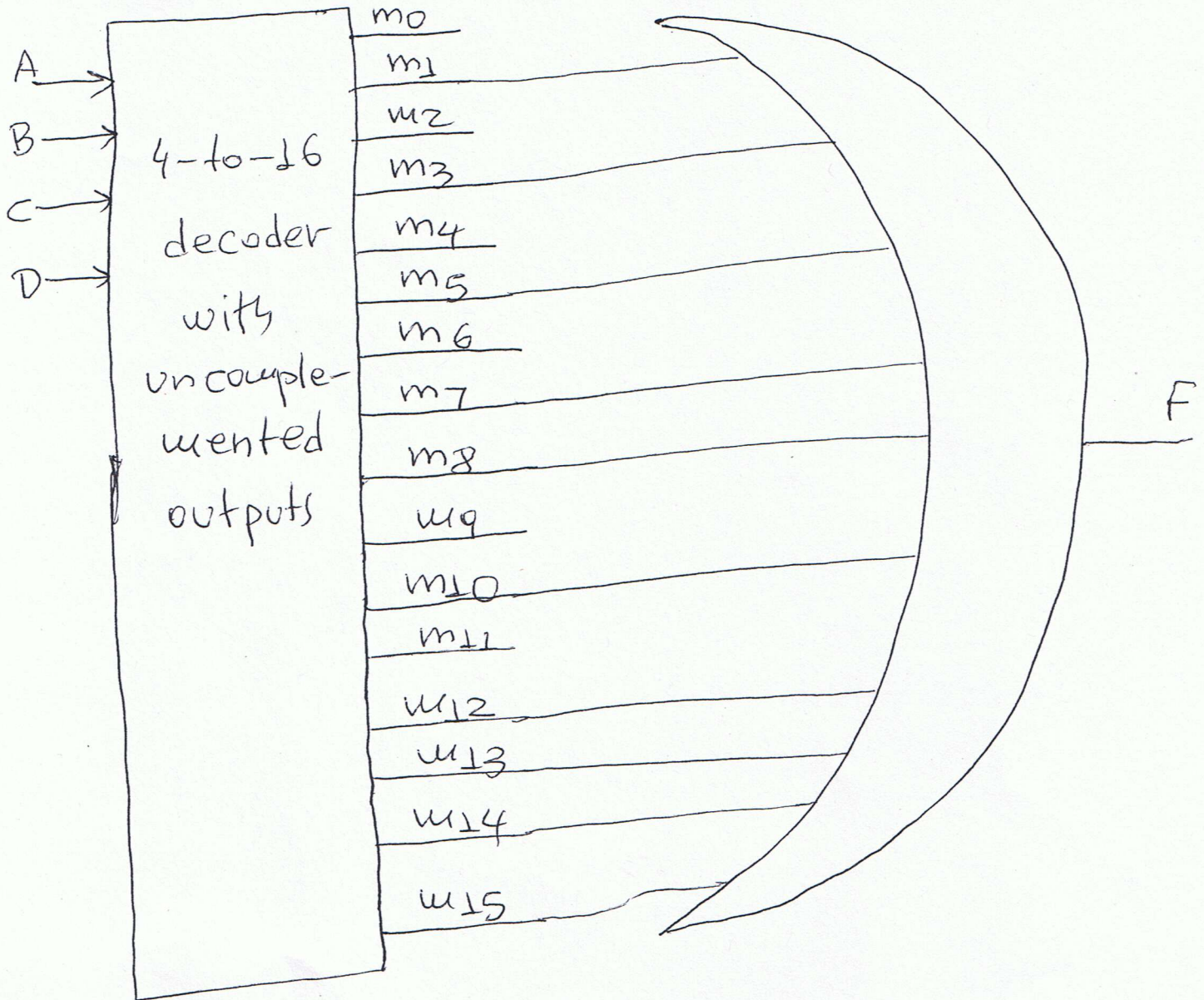(c) We have

$$F = \sum_{A,B,C,D} (1, 3, 5, 7, 8, 10, 12, 13, 14, 15)$$

From the above we get the figure shown below



(d) we have

$$F = \prod_{A,B,C,D} (0, 3, 4, 6, 9, 11)$$


$$= M_0 \cdot M_2 \cdot M_4 \cdot M_6 \cdot M_9 \cdot M_{11}$$

$$= (M_0' + M_2' + M_4' + M_6' + M_9' + M_{11}')'$$

$$= (m_0 + m_2 + m_4 + m_6 + m_9 + m_{11})'$$

From the above we get the figure shown on the next page.

Pr. 1(d) cont:

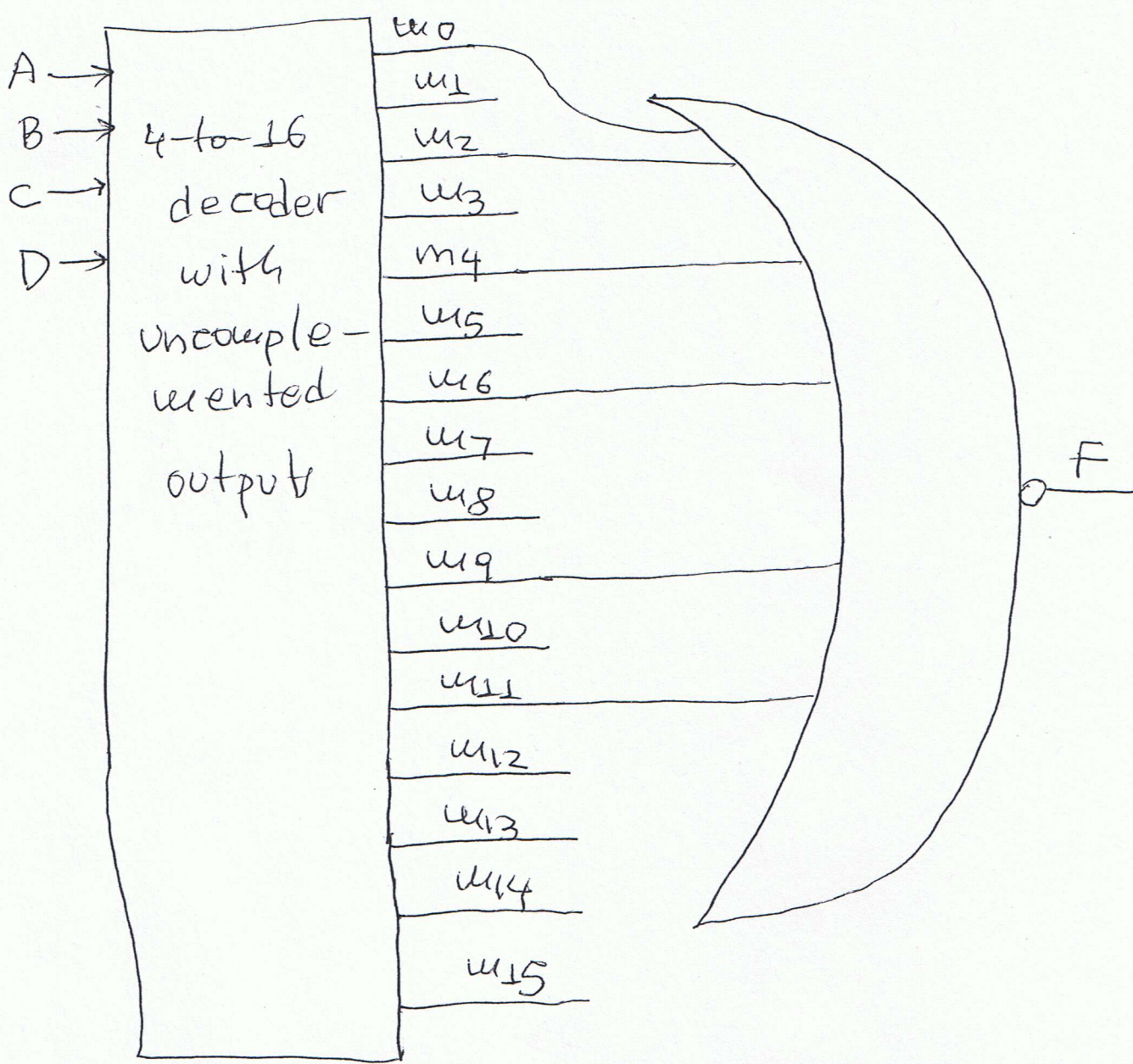

Problem 2: Since a decoder with uncomplemented outputs generates the minterms, we have to express F as a canonical sum. Since F is given as a product-of-sums expression, it is easier to obtain the canonical product from which we can easily get the canonical sum. We have:

$$F = (A+B'+C) \cdot (B'+C+D') \cdot (A'+C+D) =$$

$$(A+B'+C+D \cdot D') \cdot (B'+C+D'+A \cdot A') \cdot (A'+C+D+B \cdot B')$$

~~(A+B'+C+D) \cdot (B'+C+D')~~

$$= (A+B'+C+D) \cdot (A+B'+C+D') \cdot$$

$$(B'+C+D'+A) \cdot (B'+C+D'+A')$$

$$(A'+C+D+B) \cdot (A'+C+D+B')$$

~~(A+B'+C+D) \cdot (A+B'+C+D')~~

~~(A+B'+C+D) \cdot (A+B'+C+D')~~

$$(A+B'+C+D) \cdot (A+B'+C+D')$$


$$(A+B'+C+D) \cdot (A'+B'+C+D')$$

$$(A'+B+C+D) \cdot (A'+B'+C+D) =$$

Prob 2 cont

$$\prod_{A,B,C,D} (4,5, 8, 12, B)$$


= $\sum_{A,B,C,D} (0,1,2,3, 6,7, 9,10,11,14,15)$. We now have

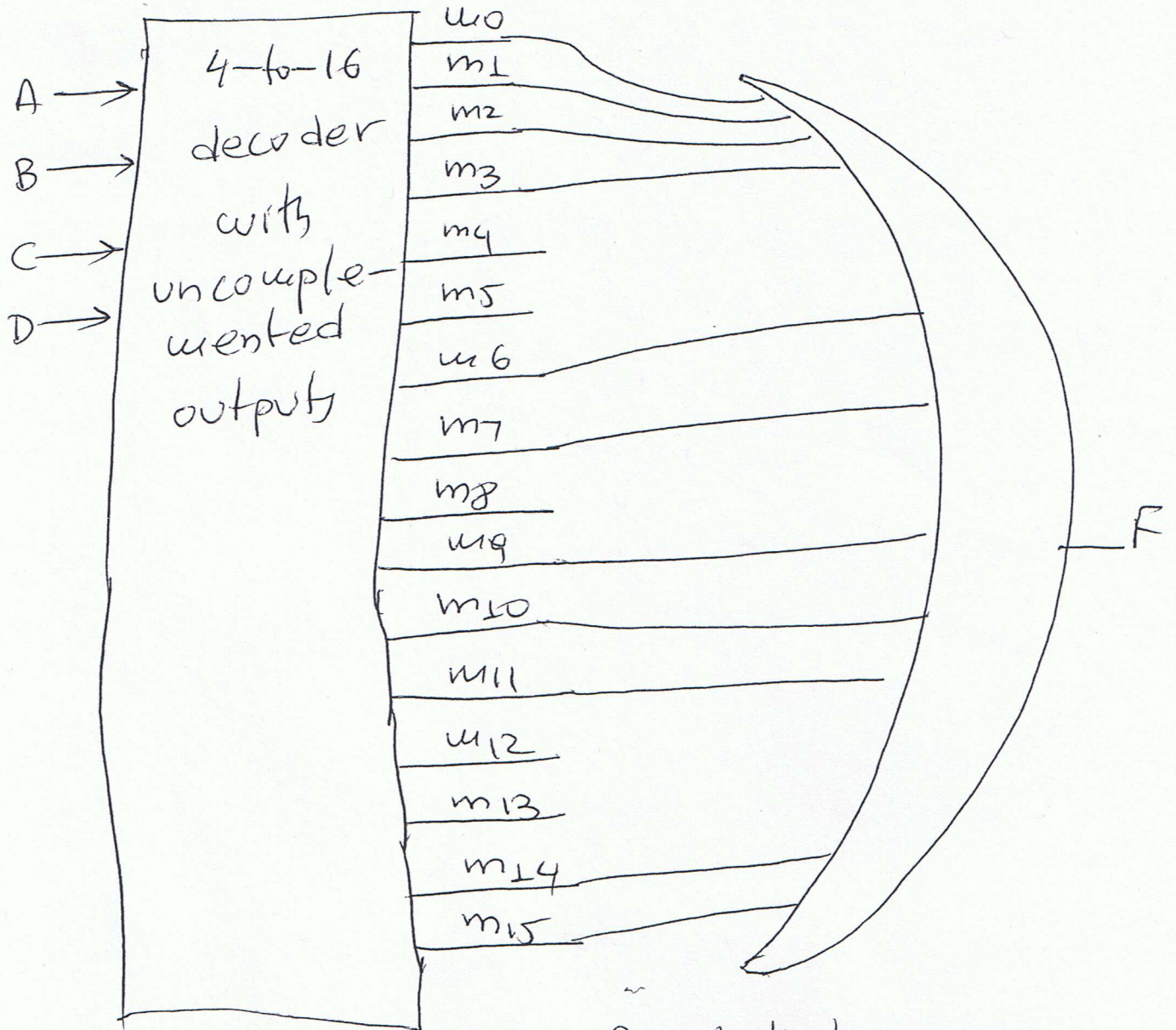

Pr. 3: From prob. 2 we found that

$F = \prod_{A,B,C,D} (4,5, 8, 12, B)$. We thus have the figure of the next page

Pro 3 cont.

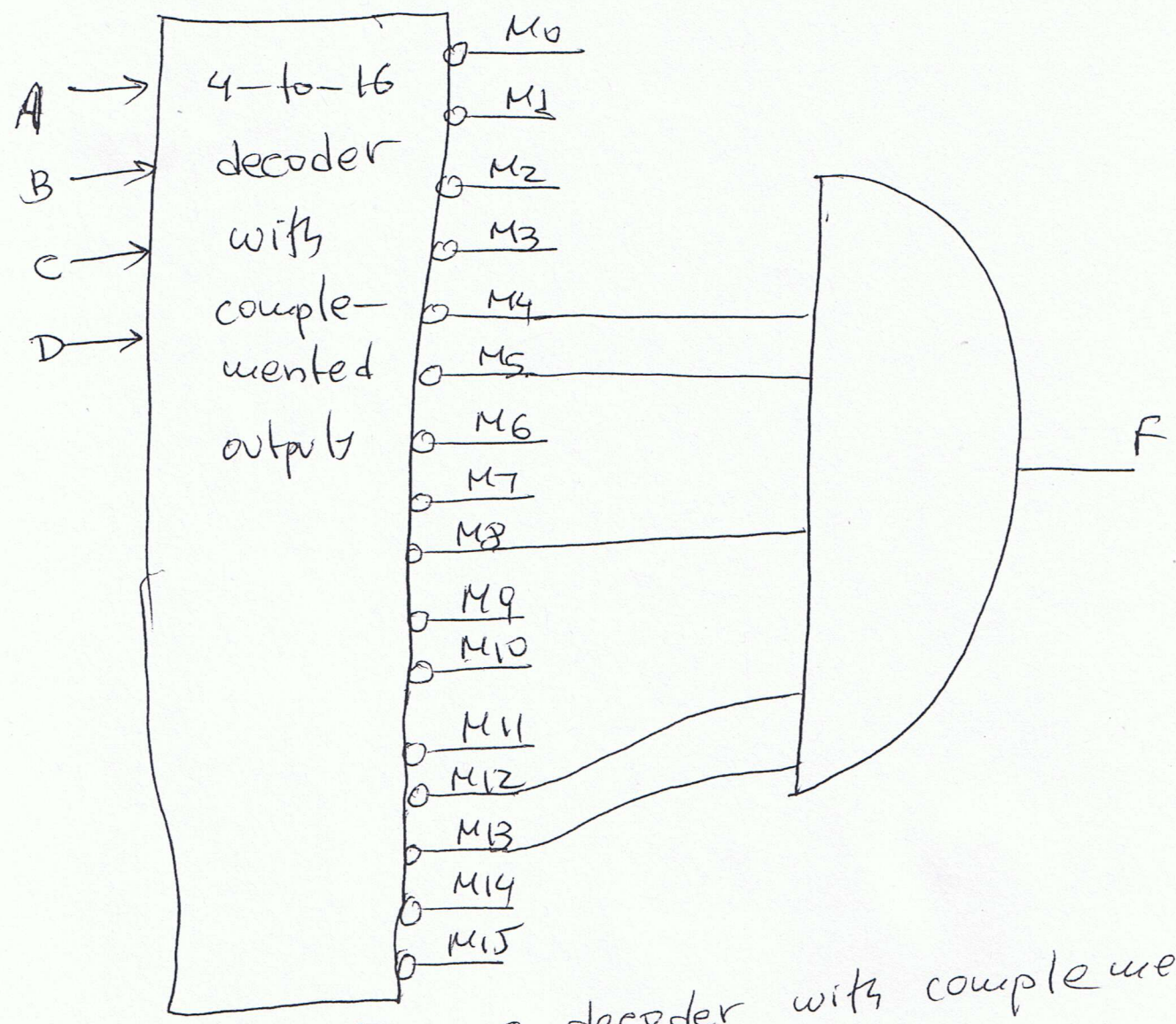

Problem 4: Since a decoder with complemented outputs generates the maxterms, we have to express F as a canonical product. Since F is given as sum-of-products, it is ~~easier~~ easier to obtain the canonical sum from which we can easily find the canonical product. We have:

$$F = A \cdot B' \cdot C + B' \cdot C \cdot D' + A' \cdot C \cdot D$$

$$= A \cdot B' \cdot C \cdot (D + D') + B' \cdot C \cdot D' \cdot (A + A') + A' \cdot C \cdot D \cdot (B + B') =$$

$$A \cdot B' \cdot C \cdot D + A \cdot B' \cdot C \cdot D'$$

$$+ B' \cdot C \cdot D' \cdot A + B' \cdot C \cdot D' \cdot A'$$

$$+ A' \cdot C \cdot D \cdot B + A' \cdot C \cdot D \cdot B'$$

$$= A \cdot B' \cdot C \cdot D + A \cdot B' \cdot C \cdot D'$$

1	0	1	1	0	0
---	---	---	---	---	---

$$+ A \cdot B' \cdot C \cdot D' + A' \cdot B' \cdot C \cdot D'$$

1	0	1	0	0	0	1	0
---	---	---	---	---	---	---	---

$$+ A' \cdot B \cdot C \cdot D + A' \cdot B' \cdot C \cdot D$$

0	1	1	1	0	0	1	1
---	---	---	---	---	---	---	---


~~$$+ A \cdot B \cdot C \cdot D + A' \cdot B \cdot C \cdot D$$~~

$$= \sum_{A,B,C,D} (2, 3, 7, 10, 11)$$

$$= \prod_{A,B,C,D} (0, 1, 4, 5, 6, 8, 9, 12, 13, 14, 15)$$

From the above we get the figure shown on next page



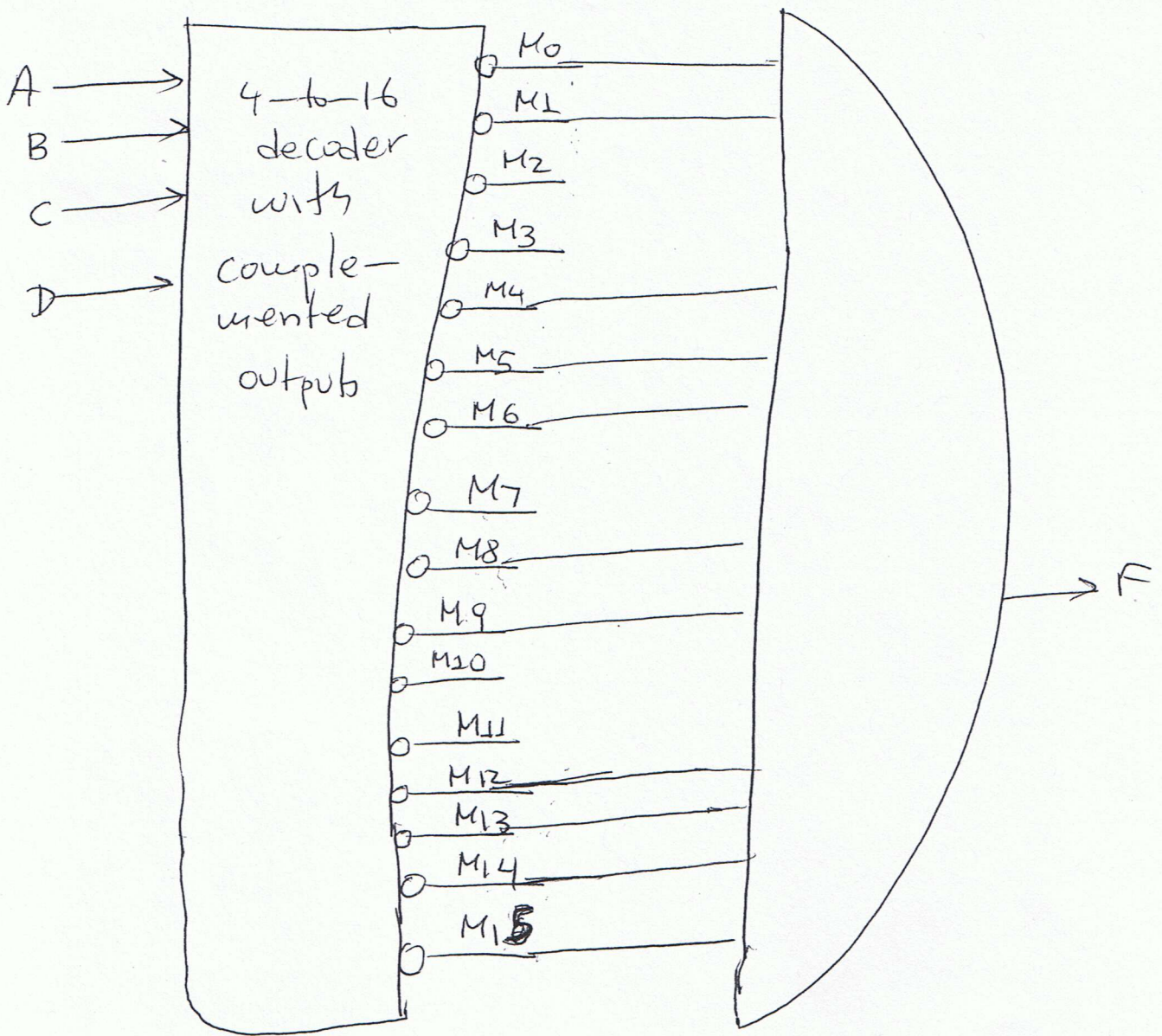

Problem 5: From problem 4 we found out

$$\text{that } F = \sum_{A, B, C, D} (2, 3, 7, 10, 11)$$

Therefore, we have the figure shown on

the next page



