

EE 3755

Verilog Handout #3

```

/// LSU EE 3755 -- Fall 2001 -- Computer Organization
///
/// Verilog Notes 3 -- Delay

/// Contents

/// Delays
/// Ripple Adder and Delays

/// References

// :P: Palnitkar, "Verilog HDL"
// :Q: Qualis, "Verilog HDL Quick Reference Card Revision 1.0"
// :H: Hyde, "Handbook on Verilog HDL"
// :LRM: IEEE, Verilog Language Reference Manual (Hawaii Section Numbering)
// :PH: Patterson & Hennessy, "Computer Organization & Design"

```

```

////////// Delays

```

```

// :P: 6.2, 6.2.2, 6.2.3
// :H: Not covered for continuous assignments.
// :LRM: 6.1

```

```

// A /delay/ is a specification of elapsed time, the amount of
// time the simulator is supposed to wait.

```

```

// The simulator keeps track of simulated time, measured in cycles.
// This is unlike conventional languages.

```

```

// The default delay is zero.

```

```

// If delays are not specified things happen instantly.

```

```

// The default delay for a gate is zero.

```

```

// The default delay for an assign is zero.
// The default delay for an assign with a really complex expression is zero.

```

```

// The default delay for a module containing a zillion gates is zero.

```

```

// Zero is NOT the same as one.

```

```

// Delays can be specified in a variety of ways.

```

```

// The following will be covered in class:

```

```

// Delays in wires and assigns (this set).
// Delays in behavioral statements (later this semester).

```

```

// See "delays" module, below, for further description.

```

```

// :Example:

```

```

// A module that just passes the signal through, like wire. Suppose
// at t=5 input a changes from 0 to 1, when does x change?

```

```

module no_delays(x,a);
  input a;
  output x;
  assign x = a;
  wire w = x;

```

```

endmodule
//
// Ans: x changes at 5 + 0 = 5.

// :Example:
//
// A module that just passes the signal through unchanged, though it
// passes through two inverters. Suppose at t=5 input a changes from
// 0 to 1, when does x change?

module no_delays2(x,a);
    input a;
    output x;
    wire b;

    not n1(b,a);
    not n2(x,b);

endmodule
//
// Ans: x changes at 5.

```

```

// :Example:
//
// Illustration and explanation of delays in assigns and wires.

module delays(x,a);
    input a;
    output x;

    // Delay (For nets.)
    //
    wire #7 w = a; a a
    //
    // w gets value of x 7 cycles after each change in x (x must hold
    // steady for at least 7 cycles).

    // Delay (For continuous assignments.)
    //
    assign #3 x = w; w w
    //
    // x gets value of a 3 cycles after each change in "a" (a must
    // hold steady for at least 3 cycles).

endmodule

```

```

///////////////////////////////  

/// Ripple Adder and Delays

```

```

// :Example:
//
// The binary full adder presented earlier. There are no delays here.

module bfa_implicit(sum,cout,a,b,cin);
    input a,b,cin;
    output sum,cout;

    assign sum =
        ~a & ~b & cin |
        ~a & b & ~cin |
        a & ~b & ~cin |
        a & b & cin;

```

```

assign cout = a & b | b & cin | a & cin;
endmodule

// :Example:
//
// The same BFA with delays.
// Suppose "a" changes at t=5 and "b" changes at t=20.
// When do sum and cout change?

module bfa_implicit_d(sum,cout,a,b,cin);
    input a,b,cin;
    output sum,cout;

    assign #3 sum =
        ~a & ~b & cin |
        ~a & b & ~cin |
        a & ~b & ~cin |
        a & b & cin;

    assign #2 cout = a & b | b & cin | a & cin;
endmodule

// Ans: sum: t=8 and t=23; cout t=7 and t=22.

// More information
//
// If a changes at t=5 and b changes at t=6 the situation is
// different because there are two changes in "sum" within the
// 3-cycle delay.

// :Example:
//
// A 4-bit ripple adder constructed using the undelayed BFA.
// If a changes at t=5 when does sum change?

module ripple_4(sum,cout,a,b);
    input [3:0] a, b;
    output [3:0] sum;
    output      cout;

    wire      c0, c1, c2;

    bfa_implicit bfa0(sum[0],c0,a[0],b[0],1'b0);
    bfa_implicit bfa1(sum[1],c1,a[1],b[1],c0);
    bfa_implicit bfa2(sum[2],c2,a[2],b[2],c1);
    bfa_implicit bfa3(sum[3],cout,a[3],b[3],c2);

endmodule

// Ans: I'm sure everyone got it.

// :Example:
//
// A 4-bit ripple adder constructed using the BFA with delays.
// Suppose at t=0 a=0 and b=4'b1111
// If a changes to 1 at t=100 when does sum stop changing?

module ripple_4_d(sum,cout,a,b);
    input [3:0] a, b;
    output [3:0] sum;
    output      cout;

```

```

    wire      c0, c1, c2;

    bfa_implicit_d bfa0(sum[0],c0,a[0],b[0],1'b0);
    bfa_implicit_d bfa1(sum[1],c1,a[1],b[1],c0);
    bfa_implicit_d bfa2(sum[2],c2,a[2],b[2],c1);
    bfa_implicit_d bfa3(sum[3],cout,a[3],b[3],c2);

endmodule

// Ans t=109  (Not checked)

// :Example:
//
// A 4-bit adder using operators and no delays. This would be
// a better way of coding a 4-bit adder in Verilog, but it's
// not a good way to demonstrate the low speed of a ripple adder
// to a computer organization class.

module another_adder(sum,cout,a,b);
    input [3:0] a, b;
    output [3:0] sum;
    output      cout;

    wire [4:0] sum_with_carry = a + b;
    assign     sum = sum_with_carry[3:0];
    assign     cout = sum_with_carry[4];

endmodule

// :Example:
//
// This is not really an example and students are not expected
// to understand it. This is a testbench for the adder, it
// instantiates the adders, generates inputs for them, and checks
// for the correct output.

module demoadd();

    wire [4:0] sum1, sum2, sum3;
    reg [4:0] shadow_sum;
    reg [3:0]  a, b;
    integer   i;

    ripple_4 adder1(sum1[3:0],sum1[4],a,b);
    ripple_4_d adder2(sum2[3:0],sum2[4],a,b);
    another_adder adder3(sum3[3:0],sum3[4],a,b);

    task check_sum;
        input [4:0] s;
        input [79:0] name;

        if( s != shadow_sum ) begin
            $display("Wrong sum in %s: %d + %d = %d != %d\n",
                    name, a, b, shadow_sum, s);
            $stop;
        end
    endtask

    initial begin

        for(i=0; i<255; i=i+1) begin
            a = i[3:0];
            b = i[7:4];
            shadow_sum = a + b;
    
```

```
#10;
check_sum(sum1,"Ripple");
check_sum(sum2,"Ripple_d");
check_sum(sum3,"Operator");
end

$display("Tests completed.");

end

endmodule
```