

**EE 3755****Homework 3** Solution**Due: Not collected**

The following problems cover material that will be on the midterm. Solution to some of these may be presented in the review, especially if someone requests some of these problems for the review. This assignment will not be collected.

Solution Verilog code in <http://www.ece.lsu.edu/ee3755/2001f/hw03sol.html>.

**Problem 1:** Write a Verilog description of a signed adder that adds a 30-bit signed quantity to a 10-bit signed quantity, producing a 31-bit result. The Verilog description can use the add operator but cannot use integers or reals. Other than declarations, a correct solution includes one line.

```
module prob1(sum,a,b);
  input [29:0] a;
  input [9:0] b;
  output [30:0] sum;

  // Sign extend the operands to the same size as the sum.
  assign      sum = {a[29],a} + { b[9] ? 21'h1ffff : 21'h0, b };

endmodule
```

**Problem 2:** Show the longhand steps for dividing 101010 by 111. Identify the quotient and remainder.

```

101010 |
-111   |
  ~~~~~| 0
101010 |
- 11100 |
  ~~~~~| 01
   1110 |
-  1110 |
  ~~~~~| 011
     0  |
-   111 |
  ~~~~~| 0110 <- Quotient
        0 <----- Remainder
```

**Problem 3:** In class both levels of a two-level CLA were themselves CLAs.

(a) Write a Verilog description of a 40-bit two-level CLA in which both levels are CLAs. The design should use 10-bit CLAs for the first level; assume they are already designed. (The description should instantiate four 10-bit CLAs. Make up a name for them.)

```
module cla40(cout,sum,a,b);
    input [39:0] a, b;
    output [39:0] sum;
    output      cout;

    // G[0] intentionally left unconnected.

    wire [3:0]    G, P, cin;

    assign        cin[0] = 0;
    assign        cin[1] = G[0];
    assign        cin[2] = G[0] & P[1] | G[1];
    assign        cin[3] = G[0] & P[1] & P[2] | G[1] & P[2] | G[2];
    assign        cout = G[0] & P[1] & P[2] & P[3]
        | G[1] & P[2] & P[3] | G[2] & P[3] | G[3];

    cla10 c0(G[0],P[0],sum[9:0], a[9:0], b[9:0],cin[0]);
    cla10 c1(G[1],P[1],sum[19:10], a[19:10], b[19:10],cin[1]);
    cla10 c2(G[2],P[2],sum[29:20], a[29:20], b[29:20],cin[2]);
    cla10 c3(G[3],P[3],sum[39:30], a[39:30], b[39:30],cin[3]);

endmodule
```

(b) In gate delays, how fast is the two-level adder.

Ten cycles. (See the two-level CLA in <http://www.ece.lsu.edu/ee3755/2001f/105.html>.)

(c) Suppose the 10-bit CLAs were really ripple adders. How much cheaper and how much slower would the 40-bit adder be?

The carry logic within the 10-bit adders would not be needed.

The carry in would be available at 5 cycles. The ten-bit ripple adder would take another  $2 \times 10 + 1 = 21$  cycles, for a total of 26 cycles.

**Problem 4:** Modify module `streamlined_mult` so that the multiplicand is a signed number (but keeping the multiplier an unsigned number). Take advantage of the existing structure of `streamlined_mult`, don't just make it look like `streamlined_signed_mult`.

```

module streamlined_usmult(product,ready,multiplier,multiplicand,start,clk);
    input [15:0] multiplier, multiplicand;
    input      start, clk;
    output     product;
    output     ready;

    reg [31:0] product;

    reg [4:0] bit;
    wire      ready = !bit;

    initial bit = 0;

    always @( posedge clk )

        if( ready && start ) begin

            bit      = 16;
            product = { 16'd0, multiplier };

        end else if( bit ) begin:A

            reg lsb;

            lsb      = product[0];
            product = {product[31],product[31:1]};
            bit      = bit - 1;

            if( lsb ) product[31:15] = product[31:15]
                + {multiplicand[15],multiplicand};

        end

endmodule

```

**Problem 5:** Show a radix-8 Booth table (in the same format as the radix-4 and -2 Booth tables in Set 7).

Radix-8 Booth Table

MB C		x	c
000 0		0 + 0	0
000 1		1 + 0	0
001 0		1 + 0	0
001 1		2 + 0	0
010 0		2 + 0	0
010 1		3 + 0	0
011 0		3 + 0	0
011 1		4 + 0	0
100 0		-4 + 8	1
100 1		-3 + 8	1
101 0		-3 + 8	1
101 1		-2 + 8	1
110 0		-2 + 8	1
110 1		-1 + 8	1
111 0		-1 + 8	1
111 1		0 + 8	1

**Problem 6:** Remember the last time you bought lunch and it did not cost an even dollar amount. If you can't assume it cost \$5.12.

(a) Convert the cost to binary. Plain, old binary, not IEEE 754. From the class account issue command “dtob 5.12” to see the answer.

$$5.12_{10} = 101.000111101011100001010001_2$$

(b) Convert the cost of lunch to binary scientific notation.

$$1.01000111101011100001010001_2 \times 2^2$$

(c) Convert the cost of lunch to an IEEE 754 single. From the class account issue command “fp 5.12” to see the answer.

$$5.12_{10} = 40a3d70a_{16}$$