

Name Solution_____

Computer Organization
EE 3755
Midterm Examination
29 October 2001, 12:40-13:30 CST

Problem 1 _____ (16 pts)

Problem 2 _____ (16 pts)

Problem 3 _____ (20 pts)

Problem 4 _____ (16 pts)

Problem 5 _____ (16 pts)

Problem 6 _____ (16 pts)

Alias Can't think of a good one_____

Exam Total _____ (100 pts)

Good Luck!

Problem 1: Add Verilog code to the 32-bit carry-lookahead adder module below for the carry[5] wire. Use the generate and propagate signals.

(16 pts)

```
module cla_32(sum,a,b);
    input [31:0] a, b;
    output [32:0] sum;

    wire [31:0] g, p, carry;

    // Code for other carry signals omitted.
    //
    // Start answer here ↓

    assign      carry[5] =
assign      carry[5] = g[0] & p[1] & p[2] & p[3] & p[4] |
                g[1] & p[2] & p[3] & p[4] |
                g[2] & p[3] & p[4] |
                g[3] & p[4] |
                g[4];

    cla_slice s0(sum[0],g[0],p[0],a[0],b[0],carry[0]);
    cla_slice s1(sum[1],g[1],p[1],a[1],b[1],carry[1]);
    cla_slice s2(sum[2],g[2],p[2],a[2],b[2],carry[2]);
    // Code for other cla_slices omitted.
    cla_slice s5(sum[5],g[5],p[5],a[5],b[5],carry[5]);
    // Code for other cla_slices omitted.

endmodule
```

Problem 2: Complete the module below so that 32-bit output `sum` is the sum of its 32-bit inputs, `a` and `b`. If input `s` is 1 then `a` and `b` are signed integers, otherwise they are unsigned integers. Output `overflow` should be set to 1 if the sum overflows.

The module should synthesize to combinational logic. The solution can (and should) use the addition operator. (16 pts)

For partial credit, explain how to detect overflow in signed and unsigned addition.

```
module add(sum,overflow,a,b,s);
    input [31:0] a, b;
    input      s;
    output [31:0] sum;
    output      overflow;
    reg [31:0]    sum;
    reg          overflow;


    always @( a or b or s ) begin

        sum = a + b;

        if( s )
            overflow = a[31] == b[31] && a[31] != sum[31];
        else
            overflow = a[31] && b[31] || ( a[31] || b[31] ) && ! sum[31];

    end
endmodule
```

 Problem 3: The module below examines a bit sequence one bit per clock cycle, as did the module in Homework 2 Problem 2. The input bit is valid on the positive edge of `clk`, that bit is the first of a new sequence if `reset` is high. The output, `lrun`, must be the longest number of consecutive 1's encountered since the last time `reset` was 1. For example, after 00111010 is received the output should be 3 since that is the length of the longest run of 1's. Also see the example timing below. As in Homework 2 the module must synthesize to sequential logic. (20 pts)



```

module longest_run(lrun,bit,reset,clk);
    output [31:0] lrun;
    input        bit, reset, clk;
    reg [31:0]   this_run, lrun;

    always @( posedge clk ) begin

        if( reset ) begin lrun = 0; this_run = 0; end

        if( bit == 1 ) begin

            this_run = this_run + 1;

        end else begin

            this_run = 0;

        end

        if( this_run > lrun ) lrun = this_run;

    end

endmodule

```

Problem 4: Show the hardware that the module below will synthesize in to. Indicate the types (edge- or level-triggered) of any registers synthesized.

(16 pts)

```
module syn(x,r,a,b,m,neg);
  input [31:0] a, b;
  input      m, neg;
  output [31:0] x, r;

  reg [31:0]    x, r, bn;

  always @( a or b or m or neg ) begin

    if( neg ) bn = -b; else bn = b;

    x = a + bn;

    if( m ) r = x + b;

  end

endmodule
```

Problem 5: Convert the following numbers: (16 pts)

Decimal 12 to 8-bit Binary:

00001100_2

Decimal -12 to 8-bit Binary:

11110100_2

Decimal $12\frac{5}{8}$ to Binary (as many bits as needed):

1100.101_2

Decimal $12\frac{5}{8}$ to Normalized Binary Scientific Notation (write as $f \times 2^e$):

$1.100101_2 \times 2^3$

Decimal $12\frac{5}{8}$ to IEEE 754 Single Precision (Show in hexadecimal):

$414a0000_{16}$

Problem 6: The high-radix Booth multiplier is faster than the radix-2 multipliers (for example, the streamlined signed multiplier). (16 pts)

(a) Compared to the streamlined signed multiplier, what additional hardware is needed for a high-radix Booth multiplier?

Hardware to compute, store, and select multiples of the multiplicand and a adder/subtractor (rather than just an adder).

(b) Name two advantages that a high-radix Booth multiplier has over an ordinary high-radix multiplier.

A Booth multiplier provides a signed product without extra hardware to take the absolute value of the multiplier and multiplicand and to negate the product. A Booth multiplier uses fewer pre-computed constants than a high-radix multiplier. Both radix- r Booth and radix- r multipliers produce a product in the same number of steps, so speed is not an advantage.