

Name _____

Computer Organization
EE 3755
Practice Midterm Examination
23 October 2001

Problem 1 _____ (10 pts)
Problem 2 _____ (30 pts)
Problem 3 _____ (10 pts)
Problem 4 _____ (10 pts)
Problem 5 _____ (10 pts)
Problem 6 _____ (10 pts)
Problem 7 _____ (10 pts)
Problem 8 _____ (10 pts)

Alias _____

Exam Total _____ (100 pts)

Good Luck!

Problem 1: Add Verilog code to the module below for the carry signals and sum[3] using the generate and propagate signals. *Hint: This is straight from the notes.* (10 pts)

```
module cla_3(sum,a,b);
  input [2:0] a, b;
  output [3:0] sum;

  wire [2:0] g, p, carry;

  assign      carry[0] =

  assign      carry[1] =

  assign      carry[2] =

  assign      sum[3] =

  cla_slice s0(sum[0],g[0],p[0],a[0],b[0],carry[0]);
  cla_slice s1(sum[1],g[1],p[1],a[1],b[1],carry[1]);
  cla_slice s2(sum[2],g[2],p[2],a[2],b[2],carry[2]);

endmodule
```

Problem 2: Complete the module below so that it determines whether its input, a floating point number in IEEE 754 single format, is positive, zero, negative, and whether it is an integer. Output `pos` is 1 if the input is positive, `neg` is 1 if it's negative, etc. The solution can ignore special values ($\pm\infty$, NaN, subnormals, etc.) (30 pts)

```
module fp_flags(pos,zero,neg,int,single);  
    input [31:0] single;  
    output      pos, zero, neg, int;
```

```
endmodule
```

Problem 3: The `for` loop in the code below looks harmless but is actually an infinite loop. Why?
Hint: It has to do with the way `i` is declared. (10 pts)

```
module iloop(z,a);
  input [31:0] a;
  output      z;

  reg [4:0] i;
  reg      s, z;

  initial begin
    s = 0;
    for(i=0; i<32; i=i+1) s = s | a[i];
    z = !s;
  end
endmodule
```

Problem 4: Consider the adder modules below.(10 pts)

(a) What kind of adders are these?

(b) How do the speed of the two adders compare?

(c) Compare the amount of hardware that the adders will synthesize into. How is the second adder penny wise and \mathcal{L} foolish?

```
module add_1(sum,a,b,clk);
    input [31:0] a,b;    input      clk;    output      sum;
    reg [31:0]  sum;    integer      i;    reg          carry;

    always @( posedge clk )
        begin
            carry = 0;

            for(i=0; i<31; i=i+1) begin

                sum[i] = ~a[i] & ~b[i] & carry |
                    ~a[i] & b[i] & ~carry |
                    a[i] & ~b[i] & ~carry |
                    a[i] & b[i] & carry;

                carry = a[i] & b[i] | b[i] & carry | a[i] & carry;

            end
        end
end
endmodule
```

```
module add_2(sum,a,b,clk);
    input [31:0] a,b;    input      clk;    output      sum;
    reg [31:0]  sum;    integer      i;    reg          carry;

    always @( posedge clk )
        begin
            i = i + 1;
            if( i == 32 ) begin carry = 0; i = 0; end

            sum[i] = ~a[i] & ~b[i] & carry |
                ~a[i] & b[i] & ~carry |
                a[i] & ~b[i] & ~carry |
                a[i] & b[i] & carry;

            carry = a[i] & b[i] | b[i] & carry | a[i] & carry;
        end
end
endmodule
```

Problem 5: Consider the module below. (10 pts)

```
module prefix_xor_4(x,a);
  input [3:0] a;
  output [3:0] x;

  assign      x[0] = a[0];

  xor x1(x[1],a[0],a[1]);
  xor x2(x[2],x[1],a[2]);
  xor x3(x[3],x[2],a[3]);

endmodule
```

(a) Suppose that each gate has a delay of one unit. How long would it take to compute the result?

(b) Suppose during a run of the simulator on the code above new inputs arrived at $t = 100$. At what simulated time would the results be available? *Hint: The first part is intentionally misleading.*

(c) How would timing obtained after synthesis relate to the times used to solve the first two parts?

Problem 6: In the module below fill in the values for c, whether the corresponding addition overflowed, and fix the last assignment. (10 pts)

```
module sums();

    reg [3:0] a, b, c;
    reg [5:0] d;

    initial begin

        a = 4'b0101; b = 4'b0001; c = a + b;

        // Unsigned decimal: c =          Overflow?
        // Signed decimal:   c =          Overflow?

        a = -6; b = 4'b0001; c = a + b;

        // Unsigned decimal: c =          Overflow?
        // Signed decimal:   c =          Overflow?

        a = -6; b = 4'b0001; c = a + b;

        // Unsigned decimal: c =          Overflow?
        // Signed decimal:   c =          Overflow?

        a = 4'b1101; b = 4'b1100; c = a + b;

        // Unsigned decimal: c =          Overflow?
        // Signed decimal:   c =          Overflow?

        // Suppose c and d are used for signed quantities.
        // Fix the assignment below.
        d = c;

    end

endmodule
```

Problem 7: Convert the module below to an explicit structural form. (10 pts)

```
module to_str(x,s,a,b);  
  input [1:0] s;  
  input      a, b;  
  output     x;  
  
  assign x = s == 2 ? a : b;  
  
endmodule
```

Problem 8: Show the longhand steps needed to multiply $00100111_2 \times 00100111_2$ using radix-4 Booth recoding. (10 pts)