

Name _____

Computer Organization
EE 3755
Midterm Examination
Wednesday, 30 October 2013, 8:30–9:20 CDT

Problem 1 _____ (21 pts)

Problem 2 _____ (15 pts)

Problem 3 _____ (25 pts)

Problem 4 _____ (11 pts)

Problem 5 _____ (11 pts)

Problem 6 _____ (11 pts)

Problem 7 _____ (6 pts)

Alias _____

Exam Total _____ (100 pts)

Good Luck!

Problem 1: [21 pts] Consider the module below:

```
module prob1is(x,y,a,b,c);
  input a, b, c;  output x, y;
  wire a, b, c, x, y;      <-- HINT: Declare types for parts b and c.
  assign x = !a ^ y;
  assign y = b || c;
endmodule
```

(a) Draw a logic diagram corresponding to the module. Don't optimize.

Logic diagram of `prob1is`.

(b) Complete the module below so that it performs the same operation as `prob1is` but is in explicit structural form.

Explicit structural form of `prob1is`. Don't forget to declare types.

```
module prob1es(x,y,a,b,c);
  input a, b, c;  output x, y;
```

```
endmodule
```


(c) Complete the module below so that it performs the same operation as `prob1is` but is in synthesizable behavioral form.

Synthesizable behavioral form of `prob1is`. Don't forget to declare types.

```
module prob1sb(x,y,a,b,c);
  input a, b, c;  output x, y;
```

```
endmodule
```

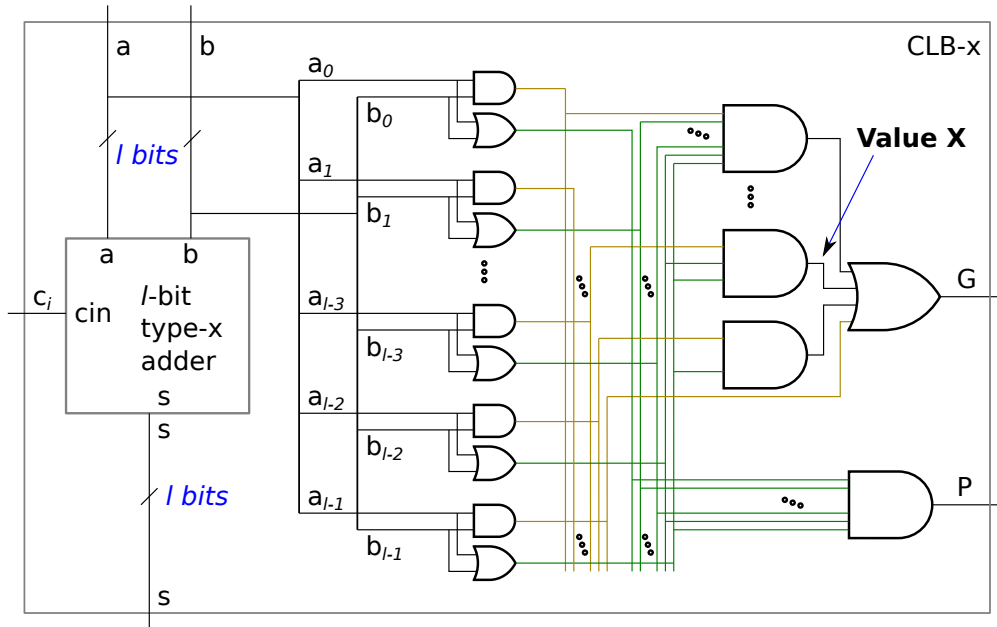Problem 2: [15 pts] Appearing below is the generic carry lookahead block from the CLA lecture slides. Remember that it is part of a hierarchical carry lookahead adder.



(a) The output of one of the AND gates is labeled *Value X*. Suppose $l = 16$. Find inputs to the module such that *Value X* is 1 but all of the other inputs to the generate OR gate are 0.

Value of module inputs needed so that *Value X* will be 1.

(b) Notice that the module does not have a carry out signal. Add logic to the module above to compute a carry out signal. (See next part.)

Logic for carry out. Do not add new inputs to the module.

(c) The carry out signal from the previous part isn't needed in real life. Why not? What if it were used?

Why doesn't the CLB need a carry out signal?

What would be the problem with using the carry out signal?

Problem 3: [25 pts] A population count module based on Homework 3 Problem 2 appears below.

```
module red_pop(p,a);
  parameter N = 20;
  parameter M = 4; // Number of parts.
  parameter N_PER_PART = N/M;
  input wire [N-1:0] a;          output reg [8:0] p;
  reg [8:0] pa;                 integer i, j;

  always @( a ) begin
    for ( j=0; j<M; j=j+1 ) begin
      pa = a[ j*N_PER_PART ];
      for ( i=1; i<N_PER_PART; i=i+1 ) pa = pa + a[ j*N_PER_PART + i ];
      if ( j == 0 ) p = pa; else p = p + pa;
    end
  end
endmodule
```

(a) Sketch the logic that would be inferred for this module (the logic that would be synthesized without optimization). Show adders as a box with a + inside.

Show synthesized logic without optimization.

Problem 3, continued: The module below is the same as the one on the previous page.

```
module red_pop(p,a);
  parameter N = 20;
  parameter M = 4; // Number of parts.
  parameter N_PER_PART = N/M;
  input wire [N-1:0] a;          output reg [8:0] p;
  reg [8:0] pa;                  integer i, j;

  always @( a ) begin
    for ( j=0; j<M; j=j+1 ) begin
      pa = a[ j*N_PER_PART ];
      for ( i=1; i<N_PER_PART; i=i+1 ) pa = pa + a[ j*N_PER_PART + i ];
      if ( j == 0 ) p = pa; else p = p + pa;
    end
  end
endmodule
```

(b) Compute the cost of the logic from the previous part assuming that all adders are ripple adders and that the cost of a BFA is 7 units. The size of the adders has been made as small as possible. Assume that the gates outside of the BFAs have a cost of one unit each.

- Cost of circuit. Show work for partial credit.
- Account for size of adders, the sizes have been minimized.

(c) Suppose the delay of each ripple adder is just 1 time unit. (Yes, just 1 time unit.) Find the delay of the circuit in terms of N and M . That is, don't assume $N=20$ and $M=4$.

- Delay in terms of N and M assuming 1-time-unit ripple adders.

(d) In the module above M was set to 4 and N to 20. Consider the case where N is some arbitrary value, and we want to compute a value for M that minimizes delay for this N . Using the delay model from the previous part, find an expression for M in terms of N that will minimize delay.


- Best value of M in terms of N .

Problem 4: [11 pts] Answer the computer arithmetic questions below.

(a) Show the longhand steps needed to multiply $1234_{16} \times 1203_{16}$ using a radix-16 (four bit) multiplication algorithm, but do not add together the partial products. Show the work in binary or hexadecimal. This is **without** Booth recoding. (The product is $147de9c_{16}$, but remember there is no need to add the partial products.)


Longhand steps for radix-16 (4 bit) $1234_{16} \times 1203_{16}$

 (b) Show the value of IEEE 754 single-precision floating point number $0x42fa0000$. For your convenience the layout of an IEEE 754 single is shown below.



Value of number (in decimal or as a formula to compute value) is:

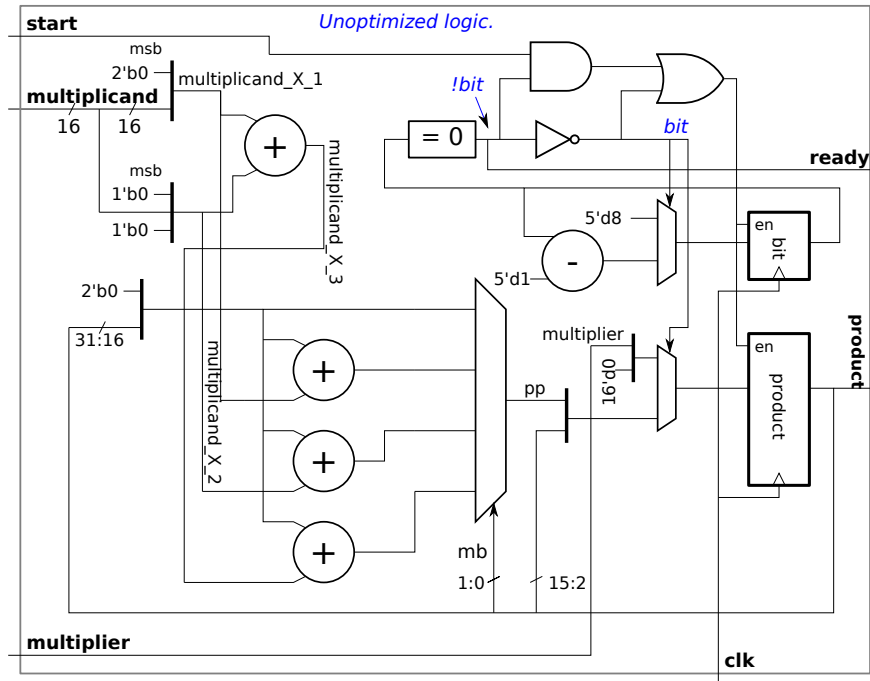Problem 5: [11 pts] Appearing below is unoptimized logic for an ordinary radix-4 multiplier.



(a) As described in class, the logic around the four-input multiplexor can be reduced in cost. Show how.

Sketch of lower-cost logic around the 4-input mux.

(b) One of the adders in the illustrated multiplier would not be necessary in a radix-4 multiplier using Booth recoding. Show which adder would not be necessary, and explain what would be done instead.

Indicate which adder not necessary.

Explain what would be done instead.

Problem 6: [11 pts] Answer the following MIPS questions.

(a) Show the values in register `$s0` after the execution of each instruction below in the spaces indicated.

Fill in the `s0 =` blanks below.

 # Initial register values: `$s1 = 0x18, $s2 = 0x30`

`or $s0, $s1, $s2`
 # `$s0 =`

`sll $s0, $s2, 2`
 # `$s0 =`

`slt $s0, $s1, $s2`
 # `$s0 =`

`addi $s0, $s1, 0xffff`
 # `$s0 =`

`ori $s0, $s1, 0xffff`
 # `$s0 =`

(b) There is a problem with the instruction below. Describe what the problem is and show replacement instruction(s) that do what was intended.



`addi $s0, $s0, 0x12345`

The problem with the instruction is:

Replacement that does the same thing:

Problem 7: [6 pts] Answer each MIPS encoding question below.

  (a) Show the encoding of each assembly language instruction below. Some field values would have to be looked up in a table, for those write “look up” instead of the value. For your convenience the layout of the MIPS R and I formats are shown, answers can be written in these or they can be copied.



Encoding for `sub $20, $21, $22`

Encoding for `lui $8, 0x1234`

Encoding for `sra $9, $2, 31`