 


Problem 1: *Note: Problems like this one have been assigned before. Please solve this problem without looking for a solution elsewhere. If you get stuck ask for hints. Copying a solution will leave you unprepared for exams, and will waste your (or your parents') hard-earned tuition dollars.* A shift unit is to be added to the EX stage of the implementation below. The shift unit has a 32-bit data input, VIN, a 5-bit shift amount input, AMT, a 1-bit input SIN, and a 1-bit control input DIR. There is a 32-bit data output, VOUT. The DIR input determines whether the shift is left (1) or right (0). If the shift is right then the value at input SIN is shifted in to the vacated bit positions. The meaning of the other inputs is self-explanatory. For a description of MIPS-I instructions see the MIPS32 Volume 2 linked to the course references page.



(a) Connect the shift unit data inputs so that it can be used for the MIPS `sll`, `sllv`, `srl`, `srlv`, `sra`, and `srav` instructions. Assume that the ALU has plenty of slack (it is not close to carrying the critical path). (Control inputs are in the next part.)

- Be sure your design does not unnecessarily inflate cost or lower performance.
- In your diagrams be sure to use the bit ranges used, for example, 27:21, when connecting a wire to an input with fewer bits than the wire.

(b) Show the logic for control inputs DIR and SIN and any multiplexors that you added.

(c) Repeat the design of the datapath but assuming that the ALU is on the critical path and that we don't want to lower the clock frequency.