 


In the problems below a new MIPS instruction, integer `fmadd`, (hypothetical of course) is to be added to our pipelined MIPS implementation. A simpler implement-the-instruction problem was the subject of Fall 2010 Homework 3, in which a shift unit is added to MIPS to implement shift instructions. The 2010 problem is simpler because the shift unit occupies just one stage, while the `fmadd` for this assignment spans multiple stages. For past assignments in which integer arithmetic hardware spans several stages see 2020 Homework 2, 3, and 4 and 2020 midterm exam Problem 5. In these 2020 problems an integer multiply instruction was to be implemented.

**Problem 1:** A fused multiply/add instruction, such as `fmadd r1, r2, r3, r4`, computes  $r_1 = r_2 r_3 + r_4$ . Such instructions are useful for both floating-point and integer calculations, and integer version is considered here. The goal in this problem is to extend MIPS with an integer multiply/add instruction, `fmadd`. The new `fmadd` instruction will be encoded in MIPS Format R with the SA field being used to specify the third source register, `r4` in the example.

	Opcode	RS	RT	RD	SA	Function
MIPS R:	0	2	3	1	4	<code>fmadd</code>
	31	26 25	21 20	16 15	11 10	6 4 0

The hardware to compute the multiply/add will consist of two types of units: a carry-save multiplier (CSM) and integer adders (labeled ADD). The connection of these two types of units needed to compute a multiply/add are shown below.




The CSM takes 0.9 clock cycles to compute a result and each adder takes 0.45 clock cycles, so the critical path through the hardware shown above is 1.8 clock cycles. Because the critical path is greater than one clock cycle the hardware cannot be placed in one stage. (Unless the clock frequency were to be decreased from  $\phi$  to  $\phi/1.8$ , which would slow everything down and so of course we don't want to do it.)

Note: For the three parts below a single hardware solution can be provided. That is, a correct solution to part c also can be a correct solution to parts b and a, and so there is no need to draw three hardware designs.

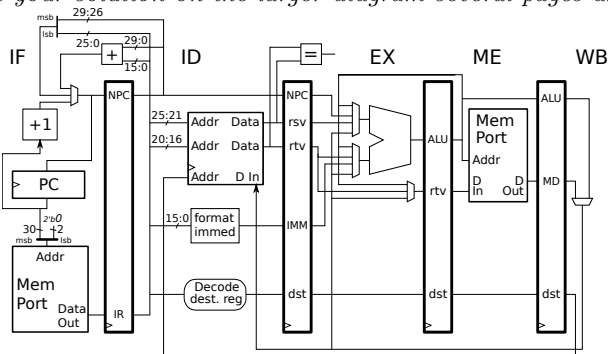(a) Add the CSM and ADD units to the MIPS implementation below to efficiently implement the `fmadd` instruction. For this sub-problem provide the hardware needed so that `fmadd` can execute without stalls when there are no nearby dependencies, such as in the execution below.

```
# There are no dependencies in this code fragment.
# Cycle      0  1  2  3  4  5  6  7  8
add r1, r2, r3      IF ID EX ME WB
sub r4, r5, r6      IF ID EX ME WB
fmadd r7, r8, r9, r10    IF ID EX ME WB
fmadd r11, r12, r13, r14  IF ID EX ME WB
xori r15, r16, 17      IF ID EX ME WB
# Cycle      0  1  2  3  4  5  6  7  8
```

Put your solution on the larger diagram several pages ahead.



Put your solution on the larger diagram several pages ahead.

- ☐ Add the CSM and ADD units to the implementation above so that the can implement the `fmadd` instruction.
- ☐ Provide the datapath needed so that operands can reach the CSM and ADD units and ☐ the result can reach the register file.
- ☐ Don't forget that this instruction has three source operands.
- ☐ Do not increase the critical path.
- ☐ As always, consider cost. Assume that an  $n$ -bit register costs twice as much as an  $n$ -bit, 2-input multiplexor.
- ☐ `fmadd` should execute without stalls when there are no nearby dependencies.
- ☐ **Do not** design control logic for this assignment.

(b) In the code fragments below the `fmadd` depends on prior instructions.

- ☐ Add bypass paths to the `fmadd` implementation so that all of the executions below are possible.

```
# Fragment A
# Cycle      0  1  2  3  4  5  6
add R1, r2, r3    IF ID EX ME WB
sub R4, r5, r6      IF ID EX ME WB
fmadd r7, R1, R4, r9    IF ID EX ME WB

# Fragment B
# Cycle      0  1  2  3  4  5  6  7
sub R9, r5, r6      IF ID EX ME WB
fmadd R7, r1, r4, R9    IF ID EX ME WB
fmadd r2, r3, r5, R7    IF ID EX ME WB
# Cycle      0  1  2  3  4  5  6  7

# Fragment C
# Cycle      0  1  2  3  4  5  6
add R1, r2, r3    IF ID EX ME WB
lw R9, 0(r10)      IF ID EX ME WB
fmadd r7, R1, r4, R9    IF ID EX ME WB
```

(c) Using additional ADD unit(s) modify the implementation so that it can execute Fragments L and D correctly. This will require some tricky bypassing. Note that stalls will be needed when the dependent instruction following the `fmadd` does not use the adder, such as in Fragment E. *Note: In the original problem just one adder was to be used. That is probably impossible without critical path impact.*

- ☐ Add a second adder and bypass paths so that fragments L and D execute as shown.

```
# Fragment L
# Cycle      0  1  2  3  4  5  6
fmadd R7, r1, r4, r9    IF ID EX ME WB
lw r10, 16(R7)          IF ID EX ME WB    # No stall!

# Fragment D
# Cycle      0  1  2  3  4  5  6
fmadd R7, r1, r4, r9    IF ID EX ME WB
add r2, R7, r3          IF ID EX ME WB    # No stall!

# Fragment E
# Cycle      0  1  2  3  4  5  6
fmadd R7, r1, r4, r9    IF ID EX ME WB
or r2, R7, r3          IF ID -> EX ME WB    # A stall. :-(
```

Use the diagram below for your solution, or download <https://www.ece.lsu.edu/ee4720/2023/mpipei3.svg> and edit with your favorite SVG editor. (The diagram was drawn with Inkscape.)

