
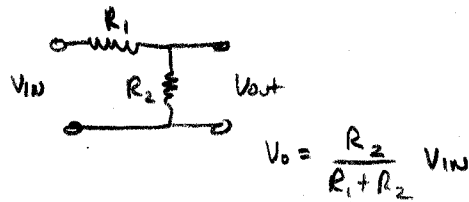


FRIDAY

OCT 1

9.2 SINUSOIDAL STEADY STATE AMP RESPONSE

SYSTEM FCN OR XFER FCN

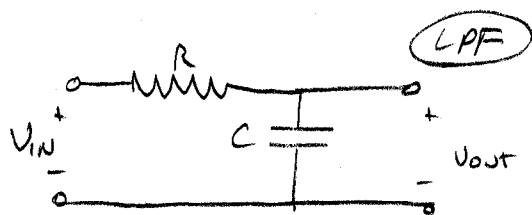

VOLTAGE DIVISION

$$\text{XFER FCN} = \frac{V_{OUT}}{V_{IN}} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC} \quad \text{LPF}$$

$$\omega \ll \frac{1}{RC} \quad \omega RC \ll 1 \quad \left| \frac{V_{OUT}}{V_{IN}} \right| = 1$$

CAP SHUNT TO GND.

22-141 50 SHEETS
22-142 100 SHEETS
22-144 200 SHEETS



12.2 SINUSOIDAL FREQUENCY ANALYSIS

A POWER SYSTEM NETWORK OPERATES AT ONLY ONE FREQUENCY - IN GENERAL WE WANT TO ANALYZE NETWORK BEHAVIOR AS A FUNCTION OF FREQUENCY.

$$\text{NETWORK FUNCTION } H(j\omega) = M(\omega) e^{j\phi(\omega)}$$

$$M(\omega) = |H(j\omega)| \quad \text{magnitude and phase characteristics}$$

$$\phi(\omega) = \angle H(j\omega)$$

FREQUENCY RESPONSE USING BODE PLOT - SEMILOG OR LOG-LOG

MAGNITUDE IS PLOTTED IN dB vs. $\log_{10}(\omega)$

dB - originally used to describe power ratio

$$\# \text{ in dB} = 10 \log \frac{P_2}{P_1}$$

$$P_2 = \frac{V_2^2}{R} \quad P_1 = \frac{V_1^2}{R}$$

$$P_2 = I_2^2 R \quad P_1 = I_1^2 R$$

$$= 10 \log \frac{V_2^2/R}{V_1^2/R} = 20 \log \frac{V_2}{V_1} = 20 \log_{10} \frac{I_2}{I_1}$$

$$H(j\omega) = \frac{K_0 (j\omega)^{\pm N} (1 + j\omega T_1) [1 + 2\zeta_3 (j\omega T_3) + (j\omega T_3)^2] \dots}{(1 + j\omega T_a) [1 + 2\zeta_b (j\omega T_b) + (j\omega T_b)^2] \dots}$$

- ① K_0 is Frequency independent factor $K_0 > 0$
- ② Poles or zeros at origin of the form $j\omega$ $(j\omega)^{+N}$ for zeros $(j\omega)^{-N}$ for poles
- ③ Poles or zeros of the form $(1 + j\omega T)$
- ④ QUADRATIC poles or zeros of the form $1 + 2\zeta (j\omega T) + (j\omega T)^2$

$$20 \log_{10} |H(j\omega)| = 20 \log_{10} K_0 \pm 20 N \log_{10} |\omega| + 20 \log_{10} |1 + j\omega T_1| + 20 \log_{10} |1 + 2\zeta_3 (j\omega T_3) + (j\omega T_3)^2| + \dots - 20 \log_{10} |1 + j\omega T_a| - 20 \log_{10} |1 + 2\zeta_b (j\omega T_b) + (j\omega T_b)^2| \dots$$

log of product = sum of logs

$$\log ab = \log a + \log b$$


$$\log a^n = n \log a$$

$$\angle H(j\omega) = 0 \pm N(90^\circ) + \tan^{-1} \omega J_1 + \tan^{-1} \left(\frac{2\zeta_3 \omega J_3}{1 - \omega^2 J_3^2} \right) + \dots$$


$$- \tan^{-1} \omega J_2 - \tan^{-1} \left(\frac{2\zeta_b \omega J_b}{1 + \omega^2 J_b^2} \right) \dots$$

PLOT EACH FACTOR INDEPENDENTLY ON A COMMON GRAPH THEN SUM THEM ALGEBRAICALLY.


CONSTANT TERM: $20 \log_{10} K_0$

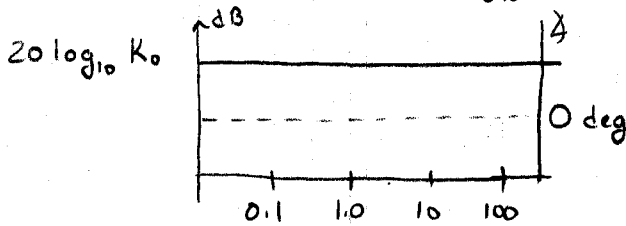

ZERO AT ORIGIN

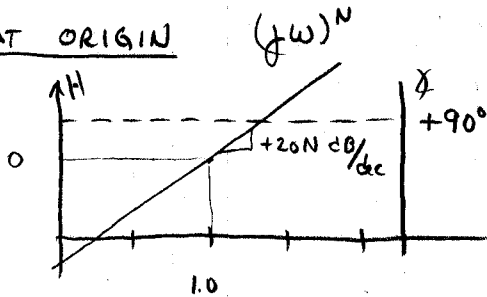

POLE AT ORIGIN

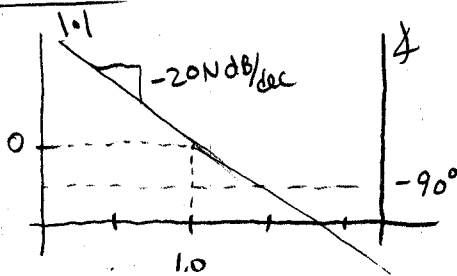

3-0235 — 50 SHEETS — 5 SQUARES
 3-0236 — 100 SHEETS — 5 SQUARES
 3-0237 — 200 SHEETS — 5 SQUARES
 3-0137 — 200 SHEETS — FILLER

COMET

SIMPLE POLE OR ZERO $(1 + j\omega T)$ LINEAR APPROXIMATIONS.

- (A) For $\omega T \ll 1$ $(1 + j\omega T) \approx 1$ $20 \log(1 + j\omega T) = 0 \text{ dB}$
- (B) $\omega T \gg 1$ $(1 + j\omega T) \approx j\omega T$ $20 \log(1 + j\omega T) \approx 20 \log_{10} \omega T$

- (A) Response is flat, 0dB
- (B) SAME AS POLE OR ZERO AT ORIGIN



THE INTERSECTION OF THESE 2 ASYMPTOTES IS CALLED A BREAK FREQUENCY, $\omega = \frac{1}{T}$

$\omega = \frac{1}{T}$ $20 \log_{10} |1 + j1| = 20 \log_{10} (2)^{1/2} = 3 \text{ dB}$



CURVE DEVIATES FROM asymptotes by 3dB at the break freq.

PHASE $\phi = \tan^{-1} \omega T$ at $\omega T = 0$ $\phi = 0^\circ$
 $\omega T \gg 0$ $\phi = 90^\circ$
 $\omega T = 1$ $\phi = 45^\circ$

POLE

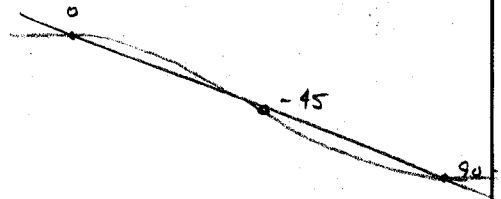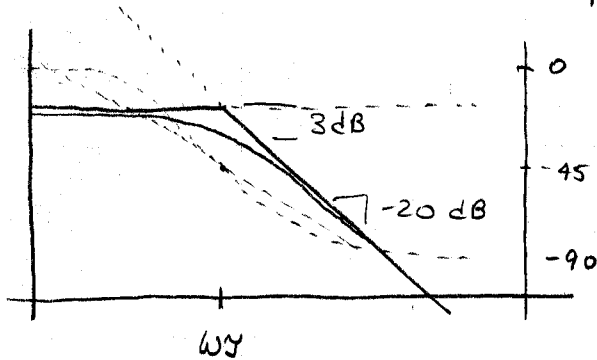

ZERO

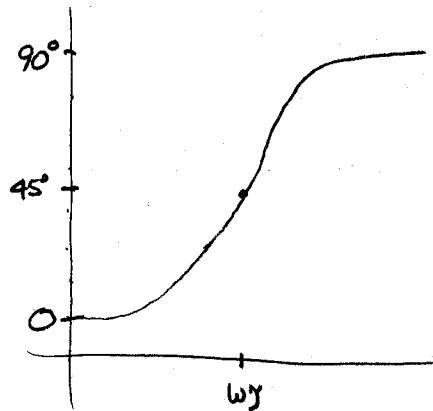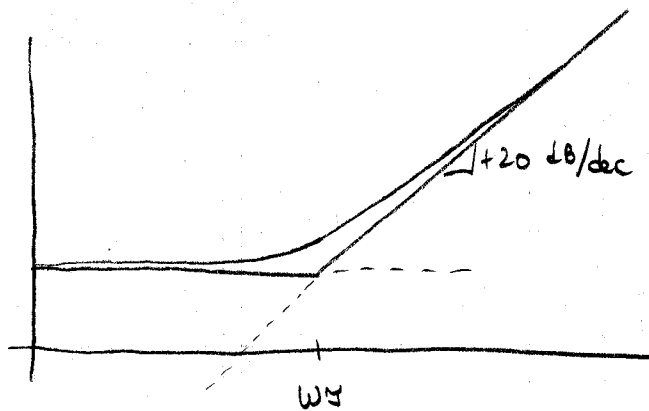

IF MULTIPLE POLES $(1 + j\omega T)^N$

SLOPE OF HIGH FREQ ASYMP. IS MULTIPLIED BY N
 DEVIATION FROM ACTUAL CURVE AT BREAK FREQUENCY IS 3NdB

PHASE CURVE EXTENDS FROM 0 TO N(90°) AND IS N(45°)
 AT BREAK FREQUENCY.

3-0235 — 50 SHEETS — 5 SQUARES
 3-0236 — 100 SHEETS — 5 SQUARES
 3-0237 — 200 SHEETS — 5 SQUARES
 3-0137 — 200 SHEETS — FILLER

COMET

QUADRATIC POLES OR ZEROS

$$1 + 2\zeta(j\omega T) + (j\omega T)^2$$

FUNCTION OF ω
AND ζ damping ratio

$\zeta > 1$ ROOTS ARE REAL AND UNEQUAL

$\zeta = 1$ REAL AND EQUAL

$\zeta < 1$ ROOTS COMPLEX CONJUGATES


FOR $\omega T \ll 1$ $20 \log [] = 0 \text{ dB}$

FOR $\omega T \gg 1$ $20 \log_{10} |1 - (\omega T)^2 + 2j\zeta(\omega T)| \approx 20 \log_{10} |(\omega T)^2| = 40 \log_{10} |\omega T|$

SLOPE OF log mag curve is $+40 \text{ dB/dec}$ FOR QUAD. ZERO
 -40 dB/dec FOR QUAD. POLE

BETWEEN THE EXTREMES, BEHAVIOR IS DEPENDENT ON ζ

FIG 12.13 p 678

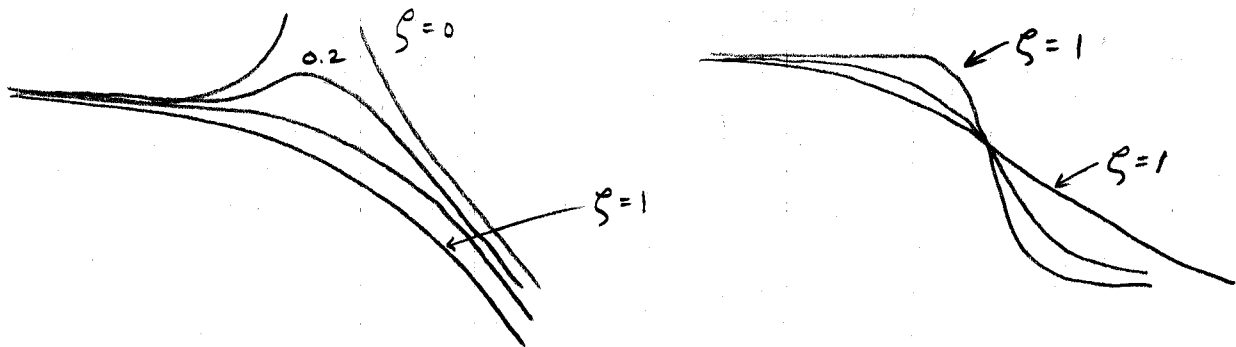

PHASE FROM 0 to -180° FOR POLES
0 to $+180$ FOR ZERO (INVERTED) $+90 \rightarrow 0^\circ$

3-0235 — 50 SHEETS — 5 SQUARES
3-0236 — 100 SHEETS — 5 SQUARES
3-0237 — 200 SHEETS — 5 SQUARES
3-0137 — 200 SHEETS — FILLER

COMET

EX 12.5

$$G_v(j\omega) = \frac{25j\omega}{(j\omega+0.5)[(j\omega)^2 + 4j\omega + 100]}$$

$$(j\omega+0.5)[(j\omega)^2 + 4j\omega + 100]$$

PUT IN STANDARD FORM

$$\frac{z}{2} = \frac{50j\omega}{(2j\omega+1)[(j\omega)^2 + 4j\omega + 100]}$$

$$\frac{\frac{1}{100}}{\frac{1}{100}} = \frac{0.5j\omega}{(2j\omega+1)\left(\left(\frac{j\omega}{10}\right)^2 + \frac{j\omega}{25} + 1\right)}$$


CONSTANT: 0.5

$$20 \log_{10}(0.5) = -6 \text{ dB} \quad 0^\circ \text{ dB}$$

ZERO AT ORIGIN:

$$+20 \text{ dB/dec} \quad +90^\circ \text{ CONSTANT}$$

POLE AT $\omega = \frac{1}{2}$:

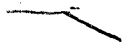

$$0 \rightarrow -90^\circ \quad -45^\circ @ \omega = \frac{1}{2}$$

QUADRATIC POLE:


$$\left(\frac{j\omega}{10}\right)^2 \quad \zeta = \frac{1}{10}$$

$$\frac{j\omega}{25}$$



$$2\zeta\gamma = \frac{1}{25}$$

$$\zeta = \frac{1}{25} \left(\frac{10}{1}\right) \left(\frac{1}{2}\right) = \frac{10}{50} = 0.2$$

pole at $\omega = 10$, $\zeta = 0.2$

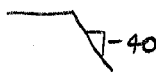

$$0 \rightarrow -180^\circ$$

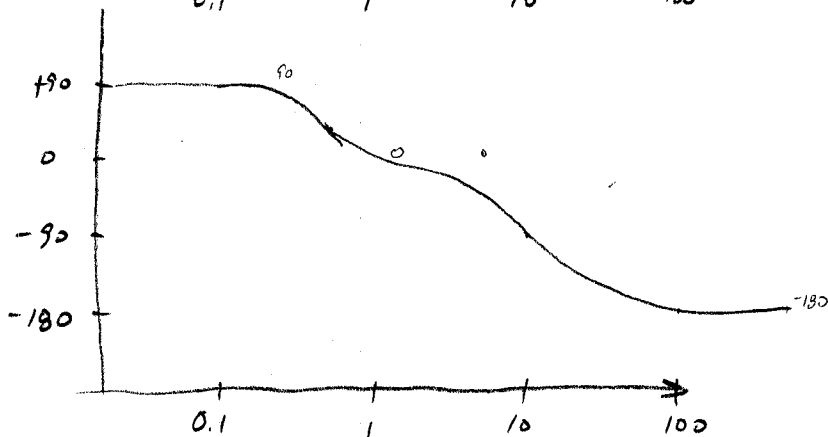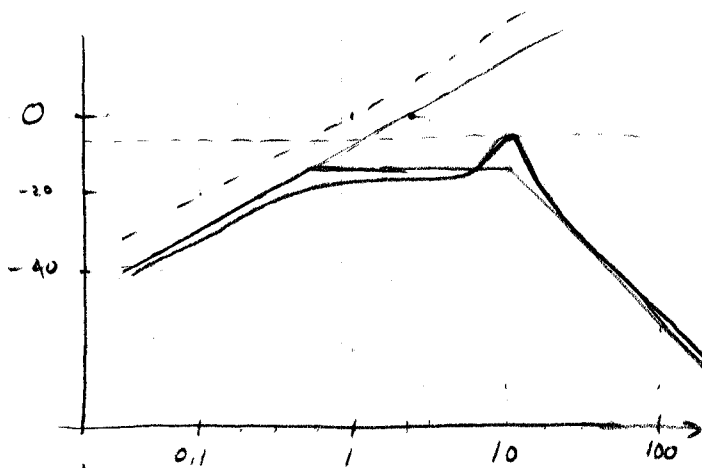


EX 12.4 $G(j\omega) = \frac{25(j\omega + 1)}{(j\omega)^2(0.1j\omega + 1)}$

CONSTANT: 25 $20 \log_{10} 25 = 28 \text{ dB}$ 0°

ORIGIN: DOUBLE POLE -40 dB/dec -180° for all ω


ZERO AT $\omega = 1$  $0 \rightarrow 90$

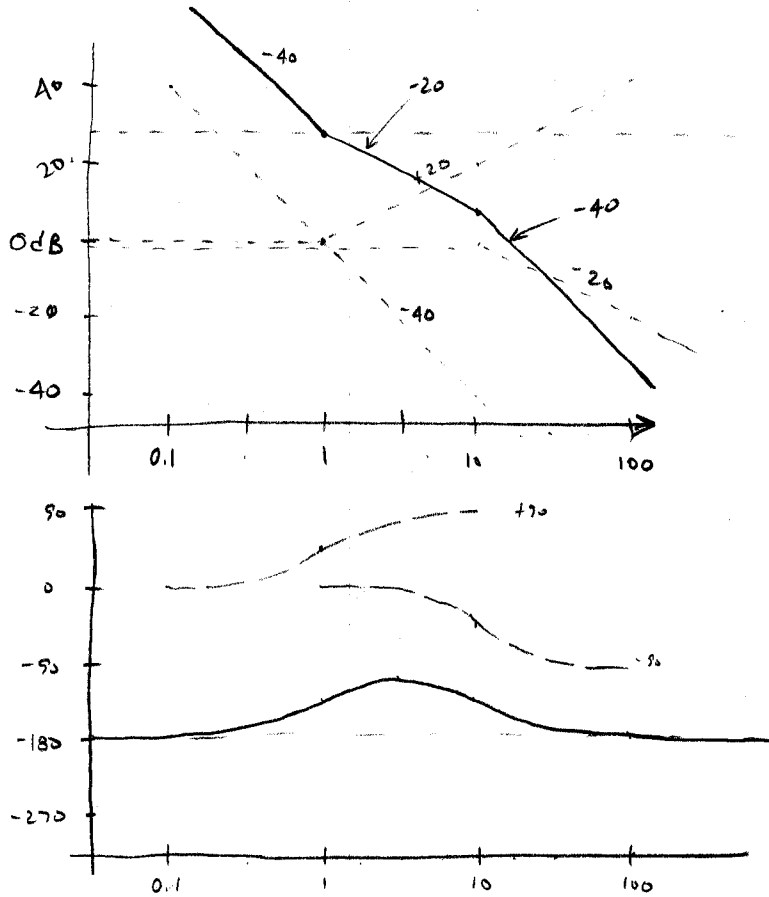POLE AT $\omega = 10$ $0 \rightarrow -90$






1/21

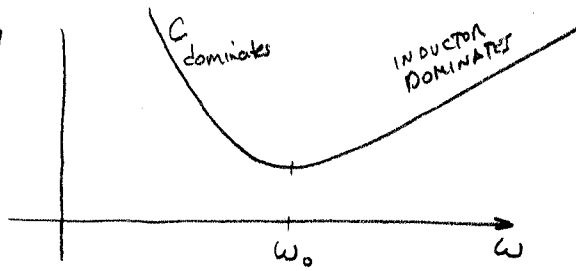

series eg goes to open
as L goes to open.


1/11

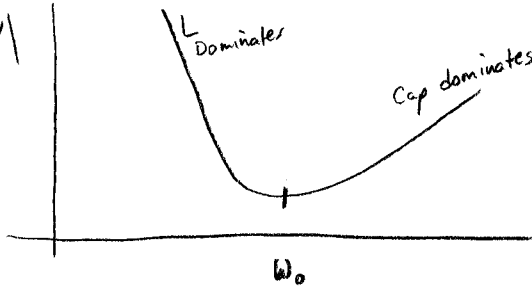

Parallel eg goes to short
as $\frac{1}{\omega C}$ goes to short

SERIES RLC - CURRENT IS COMMON TO ALL ELEMENTS
PARALLEL RLC - VOLTAGE " " " "

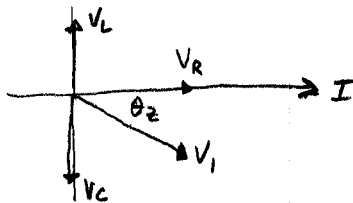SERIES CASE WHEN $\omega < \omega_0$ C DOMINATES $V_C > V_L$ θ_2 IS NEG




V_I LAGS I

$\omega = \omega_0$ $V_L = V_C$ $\theta_2 = 0$ V_I IN PHASE w/ I

$\omega > \omega_0$ $V_L > V_C$ $\theta_2 > 0$ V_I leads I

Parallel case

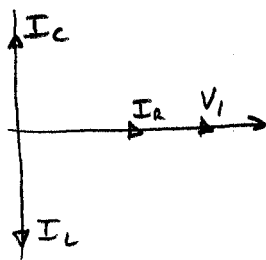

$\omega < \omega_0$ L DOMINATES $I_L > I_C$ V_I leads I

$\omega = \omega_0$ $I_L = I_C$

$\omega > \omega_0$ C DOMINATES $I_C > I_L$ I leads V

QUALITY FACTOR $Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 C R} = \frac{1}{R} \sqrt{\frac{L}{C}}$

Q IS AN IMPORTANT FACTOR

EX 12.3

$$G_r(j\omega) = \frac{10(0.1j\omega + 1)}{(j\omega + 1)(0.02j\omega + 1)}$$

CONSTANTS

$K_0 = 10$

$20 \log_{10} K_0 = 20 \text{ dB}$

Zeros
 $(0.1j\omega + 1)$

$20 \log_{10} |0.1j\omega + 1|$

0 dB for $0.1\omega \ll 1$
+20 dB/dec for $0.1\omega \gg 1$

BREAK AT $\omega = 10 \text{ rad/s}$



POLES

$(j\omega + 1)$

Break
 $\omega = 1$

$(0.02j\omega + 1)$



$\omega = 50 \text{ rad/s}$

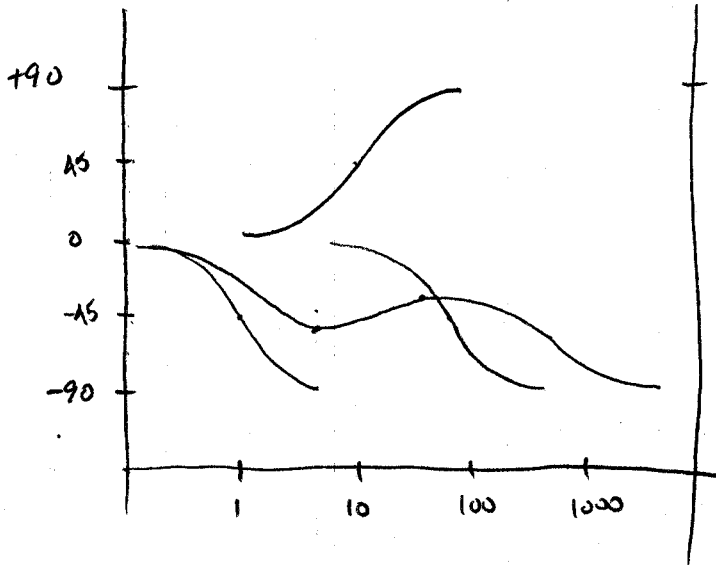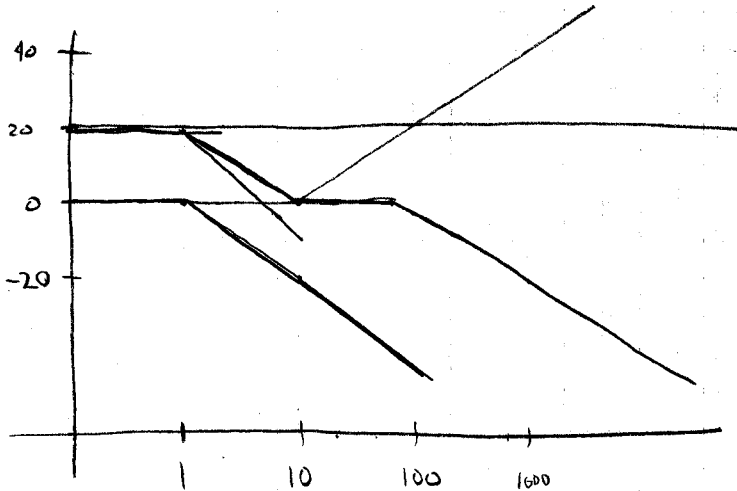

3-0235 — 50 SHEETS — 5 SQUARES
3-0236 — 100 SHEETS — 5 SQUARES
3-0237 — 200 SHEETS — 5 SQUARES
3-0137 — 200 SHEETS — FILLER

COMET
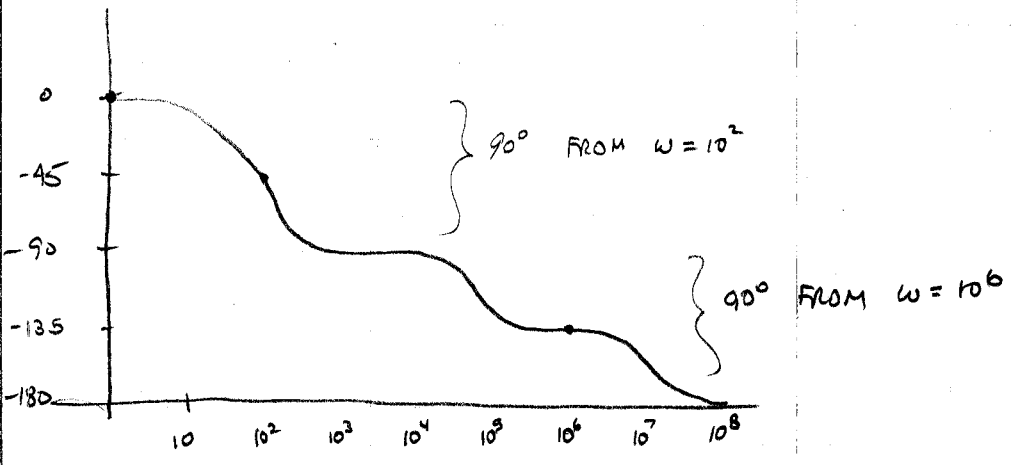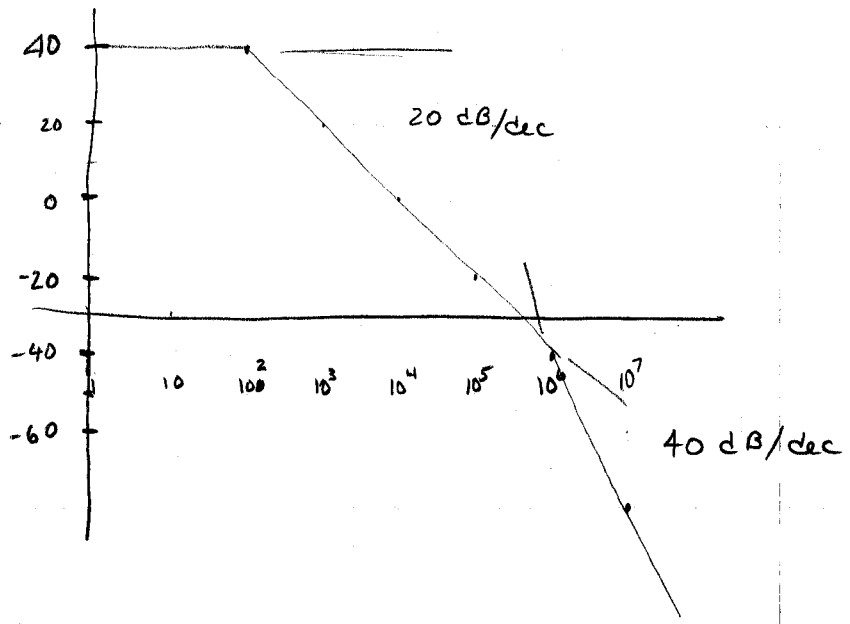
$$H(j\omega) = \frac{100}{(1 + j\omega/10^2)(1 + j\omega/10^6)}$$




22-141 50 SHEETS
22-142 100 SHEETS
22-144 200 SHEETS



SUPERPOSITION OF POLES

Ex 1

$$H(j\omega) = \frac{1}{1 + j\omega/10^4}$$

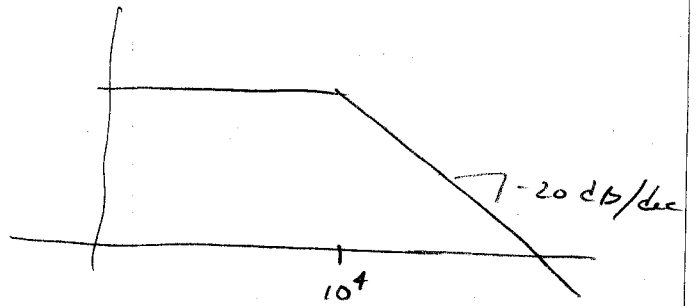

Ex 2


$$H(j\omega) = \frac{1}{(1 + j\omega/10^4)(1 + j\omega/10^4)} = \frac{1}{(1 + j\omega/10^4)^2} = \frac{1}{1 + \frac{2j\omega}{10^4} - \frac{\omega^2}{10^8}}$$

quadratic

$$\left| \frac{1}{(1 + j)(1 + j)} \right| = \left| \frac{1}{1 + 2j - 1} \right| = \left| \frac{1}{2j} \right| = \frac{1}{2}$$

$\omega = 10^4$
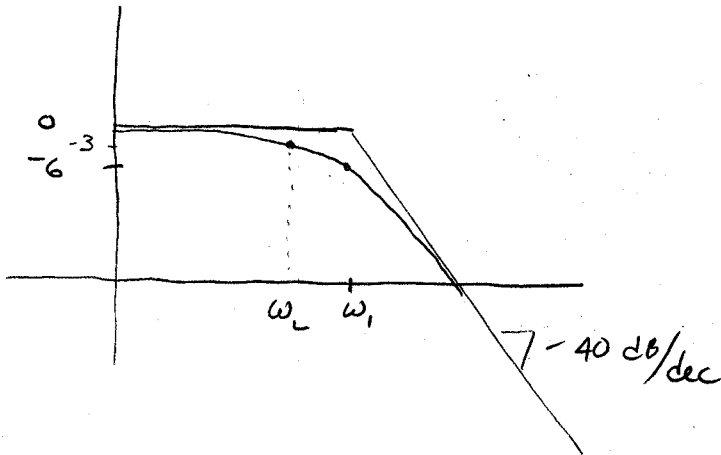
$$\frac{1}{2} \text{ or } 20 \log_{10} .5 = -6 \text{ dB}$$




$$\left(1^2 + \frac{\omega^2}{10^8} \right) = \frac{1}{\sqrt{2}} = .707$$

$$\frac{\omega^2}{10^8} = .293$$

$$\omega^2 = .293 \times 10^8 = \boxed{5.4 \times 10^3 = \omega_L}$$
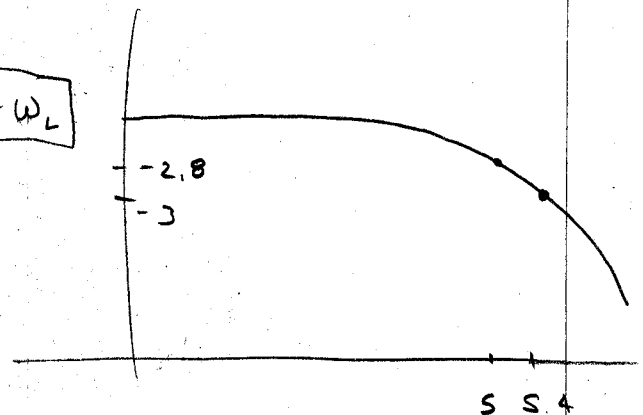
$$\frac{1}{\omega_L} \approx \frac{1}{10^4} + \frac{1}{10^4} = \frac{1}{5 \times 10^3}$$



CONT'D

INTRODUCTION TO THE SUPERPOSITION OF POLES

$$H(j\omega) = \frac{1}{(1 + j\omega/10^4)(1 + j\omega/2 \times 10^4)}$$

$\omega_1 = 10^4$

$\omega_2 = 2 \times 10^4$

FIND ω_H : $|H(j\omega)| = \frac{1}{\sqrt{2}}$

$$\frac{1}{\sqrt{2}} = \frac{1}{1 + \frac{j\omega}{2 \times 10^4} + \frac{j\omega}{2 \times 10^4} + \frac{-\omega^2}{2 \times 10^8}}$$

$1.5 + 1.5j = 2.12$

$1 + \frac{3j\omega}{2 \times 10^4} = \sqrt{2}$

$\frac{1}{2.12}$

$\textcircled{\omega = 10^4 - 6.5 \text{ dB}}$

$\frac{3\omega}{2 \times 10^4} = 1$

$\omega_H = \frac{2 \times 10^4}{3} = \textcircled{0.67 \times 10^4}$

$$\frac{1}{\omega_H} \approx \frac{1}{\omega_1} + \frac{1}{\omega_2}$$

$$= \frac{1}{10^4} + \frac{1}{2 \times 10^4}$$

$\frac{1}{\omega_H} = \frac{2 + 1}{2 \times 10^4}$

$\omega_H = \frac{2 \times 10^4}{3} = 0.67 \times 10^4$

	-1.5 dB	-2.07 dB	-2.8 dB
\textcircled{Q}	.55	.67	.8
	.151	-.224	-.320
	.275	j.335	j.4
	j.55	j.670	j.8
	j.825 + .85 544	j.78	
	$\textcircled{\approx 0.8 \times 10^4}$		

Estimation is conservative so is acceptable to use.



ALL POLES ω_1 through ω_n are higher than ω_H , so evaluated at ω_H ,
 $(j\omega)^2 \left(\frac{1}{\omega_1 \omega_2} + \frac{1}{\omega_1 \omega_3} + \dots \right)$ and higher order terms ~ 0 can be ignored.

$$H_H(j\omega) \approx \frac{A_0}{1 + j\omega \left(\frac{1}{\omega_1} + \frac{1}{\omega_2} + \dots + \frac{1}{\omega_n} \right)} = \frac{A}{1 + j \frac{\omega}{\omega_H}}$$

PARALLEL COMBINATION OF POLES
 \Rightarrow SUPERPOSITION OF POLES.

$$\left(\frac{1}{10^4} + \frac{1}{2 \times 10^4} \right) = .67 \times 10^{-4} = \omega_H$$

LO-FREQ LIMIT

$$H(j\omega) = A_0 H_L = \frac{A_0 (j\omega/\omega_a)(j\omega/\omega_b)(j\omega/\omega_n)}{(1 + j\omega/\omega_a)(1 + j\omega/\omega_b) \dots}$$

$$H(j\omega) = \frac{A_0}{\left(\frac{\omega_a}{j\omega} + 1 \right) \left(\frac{\omega_b}{j\omega} + 1 \right) \dots} = \frac{A_0}{1 + \frac{1}{j\omega} (\omega_a + \omega_b + \dots + \omega_n) + \frac{1}{(j\omega)^2} (\omega_a \omega_b + \dots)} + \frac{1}{(j\omega)^3} (\dots)$$

$\omega_a, \omega_b, \dots, \omega_n$ are lower in frequency than the actual ω_L
 so evaluating $H_L(j\omega) \Big|_{\omega=\omega_L}$, we can ignore terms

of $\frac{1}{\omega^2}$ or higher. $\frac{1}{(j\omega_L)^2} (\omega_a \omega_b + \dots + \omega_a \omega_c)$

$$A_0 H_L(j\omega) = \frac{A_0}{1 + \frac{1}{j\omega} (\omega_a + \omega_b + \dots + \omega_n)} \cdot \frac{j\omega/\omega_a + \dots}{j\omega/\omega_a + \dots}$$


$$= A_0 \frac{j\omega/(\omega_a + \omega_b + \dots)}{1 + \frac{j\omega}{\omega_L} (\omega_a + \omega_b + \dots)} = \frac{A_0 \frac{j\omega}{\omega_L}}{1 + \frac{j\omega}{\omega_L}}$$

$$\omega_L = \omega_a + \omega_b + \dots$$

"series" superposition of lo-FREQ poles

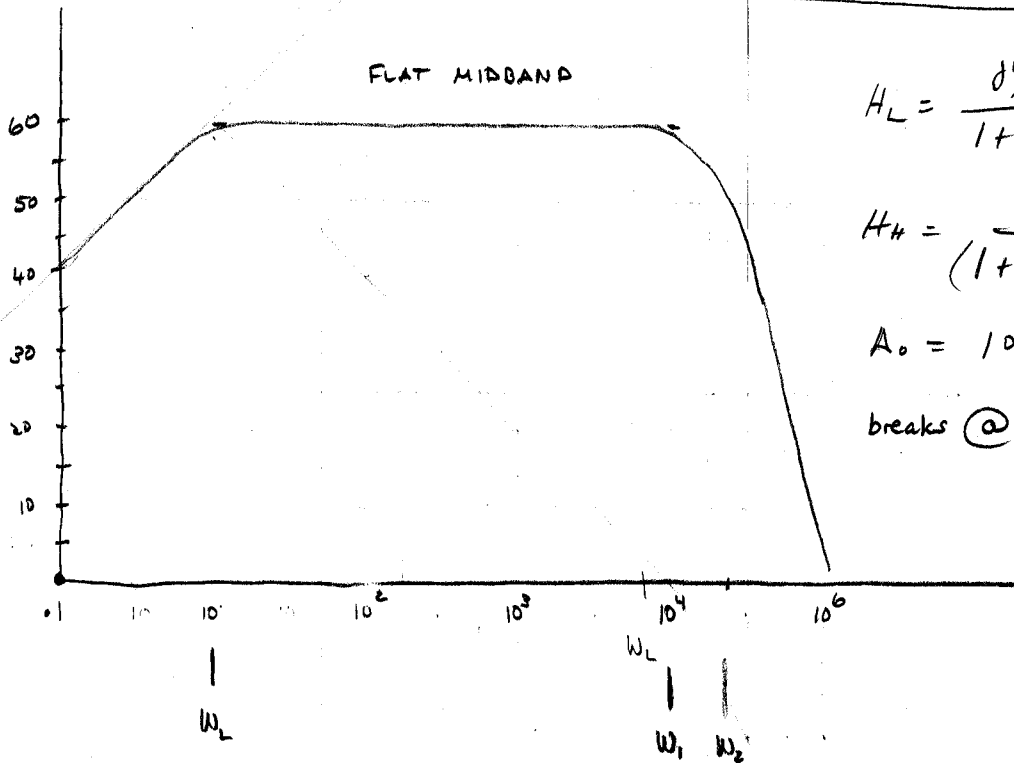9.2.3 HI, LO, AND MIDBAND FREQUENCY LIMITS CONT'D

$$H(j\omega) = 1000 \frac{j\omega/10}{(1 + j\omega/10)(1 + j\omega/10^4) [1 + j\omega/2 \times 10^4]}$$



$$H_L = \frac{j\omega/10}{1 + j\omega/10}$$

$$H_H = \frac{1}{(1 + j\omega/10^4)(1 + j\omega/2 \times 10^4)}$$

$$A_0 = 1000$$

breaks @ $\omega_2 = 10$ (zero)
 $\omega_1 = 10^4$ pole
 $\omega_2 = 2 \times 10^4$ pole

Lo 3dB Freq

$$|H|_{\omega_H} = \frac{1000}{\sqrt{2}} = \frac{100 \omega_H}{[1 + (\omega_H/10^2)]^{1/2} [1 + (\omega_H/10^4)]^{1/2} [(1 + \omega_H/2 \times 10^4)^2]^{1/2}}$$

$$\omega_H = 0.84 \times 10^4$$

SUPER POSITION OF POLES

$$H(j\omega) = A_0 H_L \cdot H_H$$

$$= A_0 \left[\left(\frac{j\omega/\omega_a}{1 + j\omega/\omega_a} \right) \left(\frac{j\omega/\omega_b}{1 + j\omega/\omega_b} \right) \dots \right] \left[\left(\frac{1}{1 + j\omega/\omega_1} \right) \left(\frac{1}{1 + j\omega/\omega_2} \right) \dots \right]$$

NEAR ω_H : $H(j\omega) \cong A_0 H_H = \frac{A}{(1 + j\omega/\omega_1)(1 + j\omega/\omega_2) \dots}$ $H_L(j\omega) \cong 1$

$$1 + j\omega \left(\frac{1}{\omega_1} + \frac{1}{\omega_2} + \dots + \frac{1}{\omega_n} \right) + j\omega^2 \left(\frac{1}{\omega_1 \omega_2} + \frac{1}{\omega_1 \omega_n} + \frac{1}{\omega_2 \omega_n} + \dots \right) + j\omega^3 \left(\frac{1}{\omega_1 \omega_2 \omega_n} \right) + \dots$$

22-141 50 SHEETS
 22-142 100 SHEETS
 22-144 200 SHEETS



SUMMARY

$$\omega_H = \omega_1 || \omega_2 || \dots || \omega_n$$

$$\omega_L = \omega_a + \omega_b \dots \omega_m$$

parallel superposition
of HI-FREQ POLES
series combination
of LO-FREQ POLES.

EX

9.34

$$H(j\omega) = \frac{100 (j\omega)^2}{(1 + j\omega/20)(1 + j\omega/50)(1 + j\omega/75)(1 + j\omega/10^4)(1 + j\omega/2 \times 10^4)}$$

$$H(j\omega) = A_0 H_L H_H = \left[\frac{100 (j\omega)^2}{(1 + \frac{j\omega}{20})(1 + \frac{j\omega}{50})(1 + \frac{j\omega}{75})} \right] \left[\frac{1}{(1 + \frac{j\omega}{10^4})(1 + \frac{j\omega}{2 \times 10^4})} \right]$$

AT $\omega < 10^4$ $\omega \sim 10^3$

$$H(j\omega) \approx \frac{100 (j10^3)^2}{(\frac{10^2}{2})(\frac{10^2}{5})(\frac{10^2}{7.5})} \left[\frac{1}{(1 + .j)(1 + .05j)} \right] \quad \begin{matrix} 137.5 \\ \text{137.5} \end{matrix}$$

AT $\omega \sim 10^2$

$$H(j\omega) \approx \frac{100 (10^2)^2}{(\frac{10}{2})(\frac{10}{5})(\frac{10}{7.5})} \quad 137.5$$

22-141 50 SHEETS
22-142 100 SHEETS
22-144 200 SHEETS



FREQUENCY AND TIME-DEPENDENT RESPONSE
(LIMITATIONS) (TIME DELAYS)

CAUSED BY ENERGY STORAGE ELEMENTS : CAPACITORS, INDUCTORS.

CAPACITORS


PURPOSELY USED ① SHAPE FREQUENCY RESPONSE
② ISOLATE BIAS VOLTAGES

NATURALLY PRESENT IN PHYSICAL STRUCTURE.

STRAY CAPACITANCE AND INDUCTANCE OF WIRES, INTERCONNECTORS

INDUCTANCE

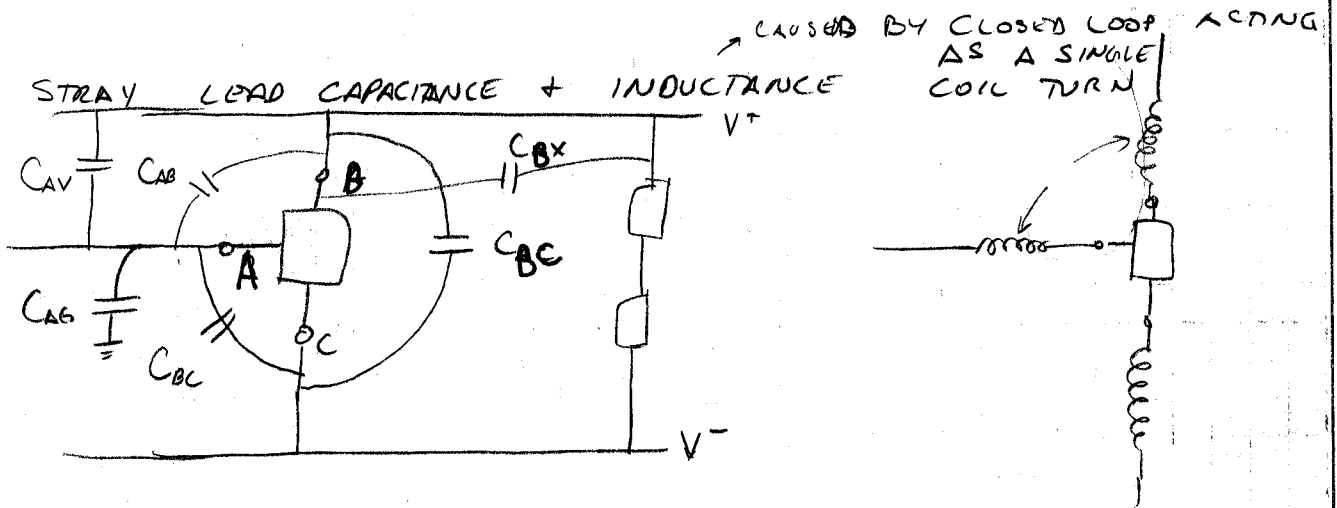MAINLY PARASITIC. IMPORTANT WELL ABOVE BREAKPOINT FREQ'S.



FOR pn Junction

DEPLETION CAPACITANCE	C_j	REVERSED BIAS	C_{CB}
DIFFUSION CAPACITANCE	C_d	FORWARD BIAS	C_{BE}

IN BJT: BE FORWARD BIASED C_{π} BC REVERSED BIAS C_{μ}



LATERAL BASE RESISTANCE r_x MUST BE INCLUDED WHEN CONSIDERING C_{π} , C_{μ}

50 SHEETS
100 SHEETS
200 SHEETS
22-141
22-142
22-146



INTERNAL CAPACITANCE IN PN JUNCTION

REVERSED BIAS :

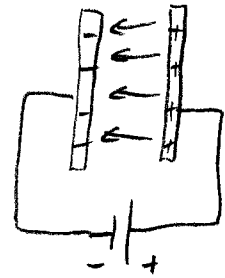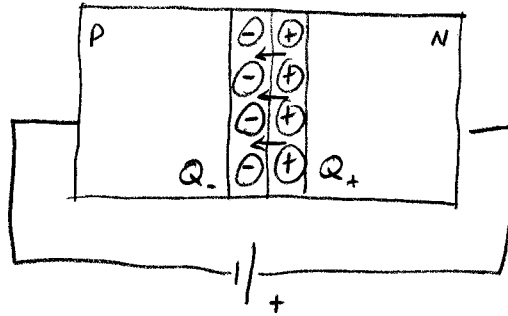

IMMOBILE ION CORES CREATE INTERNAL BUILT-IN-FIELD
SIMILAR TO CONDUCTING PLATES CAPACITOR



CAPACITANCE OF pn JUNCTION OR JUNCTION CAPACITANCE C_j

FORWARD BIAS :

current flow through the junction :


Holes injected by V_D from p-side to n-side
 e^- " " from n-side to p-side

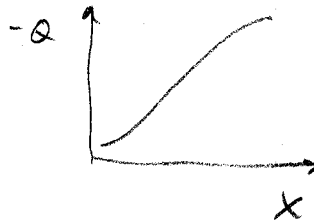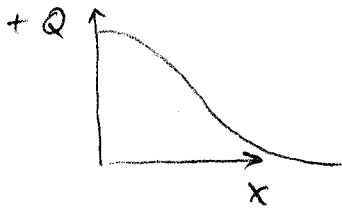INJECTED CHARGES BUILD UP CARRIER-CONCENTRATION
GRADIENTS THAT DELAY FROM THE DEPLETION REGION.



C_d

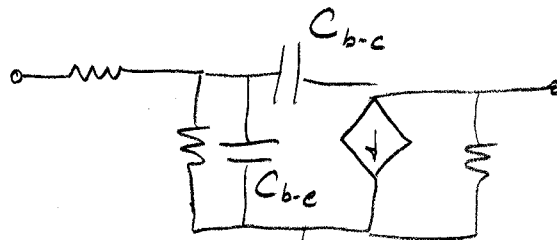INA BJT B-E IS FWD BIAS.
 B-C IS REV BIAS.



NO CAPACITANCE FROM e-c

22-141 50 SHEETS
 22-142 100 SHEETS
 22-144 200 SHEETS



9.1.6 JFET CAPACITANCE


$$C_{gs} = A \left(\frac{qE}{2} \frac{N_A N_D}{N_A + N_D} \right)^{1/2} (\psi_0 - \psi_{gs})^{-1/2}$$

$$C_{gs} \rightarrow 1-3 \text{ pF}$$

9.2 SINUSOIDAL STEADY-STATE AMPLIFIER RESPONSE

SYSTEM FUNCTION OR TRANSFER FUNCTION

Bode Plots

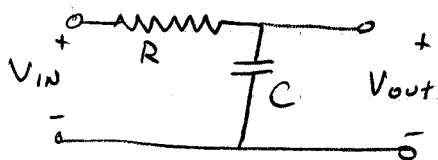


$$\begin{aligned} \text{TRANSFER FCN} = \frac{V_{out}}{V_{in}} &= \frac{1/j\omega C}{R + 1/j\omega C} \\ &= \frac{1}{1 + j\omega RC} = \frac{1}{1 + j\omega/\omega_c} \end{aligned}$$



FOR $\omega \ll \frac{1}{RC}$ $\omega RC \ll 1$ $\left| \frac{V_{out}}{V_{in}} \right| = 1$ $\angle = 0^\circ$

FOR $\omega \gg \frac{1}{RC}$ $\omega RC \gg 1$ $\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\omega RC}$ $\angle_{\omega RC} = -90^\circ$

FOR $\omega = \frac{1}{RC}$ $\omega RC = 1$ $\left| \frac{V_{out}}{V_{in}} \right| = \left| \frac{1}{1+j} \right| = \frac{1}{\sqrt{2}} = .707$

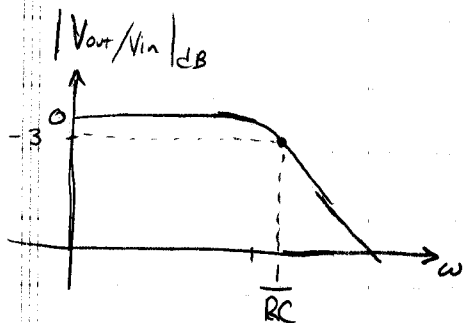

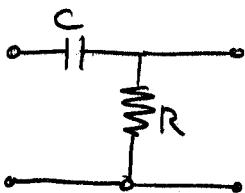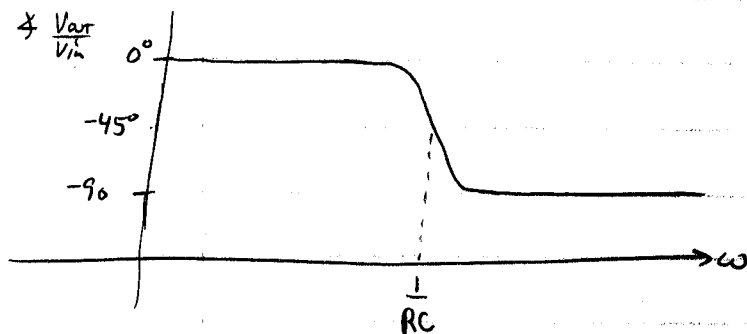
$$\angle \frac{V_{out}}{V_{in}} = \angle \frac{1}{1+j} = -45^\circ$$



$$\frac{V_{out}}{V_{in}} = \frac{R}{R + 1/j\omega C} = \frac{j\omega RC}{1 + j\omega RC}$$

$$\omega_c = \frac{1}{RC}$$

ω_c is a breakpoint

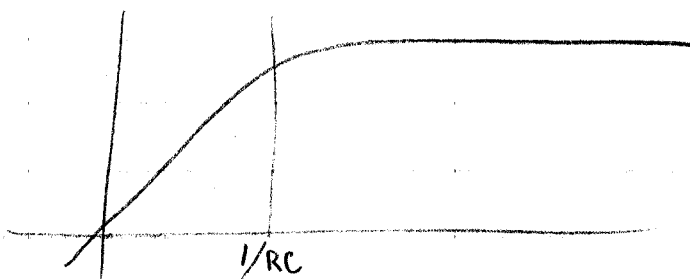

CH 9

FREQUENCY RESPONSE AND TIME-DEPENDENT CIRCUIT BEHAVIOR


C_j = depletion capacitance small signal reverse-biased junction cap.
 $C_j = k_j (V_0 - V_0)^{-n}$

C_d = diffusion capacitance forward biased
 $C_d = K_d I_s e^{-V_0/nT} \approx K_d I_D$

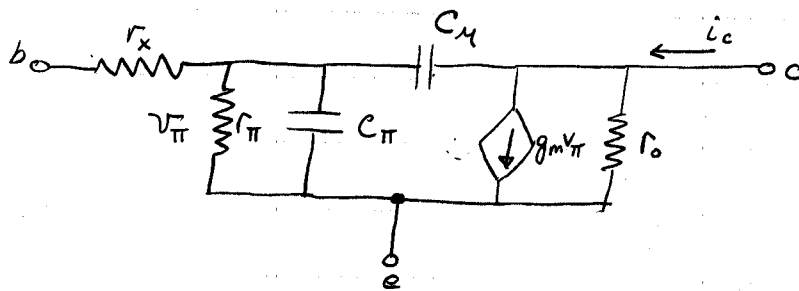9.1.4 BJT CAPACITANCE

$$C_{d-be} = \frac{W^2 I_c}{2DnV_T}$$


$W \equiv$ WIDTH OF BASE REGION
 $D \equiv$ MINORITY-CARRIER DIFFUSION CONSTANT.



$$g_m v_{\pi} = g_m (\pi i_{\pi})$$

$$= \beta_0 i_{\pi}$$


$$\neq \beta_0 i_b$$

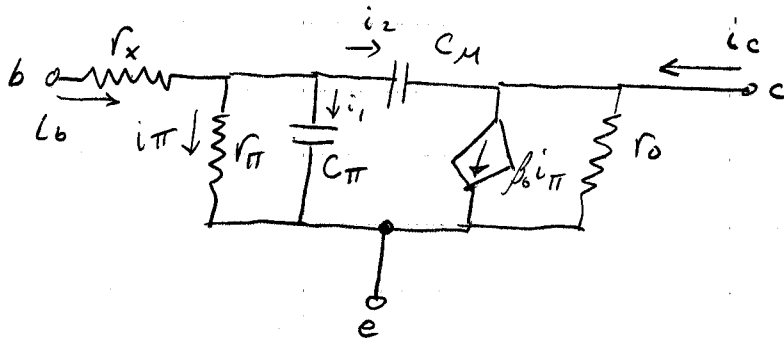

$$C_{\pi} = C_{be}$$

$$i_b = i_{\pi} + i_1 + i_2$$

$$C_{\mu} = C_{bc} = C_{ob}$$

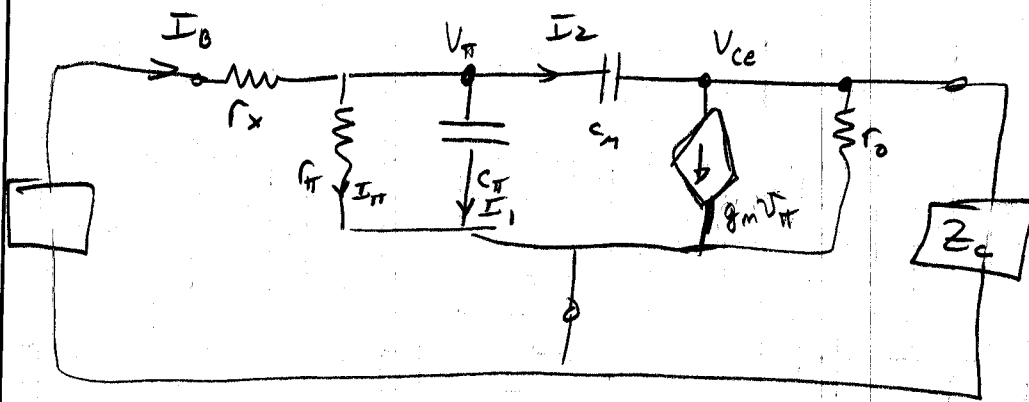

$$I_b = I_{\pi} + I_1 + I_2$$

$$\beta = g_m r_{\pi}$$

IN OTHER MODEL $I_c = \beta_0 i_b$ OR $g_m V_{\pi} = g_m (r_{\pi} i_b)$

IN THIS MODEL $g_m V_{\pi} = g_m (r_{\pi} i_{\pi}) \neq \beta_0 i_b$
 $i_b \neq i_{\pi}$

W/ C_{π}, C_{μ} INCLUDED i_{π} IS FCN OF ω .

$g_m V_{\pi}$ IS FCN OF ω

β_0 CAN BE REPRESENTED AS FCN OF ω $\beta(\omega)$

AS $\omega \uparrow$, $i_{\pi} \downarrow \Rightarrow \beta \downarrow$

$$I_{\pi} = \frac{V_{\pi}}{r_{\pi}}$$

$$I_1 = \frac{V_{\pi}}{1/j\omega C_{\mu}} = V_{\pi} (j\omega C_{\mu})$$

$$I_2 = \frac{V_{\pi} - V_{ce}}{1/j\omega C_{\mu}} = (V_{\pi} - V_{ce}) j\omega C_{\mu}$$

$$I_b = \frac{V_{\pi}}{r_{\pi}} + V_{\pi} (j\omega C_{\mu}) + V_{\pi} (j\omega C_{\mu}) - V_{ce} (j\omega C_{\mu})$$

$$V_{\pi} = \frac{I_b r_{\pi} + (j\omega r_{\pi} C_{\mu}) V_{ce}}{1 + j\omega r_{\pi} (C_{\pi} + C_{\mu})}$$

$$V_{\pi} = \frac{I_b r_{\pi} + (j\omega r_{\pi} C_M) V_{ce}}{1 + j\omega r_{\pi} (C_{\pi} + C_M)}$$

$\omega \rightarrow 0$

$$V_{\pi} = I_b r_{\pi}$$

$$g_m V_{\pi} = \beta_0 i_b$$

ω large $|j\omega C_M V_{ce}| \ll I_b$

I_2 through C_M is small, $V_{ce} \sim (\beta_0 I_{\pi})(Z_c || r_o)$

Z_c is ss Z of collector circuit.

$$|j\omega C_M \beta_0 I_{\pi} Z_c || r_o| \ll I_b$$

I_b is ALWAYS larger than I_{π} :

$$|\beta_0 Z_c || r_o| \ll \frac{1}{\omega C_M}$$

\uparrow $\beta_0 \times Z_{LOAD}$ \uparrow Z of C_M

THIS CAUSES SMALL I_2 .

SMALL $C_M \Rightarrow$ Large $\frac{1}{\omega C_M}$

$$V_{\pi} \approx \frac{I_b r_{\pi}}{1 + j\omega r_{\pi} (C_{\pi} + C_M)}$$

$$g_m V_{\pi} \approx \frac{g_m r_{\pi} I_b}{1 + j\omega r_{\pi} (C_{\pi} + C_M)} \equiv \beta(\omega) I_b$$

$$\beta(\omega) = \frac{g_m r_{\pi}}{1 + j\omega r_{\pi} (C_{\pi} + C_M)} = \frac{\beta_0}{1 + j\omega r_{\pi} (C_{\pi} + C_M)}$$

3-0235 — 50 SHEETS — 5 SQUARES
 3-0236 — 100 SHEETS — 5 SQUARES
 3-0237 — 200 SHEETS — 5 SQUARES
 3-0137 — 200 SHEETS — FILLER

COMET

\approx Become = When collector shorted to emitter

$\beta(\omega) \equiv$ short circuit s.s. current gain.

at pole $\omega_H = \frac{1}{r_{\pi}(C_{\pi} + C_{\mu})}$ $\beta(\omega) = \beta_0$

AT $\omega > \omega_H$ THINGS FALL APART.

FIGURE OF MERIT FOR BJT :

ω when $\beta(\omega) = 1$ UNITY GAIN frequency ω_T .


$\omega_T \gg \omega_H$

$$|\beta(\omega)|_{\omega=\omega_T} = \left| \frac{\beta_0}{1 + j\omega_T r_{\pi}(C_{\pi} + C_{\mu})} \right| = 1$$

$$\left[1 + \omega_T^2 r_{\pi}^2 (C_{\pi} + C_{\mu})^2 \right]^{1/2} \approx \omega_T r_{\pi}(C_{\pi} + C_{\mu}) = \beta_0$$

$$\omega_T = \frac{\beta_0}{r_{\pi}(C_{\pi} + C_{\mu})} = \frac{g_m}{C_{\pi} + C_{\mu}}$$
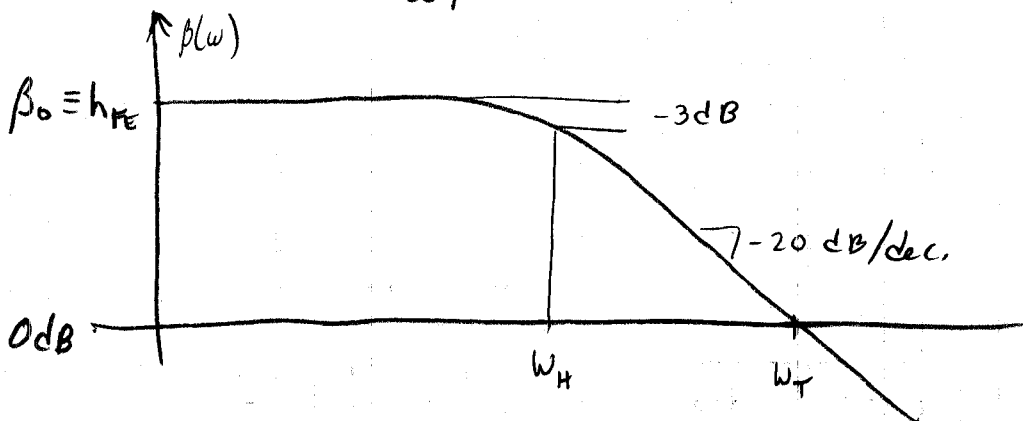
$$C_{\pi} = \frac{g_m}{\omega_T} - C_{\mu}$$



3-0235 — 50 SHEETS — 5 SQUARES
 3-0236 — 100 SHEETS — 5 SQUARES
 3-0237 — 200 SHEETS — 5 SQUARES
 3-0137 — 200 SHEETS — FILLER

COMET

UNITY GAIN frequency ω_T : A FIGURE OF MERIT.

$$|\beta(\omega)|_{\omega=\omega_T} = \left| \frac{\beta_0}{1 + j\omega_T r_{\pi} (C_{\pi} + C_M)} \right| = 1$$

$$j\omega_T r_{\pi} (C_{\pi} + C_M) = \beta_0$$

$$\omega_T = \frac{\beta_0}{r_{\pi} (C_{\pi} + C_M)} \equiv \frac{g_m}{C_{\pi} + C_M} = \omega_T$$

$$C_{\pi} = \frac{g_m}{\omega_T} - C_M$$

C_M and ω_T can be measured easily.

$$\beta(\omega) = h_{fe}(\omega) = h_{fe}$$

$$\beta_0 = h_{fe}$$

ω_H = pole frequency

$$C_{\pi} \propto g_m \propto I_C$$

9.1.5 CAPACITANCE IN THE MOSFET

$$C = \frac{\epsilon_{ox} A}{t_{ox}}$$

ϵ_{ox} \equiv dielectric of permittivity of oxide layer

A \equiv Area of conducting plates

t_{ox} \equiv THICKNESS OF OXIDE

$$C_{gs} = \frac{\epsilon_{ox} A}{t_{ox}}$$


$$A = WL$$

for



$$V_{DS} \ll V_{GS}$$

$$C_{gs} = \frac{2}{3} \frac{\epsilon_{ox} A}{t_{ox}}$$
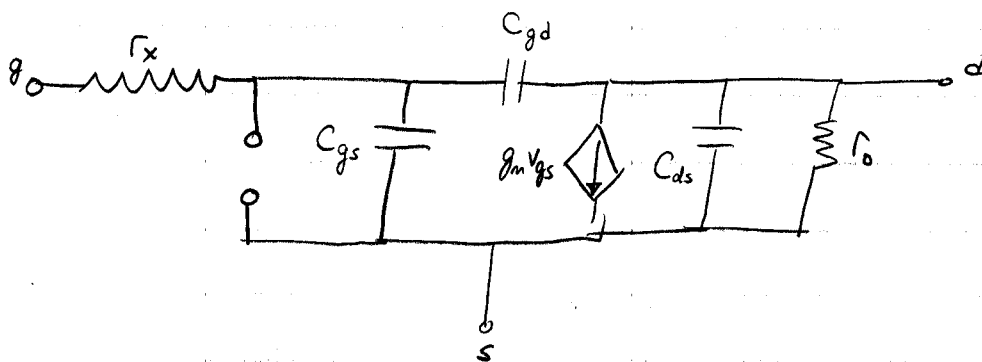
$$\text{for } V_{DS} \sim (V_{GS} - V_{TR})$$



INTERNAL CAPACITANCE IN FET

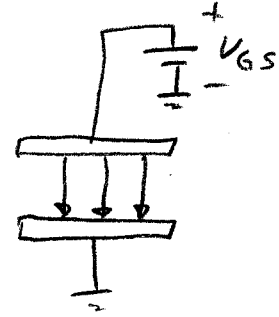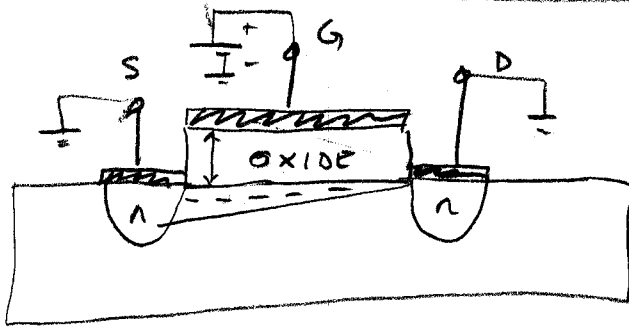


VOLTAGE APPLIED TO GATE CREATES CHARGED PLATE.
SUBSTRATE IS OTHER PLATE

E IS WEAKER NEAR DRAIN END OF CHANNEL

$$C_{gs} > C_{gd}$$

NO CAPACITANCE FROM DRAIN TO SOURCE

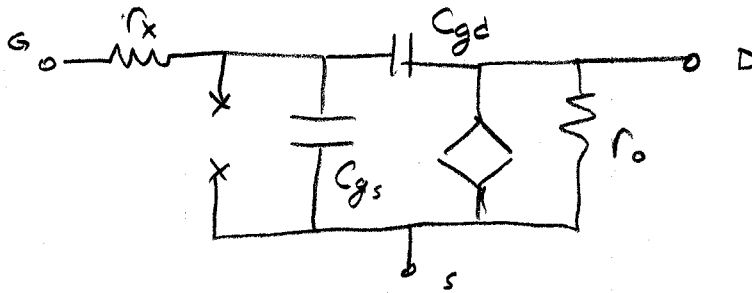

SAME MODEL FOR JFET,