

**Problem 0:** Follow the instructions for account setup and homework workflow on the course procedures page, <http://www.ece.lsu.edu/koppel/v/proc.html>. Run the testbench on the unmodified file. There should be errors on all but the `min_4` (Four-element) module. Try modifying `min_4` so that it simulates but produces the wrong answer. Re-run the simulator and verify that it's broken. Then fix it.

Note: There are no points for this problem.

**Problem 1:** Module `min_n` has an `elt_bits`-bit output `elt_min` and an `elt_count`-element array of `elt_bits`-bit elements, `elts`. Complete `min_n` so that `elt_min` is set to the minimum of the elements in `elts`, interpreting the elements as unsigned integers. Do so using a linear connection of `min_2` modules instantiated with a `genvar` loop. (A linear connection means that the output of instance  $i$  is connected to the input of instance  $i + 1$ .)

Verify correct functioning using the testbench.

**Problem 2:** Module `min_t` is to have the same functionality as `min_n`. Complete `min_t` so that it recursively instantiates itself down to some minimum size. The actual comparison should be done by a `min_2` module.

Verify correct functioning using the testbench.

**Problem 3:** By default the synthesis script will synthesize each module for two array sizes, four elements and eight elements.

(a) Run the synthesis script unmodified. Use the command `rc -files syn.tcl`. Explain the differences in performance between the different modules.

(b) Modify and re-run the synthesis script so that it synthesizes the modules with `elt_bits` set to 1.

The synthesis program should do a better job on the behavioral and linear models. Why do you think that is? *Hint: The 1-bit minimum module is equivalent to another common logic component that the synthesis program can handle well.*