

Name \_\_\_\_\_

Digital Design using HDLs  
EE 4755  
Midterm Examination  
Wednesday, 28 October 2015 11:30-12:20 CDT


Problem 1 \_\_\_\_\_ (20 pts)  
Problem 2 \_\_\_\_\_ (20 pts)  
Problem 3 \_\_\_\_\_ (20 pts)  
Problem 4 \_\_\_\_\_ (20 pts)  
Problem 5 \_\_\_\_\_ (20 pts)

Alias \_\_\_\_\_

Exam Total \_\_\_\_\_ (100 pts)

*Good Luck!*

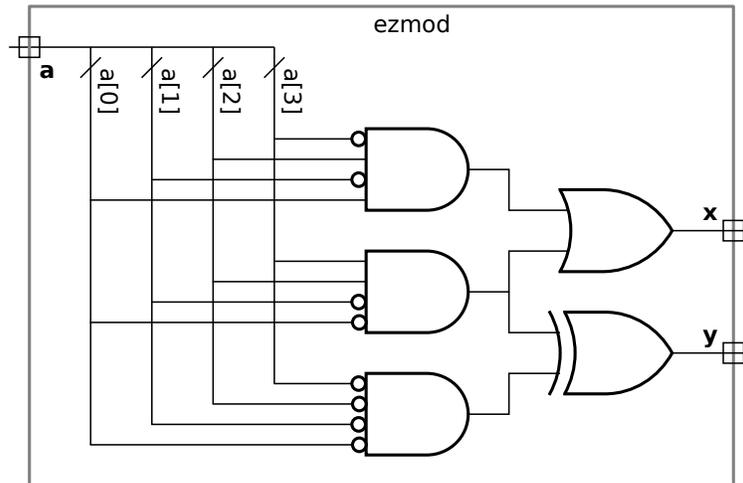Problem 1: [20 pts] Complete the Verilog description of the hardware illustrated below. It's okay—and a time saver—to use the == operator.



- Complete the port declarations.
- Complete the module.

```

module ezmod
  ( output
    input
    // DON'T FORGET
  ); // THE PORTS

```

endmodule

Problem 2: [20 pts] Consider the module below.

```
module ssum #( int n = 3,          int f = 4,          int swid = f + $clog2(n) )
              ( output logic [swid-1:0] sum,
                input uwire [n-1:0] mask,          input uwire [f-1:0] a[n] );
  always @* begin
    sum = 0;
    for ( int i=0; i<n; i++ ) if ( mask[i] ) sum += a[i];
  end
endmodule
```

(a) Show the hardware that will be synthesized without optimization and using default parameters.

Hardware without optimization.

(b) Show the hardware that will be synthesized using the default parameters with optimization. In particular, try to make use of a four-input multiplexor for the first two iterations of the *i* loop.

Hardware with optimization and using a four-input mux.

Problem 3: [20 pts] Appearing below is the `ssum` module from the previous problem and the start of a recursive version of the module, `ssum_rec`. Finish `ssum_rec` so that it performs the same computation, but does so using a tree connection of hardware rather than the linear connection that `ssum` describes. (For **partial credit only** use a generate loop to instantiate `ssum` modules of a fixed size; for full credit use recursion.)

```

module ssum #( int n = 3, int f = 4, int swid = f + $clog2(n) )
  ( output logic [swid-1:0] sum,
    input uwire [n-1:0] mask,      input uwire [f-1:0] a[n] );
  always @* begin
    sum = 0;
    for ( int i=0; i<n; i++ ) if ( mask[i] ) sum += a[i];
  end
endmodule

```

Complete module so that it describes a tree structure specified using recursion.

```

module ssum_rec
  #( int n = 3, int f = 4, int swid = f + $clog2(n) )
  ( output logic [swid-1:0] sum,
    input uwire [n-1:0] mask,
    input logic [f-1:0] a [n-1:0] );

```

```

endmodule

```

Problem 4: [20 pts] Show the hardware that will be synthesized for the module below.

```
module yam( output logic [7:0] x, y, z,
           input uwire [7:0] a, b, c,   input uwire [1:0] op,   input uwire run, clk );
  logic [7:0] x1, x2, e;

  always_ff @( posedge clk ) begin
    e = b;
    z = a + b;
    if ( op == 0 )      e = z;
    else if ( op == 1 ) e = a + x;
    else if ( op == 2 ) e = a + x1;
    x2 = x1;
    x1 = x;
    if ( run ) x = e;
  end

  always_comb y = x1 + x2 - c;

endmodule
```

Show hardware, including  registers and  module ports.

Problem 5: [20 pts] Answer each question below.

(a) Show the values of a, b, and c when the code reaches Point 1 and Point 2.

```
module short_answers;
  int a, b, c;
  initial begin
    a = 0; b = 0; c = 0;
    a = 1;
    a <= 2;
    a <= #3 3; // ---a--- ---b--- ---c---
    b = a + 10; //
    c <= a + 20; //

    // Point 1:

    #1;

    // Point 2.
  end

  my_prog my_prog_instance(a,b,c); // Ignore for part (a).
endmodule
```

- At Point 1, values for  a,  b, and  c.
- At Point 2, values for  a,  b, and  c.

(b) The definition of the my\_prog program from the previous part appears below. Show the contents of the Verilog event queue at Point 1 in the code from the previous part, include the effect of code in short\_answers as well as my\_prog. Show events in the form “t = 1969, region=NL-East, Resume Point 3” and “t = 2015, region=X, Update variable z,” but use real region names.

```
program my_prog(input int a, b, c);
  initial forever @( a or b or c ) begin
    // Point 3;
    $display("Let's go Mets!");
  end
endprogram
```

- Contents of event queue at Point 1, show  region names and  time stamps.

(c) The module below is in explicit structural form, in which only primitive gates (and module instantiations) are used. Will the synthesis program synthesize exactly that arrangement of gates? Explain.

```
module bfa_structural( output uwire sum, cout, input uwire a, b, cin );
  uwire term001, term010, term100, term111;
  uwire ab, bc, ac;
  uwire na, nb, nc;
  not n1( na, a);
  not n2( nb, b);
  not n3( nc, cin);
  and a1( term001, na, nb, cin);
  and a2( term010, na, b, nc);
  and a3( term100, a, nb, nc);
  and a4( term111, a, b, cin);
  or o1( sum, term001, term010, term100, term111);
  and a10( ab, a, b);
  and a11( bc, b, cin);
  and a12( ac, a, cin);
  or o2( cout, ab, bc, ac);
endmodule
```

Will synthesis program emit exactly these gates?  Explain.

(d) Based on a hand analysis of my\_mut we expect it to have a clock period of 12ns. Shown below is an excerpt from the testbench for my\_mut that includes the code for generating a clock. Assume that the Verilog time unit is set to 1ns. How does the clock declaration below affect the timing of the synthesized hardware?

```
module testbench();
  logic clock;
  initial clock = 0;
  always #5 clock = !clock;
  // Other declarations omitted.
  my_mut woof(x,y,a,b,clock);
endmodule
```

The effect of the declaration of clock on timing of synthesized hardware is ...  because ...