

Name \_\_\_\_\_

Digital Design using HDLs  
EE 4755  
Midterm Examination  
Friday, 21 October 2016 12:30–13:20 CDT

Problem 1 \_\_\_\_\_ (20 pts)

Problem 2 \_\_\_\_\_ (20 pts)

Problem 3 \_\_\_\_\_ (20 pts)

Problem 4 \_\_\_\_\_ (10 pts)

Problem 5 \_\_\_\_\_ (10 pts)


Problem 6 \_\_\_\_\_ (20 pts)

Alias \_\_\_\_\_

Exam Total \_\_\_\_\_ (100 pts)

*Good Luck!*

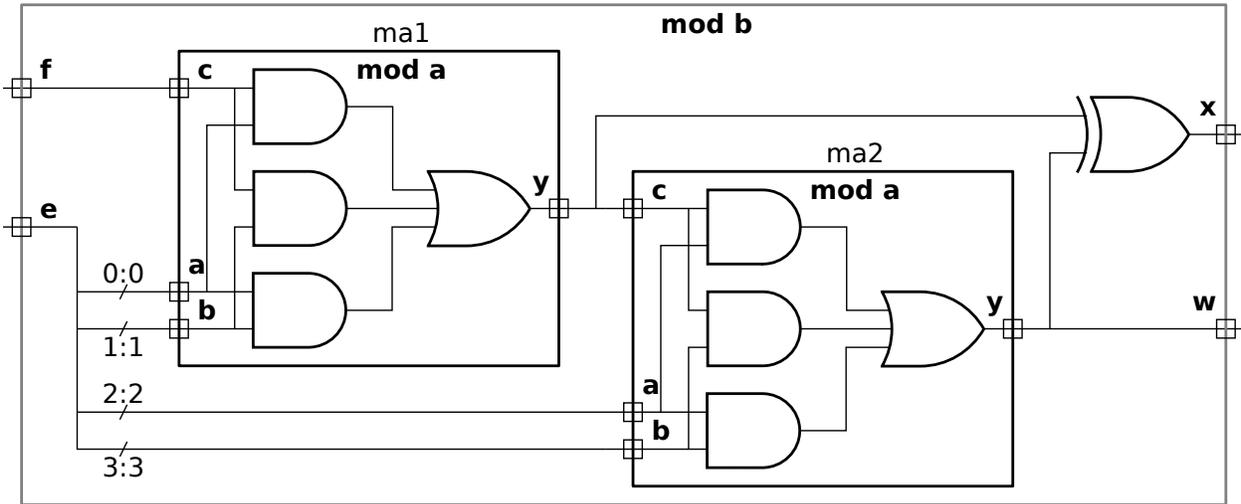Problem 1: [20 pts] Write a Verilog description of the hardware illustrated below. The description must include the modules and instantiations as illustrated. The description can be behavioral or structural, but it must be synthesizable.



Verilog corresponding to illustrated hardware.

Show instantiations,  Verilog for instantiated module(s),  and all module ports.

Problem 2: [20 pts] Appearing below is the `lookup_elt` module from Homework 4 and following that an incomplete module named `match_amt_elt`. Complete `match_amt_elt` so that the value at output port `md` is set to the number of bits in `clook` that match corresponding bits in `celt`. For example, if `clook=5'b00111` and `celt=5'b00111` then `md` should be 5, if `clook=5'b00101` and `celt=5'b00111` then `md` should be 4, and if `clook=5'b11000` and `celt=5'b00111` then `md` should be 0. Code must be synthesizable, but can be behavioral or structural.

- Complete the module so that `md` is set to the number of matching bits.
- Make sure that `md` is declared with sufficient width.

```
module lookup_elt #( int charsz = 32 ) // This module is for reference only.
  ( output logic match, input uwire [charsz-1:0] char_lookup, char_elt );
  always_comb match = char_lookup == char_elt;
endmodule
```

```
module match_amt_elt
  #( int charsz = 32 )
  ( output logic          md,
    input uwire [charsz-1:0] clook,
    input uwire [charsz-1:0] celt);
```

```
endmodule
```

Problem 3: [20 pts] Show the hardware that will be synthesized for the modules below.

(a) Show the hardware that will be inferred for the module below. Show `acme_ip_sqrt` as a box.

```
module vmag( output uwire [31:0] mag, input uwire signed [31:0] v [3] );

    logic [63:0] sos;
    acme_ip_sqrt #(32) s1(mag,sos);

    always_comb begin
        sos = 0;
        for ( int i=0; i<3; i++ ) sos += v[i] * v[i];
    end

endmodule
```

Show inferred hardware.  Don't forget `acme_ip_sqrt`.

Clearly show input and output ports of `vmag`.

Problem 3, continued:

(b) Show the hardware that will be inferred for the module below, before and after optimization. *Note: In the original exam the input was named vi.*

```
module min_elt( output logic [1:0] idx_min, input uwire signed [31:0] v [3] );
  always_comb begin
    idx_min = 0;
    for ( int i=1; i<3; i++ ) if ( v[i] < v[idx_min] ) idx_min = i;
  end
endmodule
```

Show inferred hardware.  Clearly show input and output ports.

Show hardware after some optimization.

Problem 4: [10 pts] Appearing in this problem are several variations on a counter.

(a) Show the hardware inferred for each counter below.

```
module ctr_a( output uwire [9:0] count, input clk );

    logic [9:0] last_count;
    assign count = last_count + 1;
    always_ff @( posedge clk ) last_count <= count;

endmodule

module ctr_b( output logic [9:0] count, input clk );

    uwire [9:0] next_count = count + 1;
    always_ff @( posedge clk ) count <= next_count;

endmodule
```

Inferred hardware for  ctr\_a and  ctr\_b.

(b) There is a big difference in the timing of the outputs of ctr\_a and ctr\_b. Explain the difference and illustrate with a timing diagram.


Difference between two modules.  Timing Diagram.

Problem 5: [10 pts] Appearing below is the solution to the 2015 midterm exam Problem 2. Estimate the cost of this module as illustrated but use variable  $s$  for the number of bits in `sum` (shown as `sswid`) and in each `a` element (shown as parameter `f`). Assume that the cost of a BFA is 10 units and that the cost of a  $n$ -input AND and OR gate is  $n - 1$  units. Take into account the 0 input to one of the multiplexers.

```

module ssum #( int n = 3,          int f = 4,          int swid = f + $clog2(n) )
  ( output logic [swid-1:0] sum,
    input uwire [n-1:0] mask,      input uwire [f-1:0] a[n] );
always @* begin
  sum = 0;
  for ( int i=0; i<n; i++ ) if ( mask[i] ) sum += a[i];
end
endmodule

```

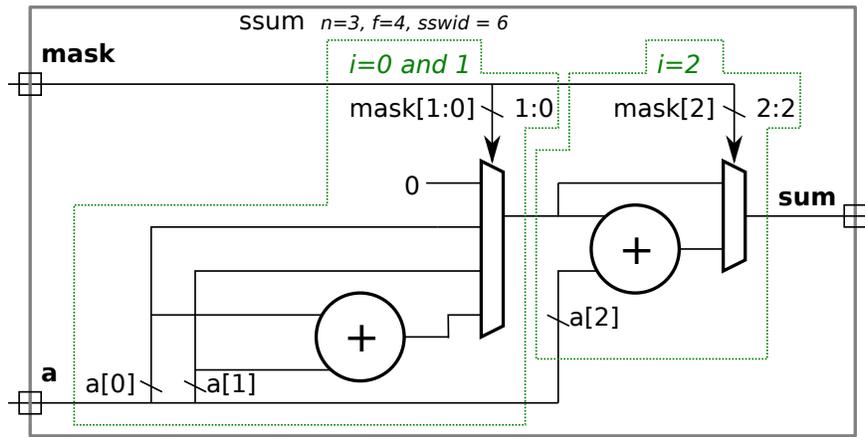

- Cost of illustrated hardware.
- Account for 0 mux input.

Problem 6: [20 pts] Answer each question below.

(a) Show the values of the variables as indicated below:

```
module tryout();
  logic [15:0] a;
  logic [0:15] b;
  logic [3:0][3:0] e;
  logic [3:0] x1, x2;

  initial begin

    a = 16'h1234;
    x1 = a[3:0]; //  Value of x1 is:

    b = 16'h1234;
    x2 = b[0:3]; //  Value of x2 is:

    e = 16'h1234;
    e[0] = e[0] + 'hf; //  Value of e is:

    e = 16'h1234;
    e[0][0] = e[0][0] + 'hf; //  Value of e is:

  end
endmodule
```

(b) Describe something that can be done during elaboration that cannot be done during simulation, and something that can be done during simulation, that cannot be done during elaboration.

Something that can be done during elaboration but **not during simulation** is:

Something that can be done during simulation but **not during elaboration** is:

(c) Appearing below are two alternatives for an integer division module, *Plan A* and *Plan B*. Both are impractical, but Plan A is not even synthesizable.

```
module div_plan_a #( int w = 16 ) ( output logic [w-1:0] quo, input uwire [w-1:0] a, b );
    always_comb begin
        for ( quo = 0; a > quo * b; quo++ );
    end
endmodule
```

```
module div_plan_b #( int w = 16 ) ( output logic [w-1:0] quo, input uwire [w-1:0] a, b );
    localparam int LIMIT = 1 << w;
    always_comb begin
        quo = 0;
        for ( int i=0; i<LIMIT; i++ ) if ( a < i * b ) quo++;
    end
endmodule
```

Why isn't Plan A synthesizable? Be specific as possible.

What might be a practical objection to the Plan B approach?

(d) The `magfp` module below is not synthesizable due to the use of the `real` data type. How would the module need to be changed so that it would be synthesizable and would operate on floating-point values.

```
module magfp( output real mag, input real vi [3] );
    real sos;
    sqrt #(32) s1(mag,sos);
    always_comb begin
        sos = 0;
        for ( int i=0; i<3; i++ ) sos += vi[i] * vi[i];
    end
endmodule
```

Show changes to port declaration for synthesizability.

Explain with a few examples how the rest of the code would need to be changed.