

Name Solution_____


Digital Design using HDLs
EE 4755
Midterm Examination
Friday, 21 October 2016 12:30–13:20 CDT

Problem 1 _____ (20 pts)
Problem 2 _____ (20 pts)
Problem 3 _____ (20 pts)
Problem 4 _____ (10 pts)
Problem 5 _____ (10 pts)
Problem 6 _____ (20 pts)
Exam Total _____ (100 pts)

Alias Loose bits sink chips.

Good Luck!

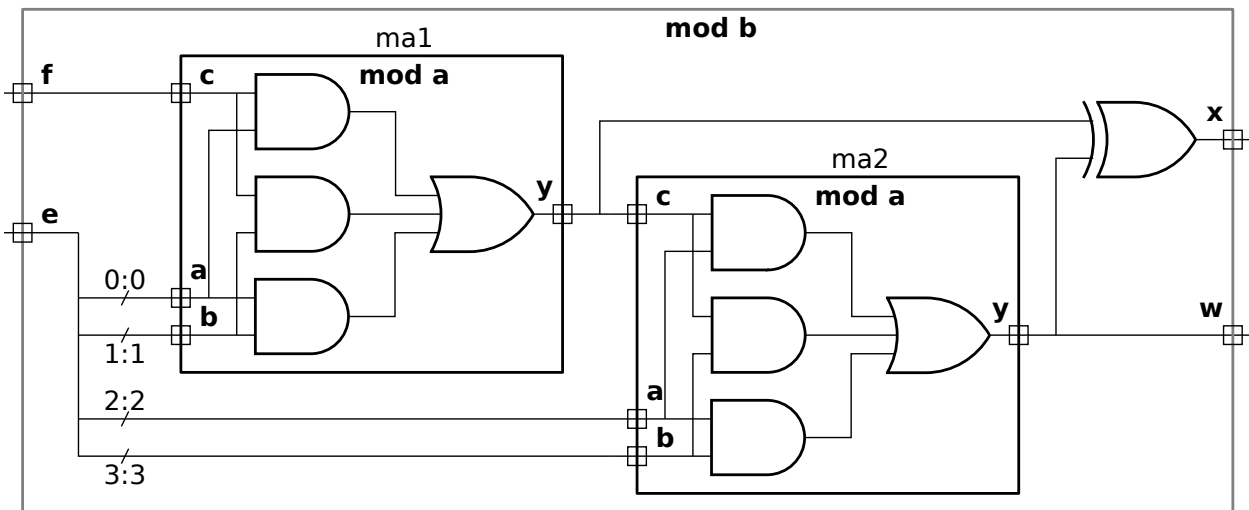Problem 1: [20 pts] Write a Verilog description of the hardware illustrated below. The description must include the modules and instantiations as illustrated. The description can be behavioral or structural, but it must be synthesizable.



- Verilog corresponding to illustrated hardware.
- Show instantiations, Verilog for instantiated module(s), and all module ports.

Solution appears below.

Grading Note: Many students chose to provide an explicit structural description, which is the most tedious descriptive style. In an explicit structural description `moda` uses four primitive instantiations plus a declaration for three wires. As can be seen from the solution the implicit structural description is just one line.

In many solutions for `modb` the output of `ma2` was connected to an intermediate wire, and an `assign` statement was used to connect the wire to the module output. As can be seen from the solution, the `ma2` output can connect directly to the `modb` output.

```
// SOLUTION
module moda(output uwire y, input uwire c, a, b);
    assign y = a && c || a && b || b && c;
endmodule

module modb(output uwire x, w, input uwire [3:0] e, input uwire f);

    uwire y1;

    moda ma1(y1,f,e[0],e[1]);
    moda ma2(w,y1,e[2],e[3]);

    assign x = y1 ^ w;

endmodule
```

Problem 2: [20 pts] Appearing below is the `lookup_elt` module from Homework 4 and following that an incomplete module named `match_amt_elt`. Complete `match_amt_elt` so that the value at output port `md` is set to the number of bits in `clook` that match corresponding bits in `celt`. For example, if `clook=5'b00111` and `celt=5'b00111` then `md` should be 5, if `clook=5'b00101` and `celt=5'b00111` then `md` should be 4, and if `clook=5'b11000` and `celt=5'b00111` then `md` should be 0. Code must be synthesizable, but can be behavioral or structural.

- Complete the module so that `md` is set to the number of matching bits.
- Make sure that `md` is declared with sufficient width.

```
module lookup_elt #( int charsz = 32 ) // This module is for reference only.
  ( output logic match, input uwire [charsz-1:0] char_lookup, char_elt );
  always_comb match = char_lookup == char_elt;
endmodule
```

The solution appears below.

For the size of `md`, notice that `md` must represent `charsz+1` distinct values, 0 to `charsz`. Therefore `clog2(charsz+1)` bits are needed. *Grading note: Full credit was given for almost any declaration that contained `clog2(charsz)`, not just those which were perfectly correct. Points were deducted for constant answers such as `[5:0]` since they only work for the default value of `charsz`.*

To count the number of matching bits a loop is used to iterate over the bits and a simple comparison is used to find matches.

Grading Notes: There was no reason to use `lookup_elt`, it was put in the problem only to help people get started. A correct solution could use `lookup_elt`, however it had to be instantiated with a `charsz=1`.

In too many solutions there was confusion between procedural code (code starting with some kind of `always`) and structural code (module declarations and `assign` statements).

```
module match_amt_elt
  #( int charsz = 32 )
  ( output logic      [$clog2(charsz+1)-1:0] md, // SOLUTION (The [$clog..])
    input uwire [charsz-1:0] clook,
    input uwire [charsz-1:0] celt);

  // SOLUTION
  always_comb begin
    md = 0;
    for ( int i=0; i<charsz; i++ ) if ( clook[i] == celt[i] ) md++;
  end
endmodule
```

Problem 3: [20 pts] Show the hardware that will be synthesized for the modules below.

(a) Show the hardware that will be inferred for the module below. Show `acme_ip_sqrt` as a box.

```
module vmag( output uwire [31:0] mag, input uwire signed [31:0] v [3] );


    logic [63:0] sos;
    acme_ip_sqrt #(32) s1(mag,sos);

    always_comb begin
        sos = 0;
        for ( int i=0; i<3; i++ ) sos += v[i] * v[i];
    end
endmodule
```

Show inferred hardware. Don't forget `acme_ip_sqrt`.

Clearly show input and output ports of `vmag`.

Solution appears below.

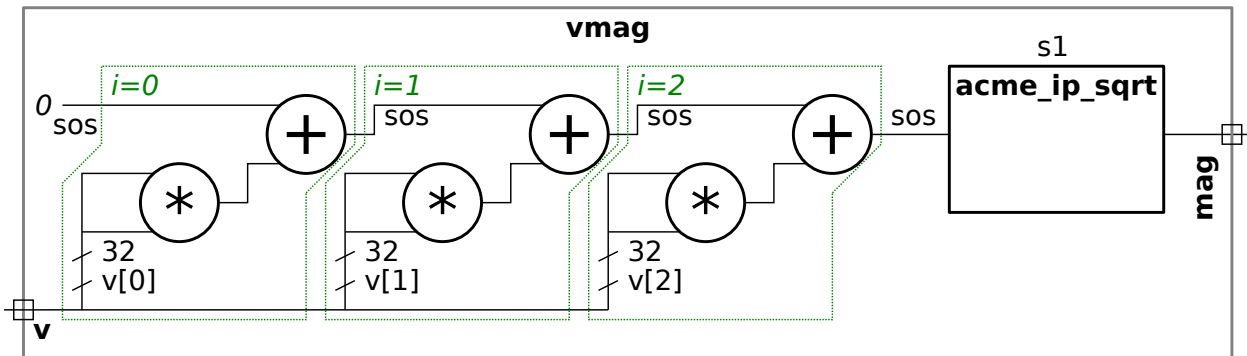

Problem 3, continued:

(b) Show the hardware that will be inferred for the module below, before and after optimization. *Note: In the original exam the input was named vi.*



```

module min_elt( output logic [1:0] idx_min, input uwire signed [31:0] v [3] );
  always_comb begin
    idx_min = 0;
    for ( int i=1; i<3; i++ ) if ( v[i] < v[idx_min] ) idx_min = i;
  end
endmodule

```

- Show inferred hardware. Clearly show input and output ports.

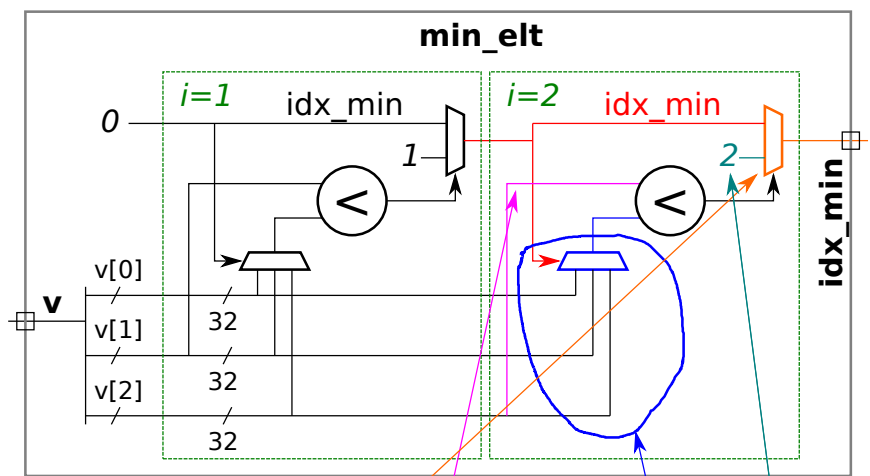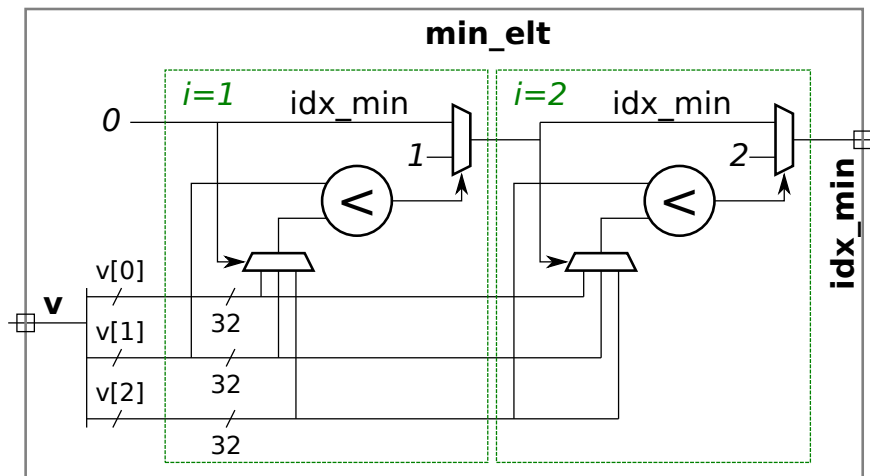Solution appears below in a plain form, followed by a version in which the hardware corresponding to the different parts of the if statement is highlighted. *Grading Note: A common difficulty was coming up with the hardware for v[idx_min].*




```

if ( v[i] < v[idx_min] ) idx_min = i;

```

✓ Show hardware after some optimization.

Solution appears below. The 3-input mux at $i=1$ has been eliminated because it always selected element 0. The 3-input mux at $i=2$ was replaced by a 2-input mux because the select input would never be 2. The 2-input mux at $i=1$ was eliminated since the select signal has the same value as the output. The 2-input mux at $i=2$ was replaced by `uwire` and a single AND gate (with a bubbled input).

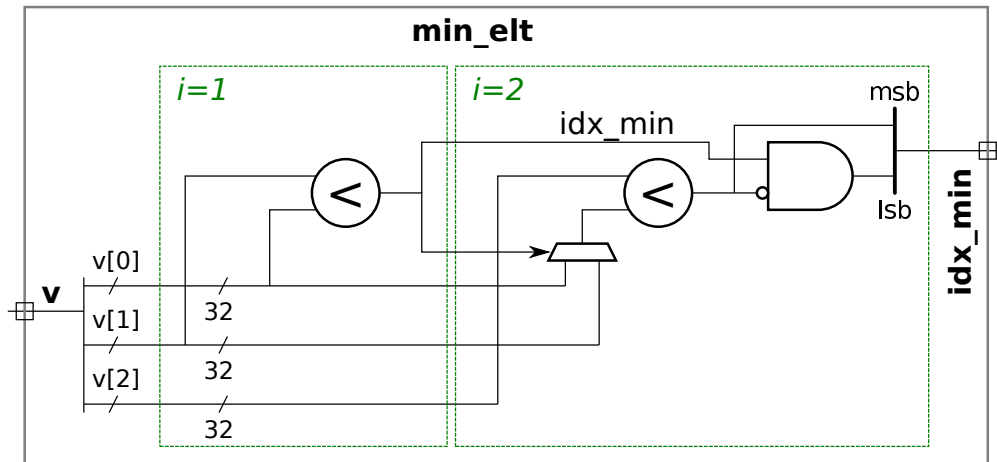

Problem 4: [10 pts] Appearing in this problem are several variations on a counter.

(a) Show the hardware inferred for each counter below.

```

module ctr_a( output uwire [9:0] count, input clk );

    logic [9:0] last_count;
    assign count = last_count + 1;
    always_ff @( posedge clk ) last_count <= count;

endmodule

```

```


module ctr_b( output logic [9:0] count, input clk );

    uwire [9:0] next_count = count + 1;
    always_ff @( posedge clk ) count <= next_count;

endmodule

```


Inferred hardware for ctr_a and ctr_b.

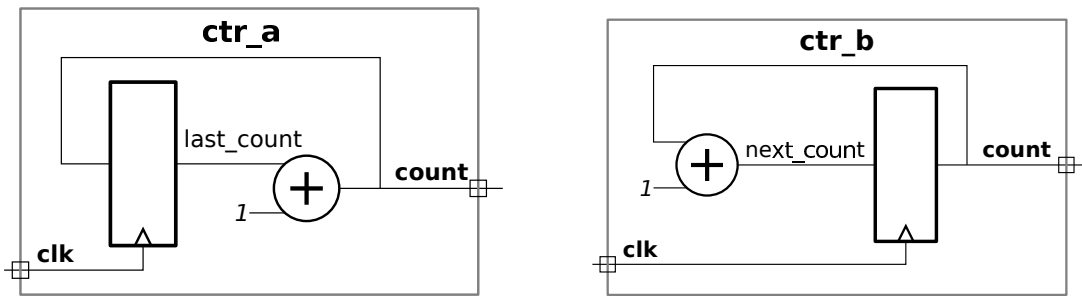

 (b) There is a big difference in the timing of the outputs of **ctr_a** and **ctr_b**. Explain the difference and illustrate with a timing diagram.

Difference between two modules. Timing Diagram.

In **ctr_a** the module output, **count**, is connected to the output of an adder. That means the value at the output will not be stable until later in the clock cycle. See the left-side timing diagram below. External hardware could not do anything with the value other than clocking it into a register for use in the next clock cycle. In contrast, the **ctr_b** module output, **count**, is connected to a register output, and so it is available for use at the beginning of the clock cycle.




Problem 5: [10 pts] Appearing below is the solution to the 2015 midterm exam Problem 2. Estimate the cost of this module as illustrated but use variable s for the number of bits in `sum` (shown as `sswid`) and in each `a` element (shown as parameter `f`). Assume that the cost of a BFA is 10 units and that the cost of a n -input AND and OR gate is $n - 1$ units. Take into account the 0 input to one of the multiplexers.

```

module ssum #( int n = 3,          int f = 4,          int swid = f + $clog2(n) )
  ( output logic [swid-1:0] sum,
    input uwire [n-1:0] mask,      input uwire [f-1:0] a[n] );
always @* begin
  sum = 0;
  for ( int i=0; i<n; i++ ) if ( mask[i] ) sum += a[i];
end
endmodule

```

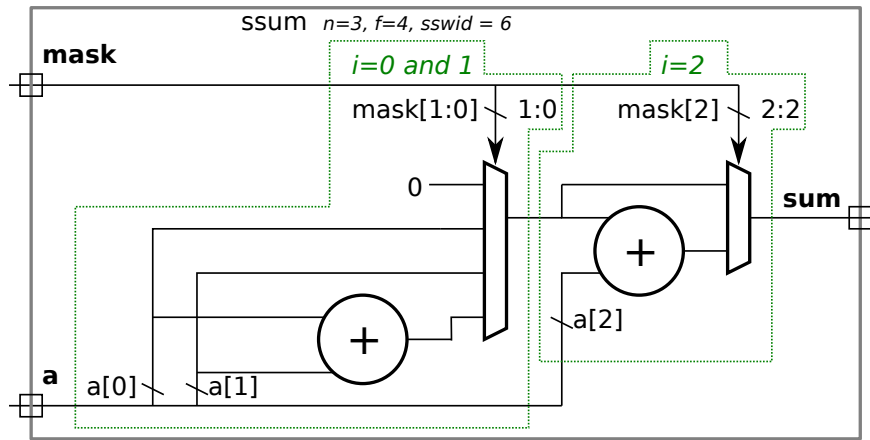

- Cost of illustrated hardware. Account for 0 mux input.

There are two adders, each uses s bits. Since the cost of a BFA is 10 units, the cost of the two adders is $2 \times 10s = 20s$ units.

A two-input mux uses three 2-input gates per bit, so the total cost of the second mux is $3s$ units. In general, an n -input, width w mux uses nw 2-input AND gates for selection, $n \lceil \lg n \rceil$ -input AND gates for decoding, and w n -input OR gates. Without optimization, the 4-input mux would cost $4s + 4 + 3s = 7s + 4$ units. The total cost without optimization is $20s + 7s + 4 + 3s = 30s + 4$ units.

Because one of the inputs to the 4-input mux is zero all of the logic connecting to that input can be eliminated, and the OR gates can be reduced from 4 to 3 inputs. So the optimized cost of the 4-input mux is $3s + 3 + 2s = 5s + 3$ units. The total cost with optimization is $20s + 5s + 3 + 3s = 28s + 3$ units.

Grading Note: Way too many students did not multiply the cost of a BFA by the number of bits in the quantities being added.

Problem 6: [20 pts] Answer each question below.

(a) Show the values of the variables as indicated below:

Solution appears below. Notice that the difference between x_1 and x_2 is with the bit numbering. In the $e[0] + 'hf$ assignment the $'hf$ (15 represented as a hexadecimal digit) is being added to the least-significant 4-bits of e . The result of that addition is $4_{16} + f_{16} = 13_{16}$, and it is placed in the 4 least significant bits of e without modifying the other bits of e . The assignment to $e[0][0]$ is similar, except that it operates only on the least-significant bit of e .

```
module tryout();
  logic [15:0] a;
  logic [0:15] b;
  logic [3:0] [3:0] e;
  logic [3:0] x1, x2;

  initial begin

    a = 16'h1234;
    x1 = a[3:0]; //  Value of x1 is: 4

    b = 16'h1234;
    x2 = b[0:3]; //  Value of x2 is: 1

    e = 16'h1234;
    e[0] = e[0] + 'hf; //  Value of e is: 16'h1233

    e = 16'h1234;
    e[0][0] = e[0][0] + 'hf; //  Value of e is: 16'h1235

  end
endmodule
```

(b) Describe something that can be done during elaboration that cannot be done during simulation, and something that can be done during simulation, that cannot be done during elaboration.

Something that can be done during elaboration but **not during simulation** is:

During elaboration one can use a generate loop to instantiate modules.

Something that can be done during simulation but **not during elaboration** is:

During simulation one can compute values that depend on module inputs.

(c) Appearing below are two alternatives for an integer division module, *Plan A* and *Plan B*. Both are impractical, but Plan A is not even synthesizable.

```
module div_plan_a #( int w = 16 ) ( output logic [w-1:0] quo, input uwire [w-1:0] a, b );
    always_comb begin
        for ( quo = 0; a > quo * b; quo++ );
    end
endmodule
```

```
module div_plan_b #( int w = 16 ) ( output logic [w-1:0] quo, input uwire [w-1:0] a, b );
    localparam int LIMIT = 1 << w;
    always_comb begin
        quo = 0;
        for ( int i=0; i<LIMIT; i++ ) if ( a < i * b ) quo++;
    end
endmodule
```

✓ Why isn't Plan A synthesizable? Be specific as possible.

It is not synthesizable because the number of iterations in the loop can not be determined at elaboration time.

✓ What might be a practical objection to the Plan B approach?

Because 2^w multipliers and multiplexors are used the cost is ridiculously high for even moderate values of w . For example, for the default value of 16, there would be 65536 multipliers and muxen. Even if the synthesis program simplified this to 65536 adders, the cost would still be enormous.

(d) The `magfp` module below is not synthesizable due to the use of the `real` data type. How would the module need to be changed so that it would be synthesizable and would operate on floating-point values.

```
module magfp( output real mag, input real vi [3] );
    real sos;
    sqrt #(32) s1(mag,sos);
    always_comb begin
        sos = 0;
        for ( int i=0; i<3; i++ ) sos += vi[i] * vi[i];
    end
endmodule
```

✓ Show changes to port declaration for synthesizability.

Change `real` to `[63:0]`.

✓ Explain with a few examples how the rest of the code would need to be changed.

The arithmetic operations would have to be replaced by bit-level operations to perform the floating-point arithmetic. This might be done by instantiating FP multipliers and adders from an IP library (such as ChipWare) or by writing the Verilog to implement FP arithmetic yourself.