

**Problem 1:** The Verilog code below is the `sort3` module from Homework 1. Draw a diagram of the hardware as described by `sort3`, showing the `sort2` modules as boxes. Be sure to label the input and output ports with the same symbols used in the module.

```

module sort3
  #( int w = 8 )
  ( output uwire [w-1:0] x0, x1, x2,
    input uwire [w-1:0] a0, a1, a2 );


  uwire [w-1:0] i10, i11, i21;

  sort2 #(w) s0_01( i10, i11, a0, a1 );
  sort2 #(w) s1_12( i21, x2, i11, a2 );
  sort2 #(w) s2_01( x0, x1, i10, i21 );

endmodule

```

Solution appears below.

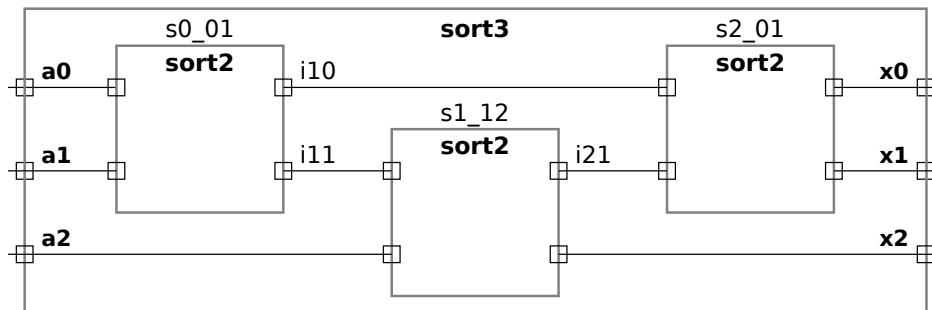

**Problem 2:** It is possible to build an  $n$ -element sorting network using  $\frac{n}{2} \lg^2 n$  two-element sorting networks in such a way that the  $n$ -element sorting network has a critical path of  $\lg^2 n$ . (Note:  $\lg n \equiv \log_2 n$ .) But this assignment is concerned with  $n$ -element sorting networks using  $n(n-1)/2$  two-element sorting networks, which we will call  *$n$ -element bad sorting networks* or *bad sorters* for short.

An  $n$ -element bad sorter has inputs  $a_0, a_1, \dots, a_{n-1}$  and outputs  $x_0, x_1, \dots, x_{n-1}$ . The largest value is routed to  $x_{n-1}$ .

A 2-element bad sorter is a single `sort2` module. An  $n$ -element bad sorter,  $n > 2$ , can be constructed using an  $(n-1)$ -element bad sorter and  $n-1$  `sort2` modules as follows. The  $n-1$  `sort2` modules are connected to the  $n$  inputs and to each other in such a way that the largest value is routed to a specific output of one of the `sort2` modules. That specific `sort2` output is connected to output  $x_{n-1}$  of the  $n$ -element sorter. The other values connect to the  $(n-1)$ -element bad sorter, and the  $(n-1)$ -element bad sorter outputs connect to outputs  $x_0, x_1, \dots, x_{n-2}$  of the  $n$ -element bad sorter that we are constructing. Note that this generalizes the solution to Homework 1 Problem 2.


The description above is recursive. At level  $i$  (the same as  $n$  above) another  $i-1$  `sort2` modules are used. For a 4-element sorter we need  $(4-1) + (3-1) + 1 = 6$  `sort2` modules. The

cost of an  $n$ -element bad sorter is found by solving the summation  $\sum_{i=2}^n i - 1$ , which is  $n(n - 1)/2$ . That's  $O(n^2)$ , which is how the bad sorter got its name.

It gets worse. The critical path through the bad sorter can range from bad to awful. That depends on two things: How the `sort2` modules are used to find the largest value, and how the `sort2` modules connect to the  $(n - 1)$ -element bad sorter.

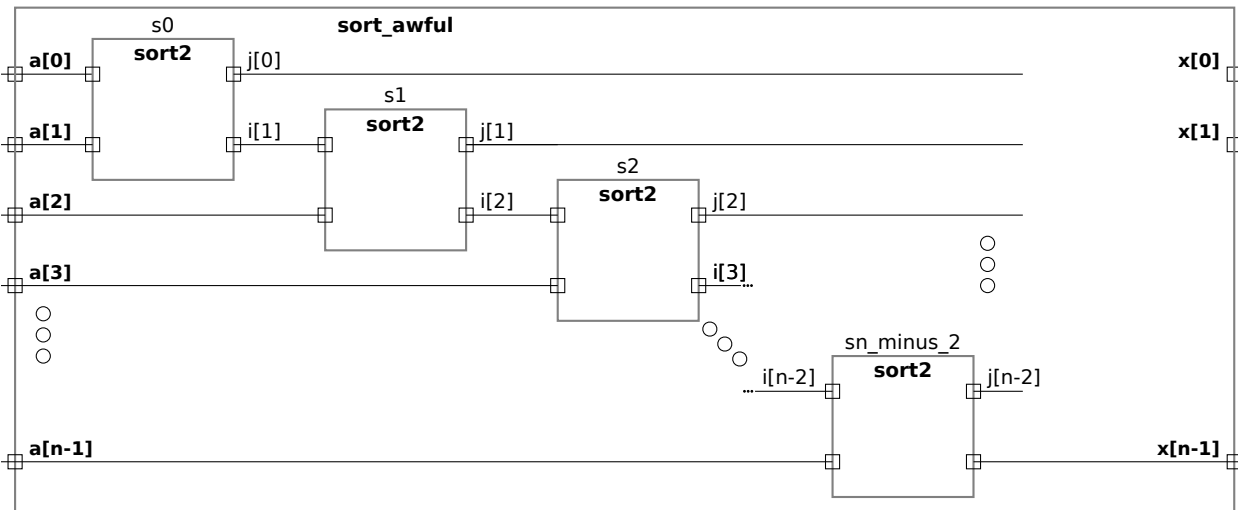
(a) Show the worst way that `sort2` modules can be connected to find the largest value. *Hint: the critical path should be  $n - 1$  `sort2` modules.* Provide a sketch for the general case, and an example for  $n = 4$ .

Call the `sort2` modules  $s_0$  to  $s_{n-2}$ . Connecting output `x1` of  $s_i$  to input `a0` of  $s_{i+1}$  for  $0 \leq i < n - 1$  is the worst way to connect  $n - 1$  modules. See the illustration below. The critical path starts at `a0` or `a1` and ends at either output of sorter  $s_{n-2}$ .



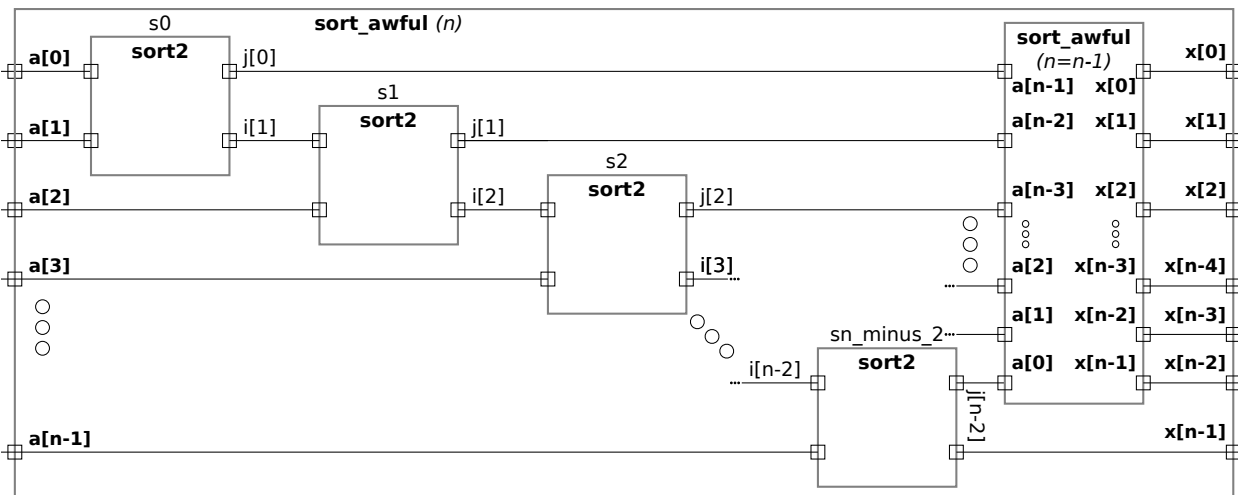(b) Show the worst way that the `sort2` modules, as connected above, can connect to the  $(n - 1)$ -element sorter. Provide a sketch.

Notice that the critical path through the `sort2` modules starts at `a[0]` and ends at `j[n-2]`. So when connecting `j[n-2]` to the smaller sort module the worst ports that it can be connected to are `a[0]` and `a[1]`. That's shown below. Note that  $n$  inside the smaller `sort_awful` is equal to  $n-1$  in the larger one.




(c) Determine the critical path for an  $n$ -element bad sorter constructed in the way described in the last two parts. *Hint: The math part should be familiar.*

In an  $n$ -input awful bad sorter the path from  $a_0$  to  $j[n-2]$  is of length  $n - 1$ . Signal  $j[n-2]$  connects to  $a_0$  of an  $n - 1$  element bad sorter where it goes through  $n - 2$  `sort2` modules. The total length of the path is  $\sum_{i=n}^2 i - 1 = n(n - 2)/2$  `sort2` modules.

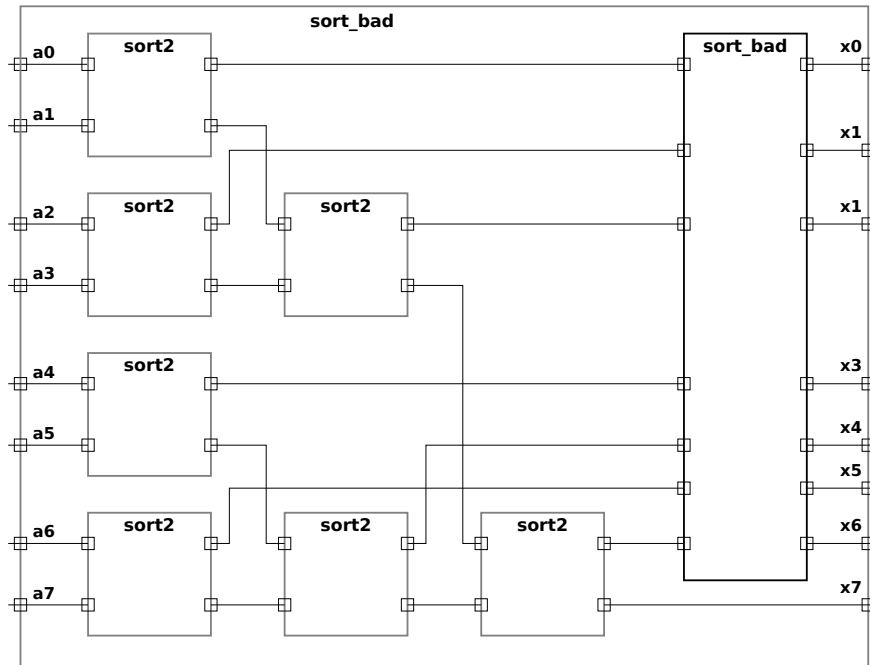(d) Show a much better way of connecting the `sort2` modules to find the largest value. It should be easy to show that the critical path is the lowest that is possible. Provide a sketch for  $n = 8$ .

Connect the `sort2` modules in a tree, the solution appears below for  $n = 8$ , and showing the recursive connection.



The problem with the approach to building the bad sorters described in this assignment is that each level in the recursion reduces the size by 1 (that is, from  $n$  to  $n - 1$ ), and so the critical path must be at least  $O(n)$ . As some students may have realized, a better approach would be to use recursion in which the  $n$  inputs were split between two  $\frac{n}{2}$ -element networks and then somehow combined. But how? The key insight, described by K. E. Batcher in a landmark 1968 paper, is not to try to recursively describe a sorting network, but to instead recursively describe a network that merges two already sorted sequences. The input to a 2-element merge network would be two 1-element sorted sequences. (Of course, every 1-element sequence is sorted.) Pairs of 2-element merge networks feed a 4-element merge network, and so on. This will be further described later in the semester.