This document contains assignments given in LSU EE 4755 over many semesters. It was automatically generated and so some solutions (and possibly some assignments) are likely missing. At the top of each page of each assignment is a link to the original assignment. Those who want to print an assignment might follow that link. All assignments and public solutions are available at https://www.ece.lsu.edu/ee4755/prev.html.

Contents

1	Fall	2024 6
	1.1	hw01.pdf
	1.2	hw02.pdf
	1.3	hw03.pdf
	1.4	hw04.pdf
	1.5	hw05.pdf
	1.6	hw06.pdf
0	T- 11	0000 07
4	Fall 0.1	2025 37
	2.1	$1 \times 10^{-1} \text{ m} m$
	2.2	nw02.pdf
	2.3	nw03.pdf
	2.4	nw04.pdf
	2.5	hw05.pdf
	2.6	hw06.pdf
3	Fall	2022 64
	3.1	hw01.pdf
	3.2	hw02.pdf
	3.3	hw03.pdf
	3.4	hw04.pdf
	3.5	hw05.pdf82
1	Fall	2021 88
-	1 1	2021 00 hw01 ndf 80
	4.1	$hw01.pdf \qquad \qquad 01$
	4.2	hw02.pdf
	4.0	hw03.pdf
	4.4	1004.pdf
	4.0	100 hm06 ndf
	4.0	Iwoo.pdi
5	Fall	2020 104
	5.1	hw01.pdf
	5.2	hw02.pdf
	5.3	hw03.pdf
	5.4	hw04.pdf
	5.5	hw05.pdf

| Fall | 2019 |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 120 |
|------|---
--
--

--|---
--
--
--
--
--
--
--
--

--
--
--
--
--

--
--
--
--
--

--
--
--|---|---
--

--
--
--

--
--
--

--
--
--

--
--

--
---|--|---
--|--|---|---|--|---|
| 6.1 | hw01.pdf . |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 121 |
| 6.2 | hw02.pdf . |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 125 |
| 6.3 | hw03.pdf . |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 127 |
| 6.4 | hw04.pdf. |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 131 |
| 6.5 | hw05.pdf. |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 134 |
| 6.6 | hw06.pdf . | •

 |
 | • | •

 |

 |

 |

 |

 |

 |

 | •

 | | | •
 | •

 |

 | •
 | •
 |

 |
 | •
 |
 |
 |
 | | • | | | • | | | 135 |
| Fall | 2018 |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 139 |
| 7.1 | hw01.pdf . |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 140 |
| 7.2 | hw02.pdf . |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 142 |
| 7.3 | hw03.pdf . |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 144 |
| 7.4 | hw04.pdf . |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 146 |
| 7.5 | hw05.pdf . |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 147 |
| 7.6 | hw06.pdf . |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 150 |
| 7.7 | hw07.pdf . |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 151 |
| 7.8 | hw08.pdf. | •

 | •
 | • | •

 | •

 | •

 | •

 | •

 | •

 | •

 | •

 | | • | •
 | •

 |

 | •
 | •
 | •

 | •
 | •
 | •
 | •
 |
 | | • | • | • | • | | • | 153 |
| Fall | 2017 |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 156 |
| 8.1 | hw01.pdf. |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 157 |
| 8.2 | hw02.pdf. |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 159 |
| 8.3 | hw03.pdf. |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 161 |
| 8.4 | hw04.pdf. |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 162 |
| 8.5 | hw05.pdf. |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 164 |
| 8.6 | hw06.pdf. |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 166 |
| 8.7 | hw07.pdf . | •

 | •
 | • | •

 |

 | •

 |

 |

 |

 |

 | •

 | | • | •
 | •

 |

 | •
 | •
 |

 | •
 | •
 | •
 |
 |
 | | • | | | • | | • | 167 |
| Fall | 2016 |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 169 |
| 9.1 | hw01.pdf. |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 170 |
| 9.2 | hw02.pdf. |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 173 |
| 9.3 | hw03.pdf. |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 175 |
| 9.4 | hw04.pdf. |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 177 |
| 9.5 | hw05.pdf. |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 179 |
| 9.6 | hw06.pdf. | •

 |
 | • | •

 |

 |

 |

 |

 |

 |

 | •

 | | | •
 | •

 |

 |
 | •
 |

 |
 |
 |
 |
 |
 | | | | | | | | 181 |
| Fall | 2015 |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 183 |
| 10.1 | hw01.pdf. |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 184 |
| 10.2 | hw02.pdf |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 188 |
| 10.3 | hw03.pdf |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 189 |
| 10.4 | hw04.pdf. |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 192 |
| 10.5 | hw05.pdf. |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 193 |
| 10.6 | hw06.pdf. |

 |
 | |

 |

 |

 |

 |

 |

 |

 |

 | | |
 |

 |

 |
 |
 |

 |
 |
 |
 |
 |
 | | | | | | | | 197 |
| | $\begin{array}{c} {\bf Fall} \\ 6.1 \\ 6.2 \\ 6.3 \\ 6.4 \\ 6.5 \\ 6.6 \\ {\bf Fall} \\ 7.1 \\ 7.2 \\ 7.3 \\ 7.4 \\ 7.5 \\ 7.6 \\ 7.7 \\ 7.8 \\ {\bf Fall} \\ 8.1 \\ 8.2 \\ 8.3 \\ 8.4 \\ 8.5 \\ 8.6 \\ 8.7 \\ {\bf Fall} \\ 9.1 \\ 9.2 \\ 9.3 \\ 9.4 \\ 9.5 \\ 9.6 \\ {\bf Fall} \\ 10.1 \\ 10.2 \\ 10.3 \\ 10.4 \\ 10.5 \\ 10.6 \\ \end{array}$ | Fall 2019 6.1 hw01.pdf. 6.2 hw02.pdf. 6.3 hw03.pdf. 6.4 hw04.pdf. 6.5 hw05.pdf. 6.6 hw06.pdf. 7.1 hw01.pdf. 7.2 hw02.pdf. 7.3 hw03.pdf. 7.4 hw04.pdf. 7.5 hw05.pdf. 7.6 hw06.pdf. 7.7 hw07.pdf. 7.8 hw08.pdf. 7.8 hw02.pdf. 8.1 hw01.pdf. 8.2 hw02.pdf. 8.3 hw03.pdf. 8.4 hw04.pdf. 8.5 hw05.pdf. 8.6 hw06.pdf. 8.7 hw01.pdf. 9.2 hw02.pdf. 9.3 hw03.pdf. 9.4 hw04.pdf. 9.5 hw03.pdf. 9.4 hw04.pdf. 9.5 hw05.pdf. 9.6 hw02.pdf. 9.7 hw03.pdf. 9.6 hw02.pdf. 9.7 <td< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw03.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw01.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf 9.6 hw02.pdf 9.6 hw</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw01.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf 9.6 hw02.pdf</td><td>Fall 2019 6.1 hw01.pdf. 6.2 hw02.pdf. 6.3 hw03.pdf. 6.4 hw04.pdf. 6.5 hw05.pdf. 6.6 hw04.pdf. 6.7 hw04.pdf. 6.6 hw06.pdf. 7.1 hw01.pdf. 7.2 hw02.pdf. 7.3 hw03.pdf. 7.4 hw04.pdf. 7.5 hw05.pdf. 7.6 hw06.pdf. 7.7 hw07.pdf. 7.8 hw02.pdf. 7.8 hw03.pdf. 8.1 hw01.pdf. 8.2 hw02.pdf. 8.3 hw03.pdf. 8.4 hw04.pdf. 8.5 hw05.pdf. 8.6 hw06.pdf. 8.7 hw07.pdf. 9.1 hw01.pdf. 9.2 hw02.pdf. 9.3 hw03.pdf. 9.4 hw04.pdf. 9.5 hw05.pdf. 9.6 hw06.pdf. 9.6 hw06.pdf. 9.6 <td< td=""><td>Fall 2019 6.1 hw01.pdf. 6.2 hw02.pdf. 6.3 hw03.pdf. 6.4 hw04.pdf. 6.5 hw05.pdf. 6.6 hw04.pdf. 6.7 hw04.pdf. 6.6 hw04.pdf. 7.1 hw01.pdf. 7.2 hw02.pdf. 7.3 hw03.pdf. 7.4 hw04.pdf. 7.5 hw05.pdf. 7.6 hw06.pdf. 7.7 hw07.pdf. 7.8 hw08.pdf. 7.8 hw02.pdf. 8.1 hw01.pdf. 8.2 hw02.pdf. 8.3 hw03.pdf. 8.4 hw04.pdf. 8.5 hw05.pdf. 8.6 hw06.pdf. 8.7 hw07.pdf. 9.1 hw01.pdf. 9.2 hw02.pdf. 9.3 hw03.pdf. 9.4 hw04.pdf. 9.5 hw05.pdf. 9.6 hw06.pdf. 9.6 hw06.pdf. 9.6 <td< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw03.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf 9.6 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.7 hw01.pdf 6.6 hw04.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw03.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.6 hw04.pdf 9.6 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.7 hw01.pdf 6.6 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw03.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf 9.6 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw02.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf 9.6 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw03.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw04.pdf 9.6 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw02.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6
 hw06.pdf 9.6 hw04.pdf 9.6 hw04.pdf 9.6 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw06.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.4 hw04.pdf 9.6 hw06.pdf 9.6 hw06.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw01.pdf 6.6 hw01.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.2 hw02.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw03.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw03.pdf 9.4 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw01.pdf 6.6 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw02.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw03.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf 9.6 hw06.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw01.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf 9.9 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw03.pdf 9.9 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.7 hw01.pdf 6.8 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.6 hw06.pdf 9.7 hw03.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t<
td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw02.pdf 9.9 hw03.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw04.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf</td><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf 9.9 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw04.pdf 7.8 hw05.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></td<></td></td<></td></td<> | Fall 2019 6.1 hw01.pdf 6.2 hw03.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw01.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf
 9.6 hw02.pdf 9.6 hw | Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw01.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf 9.6 hw02.pdf | Fall 2019 6.1 hw01.pdf. 6.2 hw02.pdf. 6.3 hw03.pdf. 6.4 hw04.pdf. 6.5 hw05.pdf. 6.6 hw04.pdf. 6.7 hw04.pdf. 6.6 hw06.pdf. 7.1 hw01.pdf. 7.2 hw02.pdf. 7.3 hw03.pdf. 7.4 hw04.pdf. 7.5 hw05.pdf. 7.6 hw06.pdf. 7.7 hw07.pdf. 7.8 hw02.pdf. 7.8 hw03.pdf. 8.1 hw01.pdf. 8.2 hw02.pdf. 8.3 hw03.pdf. 8.4 hw04.pdf. 8.5 hw05.pdf. 8.6 hw06.pdf. 8.7 hw07.pdf. 9.1 hw01.pdf. 9.2 hw02.pdf. 9.3 hw03.pdf. 9.4 hw04.pdf. 9.5 hw05.pdf. 9.6 hw06.pdf. 9.6 hw06.pdf. 9.6 <td< td=""><td>Fall 2019 6.1 hw01.pdf. 6.2 hw02.pdf. 6.3 hw03.pdf. 6.4 hw04.pdf. 6.5 hw05.pdf. 6.6 hw04.pdf. 6.7 hw04.pdf. 6.6 hw04.pdf. 7.1 hw01.pdf. 7.2 hw02.pdf. 7.3 hw03.pdf. 7.4 hw04.pdf. 7.5 hw05.pdf. 7.6 hw06.pdf. 7.7 hw07.pdf. 7.8 hw08.pdf. 7.8 hw02.pdf. 8.1 hw01.pdf. 8.2 hw02.pdf. 8.3 hw03.pdf. 8.4 hw04.pdf. 8.5 hw05.pdf. 8.6 hw06.pdf. 8.7 hw07.pdf. 9.1 hw01.pdf. 9.2 hw02.pdf. 9.3 hw03.pdf. 9.4 hw04.pdf. 9.5 hw05.pdf. 9.6 hw06.pdf. 9.6 hw06.pdf. 9.6 <td< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw03.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf 9.6 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.7 hw01.pdf 6.6 hw04.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw03.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.6 hw04.pdf 9.6 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.7 hw01.pdf 6.6 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw03.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf 9.6 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw02.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf 9.6 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw03.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw04.pdf 9.6 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw02.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw04.pdf 9.6 hw04.pdf 9.6 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw06.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.4 hw04.pdf 9.6 hw06.pdf 9.6 hw06.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw01.pdf 6.6 hw01.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.2 hw02.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4
 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw03.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw03.pdf 9.4 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw01.pdf 6.6 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw02.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw03.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf 9.6 hw06.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw01.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf 9.9 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw03.pdf 9.9 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.7 hw01.pdf 6.8 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.6 hw06.pdf 9.7 hw03.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw02.pdf 9.9 hw03.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf
 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw04.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf</td><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf 9.9 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw04.pdf 7.8 hw05.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></td<></td></td<> | Fall 2019 6.1 hw01.pdf. 6.2 hw02.pdf. 6.3 hw03.pdf. 6.4 hw04.pdf. 6.5 hw05.pdf. 6.6 hw04.pdf. 6.7 hw04.pdf. 6.6 hw04.pdf. 7.1 hw01.pdf. 7.2 hw02.pdf. 7.3 hw03.pdf. 7.4 hw04.pdf. 7.5 hw05.pdf. 7.6 hw06.pdf. 7.7 hw07.pdf. 7.8 hw08.pdf. 7.8 hw02.pdf. 8.1 hw01.pdf. 8.2 hw02.pdf. 8.3 hw03.pdf. 8.4 hw04.pdf. 8.5 hw05.pdf. 8.6 hw06.pdf. 8.7 hw07.pdf. 9.1 hw01.pdf. 9.2 hw02.pdf. 9.3 hw03.pdf. 9.4 hw04.pdf. 9.5 hw05.pdf. 9.6 hw06.pdf. 9.6 hw06.pdf. 9.6 <td< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw03.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf 9.6 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.7 hw01.pdf 6.6 hw04.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw03.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.6 hw04.pdf 9.6 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.7
hw01.pdf 6.6 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw03.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf 9.6 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw02.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf 9.6 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw03.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw04.pdf 9.6 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw02.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw04.pdf 9.6 hw04.pdf 9.6 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw06.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.4 hw04.pdf 9.6 hw06.pdf 9.6 hw06.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw01.pdf 6.6 hw01.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.2 hw02.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw03.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw03.pdf 9.4 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw01.pdf 6.6 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw02.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw03.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf 9.6 hw06.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw01.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf 9.9 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5
hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw03.pdf 9.9 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.7 hw01.pdf 6.8 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.6 hw06.pdf 9.7 hw03.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw02.pdf 9.9 hw03.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw04.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf
8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf</td><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf 9.9 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw04.pdf 7.8 hw05.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></td<> | Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw03.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf 9.6 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.7 hw01.pdf 6.6 hw04.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw03.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.6 hw04.pdf 9.6 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.7 hw01.pdf 6.6 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw03.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf 9.6 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw02.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf 9.6 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw03.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw04.pdf 9.6 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw02.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw04.pdf 9.6 hw04.pdf 9.6 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw06.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.4 hw04.pdf 9.6 hw06.pdf 9.6 hw06.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw01.pdf 6.6 hw01.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.2 hw02.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7
 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw03.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw03.pdf 9.4 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw01.pdf 6.6 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw02.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw03.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf 9.6 hw06.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw01.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf 9.9 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw03.pdf 9.9 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.7 hw01.pdf 6.8 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.6 hw06.pdf 9.7 hw03.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw02.pdf 9.9 hw03.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf
 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw04.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf</td><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf 9.9 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw04.pdf 7.8 hw05.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<> | Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.7 hw01.pdf 6.6 hw04.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw03.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.6 hw04.pdf 9.6 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.7 hw01.pdf 6.6 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw03.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf 9.6 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw02.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf 9.6 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw03.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3
 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw04.pdf 9.6 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw02.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw04.pdf 9.6 hw04.pdf 9.6 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw06.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.4 hw04.pdf 9.6 hw06.pdf 9.6 hw06.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw01.pdf 6.6 hw01.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.2 hw02.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw03.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw03.pdf 9.4 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw01.pdf 6.6 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw02.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw03.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf 9.6 hw06.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw01.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf 9.9 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw03.pdf 9.9 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.7 hw01.pdf 6.8 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.6 hw06.pdf 9.7 hw03.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4
 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw02.pdf 9.9 hw03.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw04.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf</td><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf 9.9 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw04.pdf 7.8 hw05.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf
9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<> | Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.7 hw01.pdf 6.6 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw03.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf 9.6 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw02.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf 9.6 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw03.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw04.pdf 9.6 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw02.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw04.pdf 9.6 hw04.pdf 9.6 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw06.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.4 hw04.pdf 9.6 hw06.pdf 9.6 hw06.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw01.pdf 6.6 hw01.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.2 hw02.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw03.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw03.pdf 9.4 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw01.pdf 6.6 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw02.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw03.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf 9.6 hw06.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw01.pdf 8.7 hw02.pdf 9.1 hw01.pdf
 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf 9.9 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw03.pdf 9.9 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.7 hw01.pdf 6.8 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.6 hw06.pdf 9.7 hw03.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw02.pdf 9.9 hw03.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw04.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5
hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf</td><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf 9.9 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw04.pdf 7.8 hw05.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<> | Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw02.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf 9.6 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw03.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw04.pdf 9.6 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw02.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw04.pdf 9.6 hw04.pdf 9.6 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw06.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.4 hw04.pdf 9.6 hw06.pdf 9.6 hw06.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw01.pdf 6.6 hw01.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.2 hw02.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw03.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw03.pdf 9.4 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw01.pdf 6.6 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw02.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf
 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw03.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf 9.6 hw06.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw01.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf 9.9 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw03.pdf 9.9 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.7 hw01.pdf 6.8 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.6 hw06.pdf 9.7 hw03.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw02.pdf 9.9 hw03.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw04.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf <</td><td>Fall
2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf</td><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf 9.9 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw04.pdf 7.8 hw05.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<> | Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw03.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw04.pdf 9.6 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw02.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw04.pdf 9.6 hw04.pdf 9.6 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw06.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.4 hw04.pdf 9.6 hw06.pdf 9.6 hw06.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw01.pdf 6.6 hw01.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.2 hw02.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw03.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw03.pdf 9.4 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7
 hw04.pdf 9.8 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw01.pdf 6.6 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw02.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw03.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf 9.6 hw06.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw01.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf 9.9 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw03.pdf 9.9 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.7 hw01.pdf 6.8 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.6 hw06.pdf 9.7 hw03.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw02.pdf 9.9 hw03.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf
 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw04.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf</td><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf 9.9 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw04.pdf 7.8 hw05.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<> | Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw02.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw04.pdf 9.6 hw04.pdf 9.6 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw06.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.4 hw04.pdf 9.6 hw06.pdf 9.6 hw06.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw01.pdf 6.6 hw01.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.2 hw02.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw03.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw03.pdf 9.4 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf
 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw01.pdf 6.6 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw02.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw03.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf 9.6 hw06.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw01.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf 9.9 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw03.pdf 9.9 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.7 hw01.pdf 6.8 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.6 hw06.pdf 9.7 hw03.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw02.pdf 9.9 hw03.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf
 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw04.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf</td><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf 9.9 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw04.pdf 7.8 hw05.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<> | Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw06.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.4 hw04.pdf 9.6 hw06.pdf 9.6 hw06.pdf < | Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw01.pdf 6.6 hw01.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.2 hw02.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.6 hw06.pdf < | Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw03.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw03.pdf 9.4 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw01.pdf 6.6 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw02.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw03.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf 9.6 hw06.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf
 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw01.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf 9.9 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw03.pdf 9.9 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.7 hw01.pdf 6.8 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.6 hw06.pdf 9.7 hw03.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw02.pdf 9.9 hw03.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw04.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf
 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf</td><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf 9.9 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw04.pdf 7.8 hw05.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<> | Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw01.pdf 6.6 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw02.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw03.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf 9.6 hw06.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw01.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf 9.9 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw03.pdf 9.9 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.7 hw01.pdf 6.8 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.6 hw06.pdf 9.7 hw03.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf
 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw02.pdf 9.9 hw03.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw04.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf</td><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf 9.9 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw04.pdf 7.8 hw05.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<> | Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.6 hw01.pdf 6.6 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5
hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw02.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw03.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf 9.6 hw06.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw01.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf 9.9 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw03.pdf 9.9 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.7 hw01.pdf 6.8 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.6 hw06.pdf 9.7 hw03.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw02.pdf 9.9 hw03.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw04.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2
hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf</td><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf 9.9 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw04.pdf 7.8 hw05.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<> | Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw04.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf 9.6 hw06.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw01.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf 9.9 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw03.pdf 9.9 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.7 hw01.pdf 6.8 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.6 hw06.pdf 9.7 hw03.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3
 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw02.pdf 9.9 hw03.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw04.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf</td><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf 9.9 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw04.pdf 7.8 hw05.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<> | Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw01.pdf
 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf 9.9 hw02.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw03.pdf 9.9 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.7 hw01.pdf 6.8 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.6 hw06.pdf 9.7 hw03.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw02.pdf 9.9 hw03.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw04.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf
 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf</td><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf 9.9 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw04.pdf 7.8 hw05.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<> | Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw03.pdf 9.9 hw04.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.7 hw01.pdf 6.8 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.6 hw06.pdf 9.7 hw03.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw02.pdf 9.9 hw03.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2
hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw04.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf</td><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf 9.9 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw04.pdf 7.8 hw05.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<> | Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 6.7 hw01.pdf 6.8 hw02.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.6 hw06.pdf 9.7 hw03.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw02.pdf 9.9 hw03.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019
 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw04.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf</td><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf 9.9 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw04.pdf 7.8 hw05.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""></t<></td></t<></td></t<></td></t<></td></t<></td></t<></td></t<> | Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw02.pdf 9.9 hw03.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3
hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw04.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf</td><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf 9.9 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw04.pdf 7.8 hw05.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""></t<></td></t<></td></t<></td></t<></td></t<></td></t<> | Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw02.pdf 9.9 hw03.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6
hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw04.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf</td><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf 9.9 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw04.pdf 7.8 hw05.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""></t<></td></t<></td></t<></td></t<></td></t<> | Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw02.pdf 9.9 hw03.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf
 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw04.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf</td><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf 9.9 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw04.pdf 7.8 hw05.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""></t<></td></t<></td></t<></td></t<> | Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.7 hw07.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.8 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf <t< td=""><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf
7.7 hw04.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf <</td><td>Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf</td><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf 9.9 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw04.pdf 7.8 hw05.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""></t<></td></t<></td></t<> | Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw03.pdf 9.8 hw04.pdf < | Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf < | Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw04.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf < | Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf < | Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf < | Fall 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw06.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw02.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf
 8.6 hw06.pdf 8.7 hw07.pdf 8.7 hw07.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw07.pdf 9.8 hw03.pdf 9.9 hw02.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf | Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw04.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw04.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw04.pdf 9.7 hw04.pdf 9.8 hw04.pdf 9.9 hw04.pdf <t< td=""><td>Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw04.pdf 7.8 hw05.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""></t<></td></t<> | Fail 2019 6.1 hw01.pdf 6.2 hw02.pdf 6.3 hw03.pdf 6.4 hw04.pdf 6.5 hw05.pdf 6.6 hw06.pdf 7.1 hw01.pdf 7.2 hw02.pdf 7.3 hw03.pdf 7.4 hw04.pdf 7.5 hw05.pdf 7.6 hw04.pdf 7.7 hw04.pdf 7.8 hw05.pdf 7.7 hw07.pdf 7.8 hw08.pdf 7.8 hw08.pdf 7.8 hw08.pdf 8.1 hw01.pdf 8.2 hw04.pdf 8.3 hw03.pdf 8.4 hw04.pdf 8.5 hw05.pdf 8.6 hw06.pdf 9.1 hw01.pdf 9.2 hw02.pdf 9.3 hw03.pdf 9.4 hw04.pdf 9.5 hw05.pdf 9.6 hw06.pdf 9.7 hw04.pdf 9.8 hw04.pdf <t< td=""></t<> |

11 Fall 2014	199
11.1 hw01.pdf	200
11.2 hw02.pdf	201
11.3 hw03.pdf	202
11.4 hw04.pdf \dots	203
12 Spring 2001	205
12.1 hw01.pdf	206
12.2 hw02.pdf	207
12.3 hw03.pdf	208
12.4 hw04.pdf	210
12.5 hw05.pdf	211
13 Spring 2000	213
13.1 hw01.pdf	214
13.2 hw02.pdf	215
13.3 hw03.pdf	217
13.4 hw04.pdf	218
13.5 hw05.pdf	219
13.6 $hw06.pdf$	221
14 Fall 2024 Solutions	222
14.1 hw01-sol.v.html	223
14.2 hw02 sol.pdf	232
14.3 hw02-sol.v.html	239
14.4 hw03-sol-p1.v.html	248
14.5 hw03-sol.v.html	258
14.6 hw04 sol.pdf	269
14.7 hw05-sol.v.html	275
14.8 hw06 sol.pdf \ldots	286
15 Fall 2023 Solutions	289
15.1 hw01-sol.v.html	290
15.2 hw02-sol.v.html	295
15.3 hw03-sol.v.html	303
15.4 hw04 sol.pdf	309
15.5 hw05-sol.v.html \ldots	318
16 Fall 2022 Solutions	325
16.1 hw01-sol.v.html	326
16.2 hw02-sol.v.html	332
16.3 hw03 sol.pdf	340
16.4 hw04-sol.v.html	352
16.5 hw05 sol.pdf	360
16.6 hw05-sol.v.html	371

17	Fall	2021 Solutions 3	90
	17.1	hw01 sol.pdf	391
	17.2	hw01-sol.v.html	395
	17.3	hw02-sol.v.html	399
	17.4	hw03 sol.pdf	108
	17.5	hw04 sol.pdf	114
	17.6	hw04-sol.v.html	421
	17.7	hw05 sol.pdf	129
	17.8	hw06-sol.v.html	130
18	Fall	2020 Solutions 4	37
	18.1	hw01 sol.pdf	138
	18.2	hw02-sol.v.html	144
	18.3	hw03-sol.v.html	148
	18.4	$hw04 \ sol.pdf \ldots \ldots$	156
19	Fall	2019 Solutions 4	63
	19.1	hw01 sol.pdf	164
	19.2	hw01-sol.v.html	170
	19.3	hw02 sol.pdf	174
	19.4	hw02-sol-try.v.html	180
	19.5	hw02-sol.v.html	185
	19.6	hw03 sol.pdf	190
	19.7	hw04 sol.pdf	195
	19.8	hw05 sol.pdf	501
	19.9	hw06-sol.v.html	503
20	T-11	2018 Solutions	00
20	Fan 20.1	2018 Solutions 5 hm01 col w html 5	109 10
	20.1	hw01-sol.v.litilli)10 :15
	20.2	hw02 sol.pdf)1) (10
	20.5)10 (04
	20.4)24 505
	20.0 20.6	hw06 col m df)20 :91
	20.0))) ())
	20.7	hw02 col p df)04 : 41
	20.8)41
21	Fall	2017 Solutions 5	48
41	21.1	hw01 sol pdf	549
	21.1	hw01-sol.v.html	551
	21.3	hw02-sol v html	554
	21.0	hw04-sol v html	560 560
	21.4	hw05-sol v html	565 565
	21.6	hw06 sol pdf	500 570
	21.0	hw07-sol.v.html	575

	Fall 2016 Solutions	583
	22.1 hw01 sol.pdf	584
	22.2 hw02-sol.v.html	589
	$22.3 \text{ hw03 sol.pdf} \dots \dots$	594
	22.4 hw04 sol.pdf	599
	22.5 hw04-sol.v.html	607
	22.6 hw05 sol.pdf	513
	22.7 hw06-sol.v.html	618
23	Fall 2015 Solutions	626
	23.1 hw01 sol.pdf	627
	$23.2 \text{ hw}02 \text{ sol.pdf} \dots \dots$	633
	23.3 hw02-sol.v.html	637
	23.4 hw03 sol.pdf	642
	23.5 hw04 sol.pdf	649
	23.6 hw04-sol.v.html	354
	23.7 hw05 sol.pdf	666
	$23.8 hw06 sol.pdf \dots \dots$	672
24	Fall 2014 Solutions	675
	24.1 hw01-sol.v.html	676
	24.2 hw02-sol v html	380
		500
	$24.3 hw03 sol.pdf \dots \dots$	586
	$\begin{array}{c} 44.3 \mathrm{hw03 \ sol.pdf} \\ 44.4 \mathrm{hw03-sol.v.html} \\ \end{array}$	586 590
	24.3 hw03 sol.pdf	586 586 590 598
	24.3 hw03 sol.pdf	586 590 598 700
25	24.3 hw03 sol.pdf	500 586 590 598 700 700
25	24.3 hw03 sol.pdf	500 586 590 598 700 700
25	24.3 hw03 sol.pdf	500 586 590 598 700 700 706 707 709
25	24.3 hw03 sol.pdf	500 586 590 598 700 700 700 707 709 721
25	24.3 hw03 sol.pdf 24.4 hw03-sol.v.html 24.4 hw03-sol.v.html 24.5 hw04 sol.pdf 24.5 hw04 sol.pdf 24.6 hw04-sol.v.html 24.6 hw04-sol.v.html 24.6 hw04-sol.v.html 25.1 hw01 sol.html 25.2 hw03 sol.html 25.2 hw03 sol.html 25.3 hw04 sol.html 25.4 hw05 sol.html 25.4 hw05 sol.html	 586 590 598 700 706 707 709 721 735
25	24.3 hw03 sol.pdf 24.4 hw03-sol.v.html 24.4 hw03-sol.v.html 24.5 hw04 sol.pdf 24.5 hw04 sol.pdf 24.6 hw04-sol.v.html 24.6 hw04-sol.v.html 26.1 hw01 sol.html 25.1 hw01 sol.html 27.1 hw01 sol.html 25.2 hw03 sol.html 27.1 hw01 sol.html 25.3 hw04 sol.html 27.1 hw05 sol.html 25.4 hw05 sol.html 27.1 hw05 sol.html	 500 500
25 26	24.3 hw03 sol.pdf 24.4 hw03-sol.v.html 24.4 hw03-sol.v.html 24.5 hw04 sol.pdf 24.5 hw04 sol.pdf 24.6 hw04-sol.v.html 24.6 hw04-sol.v.html 25.2 hw03 sol.html 25.2 hw03 sol.html 25.2 hw03 sol.html 25.3 hw04 sol.html 25.4 hw05 sol.html 25.4 hw05 sol.html 25.2 hw03 sol.html 25.4 hw05 sol.html 25.4 hw05 sol.html	 586 586 586 590 598 700 706 707 709 721 735 743 744

1 Fall 2024

LSU EE 4755

Homework 1 Due: 20 September 2024

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2024/hw01.v.html.

Collaboration Rules

Each student is expected to complete his or her own assignment. It is okay to work with other students and to ask questions in order to get ideas on how to solve the problems or how to overcome some obstacle (be it a question of Verilog syntax, interpreting error messages, how a part of the problem might be solved, etc.) It is also acceptable to seek out digital design resources for help on Verilog, digital design, etc. It is okay to make use of AI LLM tools such as ChatGPT and Copilot to generate sample Verilog code. (Do not assume LLM output is correct. Treat LLM output the same way one might treat legal advice given by a lawyer character in a movie: it may sound impressive, but it can range from sage advice to utter nonsense.)

After availing oneself to these resources each student is expected to be able to complete the assignment alone. Test questions will be based on homework questions and the assumed time needed to complete the question will be for a student who had solved the homework assignment on which it was based.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account, copy the assignment, and run the Verilog simulator on the unmodified homework file, hw01.v. Do this early enough so that minor problems (*e.g.*, password doesn't work) are minor problems.

Homework Introduction

In this assignment various modules computing dot products will be completed. The actual computation needed is shown in the comments, so forgetting what a dot product is should not be an impediment to this assignment, but it is something you should know. The dot product of *n*-element vector *a* with *n*-element vector *b* is given by $a \cdot b = \sum_{i=0}^{n-1} a_i b_i$.

The modules for Problem 1, dot2, dot3, dot4, compute the dot product efficiently. That's why they are first. The modules for Problem 2, dot2m, dot4m, and dot6m, compute the same result, but the way in which the data flows through the modules is different (and may result in slower hardware if the synthesis program does not come to the rescue). The modules in Problem 3 share the tree structure of those in Problem 1, but precision of the two input vectors can be different, for example one vector can consist of 8-bit elements and the other of 4-bit elements. The pedagogical motivation is to exercise skill with module parameters, but it also is good exposure to an important feature of hardware used for neural network computations: mixed precision.

Testbench

To compile your code and run the testbench press [F9] in an Emacs buffer in a properly set up account. (Of course the testbench won't run until compilation errors are fixed.) The testbench will test modules for all three problems in this assignment. The beginning of the testbench output, which may quickly scroll by, will look something like this: Compilation started at Sat Sep 14 17:18:51

```
xrun -sv -batch -exit hw01.v
TOOL: xrun(64) 24.03-s005: Started on Sep 14, 2024 at 17:18:51 CDT
xrun(64): 24.03-s005: (c) Copyright 1995-2024 Cadence Design Systems, Inc.
Recompiling... reason: file './hw01.v' is newer than expected.
```

expected: Sat Sep 14 17:06:07 2024 actual: Sat Sep 14 17:18:50 2024

At the end of the testbench output is a tally of the number of errors in each module. For a correctly solved assignment the output will be:

```
End of tests. For dot2: 0 errors out of 2000 tests.
End of tests. For dot2m: 0 errors out of 2000 tests.
End of tests. For dot2y: 0 errors out of 2000 tests.
End of tests. For dot3: 0 errors out of 2000 tests.
End of tests. For dot4: 0 errors out of 2000 tests.
End of tests. For dot4m: 0 errors out of 2000 tests.
End of tests. For dot4y: 0 errors out of 2000 tests.
End of tests. For dot4y: 0 errors out of 2000 tests.
End of tests. For dot6m: 0 errors out of 2000 tests.
xmsim: *W,RNQUIE: Simulation is complete.
xcelium> exit
TOOL: xrun(64) 24.03-s005: Exiting on Sep 14, 2024 at 17:18:52 CDT (total: 00:00:01)
```

Further up in the output the testbench shows the details for modules that produced incorrect output. The testbench will show the name of the module, the parameters (w or wa and wb), the module output, the expected value (just to the right of "(correct)". On the following lines the input to the module will be shown, first in decimal, then in hexadecimal. For example, in an unmodified assignment the first reported errors are:

```
Starting tests for Prob 1 w=2.
Error, dot2, w=2, z != 0 (correct)
0 * 0 + 0 * 0
0x0 * 0x0 + 0x0 * 0x0
Error, dot2, w=2, z != 0 (correct)
0 * 1 + 0 * 1
0x0 * 0x1 + 0x0 * 0x1
```

The output of the module here is z, meaning it isn't connected to anything.

The testbench starts off with debug-friendly inputs. In the first input all elements of **a** and **b** are zero (seen above), in the second all elements of **a** are zero and elements of **b** are 1. After about six debug-friendly sets of inputs the inputs are randomly chosen. If you'd like to set your own debug-friendly inputs, search for "Test Patterns" and add (or modify) one of the cases. It would be a good idea not to modify the default case. For grading, your assignment will be tested with a fresh copy of the testbench.

Here are some more examples of errors reported by the testbench:

```
Starting tests for Prob 1 w=2.
Error, dot2, w=2, 0 != 1 (correct)
1 * 0 + 1 * 1
0x1 * 0x0 + 0x1 * 0x1
Error, dot2, w=2, 1 != 3 (correct)
1 * 3 + 2 * 0
0x1 * 0x3 + 0x2 * 0x0
Error, dot2, w=2, 1 != 3 (correct)
2 * 1 + 3 * 3
0x2 * 0x1 + 0x3 * 0x3
```

The testbench will only show details of the first five errors in each module.

Common Problems

Here are some common errors messages, which will be encountered when the code is compiled (for example, by pressing $\boxed{F9}$).

file: hw01.v
 mult mym(p, a[0], b[0]);

xmvlog: *E,NODFNT (hw01.v,105!13): Implicit net declaration (p) is NOT allowed, since 'default_nettype is declared as NONE [19.2(IEEE 2001)].

The problem above is that **p** was never declared. "Implicit net declaration" refers to a Verilog feature in which an object is assumed to be a **wire** if it had not been declared. That feature has been turned off since it can hide typos. The solution is to declare something like **uwire** [um-1:0] **p**;.

mult mym(p, a[0], b[0]);
 !

mislabel: *F,CUVMPW (./hw01.v,106!16): port sizes differ in port connection(8/5) for the instance(testbench.genblk1[1].tb.genblk1.d2) .

The problem above is that the number of bits in a[0] is not the same as the number of bits in the second input to mult. The solution is to specify the mult w parameter value in the instantiation.

Helpful Examples

A good past assignment to look at is 2023 Homework 1. Like this assignment, a module, say minmax8, is completed by instantiating other modules and splitting minmax8's inputs among the instantiations. The tree-like structure of the modules in Problem 1 and 3 of this (2024) assignment matches those in the 2023 assignment. Problem 2 is sort of tree-like. Problem 3 in this assignment requires more attention to parameters and port sizes than in past assignments.

Problem 1: Modules dot2, dot3, and dot4, each have two inputs, a and b, and one output dp, and parameter w. In all modules output dp is a w-bit value. In dot2 inputs a and b are each 2-element arrays of w-bit values. In dot3 and dot4 inputs a and b are 3- and 4-element arrays of w-bit values. The inputs and outputs are (to be interpreted as) unsigned integers. Output dp is to be set to the dot product of vectors a and b (the computation is shown in the comments of each module).

(a) Complete module dot2 using instantiations of modules mult and add. These modules are shown below and are in the Problem 1 part of the assignment file.

module mult

```
#( int w = 5 ) ( output uwire [w-1:0] p, input uwire [w-1:0] a, b );
assign p = a * b;
endmodule
module add
#( int w = 5 ) ( output uwire [w-1:0] s, input uwire [w-1:0] a, b );
assign s = a + b;
endmodule
module dot2
#( int w = 5 )
( output uwire [w-1:0] dp,
    input uwire [w-1:0] a[1:0], b[1:0] );
// Compute
// dp = a[0] * b[0] + a[1] * b[1];
// Using instantiation(s) of
// mult, add.
```

endmodule

Do not use procedural code and do not use continuous assignments in dot2 and in the other modules to be completed in this assignment. Continuous assignments start with the assign keyword, and procedural code starts with always_comb, always, initial, etc. In addition to instantiating add and mult modules it will be necessary to declare uwire objects. These requirements are listed in the checkbox items in the code.

(b) Complete module dot3. As with dot2, procedural code and continuous assignments cannot be used. However, to complete dot3 use an instantiation of dot2 and as many add and mult modules as needed. (Obviously the fewer the better.) These requirements are listed in the checkbox items in the code.

(c) Complete module dot4. Consider instantiations of modules add, mult, dot2, and dot3. There are several ways to solve this. Instantiate as few modules as is reasonable and also consider how long it will take to compute the result. (The time to compute a result has not been covered, but one should be able to get a feel for it by drawing a diagram of the hardware.)

If the instructions above were followed the modules should be synthesizable. This can be verified by using the command genus -files syn.tcl.

Problem 2: Modules dot2m, dot4m, and dot6m, each have three inputs, si, a and b, and one output dp, and parameter w. In all of these modules output dp and input si are w-bit values. Inputs a and b are arrays with the number of elements matching the digit in the module name (two for dot2m, four for dot4m, etc). The inputs and outputs are (to be interpreted as) unsigned integers. When complete the output dp is set to the dot product of vectors a and b plus the scalar si (the computation is shown in the comments). Like those in Problem 1, these modules compute a dot product, but they have an extra input, si, which is added to the dot product. That extra input will come in handy when, say, using two dot2m modules in a dot4m module. (It will turn out that the Problem 1 dot product modules are better than the modules in this problem, and the disadvantage is more than just the need to do one extra addition.)

(a) Shown below is a completed multiply-add module and an incomplete dot2m module. Complete dot2m using instantiations of madd. As in Problem 1 do not use procedural code nor continuous assignments. See the checkbox items in the code for these and other requirements.

```
module madd
```

```
#( int w = 8 )
  ( output uwire [w-1:0] s, input uwire [w-1:0] si, a, b );
  assign s = si + a * b;
endmodule
```

```
module dot2m
```

```
#( int w = 5 )
  ( output uwire [w-1:0] dp,
    input uwire [w-1:0] si, a[1:0], b[1:0] );
// Compute:
// dp = si + a[0] * b[0] + a[1] * b[1];
// Using instantiations of:
// madd.
```

endmodule

(b) Complete modules dot4m and dot6m. Consider using instantiations of madd, dot2m, and dot4m. (Don't instantiate dot4m in dot4m, we'll get to recursive instantiation soon enough.) As before, instantiate the minimum number of modules, and no procedural code and no continuous assignments can be used. See the checkbox items in the code for these and other requirements.

Problem 3: Modules dot2y and dot4y each have an output dp and inputs a and b, and two parameters wa and wb. Input a is an array of wa-bit elements and input b is an array of wb-bit elements. The number of bits in the output of dot2y is wa + wb + 1, which is the minimum number of bits needed to avoid overflow. (The number of bits in the product of a w_a -bit unsigned integer with a w_b -bit unsigned integer is $w_a + w_b$. If two w-bit unsigned integers are added the sum will require no more than w + 1 bits.) Similarly, dp in dot4y is wa + wb + 2 bits.

Why go to the trouble of making the elements of **a** and **b** different sizes? To reduce cost and improve performance. In some applications, most notably neural networks, a large number of dot products (a component of matrix/vector multiplication) need to be computed. Furthermore, in neural network applications the precision of the operands can be made much lower than operands used in other application areas needing dot products, such as scientific computation. For that reason, specialized hardware for neural network computation often use lower-precision and mixed-precision arithmetic units.

(a) Complete dot2y using instantiations of modules multy and addy. Unlike the previous problems, here the connections of multy and addy will need to be modified. Consider the unsolved modules:

```
module multy
```

```
#(int w = 5)
   ( output uwire [w-1:0] p,
     input uwire [w-1:0] a,
     input uwire [w-1:0] b );
   // Modify the connections to this module. (The stuff above this line.)
   assign p = a * b;
endmodule
module addy
  #(int w = 3)
   ( output uwire [w-1:0] s,
     input uwire [w-1:0] a,
     input uwire [w-1:0] b );
  // Modify the connections to this module. (The stuff above this line.)
   assign s = a + b;
endmodule
module dot2v
  \#( int wa = 5, wb = 6, wo = wa + wb + 1 )
   ( output uwire [wo-1:0] dp,
     input uwire [wa-1:0] a[1:0],
     input uwire [wb-1:0] b[1:0] );
  // Compute:
  // dp = a[0] * b[0] + a[1] * b[1];
  // Using instantiations of:
   11
        multy, addy
```

endmodule

To compute a[0] * b[0] needed for dot2y a multiply module is needed in which the two inputs and the output can each be different sizes. Modify multy so that it can be used in dot2y. Do the same for addy, then complete dot2y using these modules. Modify multy and addy so that they can also be used for ${\tt dot4y},$ if needed.

Make sure that the sizes of the ports are the minimum size needed. That is, don't make the number of bits in the multiplier output more than the sum of the bits in the two inputs. See the checkbox items in the code for these and other requirements.

(b) Complete dot4y. Consider instantiations of dot2y, multy, and addy. Take care to set parameter values so that the minimum number of bits are used in the ports. That is, when instantiating dot2y to make dot4y don't set the third dot2y parameter to something larger than wa+wb+1. (There is no need to set the third parameter at all.) See the checkbox items in the code for these and other requirements.

Verify that code is synthesizable by running the synthesis script. If there are no errors, running this command will generate output that includes like the following: Synthesizing at effort level "high"

Module Name	Area	Delay	Delay		Synth	
		Actual	Target		Time	
dot2_w4	13288	1.89	100.0	ns	5	s
dot2m_w4	15482	2.45	100.0	ns	1	s
dot3_w4	20154	2.20	100.0	ns	2	s
dot4_w4	28021	2.80	100.0	ns	2	s
dot4m_w4	29645	2.66	100.0	ns	2	s
dot6m_w4	44379	3.67	100.0	ns	3	s
dot2_w10	87617	4.21	100.0	ns	6	s
dot2m_w10	94012	4.31	100.0	ns	6	s
dot3_w10	132035	4.67	100.0	ns	8	s
dot4_w10	177361	4.72	100.0	ns	10	s
dot4m_w10	183139	4.83	100.0	ns	11	s
dot6m_w10	272976	6.01	100.0	ns	16	s
dot2y_wa4_wb2	12180	2.51	100.0	ns	2	s
dot2y_wa6_wb4	40359	4.42	100.0	ns	4	s
dot4y_wa4_wb2	27229	3.46	100.0	ns	3	s
dot4y_wa6_wb4	85180	5.40	100.0	ns	7	s

LSU EE 4755

Homework 2

Due: 4 October 2024

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2024/hw02.v.html.

Collaboration Rules

Each student is expected to complete his or her own assignment. It is okay to work with other students and to ask questions in order to get ideas on how to solve the problems or how to overcome some obstacle (be it a question of Verilog syntax, interpreting error messages, how a part of the problem might be solved, etc.) It is also acceptable to seek out digital design resources for help on Verilog, digital design, etc. It is okay to make use of AI LLM tools such as ChatGPT and Copilot to generate sample Verilog code. (Do not assume LLM output is correct. Treat LLM output the same way one might treat legal advice given by a lawyer character in a movie: it may sound impressive, but it can range from sage advice to utter nonsense.)

After availing oneself to these resources each student is expected to be able to complete the assignment alone. Test questions will be based on homework questions and the assumed time needed to complete the question will be for a student who had solved the homework assignment on which it was based.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account (if necessary), copy the assignment, and run the Verilog simulator on the unmodified homework file, hw02.v. Do this early enough so that minor problems (*e.g.*, password doesn't work) are minor problems.

Homework Overview

In this assignment modules will be completed that compute $a2^s + b > c$ where inputs a and b are real and inputs s and c are non-negative integers. Each module has an output gt, which should be set to 1 if the comparison is true and 0 otherwise. There is also an output ssum which should be set to $a2^s + b$. What makes this interesting is that the sizes of all inputs are parameters, and that in the instantiations tested the number of bits in the significands of a and b can be less than the number of bits in c.

The floating point calculations and conversion(s) are to be done using Chipware modules. Solving this assignment requires a straightforward application of Verilog techniques for instantiating modules and wiring them together. It also requires an understanding of when and how to convert numbers from floating-point to integer representations.

As of this writing two modules are to be completed, comp_fp and comp_int. In comp_fp the greater-than comparison is to be done in floating point (using a Chipware module) and in comp_int it is to be done using an integer comparison (using the > operator).

Testbench

To compile your code and run the testbench press [F9] in an Emacs buffer in a properly set up account. The testbench will apply inputs to several instantiation of modules comp_fp and comp_int. The instantiations differ on the number of bits used for the integer inputs and the format of the floating-point output. The instantiation parameters are shown at the end of the testbench along with a summary of the errors for that module. The end of the testbench output for an unmodified assignment appears below:

```
Total comp_int exp=7, sig=6, wc= 6, s=0: Errors: 50000 ss, 31394 gt.
Total comp_int exp=7, sig=6, wc= 6, s>0: Errors: 50000 ss, 28962 gt.
Total comp_int exp=7, sig=7, wc=10, s=0: Errors: 50000 ss, 33366 gt.
```

Total comp_int exp=7, sig=7, wc=10, s>0: Errors: 50000 ss, 31052 gt. Total comp_int exp=8, sig=5, wc=12, s=0: Errors: 50000 ss, 35958 gt. Total comp_int exp=8, sig=5, wc=12, s>0: Errors: 50000 ss, 33117 gt. Total comp_fp exp=7, sig=6, wc= 6, s=0: Errors: 50000 ss, 31310 gt. Total comp_fp exp=7, sig=6, wc= 6, s>0: Errors: 50000 ss, 29113 gt. Total comp_fp exp=7, sig=7, wc=10, s=0: Errors: 50000 ss, 33478 gt. Total comp_fp exp=7, sig=7, wc=10, s>0: Errors: 50000 ss, 30957 gt. Total comp_fp exp=8, sig=5, wc=12, s=0: Errors: 50000 ss, 33073 gt. Total comp_fp exp=8, sig=5, wc=12, s>0: Errors: 50000 ss, 33073 gt. TO0L: xrun(64) 24.03-s005: Exiting on Sep 29, 2024 at 14:00:48 CDT (total: 00:00:02)

Compilation finished at Sun Sep 29 14:00:48, duration 2.14 s

Each line starting with Total shows a tally of results. After Total the line shows the module name, either comp_int or comp_fp, and three parameter values. The label exp shows the value of parameter w_exp, which is the size of the exponent of the FP numbers; label sig shows the value of parameter w_sig, which the size of the significand of inputs a and b, and wc shows the value of parameter w_c, the number of bits in input c. The lines with label s=0 show the results of tests in which module input s is set to zero, the lines with label s>0 show the results of tests in which module input s can be non-zero. Tallies of errors are shown after Errors:, first of the ssum output (scaled sum), and then for the gt output. In the unmodified assignment the ssum is unconnected, and so its output is always wrong. Output gt is set to 1, which is mostly but not always wrong.

Further up, the testbench shows some examples of incorrect output:

```
Starting comp_int tests iwth exp=7, sig=6, wc=6
Error in #(7,6,6) a=-17.50, s=0, b=0.04, c=3. ss 0.0000e+00 != -1.7464e+01 (correct)
Error in #(7,6,6) a=-17.50, s=0, b=0.04, c=3. gt 1 != 0 (correct) -20.4644
Error in #(7,6,6) a=-0.80, s=0, b=18.25, c=12. ss 0.0000e+00 != 1.7445e+01 (correct)
Error in #(7,6,6) a=12.62, s=0, b=13.62, c=0. ss 0.0000e+00 != 2.6250e+01 (correct)
Error in #(7,6,6) a=-3.62, s=0, b=3.72, c=0. ss 0.0000e+00 != 9.3750e-02 (correct)
```

In the sample above the first Error line indicates that the module output was 0.0000e+00 (that's what a z would look like) but $-1.7464 \times 10^1 = -17.464 = -1.7454e+01$ was expected. The second Error line indicates that the gt output was 1 but should have been 0. The -20.4544 is the correct difference between c = 3 and -17.5 + 0.04 = -17.46, indicating that it was not even close. Note that the number of digits past the decimal point is limited and so the full number is not shown. About the first five errors of each type will be shown.

Whether or not there are errors, at least one pair of lines is printed for each test. That output is preceded by the word **Sample** if the output is correct. Appearing below is the beginning and end of the output for correct modules:

```
Starting comp_int tests iwth exp=7, sig=6, wc=6
Sample in #(7,6,6) a=-17.50, s=0, b=0.04, c=3. ss -1.7500e+01 == -1.7464e+01 (cor-
rect)
Sample in #(7,6,6) a=-17.50, s=0, b=0.04, c=3. gt 0 == 0 (correct) -20.4644
Finished comp_int tests exp=7, sig=6, wc=6, s=0. Errors: 0 ss, 0 gt
Finished comp_int tests exp=7, sig=6, wc=6, s>0. Errors: 0 ss, 0 gt
```

[snip]

Total comp_int exp=7, sig=6, wc= 6, s=0: Errors: 0 ss, 0 gt.

```
Total comp_int exp=7, sig=6, wc= 6, s>0: Errors: 0 ss, 0 gt.
Total comp_int exp=7, sig=7, wc=10, s=0: Errors: 0 ss, 0 gt.
Total comp_int exp=7, sig=7, wc=10, s>0: Errors: 0 ss, 0 gt.
Total comp_int exp=8, sig=5, wc=12, s=0: Errors: 0 ss, 0 gt.
Total comp_int exp=8, sig=5, wc=12, s>0: Errors: 0 ss, 0 gt.
Total comp_fp exp=7, sig=6, wc= 6, s=0: Errors: 0 ss, 0 gt.
Total comp_fp exp=7, sig=6, wc= 6, s>0: Errors: 0 ss, 0 gt.
Total comp_fp exp=7, sig=7, wc=10, s=0: Errors: 0 ss, 0 gt.
Total comp_fp exp=7, sig=7, wc=10, s=0: Errors: 0 ss, 0 gt.
Total comp_fp exp=8, sig=5, wc=12, s=0: Errors: 0 ss, 0 gt.
Total comp_fp exp=8, sig=5, wc=12, s=0: Errors: 0 ss, 0 gt.
```

To add or change instantiation parameters search for the place where variable **pset** is assigned and edit the initialization of **pset** (and change **npsets** if needed):

The testbench will report on the correctness and accuracy of the output.

References and Helpful Examples

For this assignment Chipware modules are to be instantiated to perform floating-point computation and floating-point/integer conversion. A link to the Genus ChipWare IP Components Guide can be found on the course references page. The IEEE 754 floating point standard is described in the types lecture code, be sure to scroll down to reach it.

See 2023 Homework 2 for examples of how to instantiate these modules to perform a computation and for integer/floating-point conversion. A copy of the solution to the 2023 assignment is included in the 2024 assignment directory. As in this (2024) assignment the floating-point formats in the 2023 assignment vary and so parameters must be used when instantiating the Chipware modules to specify the exponent and significand length. In 2021 Homework 2 Chipware modules were instantiated with non-default exponent and significand lengths. Also see 2022 Homework 5. That assignment uses both combinational and sequential modules. (Sequential material has not yet been covered.) See ms_comb in 2022 Homework 5 for a straightforward connection of FP modules (but without format conversion). **Problem 1:** Module comp_fp has two floating-point (FP) inputs, a and b, two integer inputs s and c, one-bit output gt, and a FP output ssum; it also has integer parameters w_c, w_s, w_exp, w_sig and w_sig2. (The remaining parameters, w_fp and w_fp2, are set to the full size of the two FP formats used, don't change them.) Inputs a and b carry values in a custom IEEE 754 FP format with a w_exp-bit exponent and a w_sig-bit significand. The total size of each of these inputs is 1+w_exp+w_sig bits. (The custom format is recognized by the Chipware modules.) The value on input c is a w_c-bit unsigned integer. The value on output ssum is expected to be a IEEE-format FP number with a w_exp-bit exponent and w_sig2-bit significand.

The output ssum (scaled sum) is to be set to $a2^s + b$ and output gt is to be set to 1 if $a2^s + b > c$ and 0 otherwise.

For this problem one should review the IEEE 754 notes, plus the use of the Verilog concatenation (like $\{2'b11,a,4'd0\}$), shift (a<<2), and bit slice (a[6:1]) operators.

(a) Modify comp_fp so that it computes $a2^s$ without using Chipware modules. The value does not have to be assigned to any particular object, but it should be used to compute $a2^s + b$. To solve this subproblem one must understand the IEEE 754 format. A correct solution requires just a line or two of Verilog code. (Just one line if overflow is ignored, which is okay.)

Compute $a2^s$ without Chipware modules.

(b) Modify comp_fp so that ssum is set to $a2^s + b$. (For partial credit, or to get started quickly set ssum to a + b. If this is done correctly the testbench s=0 tests should show zero ss errors.) Compute the sum using Chipware modules and the value of $a2^s$ from the previous part.

Note that a and b have a w_sig -bit significand, but the sum should have a w_sig2 -bit significand. So, the significands of $a2^s$ and b must be lengthened (assume that $w_sig2 > w_sig$). See the description of the IEEE 754 format. Please don't look for a module to do this for you.

Convert $a2^s$ and b into FP types with a w_sig2-bit significand.

Using the value from the previous part, set ssum to $a2^s + b$.

(c) Modify comp_fp so that gt is correctly set using a floating-point comparison. Don't forget that input c carries an unsigned integer so that to do a FP comparison c will need to be converted.

Set gt.

Use Chipware modules for floating-point computation and floating-point/integer conversion.

Use procedural or implicit structural (assign) code for any integer computation.

Pay attention to cost: don't use more bits than are needed.

The modules must be synthesizable.

Problem 2: Module comp_int has the same connections as comp_fp and its outputs should be set to the same values.

(a) Modify comp_int so that it computes ssum using an instantiation of comp_fp. The ssum output of the comp_fp instance should connect to the ssum output of comp_int. Don't use the gt output of comp_fp so that the synthesis program doesn't synthesize comp_fp hardware for gt.

Compute ssum using an instance of comp_fp i with the gt output unconnected.

(b) Modify comp_int so that gt is correctly set using an integer comparison. That is, instead of converting c, convert ssum. For maximum credit convert ssum into an integer of as few bits as possible. Don't forget that c is unsigned but ssum is signed.

Compute gt using an integer comparison.

Try to use as few bits as possible.

Problem 3: Predict which version will be less expensive, comp_fp or comp_int. Then run the synthesis program to see which cost less.

Use the command genus -files syn.tcl to run synthesis. Be sure to correct any errors that prevent synthesis.

Predict which will be less costly.

Run synthesis to find out which really is.

Homework 3 Due: 20 Oct 2024 (evening)

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2024/hw03.v.html.

Collaboration Rules

LSU EE 4755

Each student is expected to complete his or her own assignment. It is okay to work with other students and to ask questions in order to get ideas on how to solve the problems or how to overcome some obstacle (be it a question of Verilog syntax, interpreting error messages, how a part of the problem might be solved, etc.) It is also acceptable to seek out digital design resources for help on Verilog, digital design, etc. It is okay to make use of AI LLM tools such as ChatGPT and Copilot to generate sample Verilog code. (Do not assume LLM output is correct. Treat LLM output the same way one might treat legal advice given by a lawyer character in a movie: it may sound impressive, but it can range from sage advice to utter nonsense.)

After availing oneself to these resources each student is expected to be able to complete the assignment alone. Test questions will be based on homework questions and the assumed time needed to complete the question will be for a student who had solved the homework assignment on which it was based.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account (if necessary), copy the assignment, and run the Verilog simulator on the unmodified homework file, hw03.v. Do this early enough so that minor problems (*e.g.*, password doesn't work) are minor problems.

Homework Overview

In string ((I am balanced)) the parentheses are balanced, but in ((Not balanced) they are not because a closing parenthesis is missing and so an opening parenthesis is unmatched. The modules in this assignment examine a string containing parentheses and report the number of unmatched closing,), and opening, (, parentheses. Both modules put these numbers on outputs left_out_n_unmat_close and right_out_n_unmat_open. The parentheses in a(b)c and (()a)() are correctly matched. The parentheses in ()), ((()), and))((are not. For inputs like (), (()), and ()() both outputs should be zero. For) and ()) the number of unmatched closing parentheses is one and so output left_out_n_unmat_close should be 1 and output right_out_n_unmat_open should be 0. See the testbench output for more examples.

In both modules, pmatch_base (Problem 1) and pmatch_mark (Problem 2), the string appears on input str. In pmatch_mark there is an additional output, str_marked, which should be set to a version of the string in which the correctly matched parentheses are replaced by angle brackets. For example, for input str='(()' the output shold be str_marked='(<>'. See the testbench output for more examples.

The modules each have parameter n. Input str and output str_marked are n-element unpacked (ordinary) arrays of 4-bit quantities. For convenience enumeration constants are defined for the characters used in this assignment:

typedef enum logic [3:0]
{ Char_Blank, Char_Dot,

```
Char_Open, Char_Close,
```

```
Char_Open_Okay, Char_Close_Okay } Char;
```

The input str can consist of any of the first four values. There is no distinction between Char_Blank and Char_Dot, they are stand-ins for arbitrary characters and neither affects paren-

thesis matching. The last two, Char_Open_Okay and Char_Close_Okay are to be used in Problem 2 for replacing properly matched parenthesis.

Those who are unsure of how to work with str or of just what the modules are supposed to do should examine modules pmatch_comb_base and pmatch_comb_mark. Module pmatch_comb_base will pass the testbench for Problem 1 (if it were renamed pmatch_base) and pmatch_comb_mark would pass the testbench for Problem 2 (if renamed).

These **comb** modules compute their results by scanning the string from left to right. In their synthesized hardware the critical path appears to be proportional to n, the string length. That's too long a critical path for our purposes. In Problems 1 and 2 this is to be overcome by using a recursive module structure that describes tree-like hardware. In a correct solution the critical path will be closer to log n, and the cost will be lower too.

The synthesis output below shows the result of synthesizing the comb base module and a correct solution to Problem 1 at exponentially increasing string lengths (n = 4, 8, 16, 32). Notice that in the comb version the delay too increases exponentially (in proportion to n) while the delay in the Problem 1 solution increases more linearly. Absolute costs are lower too. The differences are less stark with a larger delay target. The default synthesis script uses the larger delay target to save time.

Module Name	Area	Delay	Delay	Synth	
		Actual	Target	Time	
pmatch_comb_base_n4_13	43915	0.82	0.1 n	.s 24 s	5
pmatch_comb_base_n8_29	175285	2.31	0.1 n	.s 185 s	5
pmatch_comb_base_n16_61	221959	6.99	0.1 n	.s 256 s	5
pmatch_comb_base_n32_125	771830	15.69	0.1 n	.s 772 s	;
pmatch_base_n4	22979	1.22	0.1 n	.s 15 s	3
pmatch_base_n8	73381	1.93	0.1 n	.s 50 s	5
pmatch_base_n16	142421	3.24	0.1 n	.s 86 s	5
pmatch_base_n32	341921	4.49	0.1 n	.s 179 s	;
pmatch_comb_base_n4	11039	2.14	900.0 n	.s 8 s	3
pmatch_comb_base_n8	33748	7.11	900.0 n	.s 77 s	5
pmatch_comb_base_n16	93278	18.98	900.0 n	.s 53 s	5
pmatch_comb_base_n32	248862	48.57	900.0 n	.s 117 s	;
pmatch_base_n4	15550	3.10	900.0 n	.s 6 s	3
pmatch_base_n8	41187	5.99	900.0 n	.s 5 s	5
pmatch_base_n16	98336	9.91	900.0 n	.s 18 s	5
pmatch_base_n32	216143	14.60	900.0 n	.s 23 s	5

Testbench

To compile your code and run the testbench press [F9] in an Emacs buffer in a properly set up account. The testbench will apply inputs to several instantiations of modules pmatch_base and pmatch_mark. The instantiations differ in the length of the string. At the end of execution the number of errors for each module at each size are shown. The output below is from a correctly solved assignment:

Total pmatch_base n=4: Errors: 0 cl, 0 op, 0 mk. Total pmatch_base n=5: Errors: 0 cl, 0 op, 0 mk.

```
Total pmatch_base n=7: Errors: 0 cl, 0 op, 0 mk.
Total pmatch_base n=8: Errors: 0 cl, 0 op, 0 mk.
Total pmatch_base n=9: Errors: 0 cl, 0 op, 0 mk.
Total pmatch_base n=17: Errors: 0 cl, 0 op, 0 mk.
Total pmatch_mark n=4: Errors: 0 cl, 0 op, 0 mk.
Total pmatch_mark n=5: Errors: 0 cl, 0 op, 0 mk.
Total pmatch_mark n=7: Errors: 0 cl, 0 op, 0 mk.
Total pmatch_mark n=8: Errors: 0 cl, 0 op, 0 mk.
Total pmatch_mark n=9: Errors: 0 cl, 0 op, 0 mk.
Total pmatch_mark n=9: Errors: 0 cl, 0 op, 0 mk.
```

Each line starting with Total shows a tally of results. After Total the line shows the module name, either pmatch_base or pmatch_mark, and n, the length of the string. A tally of each output's error is shown after Errors:, cl is the number of incorrect closing-parentheses values, op is the number of opening-parenthesis values, and mk is the number of incorrectly marked strings.

Further up, the testbench shows sample output and error details. For each instantiation the first $n_{errors_show} = 5$ incorrect outputs are shown on lines starting with Error. If it would help to see more then feel free to search for n_{errors_show} and increase the value. In addition the details of the first $n_{samples_show} = 6$ correct outputs are shown on lines starting with Sample. The output below shows correct outputs:

Starting pmatch_base tests for n=5.

Sample	pmatch_base	n=5	'() '	':	close = 0,	open = 0	(both	correct)
Sample	pmatch_base	n=5	'.()'	':	close = 0,	open = 0	(both	correct)
Sample	pmatch_base	n=5	')('	':	close = 1,	open = 1	(both	correct)
Sample	pmatch_base	n=5	') '	':	close = 1,	open = 0	(both	correct)
Sample	pmatch_base	n=5	')) '	':	close = 2,	open = 0	(both	correct)
Sample	pmatch_base	n=5	'())) '	':	close = 2,	open = 0	(both	correct)
Sample	pmatch_base	n=5	'())('	':	close = 1,	open = 1	(both	correct)
Sample	$pmatch_base$	n=5	'())(('	':	close = 1,	open = 2	(both	correct)
Sample	pmatch_base	n=5	'))(('	':	close = 2,	open = 2	(both	correct)

In the sample above the first Sample line indicates that for input () both the left_out_n_unmat_close and right_out_n_unmat_open outputs were 0, which is correct because there were no unmatched parentheses. The second sample is also properly matched. It consists of a dot (which is just an ordinary character), parentheses, and spaces. The third sample has both one unmatched opening parenthesis and an unmatched closing parenthesis.

The testbench starts applying patterns found in str_special. Feel free to add your own to help with debugging. After the patterns in str_special are used the testbench will make up random patterns.

The output below is of a run using a partially correct pmatch_base:

```
Sample pmatch_base n=5 '()
                            ': close = 0,
                                           open = 0 (both correct)
Sample pmatch_base n=5 '.( ) ': close = 0,
                                           open = 0 (both correct)
Sample pmatch_base n=5 ')(
                          ': close = 1,
                                           open = 1 (both correct)
Sample pmatch_base n=5 ')
                                           open = 0 (both correct)
                            ': close = 1,
Error pmatch_base n=5 '))
                           ': close 0 != 2 (correct)
Sample pmatch_base n=5 '())) ': close = 2, open = 0 (both correct)
Error pmatch_base n=5 '))(( ': close 0 != 2 (correct)
Error pmatch_base n=5 ')) ': close 0 != 2 (correct)
```

The errors reported above seem to show that the left_out_n_unmat_close is wrong when the string starts with two consecutive closing parentheses.

The str_marked output of module pmatch_mark is supposed to show the string with the correctly matched parentheses replaced by angle brackets (actually less-than and greater-than symbols). Appearing below is sample output of the module in a correctly solved assignment. Two lines are used to show the result of each input. The first shows the input string, such as () in the first sample, the second line shows the marked string, such as <>.

```
Sample pmatch_mark n=5 '()
                             ': close = 0, open = 0 (both correct)
Sample pmatch_mark n=5 '<>
                           ' (marked_outpuut)
Sample pmatch_mark n=5 '.( ) ': close = 0,
                                           open = 0 (both correct)
Sample pmatch_mark n=5 '.< > ' (marked_outpuut)
Sample pmatch_mark n=5 ')(
                           ': close = 1,
                                           open = 1 (both correct)
Sample pmatch_mark n=5 ')(
                           ' (marked_outpuut)
Sample pmatch_mark n=5 ')
                            ': close = 1,
                                           open = 0 (both correct)
Sample pmatch_mark n=5 ')
                            ' (marked_outpuut)
Sample pmatch_mark n=5 '))
                            ': close = 2, open = 0 (both correct)
Sample pmatch_mark n=5 '))
                           ' (marked_outpuut)
Sample pmatch_mark n=5 '())) ': close = 2,
                                           open = 0 (both correct)
Sample pmatch_mark n=5 '<>)) ' (marked_outpuut)
Sample pmatch_mark n=5 '())( ': close = 1, open = 1 (both correct)
Sample pmatch_mark n=5 '<>)( ' (marked_outpuut)
Sample pmatch_mark n=5 '())((': close = 1,
                                           open = 2 (both correct)
Sample pmatch_mark n=5 '<>)((' (marked_outpuut)
Sample pmatch_mark n=5 '))(( ': close = 2, open = 2 (both correct)
Sample pmatch_mark n=5 '))(( ' (marked_outpuut)
```

The output below is of a run using an incorrect pmatch_mark module. An error line is printed for each incorrect output, left_out_n_unmat_close, right_out_n_unmat_open, and str_marked. For a particular input, say (), a module can have one incorrect output, such as left_out_n_unmat_close, while the other two outputs, right_out_n_unmat_open and str_marked are correct. That's the case in the first and last error below:

```
Starting pmatch_mark tests for n=5.
Error pmatch_mark n=5 '() ': close 1 != 0 (correct)
Error pmatch_mark n=5: '<<>>)' != '<> ' (correct)
Error pmatch_mark n=5 '.() ': open 3 != 0 (correct)
Error pmatch_mark n=5: '..(((' != '.< > ' (correct)
Error pmatch_mark n=5 ')( ': close 2 != 1 (correct)
```

References and Helpful Examples

The modules in this assignment must be recursively defined, so that they describe a tree-like structure. See the CLZ module from 2019 Homework 2. The assignment, solution, and live version done in class are part of the 2024 assignment directory, look for the file names starting 2019. Understanding the clz_tree_fat solution is sufficient. The trick used to avoid the adder in the clz module is not relevant to this 2024 assignment.

Problem 1: Module pmatch_base has one input, str, and two outputs left_out_n_unmat_close and right_out_n_unmat_open, and parameters n and wn. Input str is an n-element array of 4-bit quantities called characters, with str[0] being the leftmost character and str[n-1] being the rightmost character. Outputs left_out_n_unmat_close and right_out_n_unmat_open are each wn bits. They should be set to the number of unmatched parentheses as described in the introduction to the assignment represented as an unsigned integer. The default value of wn, $\lceil lg(n + 1) \rceil$, is the minimum value needed to correctly report n mismatched parentheses. (Setting wn to a larger values is a potential waste.)

Complete the module so that it produces these outputs and so that it describes tree-structured hardware by using recursion. The critical path should be proportional to $\log n$, which can be achieved by splitting the **str** input between two recursive instantiations and combining their outputs. It may help to examine **pmatch_comb_base**, which produces the same outputs, though not recursively.

Complete the module so that the testbench reports zero errors.

The module description must be recursive and describe tree-like hardware.

Set wn to the smallest correct value in the recursive instantiations.

Make sure the module is synthesizable using command genus -files syn.tcl.

Hint: Consider checking str only in the base (terminal) case of the recursion.

Problem 2: Module pmatch_mark has three inputs, str, left_in_n_unmat_open,

right_in_n_unmat_close, and three outputs left_out_n_unmat_close, right_out_n_unmat_open, str_marked, and parameter n. Input str and output str_marked are n-element 4-bit arrays. Input str carries a string, and output str_marked is to be set to a version of the input string with each properly matched Char_Open replaced with a Char_Open_Okay and each properly matched Char_Close_Okay.

Input left_in_n_unmat_open is set to the number of unmatched opening parentheses to the left of str. For example, suppose str='))' and left_in_n_unmat_open=1. Then that means that one of the unmatched parentheses in str is matched by something to the left of str. For this example, the value of str_marked='>)' because left_in_n_unmat_open=1. Similarly input right_in_n_unmat_close is set to the number of unmatched closing parentheses to the right of the string.

The testbench will always set left_in_n_unmat_open and right_in_n_unmat_close to zero. Your module should set them correctly in connections to recursive instantiations so that they can determine which of their parentheses are matched.

Outputs left_out_n_unmat_close, right_out_n_unmat_open should have the same values as they would in Problem 1. That is, they should show the number of unmatched opening and closing parentheses in str even if those parentheses are marked as matched due to values of left_in_n_unmat_open and right_in_n_unmat_close. For example, suppose str=')))()(' and left_in_n_unmat_open=2 and right_in_n_unmat_close=1. The module should set output left_in_n_unmat_open=3 (ignoring the 2 matches) and right_in_n_unmat_close=1 (ignoring the one match), and set output str_marked='>>)<><', showing the matched parentheses. Parentheses are set as matched both when they are matched by parentheses within str and when they are matched by parentheses reported by left_in_n_unmat_open and right_in_n_unmat_close.

Complete the module so that the testbench reports zero errors.

The module description must be recursive and describe tree-like hardware.

 $\leftarrow \ \rightarrow \ \text{Homework} \ 3$

] Set wn to the smallest correct value in the recursive instantiations.

Make sure the module is synthesizable using command genus -files syn.tcl.

Hint: Consider writing str_marked only in the base (terminal) case of the recursion.

LSU EE 4755

Homework 4

Due: 8 Nov 2024

Student Expectations

To solve this assignment students are expected to avail themselves of references provided in class and on the Web site, such as for Verilog programming and synthesis examples, and to seek out any additional help and resources that might be needed. (Of course this doesn't mean asking someone else to solve it for you.) It is the students' responsibility to resolve frustrations and roadblocks quickly. (If you get stuck *just ask for help!*)

This assignment cannot be solved by blindly pasting together parts of past assignments. Solving the assignment is a multi-step learning process that takes effort, but one that also provides the satisfaction of progress and of developing skills and understanding.

Collaboration Rules

Each student is expected to complete his or her own assignment. It is okay to work with other students and to ask questions in order to get ideas on how to solve the problems or how to overcome some obstacle (be it a question of Verilog syntax, interpreting error messages, how a part of the problem might be solved, etc.) It is also acceptable to seek out digital design resources for help on Verilog, digital design, etc. It is okay to make use of AI LLM tools such as ChatGPT and Copilot to generate sample Verilog code. (Do not assume LLM output is correct. Treat LLM output the same way one might treat legal advice given by a lawyer character in a movie: it may sound impressive, but it can range from sage advice to utter nonsense.)

After availing oneself to these resources each student is expected to be able to complete the assignment alone. Test questions will be based on homework questions and the assumed time needed to complete the question will be for a student who had solved the homework assignment on which it was based.

Problems start on next page.

Problem 1: Appearing below is the base case from module pmatch_mark in the solution to Homework 3 Problem 2.

```
typedef enum logic [3:0]
  { Char_Blank = 0,
                         Char_Dot = 1,
    Char_{Open} = 2,
                         Char_Close = 3,
    Char_Open_Okay = 4, Char_Close_Okay = 5 } Char;
module pmatch mark
  \#( int n = 5, wn = \frac{clog2(n+1)}{}
   ( output logic [wn-1:0] left_out_n_unmat_close, right_out_n_unmat_open,
     output uwire [3:0] str_marked [0:n-1],
     input uwire [wn-1:0] left_in_n_unmat_open, right_in_n_unmat_close,
     input uwire [3:0] str [0:n-1] );
   if ( n == 1 ) begin
      assign left_out_n_unmat_close = str[0] == Char_Close;
      assign right_out_n_unmat_open = str[0] == Char_Open;
      assign str_marked[0] =
             str[0] == Char_Close && left_in_n_unmat_open ? Char_Close_Okay :
             str[0] == Char_Open && right_in_n_unmat_close ? Char_Open_Okay :
             str[0];
Show the hardware that will be inferred for the base case (n==1) shown above.
Show the hardware after optimization and | for the default value of wn.
```

In the optimized hardware do not show comparison units, instead show the individual gates performing the comparison, \Box optimizing for constant values. **Problem 2:** Appearing below are three variations on a module that will set its output to either the input value, or a maximum value if the input is larger. The module will always be instantiated with wl < wn. All of them are functionally equivalent, but were synthesized to different costs (by Genus 23.12-s086.1 when similar code was used in the solution to Homework 3). Because they are functionally equivalent a perfect synthesis program would synthesize each to the same hardware (with equal costs).

```
module clamp_plan_a
```

```
#( int wl = 3, wn = 4 ) ( output uwire [wl-1:0] x, input uwire [wn-1:0] a );
localparam logic [wl-1:0] nl_max = ~(wl)'(0); // Sequence of wl 1s.
assign x = a <= nl_max ? a : nl_max;
endmodule
```

```
module clamp_plan_b
  #( int wl = 3, wn = 4 ) ( output uwire [wl-1:0] x, input uwire [wn-1:0] a );
   localparam logic [wl-1:0] nl_max = ~(wl)'(0); // Sequence of wl 1s.
   assign x = a < nl_max ? a : nl_max;
endmodule</pre>
```

```
module clamp_plan_c
  #( int wl = 3, wn = 4 ) ( output uwire [wl-1:0] x, input uwire [wn-1:0] a );
  localparam logic [wl-1:0] nl_max = ~(wl)'(0); // Sequence of wl 1s.
  assign x = !a[wn-1:wl] ? a : nl_max;
endmodule
```

Show the optimized hardware for the low-cost version(s).

Find the simple-model cost of each after optimization. The costs should be in terms of wn and wl.

Find the simple-model delay of each after optimization. The delays should be \Box in terms of wn and wl.

Problem 3: Appearing on the next page is a simplified solution to Homework 3, Problem 2. In this module the number of bits in the connections carrying parentheses counts is hardcoded to 8. Though the hardware is correct for n < 256 it is more costly and slower than it needs to be. But for this problem it's good enough.

Show the Homework 3, Problem 2 hardware that will be inferred for this module for n > 1 (the non-base case). That is, don't show the hardware computing left_out_n_unmat_close and right_out_n_unmat_open.

Show the inferred hardware at one level for n > 1.

Feel free to use abbreviations.

Don't show the Homework 3 Problem 1 hardware (the last always_comb).

Don't confuse elaboration-time computation with hardware.

For reference, the hardware for the Homework 3 Problem 1 part of this module is shown below.



```
module pmatch_mark_big #( int n = 5, wn = 8 )
   ( output logic [wn-1:0] left_out_n_unmat_close, right_out_n_unmat_open,
     output uwire [3:0] str_marked [0:n-1],
     input uwire [wn-1:0] left_in_n_unmat_open, right_in_n_unmat_close,
     input uwire [3:0] str [0:n-1] );
   if (n == 1) begin
      assign left_out_n_unmat_close = str[0] == Char_Close;
      assign right_out_n_unmat_open = str[0] == Char_Open;
      assign str_marked[0] =
             str[0] == Char_Close && left_in_n_unmat_open ? Char_Close_Okay :
             str[0] == Char_Open && right_in_n_unmat_close ? Char_Open_Okay : str[0];
   end else begin
      localparam int n_left = n/2, n_right = n - n_left;
      localparam int wl = 8,
                                     wr = 8; // Note: this is wasteful.
      uwire [wl-1:0] lt_close, lt_open;
      uwire [wr-1:0] rt_close, rt_open;
      logic [wl-1:0] lt_matched_op, lt_matched_cl;
      logic [wr-1:0] rt_matched_op, rt_matched_cl;
      pmatch_mark_big #(n_left,wl) plt // Recursive Instantiation
        ( lt_close, lt_open, str_marked[0:n_left-1],
          lt_matched_cl, lt_matched_op, str[0:n_left-1] );
      pmatch_mark_big #(n_right,wr) prt // Recursive Instantiation
        ( rt_close, rt_open, str_marked[n_left:n-1],
          rt_matched_cl, rt_matched_op, str[n_left:n-1] );
      always_comb begin
         logic signed [wn-1:0] more_op, more_cl;
         lt_matched_cl = left_in_n_unmat_open;
         rt_matched_op = right_in_n_unmat_close;
         more_op = left_in_n_unmat_open - lt_close;
         rt_matched_cl = more_op < 0 ? lt_open : more_op + lt_open;</pre>
         more_cl = right_in_n_unmat_close - rt_open;
         lt_matched_op = more_cl < 0 ? rt_close : more_cl + rt_close;</pre>
     end
      always_comb begin
                                 // Same as Homework 3 Problem 1
         logic signed [wn-1:0] delta;
         delta = lt_open - rt_close;
         left_out_n_unmat_close = delta >= 0 ? lt_close : lt_close - delta;
         right_out_n_unmat_open = delta < 0 ? rt_open : rt_open + delta;</pre>
      end
   end
endmodule
```

LSU EE 4755 Homework 5 Due: 18 Nov 2024 (evening)

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2024/hw05.v.html.

Student Expectations

To solve this assignment students are expected to avail themselves of references provided in class and on the Web site, such as for Verilog programming and synthesis examples, and to seek out any additional help and resources that might be needed. (Of course this doesn't mean asking someone else to solve it for you.) It is the students' responsibility to resolve frustrations and roadblocks quickly. (If you get stuck *just ask for help!*)

This assignment cannot be solved by blindly pasting together parts of past assignments. Solving the assignment is a multi-step learning process that takes effort, but one that also provides the satisfaction of progress and of developing skills and understanding.

Collaboration Rules

Each student is expected to complete his or her own assignment. It is okay to work with other students and to ask questions in order to get ideas on how to solve the problems or how to overcome some obstacle (be it a question of Verilog syntax, interpreting error messages, how a part of the problem might be solved, etc.) It is also acceptable to seek out digital design resources for help on Verilog, digital design, etc. It is okay to make use of AI LLM tools such as ChatGPT and Copilot to generate sample Verilog code. (Do not assume LLM output is correct. Treat LLM output the same way one might treat legal advice given by a lawyer character in a movie: it may sound impressive, but it can range from sage advice to utter nonsense.)

After availing oneself to these resources each student is expected to be able to complete the assignment alone. Test questions will be based on homework questions and the assumed time needed to complete the question will be for a student who had solved the homework assignment on which it was based.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account (if somehow necessary at this point), copy the assignment, and run the Verilog simulator on the unmodified homework file, hw05.v. Do this early enough so that minor problems (*e.g.*, password doesn't work) are minor problems.

Homework Overview

The module in this assignment, dot_seq_2, computes a dot product of two vectors, a and b, each of length n, where n is even (and greater than zero). At each cycle two elements of a and b arrive, so it takes n/2 cycles for the complete vectors to arrive. The connections to dot_seq_2 are:

```
module dot_seq_2 #( int w = 5, wi = 4 )
  ( output logic [w-1:0] dp,
    output logic [wi-1:0] first_id, last_id,
    input uwire [w-1:0] a[2], b[2],
    input uwire [wi-1:0] in_id,
    input uwire reset, first, last,
    input uwire clk );
```

Each element of input vector **a** and **b** is **w** bits. Inputs **a** and **b** carry the first two elements of each vector when input first=1. At each subsequent cycle **a** and **b** will carry two more elements of the vector until reaching a cycle where last=1, in which case **a** and **b** carry the last two elements of each vector. (See the testbench section for examples.) If first=1 and last=1 in the same cycle

then the vectors are just of length 2. There is no upper bound on the vector length. Some time after last=1 output dp is to be set to the dot product of the vectors.

In the unmodified assignment dp is set to the correct value in the same cycle that last=1. In a correct solution dp should be set three cycles later to limit the critical path (see the problem description).

Input in_id is a wi-bit ID number which is used to identify the beginning and end of the vector. Outputs first_id and last_id are each wi-bit ID numbers. In a correctly solved assignment first_id is the ID of the beginning of the vector whose dot product appears on dp and last_id is the ID appearing at the end of that vector. In the unmodified assignment last_id is set to the correct value (though along with dp it is set too soon).

When input reset=1 any in-progress dot-product computation is abandoned that outputs first_id and last_id are set to zero.

Testbench

To compile your code and run the testbench press [F9] in an Emacs buffer in a properly set up account. The testbench will apply inputs to dot_seq_2 and report on the results. Unlike other assignments, only one module instantiation will be tested.

The testbench will show a trace for at least the first 20 cycles, with additional trace output shown before errors. The trace lines from a correctly solved assignment appear below.

2 _F_ ID a8	3 A 01,01	B 01,10	exp: :	fid OO	lid 00	dp 00	MOD: FID 00	LID 00	DP xx
3 ID aa	a A 01,01	B 01,10	exp: :	fid OO	lid 00	dp 00	MOD: FID 00	LID 00	DP xx
4 ID ad	d A 01,01	B 01,10	exp: :	fid OO	lid 00	dp 00	MOD: FID 00	LID 00	DP xx
5 ID at	f A 01,01	B 01,10	exp: :	fid OO	lid 00	dp 00	MOD: FID 00	LID 00	DP xx
6L ID b:	1 A 01,01	B 01,10	exp: :	fid a8	lid b1	dp 55	MOD: FID 00	LID 00	DP xx
7 ID b3	3 A 01,01	B 01,10	exp: :	fid a8	lid b1	dp 55	MOD: FID 00	LID 00	DP xx
8 _F_ ID b	5 A 01,01	B 01,10	exp: :	fid a8	lid b1	dp 55	MOD: FID 00	LID 00	DP xx
9 ID b8	3 A 01,01	B 01,10	exp: :	fid a8	lid b1	dp 55	MOD: FID a8	LID b1	DP 55
LO ID b9	9 A 01,01	B 01,10	exp: :	fid a8	lid b1	dp 55	MOD: FID a8	LID b1	DP 55
l1L ID ba	a A 01,01	B 01,10	exp: :	fid b5	lid ba	dp 44	MOD: FID a8	LID b1	DP 55
l2 _FL ID bo	c A 01,01	B 01,10	exp: :	fid bc	lid bc	dp 11	MOD: FID a8	LID b1	DP 55
13 ID bo	d A 01,01	B 01,10	exp: :	fid bc	lid bc	dp 11	MOD: FID a8	LID b1	DP 55
14 ID c0	O A 01,01	B 01,10	exp: :	fid bc	lid bc	dp 11	MOD: FID b5	LID ba	DP 44
15 ID c3	3 A 01,01	B 01,10	exp: :	fid bc	lid bc	dp 11	MOD: FID bc	LID bc	DP 11
16 _F_ ID c4	4 A 01,01	B 01,10	exp: :	fid bc	lid bc	dp 11	MOD: FID bc	LID bc	DP 11
l7 ID c7	7 A 01,01	B 01,10	exp: :	fid bc	lid bc	dp 11	MOD: FID bc	LID bc	DP 11
18 ID ca	a A 01,01	B 01,10	exp: :	fid bc	lid bc	dp 11	MOD: FID bc	LID bc	DP 11
19 ID co	c A 01,01	B 01,10	exp: :	fid bc	lid bc	dp 11	MOD: FID bc	LID bc	DP 11

Trace lines start with a cycle number, in the sample above they go from 2 to 19 as of this writing. That is followed by three characters that show the state of the reset, first, and last inputs (in that order). In cycle 2 first=1 and the other two are zero. In cycle 12 first=1 and last=1. In the sample above reset is always 0.

Upper-case labels, such as ID and FID are used for module inputs and outputs. Lower-case labels, such as lid and dp are used to show what the testbench expects to find at the outputs (though the expectation can be for several cycles later). Label exp: is an abbreviation for expected outputs, and label MOD: indicates module outputs. (A reminder of what the lower- and upper-case labels signify.)

Each a and b input has two values. Both values appear next to A and B, shown in hexadecimal. In the first tests the a and b vectors are set to make it easy to debug problems: each component of vector a is 1. The even components of b are 1 and the odd components of b are set to $16_{10} = 10_{16}$.

Consider the trace for cycle 9. The dp output is 55 and the IDs are a8 (first) and b1 (last). The vectors started arriving in cycle 2 (note the matching a8 on the module input, labeled ID), and the last pair of elements arrived at cycle 6. Though the vector finished arriving at cycle 6, its dot product did not appear at the module output until cycle 9. Also consider cycle 8. A new vector starts arriving, as one can tell by the first=1 signal. The newly arriving vector does not interfere with the computation of the vector that finished arriving in cycle 6. Dot products for both will be computed.

The testbench will print a summary of results at the end, for the correct solution:

```
Done with 10000 tests. 0 dp errs ( 9718 correct )
Done with 10000 tests. 0 FID errs, 0 LID errs.
Done with 10000 tests. Correct 9718, avg latency 3.0 cyc Okay
```

The first line above indicates that there were zero errors with the dp output. A total of 10000 vectors were offered to the module and the module finished 9718 of them. The 10000 - 9718 = 282 other vectors were interrupted by the reset signal. In the second line FID errs indicates how many first_id outputs were incorrect, the same for LID errs. The last line indicates the average number of cycles to compute a dot product. In this assignment that's expected to be an integer, and equal to 3.

When there are errors the trace indicates which outputs are wrong by changing labels FID, LID, and DP to ERR if the respective output value is incorrect. The expected correct values of first_ID and last_ID are based on the dp output. For example, if first_ID and last_ID are changed for a new vector but dp shows the dot product of the previous vector, then the values of first_ID and last_ID and last_ID and last_ID and so FID and LID will show ERR.

If the dp value is correct but arrives in less than 3 cycles an error message will be printed. Also, the DP label will be changed to EY (early) for a correct dot product value that appears earlier than 3 cycles after last arrived.

Note that the exp (lower case) labels show values that are expected now or in the future. For example, in cycle 6 below the dp label shows a 55 based on the arrival of the last signal. However, that dp value should not be seen at the outputs until 3 cycles later.

Also additional detail is provided in the first line following an error. Consider the output from the unmodified assignment:

2 _F_ ID a8 A 01,01 B 01,10 exp: fid 00 lid OO dp 00 MOD: FID 00 LID 00 EY 11 lid OO 3 ___ ID aa A 01,01 B 01,10 exp: fid 00 dp 00 MOD: FID 00 LID 00 DP 22 4 ____ ID ad A 01,01 B 01,10 exp: fid 00 lid OO dp 00 MOD: FID 00 LID 00 DP 33 5 ___ ID af A 01,01 B 01,10 exp: fid 00 lid 00 dp 00 MOD: FID 00 LID 00 DP 44 6 __L ID b1 A 01,01 B 01,10 exp: fid a8 lid b1 dp 55 MOD: ERR 00 LID b1 EY 55 Error first ID: 0 != a8 (correct) Error dp timing: latency 0 cyc < 3 cyc (minimum) 7 ___ ID b3 A 01,01 B 01,10 exp: fid a8 lid b1 dp 55 MOD: FID 00 LID b1 ER 66 Error dp: 66 != 55 (correct)

At cycle 6 output dp is set to the correct value, 55 (see the dp item) as is the LID, but since dot product arrives early the label is EY rather than DP. Also, the first_id output is incorrect, 0, so it is labeled ERR in the trace and the correct value is shown, a8. At cycle 7 the DP output is incorrect, it should have stayed at 55.

Helpful Examples

A pipelined execution unit was the subject of 2016 Homework 6. Other than the need to do

floating-point computation, the 2016 Homework 6 pipeline was simpler than the one in this assignment. Another pipelined calculation (something to be covered in class on on Friday 15 November 2024) is the subject of 2021 Homework 6. Past assignments and their solutions are linked to the assignments and exams page.

Problem 1: In the unsolved assignment dot_seq_2 computes the correct dot products, but does not accompany those with the correct first_id value, and the synthesized module would have a longer critical path then desired. Complete the module so that first_id is set to the correct ID and meeting the following timing requirements:

Don't perform any computation on values arriving at inputs. Instead, write them to registers and start computation in the next cycle.

The critical path can include at most one arithmetic operation on the vector components. For example, don't compute a[0]*b[0]+a[1]*b[1] because that operation has a critical path of 2 operations: a multiply and add. Instead compute the products on one cycle and the sum in another.

The correct dp should be available three cycles after the <code>last=1</code>.

Once the dp, first_id, and last_id outputs are set they should remain unchanged until either the reset is asserted or until the next dot product is ready.

The module must be synthesizable. Verify with the command genus -files syn.tcl.

LSU EE 4755

Homework 6

Due: 1 Dec 2024

Student Expectations

To solve this assignment students are expected to avail themselves of references provided in class and on the Web site, such as for Verilog programming and synthesis examples, and to seek out any additional help and resources that might be needed. (Of course this doesn't mean asking someone else to solve it for you.) It is each student's duty to himself or herself to resolve frustrations and roadblocks quickly. (If you get stuck *just ask for help!*)

This assignment cannot be solved by blindly pasting together parts of past assignments. Solving the assignment is a multi-step learning process that takes effort, but one that also provides the satisfaction of progress and of developing skills and understanding.

Collaboration Rules

Each student is expected to complete his or her own assignment. It is okay to work with other students and to ask questions in order to get ideas on how to solve the problems or how to overcome some obstacle (be it a question of Verilog syntax, interpreting error messages, how a part of the problem might be solved, etc.) It is also acceptable to seek out digital design resources for help on Verilog, digital design, etc. It is okay to make use of AI LLM tools such as ChatGPT and Copilot to generate sample Verilog code. (Do not assume LLM output is correct. Treat LLM output the same way one might treat legal advice given by a lawyer character in a movie: it may sound impressive, but it can range from sage advice to utter nonsense.)

After availing oneself to these resources each student is expected to be able to complete the assignment alone. Test questions will be based on homework questions and the assumed time needed to complete the question will be for a student who had solved the homework assignment on which it was based.

Problems start on next page.

Problem 1: Show the hardware that will be synthesized for the posted solution to Homework 5. The solution (with fewer comments than the posted version) is shown below.

```
module dot_seq_2 #( int w = 5, wi = 4 )
   ( output logic [w-1:0] dp,
                                        output logic [wi-1:0] first_id, last_id,
     input uwire [w-1:0] a[2], b[2], input uwire [wi-1:0] in_id,
     input uwire reset, first, last, input uwire clk );
   logic [w-1:0] pl_a[1:1][2], pl_b[1:1][2]; // Arriving vector elements.
                                         // Vector products.
   logic [w-1:0] pl_prod[2:2][2];
   logic [w-1:0] pl_sum[3:3];
                                               // Dot prod of 2-element segment.
   logic [wi-1:0] pl_id[1:3];
                                               // ID.
                                               // The first and last signals.
   logic [1:0] pl_fl[1:3];
   logic [wi-1:0] acc_id;
   logic [w-1:0] acc_sum;
   always_ff @( posedge clk ) begin
      /// Stage 0
      pl_a[1] <= a; // This copies both elements of a.</pre>
      pl_b[1] <= b;
      pl_id[1] <= in_id;</pre>
      pl_fl[1] <= reset ? 2'b0 : {last,first};</pre>
      /// Stage 1
      for ( int i=0; i<2; i++ ) pl_prod[2][i] <= pl_a[1][i] * pl_b[1][i];</pre>
      pl_id[2] <= pl_id[1];</pre>
      pl_f1[2] <= reset ? 2'd0 : pl_f1[1];</pre>
      /// Stage 2
      pl_sum[3] <= pl_prod[2][0] + pl_prod[2][1];</pre>
      pl_id[3] <= pl_id[2];</pre>
      pl_f1[3] <= reset ? 2'h0 : pl_f1[2];
      /// Stage 3
      begin
         automatic logic s3_first = pl_f1[3][0]; // For readability.
         automatic logic s3_last = pl_fl[3][1]; // For readability.
         automatic logic [w-1:0] s3_sum = s3_first ? pl_sum[3] : pl_sum[3] + acc_sum;
         acc_sum <= s3_sum;</pre>
         if (reset ) begin
            first_id <= 0;</pre>
            last_id <= 0;</pre>
         end else begin
            if ( s3_first ) acc_id <= pl_id[3];</pre>
            if ( s3_last ) begin
               first_id <= s3_first ? pl_id[3] : acc_id;</pre>
               last_id <= pl_id[3];</pre>
               dp <= s3_sum;
            end
         end
      end
   end
```

endmodule

Problem 2: Solve 2023 Final Exam Problem 2, which asks for a cost and delay analysis of a word count module.
2 Fall 2023

LSU EE 4755

Homework 1 Due: 7 September 2023

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2023/hw01.v.html.

Collaboration Rules

Each student is expected to complete his or her own assignment. It is okay to work with other students and to ask questions in order to get ideas on how to solve the problems or how to overcome some obstacle (be it a question of Verilog syntax, interpreting error messages, how a part of the problem might be solved, etc.) It is also acceptable to seek out digital design resources for help on Verilog, digital design, etc. It is okay to make use of AI LLM tools such as ChatGPT and Copilot to generate sample Verilog code. (Do not assume LLM output is correct. Treat LLM output the same way one might treat legal advice given by a lawyer character in a movie: it may sound impressive, but it can range from sage advice to utter nonsense.)

After availing oneself to these resources each student is expected to be able to complete the assignment alone. Test questions will be based on homework questions and the assumed time needed to complete the question will be for a student who had solved the homework assignment on which it was based.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account, copy the assignment, and run the Verilog simulator on the unmodified homework file, hw01.v. Do this early enough so that minor problems (*e.g.*, password doesn't work) are minor problems.

Testbench

To compile your code and run the testbench press [F9] in an Emacs buffer in a properly set up account. The testbench will test 3 modules, minmax2p1 (n = 2), minmax4 (n = 4), and minmax8 (n = 8). Each module will be tested on 100 inputs. If a module's output on a particular input is incorrect, a message will be printed showing the incorrect and correct output. This output will only be shown for the first few errors, but a tally will be shown near the end counting all errors.

In an unmodified assignment the testbench will generate output that includes the following near the end:

```
z != 8107 (correct)
Error n=8
          \max
                  z !=
Error n=8
          min
                        907 (correct)
Error n=8
                  z != 8156 (correct)
          max
                  z != 243 (correct)
Error n=8
          min
                  z != 6424 (correct)
Error n=8 max
Done with n=8, tests, 100 min 100 max errors found.
xmsim: *W,RNQUIE: Simulation is complete.
xcelium> exit
Total number of errors: 600
```

The z in the output above means that the minmax8 outputs (both min and max) were set to z, meaning the output was not connected (z is often used to indicate high impedance). The output of the testbench for a correctly completed assignment is:

Done with n=2, tests, 0 min 0 max errors found. Done with n=4, tests, 0 min 0 max errors found. Done with n=8, tests, 0 min 0 max errors found. xmsim: *W,RNQUIE: Simulation is complete. xcelium> exit Total number of errors: 0

Helpful Examples

A good past assignment to look at is 2017 Homework 1. A question very similar to Problem 1 was asked in 2018 Homework 1 Problem 1. So, do not look at 2018 Homework 1 until after you have made a very serious attempt at Problem 1.

Problem 1: Module minmax2, shown below, sets output min to the smaller of its two inputs a0 and a1, and sets max to the larger of those two inputs:

```
module minmax2
#( int w = 10 )
   ( output uwire [w-1:0] min, max, input uwire [w-1:0] a0, a1 );
   assign { min, max } = a0 <= a1 ? { a0, a1 } : { a1, a0 };
endmodule</pre>
```

Notice that minmax2 uses a continuous assignment statement. Complete module minmax2p1 so that it does the same thing as minmax2, but without a continuous assignment and without procedural code. Instead instantiate compare_lt and mux2 modules (shown below). Follow other guidelines and requirements shown in the checkboxes in the Verilog file.

```
module compare_lt
  #( int w = 31 )
  ( output uwire lt, input uwire [w-1:0] a0, a1 );
  // Set lt to 0 if a1 < a0, set lt to 1 otherwise.
  assign lt = a0 <= a1;
endmodule

module mux2
  #( int w = 3 )
  ( output uwire [w-1:0] x, input uwire s, input uwire [w-1:0] a0, a1 );
  assign x = s ? a1 : a0;
endmodule</pre>
```

There is another problem on the next page.

Problem 2: Modules minmax4 and minmax8 each have outputs min and max, which are to be set to the smallest and largest values of their input. Input a to minmax4 is a 4-element array of w-bit unsigned integers, and input a to minmax8 is an 8-element array. Complete these modules as described below.

For this problem use modules minmax2, min2, and max2. Module min2, as one might guess, sets its output to the smaller of its two inputs. Module max2 is similar. Assume that the combined cost of a min2 and max2 module is greater than one minmax2 (but less than the cost of two minmax2 modules).

```
( output uwire [w-1:0] max, input uwire [w-1:0] a0, a1 );
assign max = a0 < a1 ? a1 : a0;
endmodule
```

(a) Complete module minmax4 using instantiations of modules minmax2, and possibly min2 and max2 as needed. Do not use assign statements or procedural code. Follow other guidelines shown in the checklist in the code. Pay attention to the relative cost of the min2, max2, and minmax2 modules.

(b) Complete module minmax8 using instantiations of modules minmax4, and possibly minmax2, min2, and max2 as needed. Do not use assign statements or procedural code. Follow other guidelines shown in the checklist in the code. Pay attention to the relative cost of the min2, max2, and minmax2 modules.

The code must by synthesizable. To synthesize your code issue the command genus -files syn.tcl. If there are no errors, running this command will generate output that includes like the following:

Module Name	Area	Delay	Delay
		Actual	Target
minmax2p1_w8	15086	2.191	10.000 ns
minmax2_w8	15086	2.191	10.000 ns
minmax4_w8	49094	4.412	10.000 ns
minmax8_w8	117111	6.632	10.000 ns
minmax2p1_w8_1	19678	1.029	0.100 ns
minmax2_w8_1	19678	1.029	0.100 ns
minmax4_w8_1	75084	1.496	0.100 ns
minmax8_w8_1	214774	2.567	0.100 ns

LSU EE 4755

Homework 2 Due: 29 September 2023

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2023/hw02.v.html.

Collaboration Rules

Each student is expected to complete his or her own assignment. It is okay to work with other students and to ask questions in order to get ideas on how to solve the problems or how to overcome some obstacle (be it a question of Verilog syntax, interpreting error messages, how a part of the problem might be solved, etc.) It is also acceptable to seek out digital design resources for help on Verilog, digital design, etc. It is okay to make use of AI LLM tools such as ChatGPT and Copilot to generate sample Verilog code. (Do not assume LLM output is correct. Treat LLM output the same way one might treat legal advice given by a lawyer character in a movie: it may sound impressive, but it can range from sage advice to utter nonsense.)

After availing oneself to these resources each student is expected to be able to complete the assignment alone. Test questions will be based on homework questions and the assumed time needed to complete the question will be for a student who had solved the homework assignment on which it was based.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account (if necessary), copy the assignment, and run the Verilog simulator on the unmodified homework file, hw02.v. Do this early enough so that minor problems (*e.g.*, password doesn't work) are minor problems.

Homework Overview

In this assignment modules will be completed to compute the expression (1 - b/c)/a. For example, if the inputs to one of these modules are a = 10, b = 20, and c = 80, the output would be (1 - 20/80)/10 = 0.075. The inputs are unsigned integers, but the output is floating point. Module parameters provide the widths of the integer inputs and the significand and exponent size of the floating-point output.

In Problem 1 module $comp_p1$ is to be completed so that the calculation is foolishly done in the order given by the expression, (1 - b/c)/a. The floating point conversion and calculation are to be done using Chipware modules. Solving it requires a straightforward application of Verilog techniques for instantiating modules and wiring them together. It also requires an understanding of when and how to convert numbers from integer to floating-point representations.

In Problem 2 module comp_p2 is to be completed so that the expression is computed much more efficiently (not foolishly as in Problem 1). The expression (1 - b/c)/a is to be transformed so that some of the computation can be done by integer arithmetic and in a way that requires less computation precision.

In a correctly completed assignment the testbench will show that module comp_p2 has greater accuracy, and the synthesis program will show that module comp_p2 is both faster and less expensive than comp_p1. That is, by transforming (1 - b/c)/a all factors of interest improve, there's no cost/ performance tradeoff to balance! That's why the method used by comp_p1 is foolish.

Testbench

To compile your code and run the testbench press [F9] in an Emacs buffer in a properly set up account. The testbench will apply inputs to several instantiation of modules comp_p1 and comp_p2. The instantiations differ on the number of bits used for the integer inputs and the format of the floating-point output. The instantiation parameters are shown at the end of the testbench along with a summary of the errors for that module. The output for an unmodified assignment is:

```
Total comp_p1 exp= 7, sig= 6, w= 4:
                                      9258 errors. Err bits: avg
                                                                    8.83, max
                                                                               18
Total comp_p1 exp= 7, sig= 8, w= 4:
                                                                   10.60, max
                                                                               20
                                      9207 errors. Err bits: avg
Total comp_p1 exp= 8, sig=10, w= 5:
                                      9533 errors. Err bits: avg
                                                                   13.60, max
                                                                               25
Total comp_p1 exp= 8, sig=10, w=10:
                                      9918 errors. Err bits: avg
                                                                   18.49, max
                                                                               38
                                                                   20.38, max
Total comp_p1 exp= 8, sig=12, w=10:
                                      9893 errors. Err bits: avg
                                                                               39
                                                                    9.06, max
Total comp_p2 exp= 7, sig= 6, w= 4:
                                      9228 errors. Err bits: avg
                                                                               18
Total comp_p2 exp= 7, sig= 8, w= 4:
                                      9268 errors. Err bits: avg
                                                                   10.91, max
                                                                               20
Total comp_p2 exp= 8, sig=10, w= 5:
                                                                   14.04, max
                                      9529 errors. Err bits: avg
                                                                               25
Total comp_p2 exp= 8, sig=10, w=10:
                                      9906 errors. Err bits: avg
                                                                   19.11, max
                                                                               39
Total comp_p2 exp= 8, sig=12, w=10:
                                      9903 errors. Err bits: avg
                                                                   21.15, max
                                                                               41
Total number of errors: 95643
```

The text exp=7 shows the value of parameter w_exp , etc. To add or change instantiation parameters search for the place where variable pset is assigned and edit the initialization of pset (and change npsets if needed):

The testbench will report on the correctness and accuracy of the output. The output of a module does not need to exactly match a correct output to be considered correct, it just needs to be close enough. Module comp_p2 is expected to be more accurate, so an output of comp_p2 can be considered wrong even though the same output of comp_p2 is considered correct.

The difference between the expected output and the output provided by your module is measured in error bits (EB). Zero error bits means the output exactly matches. When the exponents of the module and expected output are the same the EB is the size (in bits) of a number that would have to be added to one significand (treating it as an integer) to make it equal to the other. For example, an EB of 1 means that a 1-bit number can be added to one significand to make it equal to the other. An EB of 2 means that a two-bit number can be added. If the exponents differ by more than one then the exponent difference is the EB. See routine $conv::err_bits$ for details.

For Problem 2 an output with an EB less than 2 is considered correct. For Problem 1 a per-input tolerance is computed and is used to determine if the output is correct. The testbench keeps track of the average and maximum EB for each module, and these are shown at the end of execution along with an error count. The output for a correct solution is:

Total	comp_p1	exp=	7,	sig= 6,	w= 4:	0	errors.	Err	bits:	avg	0.37,	max	4
Total	comp_p1	exp=	7,	sig= 8,	w= 4:	0	errors.	Err	bits:	avg	0.40,	max	4
Total	comp_p1	exp=	8,	sig=10,	w= 5:	0	errors.	Err	bits:	avg	0.48,	max	5
Total	comp_p1	exp=	8,	sig=10,	w=10:	0	errors.	Err	bits:	avg	0.71,	max	10
Total	comp_p1	exp=	8,	sig=12,	w=10:	0	errors.	Err	bits:	avg	0.71,	max	9
Total	$comp_p2$	exp=	7,	sig= 6,	w= 4:	0	errors.	Err	bits:	avg	0.00,	max	0
Total	comp_p2	exp=	7,	sig= 8,	w= 4:	0	errors.	Err	bits:	avg	0.00,	max	0
Total	comp_p2	exp=	8,	sig=10,	w= 5:	0	errors.	Err	bits:	avg	0.00,	max	0
Total	comp_p2	exp=	8,	sig=10,	w=10:	0	errors.	Err	bits:	avg	0.07,	max	1
Total	comp_p2	exp=	8,	sig=12,	w=10:	0	errors.	Err	bits:	avg	0.04,	max	1

Total number of errors: 0

Notice that both modules have zero errors, but that instances of comp_p2 are more accurate (lower EB). The maximum error bits occurred for comp_p1 instantiated with a significand width of 10 bits and an integer width of 10 bits. The average EB though is just 0.71, so those big 10-bit errors don't occur very often.

To help in debugging details of errors are shown. Here are the first two errors shown for comp_p1 with the unmodified code:

```
Error p1 #(7,6,4) a= 1 b=13 c= 1: Err bits 8 (tol 2)

Output 2.0000e+00 != -1.2000e+01 (correct).

Output 'h00 * 2^( 64-63) != 'h20 * 2^( 66-63) (correct)

Error p1 #(7,6,4) a= 5 b=10 c= 5: Err bits 11 (tol 2)

Output 6.0000e+00 != -1.9922e-01 (correct).

Output 'h20 * 2^( 65-63) != 'h26 * 2^( 60-63) (correct)
```

The first list of each error shows the instantiation size (7,6,4), inputs (a=1, b=13,c=1), the EB value, 8, and the tolerance, 2. The tolerance of 2 indicates that an EB of 2 or lower would have been considered correct, but alas the EB is 8. The next two lines (starting with Output) show the provided and correct output, in decimal (the first line) and in binary scientific notation (the second line). These lines show for the first error that the expected correct output is -12, but the provided output is 2. The second line shows the significand (in hex) and exponent of the provided and correct output.

Details are not shown for every incorrect output. Instead, details are shown if the EB exceeds the highest EB encountered for that module.

Helpful Examples

For this assignment Chipware modules are to be instantiated to perform floating-point computation and integer/floating-point conversion. See 2017 Homework 2 for examples of how to instantiate these modules to perform a computation and integer/floating-point conversion. In the 2017 assignment all FP numbers were IEEE single 32-bit format. But in this (2023) assignment the formats vary and so parameters must be used when instantiating the Chipware modules to specify the exponent and significand length. In 2021 Homework 2 Chipware modules were instantiated with non-default exponent and significand lengths. Also see 2022 Homework 5. That assignment uses both combinational and sequential modules. (Sequential material has not yet been covered.) See ms_comb in 2022 Homework 5 for a straightforward connection of FP modules (but without format conversion). **Problem 1:** Module comp_p1 has three w_int-bit integer inputs, a, b, and c, and a wfp-bit floating-point output, h. The module has three parameters, w_int, w_exp, and w_sig. (A fourth parameter, wfp is set to $1+w_exp+w_sig$ and its value should not be changed.) Complete module comp_p1 so that h is set to the value of (1 - b/c)/a. The module inputs, a, b, and c are unsigned integers but the calculation must be done in floating-point in this problem. Output h is a floating-point number with a w_exp-bit exponent, a w_sig-bit significand, and one sign bit. The format of h is the same as the format used by the Chipware modules.

In the unmodified code $comp_p1$ computes h = a + 1, which is clearly wrong but it does show a quick example of how to convert a to floating point, how to get a FP constant, and how to instantiate a Chipware adder.

Complete comp_p1 so that it foolishly computes h based on the calculation order in the expression $\frac{1-b/c}{a}$. (The foolishness is avoided in Problem 2.) That is, first compute $x_1 = b/c$, then compute $x_2 = 1 - x_1$, and finally compute $h = x_2/a$.

Use Chipware modules for the floating-point arithmetic and for conversions between integer and floating-point representations. Pay attention to cost.

A correct solution should show zero errors, but the average bit error can be 0.5 and the maximum bit error can be larger than 5. Lower error rate and lower cost and lower delay will be possible in Problem 2.

Use Chipware modules for floating-point computation.

Use procedural or implicit structural code for any integer computation.

Pay attention to cost: The significand size of the floating-point units can be at most w_sig+1 bits. To achieve this one must provide parameter inputs to the Chipware modules.

Pay attention to cost: don't use more bits than are needed.

The modules must be synthesizable.

To synthesize your code issue the command genus -files syn.tcl. Synthesis should take two or three minutes. If there are no errors, running this command will generate output that includes like the following:

Synthesizing at effort level "high"

Module Name	Area	Delay	Delay	Synth
		Actual	Target	Time
comp_p1_w4_w_exp7_w_sig6	183394	31.57	900.0 ns	66 s
comp_p2_w4_w_exp7_w_sig6	129109	18.07	900.0 ns	36 s

Problem 2: Expression $\frac{1-b/c}{a}$ might be easy for a human to read, but it does not describe the best way to compute the value with finite-precision computations on non-zero cost hardware. One place accuracy is lost is computing $1 - \frac{b}{c}$ when $b/c \approx 1$. Furthermore all computation must be done in floating-point. Fortunately it is easy to transform $\frac{1-b/c}{a}$ to eliminate the $1 - \frac{b}{c}$ calculation and also to put it in a form where some computation can be done using integer arithmetic. One possible way of transforming the expression is to multiply by 1. Not just any 1 of course, but $\frac{c}{c}$. A few further manipulations should bring it to a form that can be more easily computed.

Module comp_p2 has the same ports and parameters as comp_p1. Complete comp_p2 so that it computes $\frac{1-b/c}{a}$ much more efficiently, following the guidelines described above. When transforming the expression keep in mind that integer addition and subtraction is less costly than floating-point

subtraction and division (floating-point or integer) is much more costly (time and area) than other operations.

Module comp_p2 should use a mix of integer and floating-point computation. Pay attention to precision, especially for integer arithmetic where the result of a computation can require more bits than the operands. (If you don't remember try looking it up.)

The test bench applies a stricter test to the output of comp_p2, which affects the expected output for inputs in which $b\approx c.$

Use Chipware modules for floating-point computation.

Use procedural or implicit structural code for integer computation.

Pay attention to cost: The significand size of the floating-point units can be at most w_sig+1 bits. To achieve this one must provide parameter inputs to the Chipware modules.

Pay attention to cost: don't use more bits than are needed.

The modules must be synthesizable. (Use the same synthesis command as used in Problem 1.)

LSU EE 4755

Homework 3

Due: 13 October 2023

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2023/hw03.v.html.

Collaboration Rules

Each student is expected to complete his or her own assignment. It is okay to work with other students and to ask questions in order to get ideas on how to solve the problems or how to overcome some obstacle (be it a question of Verilog syntax, interpreting error messages, how a part of the problem might be solved, etc.) It is also acceptable to seek out digital design resources for help on Verilog, digital design, etc. It is okay to make use of AI LLM tools such as ChatGPT and Copilot to generate sample Verilog code. (Do not assume LLM output is correct. Treat LLM output the same way one might treat legal advice given by a lawyer character in a movie: it may sound impressive, but it can range from sage advice to utter nonsense.)

After availing oneself to these resources each student is expected to be able to complete the assignment alone. Test questions will be based on homework questions and the assumed time needed to complete the question will be for a student who had solved the homework assignment on which it was based.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account (if necessary), copy the assignment, and run the Verilog simulator on the unmodified homework file, hw03.v.

Homework Overview

As we probably know a *permutation* is a rearrangement of distinct objects. If there are *n* objects there are *n*! permutations, including the identity permutation (which leaves the objects in their original positions). For example, the three-letter sequence abc can be permuted 6 ways: abc, acb, bca, cab, cba. (In module perm input pdata_in is an unpermuted sequence and output pdata_out should be set to a permutation of the input.) There are many ways to specify which permutation we want. We could just say, I want permutation acb, meaning leave the first element unchanged and swap the next two. So permutation acb of xyz would be xzy. When specifying permutations this way it is more common to use digits, so rather than acb we would say permutation 021 of xyz. Here 021 indicates how we want things rearranged and xyz are the objects before being re-arranged and xzy are after the rearrangement.

Suppose we want to generate all permutations in, say, a loop. We might have a current permutation, 021, and would like to generate the next one, say 102 (or bac). One way of doing that is using a factorial number. (This was the subject of https://xkcd.com/2835.) A factorial number is a mixed-radix number. (In module perm input pnum_in and output pnum_out are both factorial numbers. In the testbench the factorial numbers are called indices.) In an n-digit factorial number digit 0 (the LSD) is radix 1, digit 1 is radix 2 (binary), digit 2 is radix 3, and so on, to digit n - 1. Digit 0, by the way, being radix 1, must always be zero. Digit 1 can be 0 or 1, digit 2 can be 0,1,2, etc. When all digits are zero the number specifies an identity permutation. Digit *i* of a factorial number specifies where to get the value to put in position *i* of the permuted sequence. To see examples of factorial numbers and the respective permutations look at the sample testbench outputs below.

With factorial numbers it's easy to compute the next permutation in a sequence: just add one. Start at the least significant digit. If there is a carry out (and there always is at the least significant digit) proceed to the next digit. Denote the value of digit i (radix i + 1) as $d_i \in [0, i]$. Adding a carry in to the digit yields $d_i + 1$. If $d_i + 1 \le i$ then that is the new value of d_i and the carry out propagation stops. Otherwise the new value of d_i is zero and proceed to digit i + 1.

Code for computing the next permutation is shown in module perm_behavioral. That module also shows how to apply a factorial number (pnum_in) to permute items in pdata_in and connect them to pdata_out.

Testbench

To compile your code and run the testbench press [F9] in an Emacs buffer in a properly set up account. The testbench will apply inputs to several instantiation of module perm. The instantiations differ on the number of items to permute, n, and the number of bits in each item, w. The testbench shows sample outputs and errors, and ends with a tally of errors for each instantiation. The output for an unmodified assignment includes:

```
Starting tests for w=8, n=3
Trace of permutation: 0 0 0 -> a b c
Error in next index: 0 0 0 -> 0 0 0 != 0 1 0 (correct)
Error in permutation: 0 1 0 -> a b c != a c b (correct)
Error in next index: 0 1 0 -> 0 1 0 != 1 0 0 (correct)
[snip]
Finished with n=10, 999 perm errors, 1000 next idx errors in 1000 tests.
```

End of tests n=3, 5 perm errors, 6 next idx errors for 6 tests. End of tests n=4, 23 perm errors, 24 next idx errors for 24 tests. End of tests n=8, 999 perm errors, 1000 next idx errors for 1000 tests. End of tests n=10, 999 perm errors, 1000 next idx errors for 1000 tests. xmsim: *W,RNQUIE: Simulation is complete.

In the unmodified assignment perm connects the permutation (pdata_out) output to the permutation input (pdata_in), which is wrong except for the identity permutation. That's why each module gets one permutation correct, as can be seen in the output above. (For example, for n = 3, 5 perm errors out of 3! = 6 tests.)

The testbench always shows the first few outputs of each instance. For a correct assignment the output would include:

```
Starting tests for w=8, n=3

Trace of permutation: 0 \ 0 \ -> a \ b \ c

Trace of permutation: 1 \ 0 \ -> b \ a \ c

Trace of permutation: 1 \ 1 \ 0 \ -> b \ c \ a

Trace of permutation: 2 \ 0 \ -> c \ a \ b

Trace of permutation: 2 \ 1 \ 0 \ -> c \ b \ a

Finished with n=3, 0 perm errors, 0 next idx errors in 6 tests.

Starting tests for w=7, n=4

Trace of permutation: 0 \ 0 \ 0 \ -> a \ b \ c \ d

Trace of permutation: 0 \ 1 \ 0 \ -> a \ b \ d \ c

Trace of permutation: 0 \ 1 \ 0 \ -> a \ c \ b \ d
```

For n = 3 the testbench sets pdata_in[0]='c', pdata_in[1]='b', and pdata_in[2]='a'. The module needs to work for any settings for pdata_in, but the testbench sets pdata_in to values in a,b,c,.. to make debugging easy.

Testbench output starting Trace of permutation shows the value of pnum_in (index, a factorial number) and pdata_out when pdata_out is correct. For the n = 3 module notice that all 6 permutations (permuted inputs) are shown, such as a b c. The sample above also shows the first few outputs of the n = 4 instance.

The digits of the permutation number are separated by spaces. The leftmost digit is (of course) the most significant, at position n-1. Being a permutation number, the least significant digit is always zero.

For each instance the first permutation is always identity (pnum_in=0), and the first 5 permutations are shown. For instances where $n! \leq 1000$ (or the value of max_tests) all permutations are tried. Otherwise, after showing 5 consecutive permutations a new random permutation is chosen. That can be seen below.

If there is an error the provided and correct outputs are shown. Here again is the output from the unmodified assignment:

```
Starting tests for w=8, n=3

Trace of permutation: 0 \ 0 \ 0 \ -> a \ b \ c

Error in next index: 0 \ 0 \ 0 \ -> 0 \ 0 \ 0 \ != \ 0 \ 1 \ 0 \ (correct)

Error in permutation: 0 \ 1 \ 0 \ -> a \ b \ c \ != \ a \ c \ (correct)

Error in next index: 0 \ 1 \ 0 \ -> 0 \ 1 \ 0 \ != \ 1 \ 0 \ (correct)
```

The first permutation output, a b c, is correct. The pnum_out value is wrong, that's shown in the line starting Error in next index. That line shows the value of pnum_in (the factorial number) to the left of the -> and the value of pdata_out to the right of ->. The correct value is shown to the right of !=. Similar information is shown for incorrect permutations.

Helpful Examples

An example that might help in computing pnum_out is from the class notes on generate statements. Module ripple_w_r recursively implements an adder. Pay attention to how bfa computes the LSB of the sum, and the recursive instance computes the remaining bits:

```
module ripple_w_r #( int w = 16 )
  ( output uwire [w-1:0] sum, output uwire cout,
    input uwire [w-1:0] a, b, input uwire cin);
  uwire c;
  // Instantiate a BFA to handle least-significant bit.
  //
  bfa bfa( sum[0], c, a[0], b[0], cin );
  if ( w == 1 )
    // If just one bit, we're done.
```

```
//
   assign cout = c;
else
   // Recursively instantiate this module to handle remaining bits.
   //
   ripple_w_r #(w-1) r(sum[w-1:1], cout, a[w-1:1], b[w-1:1], c);
endmodule
```

There's no need to use a BFA for this assignment. Use continuous assignments or procedural code to compute one digit of pnum_out.

In most examples of where we recursively describe a module we omit a particular bit (bit 0 in the ripple adder example above) in the connection to the recursive instance, or we have two recursive instances, each connected to half the inputs. The perm module is different because the digit to omit depends on the pdata_in. So, we need to use procedural code to compute an input to the recursive module and there are no good past assignment that do that. The closest is the Batcher merge module from 2018 Homework 5 where the odd and even elements of each of two the inputs were separated and recombined as inputs to two recursive instances:

```
module batcher merge \#( int n = 4, int w = 8 )
   ( output uwire [w-1:0] x[2*n], input uwire [w-1:0] a[n], b[n] );
   uwire [w-1:0] xlo[n], xhi[n];
   if (n == 1) begin
      assign xlo[0] = a[0];
      assign xhi[0] = b[0];
   end else begin
      localparam int nh = n/2;
      uwire [w-1:0] ae[nh], ao[nh], be[nh], bo[nh];
      for ( genvar i=0; i<nh; i++ )</pre>
        begin
           assign ae[i] = a[2*i];
           assign ao[i] = a[2*i+1];
           assign be[i] = b[2*i];
           assign bo[i] = b[2*i+1];
        end
      batcher_merge #(nh,w) mlo( xlo, ae, bo );
      batcher_merge #(nh,w) mhi( xhi, ao, be );
   end
   for ( genvar i=0; i<n; i++ )</pre>
     sort2 #(w) s2( x[2*i], x[2*i+1], xlo[i], xhi[i] );
endmodule
```

Problem 1: Module perm has two data inputs, pdata_in and pnum_in. Input pdata_in is an array of n items, each w bits wide, where n and w are module parameters. Input pnum_in is an n-element array of dw-bit digits, where dw is a parameter. Module perm has three outputs, pdata_out, pnum_out, and carry_out. Like pdata_in, output pdata_out is an n-element array of w-bit items, and like pnum_in, output pnum_out is an n-element array of dw-bit digits. Output carry_out is one bit.

Output pdata_out is to be set to a permutation (rearrangement) of the elements of pdata_in. Suppose pdata_in = $\{a,b,c\}$ (which means n = 3, and perhaps w = 8) and that the elements of pdata_in and pdata_out are ASCII characters. Then valid outputs could be pdata_out = $\{a,b,c\}$, pdata_out = $\{b,a,c\}$, etc. An invalid output would be pdata_out = $\{a,a,c\}$, it's invalid because a appears twice and b does not appear.

Input pnum_in, a factorial number, specifies how pdata_in should be permuted. A permutation is constructed iteratively, starting from the most-significant digit of pnum_in, which is pnum_in[n-1] and specifies where the value of pdata_out[n-1] should be drawn from. The Verilog code below (also part of the assignment file) shows how pdata_out is computed:

```
module perm_behavioral
```

```
#( int w = 8, n = 20, dw = $clog2(n) )
( output logic [w-1:0] pdata_out[n], output logic (dw-1:0] pnum_out[n],
    output logic carry_out,
    input uwire [w-1:0] pdata_in[n], input uwire [dw-1:0] pnum_in[n] );
always_comb begin
    pdata_out = pdata_in;
    for ( int i=n-1; i>0; i-- ) begin
        automatic logic [dw-1:0] pos = i-pnum_in[i];
        automatic logic [w-1:0] x = pdata_out[pos];
        for ( int j=pos; j<i; j++ ) pdata_out[j] = pdata_out[j+1];
        pdata_out[i] = x;
    end
end</pre>
```

Notice that pdata_out is written multiple times, each iteration of the i loop permanently writes pdata_out[i] but also changes some other elements.

(a) Add code to perm, including recursive instantiation, so that pdata_out is a permutation of pdata_in as specified by pnum_in. Module perm with parameter n>1 must recursively instantiate itself and the module must be synthesizable. Use command genus -files syn.tcl to synthesize.

(b) Add code to perm, including recursive instantiation, so that output pnum_out is the factorial number that follows pnum_in. The module must be synthesizable. As a reference the Verilog code below computes the next factorial number.

```
always_comb begin
  // Compute next factorial (permutation) number.
  carry_out = 1;
  for ( int i=0; i<n; i++ ) begin
    automatic int radix = i + 1;
    automatic logic [dw:0] next_val = pnum_in[i] + carry_out;
    if ( next_val < radix ) begin</pre>
```

```
pnum_out[i] = next_val;
    carry_out = 0;
    end else begin
        pnum_out[i] = 0;
        end
    end
end
```

LSU EE 4755

Homework 4

Due: 6 November 2023

Collaboration Rules

Each student is expected to complete his or her own assignment. It is okay to work with other students and to ask questions in order to get ideas on how to solve the problems or how to overcome some obstacle (be it a question of Verilog syntax, how a part of the problem might be solved, etc.) It is also acceptable to seek out digital design resources for help on Verilog, digital design, etc. It is okay to make use of AI LLM tools such as ChatGPT to answer these questions. Just don't trust the answers. (Do not assume LLM output is correct. Treat LLM output the same way one might treat legal advice given by a lawyer character in a movie: it may sound impressive, but it can range from sage advice to utter nonsense.)

After availing oneself to these resources each student is expected to be able to complete the assignment alone. Test questions will be based on homework questions and the assumed time needed to complete the question will be for a student who had solved the homework assignment on which it was based.

Helpful Examples

See the simple model slides for material on computing cost and delay, and also for a list of some sample problems. Also see 2022 Homework 3.

 $\leftarrow \rightarrow$ Fall 2023

Permutation Module

This assignment is based on the solution to Homework 3, the recursive permutation module perm, and the solution to Midterm Exam Problem 1, the inferred hardware for the permutation module. See Homework 3 for details on what the permutation module does. Appearing below is the Homework 3 solution with some comments removed. For the unabridged version visit https://www.ece.lsu.edu/koppel/v/2023/hw03-sol.v.html.

```
module perm
```

```
#( int w = 8, n = 20, wd = (100) )
 ( output uwire [w-1:0] pdata_out[n],
                                         output uwire [wd-1:0] pnum_out[n],
  output uwire carry_out,
  input uwire [w-1:0] pdata_in[n],
                                    input uwire [wd-1:0] pnum_in[n] );
if ( n == 1 ) begin
   assign pdata_out[0] = pdata_in[0];
   assign carry_out = 1;
   assign pnum_out[0] = 0;
 end else begin
   // Set pos to the position of the element to be moved.
   uwire [wd-1:0] pos = n - 1 - pnum_in[n-1];
   // Copy the element at position pos to position n-1 in the output.
    assign pdata_out[n-1] = pdata_in[pos];
   // Prepare an array of n-1 elements and set to ...
   // .. the elements of pdata_in except for the element at pos.
   uwire [w-1:0] prdata_in[n-1];
   for ( genvar i=0; i<n-1; i++ )</pre>
     assign prdata_in[i] = i < pos ? pdata_in[i] : pdata_in[i+1];</pre>
   // Recursively instantiate perm.
    uwire co;
    perm #(w,n-1,wd) rp( pdata_out[0:n-2], pnum_out[0:n-2], co,
                        prdata_in, pnum_in[0:n-2] );
   // Compute a tentative next value of digit n-1.
   uwire [wd-1:0] dnext = pnum_in[n-1] + co;
   // Determine whether there is a carry.
   assign carry_out = dnext >= n;
   // Set the next value of digit n-1 based on whether there is a carry.
   assign pnum_out[n-1] = carry_out ? 0 : dnext;
```

end

endmodule

Permutation Module Inferred Hardware

Midterm Exam Problem 1 asked for the inferred hardware for the perm module instantiated with n=4. The solution appears below on the left. For this assignment the inferred hardware for a non-specific value of n will be needed, that is shown on the right.



There's no need to squint, the diagrams appear again in larger size at the end of this assignment. Also, SVG source for these modules are at https://www.ece.lsu.edu/koppel/v/2023/mt-p1-sol.svg and https://www.ece.lsu.edu/koppel/v/2023/hw04-perm-gen.svg.

Problem 1: Compute the cost and delay of the following arithmetic hardware from the perm module. Assume that ripple units are used for addition, subtraction, and comparison.
(a) Compute the cost and delay of the hardware computing $pos = n - 1 - pnum_in[n-1]$ in terms of w_d , the value of parameter wd. Optimize for constants, including n.
Cost of hardware in terms of w_d . \Box Delay of hardware in terms of w_d .
Optimize for constants, don't confuse elaboration-time computation with computation hardware.
(b) Compute the cost and delay of the hardware computing $dnext = pnum_in[n-1] + co$ in terms of w_d , the value of parameter wd. Optimize for constants and for the size of co. Assume in this problem that pnum_in and co arrive at $t = 0$.
Cost of hardware in terms of w_d . \Box Delay of hardware in terms of w_d .
Optimize considering the size of co. Optimize for constants, don't confuse elaboration-time computation with computation hardware.
(c) Compute the cost and delay of the hardware described by these lines:
<pre>uwire [wd-1:0] dnext = pnum_in[n-1] + co; assign carry_out = dnext >= n;</pre>
Assume in this problem that co and pnum_in arrive at $t = 0$. The cost, of course, includes the cost of computing dnext in the previous part. The delay must be computed taking both lines into account.
Cost of hardware in terms of w_d . \Box Delay of co in terms of w_d .
Optimize considering the size of co. Optimize for constants, don't confuse elaboration-time computation with computation hardware.

There are more problems on the next page.

Problem 2: In this problem consider the multiplexors with inputs connecting to pdata_in. (In the diagram they are the multiplexors on the upper-left including the 2-input muxes the *n*-input mux.) Call these the pdata multiplexors. In the solutions to the parts below use w for the value of parameter w and w_d for the value of parameter w_d .

(a) Compute the cost of the pdata multiplexors for a module instantiated at size n = N including only the hardware in the n=N instantiation, not in the recursive instantiations. The answer should be in terms of N and w. *Hint: this is easy.*

Cost of the pdata multiplexors at one level in terms of N, w, and (if needed) w_d .

(b) This is important. Expect to expend brain energy. Don't skip. Compute the total cost of the pdata multiplexors for an instantiation at size n = N including the recursive instantiations all the way down. The answer should be in terms of N and w.

Cost of the pdata multiplexors including recursive instantiations in terms of N, w, and (if needed) w_d .

Problem 3: In this problem compute delays for pdata_out and pnum_out. In the solutions use d for the value of parameter wd. This is also important and even more interesting. Expect to expend brain energy. Don't skip.

(a) Assume that the delay of the subtractors computing **pos** is $\lg w_d$, where w_d is the value of parameter wd. (Note that $\lg w_d$ is not an answer to Problem 1.) Further, suppose the delay of the less-than units providing a select signal to the 2-input pdata multiplexors is zero. Using these assumptions compute the delay of the first and last elements of **pdata_out** for an instantiation at **n=N** and show the critical path. The delay should be in terms of N and w_d . To solve this problem it might be helpful to draw two instantiation levels to help find the critical path.

Delay of pdata_out[0] in terms of N and w_d accounting for recursive instantiations. \Box Show critical path.

Delay of pdata_out[N-1] in terms of N and w_d accounting for recursive instantiations. \Box Show critical path.

SVG source for the module below is at https://www.ece.lsu.edu/koppel/v/2023/mt-p1-sol.svg.



SVG source for the module below is at https://www.ece.lsu.edu/koppel/v/2023/hw04-perm-gen.svg.



LSU EE 4755 Homework 5 Due: 27 November 2023

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2023/hw05.v.html.

Collaboration Rules

Each student is expected to complete his or her own assignment. It is okay to work with other students and to ask questions in order to get ideas on how to solve the problems or how to overcome some obstacle (be it a question of Verilog syntax, interpreting error messages, how a part of the problem might be solved, etc.) It is also acceptable to seek out digital design resources for help on Verilog, digital design, etc. It is okay to make use of AI LLM tools such as ChatGPT and Copilot to generate sample Verilog code. (Do not assume LLM output is correct. Treat LLM output the same way one might treat legal advice given by a lawyer character in a movie: it may sound impressive, but it can range from sage advice to utter nonsense.)

After availing oneself to these resources each student is expected to be able to complete the assignment alone. Test questions will be based on homework questions and the assumed time needed to complete the question will be for a student who had solved the homework assignment on which it was based.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account (if necessary), copy the assignment, and run the Verilog simulator on the unmodified homework file, hw03.v.

Homework Overview

In previous assignments there were modules that permuted their inputs, the one called pdata_in. What would happen if the pdata_in input to our permutation module, perm, did not consist of *n* distinct elements? Let's suppose there would be some dire consequences that we need to avoid. That's what this assignment is about, module uniq_vector_seq will be used to determine if elements are distinct.

Module uniq_vector_seq has one we-bit data input, element, where we is a module parameter. There are two outputs, n-bit output uniq_bvec and wc-bit output n_match, where n and wc are module parameters. There is also a 1-bit input start.

At each positive clock edge a new element will be placed on input element. The module output uniq_bvec indicates the elements arriving in the prior n cycles (or since the last start) that appear only once. An element that appears only once is called *unique*. Output uniq_bvec (unique bit vector) has one bit for each of the past n cycles, with the least significant bit corresponding to the previous cycle. Let t denote the current cycle and let e_t denote the element at the element input in cycle t. The previous cycle is t-1, the one before that is t-2, and so on. (If this is starting to get confusing look at the examples in the description of the testbench.)

First, consider the case where start=0 for at least the last n cycles. If uniq_bvec[i] is 1 then e_{t-i-1} is unique, meaning that $e_{t-i-1} \neq e_{t-j-1}$ for $i, j \in [0, n-1]$ and $i \neq j$. If uniq_bvec[i] is 0 then $e_{t-i-1} = e_{t-j-1}$ for some $i \neq j$.

For example, suppose n = 4 and suppose the most recent elements are 4, 7, 5, 5, with 4 the least recent of those. Then uniq_bvec will be 1100_2 because 5 appears twice. For 7, 7, 2, 2 uniq_bvec will be 0000_2 , for 4, 7, 2, 0 uniq_bvec will be 1111_2 , and finally for 3, 7, 7, 0 uniq_bvec will be 1001_2 . The testbench shows the recent elements and the provided (module output) and if different, the correct value of uniq_bvec.

Output n_match should be set to the number of elements that the most recent element matches, including itself. For 4, 7, 5, 5 n_match=2, for 4, 7, 2, 0 n_match=1 and for 9, 0, 9, 9 n_match=3 but for 8, 8, 8, 6 n_match=1.

In a cycle where start=1 the element on element starts a new sequence. So for the purposes of computing uniq_bvec and n_match element is considered not equal to any element that arrived in a previous cycle.

Testbench

To compile your code and run the testbench press [F9] in an Emacs buffer in a properly set up account. The testbench will apply inputs to several instantiation of module uniq_vector_seq. The instantiations differ in n and in whether the start signal will be set to 1 during testing.

The testbench will always show information about at least 5 (or the value of trace_len) sets of inputs for each instantiation. If there are errors it will show information on at least 4 inputs that generate each kind of error.

Here is sample testbench output from a working module:

```
** Starting tests for n=4, input start used = No **
Trace, uniq_bvec: t=33, 1001
    ], 1, 0, 0, 1 <-- uniq_bvec
[,
[13, 8], 7, 9, 9, 4 <-- Element
[0, 0], 0, 0, 0, 0 <-- Start
Trace, uniq_bvec: t=34,
                     0011
[,
    ], 0, 0,
               1, 1 <-- uniq_bvec
[8, 7], 9, 9, 4, 14 <-- Element
[0, 0], 0, 0, 0, 0 <-- Start
Trace, uniq_bvec: t=35,
                     1100
     ], 1, 1, 0, 0 <-- uniq_bvec
Γ.
[7, 9], 9, 4, 14, 14 <-- Element
[0, 0], 0, 0, 0, 0 <-- Start
```

The text above shows information on three inputs, they occur at t = 33 through t = 35. (Actually those numbers refers to test numbers, not cycles.) The rows labeled **Elements** show the elements that have arrived over the past six cycles. The rightmost one is the most recent. The output above was for a module instantiated with n=4, so only the last 4 elements should matter. As an aid in debugging two additional elements are shown. So, for t = 33 the module should only pay attention to elements 7, 9, 9, 4, and the module should ignore 13, 8. The value of uniq_bvec is shown on the lines that start with Trace. The same value is shown in the rows labeled uniq_bvec. Note that the value 1001 is the output at t = 33. But the values shown in the **Element** and **Start** rows are from the past n + 2 cycles.

Notice that a bit of uniq_bvec is 0 if the corresponding element appears more than once. That is the case for 9 in the t = 33 input. At t = 35 the 9 element becomes uniq because the other 9 has arrived more than n cycles ago. For the examples above n_matches should be 1 at t = 33 and t = 34 and 2 at t = 35 (because there are two 14s).

The start input is used to reset the module. When start=1 the prior elements are forgotten or ignored. The output below shows the correct effect of start.

** Starting tests for n=6, input start used = Yes **
Trace, uniq_bvec: t=53, 000111
[,], 0, 0, 0, 1, 1, 1 <-- uniq_bvec
[13, 99], 1, 1, 1, 19, 95, 53 <-- Element
[0, 0], 0, 0, 0, 0, 0, 0 <-- Start
Trace, uniq_bvec: t=54, 111111
[,], 1, 1, 1, 1, 1, 1 <-- uniq_bvec
[99, 1], 1, 1, 19, 95, 53, 19 <-- Element
[0, 0], 0, 0, 0, 0, 0, 1 <-- Start</pre>

```
Trace, uniq_bvec: t=55, 111111
[, ], 1, 1, 1, 1, 1, 1, 1 <-- uniq_bvec
[ 1, 1], 1, 19, 95, 53, 19, 32 <-- Element
[ 0, 0], 0, 0, 0, 0, 1, 0 <-- Start
```

At t = 53 in the output above there are three elements equal to 1, setting the uniq_bvec bits to zero. A t = 54 the start input is asserted and so the positions with 1 elements become unique. Also arriving element 19 is also considered uniq. If in t = 56 a 19 arrived then the 19 elements would no longer be unique.

Here is testbench output for a module with errors:

```
** Starting tests for n=4, input start used = No **
Error, uniq_bvec: t=9, 0100!= 1100 ( correct )
[ , ], E0, 1, 0, 0 <-- uniq_bvec
[ 9, 9], 9, 2, 13, 13 <-- Element
[ 0, 0], 0, 0, 0, 0 <-- Start
Error, uniq_bvec: t=11, 0001!= 0011 ( correct )
[ , ], 0, 0, E0, 1 <-- uniq_bvec
[ 9, 2], 13, 13, 2, 1 <-- Element
[ 0, 0], 0, 0, 0, 0 <-- Start</pre>
```

The Error line shows first the value of $uniq_bvec$ exiting the module, and then the correct value. The $uniq_bvec$ line shows the value from the module, preceded with an E if that value is wrong. At t = 9 the MSB should have been a 1 because 9 is unique. Perhaps it is being dubbed not unique because there was another 9 earlier, but that should be too early to matter. A common mistake is to leave an output unconnected. The value would be shown as x, say Ex for a $uniq_bvec$ bit.

Error lines are also shown if n_match is wrong:

```
** Starting tests for n=4, input start used = No **
Trace, uniq_bvec: t=10, 0000
Error: n_match: 1 != 2 (correct)
[ , ], 0, 0, 0, 0 <-- uniq_bvec
[ 9, 9], 7, 13, 13, 7 <-- Element
[ 0, 0], 0, 0, 0, 0 <-- Start</pre>
```

In the output above n_match should have been 2 (since element 7 appears twice), but the module output is 1.

The testbench checks instantiations with two values of n, and does one set of tests where start is always 0 (after initialization) and another set of tests where start is occasionally set to 1.

At the end of the testbench a summary of error counts is printed:

```
End of tests n= 4, s=0: 0 bvec errors, 33368 n_match errors for 99992 tests.
End of tests n= 4, s=1: 0 bvec errors, 19771 n_match errors for 99992 tests.
End of tests n= 6, s=0: 0 bvec errors, 18240 n_match errors for 99988 tests.
End of tests n= 6, s=1: 0 bvec errors, 9326 n_match errors for 99988 tests.
xmsim: *W,RNQUIE: Simulation is complete.
```

The output above shows lots of n_match errors but no bvec_uniq errors.

Helpful Examples

The demo module computing a running sum will probably be most helpful. That and other pipelined modules are in file pipe.v in the homework file and can be viewed, with images, at https://www.ece.lsu.edu/koppel/v/2023/pipe.v.html. Look for module simple_pipe_avg.

Problem 1: In the unmodified assignment module $uniq_vector_seq$ has some starter code, and it will actually generate the correct outputs for the start=0 tests. It does so using combinational module $uniq_vector_comb$. The problem with the combinational module is that it is too costly, and also slow. Also, it ignores the start signal. So for this problem remove the instantiation of $uniq_vector_comb$ from $uniq_vector_seq$ and complete $uniq_vector_seq$ so that it operates as described above. It is important that the cost is reasonable. The reason that $uniq_vector_comb$ is costly is that it does n^2 comparisons. Module $uniq_vector_seq$ should only perform about ncomparisons per clock cycle.

(a) Add code to uniq_vector_seq so that n_match works as described above. The code must be synthesizable. Use command genus -file syn.tcl to synthesize. This part is easy.

Complete module so that n_match is correct.

Follow the checkbox items in hw05.v.

(b) Add code to uniq_vector_seq so that uniq_bvec works as described above. This is trickier, at least for a low-cost solution. It might be easier to get the start=0 version working first.

Complete module so that uniq_bvec is correct.

Pay attention to cost, cost should not be proportional to n^2 .

Follow the checkbox items in $\tt hw05.v.$

LSU EE 4755 Homework 6 Due: 1 December 2023

This assignment will be collected and graded, but the grades will not count.

Problem 1: Solve 2022 Final Exam Problem 1. In part a, a timing analysis is to be performed on a combinational vector normalization module norm_comb, and in part b a pipelined version of the module is to be designed.

Problem 2: Solve 2022 Final Exam Problem 2, in which Verilog code describing a vector normalization module, norm_comb_n, is to be completed.

Problem 3: Solve 2022 Final Exam Problem 3, in which a cost and timing analysis is to be done for an illustration of hardware for the add_accum module from 2019 Homework 6.

3 Fall 2022

LSU EE 4755 Homework 1 Due: 21 September 2022

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2022/hw01.v.html.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account, copy the assignment, and run the Verilog simulator and synthesis program on the unmodified homework file, hw01.v. Do this early enough so that minor problems (*e.g.*, password doesn't work) are minor problems.

Homework Background

The goal of this homework assignment and follow-on assignments is to convert an ASCII string into a number. For example, to convert "12" (equivalently 'h3132) into 12 (equivalently 'b1100 or 'd12 or 'hc). An ASCII string is a sequence of bytes, but in this assignment there is just one byte. The follow-on assignments there will be multiple bytes.

The input to the module for this assignment, atoi1, is the character. The module has two outputs, the value, val, and whether the character is a valid digit. For example, "1" is a valid digit, but "#" is not.

The module has a parameter **r** which indicates the radix of the number that's expected. If r=2 and the character is "3" then it is not a valid digit and the returned value should be zero. Further details are provided in the problem description below. For r=16 the valid characters are 0 to 9, A to F, and a to f, with a and A, b and B, ... treated equivalently. The module should work for any **r** up to 36. As of this writing the testbench evaluates radices 4, 8, 10, 14, 16, 19. The TA-bot might test with different radices. Feel free to modify the testbench to try different radices. (Search for testbench and figure out the code.)

This assignment exercises basic Verilog skills like instantiating modules and understanding the difference between structural and procedural code. In the follow-on assignment the **atoi** modules will be connected to handle longer strings.

Testbench

To run compile your code and run the testbench press [F9] in an Emacs buffer in a properly set up account. In an unmodified assignment the testbench will generate output that includes the following near the end:

```
Radix 4, done with 256 tests, 0 val errors, 0 is_digit errors.
Radix 8, done with 256 tests, 0 val errors, 0 is_digit errors.
Radix 10, done with 256 tests, 0 val errors, 0 is_digit errors.
Radix 14, done with 256 tests, 0 val errors, 0 is_digit errors.
Radix 16, done with 256 tests, 0 val errors, 0 is_digit errors.
Radix 19, done with 256 tests, 0 val errors, 0 is_digit errors.
xmsim: *W,RNQUIE: Simulation is complete.
xcelium> exit
Total number of errors: 0
```

There are zero errors because the procedural code in **atoi1** is correct. Notice that there are separate tallies for each radix plus a grand total. Detailed messages are printed for the first few errors, after which only a tally is provided. For example, here is what the error messages would look like if the conversion to upper case were wrong:

xcelium> run Radix 4, done with 256 tests, 0 val errors, 0 is_digit errors.

Radix 8, done with 256 tests, 0 val errors, 0 is_digit errors. Radix 10, done with 256 tests, 0 val errors, 0 is_digit errors. R 14 Error val 'hOd or D != A (correct) for string " a" R 14 Error val 'h00 or 0 != B (correct) for string " b" R 14 Error is_digit 0 != 1 (correct) for string " b" R 14 Error val 'h00 or 0 != C (correct) for string " c" R 14 Error is_digit 0 != 1 (correct) for string " c" R 14 Error val 'h00 or 0 != D (correct) for string " d" R 14 Error is_digit 0 != 1 (correct) for string " d" Radix 14, done with 256 tests, 4 val errors, 3 is_digit errors. R 16 Error val 'hOd or D != A (correct) for string " a" R 16 Error val 'hOe or E != B (correct) for string " b" R 16 Error val 'hOf or F != C (correct) for string " c" R 16 Error val 'h00 or 0 != D (correct) for string " d" R 16 Error is_digit 0 != 1 (correct) for string " d" Error is_digit 0 != 1 (correct) for string " e" R 16 R 16 Error is_digit 0 != 1 (correct) for string " f" Radix 16, done with 256 tests, 6 val errors, 3 is_digit errors. R 19 Error val 'hOOd or D != A (correct) for string " a" R 19 Error val 'h00e or E != B (correct) for string " b" R 19 Error val 'h00f or F != C (correct) for string " c" R 19 Error val 'h010 or G != D (correct) for string " d" R 19 Error is_digit 0 != 1 (correct) for string " g" R 19 Error is_digit 0 != 1 (correct) for string " h" R 19 Error is_digit 0 != 1 (correct) for string " i" Radix 19, done with 256 tests, 9 val errors, 3 is_digit errors. xmsim: *W,RNQUIE: Simulation is complete. xcelium> exit Total number of errors: 28

Consider one of those lines with some ASCII-art underlining:

```
Error val 'hOd or D != A (correct) for string " a"
R 14
0000
                                                       44 <- ASCII art underlining
                1111
                         2
                              3
```

The part underlined with 0000 indicates that this result is for radix r=14. The character to be converted is a, though it's called a string and shown with a leading space. That's the part underlined with 44. The part underlined with 3 is what the value should be in radix 14, and the part underlined with 2 is what the atoi1 module's val output is, in radix 14. The part underlined in 1111 is the module output in hexadecimal. In this case, the value should be 10 (decimal) or A (base 14), but the module output is D (which is 13 in decimal).

That's one error line. Going back to the more complete testbench output notice that only strings with lower-case letters are wrong. This is what one would expect since we intentionally broke the lower-to-upper conversion.

The testbench only shows details for the first 4 errors of each type at each radix. If you want to see more errors feel free to edit the testbench. Search for err < 5. Feel free to edit the testbench in other ways to facilitate debugging. The TA-bot will run your code using its own testbench, so don't worry about being accused of cheating by modifying the testbench.

Problem 1: Appearing below (and in the assignment file hw01.v) is module atoi1, ASCII to Integer of 1 character. The module has an 8-bit input char, a 1-bit output is_digit, and a w-bit output val. There are also two parameters, w (width) and r (radix). Output is_digit is set to 1 iff (if and only if) str is a radix-r digit. If char is a digit output val is set to its value, otherwise val is set to zero.

```
module atoi1 #( int r = 32, w = clog2(r) )
   ( output logic [w-1:0] val, output uwire is_digit, input uwire [7:0] char );
  logic [7:0] char_uc;
  logic [w-1:0] val_09, val_az;
  logic is_09, is_az;
  digit_valid_09 #(r,w) v09( is_09, val_09, char );
  assign is_digit = is_09 || is_az;
  always_comb begin
      char_uc = char >= Char_a && char <= Char_z ? char - Char_a + Char_A : char;</pre>
      val_az = 10 + char_uc - Char_A;
      is_az = char_uc >= Char_A && char_uc < Char_A + r - 10;</pre>
      if ( is_09 )
                         val = val_09;
      else if ( is_az ) val = val_az;
      else
                         val = 0;
   end
endmodule
```

For example, suppose w=4 and r=10. If char=51 (ASCII for the digit 3), then output val is set to 3 and is_digit is set to 1. If char=58 (ASCII for : [colon]), then output val is set to 0 and is_digit is set to 0. If char=65 (ASCII for A), then output val is set to 0 and is_digit is set to 0. Now suppose that atoi1 is instantiated with r=16 (hexadecimal). If char=65 (ASCII for A), then output val is set to 10 and is_digit is set to 1. If char=97 (ASCII for a), then output val is also set to 10 and is_digit is set to 1.

Module atoi1 includes an instantiation of module digit_valid_09, a continuous assignment (of is_digit), and procedural code. Module digit_valid_09, which is finished, converts an ASCII character into a value if the character is a digit from 0 to 9, and if the value is valid (less than r). (Those who are not sure what digit_valid_09 is doing might want to inspect module atoi1_behavioral, which uses only procedural code.)

Make the following changes to atoi1: Instantiate module char_to_uc (character to upper case) and use it to convert char to upper case. Instantiate module digit_valid_az and use it to compute is_az and val_az. Instantiate mux2 modules and use them to route the correct value to the val output of atoi1. As you instantiate and connect these modules remove the procedural code that's no longer needed.

Also, add code to digit_valid_az and char_to_uc so that they compute their proper values.

To help with debugging, do this in small steps. For example, first complete the char_to_uc module and make sure there are no compilation errors. Then instantiate it in atoi1, and make sure there are no compilation errors and no testbench errors.

Pay attention to compilation errors and ask for help with any that you can't understand.

The code must by synthesizable. To synthesize your code issue the command genus -files syn.tcl. If there are no errors, running this command will generate output that includes like the following:

Module Name	Area	Delay	Delay	
		Actual	Target	
atoi1_r2	1796	0.454	10.000	ns
atoi1_behavioral_r2	1796	0.454	10.000	ns
atoi1_r8	2047	0.495	10.000	ns
atoi1_behavioral_r8	2047	0.495	10.000	ns
atoi1_r10	2517	0.529	10.000	ns
atoi1_behavioral_r10	2517	0.529	10.000	ns
atoi1_r16	5792	0.752	10.000	ns
atoi1_behavioral_r16	5792	0.752	10.000	ns
atoi1_r2_3	3754	0.274	0.100	ns
atoi1_behavioral_r2_4	3754	0.274	0.100	ns
atoi1_r8_3	5762	0.260	0.100	ns
atoi1_behavioral_r8_4	5762	0.260	0.100	ns
atoi1_r10_3	7371	0.259	0.100	ns
atoi1_behavioral_r10_4	6937	0.260	0.100	ns
atoi1_r16_3	18302	0.363	0.100	ns
atoi1_behavioral_r16_4	18302	0.363	0.100	ns

The synthesis script is synthesizing both the module for this assignment, atoi1, and the behavioral version, atoi1_behavioral. The radix at which it is instantiated is appended to the name.

LSU EE 4755

Homework 2

Due: 7 October 2022

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2022/hw02.v.html.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account, copy the assignment, and run the Verilog simulator and synthesis program on the unmodified homework file, hw02.v. Do this early enough so that minor problems (*e.g.*, password doesn't work) are minor problems.

Homework Background

This assignment is a follow-on to Homework 1, in which the atoi1 modules will be used to convert an ASCII string holding a number into a value. For example, to convert "12" (equivalently 'h3132) into 12 (equivalently 'b1100 or 'd12 or 'hc). An ASCII string is a sequence of bytes, in this assignment there can be one or more bytes.

The string is on module input str and it is declared so that str[0] is the rightmost (least-significant) character of the ASCII string. For example, if the string were " 987" then str[0] would be the 7 (ASCII value 48 + 7 = 55), str[1] would be the 8, str[2] the 9, and str[3] the space (ASCII value 32).

Let *n* denote the number of characters in the string. The ASCII number may take up *n* or fewer characters. For example, for n = 4 the number 1 would only need one character. The remaining characters can be any non-digit character. For example for the 1 in radix 10 the string can be "1", or "abc1", but not "ab21" since that would be the number 21.

The input to the modules for this assignment, atoi_it and atoi_tr, is the string. The modules have two outputs, the value, val, and the number of digits in the number, nd. For example, for input "9 43" in radix 10 the value is 43 and the number of digits is 2. The 9 does not count because it is separated by a non-digit character from the 43. For radix 16 and input " a12" the value is 2578 and the number of digits is 3. If the radix is 3 and the string is "32" then the value is 2 and the number of digits is 1. The 3 is not a valid digit in trianary, and so it ends the number.

For r=16 the valid characters are 0 to 9, A to F, and a to f, with a and A, b and B, ... treated equivalently. The module should work for any r up to 36.

As of this writing the testbench evaluates radices 10 and 16 and a variety of string lengths. Feel free to modify the testbench to try different radices. (Search for testbench and figure out the code.)

Reference Module

To help you get started, there is a reference module, atoi_pr, that correctly computes the value of a string. This module would not be a correct solution to either problem.

```
module atoi_pr
#( int r = 11, n = 5, wv = $clog2( r**n ), wd = $clog2(n+1) )
( output logic [wv-1:0] val,
    output logic [wd-1:0] nd,
    input uwire [7:0] str [n-1:0] );
always_comb begin
    val = 0; nd = 0;
    for ( int i=0; i<n; i++ ) begin
        // Get val of current char. If val is < 0 then char is not a digit.
        automatic int dval = atoi1_func(str[i],r);</pre>
```

```
if ( dval < 0 ) break;
val += dval * r**i;
nd++;
end
end
end
endmodule
```

Testbench

To compile your code and run the testbench press [F9] in an Emacs buffer in a properly set up account. In an unmodified assignment the testbench will generate output that includes the following near the end:

Total errors for radix 10: 14000 len, 14140 val Total errors for radix 16: 14000 len, 14224 val Total errors for string length 1: 4000 len, 4052 val Total errors for string length 2: 4000 len, 4052 val Total errors for string length 3: 4000 len, 4052 val Total errors for string length 4: 4000 len, 4052 val Total errors for string length 7: 4000 len, 4052 val Total errors for string length 4000 len, 8: 4052 val Total errors for string length 9: 4000 len. 4052 val Total errors for mod atoi_it: 14000 len, 14182 val Total errors for mod atoi_tr: 14000 len, 14182 val

The errors are tallied above three ways: by radix, by string length, and by module (atoi_it and atoi_tr). In the output above both modules have errors, and their are errors at each radix and length. In the output below module atoi_it has zero errors, and errors only occur at lengths 3, 7, 9. The errors would have to be due to atoi_tr:

```
Total errors for radix 10: 1201 len,
                                        1201 val
Total errors for radix 16:
                             1144 len,
                                        1036 val
Total errors for string length
                                        0 len.
                                 1:
                                                    0 val
Total errors for string length
                                 2:
                                        0 len,
                                                    0 val
Total errors for string length
                                                  687 val
                                 3:
                                      687 len,
Total errors for string length
                                 4:
                                        0 len.
                                                    0 val
Total errors for string length
                                 7:
                                     1434 len,
                                                 1434 val
Total errors for string length
                                 8:
                                         0 len,
                                                    0 val
                                      224 len,
Total errors for string length
                                 9:
                                                  116 val
Total errors for mod atoi_it:
                                   0 len,
                                               0 val
Total errors for mod atoi_tr:
                                2345 len,
                                            2237 val
Total number of errors: 4582
```

The messages above are tallies printed near the end. Detailed messages are printed for the first few errors. Here are two error messages (of many from the same run as above: Mod-atoi_tr R-10 n- 7 Ty-SP Error val 1 != 2011 (correct) for string " 2011" Mod-atoi_tr R-10 n- 7 Ty-SP Error len 1 != 4 (correct) for string " 2011"

Each of the two lines indicates that the error was with module $\mathtt{atoi_tr}$ instantiated at r=10 (radix 10) and string length of n = 7. (Don't confuse string length with the length of the number in the string.) Ty-SP indicates the type of test, in this case a number padded with spaces. The first line indicates that the value should have been 2011 but the module output was 1. The second line informs us that the length should have been 4, but the module nd output was 1.

There are three types of tests: Ty-SC, Ty-SP, and Ty-GE. For Ty-SC tests the number is always

one digit (regardless of the string length). For Ty-SP tests the number is followed spaces. For Ty-GE the number is followed by any non-digit character.

The testbench only shows details for the first 4 errors of each type at each radix. If you want to see more errors feel free to edit the testbench. Search for err < 5. Feel free to edit the testbench in other ways to facilitate debugging. The TA-bot will run your code using its own testbench, so don't worry about being accused of cheating by modifying the testbench.

Similar Problems

See the l025-gen-elab.v demo code for examples of how to use generate statements iteratively (needed for Problem 1) and recursively (needed for Problem 2). An easy example is ripple_w from that set. Pay attention to how the carry signals are connected from one BFA to the other: module ripple w

```
\#( int w = 4 )
   ( output uwire [w-1:0] sum,
                                  output uwire cout,
     input uwire [w-1:0] a, b,
                                  input uwire cin);
   uwire
                 c[w-1:-1];
   assign
                 c[-1] = cin;
   assign
                 cout = c[w-1];
   for ( genvar i = 0; i<w; i++ )</pre>
     bfa bfai( sum[i], c[i], a[i], b[i], c[i-1] );
endmodule
    A simple recursive module is min_t which finds the minimum of its n inputs:
module min t
  #(int w = 4, n = 8)
   ( output uwire [w-1:0] e_min, input uwire [w-1:0] e [ n-1:0 ] );
   if ( n == 1 ) begin
      assign e_min = e[0];
   end else begin
      localparam int n_lo = n / 2;
      localparam int n_hi = n - n_lo;
      uwire [w-1:0] m_lo, m_hi;
      min_t #(w,n_lo) mlo( m_lo, e[n_lo-1:0] );
      min_t #(w,n_hi) mhi( m_hi, e[n-1:n_lo] );
      min_2 #(w) m2( e_min, m_lo, m_hi);
   end
```

endmodule

See the count-leading-zeros assignment from 2019 Homework 2 for an example of how to recursively instantiate a module and combine results.

Problem 1: Module atoi_it has an n-character input str, and outputs val (value) and nd (number of digits), as well as parameters r (radix) and n (number of characters in string). Following the rules further below, complete module atoi_it so that val is the value of the radix-r ASCII representation of a number in str and nd is set to the number of digits in the number (not to be confused with the number of characters in the string). Further details are described in the background section above.

Module atoi_it must use instantiations of module atoi1 to convert characters to their values and it must use instantiations of mult_by_c to do multiplication by a constant. The module may also instantiate add and mux2 modules, but it doesn't have to. A selection of modules is defined under the Problem 0 section of hw02.v.

Module atoi_it must not instantiate itself (that's Problem 2). Instead, use a generate loop to instantiate the atoi1 and mult_by_c modules.

To help you get started, module atoi_it includes an instantiation of atoi1 and mult_by_c. But, those are not in a generate loop and won't work. They are only there to show you how to instantiate something correctly.

Make sure that your module is synthesizable by running the synthesis script. The command is genus -files syn.tcl.

Problem 2: Module atoi_tr has the same ports and parameters as atoi_it and should produce the same outputs. Complete atoi_tr so that it does so by recursively instantiating two instances of itself, with each instance operating on about half of the string. As with atoi_it, it must use instantiations of atoi1 to convert characters and mult_by_c to perform multiplication. Make sure that the module is synthesizable.

Some may have realized (or will come to realize) that for certain radices neither multiplication nor addition (at least for values) is needed. Don't worry about that, it's okay to use mult_by_c even when not needed.

The module must be synthesizable. See the comments in the code for other requirements and things to look out for.
LSU EE 4755

Homework 3 Due: 17 Oct 2022, 11:30 CDT

Resources

To help with this assignment review the simple cost model slides and the material in generate statement demo code.

The following problems ask for both inferred hardware and a cost/performance analysis: 2019 Midterm Exam Problem 3c (equality module with shifted inputs), 2021 Midterm Exam Problem 2 (a concentrator for neural network hardware reading sparse weights).

The following are good cost and performance analysis questions (these are the same ones mentioned in the simple model slides): The "find oldest" (big mux) problem covered in class can be found in 2017 Final Exam Problem 3, the knapsack problem hardware covered in class can be found in 2016 Final Exam Problem 2 and 4.

The following are good inferred hardware and optimization problems. Start with 2019 Midterm Exam Problem 1 (a recursively described clz [count leading zeros] module). A problem combining both recursive and iterative generate statements can be found in 202 Midterm Exam Problem 4.

A sequential version of the ASCII-to-value hardware was also assigned in this course. The hardware was described by procedural code and it operated sequentially, so I don't suggest that it specifically be studied for clues on how to solve this assignment.

Problem 1: Compute the cost and delay, using the simple model, of the atoi1 module (from the solution to Homework 1) instantiated with r=12. Base this on a module with reasonable optimizations applied and be sure to account for constants when computing cost and delay.

- Base your analysis of ripple implementations of the adder and magnitude comparison units.
- Show cost.
- Show delay of each output and identify the critical path.
- Account for constants when computing cost and delay.

```
module atoi1
```

```
#( int r = 32, w = $clog2(r) )
 ( output logic [w-1:0] val, output logic is_digit,
    input uwire [7:0] char );
logic [w-1:0] val_09, val_az, val_n;
logic is_09, is_az;
digit_valid_09 #(r,w) v09( is_09, val_09, char );
uwire [7:0] char_uc;
char_to_uc tuc(char_uc,char);
digit_valid_az #(r,w) vaz( is_az, val_az, char_uc );
uwire [w-1:0] z = 0;
mux2 #(w) mval(val_n,is_09,val_az,val_09);
mux2 #(w) mval0(val,is_digit,z,val_n);
```

```
assign is_digit = is_09 || is_az;
endmodule
typedef enum
  { Char_0 = 48, Char_9 = 57, Char_A = 65, Char_Z = 90, Char_a = 97, Char_z = 122 }
  Chars_Special;
module digit valid 09
  #(int r = 9, vw = (clog2(r)))
   ( output uwire valid, output uwire [vw-1:0] val, input uwire [7:0] char );
   assign val = char - Char_0;
   assign valid = char >= Char_0 && char <= Char_9 && char < Char_0 + r;
endmodule
module char_to_uc( output uwire [7:0] uc, input uwire [7:0] c );
   uwire is_lc = c >= Char_a && c <= Char_z;</pre>
   uwire [7:0] uc_if_lc = c - Char_a + Char_A;
   mux2 #(8) m( uc, is_lc, c, uc_if_lc );
endmodule
module digit_valid_az
  \#( int r = 11, vw = \frac{1}{clog2}(r) )
   ( output uwire valid, output uwire [vw-1:0] val, input uwire [7:0] char );
   assign val = 10 + char - Char_A;
   assign valid = char >= Char_A && char < Char_A + r - 10;</pre>
endmodule
module mux2
  #(int w = 3)
   ( output uwire [w-1:0] x,
     input uwire s, input uwire [w-1:0] a0, a1 );
   assign x = s? a1 : a0;
endmodule
```

Problem 2: Appearing further below is the atoi_it from the solution to Homework 2. (a) Show the hardware inferred for an atoi_it module instantiated with r=14 (yes, radix 14) and n=3.

- Show atoi1, mult_by_c, and add instances as modules, do not show what is inside.
- Show the hardware inferred for the operators, such as && and ?:.
- Do not confuse parameters and ports.
- Omit hardware that does not belong, such as "hardware" to compute values needed at elaboration time.
- Be sure to show the inferred logic. Remember that generate statements describe what happens at elaboration time, not what happens at simulation time nor does it describe operations performed by the hardware.

(b) Show the hardware inferred for an $\texttt{atoi_it}$ module instantiated with r=16 (hexadecimal this time) and n=3, and show the hardware after optimization. Consider the impact of optimization on the $\texttt{mult_by_c}$ and add modules, which should be considerable since r is a power of 2.

```
module atoi it
 #( int r = 11, n = 5, wv = $clog2( r**n ), wd = $clog2(n+1) )
   ( output logic [wv-1:0] val,
     output logic [wd-1:0] nd,
     input uwire [7:0] str [n-1:0] );
   uwire [wv-1:0] vali[n-1:-1];
   uwire is_valid[n-1:-1];
   uwire [wd-1:0] ndi[n-1:-1];
   assign is_valid[-1] = 1;
   assign ndi[-1] = 0;
   assign vali[-1] = 0;
   assign nd = ndi[n-1];
   assign val = vali[n-1];
   localparam int wcv = $clog2(r);
   for ( genvar i=0; i<n; i++ ) begin</pre>
      // Find Value of Digit i
      11
      uwire [wcv-1:0] valdr;
      uwire is_digit;
      atoi1 #(r,wcv) a( valdr, is_digit, str[i] );
      // Determine if this digit continues a sequence of valid digits
      // starting at str[0].
      11
      assign is_valid[i] = is_digit && is_valid[i-1];
      // Replace value with zero if str[i] is not a digit, or if the
      // string of valid digits has already ended.
      11
      uwire [wcv-1:0] vald = is_valid[i] ? valdr : 0;
      // Multiply (scale) the digit value based on its position in the number.
      11
      uwire [wv-1:0] vals;
      mult_by_c #( .w_in(wcv), .c(r**i), .w_out(wv) ) mc( vals, vald );
      // Add the scaled digit to the value accumulated so far.
      11
      add #(wv) a1( vali[i], vali[i-1], vals );
      // Update the number of digits so far.
      11
      assign ndi[i] = is_valid[i] ? i+1 : ndi[i-1];
   end
endmodule
```

Problem 3: Appearing further below is the atoi_tr from the solution to Homework 2. Show the inferred logic for an instantiation with r=10 and n=9.

- Show the logic for one level. That is, show the two instantiations of atoi_tr, alo and ahi, but don't show what is inside of alo nor ahi.
- Show the mult_by_c instantiations as modules, do not show what is inside.
- Show the hardware inferred for the operators, such as && and ?:.
- Omit hardware that does not belong, such as "hardware" to compute values needed at elaboration time.
- Do not confuse parameters and ports.
- Be sure to show the inferred logic. Remember that generate statements describe what happens at elaboration time, not what happens at simulation time nor does it describe activities performed by the hardware.

```
module atoi_tr
 #( int r = 11, n = 5, wv = \frac{c\log^2(r**n)}{wd} = \frac{c\log^2(n+1)}{r})
   ( output uwire [wv-1:0] val, output var logic [wd-1:0] nd,
     input uwire [7:0] str [n-1:0] );
   if (n == 1) begin
      uwire is_dd;
      uwire [wv-1:0] valr;
      atoi1 #(r,wv) a( valr, is_dd, str[0] );
      assign val = is_dd ? valr : 0;
      assign nd = is_dd; // Note: nd may be more than one bit.
   end else begin
      // Prepare to split the input string into two halves. Note that
      // the hi half may be larger, and so we use nhi to compute the
      // number of bits needed in the value output (vwh) and the
      // number of digits output (dwh).
      11
      localparam int nlo = n/2;
      localparam int nhi = n - nlo;
      localparam int vwh = $clog2( r**nhi );
      localparam int dwh = $clog2( nhi+1 );
      //
      uwire [vwh-1:0] vallo, valhi;
      uwire [dwh-1:0] ndlo, ndhi;
      // Split input string between two recursive instantiations
      11
      atoi_tr #(r,nlo,vwh,dwh) alo( vallo, ndlo, str[nlo-1:0] );
      atoi_tr #(r,nhi,vwh,dwh) ahi( valhi, ndhi, str[n-1:nlo] );
      // Determine whether the hi half of the string may be part
      // of the number.
      11
      uwire hitoo = ndlo == nlo;
      uwire [vwh-1:0] valhid = hitoo ? valhi : 0;
      // Scale the upper half.
      11
      uwire [wv-1:0] valhis; // Value High Scaled
      mult_by_c #(vwh,r**nlo,wv) mc( valhis, valhid );
      assign val = vallo + valhis;
      assign nd = hitoo ? nlo + ndhi : ndlo;
   end
endmodule
```

LSU EE 4755 Homework 4 Due: 4 November 2022

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2022/hw04.v.html.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account, copy the assignment, and run the Verilog simulator and synthesis program on the unmodified homework file, hw04.v. Do this early enough so that minor problems (*e.g.*, password doesn't work) are minor problems.

Helpful Past Homework Assignments

For those who would like to see a fairly simple sequential circuit, and one that counts characters, see 2017 Homework 4, maxrun.

Problem 1: Module word_count has three inputs, an 8-bit char input, and 1-bit inputs clk and reset. At each positive edge of clk a new ASCII character will be available at input char. The characters might be from a text file, a keyboard, or some other source of English text. Based on the word rules given below these characters form words, and the module is to count the words and provide other information.

Module word_count has three parameters, w1, wn, and n_avg_of. The module has six outputs. Output len_word, which is w1 bits, is the length so far of the current word, or the length of the most recent word. Output n_words, which is wn bits, is the number of complete words counted since the last reset.

Output len_avg, which is also wl bits, is the average length of the n_avg_of most recent completed words with the fractional part truncated. If fewer than n_avg_of words have ended since the last reset then len_avg should be zero. For example, if n_avg_of=4 and the lengths of the four most recent words are 8, 4, 12, and 15 then len_avg should be set to $\lfloor (8+4+12+15)/4 \rfloor = \lfloor 39/4 \rfloor = \lfloor 9.75 \rfloor = 9$. If there is a reset and then only three words have ended, len_avg should be 0.

Output word_start should be set to 1 iff the current character starts a word. Output word_part should be set to 1 if the current character is part of a word based on the word rules described further below. (If word_start is 1 then word_part is 1.) Output word_ended is 1 if the character in the previous cycle was the last character of a word.

For an example of how these output should be set examine the testbench output below, collected for the text "A or bee":

	W-M	I	Text>!	SPE L	N A {D}
Trace	2-5	0	" A"	SP 1	0 0 {1}
Trace	2-5	1	" A "	spE 1	1 0 {0}
Trace	2-5	2	" A o"	e SP_ 1	1 0 {1}
Trace	2-5	3	" A or"	spP_ 2	1 0 {1}
Trace	2-5	4	" A or "	_pE 2	2 1 {0}
Trace	2-5	5	" A or b"	e SP_ 1	2 1 {1}
Trace	2-5	6	" A or be"	spP_ 2	2 1 {1}
Trace	2-5	7	" A or bee"	_pP_ 3	2 1 {1}
Trace	2-5	8	" A or bee "	_pE 3	3 2 {0}
Trace	2-5	9	"A or bee 2"	e 3	3 2 {0}
Trace	2-5	10	" or bee 2n"	3	3 2 {1}

Each line shows the output at one cycle, the I column shows an index (which is something like a cycle number). The W column shows the value of n_avg_of and the M column shows the maximum possible word length. The last column, {D}, is for debugging, see the discussion further below.

The most-recent ten characters are shown under the Text heading, in the first line (index 0), A is the most recent character. There will be an R to the right of the text in a cycle when reset is 1.

The L column shows the length of the word so far, or the length of the most recent word. The N column shows the number of words (incremented when the word ends), and the A column shows a running average of the last word lengths, the last 2, in this case. The column headed SPE shows the state of the outputs of word_start, word_part, and word_ended outputs. An upper case letter shows the state after the positive edge of the clock (which is the one that is needed). To help with debugging, the lower case letters show the state just before the positive edge.

Note: word_part should only be 1 if char is a word-part char and a word has already started. Notice that at index 10 the arriving character is an n, which is a word-part character. But because it was not preceded by a non-word-part character a word does not start at index 10 (nor 9).

Notice that L is updated as each character arrives, while ${\tt N}$ and ${\tt A}$ only update when the word ends.

The testbench will trace the first few lines, and then only show trace lines when there are errors (along with a few trace lines preceding the error). For lines with an error the correct output is also shown:

	W-M	I Text>!	SPE L	N A			
Trace	2-5	5 " I II I"	e SP_ 1	2 1			
Trace	2-5	6 " I II II"	spP_ 2	2 1			
Trace	2-5	7 " I II III"	_pP_ 3	2 1			
Trace	2-5	8 " I II III "	_pE 3	3 3 <- Error	Correct ->	E 3	32
	W-M	I Text>!	SPE L	N A		SPE L	N A

In the example above, the running average, A, is wrong. The module output is 3 but the testbench expects a 2.

Reset Behavior

If input reset is 1 on a positive edge then len_word, num_words, and len_avg should all be set to zero and input char should be considered a non-word character (regardless of its value). The trace below shows an example of reset behavior. The reset occurs at index 6. Because of when the reset occurs bee, rather than being a three-letter word is considered a one-letter word, the last e. Notice also that the average length (column A) does not show a value until two complete words arrive.

	W-M	I	Text>!	SPE L	N A {D}
Trace	2-5	3	" A or"	spP_ 2	1 0 {1}
Trace	2-5	4	" A or "	_pE 2	2 1 {0}
Trace	2-5	5	" A or b"	e SP_ 1	2 1 {1}
Trace	2-5	6	" A or be"	R sp 0	0 0 {1}
Trace	2-5	7	" A or bee"	SP_ 1	0 0 {1}
Trace	2-5	8	" A or bee "	spE 1	1 0 {0}
Trace	2-5	9	"A or bee k"	e SP_ 1	1 0 {1}
Trace	2-5	10	" or bee kn"	spP_ 2	1 0 {1}
Trace	2-5	11	"or bee kno"	_pP_ 3	1 0 {1}
Trace	2-5	12	"r bee knot"	_pP_ 4	1 0 {1}
Trace	2-5	13	" bee knot "	_pE 4	2 2 {0}
Trace	2-5	14	"bee knot "	e 4	2 2 {0}

Testbench Information

The testbench will instantiate and test word_count at three different sizes, varying both the value of n_avg_of and the maximum word size. The values of n_avg_of will be 2, 1, and 9. To change these sizes search for pset in hw04.v. Several items in the testbench can be changed to facilitate debugging and familiarization. Search for HW04 and read the comments for more info. The testbench will start streaming characters from the string test_one, and after that will construct a stream of random characters. Feel free to change test_one to facilitate debugging.

The testbench shows the first few errors encountered, and then silently tallies errors. After each instantiation is tested a summary of errors is shown:

```
Trace 9-7 10 " or bee " ____ 3 3 0 {0}
Trace 9-7 11 "or bee " ____ 3 3 0 {0}
Done with n_avg_of=9, max wd len=7. Errors: st 0, pa 0, en 0, nc 0, nw 0, av 0
```

The line starting Done shows a tally of errors by type after the word Errors. Six types of errors are tallied (all have zero errors in the output above). They are st, the word_start output, pa, the word_part output, en, the word_ended output, nc, the len_word output, nw, the num_words output, and av, the len_avg output. Remember that the line describes one instantiation, so there should be three lines printed.

The trace can be helpful for looking at values of objects in your module (not just inputs and outputs). As an example, the trace shows the value of object char_az, but feel free to change that or add others. To do so search for wd_cnt.char_az. It appears as an argument to \$sformatf which prepares part of the trace text. Here wd_cnt is the instance name that the testbench uses for word_count. Change or add arguments to \$sformatf to examine additional objects in your module. Be sure to change the format string to match the arguments. The end of the format string, the part in curly braces, handles the last argument wd_cnt.char_az.

The value of wc will always be chosen so that output len_chars never overflows. It is unlikely but not impossible that the number of words is too large for wn.

Word Rules

A character is an 8-bit quantity. A character is called a word-start character if it an ASCII alphabetic character (upper or lower case). In word_char net char_wd_start is set to one if the char input is a word-start character. A character is called a *word-part character* if it an ASCII alphabetic character (upper or lower case), a digit, or an underscore character. The word_count module net char_wd_part is set to one if the char input is a word-part character. Note that all word-start characters are word-part characters.

A word starts when the current character is a word-start character and the previous character was not a word-part character or if the module was reset in the previous cycle. A word ends when an arriving character is not a word-part character.

The length of a word is the number of characters. The output len_word should only be zero after a reset and until the next word starts.

Design Requirements and Goals

As always, avoid costly designs. Pay particular attention to the logic computing len_avg. Do not use n_avg_of-1 adders to compute this. And definitely don't use n_avg_of division units.

The design can use procedural code, but it must be synthesizable. Use command genus -files syn.tcl to synthesis. Timing and area (cost) reports will be placed in a file named syn-report.log.

LSU EE 4755 Homework 5 Due: 22 November 2022

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2022/hw05.v.html.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account, copy the assignment, and run the Verilog simulator and synthesis program on the unmodified homework file, hw05.v. Do this early enough so that minor problems (*e.g.*, password doesn't work) are minor problems.

Assignment Background

As we should know the synthesis program, given a Verilog description of a module, writes a design file with an optimized version of the module mapped to the chosen technology. For this assignment the chosen technology is the same Oklahoma University ASIC process we've been using throughout the semester.

An important skill for those writing Verilog descriptions is to estimate the cost and performance of those synthesized modules. In this assignment we'll look at how well the synthesis program handles the different modules we considered for computing the floating-point expression $v_0^2 + v_0 v_1 + v_1^2$. We will consider the combinational, sequential, and pipelined modules covered in class.

A synthesis script will be used to synthesize these modules, plus three arithmetic unit modules, plus additional modules created for the solution to this problem. To complete the assignment the output of the script must be understood and the synthesis script must be modified. The output of the synthesis script is similar to the output of the scripts used in prior assignments, so it should be familiar. Modifying the script will be something new, and might be a challenge for some of you. It is okay to seek help modifying the script from classmates and others, though the solutions to the problems themselves must be completed individually.

Modules

This assignment includes modules for the combinational, sequential, and pipelined implementations of the multi-step computation. They are named ms_comb, ms_seq, and ms_pipe. For comparison the assignment also includes modules containing a single floating-point unit, they are named try_mult, try_add, and try_sq (square).

Four additional modules are provided for experimentation, $m1_func$, $m1_comb$, $m1_seq$, and $m1_pipe$. These modules initially perform the computation $v_0 + v_0v_1 + v_1^2$, but they can be modified to perform other computations. Module $m1_func$ is used by the testbench to obtain a correct value, so modify it first so that it computes the desired computation. Then modify the others that you want to synthesize. (The synthesis program does not care whether a module passes the testbench, but no conclusion can be drawn from the area and delay of module that does not work correctly.)

All of these modules have the same parameters and ports, though not every module uses every port. For example, only ms_seq and ms_pipe are sequential so that the clk and reset ports on the others serve no function. These unused ports will be eliminated during optimization so they won't affect cost or timing.

Module Parameters and Floating Point Format

The modules used in this assignment all have the same parameters, these parameters specify the floating-point number format to be used. The first parameter, wsig, specifies the number of bits in the significand (fractional part) of the floating point number. The default value is 23, which is the same as an IEEE 754 single (C float). The second parameter, wexp, is the number of bits in the exponent. The default value is 8, which matches an IEEE single. The third parameter, ieee, specifies whether the IEEE floating-point format should be strictly followed. The default value

is 1, which means yes; a 0 means that special cases do not have to be handled correctly. These include NaN (not a number) and subnormal values. The size of the floating point number using these parameters is 1+wexp+wsig, the extra 1 is for the sign bit.

For this assignment all modules are instantiated with ieee=0. This is done to explore the fuller range of optimization possibilities and also to reduce the time needed for synthesis.

The sample synthesis runs consider two formats, IEEE single in which wsig=23 and wexp=8, and the ML-friendly BF16 (informally known as brain float) in which wsig=7 and wexp=8. The advantage of BF16 for machine learning is that it is half the size of a single, and with a 7-bit significand, requires half the energy for multiplication than the older 16-bit FP16 format. For us the big advantage is that it takes less time to synthesize than a single.

Testbench

The testbench exercises the six modules, ms_comb, ms_seq, ms_pipe, m1_comb, m1_seq, and m1_pipe instantiated with a significand size of 7 and 23. They should all initially pass. As with other testbenchs in this class, a line will be printed for the first few module errors, and a tally will be provided for each module and size. The testbench uses ms_func to determine the correct output of the ms modules and m1_func to determine the correct output of the m1 modules. When modifying the m1 modules be sure to also modify m1_func so that the testbench can show you whether your modified modules do what you think they are doing.

The Synthesis Script

As with past assignments, the modules in the assignment file should be synthesized using the script syn.tcl. Unlike other assignments, this script will have to be modified.

The synthesis script itself is written in TCL (Tool Control Language, the abbreviation is pronounced tickle) a scripting language chosen by Cadence for scripting their EDA software. (Nowadays Python would be used. If it were up to me it would be Perl. But it's TCL.) Documentation for TCL can be found at https://tmml.sourceforge.net/doc/tcl/. This describes TCL, not the functionality needed to run Genus or other tools. For Genus-specific commands see the synthesis documentation linked to https://www.ece.lsu.edu/koppel/v/ref.html.

For this assignment it should not be necessary to use new Genus commands, just to change which modules are synthesized and which parameters to instantiate with. For that, one needs only a rudimentary knowledge of TCL, perhaps what can be learned just by looking at syn.tcl.

The synthesis script starts by setting some script variables, using the TCL set command, and by setting Genus attributes, using the Genus set_db command:

```
set verilog_source hw05.v
set syn_level "high"
set spew_file "spew.log"
set report_file "syn-report.log"
set_db syn_global_effort $syn_level
set rpt_chan [open $report_file w]
puts "Synthesizing at effort level \"$syn_level\"\n"
```

As one might guess syn_level is the amount of effort used for synthesis. Possible values are none, low, medium, and high. These initial lines are followed by the definition of a TCL procedure syn_mod, which emits the commands needed to synthesize a module, followed by commands to retrieve the area and delay of the synthesized module. A line of text is written showing the area and delay. It should not be necessary to modify syn_mod for this assignment.

Module syn_mod is called in a loop nest near the end of the file:

```
# List of combinational modules.
```

```
set mods_comb { ms_comb try_mult try_add try_sq }
set delay_targets { 100 0.1 }
set mods { try_mult try_add try_sq }
set mods { ms_comb ms_seq ms_pipe try_mult try_add try_sq }
set wsigs { 7 14 23 }
foreach delay_target $delay_targets {
    foreach ws $wsigs {
        foreach mod $mods {
            syn_mod $mods {delay_target " $ws 8 0 "
            }
        }
}
```

The loop nest above synthesizes each of the modules listed in mods (that's the inner loop). Each of these six modules is synthesized for each significand size found in wsigs. These modules are synthesized with each delay constraint in delay_target. For the code above there would be a total of $2 \times 6 \times 3$ synthesis runs. That would probably take hours.

The first set line writes variable mods_comb with a list of combinational modules. This variable must be updated with any new combinational modules that you use. Variable mods is set twice, first to a list of the arithmetic modules, then those are replaced with a list of the arithmetic modules and our multi-step modules. (Because of the second assignment the first assignment has no effect.) If one wanted to only synthesize the arithmetic modules one would comment out the second mods line. There is no need to use a loop nest. It is possible to write a syn_mod call for each synthesis, for example:

```
set delay_targets { 100 }
set wsigs { 7 14 23 }
syn_mod try_mult 5 "7 8 0"
syn_mod try_mult 5 "7 6 0"
# Exit before the loop nest.
close $rpt_chan
quit
foreach delay_target $delay_targets {
```

The example above does two synthesis runs. The 5 is the delay target and the quoted part are the parameters. (The parameters must be quoted so that they are read as a single argument to syn_mod.) In the example above, try_mult is synthesized with two exponent sizes, 8 bits and 6 bits, both are synthesized with a delay target of 5 ns.

To synthesize a new module (for example, one you wrote) add the name to one of the mod lists, or just use the name on a direct call to syn_mod as in the example above. Iff the module is combinational add the module to mods_comb. Not adding a combinational module to mods_comb will result in an error. Adding a sequential module to mods_comb will result in incorrect timing.

Synthesis Script Output

The synthesis script syn.tcl is run using the command genus -files syn.tcl. The run starts with a substantial amount of header output, including warnings, copyright information, and system information. Some is shown below:

[cyc.ece.lsu.edu] % genus -files syn.tcl

2022/11/13 16:52:05 WARNING This OS does not appear to be a Cadence supported Linux configuration. 2022/11/13 16:52:05 For more info, please run CheckSysConf in <cdsRoot/tools.lnx86/bin/checkSysConf <productId> TMPDIR is being set to /tmp/genus_temp_566634_cyc.ece.lsu.edu_koppel_nvftYI Cadence Genus(TM) Synthesis Solution. Copyright 2022 Cadence Design Systems, Inc. All rights reserved worldwide. Cadence and the Cadence logo are registered trademarks and Genus is a trademark of Cadence Design Systems, Inc. in the United States and other countries.

[16:52:12.338826] Configured Lic search path (21.01-s002): /apps/linux/cadence/share/license/license.dat:/opt/pgi/license.dat

The output of the script proper (as opposed to Genus, the synthesis program) starts with an announcement of the synthesis effort level followed by a table of synthesis results:

Synthesizing at effort level "high"

Module Name	Area	Delay	Delay	Synth
		Actual	Target	Time
ms_comb_wsig7_wexp8_ieee0	600190	12.219	0.1 ns	423 s
ms_seq_wsig7_wexp8_ieee0	445400	5.754	0.1 ns	236 s
ms_pipe_wsig7_wexp8_ieee0	797327	5.678	0.1 ns	309 s
ms_comb_wsig14_wexp8_ieee0	1363980	14.391	0.1 ns	707 s

Each line of the table shows the result of one synthesis run. The Module Name column shows the name of the module followed by the parameter values used in its instantiation. In the sample above three different modules are synthesized, ms_comb, ms_seq, and ms_pipe. Module ms_comb is synthesized once with significand of 7 bits and once with a significand of 14 bits.

The Area column shows the area given by the Genus report area command. The units are relative to the OSU technology. The Delay Actual column shows the length of critical path through the module in units of nanoseconds. The Delay Target column shows the delay constraint that the synthesis program was set to meet. In the example above the constraint is 0.1 ns, which means the critical path can be no longer than 0.1 ns. This constraint was intentionally set to an impossibly low value, to determine the minimum delay that the synthesis program could achieve. Normally the delay constraint is set to something achievable, perhaps 4 ns in the example above, and the synthesis program would generate the least expensive design that meets the delay constraint. The Synth Time column shows the wall-clock (elapsed) time needed to perform the synthesis. The wall-clock time is shown to help plan the synthesis runs, it does not directly affect or describe the design itself.

Problem 1: In class we considered three ways of implementing multi_step, the modules that computed $v_0^2 + v_0v_1 + v_1^2$: A combinational version, a sequential version, and a pipelined version. Appearing below are the results from synthesizing these three modules, named ms_comb, ms_seq, and ms_pipe, followed by results of synthesizing modules consisting only of the Chipware floating-point multiplier, adder, and a multiplier with the same value used for both operands. These are synthesized with a large delay constraint, meaning that the cost has been minimized.

Module Name	Area	Delay	Delay Targat	Synth
		ACTUAL	larget	1 Time
ms_comb_wsig23_wexp8_ieee0	1597692	75.142	100.0 n	s 229 s
ms_seq_wsig23_wexp8_ieee0	<mark>945</mark> 919	29.324	100.0 n	s 111 s
ms_pipe_wsig23_wexp8_ieee0	1866509	28.273	100.0 n	s 205 s
try_mult_wsig23_wexp8_ieee0	525991	28.231	100.0 n	s 62 s
try_add_wsig23_wexp8_ieee0	339036	27.396	100.0 n	s 53 s
try_sq_wsig23_wexp8_ieee0	297753	25.504	100.0 n	s 38 s
ms_comb_wsig7_wexp8_ieee0	375767	34.708	100.0 n	s 75 s
ms_seq_wsig7_wexp8_ieee0	275858	15.305	100.0 n	s 34 s
ms_pipe_wsig7_wexp8_ieee0	526000	14.466	100.0 n	s 62 s
try_mult_wsig7_wexp8_ieee0	94274	9.346	100.0 n	s 13 s
<pre>try_add_wsig7_wexp8_ieee0</pre>	140221	14.196	100.0 n	s 21 s
try_sq_wsig7_wexp8_ieee0	57802	6.085	100.0 n	s 8s

(a) Based on the data above, show the latency and throughput of each module for the 23-bit significand. It might be necessary to look at the module descriptions (Verilog code) to answer this question.

(b) For each of the two significand sizes, show that the delay of the three ms modules are what one would expect given the delays of the three arithmetic modules.

(c) Using the cost of the arithmetic units, show that the cost of ms_comb is lower than expected, but the cost of ms_seq and ms_pipe are about or perhaps a little more than what one would expect.

Problem 2: It is welcome that the cost of ms_comb is lower than what one would expect based on the cost of the arithmetic units. There are several possible reasons for this, for example the synthesis program may be simplifying the two adders used in computations such as a + b + c or it may be sharing hardware used to process the common b operand in expressions like $a \times b$ and $b \times c$, or perhaps it may even be transforming $v_0^2 + v_0v_1 + v_1^2$ into $(v_0 + v_1)^2 - v_0v_1$. Or maybe the costs for the arithmetic units shown in the table are higher than they should be.

Perform a set of synthesis runs to provide evidence for a reason that ms_comb cost less than its constituent parts. Consider the possible reasons given above, or one of your own. These synthesis runs can operate on one of the existing modules, a slightly modified version of the modules, or something wholly different. The modules m1_comb, m1_seq, m1_pipe can be used for experimentation. See the Modules section above.

Describe the results of these experiments and how they convincingly support a particular reason for the lower cost. Data from a single synthesis run, or a series of very similar runs will not be considered convincing.

The Verilog file for this assignment will be collected, but submit the answers to this question on paper or by E-mail. Please E-mail PDF files. Sending word processor source files as a final product is unprofessional, even if they are T_EX files.

In your writeup:

- Indicate how you believe the synthesis program is optimizing ms_comb.
- Describe the modules you synthesized to come to this conclusion, and the results of synthesis. Most credit will be given for this part of the assignment.
- Explain why your experiments show that the lower cost was not due to other optimizations.

4 Fall 2021

LSU EE 4755 Homework 1 Due: 24 September 2021

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2021/hw01.v.html.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account, copy the assignment, and run the Verilog simulator and synthesis program on the unmodified homework file, hw01.v. Do this early enough so that minor problems (*e.g.*, password doesn't work) are minor problems.

Problem 1: The partially completed insert_at module below and in the homework assignment file has three inputs, a wa-bit input ia, a wb-bit input ib, and a $\lceil \lg(wa+1) \rceil$ -bit input pos, and there is one output, a wa+wb-bit output o. Complete the module following the coding requirements given further below so that o consists of the bits of ia with ib inserted at pos. That is, o[pos-1:0] should be set to ia[pos-1:0], o[wb+pos-1:pos] should be set to ib, and o[wa+wb-1:wb+pos] should be set to ia[wa-1:pos].

For example, let wa=6 and wb=2, ia=111111, ib=00, and pos = 2. Then o=11110011. For pos=5, o=10011111. For those still not 100% sure of what o should be set to should look at how o_shadow is computed in the testbench module. Also, the testbench will show what the output should be when it isn't.

```
module insert_at
#( int wa = 20, wb = 10, wo = wa+wb, walg = $clog2(wa+1) )
( output logic [wo-1:0] o,
    input uwire [wa-1:0] ia, input uwire [wb-1:0] ib,
    input uwire [walg-1:0] pos );
// The line assigning mask_low must be replaced with a mask module.
uwire [wo-1:0] mask_low = ( 1 << pos ) - 1; // REPLACE ME!
uwire [wo-1:0] ib_at_pos;
shift_left #(wb,wo,walg) sl1( ib_at_pos, ib, pos );
assign o = ia & mask_low | ib_at_pos;
endmodule</pre>
```

The insert_at module must be synthesizable and must not use procedural code and must not use shift operators. (That includes the line assigning mask_low, it must be replaced.) Instead, rely on instantiations of the provided shift and mask modules.

The testbench will test your module and report the first few errors. For example, here is the testbench output for the unmodified module:

```
Error for ia=11111111 ib=000
                              pos= 0
                                      00000000000 != 11111111000 (correct)
                                      0000000001 != 11111110001 (correct)
Error for ia=11111111
                      ib=000
                              pos= 1
Error for ia=11111111 ib=000
                                      0000000011 != 11111100011 (correct)
                              pos= 2
Error for ia=11111111 ib=000
                             pos= 3
                                      00000000111 != 11111000111 (correct)
Error for ia=11111111
                      ib=000
                                      00000001111 != 11110001111 (correct)
                              pos= 4
Done with 27 tests, 15 errors found.
```

The text 00000001111 != 11110001111 (correct) shows the output of insert_at to the left of the != and the correct answer to the right. So in this case 00000001111 is the module output

and 11110001111 is what the module output should have been. Only the first few errors are shown, but the total number of errors is reported at the end, 15 in this case.

Synthesizability can be checked by running the synthesis script using the command genus -files syn.tcl. If the module is synthesizable (though not necessarily correct) a table of area and delay will be shown, for example:

Module Name	Area	Delay	Delay
		Actual	Target
insert_at	51832	0.987	1.000 ns
insert_at_1	97968	0.616	0.100 ns
Normal exit.			

One common problem encountered by beginners is setting the correct port sizes. For example, the shift_left module the port sizes are wi, wo, and wolg:

```
module insert_at #( int wa = 20, wb = 10, wo = wa+wb, walg = $clog2(wa+1) )
  ( output logic [wo-1:0] o,
    input uwire [wa-1:0] ia, input uwire [wb-1:0] ib,
    input uwire [walg-1:0] pos );
    uwire [wo-1:0] ib_at_pos;
    shift_left #(wb,wo,walg) sl1( ib_at_pos, ib, pos );
```

So the first connection to a shift_left instantiation must be wi bits, the second must be wo bits, and the third wolg bits. In the unmodified insert_at these parameters to insert_at were set explicitly to match the connection sizes. Sometimes it may be necessary to use an intermediate object or to cast in order to get the correct connection size. For example, if we wanted to shift by pos+1 the following would not work:

shift_left #(wb,wo,walg) sl1(ib_at_pos, ib, pos + 1); because the 1 in the pos+1 expression implicitly expands it to 32 bits. (This results in a warning, but it's not good to clutter compiler output with ignorable warnings.) The problem can be solved using a cast:

```
shift_left #(wb,wo,walg) sl1( ib_at_pos, ib, walg'(pos + 1) );
```

LSU EE 4755

Homework 2

Due: 11 October 2021

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2021/hw02.v.html.

Problem 0: If necessary, follow the instructions at https://www.ece.lsu.edu/koppel/v/proc.html to set up your class account, copy the assignment, and run the Verilog simulator and synthesis program on the unmodified homework file, hw02.v. Do this early enough so that minor problems (*e.g.*, password doesn't work) are minor problems.

Background

The flurry of activity machine learning is due to the success of deep neural networks (DNNs) in providing much improved solutions to otherwise hard-to-tackle problems such as natural language translation and image recognition. Deep neural network consists of multiple layers (more than two or three, otherwise they would not be deep). A *fully connected* layer computes matrix/vector products. The matrix coefficients are called *weights*, and in typical computations there are a large number of weights, so many that performance is limited by the time needed to move them around. Normally with n_i input neurons and n_o output neurons, there would be $n_i n_o$ weights, one for each input/output pair. One way to reduce the number of weights is to not require a weight for each input/output pair. In trained networks many weights are close to zero, so their removal ought to have little effect. If inference hardware (the hardware that computes the output of a layer) supports sparse weights then the network can be trained taking into account that some weights will be zero.

Sparsity is easier said than done because it makes the task of moving inputs and their weights to a functional unit (a multiply/add unit) more difficult. One way of lessening the difficulty is limiting which weights can be set to zero. NVidia Volta-generation GPUs support sparsity in which each group of four inputs used to compute one output is limited to two non-zero weights. Two inputs will go unused for that output (but may be used for others.)

In this assignment a module for sparse computation will be completed, nn_sparse. Like the Nvidia design it will operate on four inputs. But unlike the Nvidia design it can operate in both sparse and dense modes, determined by a fmt input. In dense mode there are four weights, but those weights have a very low precision. In sparse mode there are two weights with higher precision.

There are two challenges. One is a Verilog coding issue: instantiating an nn2 module (see problem description) for the sparse case, and connecting it to the correct inputs, and making sure the nn2 output reaches the module output. The other challenge is to do this in a way that maintains high performance. That is, the wider multipliers used for the sparse case will take more time and so we want to take care to not increase the critical path more than is necessary.

Testbench Output

The testbench will instantiate the nn_sparse module with several different parameter sets. It will then present dense and sparse patterns and check for the correct outputs. In the unmodified code all of the dense patterns should pass but nearly all of the sparse patterns should fail.

The testbench will show details on the first four errors for each configuration, followed by a tally of the total. Here is a sample showing the last error and the tally:

Here is what is shown for each reported error: tn gives a test number, fmt shows the value of the fmt input. Note that fmt[0] is the least significant big. After the format the error line shows the output value in hexadecimal and decimal. In the sample above they are 084cca0 = 4.7993. After that the correct (or at least what the testbench assumes is correct) value is shown: 4.4000 (correct). The next line shows the expression to be computed, which will consist of four terms if the error is for a dense calculation and two terms for a sparse calculation. The example above is for a sparse calculation. The next line, 2.0000 + 2.4000, shows the products.

Finally, the value of an object in the module is shown, acc1. It is shown in hexadecimal, and in decimal. Note that acc1 is floating point, so that the hexadecimal value will let you see the sign, exponent, and significand. In most cases though, it will let you see if the value has any x or z bits.

You are encouraged to add code at this point to print out values of other signals in your module. The code to do that is:

nnsp.acc1, conv#(wexp,wsig_ac)::ftor(nnsp.acc1));

The nn_sparse instance is named nnsp, so nnsp.acc1 refers to an object in the module. The function conv#(wexp,wsig_ac)::ftor(X) converts X from a floating-point format with exponent length wexp and significand length wsig_ac into a real. The code for this function is in hw02.v. Any object could be named, but remember to adjust the \$write for data type, and the parameters to conv if necessary.

To aid in debugging the testbench starts out with sparse patterns in which only one weight is 1 and the others are zero. It will then use weights of 2, 0.1, 10.1. It will repeat the pattern again with two non-zero weights. After that it will use randomly chosen weights and formats. Feel free to modify the testbench to aid in your debugging. Keep in mind that the ta-bot won't test your module using the testbench in your file so removing the tests that your module fails won't help.

Synthesis Script

The synthesis script will synthesize the module at two different target delays. It takes a significant amount of time to run, so only one set of parameters is included. Feel free to modify the script, syn.tcl to add other sets.

Problem 1: Module nn_sparse, has one w_o -bit output, o, four w_i -bit inputs, i[0] to i[3], a w_w -bit input, w, and a four-bit input, fmt. Input w can carry either two or four values, called weights. If fmt=4'b1111 then w carries four weights, each $w_w/4$ bits. These are called dense weights. Otherwise w carries two weights, each $w_w/2$ bits, called sparse weights. To help get started quickly the module assigns the dense weights to four-element net wd.

The module is to compute o in one of two possible ways, depending on the value of fmt. When fmt=4'b1111 the module computes o using the dense weights and all four values of i: $o = i_0w_0 + i_1w_1 + i_2w_2 + i_3w_3$, where i_0 and w_0 are values of i[0] and wd[0]. The Verilog code to do this is already in the module.

The module should work for six additional values of fmt: 4'b0011, 4'b0110, 4'b1100, 4'b1010, 4'b1010, 4'b1010, 4'b1010, 4'b1010, 4'b1010, and 4'b1001, these will be referred to as the sparse formats. For each of these the module should set the output to $o = i_a W_0 + i_b W_1$, where W_0 and W_1 are the two sparse weights and where a is the position of the rightmost (least significant) 1 in fmt and b is the position of the leftmost (most significant) 1 in fmt. For example, if fmt=4'b0011 then a = 0 and b = 1 and the hardware should compute $o = i_0 W_0 + i_1 W_1$, and if fmt=4'b1010 then a = 1 and b = 3 and the hardware $o = i_1 W_0 + i_3 W_1$.

All values are floating-point. They share a common exponent, specified by parameter wexp. The width of the significand of the output is specified by parameter sig_ac, the width of the

significand of the inputs is specified by wsig_in, and the width of the significand of the dense weights is specified by parameter wsig_wd. The layout follows IEEE 754: The most significant bit is a sign bit, that is followed by the exponent, and that is followed by the significand. So the total size of the output is 1+wexp+wsic_ac.

To compute the dense output nn_sparse instantiates three modules: two nn2 modules and fp_add. The nn2 module computes $i_0w_0 + i_1w_1$. The nn2 module instantiates two hy_mult and one fp_add (both described below). Details on the nn2, including parameters, can be learned by inspecting the module (it is in the homework file).

The fp_add module is a convenience wrapper around the Chipware CW_fp_add module.

Module hy_mult wraps CW_fp_mult, but it provides functionality that you'd think would be part of the Chipware library. Unlike the Chipware module, hy_mult can be instantiated so that the multiplier, multiplicand, and product each have different significand sizes, though they all share the same exponent size. (The hy is for hybrid, referring to the different sizes.) The module instantiates the Chipware module using the product significand size. It then widens (or shrinks) the significands of the multiplier and multiplicand inputs (called a and b). The inputs are widened by placing zeros in the least significant bits of the widened significands. This was done with the hope that the synthesis program, when performing optimization, would see that these bits were zero and so optimize away the affected partial products. Experiments using Genus (version 211) confirmed that optimization was occurring.

(a) The table below shows synthesis script output for the hybrid multiplier at a variety of sizes. Based on this table there is a good and bad way to connect the hybrid multiplier. Design your module taking this data into account. In the table the parameter values are concatenated with the module name, and numbers are added on the end to avoid duplicating a name. Remember that with a large delay target cost is the only goal, and with a 1ns goal speed is the primary goal.

For purposes of interpreting the data below, assume your design will be instantiated with parameters {wexp 5} {wsig_ac 14} {wsig_in 8} {wsig_wd 4}. (These can be found in the synthesis script.)

Module Name	Area	Delay	Delay	
		Actual	Target	
hy_mult_wsig_a5_wsig_b5_wsig_p20	62541	7.466	100.000	ns
hy_mult_wsig_a10_wsig_b10_wsig_p20	131839	12.799	100.000	ns
hy_mult_wsig_a10_wsig_b5_wsig_p20	84546	10.636	100.000	ns
hy_mult_wsig_a5_wsig_b10_wsig_p20	92111	9.851	100.000	ns
hy_mult_wsig_a15_wsig_b5_wsig_p20	108593	13.440	100.000	ns
hy_mult_wsig_a5_wsig_b15_wsig_p20	123209	12.643	100.000	ns
hy_mult_wsig_a4_wsig_b8_wsig_p14	71354	8.435	100.000	ns
hy_mult_wsig_a8_wsig_b4_wsig_p14	63890	9.007	100.000	ns
hy_mult_wsig_a14_wsig_b8_wsig_p14	131244	12.047	100.000	ns
hy_mult_wsig_a8_wsig_b14_wsig_p14	144388	11.824	100.000	ns
hy_mult_wsig_a3_wsig_b7_wsig_p12	59985	7.737	100.000	ns
hy_mult_wsig_a7_wsig_b3_wsig_p12	53501	8.081	100.000	ns
hy_mult_wsig_a12_wsig_b7_wsig_p12	110260	12.113	100.000	ns
hy_mult_wsig_a7_wsig_b12_wsig_p12	117097	11.660	100.000	ns
hy_mult_wsig_a5_wsig_b5_wsig_p20_22	130160	2.398	1.000	ns
hy_mult_wsig_a10_wsig_b10_wsig_p20_22	324729	3.046	1.000	ns
hy_mult_wsig_a10_wsig_b5_wsig_p20_22	189191	2.690	1.000	ns
hy_mult_wsig_a5_wsig_b10_wsig_p20_22	214533	2.684	: 1.000 J	ns
hy_mult_wsig_a15_wsig_b5_wsig_p20_22	248189	2.742	1.000	ns

hy_mult_wsig_a5_wsig_b15_wsig_p20_22	302877	2.900	1.000 ns
hy_mult_wsig_a4_wsig_b8_wsig_p14_22	171041	2.369	1.000 ns
hy_mult_wsig_a8_wsig_b4_wsig_p14_22	135568	2.232	1.000 ns
hy_mult_wsig_a14_wsig_b8_wsig_p14_22	296160	3.030	1.000 ns
hy_mult_wsig_a8_wsig_b14_wsig_p14_22	321123	3.232	1.000 ns
hy_mult_wsig_a3_wsig_b7_wsig_p12_22	127217	2.308	1.000 ns
hy_mult_wsig_a7_wsig_b3_wsig_p12_22	132936	1.994	1.000 ns
hy_mult_wsig_a12_wsig_b7_wsig_p12_22	263353	2.823	1.000 ns
hy_mult_wsig_a7_wsig_b12_wsig_p12_22	260279	2.951	1.000 ns

(b) Modify nn_sparse so that it computes the correct outputs for both sparse and dense inputs, and is coded for higher speed. Since a sparse weight is larger than a dense weight a multiplier designed to use sparse weights would cost more and take more time than one designed for dense weights. But, when computing sparse weights only one addition operation is needed. Design your module so that this benefit is realized.

Modify only nn_sparse to solve the problem, and use the provided FP units. (Contact me if you feel modifying other modules is needed. (Note that you are free to modify the testbench and related files to help with debugging. But the solution itself should only involve changes to nn_sparse.)

Solving this problem requires good debugging skills. Use SimVision (see the course procedures page) to view what is going on inside your module. Also take advantage of the testbench output, and don't hesitate to modify it so that it provides tests that will help you better understand your module.

LSU EE 4755 Home

Homework 3

Due: 18 October 2021

To help solve the problems below, look at problems listed in the simple model slides, 2020 Homework 4, 2019 Midterm Exam Problem 2b and c, and especially 2018 Final Exam problems 1 and 2.

Problem 1: As requested in the subproblems below use the simple model to determine the cost and delay of the insert_at module from the solution to Homework 1 (see last page) instantiated with $wa = w_a$ and $wb = w_b$, and using $C_{lsb}(w_a)$ for the cost of the mask_lsb module and $D_{lsb}(w_a)$ for the delay of the mask_lsb module. The wo and walg parameters are not set so you can use their default values, $w_o = w_a + w_b$, $l_a = \lceil \lg(w_a + 1) \rceil$, and $l_b = \lceil \lg w_b \rceil$, in your answers.

For partial credit, and to help you solve the problems provide a sketch of the inferred hardware. It may help to first solve the problem for specific values of w_a and w_b , and then to generalize for arbitrary w_a and w_b .

(a) Find the cost and delay of the hardware inferred for the line of Verilog from insert_at shown below. Just for the hardware described on the line. There's no trick, this part is easy. Just remember to express your answers in terms of w_a , w_b , and w_o .

assign o = ia_high | ib_at_pos | ia_low;

(b) Find the cost and delay of the shift_left module instances slc and slb taking into account any constant inputs and assuming that the synthesis program infers a logarithmic shifter. Don't forget that your answer must be in terms of w_a , w_b , w_o , l_a , and l_b , and that these denote the parameters of insert_at, not the parameters of the shifters. For more information on the logarithmic shifter see the additional material provided for the Set 1 lectures on the course lectures page.

Before cutting-and-pasting simple-model cost and delay expressions for a logarithmic shifter, take a close look at the parameters set for **slc** and **slb** and be sure to optimize for them. Notice that unlike typical shifters, the shift-out and shift-in ports are not the same size and that the shift amount is not necessarily ceiling-log-two of the input width.

Hint: The cost and delay for one of these shifters will be really easy to compute.

(c) Find the cost and delay of insert_at. Use the answers above and work out cost and delay for the remaining hardware in the module. Don't forget to use $C_{lsb}(w_a)$ for the cost of the mask_lsb module and $D_{lsb}(w_a)$ for the delay of the mask_lsb module.

Problem 2: Some of you may have seen this coming: Find expressions for $C_{lsb}(w)$, the cost of the mask_lsb module and $D_{lsb}(w)$, the delay of the mask_lsb module, in both cases wo = w, where wo is the parameter used in the mask_lsb definition. Assume a well-optimized design, not something that uses $w [\lg w]$ -bit magnitude comparison units.

Hint: Think about the problem for about 30 minutes, then look at 2018 Final Exam Problems 1 and 2.

An uncommented Homework 1 solution appears below. For the full version visit https://www.ece.lsu.edu/koppel/v/2021/hw01-sol.v.html.

```
module insert at
  #( int wa = 20, wb = 10, wo = wa+wb, walg = clog2(wa+1) )
   ( output logic [wo-1:0] o,
     input uwire [wa-1:0] ia,
     input uwire [wb-1:0] ib,
     input uwire [walg-1:0] pos );
   uwire [wa-1:0] mask_low;
   mask_lsb #(wa) ml(mask_low, pos);
   uwire [wa-1:0] ia_low = ia & mask_low;
   uwire [wa-1:0] ia_high_low = ia & ~mask_low;
   localparam int wblg = $clog2(wb);
   uwire [wo-1:0] ia_high;
   shift_left #(wa,wo,wblg) slc( ia_high, ia_high_low, wblg'(wb) );
   uwire [wo-1:0] ib_at_pos;
   shift_left #(wb,wo,walg) slb( ib_at_pos, ib, pos );
   assign o = ia_high | ib_at_pos | ia_low;
endmodule
module shift left
  #( int wi = 4, wo = wi, wolg = $clog2(wo) )
   ( output uwire [wo-1:0] o,
     input uwire [wi-1:0] i,
     input uwire [wolg-1:0] amt );
   assign o = i << amt;</pre>
endmodule
module mask lsb
  #(int wo = 6, wp = (clog2(wo+1)))
   ( output logic [wo-1:0] o, input uwire [wp-1:0] n1 );
   always_comb for ( int i=0; i<wo; i++ ) o[i] = i < n1;</pre>
endmodule
```

LSU EE 4755 Homework 4 Due: 11 November 2021

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2021/hw04.v.html.

Problem 0: If necessary, follow the instructions at https://www.ece.lsu.edu/koppel/v/proc.html to set up your class account, copy the assignment, and run the Verilog simulator and synthesis program on the unmodified homework file, hw04.v. Do this early enough so that minor problems (*e.g.*, password doesn't work) are minor problems.

Teamwork

Students can work on this assignment in teams. Each student should submit his or her own assignment but list team members. It is recommended that one team member be responsible for learning SimVision.

Every member of a team that has completed a project, must be capable of re-solving the problem. It is recommended that all team members re-solve the problem on their own for their own pedagogical benefit.

Problem 1: Module bit_keeper has a w_b -bit output bits ($_b$ is for width of buffer) and a 1-bit output ready. Think of output bits as a long bit vector (w_b bits long) that is edited using the module's inputs. Commands to edit bits are given using four-bit input cmd (command), w_i -bit input din (data in), and w_s -bit input pos (position). The module is to operate sequentially using input clk.

Complete bit_keeper as described below, and make sure that it is synthesizable. As always, code should be written clearly, and designs should not be costly or slow.

When completed bit_keeper should operate as follows. On a positive edge of clk action is taken based on the value of cmd. The possible values of cmd are: Cmd_Reset, Cmd_None, Cmd_Write, and Cmd_Rot_To. (These can be used as constants in your code. The constants are defined by enum Command.) Some commands will be complete in one cycle (the cycle in which the cmd is set up to the positive edge of clk). Other commands will take multiple cycles.

Be sure to understand the details of how multi-cycle commands execute. When a multi-cycle command starts the ready output must be set to zero and must be held at zero until the command completes. The command and its arguments will only be held at the inputs for one cycle, and so at the next positive clock edge they will be gone. The cmd input will be set to Cmd_Nop, and the pos and din inputs will be set to random values. This means that the inputs of multi-cycle commands that will be needed in subsequent cycles must be saved in registers.

The testbench can emit a trace of commands and their effects. This trace is used below to illustrate what the module is supposed to do. The trace is collected after the command completes. A trace entry starts with the word Cycle. The cycle number is shown, followed by command details, followed by the state of bits.

For Cmd_Reset output bits should be set to zero. Also, any internal registers should be set to zero. The command should complete at the positive edge. This should set ready to 1. In the trace below the reset command set bits back to zero. Notice that the command completes in one cycle (based on the cycle numbers).

Cycle	307 -	- test	73:	Cmd_Nop	:	bits = 01401f4
Cycle	308 -	- test	74:	Cmd_Reset	:	bits = 0000000

For Cmd_Rot_To the value in bits must be rotated so that the contents of bits[0] is moved to bits[pos], bits[1] is moved to bits[(pos+1)%wb], and so on. This is like a left shift of pos bits, except that the most significant pos bits of bits are rotated into the the pos least significant bits. In the trace below the rotate command rotates four bits (one hexadecimal digit). Notice that the most-significant digit on the first line is rotated to the least significant digit after the rotation command.

Cycle 301 te	st 71: Cmd_Nop	: bits = 40	1401f
Cycle 306 te	st 72: Cmd_Rot_	_To pos 4 : bits = 01	401f4

This rotation **must be performed** using two instances of module rot_left . One instance should rotate by 1, the other rotates by a larger value, call it r_b , of your choosing. Each clock cycle the value of **bits** is rotated using one of these, but never both in the same clock cycle. Use the r_b -bit rotate instance until the number of bit positions to shift is $\leq r_b$, then use the 1-bit rotate instance.

Command Cmd_Write has two forms based on the value of input pos. If pos is zero then the least significant w_b bits of bits should be written with din. This should complete at the positive edge. Otherwise, bits pos through pos+wi-1 of bits should be written with din—but not directly. Instead, bits should be rotated so that bit pos is at the least-significant position, then the data should be written, then bits should be rotated back to its original position. Use only the two rot_left instances.

The trace below shows a write with **pos=0**:

Cycle	417		test	86:	Cmd_Nop					:	bits	=	0000240000
Cycle	418		test	87:	Cmd_Write	pos	0, 0	data 7	7	:	bits	=	0000240007
W	Then g	pos	is nor	n-zero	the writes t	ake lo	ongei	r:					
Cycle	96		test	20:	Cmd_Nop					:	bits	=	0a000003c
Cycle	107		test	21:	Cmd_Write	pos	27,	data	4	:	bits	=	0a2000003c

No action is needed for command Cmd_Nop. In fact, this is the command that will be present while the external hardware, including the testbench, is waiting for other commands to complete.

The testbench will test bit_keeper at two sizes. At each size detailed information is given for the first few errors. That includes a trace of commands leading up to the error, followed by the erroneous command, and what the bits should have been. After each error the testbench sets its shadow value of bits to the erroneous output so that subsequent tests can pass. Here is in example of the output:

```
Cycle 22 -- test
                  0: Cmd_Rot_To pos 20
                                               : bits = 000000000
Cycle 54 -- test
                  1: Cmd_Rot_To pos 31
                                               : bits = 000000000
Cycle 55 -- test
                  2: Cmd_Nop
                                               : bits = 000000000
                  3: Cmd_Write pos 37, data 2 : bits = 4000000000
Cycle 96 -- test
                  4: Cmd_Nop
Cycle 97 -- test
                                               : bits = 400000000
                  5: Cmd_Rot_To pos 5
                                               : bits = 000000008
Cycle 103 -- test
                  6: Cmd_Write pos 0, data 3
                                              : bits = 000000003
Cycle 104 -- test
Error in test 7: Cmd_Write pos 1, data 2 : 0000000c04 != 0000000005 (correct)
```

For multi-cycle commands the testbench will wait for ready to go to zero and then back to one. If that does not happen after a certain number of cycles the testbench will *timeout*, meaning that it will give up waiting and print a CYCLE LIMIT EXCEEDED message. If there is a timeout while a command is in progress (meaning that ready did go to zero, but did not return to one) the testbench will show a trace of recent history, followed by an indication of what it was waiting for: Exit from clock loop at cycle 16000, limit 16000, ** CYCLE LIMIT EXCEEDED **

```
** Preceding Commands **
Cycle 7 -- test 0: Cmd_Rot_To pos 20 : bits = 000000000
Cycle 14 -- test 1: Cmd_Rot_To pos 31 : bits = 000000000
Cycle 15 -- test 2: Cmd_Nop : bits = 000000000
** In-Progress Command **
test 3: Cmd_Write pos 37, data 2
-- Awaiting ready = 1.
```

If the testbench does not timeout then it will print a tally of the number of errors after testing each bit_keeper instance. Also, as a measure of quality, the testbench reports the average number of cycles to perform Cmd_Rot_To and Cmd_Write (with non-zero pos). For example,

```
Starting tests for (wb=40,wi=4)
Finished 200 tests for (wb=40,wi=4), 0 errors.
Avg cyc Cmd_Rot_To 5.5 (67) Cmd_Write 10.6 (35)
```

Starting tests for (wb=28,wi=8)
Finished 140 tests for (wb=28,wi=8), 0 errors.
Avg cyc Cmd_Rot_To 4.2 (57) Cmd_Write 8.2 (18)

The lines starting Avg cyc report timing. The number in parentheses is the number of times the command was issued. So for the first set of tests Cmd_Rot_To was tried 67 times, and the average number of cycles taken to complete it was 5.5.

A lower number for Avg cyc can indicate a good design, or that certain rules were not followed.

It is very important that debugging tools are used. Take advantage of the testbench messages to see what is going wrong. Run SimVision to get a detailed look at what your module is doing.

LSU EE 4755 Homework 5 Due: 17 November 2021

Problem 1: Solve 2020 Solve-Home Final Exam Problem 1, which asks for the inferred hardware for the $v_0^2 + v_0v_1 + v_1^2$ module that we covered in class. For those who may have forgotten how to use a pencil, or never learned, an SVG version of the illustration is available at https://www.ece.lsu.edu/koppel/v/2020/fe-ms.svg. Use Inkscape or your favorite SVG editor on the file.

Problem 2: This assignment does not have a Problem 2. I know that's confusing but the alternative is also confusing.

Problem 3: Solve 2020 Solve-Home Final Exam Problem 3, which asks for a timing analysis of the $v_0^2 + v_0v_1 + v_1^2$ module. An SVG version of the diagram is at https://www.ece.lsu.edu/koppel/v/2020/fe-ms-t.svg.

LSU EE 4755 Homework 6 Due: 22 November 2021

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2021/hw06.v.html.

Problem 0: If necessary, follow the instructions at https://www.ece.lsu.edu/koppel/v/proc.html to set up your class account, copy the assignment, and run the Verilog simulator and synthesis program on the unmodified homework file, hw06.v. Do this early enough so that minor problems (*e.g.*, password doesn't work) are minor problems.

Teamwork

Students can work on this assignment in teams. Each student should submit his or her own assignment but list team members. It is recommended that one team member be responsible for learning SimVision.

Every member of a team that has completed a project, must be capable of re-solving the problem. It is recommended that all team members re-solve the problem on their own for their own pedagogical benefit.

Problem 1: Complete module multi_step_pipe so that it is a pipelined version of the multi_step_functional or multi_step_seq modules. All of modules are in hw06.v. (This is based on 2020 Solve-Home Final Exam Problem 2.)

The module must accept a new set of v0 and v1 values each clock cycle and produce a new result each clock cycle. In the module set nstages to the number of stages in your module, so that the value of output result is based on the inputs that appeared nstages clock cycles ago.

Instantiate as many Chipware floating-point multiplication and addition modules as needed. (Do not use procedural code for the arithmetic.) The critical path should pass through at most one floating-point module.

Also, set the ready output at the correct time. Output ready should be set to the value that start has nstages ago.

The testbench will show a trace for about the first three computations (inputs in which **start** was 1), and will show a trace for the ten cycles preceding each error, up to seven errors. A tally of errors will be shown at the end. Here is a sample of the testbench for a working module:

MS	Pipe	Cyc	20	In:	0.0,	0.0	->	0.0	Rdy	0	,	Res:	0.0	
MS	Pipe	Cyc	21	start=	=0				Rdy	0	,	Res:	0.0	
MS	Pipe	Cyc	22	start=	=0				Rdy	0	,	Res:	0.0	
MS	Pipe	Cyc	23	start=	=0				Rdy	1	,	Res:	0.0	Good
MS	Pipe	Cyc	24	start=	=0				Rdy	0	,	Res:	0.0	
MS	Pipe	Cyc	25	In:	1.0,	0.0	->	1.0	Rdy	0	,	Res:	0.0	
MS	Pipe	Cyc	26	start=	=0				Rdy	0	,	Res:	0.0	
MS	Pipe	Cyc	27	start=	=0				Rdy	0	,	Res:	0.0	
MS	Pipe	Cyc	28	In:	0.0,	1.0	->	1.0	Rdy	1	,	Res:	1.0	Good
MS	Pipe	Cyc	29	start=	=0				Rdy	0	,	Res:	0.0	
MS	Pipe	Cyc	30	start=	=0				Rdy	0	,	Res:	0.0	
MS	Pipe	Cyc	31	start=	=0				Rdy	1	,	Res:	1.0	Good
For	For MS Pipe ran 400 tests: Errors: 0 wrong val, 0 bad timing													

On a cycle in which input start is 1 the trace line will show the word In: followed by the values of v0 and v1, and to the right of -> the correct result (which should appear nstages cycles later). The text to the right of Rdy shows the value of the ready output. If the value is incorrect it is followed by an x, for example, Rdy 1x,.

The text to the right of Res: shows the value on the module result output. That is followed by text commenting on the result. A comment will be shown if Rdy is 1 or if an output is expected. Good indicates a correct value at the correct time. XX: Need Rdy indicates that the correct value appears at the correct time, but the ready output isn't 1. XX: Wrong indicates the wrong value at the time when an output was expected. XX: Early indicates the correct value arriving too early. XX: Unexpected indicates the wrong value at a time when no value at all is expected.

Below are excerpts from the testbench output on the unmodified module.

MS	Pipe	Cyc	20	In:	0.0,	0.0	->	0.0	Rdy	OX,	Res:	0.0	XX:	Need R	.dy	
MS	Pipe	Cyc	21	start=	=0				Rdy	1X,	Res:	0.0	XX:	Early		
MS	Pipe	Cyc	22	start=	=0				Rdy	ο,	Res:	0.0				
MS	Pipe	Cyc	23	start=	=0				Rdy	Ο,	Res:	0.0				
MS	Pipe	Cyc	24	start=	=0				Rdy	Ο,	Res:	0.0				
MS	Pipe	Cyc	25	In:	1.0,	0.0	->	1.0	Rdy	OX,	Res:	0.0	XX:	Wrong		
MS	Pipe	Cyc	26	start=	=0				Rdy	1X,	Res:	1.0	XX:	Unexpe	cted	
MS	Pipe	Cyc	27	start=	=0				Rdy	Ο,	Res:	0.0				
MS	Pipe	Cyc	28	In:	0.0,	1.0	->	1.0	Rdy	OX,	Res:	0.0	XX:	Wrong		
MS	Pipe	Cyc	29	start=	=0				Rdy	1X,	Res:	0.0	XX:	Early		
MS	Pipe	Cyc	30	start=	=0				Rdy	Ο,	Res:	0.0				
MS	Pipe	Cyc	31	start=	=0				Rdy	Ο,	Res:	0.0				
MS	Pipe	Cyc	32	start=	=0				Rdy	Ο,	Res:	0.0				
MS	Pipe	Cyc	33	In:	1.0,	1.0	->	3.0	Rdy	OX,	Res:	0.0	XX:	Wrong		
MS	Pipe	Cyc	34	start=	=0				Rdy	1X,	Res:	1.0	XX:	Unexpe	cted	
MS	Pipe	Cyc	35	In: -	-8.6,	5.0	->	55.9	Rdy	OX,	Res:	0.0	XX:	Wrong		
MS	Pipe	test	4: 1	Inputs	at cy	c 35,	res	sult ex	cpect	ed a	at cyc 3	35. V	lrong	g val:	h'000000)22
0.0	-! 0000	= 55.8	3659	(corre	ect)											
MS	Pipe	Cyc	36	In:	0.4,	3.9	->	16.7	Rdy	1,	Res: -	-8.6	XX:	Wrong		
MS	Pipe	test	5: 1	Inputs	at cy	c 36,	res	sult ex	cpect	ed a	at cyc 3	36. V	lrong	g val:	h'c10965	57e
-8	.5873	= 16	.7235	5 (cori	cect)											

The following is the testbench output on a module in which nstages is set too low by 1, and in which v00 is used where v01 should be:

MS F	Pipe	Cyc	20	In:	0.0,	0.0	->	0.0	Rdy	Ο,	Res:	0.0				
MS F	Pipe	Cyc	21	start=	=0				Rdy	Ο,	Res:	0.0				
MS F	Pipe	Cyc	22	start=	=0				Rdy	OX,	Res:	0.0	XX:	Need R	.dy	
MS F	Pipe	Cyc	23	start=	=0				Rdy	1X,	Res:	0.0	XX:	Early		
MS F	Pipe	Cyc	24	start=	=0				Rdy	Ο,	Res:	0.0				
MS F	Pipe	Cyc	25	In:	1.0,	0.0	->	1.0	Rdy	Ο,	Res:	0.0				
MS F	Pipe	Cyc	26	start=	=0				Rdy	Ο,	Res:	0.0				
MS F	Pipe	Cyc	27	start=	=0				Rdy	OX,	Res:	0.0	XX:	Wrong		
MS F	Pipe	Cyc	28	In:	0.0,	1.0	->	1.0	Rdy	1Χ,	Res:	2.0	XX:	Unexpe	cted	
MS F	Pipe	Cyc	29	start=	=0				Rdy	ο,	Res:	0.0				
MS F	Pipe	Cyc	30	start=	=0				Rdy	OX,	Res:	0.0	XX:	Wrong		
MS F	Pipe	test	2: I	nputs	at cyc	: 28,	rest	ılt ex	pect	ed a	at cyc 3	80. W	rong	val:	h'00000)000
0.00)00 !=	1.0	000	(corre	ect)											
MS F	Pipe	Cyc	31	start=	=0				Rdy	1X,	Res:	1.0	XX:	Unexpe	cted	

MS Pipe	Cyc	32	star	t=0			Rdy 0 , Res:	0.0	
MS Pipe	Сус	33	In:	1.0,	1.0 ->	3.0	Rdy 0 , Res:	0.0	
MS Pipe	Cyc	34	star	t=0			Rdy 0 , Res:	0.0	
MS Pipe	Cyc	35	In:	-8.6,	5.0 ->	55.9	Rdy OX, Res:	0.0 XX:	Wrong
MS Pipe	Cyc	36	In:	0.4,	3.9 ->	16.7	Rdy 1X, Res:	3.0 XX:	Unexpected
MS Pipe	Cyc	37	In:	-9.5,	-4.5 ->	152.0	Rdy OX, Res:	0.0 XX:	Wrong

Make sure that your modules are synthesizable.

The smart way to solve the problem is to base the design on ms_functional. Remember that the control logic in multi_step_seq, such as logic related to step, is not needed in a pipelined implementation. The solution should be relatively short and uncomplicated. For example, no conditionals are needed.

A good way to start is to compute everything in one stage, and when that's correct break the logic into stages so that the critical path passes through at most one floating-point module.

5 Fall 2020

LSU EE 4755 Homework 1 Due: 16 September 2020

Dependence of the second secon

Problem 1: In the Module-Port-versus-Module-Parameter section of lecture code

https://www.ece.lsu.edu/koppel/v/2020/1005-review.v.html there are several module designs for computing $c_1x + c_2y$, where c_1 and c_2 are constants and x and y are module inputs. The point of that section and of the modules was to illustrate the SystemVerilog differences between module parameters and ports (syntax issues, for example) and also how they relate to the hardware being modeled.

(a) Draw a diagram of module c1x_c2y_good, shown below, using its default parameter values (which are different than the ones in the lecture code). Show the contents of all instantiated modules and appropriately label ports and wires. (See 2016 Homework 1 Problem 3 for a diagram showing instantiated modules. Also see module arb_exp and the illustration that follows in https://www.ece.lsu.edu/koppel/v/2020/1015-syn-comb-str.v.html.)

- Use the default parameter values of the module $c1x_c2y_good$ shown below.
- Use the appropriate parameter values for the mult_by_c instances. *Hint: appropriate is not a synonym for default.*
- Show the ports for all modules.
- Show the number of bits in each wire.
- Label wires with the symbols used below (such as p1 and prod) and take care to place the label on the correct side of a module boundary. (In the two_pie illustration from https://www.ece.lsu.edu/koppel/v/2020/1005-review.v.html look at the wire carrying labels x, i1, and a.).

```
module mult_by_c
  #( int w = 8, int c = 16, int w2 = w+$clog2(c) )
  ( output uwire signed [w2-1:0] prod, input uwire signed [w-1:0] a );
  assign prod = a * c;
endmodule
module c1x_c2y_good
  #( int c1 = 4, int c2 = 7, int w = 15,
    int w2 = w + $clog2(c1) + $clog2(c2) )
  ( output logic signed [w2-1:0] s, input uwire signed [w-1:0] x, y );
  uwire [w2-1:0] p1, p2;
  mult_by_c #(w,c1,w2) m1(p1,x);
  mult_by_c #(w,c2,w2) m2(p2,y);
  assign s = p1 + p2;
endmodule
```

(b) Draw a diagram of module $c1x_c2y_okay$ below using its default parameter values (which are different than the defaults used in the lecture code). Show the same details, such as ports, as was requested for the previous part.

```
module mult
#( int w = 8, int w2 = 2 * w )
  ( output uwire signed [w2-1:0] prod, input uwire signed [w-1:0] a, b );
  assign prod = a * b;
endmodule
module C1x_C2y_okay
#( int c1 = 4, int c2 = 7, int w = 15,
    int w2 = w + $clog2(c1) + $clog2(c2) )
  ( output logic signed [w2-1:0] s, input uwire signed [w-1:0] x, y );
  uwire [w2-1:0] p1, p2;
  uwire [w2-1:0] p1, p2;
  uwire [w:1] C1 = c1, C2 = c2; // Convert constants to desired size.
mult #(w,w2) m1(p1, x, C1);
mult #(w,w2) m2(p2, y, C2);
  assign s = p1 + p2;
```

endmodule

Problem 2: Synthesis programs optimize a design to minimize cost while meeting timing constraints. The illustration below for the mult and mult_by_c modules (used in the slides) show how the multiplier can be simplified when one of the inputs is a convenient constant, 1.

Show how the $c1x_c2y_good$ module from the first problem can be optimized based on the default c1=4 and c2=7 values. To do so show the multiplier replaced by much simpler hardware, such as adder(s). A correct solution uses only one adder for both multipliers, bit relabeling, *plus the adder used to combine* p1 and p2.

Note: As originally assigned, and until Tuesday, 15 September 2020 at about 16:15, the problem stated that a correct solution uses only one adder, implying but not specifically stating that the one adder was the replacement for the multipliers and that there would also be and adder computing p1+p2, for a total of two adders.

Before instantiation and optimization.





LSU EE 4755

Homework 2 Due: 18 September 2020

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2020/hw02.v.html.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account, copy the assignment, and run the Verilog simulator and synthesis program on the unmodified homework file, hw02.v. Do this early enough so that minor problems (*e.g.*, password doesn't work) are minor problems.

Problem 1: Module nn4x4, below, has two inputs, a 4-element vector ai and a 4×4 matrix wht, and one output, a 4-element vector ao. Output ao is set to the product of wht and ai. Parameter ww (width of weight) gives the number of bits in the elements wht and parameter wa (width of activation) gives the number of bits in the elements of ai and ao.

The illustration below the module shows hardware that might be inferred for nn4x4. The illustration also includes three dotted green boxes. These are suggestions on how to hierarchically decompose this large, some would say unwieldy, module.

The two smaller boxes, labeled nn1x2b, show hardware computing part of one output using two inputs. The larger box, labeled nn1x4b shows hardware computing one output using four inputs. As those who took the time to look at the illustration might have guessed by now the module suggested by nn1x4b can be constructed using two instances of nn1x2b. Further, a nn4x4b can be constructed using four instances of nn1x4b. Sounds interesting? Good!

The homework file hw02.v contains module nn4x4, it is there for your reference. The file also contains mostly empty modules nn4x4b, nn1x4b, and nn1x2b. Complete these so that they compute the same output as nn4x4 and are constructed as suggested in the illustration and follow the guidelines below.

Module nn4x4b must instantiate exactly four nn1x4b modules and nn1x4b must instantiate exactly two nn1x2b modules. Module nn1x4b will also need an adder. Module nn4x4b has parameters. Don't change them. The other modules should have similar parameters with the same default values as nn4x4b. Do not ignore the parameters when declaring inputs and outputs. A standing rule in this class is that all code must be clearly written.

The modules must be synthesizable. This should not be a challenge for this assignment. Verify synthesizablity by running the synthesis script using the command genus -files syn.tcl.

Those who fear they might forget to address some part of the problem described here can rest easy. There is a checklist in the part of the Verilog file where the solution goes.

To help you solve the problem in stages the testbench will perform three rounds of tests. In the first round, labeled n12, only output ao[0] will be examined and only inputs ai[0] and ai[1] will have non-zero values. In the second round, labeled n14, only output ao[0] will be examined but all inputs will have non-zero values. The full test, all outputs checked and all inputs are non-zero, is labeled n44.

Some might find it helpful to look at two past homework assignments in which a flat module was to be decomposed hierarchically. The simpler one (perhaps) is 2019 Homework 1, in which a multiplier is decomposed. But the multiplier had two scalar inputs, **a** and **b**. In this (2020) assignment one input is a 1-D array (**ai**) and the other is a 2-D array (**wht**). In the Fall 2017 Homework 1 Problem 2 an 8-input multiplexor is to be decomposed. The mux input **a** is a 1-D array that had to be split between two instances.

Module and illustration on the next page.
endmodule



LSU EE 4755

Homework 3 Due: 13 October 2020

The deadline has been extended by one day, to 13 October (late at night) due to power outages caused by Hurricane Delta.

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2020/hw03.v.html.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account (if you haven't already), copy the assignment, and run the Verilog simulator and synthesis program on the unmodified homework file, hw03.v.

Homework Overview and Neural Network Background

The goal of Homework 2 was to describe a 4×4 matrix/vector multiply circuit hierarchically. That goal is generalized here where an $n_i \times n_o$ matrix is multiplied by an n_i -element vector. In Homework 2 each ao[o] was computed by a tree connection of multipliers. Here both linear and tree connections will be tried. Also, the module in this assignment will optionally do something about overflow.

The modules in this assignment and in Homework 2 could be used any place where matrix/ vector multiplication is needed, but they were designed with a particular application in mind that some students might have guessed from the names used: artificial neural networks. The nn prefix is for neural network. The output and one input name starts with **a**, that's for *activation*, which can be though of as a neuron. The weights model connections between neurons.

A completely connected neural network layer performs a matrix vector multiplication. The multiply/add operation needed to compute that is also an important operation for other compute-intensive workloads, including graphics and many forms scientific computation. General-purpose CPUs and GPUs were designed in part to perform multiply/add operations efficiently—on some workloads, including graphics and scientific computation.

One thing that sets neural network (a technique for machine-learning [ML]) workloads apart is operand precision. Graphics uses 32-bit values for coordinates, many scientific computation uses 64-bit values. Lower precision would be less effective. But machine learning can get by with less precision, and with different precision for the weights than the activations. Lower precision reduces the amount of energy needed for computation (which is often a limiter), and the amount of data that needs to be moved. This is especially important for weights in fully-connected layers.

The modules in this assignment allow for different precision for inputs, outputs, and weights. When the precision of the output is low there is a danger of overflow. That is often handled by saturating a value at the maximum representable quantity.

Reference Module, nnOxIbe

A goal of this assignment is to write a Verilog description of a module performing the same computation as a reference module, nn0xIbe. Module nn0xIbe has two inputs, an n_i -element vector of w_i -bit integers, ai, and an $n_o \times n_i$ matrix of w_w -bit integers, wht; the module has one output, an n_o -element vector of w_o -bit integers, ao, where n_i , n_o , w_i , w_w , and w_o are the values of the similarly named module parameters. All integers are unsigned. Output ao is set to the product of matrix wht and column vector ai with overflow handled as described further below.

Most will find it easiest to inspect the code in nnOxIbe (below) to resolve any remaining certainty about what this module does. For the others let $r(p) = \sum_{q=0}^{n_i-1} H_{p,q}a_i(q)$, where $H_{p,q}$ is the equivalent of the Verilog wht[p][q], and $a_i(q)$ is the equivalent of ai[q]. Then either

 $a_o(p) = \min\{r(p), 2^{w_o} - 1\}$ or $a_o(p)$ is set to the low w_o bits of r(p), depending on the value of parameter sat.

Module nn0xIbe initially computes a 32-bit precision value (see variable acc) for each ao[i]. If sat=0 then ao[i] is assigned the low wo bits of this value. If sat!=0 then ao[i] is set to the minimum of acc and $2^{w_o} - 1$. As some may have guessed, sat is short for saturating arithmetic. (In saturating arithmetic an overflow is replaced by the maximum representable value. For example, for 4-bit unsigned integers and a saturating add: $11_2 + 1110_2 = 1111_2$.)

```
module nnOxlbe
```

```
#( int no = 4, ni = 4, wo = 10, wi = 4, ww = 5, sat = 0 )
( output logic [wo-1:0] ao[no],
    input uwire [wi-1:0] ai[ni], input uwire [ww-1:0] wht[no][ni] );
// The maximum possible value of each element of ao.
localparam logic [wo-1:0] smax = ~wo'(0);
always_comb
for ( int o = 0; o < no; o++ ) begin
    automatic int unsigned acc = 0;
    for ( int i=0; i<ni; i++ ) acc += ai[i] * wht[o][i];
    // If sat is non-zero replace a value that would overflow
    // ao[o] with the maximum value that ao[o] can hold.
    ao[o] = sat && acc > smax ? smax : acc;
end
```

endmodule

Testbench

(This part is best read after looking at Problems 1 and 2.) The testbench will instantiate sixteen (as of this writing) configurations of nnOxI. For each configuration, three sets of tests are performed, similar to the ones performed for Homework 2. A grand total of errors is printed at the end, such as Total number of errors: 660. Above that the number of errors are grouped in various ways. For example:

All Sat 0 220 errors.
All Sat 1 220 errors.
All Sat 2 220 errors.
Linear 330 errors.
Linear Sat 0 110 errors.
Linear Sat 1 110 errors.
Linear Sat 2 110 errors.
Tree 330 errors.
Tree Sat 0 110 errors.
Tree Sat 1 110 errors.
Tree Sat 2 110 errors.
Total number of errors: 660

The line reading Linear 330 errors shows the total number of errors of all configurations for which tr=0. The line Linear Sat 0 110 errors. shows the number of errors on linear modules with sat=0.

Further up specific inputs and incorrect outputs are shown. For example:

```
** Starting tests for no=3, ni=5, wo=15, wi=9, ww=8, sat=2
Testing module Linear
```

```
** Starting test set n12 (1 outputs, 2 inputs) for Linear **
Error test # 0, output 0: z != 32767 (correct)
Error test # 1, output 0: z != 32767 (correct)
Error test # 2, output 0: z != 26759 (correct)
Done with 10 n12 tests on Linear: 10 errors found.
```

In the example above output ao[0] was z (unconnected) but should have been 32767.

In test set n12 the inputs and weights are chosen so that the only non-zero output should be ao [0] and so that only ai [0] and ai [1] are non-zero. In set n1* all inputs can have non-zero values but weights are chosen so that only ao [0] is non-zero. In test set n** all inputs can be non-zero and all outputs can be non-zero.

Problem 1: Complete module nnOxI so that it produces the same output as nnOxIbe and does so using generate statements to either describe a linear or recursive module as described below.

Module nn0xI is to be the starting point in all cases. It has the same parameters as nn0xIbe, plus it also has a parameter tr. The solution to this problem requires modification to nn0xI and to module nn1xI. Both are in hw03.v.

Multiplication and addition of values should be performed by instances of the provided arithmetic modules, nnAdd, nnMult, and nnMADD (multiply/add). These modules can perform saturating arithmetic.

Module nnOxI should instantiate no (that's a number) nn1xI modules. Each nn1xI instance should compute one output of nnOxI. The tr parameter in nnOxI indicates whether each nn1xI should compute its output using a linear arrangement of modules or a tree arrangement.

For the linear arrangement nn1xI should use a generate loop to instantiate nnMADD modules. The critical path (without optimization) should be $O(n_i)$ multiply/add operations. For the tree arrangement nn1xI should either instantiate two copies of itself or for the base case, the arithmetic modules.

For an example of a module describing a linear arrangement of hardware see min_n in the generate/elaborate lecture code, https://www.ece.lsu.edu/koppel/v/2020/1025-gen-elab.v.html. For an example of a module describing a tree arrangement of hardware see min_t in the lecture code.

Be sure to specify the appropriate parameters when instantiating modules, including the **sat** parameter.

- Do not make ports wider than they need to be.
- Make sure that the modules pass all tests.
- Make sure that the module is synthesizable. (Use command genus -files syn.tcl to synthesize.) The area should be > 0.
- Code should be clearly written.

Problem 2: Module nnOxIbe honors the sat parameter after it has computed a 32-bit ao[o] value. (That is, it first computes a 32-bit result, then it checks if it's too large.) That's fine for software, but it would be wasteful for our hardware because we'd need to provide 32-bit precision

hardware for all arithmetic. Or is it really that wasteful? First, we don't necessarily need 32 bits. The maximum value of ao[o] depends on wi, ww, and ni, so we only need enough bits to hold that. Also, the saturating arithmetic modules may be inflating cost for two reasons: the cost of detecting and handling saturation, and the fact that algebraic optimizations are impeded when saturation is performed. So, it may be less expensive to compute a value for ao[o] to a precision greater than wo, and then just saturate that value. This way saturation is performed once per output, rather than ni times.

Modify your modules so that when **sat=2** saturation is performed as described above.

LSU EE 4755 Homework 4 Due: 28 October 2020

Dependence of the second secon

This assignment refers to the solution to Homework 3. Pieces are shown below, the complete solution can be found at https://www.ece.lsu.edu/koppel/v/2020/hw03-sol.v.html and in the directory where the original assignment was copied from.

Problem 1: Using the simple model compute the cost and delay of the nnAdd module from Homework 3 (shown below) for both sat=0 and sat=1. Do so after applying optimizations for constants. Show the cost and delay in terms of w. Hint: See the simple model notes, https://www.ece.lsu.edu/koppel/v/2020/lsli-simple-model.pdf, for the cost of a ripple adder.

- Show cost and delay in terms of w.
- Don't forget to optimize for constant values.
- Assume that the adder will be implemented using a ripple circuit.
- Indicate both the delay of the least-significant bit of the sum and the delay of the most significant bit of the sum. Answering this part correctly and applying it to the other problems in this assignment will reveal something important about the impact of detecting overflow and of the different methods of doing so.

There are more problems on the next pages.

Problem 2: Using the simple model compute the cost and delay of the nnMult module from Homework 3 for sat=1. Let w denote the setting of both wa and wb (they are to be set to the same value), and let y denote the setting of wp. Solve this for y < 2w. Do so after applying optimizations for constants.

Solve this using the following cost for an unsigned integer multiplier with two w-bit inputs and a 2w-bit output: the cost using the simple model is $10w^2 u_c$ and the delay is $[8w + 2] u_t$ for the complete product and $[4i + 2] u_t$ for bit position *i*. (The LSB is at position i = 0.) (For more details on how those were derived see the comments after the Linear Multiplier in https://www.ece.lsu.edu/koppel/v/2020/mult-seq.v.html.)

- Show the cost and delay in terms of w and y.
- Solve this for y < 2w.
- Don't forget to optimize for constant values.

```
module nnMult #( int wa = 5, wb = 6, wp = wa + wb, sat = 0 )
  ( output uwire [wp-1:0] p, input uwire [wa-1:0] a, input uwire [wb-1:0] b );
  localparam logic [wp-1:0] pmax = ~wp'(0);
  localparam int wmx = wp > wa+wb ? wp : wa+wb;
```

```
uwire [wmx-wp:0] phi;
uwire [wp-1:0] plo;
```

assign {phi,plo} = a * b; assign p = sat && wp < wa + wb && phi ? pmax : plo;</pre>

endmodule

There are more problems on the next pages.

Problem 3: Using the simple model determine the cost and performance of module nn1xI (shown on the next page) for the configurations described below. In all cases, let *n* denote the value of ni, *w* denote the value of ww and wi (which are the same) and *y* denote the value of wo. Assume the same hardware costs as the first two problems (modifying sizes and accounting for cascading where appropriate).

(a) Find the cost (not delay in this part) for sat=0, tr=0, and y > 2w (that's one configuration) and for sat=0, tr=1, and y > 2w (that's a second configuration). The two costs will be very similar.

• Show the costs in terms of n, w, and y.

(b) Find the delay (not cost in this part) for sat=0, tr=0, and y > 2w (that's one configuration) and for sat=0, tr=1, and y > 2w (that's a second configuration). The two delays will be very different.

- Show the delays in terms of n, w, and y.
- When computing the total delay don't forget to take into account the time that inputs arrive at each port, especially for the multiplier.
- When computing total delay account for cascading of ripple units.

(c) Find the delay for sat=1, tr=0, and y > 2w (that's one configuration) and for sat=1, tr=1, and y > 2w (that's a second configuration). The two delays should be very different from each other and from the delays from the previous problem.

```
module nn1x1 #( int wo = 10, wi = 4, ww = 5, ni = 2, tr = 0, sat = 0 )
   ( output uwire [wo-1:0] ao,
     input uwire [wi-1:0] ai[ni],
     input uwire [ww-1:0] wht[ni] );
  if ( tr ) begin
      if ( ni == 1 ) begin
         nnMult #(wi,ww,wo,sat) mult(ao, ai[0], wht[0] );
      end else begin
         localparam int nlo = ni / 2;
         localparam int nhi = ni - nlo;
         uwire [wo-1:0] aolo, aohi;
         nn1xI #(wo,wi,ww,nlo,1,sat) nnlo(aolo, ai[0:nlo-1], wht[0:nlo-1]);
         nn1xI #(wo,wi,ww,nhi,1,sat) nnhi(aohi, ai[nlo:ni-1], wht[nlo:ni-1]);
         nnAdd #(wo,sat) add(ao,aolo,aohi);
      end
  end else begin
      uwire [wo-1:0] s[ni-1:-1];
      assign s[-1] = 0;
      assign ao = s[ni-1];
      for ( genvar i = 0; i < ni; i++ )</pre>
        nnMADD #(ww,wi,wo,sat) madd( s[i], wht[i], ai[i], s[i-1] );
   end
endmodule
module nnMADD #( int wa = 10, wb = 5, ws = wa + wb, sat = 0 )
   ( output uwire [ws-1:0] so,
     input uwire [wa-1:0] a, input uwire [wb-1:0] b, input uwire [ws-1:0] si);
  uwire [ws-1:0] p;
  nnMult #(wa,wb,ws,sat) mu(p, a, b);
  nnAdd #(ws,sat) ad(so, si, p);
```

endmodule

There are even more problems on the next pages.

endmodule

Problem 4: Consider module nn0xI instantiated with no=1, tr=0, for both sat=1 and sat=2. (A slightly simplified version appears below.) Let n denote the value of ni, w denote the value of wi and ww (which are the same), and let y denote the value of wo.

Assume that $2w < y < \lceil \lg n(2^w - 1)^2 \rceil$. That is, y is large enough so that the multipliers can't overflow but not so large that the adders can't overflow.

(a) Compute the cost and delay for both the sat=1 and sat=2 cases. For sat=1 just re-use answers from the previous problems.

- Show answers in terms of n, w, and y.
- Don't forget that the value of wo in the nn1xI instantiations depends upon sat.

(b) In terms of the costs computed above is **sat=2** always better, always worse, or sometimes better than **sat=1**? Be specific of course.

```
module nnOxI #( int no = 4, ni = 2, wo = 10, wi = 4, ww = 5, tr = 0, sat = 0 )
   ( output uwire [wo-1:0] ao[no],
     input uwire [wi-1:0] ai[ni],
                                    input uwire [ww-1:0] wht[no][ni] );
  // Compute number of bits to represent largest possible value that
  // can appear on an ao.
  localparam int wr = $clog2((2**wi - 1) * (2**ww - 1) * ni);
  if ( sat < 2 ) begin
      for ( genvar i = 0; i < no; i++ )</pre>
        nn1xI #(wo,wi,ww,ni,tr,sat) row( ao[i], ai, wht[i] );
  end else begin
      for ( genvar i = 0; i < no; i++ ) begin</pre>
         uwire [wr-1:0] ar;
         nn1xI #(wr,wi,ww,ni,tr,0) row( ar, ai, wht[i] );
         assign ao[i] = ar[wr-1:wo] ? ~wo'(0) : ar[wo-1:0];
      end
   end
```

Problem 5: Zero points will be given for the answer to this question, but please try your very best to answer it. Suggest a method of saturating **ao** that avoids the extra **wo** bits needed (for nn1xI) when sat=2 but also avoids the critical-path-killing saturation logic used when sat=1. Your solution could add extra ports to all modules except nn0xI. A correct solution would detect overflow under the same conditions as nn0xI does with sat=1.

LSU EE 4755 Homework 5 Due: 3 December 2020

Dependence of the second secon

Problem 1: Complete 2019 Final Exam Problem 2, which asks for a timing analysis of a best_match module, and related questions.

Problem 2: Complete 2019 Final Exam Problem 3, in which code implementing an illustrated module is to be completed. The module computes a Fibonacci sequence. Submit your solution by E-mail, handwritten is acceptable. However, those wishing to write Verilog code and to use a testbench can copy /home/faculty/koppel/pub/ee4755/hw/2020/hw05 to class account and solve it. Instructions for remote access are in https://www.ece.lsu.edu/koppel/v/proc.html (look for the "Remote Access" heading).

6 Fall 2019

LSU EE 4755 Homework 1 Due: 18 September 2019

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2019/hw01.v.html.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account, copy the assignment, and run the Verilog simulator and synthesis program on the unmodified homework file, hw01.v. Do this early enough so that minor problems (*e.g.*, password doesn't work) are minor problems.

Homework Overview

In class you were told that for common operations, such as shifting, addition, and multiplication, it's better to use Verilog operators in procedural code than to re-invent the wheel by writing Verilog to implement those operations. This point was made when covering the shift module in the introductory lectures. For example, if you need a shifter it's better to just use the shift operator: module shift_right_operator

```
( output uwire [15:0] shifted,
    input uwire [15:0] unshifted, input uwire [3:0] amt );
    assign shifted = unshifted >> amt;
    dredule
```

endmodule

than to write code for your own shifter:

module shift_right_logarithmic

endmodule

The reason for showing the implementation of shifters, and other common operations, was to teach general design concepts using operations that you should be familiar with. That will be the approach in this homework, in which a multiplier is to be implemented.

Testbench Code

The testbench for this assignment, which can be run when visiting the file in Emacs in a properly set-up account by pressing F9, tests the multiply modules. Modules mult_operator and mult16 should pass, mult16_tree awaits your solution. A sample of the end of the testbench output appears below:

```
Starting testbench...
Error in mult16_tree test 0: xxxxxxxx != 00000001 (correct)
Error in mult16_tree test 1: xxxxxxxx != 00000002 (correct)
Error in mult16_tree test 2: xxxxxxxx != 00000020 (correct)
Error in mult16_tree test 3: xxxxxxxx != 00000020 (correct)
```

```
Error in mult16_tree test
                                 xxxxxxxx != 139dff24 (correct)
                             4:
Error in mult16_tree test
                                 xxxxxxxx != 4839cb7b (correct)
                             5:
Mut mult_operator ,
                        0 errors (0.0% of tests)
Mut mult16_flat
                        0 errors (0.0% of tests)
Mut mult16_tree
                   , 1000 errors (100.0% of tests)
Memory Usage - 38.6M program + 154.6M data = 193.2M total
CPU Usage - 0.0s system + 0.0s user = 0.1s total (70.4% cpu)
Simulation complete via $finish(2) at time 10 US + 0
./hw01.v:218
                   $finish(2);
```

ncsim> exit

A count of the number of tests and errors is shown for three modules. The testbench shows the first six errors it finds on each module. To see more than six modify the testbench (search for err_limit). In the output above the testbench is showing that the module outputs are x (uninitialized) which of course don't match the expected outputs.

Use Simvision to debug your modules. Feel free to modify the testbench so that it presents inputs that facilitate debugging.

Synthesis

The synthesis script, syn.tcl, will synthesize the three modules each with two delay targets, an easy 10 ns and a un-achievable 0.1 ns. If the module doesn't synthesize -.001 s is shown for the delay. The script is run using the shell command genus -files syn.tcl, which invokes Cadence Genus.

The synthesis script shows area (cost), delay, and the delay target in a neat table. Additional output of the synthesis program is written to file **spew.log**. Sample synthesis script output appears below:

Problem 1 on next page.

 $\leftarrow \rightarrow$ Homework 1

Problem 1: The illustration to the right shows a sketch of a multiplier, mult16, with two 16-bit inputs and a 32-bit output. The multiplier is constructed from mult2 modules, shifters (<<), and adders. The illustrated module is similar to the multiplier in mult16_flat in hw01.v. The mult2 modules have two inputs, one is two bits, the other is 16 bits. Each input holds an unsigned integer. The output, 18 bits, is the product of the two inputs. Notice that each mult2 module is connected to two bits of a and all bits of b. The outputs of the mult2 modules are shifted and added together in such a way that **prod** is the correct product of a and b.

There are two parts of mult16 surrounded by green boxes. The upper one, labeled 16b by 4b, contains two mult2 modules. The label is explaining that the boxed material multiplies a 16-bit number by a 4-bit number. A similar box could have been put around the next pair of mult2 modules, etc.



The hardware within each of these four boxes would be identical. (The bit slices at the upper mult2 inputs, such as 1:0 and 5:4 are different, but that can be taken care of outside the green box.) Think about the poor soul who might have just typed in all the Verilog for mult16 and then suddenly realizes this. All that person would have had to do would be to code one module, call it mult4_tree, and just instantiate it four times. Here is an almost empty version of mult4_tree:

module mult4_tree

```
( output uwire [0:0] prod, // Need to change output size.
input uwire [3:0] a, input uwire [15:0] b );
mult2 mlo( /* finish */ );
mult2 mhi( /* finish */ );
```

endmodule

Alert students might suspect that we don't actually instantiate mult4_tree four times because the 16b by 8b section itself could be a module which would contain only two instantiations of mult4_tree. That would be correct.

Modify modules mult16_tree, mult8_tree, and mult4_tree found in hw01.v so that they implement the multiplier described above. Module mult16_tree must instantiate exactly two mult8_tree modules, module mult8_tree must instantiate exactly two mult4_tree modules, and

mult4_tree must use the two mult2 modules that are already instantiated (but with the ports missing).

In each module use implicit structural code or behavioral code to combine the outputs of that module's two instantiated modules. It might be helpful to look at mult16_flat for examples of instantiation and implicit procedural code.

Start with module mult16_tree. You can test your changes to mult16_tree by putting placeholder code in mult8_tree, such as assign prod = a*b;. Don't forget to change the port sizes on mult8_tree to what they should be based on the diagram.

Once the testbench reports zero errors move the placeholder to mult4_tree and complete mult8_tree. Continue until the three modules are finished.

Some of the port sizes are set to 1 bit, [0:0]. Those are placeholders, change those to the correct sizes, but no larger. Credit will be deducted for oversized ports, especially if all ports are made 32 bits.

Pay attention to port-size warnings when running the simulator.

Problem 2: The synthesis script will synthesize mult16_tree from Problem 1, plus two already working modules, mult16_flat and mult_operator, which just uses the multiply operator.

If the synthesis program were perfect then all three modules would have the same cost and delay because they each do exactly the same thing (multiply) and so the optimization algorithms would have found the same lowest-cost circuit from each one. Spoiler alert: Genus is not perfect.

Guess which module you think will be the fastest or least expensive, and explain why. Then run the synthesis script and comment on whether the results met your expectations.

LSU EE 4755

Homework 2 Due: 8 October 2019

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2019/hw02.v.html.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account, copy the assignment, and run the Verilog simulator and synthesis program on the unmodified homework file, hw02.v. Do this early enough so that minor problems (*e.g.*, password doesn't work) are minor problems.

Homework Correction (December 2019)

When assigned in October 2019 this assignment defined clz backward, starting at the least-significant bit. That has been corrected in this version and in the posted code.

Homework Overview

A count leading zeros (clz) operation returns the number of consecutive zeros starting at the most significant bit of an integer's binary representation. For example, the clz of 00101_2 is 2, the clz of 101_2 is 0, and the clz of 32-bit number 0_2 is 32. The Verilog module below computes the clz of its input:

```
module Clz
```

```
#( int w = 19, int ww = $clog2(w+1) )
  ( output var logic [ww-1:0] nlz, input uwire logic [w-1:0] a );
  uwire [w:0] aa = { a, 1'b1 };
  always_comb for ( int i=0; i<=w; i++ ) if ( aa[i] ) nlz = w-i;
endmodule</pre>
```

The module was written as behavioral code, but it does turn out to be synthesizable. Nevertheless, one may wonder if the synthesis program will do a good job with this. (Later in the semester we will learn what kind of hardware will be inferred for the description above.) One way to find out is to design a module which *should* be efficient and see how well it compares to what the synthesis program does with the module above. That, and the use of generate statements, is the subject of this assignment.

Testbench Code

The testbench for this assignment, which can be run when visiting the file in Emacs in a properly set-up account by pressing F9, tests the clz_tree module at several different widths. All should initially fail. A shortened sample of the testbench output appears below:

```
ncsim> run
** Starting tests for width 1.
Error for width 1: input 1: z != 0 (correct).
Error for width 1: input 0: z != 1 (correct).
Error for width 1: input 1: z != 0 (correct).
Error for width 1: input 0: z != 1 (correct).
Width 1, done with 10 tests, 10 errors.
** Starting tests for width 2.
Error for width 2: input 3: z != 0 (correct).
Width 2, done with 20 tests, 20 errors.
** Starting tests for width 5.
```

```
[snip]
Error for width 17: input 08959: z != 0 (correct).
Width 17, done with 170 tests, 170 errors.
ncsim: *W,RNQUIE: Simulation is complete.
ncsim> exit
Total number of errors: 610
```

The testbench prints the details of the first four errors it finds, and after that prints just one detail time per width. A total for each width and a grand total are printed, see the transcript above.

Use Simvision to debug your modules. Feel free to modify the testbench so that it presents inputs that facilitate debugging.

Synthesis

The synthesis script, syn.tcl, will synthesize clz (for reference) and clz_tree (your solution). Each module will be synthesized at three widths, and with two delay targets, an easy 10 ns and a un-achievable 0.1 ns. If a module doesn't synthesize -.001 s is shown for its delay. The script is run using the shell command genus -files syn.tcl, which invokes Cadence Genus. If you would like to synthesize additional modules or sizes edit syn.tcl near the bottom.

The synthesis script shows area (cost), delay, and the delay target in a neat table. Additional output of the synthesis program is written to file spew.log.

Problem 1: Complete module clz_tree so that it computes the clz of its input in a tree-like fashion. For the non-terminal case it should instantiate two clz_tree modules and each should operate on part of the input, a. The outputs of these two modules should be appropriately combined. To help you get started, a recursive solution to Homework 1, mult_tree, is in hw02.v.

An easy mistake to make is using the wrong sized variable in a module port connection. Previously the Verilog software (ncelab to be precise) would issue a warning which was easy to miss. Now a port size mismatch is a fatal error.

For maximum credit do not use adders in your design. Adders can be avoided if the size of the low module is always a power of 2.

See the Verilog code check boxes for additional items to check for.

Problem 2: Run the synthesis program and indicate how your module compares to the behavioral module, clz. Indicate which results are expected, and which are not expected, and explain why.

LSU EE 4755

Homework 3

```
Due: 23 October 2019
```

Problem 1: Appearing below is a module excerpted from the solution to Homework 1. Compute the cost and delay of this module using the simple model under the following assumptions:

- The inputs arrive at t = 0. Don't assume that any bit is early or late, they all arrive at exactly t = 0.
- A ripple adder will be used to implement addition.
- Apply obvious optimizations. In particular, don't use a BFA if a BHA would suffice. And only use a BHA if that is needed.
- Don't overlook the fact that one of the shifter inputs is a constant.

Show the cost and delay in terms of wa and wb, but use symbol a for wa and b for wb. For example, "The cost is $(a + b)9 u_c$ and the delay is $(a + b)2 u_t$." (Those answers assume that BFAs are used for the entire module, which is wrong.)

The simple model slides (AOTW) don't show the cost and delay of a BHA, so work that out yourselves.

endmodule

There's another problem on the next page!

Problem 2: A *w*-bit multiplier needs to add together *w* partial products using w - 1 adders. A naïve timing analysis of a non-tree ripple adder implementation would compute a delay of $w(2 \times 2w + 2) = (4w^2 + w)u_t$ for the 2*w*-bit product using the simple model and ignoring ripple-unit cascading. As we should know $4w^2$ is not a good term to have in an expression for time. The goal of this problem is to see how the tree multiplier compares to this naïve timing.

Appearing below is the Bonus Solution to Homework 1 in which a single mult_tree module is used rather than separate modules mult16_tree, mult8_tree, etc. Also shown is a module, my_module that instantiates the mult_tree. Also shown a page or two ahead is the diagram from Homework 1. You may want to use this to help work out the solution to this problem.

Analyze the cost and performance of my_module as described below. When computing the cost and performance don't forget to account for the full elaboration, not just the top level. For example, my_module with w=4 consists of one mult_tree at w=4 and two mult_tree modules at w=2, and four mult_tree modules at w=1.

```
module mult tree
  #( int wa = 16, int wb = 16, int wp = wa + wb )
   ( output logic [wp:1] prod,
     input uwire [wa:1] a,
     input uwire [wb:1] b );
  if (wa == 1) begin
      assign prod = a ? b : 0;
      // Equivalent to: prod = a * b;
  end else begin
      // Split a in half and recursively instantiate a module for each half.
      localparam int wn = wa / 2;
      localparam int wx = wb + wn;
      uwire [wx:1] prod_lo, prod_hi;
      mult_tree #(wn,wb) mlo( prod_lo, a[wn:1], b );
      mult_tree #(wn,wb) mhi( prod_hi, a[wa:wn+1], b );
      // Combine the partial products.
      always_comb prod = prod_lo + ( prod_hi << wn );</pre>
   end
endmodule
module my module
  \#( int w = 8, int wp = 2 * w )
   ( output uwire [wp-1:0] p,
     input uwire [w-1:0] x, y );
  mult_tree #(w,w) mt1(p,x,y);
```

```
endmodule
```

(a) Compute the cost of my_module using the same assumptions as in Problem 1. The cost must

be in terms of w. It's okay, indeed encouraged, to use sample values like w = 16 when working out the problem, but once you have it figured out give the answer in terms of w. (If you have not solved Problem 1 then use the incorrect sample answers provided in Problem 1.)

The following identity may be helpful: $\sum_{i=0}^{m-1} 2^i = 2^m - 1$. In such a summation *i* might indicate the level of recursion and 2^i might indicate the number of modules at that recursion level. For the top level of the recursion i = 0.

(b) Compute the delay of the multiplier using a simplifying assumption similar to the one used in Problem 1: when computing the delay of prod = prod_lo + (prod_hi << wn) assume that all bits for prod_lo and prod_hi arrive at the same time and that all bits of prod are sent to the outputs at the same time. (Don't like simplifying assumptions? The next subproblem is for you!)

Show your answer for w=8 and as an expression in terms of w. Don't forget to consider the entire elaboration, not just the top-level module.

(c) Compute the delay of the multiplier without the simplifying assumption. That is, account for the fact that the less-significant bits of $mult_tree$ will be ready before the more-significant bits.

Show your answer for w=8 and as an expression in terms of w. Don't forget to consider the entire elaboration, not just the top-level module.

Useful diagram on next page.



Use the diagram below to help work out solutions.

LSU EE 4755 Homework 4 Due: 11 November 2019

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2019/hw04.v.html.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account (if for whatever reason you haven't done so or neeed to do it again), copy the assignment, and run the Verilog simulator and synthesis program on the unmodified homework file, hw04.v. Do this early enough so that minor problems (*e.g.*, password doesn't work) are minor problems.

Homework Overview

Module best_match_behavioral has two inputs, a longer vector, val, and a short vector, k. It sets pos to the start of a subvector of val that best matches k and sets err to the number of bit positions that don't match. For example, suppose val = 8'b11110000 and k=4'b1100. Then pos would be set to 2 and err to 0 because there is an exact match at position 2 in val. If k=4'b1101 then there isn't an exact match for k in val, but at position 2 there is a match with one error. If k=2'b00 then there are matches at positions 0, 1, and 2, all with zero errors.

Module **best_match_behavioral** is combinational (and was written as a behavioral module). In this assignment a sequential version will be written and analyzed.

Testbench Code

The testbench for this assignment, which can be run when visiting the file in Emacs in a properly set-up account by pressing [F9], tests the modules. Initially, the testbench will exit because module best_match has not responded in sufficient time. When that happens one of the last lines of the testbench output shows that the final cycle count is the same as the cycle limit (128 below), and "CYCLE LIMIT EXCEEDED" is shown.

```
ncsim> run
Exit from clock loop at cycle 128, limit 128. ** CYCLE LIMIT EXCEEDED **
ncsim: *W,RNQUIE: Simulation is complete.
ncsim> exit
```

Compilation finished at Mon Nov 4 17:56:24

To get rid of this message best_match must handshake correctly, see Problem 1. If best_match responds in time, the testbench will check to see if pos is in the right range. The output below shows errors when pos is out of range: Error in best_match, test # 3, pos out of range: 0xff

```
Error in best_match, test # 4, pos out of range: 0xff
Done with best_match_behavioral tests, 0 errors found.
Done with best_match tests, 1000 errors found.
Exit from clock loop at cycle 59001, limit 59069.
ncsim: *W,RNQUIE: Simulation is complete.
ncsim> exit
```

The output err is supposed to be the number of non-matching bits at **pos**. If not, the testbench shows output like:

```
Error in best_match, test #2, err wrong 1 != 3 (correct) pos284 ^ 01Error in best_match, test #3, err wrong 1 != 2 (correct) pos131f ^ 3dError in best_match, test #4, err wrong 1 != 2 (correct) pos478 ^ f9Done with best_match_behavioral tests,0errors found.
```

Done with best_match tests, 972 errors found. Exit from clock loop at cycle 59001, limit 59069. ncsim: *W,RNQUIE: Simulation is complete. ncsim> exit

For test # 4, the testbench reports that err was 1 but should have been 2. The line also shows that pos was set to 4, and that val at that position was 78 (in hexadecimal) and that k=f9.

The testbench also checks whether the ${\tt err}$ returned is the minimum error for that value of val and k.

The testbench prints the details of the first few errors it finds. A grand total is printed at the end, see the transcript above.

Use Simvision to debug your modules. Feel free to modify the testbench so that it presents inputs that facilitate debugging.

Synthesis

The synthesis script, syn.tcl, will synthesize best_match_behavioral (for reference) and best_match (your solution). Each module will be synthesized at three widths, and with two delay targets, an easy 90 ns and a un-achievable 0.1 ns. If a module doesn't synthesize -.001 s is shown for its delay. The script is run using the shell command genus -files syn.tcl, which invokes Cadence Genus. If you would like to synthesize additional modules or sizes edit syn.tcl near the bottom.

The synthesis script shows area (cost), delay, and the delay target in a neat table. Additional output of the synthesis program is written to file spew-file.log.

Problem 1: Complete module best_match so that it computes the best match sequentially as described below. In addition to val and k, the module has 1-bit inputs start and clk and 1-bit output ready.

Handshaking works as follows: When start=1 at a positive edge the module should set ready to zero. It should then start scanning for the best match, checking one shifted position per cycle. The maximum number of cycles needed should be wv-wk plus one or two more needed for handshaking. (The testbench will wait 2*wv cycles before giving up.) The module should set err and pos to their correct values and ready to 1.

The inputs, val and k will be held steady at least until ready is set to 1.

The module must use the pop (population) module (in hw04.v) to compute possible values for err. That is, don't use something like the b loop in best_match_behavioral to accumulate the sum e. Instead compute the XOR of the appropriate bit range and provide that to the pop module as an input.

For maximum credit avoid the use of large (such as wv-input) multiplexors in your design, or the use of a non-constant shifter.

The module must be synthesizable and correct.

The behavioral best match module is shown below for reference.

module best_match_behavioral

```
#( int wv = 32, int wk = 10, int wvb = $clog2(wv), int wkb = $clog2(wk+1) )
( output logic [wvb:1] pos, // Position of best match.
    output logic [wkb:1] err, // Number of non-matching bits.
    input uwire [wv-1:0] val, input uwire [wk-1:0] k );
```

always_comb begin

automatic int best_err = wk + 1; automatic int best_pos = -1;

```
for ( int p=0; p<=wv-wk; p++ ) begin
    automatic int e = 0;
    for ( int b=0; b<wk; b++ ) e += k[b] !== val[p+b];
    if ( e < best_err ) begin
        best_err = e;
        best_pos = p;
    end
end
err = best_err;
pos = best_pos;
end</pre>
```

endmodule

Problem 2: Run the synthesis program and indicate how your module compares to the behavioral module.

(a) Compare the amount of time needed for your module compared to the behavioral one. The answer to this question requires some manipulation of the values in the Delay Actual column. Indicate which results are expected, and which are not expected, and explain why.

(b) Compare the area of your design to the behavioral one. Indicate which results are expected, and which are not expected, and explain why.

LSU EE 4755

Homework 5 Due: 20 November 2019

Problem 1: Solve 2018 Final Exam Problem 3, in which the inferred hardware for a misc module is to be found (a) and the state of the event queue over time simulating misc (b) is to be found.

Problem 2: Appearing below is a solution to Homework 4 Problem 1. Show the hardware that will be inferred for this module after some optimization. Show the pop module as a box.

- Clearly show all input and output ports.
- Please don't get parameters and ports confused.

```
module best match
  #( int wv = 32, int wk = 10, int wvb = clog2(wv), int wkv = clog2(wk+1))
  ( output logic [wvb:1] pos, output logic [wkv:1] err, output logic ready,
    input uwire [wv-1:0] val, input uwire [wk-1:0] k,
                                                          input uwire start, clk );
  logic [wvb-1:0] curr_pos;
  logic [wv-1:0] sh_val;
  uwire [wkv-1:0] e;
  pop #(wk,wkv) p( e, k ^ sh_val[wk-1:0] );
  always_ff @( posedge clk )
    if ( start == 1 ) begin
       ready = 0;
       curr_pos = 0;
       sh_val = val;
       err = ~0;
    end else if ( !ready ) begin
       if ( e < err ) begin err = e; pos = curr_pos; end
       ready = curr_pos == wv - wk;
       curr_pos++;
       sh_val >>= 1;
    end
```

endmodule

LSU EE 4755

Homework 6 Due: 4 December 2019

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2019/hw06.v.html.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account (if for whatever reason you haven't done so or need to do it again), copy the assignment, and run the Verilog simulator and synthesis program on the unmodified homework file, hw06.v. Do this early enough so that minor problems (*e.g.*, password doesn't work) are minor problems.

Homework Overview

Module add_accum keeps a running total of values appearing at its inputs. A 1-bit input ai_valid indicates whether the value on w-bit input ai should be added to the total (ai_valid==1) or ignored (ai_valid==0). These signals should be examined on the positive edge of input clk. The module places a running sum of these values on output sum. The sum should be reset to 0 when input reset is 0 at a positive edge. The Verilog below implements the behavior described so far.

```
module add accum
```

```
#( int w = 20, n_stages = 3 )
 ( output logic [w-1:0] sum,
  output logic sum_valid,
  input uwire [w-1:0] ai,
  input uwire ai_valid, reset, clk );
 always_ff @ ( posedge clk )
  if ( reset ) sum = 0; else if ( ai_valid ) sum += ai;
 always_comb sum_valid = 1;
```

endmodule

A student at this point might wonder if this is going to be a dull assignment. No, of course not! Did you notice the parameter n_stages? That indicates that the module shall [I understand why shall is used instead of should in some contexts, but still it sounds too bossy to me] use a pipelined adder of n_stages stages. The point of this assignment is to modify the module above so that it uses the provided (and pre-instantiated) pipelined adder.

There are two challenges here. The straightforward challenge of connecting the pipelined input and output ports properly. Then there's the perhaps unexpected and interesting challenge of properly updating the running sum when input values arrive even while the calculation of a sum is still in the pipeline. The module has an output sum_valid that should only be set to 1 when output sum is the correct sum of all arriving valid values since the most recent reset.

After a reset sum should be set to zero and sum_valid to 1. When the first value arrives sum might change to that arriving value by the next clock cycle (no adder needed). But when the second value arrives it will be necessary to add it to the first (the current sum) and since the pipelined adder takes several cycles sum_valid will have to be set to zero while the adder is computing. If no other new values arrive before the adder is finished sum can be set to the sum and sum_valid should again be set to 1. Suppose instead that while the adder is operating on the first two values, a third value arrives? Then when the adder is finished the third value will have to be added to the just-completed sum. There is no restriction on when values can arrive. They may arrive every cycle or with large gaps between arrivals. If values arrive frequently then sum_valid may remain

0. But if values stop arriving sum_valid should eventually be set to 1 and sum should be set to the correct sum.

Testbench Code

The testbench for this assignment, which can be run when visiting the file in Emacs in a properly set-up account by pressing [F9], tests add_accum instantiated for different pipeline lengths. It will check that the output values are correct, and that they don't appear too early or too late. Initially the testbench will report that there were 0 incorrect values but that they all arrived too early. The testbench will report the first four errors of each time for each pipeline length. The error message is followed by a string describing when the module was last reset and when values have since arrived. For example:

```
At cyc 7, value ready too soon, 0, cyc. (Min cyc 8.) R(4)+42(5)+40(7)
```

This indicates that at cycle 7 the value arrived too soon, after 0 cycles instead of after a minimum of 8 cycles. (The first value can appear after 0 cycles since there's nothing to add.) The R(4) indicates that the most recent reset was in cycle 4. The +42(5) indicates that the value 42 was at the input to the module in cycle 5.

A tally of errors and other information is shown after each pipeline length:

```
Done with 6-stage tests, 10000 series.
Correct, 65271; errors : 0 not done, 0 val, 45273/0 early/late.
For 6 stages average latency 0.15 cycles.
```

The number after correct was the number of correct values found. To the left of "not done" is the number of tests skipped due to unresponsiveness. The number to the left of val is the number of incorrect results. The numbers to the left of early/late indicate the number of values appearing too early (45273 in the example above) or too late (0 in the example).

The testbench enforces a minimum time for all but the first value after a reset. The minimum time, n_stages, is assigned to parameter lat_min_empty in module testbench_n. The testbench enforces two maximum times. If the module is asserting sum_valid and a new value arrives, the updated sum should appear within lat_limit_empty = n_stages + 2 cycles. (That's also a testbench parameter.) If sum_valid is 0 and a new value arrives the testbench will patiently wait lat_limit_full = 2 + (1+\$clog2(n_stages)) * (n_stages + 1) cycles. These testbench parameters can be changed to help with debugging, but they should be set back. The ta-bot will test the code using a different copy of the testbench module.

Following the error tally an average latency is shown, in this case less than 1 cycle. A low number is good so long as the pipelined adder is being used (which it isn't in the example above).

The following is output if the problem is solved correctly:

```
Starting tests for 2-stage pipeline.
Done with 2-stage tests, 10000 series.
Correct, 35763; errors : 0 not done, 0 val, 0/0 early/late.
For 2 stages average latency 3.26 cycles.
Starting tests for 3-stage pipeline.
Done with 3-stage tests, 10000 series.
Correct, 32338; errors : 0 not done, 0 val, 0/0 early/late.
For 3 stages average latency 4.64 cycles.
Starting tests for 5-stage pipeline.
Done with 5-stage tests, 10000 series.
Correct, 28774; errors : 0 not done, 0 val, 0/0 early/late.
For 5 stages average latency 7.77 cycles.
Starting tests for 6-stage pipeline.
```

```
Done with 6-stage tests, 10000 series.
Correct, 27737; errors : 0 not done, 0 val, 0/0 early/late.
For 6 stages average latency 9.48 cycles.
ncsim: *W,RNQUIE: Simulation is complete.
ncsim> exit
Total number of errors: 0
```

Use Simvision to debug your modules. Finding errors in sequential code without a debugger is time consuming and tedious. Feel free to modify the testbench so that it presents inputs that facilitate debugging.

Synthesis

The synthesis script, syn.tcl, will synthesize add_pipe (for reference) and add_accum. Each module will be synthesized at several pipeline depths, and with two delay targets, a delay-is-nothing-to-worry-about 10 ns and an unachievable 0.1 ns. If a module doesn't synthesize -.001 s is shown for its delay. The script is run using the shell command genus -files syn.tcl, which invokes Cadence Genus. If you would like to synthesize additional modules or sizes edit syn.tcl near the bottom.

The synthesis script shows area (cost), delay, and the delay target in a neat table. Additional output of the synthesis program is written to file spew-file.log.

Problem 1: Modify module add_accum so that it keeps an accumulated sum (see the intro above) using a pipelined adder. The module must be synthesizable. A pipelined adder has been instantiated and some starter solution code has been included:

```
module add_accum
```

```
#( int w = 20, n_stages = 3 )
  ( output logic [w-1:0] sum, output logic sum_valid,
    input uwire [w-1:0] ai, input uwire ai_valid, reset, clk );
  always_ff @ ( posedge clk )
    if ( reset ) sum = 0; else if ( ai_valid ) sum += ai;
```

always_comb sum_valid = 1;

/// The code above must be removed and the pipelined adder, add_p0, used instead.

```
uwire [w-1:0] aout;
uwire [w-1:0] a0 = ai; // May need other connections.
uwire [w-1:0] a1;
add_pipe #(w,n_stages) add_p0(aout,a0,a1,clk);
logic [n_stages:0] st_occ; // Indicate which stage of add_p0 is occupied.
uwire aout_valid = st_occ[n_stages-1];
always_ff @( posedge clk ) if ( reset ) begin
st_occ <= 0;
end else begin
    // Keep track of which stage of add_p0 is occupied.
st_occ[0] <= ai_valid; // Lets initially assume all values enter pipe.</pre>
```

```
// Advance other occupied signals.
   for ( int i=1; i<=n_stages; i++ ) st_occ[i] <= st_occ[i-1];
end</pre>
```

endmodule

The module above correctly computes the accumulated sum, however it does not use the pipelined adder. The pipelined adder has been instantiated and one input has been connected (though it may need to be connected to additional items).

Beneath the pipelined adder is code needed to keep track of which stages of the adder have values. Bit st_occ[i] is 1 if stage i of the adder has a valid value. Stage 0 is initialized with the module input's valid signal. Values are advanced one position per cycle. Net aout_valid is 1 if the adder output is valid, which will be true n_stages cycles after ai_valid is 1.

As described in the introduction, this problem would be easy if new values arrived at least **n_stages** cycles apart, because in that case the accumulated sum and the new value could be placed in the adder without worry. But a new value can arrive while the adder is busy with one or more computations, so the new value must be buffered until there is something to add it to, either a second new value or something emerging from the pipeline.

See the checkbox items in the Verilog code for additional items to look for. A diagram like the one below might help in solving this problem.

Cycle	0	1	2	3	4	5	6
ai_valid	1			1			
a0	ai			ai			
a1	sur	n		sum			
aout_valid	0		1	0		1	
sum			=ao		=ai		
Cycle	0	1	2	3	4	5	6

7 Fall 2018

LSU EE 4755 Homework 1 Due: 5 September 2018

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2018/hw01.v.html.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account, copy the assignment, and run the Verilog simulator and synthesis program on the unmodified homework file, hw01.v. Do this early enough so that minor problems (*e.g.*, password doesn't work) are minor problems.

Homework Overview

An *n*-input sorting network is a combinational circuit with n inputs and n outputs. The n values at the inputs appear at the outputs in sorted order. The illustration below shows a four-input sorting network with example values shown in green.



File hw01.v contains correctly functioning 2-input and 3-input sorting networks, sort2_is, and sort3. Modules sort2 and sort4 are empty and are to be completed for this assignment as described in the problems. File hw01.v contains several other modules for use in solutions, and a testbench.

Testbench Code

The testbench for this assignment, which can be run when visiting the file in Emacs in a properly set-up account by pressing F9, tests four modules: sort2_is, sort2, sort3, and sort4. Modules sort2_is and sort3 should pass, the others await your solution. A sample of the end of the testbench output appears below:

```
Mod sort2, sort 2 index 0, wrong elt
                                         z !=
                                                0 (correct)
Tests for sort2 done, errors in
                                        100 of
                                                        100 sorts.
Tests for sort2_is done, errors in
                                             0 of
                                                           100 sorts.
Tests for sort3 done, errors in
                                          0 of
                                                        100 sorts.
                                         z !=
Mod sort4, sort 0 index 0, wrong elt
                                               24 (correct)
                0 index 1, wrong elt
Mod sort4, sort
                                         z !=
                                               26 (correct)
Mod sort4, sort
                0 index 2, wrong elt
                                         z !=
                                               64 (correct)
Mod sort4, sort 0 index 3, wrong elt
                                         z !=
                                               94 (correct)
Mod sort4, sort
                1 index 0, wrong elt
                                         z !=
                                                0 (correct)
Tests for sort4 done, errors in
                                        100 of
                                                        100 sorts.
ncsim: *W,RNQUIE: Simulation is complete.
ncsim> exit
```

Compilation finished at Tue Aug 28 16:53:25

A count of the number of tests and errors is shown for four modules. The testbench shows the first five errors it finds on each module, to see more modify the testbench (search for $g_elt_err_count$). In the output above the testbench is showing that the module outputs are z (an unconnected wire) which of course don't match the expected outputs.

Use Simvision to debug your modules. Feel free to modify the testbench so that it presents inputs that facilitate debugging.

Synthesis

The synthesis script, syn.tcl, will synthesize the four modules each with two delay targets, an easy 10 ns and a un-achievable 0.1 ns. If the module doesn't synthesize -.001 s is shown for the delay. The script is run using the shell command genus -files syn.tcl, which invokes Cadence Genus. In past semesters Cadence RTL Compiler (rc) was used, which would be invoked using rc -files syn.tcl, but that won't work on the 2018 homework assignments.

The synthesis script shows area (cost), delay, and the delay target in a neat table. Additional output of the synthesis program is written to file **spew.log**. Sample synthesis script output appears below:

Problem 1: Complete module **sort2** so that it implements a 2-input sorter using a comparison unit and two 2-input multiplexors, as illustrated below. The module must pass the testbench and be synthesizable.



Use only structural code in the module (do not use assign, initial, or always blocks). Instantiate mux2 for the multiplexors and compare_le for the comparison unit. See the check boxes in hw01.v near the problem for other requirements and tips.

Problem 2: Complete module sort4 so that it implements a 4-input sorting network. Do so by instantiating sort3 and sort2 (or sort2_is) modules. As with sort2, use only structural code and make sure that the module passes the testbench and synthesizes.

For this assignment, implement sort4 using one sort3 and several sort2 modules. Use the sort2 modules to find the largest of the four inputs to sort4 and connect that largest value to output x3. Use sort3 to handle the remaining three values.

Implement sort4 to minimize the critical path (measured in sort2 or sort2_is modules). That is, minimize the maximum number of sort2 (or sort2_is) modules traversed by any signal. The critical path for sort3 is 3: from input a0, through s0_01, i11, s1_12, i21, s2_01, to output x0.

The sort3 module uses three sort2_is modules. Feel free to examine sort3 to see how modules are instantiated and interconnected.

LSU EE 4755

Homework 2 Due:

Due: 12 September 2018

Problem 1: The Verilog code below is the **sort3** module from Homework 1. Draw a diagram of the hardware as described by **sort3**, showing the **sort2** modules as boxes. Be sure to label the input and output ports with the same symbols used in the module.

```
module sort3
#( int w = 8 )
  ( output uwire [w-1:0] x0, x1, x2,
    input uwire [w-1:0] a0, a1, a2 );
  uwire [w-1:0] i10, i11, i21;
  sort2 #(w) s0_01( i10, i11, a0, a1 );
  sort2 #(w) s1_12( i21, x2, i11, a2 );
  sort2 #(w) s2_01( x0, x1, i10, i21 );
```

endmodule

Problem 2: It is possible to build an *n*-element sorting network using $\frac{n}{2} \lg^2 n$ two-element sorting networks in such a way that the *n*-element sorting network has a critical path of $\lg^2 n$. (Note: $\lg n \equiv \log_2 n$.) But this assignment is concerned with *n*-element sorting networks using n(n-1)/2 two-element sorting networks, which we will call *n*-element bad sorting networks or bad sorters for short.

An *n*-element bad sorter has inputs $a_0, a_1, \ldots, a_{n-1}$ and outputs $x_0, x_1, \ldots, x_{n-1}$. The largest value is routed to x_{n-1} .

A 2-element bad sorter is a single **sort2** module. An *n*-element bad sorter, n > 2, can be constructed using an (n-1)-element bad sorter and n-1 **sort2** modules as follows. The n-1**sort2** modules are connected to the *n* inputs and to each other in such a way that the largest value is routed to a specific output of one of the **sort2** modules. That specific **sort2** output is connected to output x_{n-1} of the *n*-element sorter. The other values connect to the (n-1)-element bad sorter, and the (n-1)-element bad sorter outputs connect to outputs $x_0, x_1, \ldots, x_{n-2}$ of the *n*-element bad sorter that we are constructing. Note that this generalizes the solution to Homework 1 Problem 2.

The description above is recursive. At level *i* (the same as *n* above) another i - 1 sort2 modules are used. For a 4-element sorter we need (4 - 1) + (3 - 1) + 1 = 6 sort2 modules. The cost of an *n*-element bad sorter is found by solving the summation $\sum_{i=2}^{n} i - 1$, which is n(n-1)/2. That's $O(n^2)$, which is how the bad sorter got its name.

It gets worse. The critical path through the bad sorter can range from bad to awful. That depends on two things: How the **sort2** modules are used to find the largest value, and how the **sort2** modules connect to the (n-1)-element bad sorter.

(a) Show the worst way that sort2 modules can be connected to find the largest value. *Hint: the critical path should be* n-1 sort2 *modules.* Provide a sketch for the general case, and an example for n = 4.

(b) Show the worst way that the sort2 modules, as connected above, can connect to the (n-1)-element sorter. Provide a sketch.

(c) Determine the critical path for an n-element bad sorter constructed in the way described in the last two parts. *Hint: The math part should be familiar.*

(d) Show a much better way of connecting the **sort2** modules to find the largest value. It should be easy to show that the critical path is the lowest that is possible. Provide a sketch for n = 8.

The problem with the approach to building the bad sorters described in this assignment is that each level in the recursion reduces the size by 1 (that is, from n to n - 1), and so the critical path must be at least O(n). As some students may have realized, a better approach would be to use recursion in which the n inputs were split between two $\frac{n}{2}$ -element networks and then somehow combined. But how? The key insight, described by K. E. Batcher in a landmark 1968 paper, is not to try to recursively describe a sorting network, but to instead recursively describe a network that merges two already sorted sequences. The input to a 2-element merge network would be two 1-element sorted sequences. (Of course, every 1-element sequence is sorted.) Pairs of 2-element merge networks feed a 4-element merge network, and so on. This will be further described later in the semester.

LSU EE 4755

Homework 3 Due: 25 September 2018

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2018/hw03.v.html.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account, copy the assignment, and run the Verilog simulator and synthesis program on the unmodified homework file, hw03.v.

Homework Overview

The sorting networks from Homework assignments 1 and 2 sorted keys only, and they only sorted unsigned integer keys. In this assignment sorter inputs will consist of keys and data, and those keys can be signed integers or floating-point values. The only module to be modified for this assignment is **sort2**.

Module sort2 has two inputs, a0 and a1, and parameters w, k, exp, and sig. Parameter w is the total size of each input, k is the size of the key, exp is size of the exponent (for FP keys) and sig is the size of the significand (for FP keys). All sizes are in bits. Each input consists of data, in bit positions w-1:k+1, a key type, in bit position k, and a key, in bit positions k-1:0. If bit k is zero the key is a signed integer in 2's complement representation. If bit k is one the key is a FP value in a format similar to IEEE 754: Bit k-1 is the sign, bits k-2:sig are the exponent, and bits sig-1:0 are the significand. For a description of these fields see the floating-point modules in the ChipWare documentation (linked to the course references page, https://www.ece.lsu.edu/koppel/v/ref.html, and also linked to the HTMLized assignment code, https://www.ece.lsu.edu/koppel/v/2018/hw03.v.html). Also see the fp_to_val function in the testbench code, this function converts this floating-point representation to a value.

In the unmodified file the **sort2** module compares the inputs as unsigned integers. This is wrong because the high bits of each input are data, not the keys. The **mux** connections are correct because each input should be sent to the appropriate output unmodified. The solution to the problems below involve setting **c** (the mux select signal) to the correct value.

Testbench Code

The testbench for this assignment, which can be run when visiting the file in Emacs in a properly set-up account by pressing F9, tests module sort2 at two different sizes and using a mix of input types. It first tries integer-only keys (labeled ii in the output), then floating-point only keys (labeled ff), and finally integer/FP keys (labeled if). It reports the first five errors of each type, and for each module size reports a tally by type.

Here is a transcript showing the start of the testbench (after the compiler's own messages):

The transcript above shows two errors, both for integer key pairs. The first line shows the actual output followed by the correct output (labeled correct). The number before error is a
test number, these start at zero and go up to num_tests-1 (see the testbench code). The next two lines show the input values broken into data and key, including the value and representation details. The last line of each error report has text that can be put into the testbench code so that particular test can be re-run as one of the first tests.

The testbench tests the **sort2** module at two sizes. At the end of the code for each is a tally of the number of errors:

Done with 3000000 tests for k=16, exp=6: 499679 ff errs, 499666 if errs, 499400 ii errs,

In the sample above there are many errors for each type of test. Here is the output when all tests pass:

Starting testbench for w=32, k=16, exp=6 sig width=9... Done with 3000000 tests for k=16, exp=6: 0 ff errs, 0 if errs, 0 ii errs, Starting testbench for w=24, k=14, exp=5 sig width=8... Done with 3000000 tests for k=14, exp=5: 0 ff errs, 0 if errs, 0 ii errs,

All done.

Debugging

To debug your code identify an error that looks easy to figure out and copy the text to the right of paste: into the testbench_size module near the comment Add tests below. Also change the value of num_tests to a small number, say 3. (Don't forget to change it back!) Verify that the code fails on test 0 (or some other small number). Next, run SimVision: irun -gui hw03.v. Locate your module (it will be under t1 or t2) and copy symbols from s2 to the waveform viewer. See the SimVision instructions on the https://www.ece.lsu.edu/koppel/v/proc.html page.

Synthesis

The synthesis script, syn.tcl, will synthesize sort2 with two delay targets, an easy 10 ns and a unachievable 0.1 ns. If the module doesn't synthesize -.001 s is shown for the delay. The script is run using the shell command genus -files syn.tcl, which invokes Cadence Genus. In past semesters Cadence RTL Compiler (rc) was used, which would be invoked using rc -files syn.tcl, but that won't work on the 2018 homework assignments.

The synthesis script shows area (cost), delay, and the delay target in a neat table. Additional output of the synthesis program is written to file **spew.log**. Sample synthesis script output appears below:

Problem 1: Complete module sort2 so that it correctly sorts inputs with signed integer keys. Avoid unnecessarily costly or slow designs.

Problem 2: Complete module sort2 so that it also correctly sorts inputs with floating-point keys. Instantiate at least one ChipWare module, it's okay to use more. When adding ChipWare modules be sure to put in an include directive at the end of the file. Avoid unnecessarily costly or slow designs.

Problem 3: Complete module **sort2** so that it also correctly sorts inputs when one key is a signed integer and the other is floating point. Avoid unnecessarily costly or slow designs. Try to avoid solutions that use a larger significand than is specified by the parameters or other brute-force approaches.

Homework 4

Due: 3 October 2018

Problem 1: Solve 2017 Final Exam Problem 3, in which the cost and delay of two alternative designs are to be compared.

LSU EE 4755 Homework 5 Due: 12 October 2018

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2018/hw05.v.html.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account, copy the assignment, and run the Verilog simulator and synthesis program on the unmodified homework file, hw05.v.

Homework Overview

The sorting networks used in past assignments were not very efficient, they were the rough hardware equivalent of bubble sorts. In this assignment much better sorters will be implemented, sorting networks based on Batcher's odd/even merge design.

Testbench Code

The testbench for this assignment, which can be run when visiting the file in Emacs in a properly set-up account by pressing F9, tests module batcher_sort and batcher_merge at several different sizes.

Here is a transcript showing the output of the testbench (after the compiler's own messages):

```
ncsim> run
```

```
Starting testbench.
```

```
Mod batcher_merge, n=2, sort 1 idx 0, wrong elt
                                                  18 !=
                                                          7 (correct)
                             1 idx 1, wrong elt
Mod batcher_merge, n=2, sort
                                                   7 != 18 (correct)
Mod batcher_merge, n=2, sort 4 idx 0, wrong elt 216 != 120 (correct)
Mod batcher_merge, n=2, sort 4 idx 1, wrong elt 120 != 216 (correct)
Mod batcher_merge, n=2, sort 7 idx 0, wrong elt 150 != 12 (correct)
Tests for batcher_merge (idx 1)
                                n=2 done, errors in 3 of 10 sorts.
Tests for batcher_merge (idx 2)
                                n=4 done, errors in 6 of 10 sorts.
                                n=8 done, errors in 10 of 10 sorts.
Tests for batcher_merge (idx 3)
Tests for batcher_merge (idx 4)
                                n=16 done, errors in 10 of 10 sorts.
Tests for batcher_merge (idx 5) n=32 done, errors in 10 of 10 sorts.
Tests for batcher_sort (idx 7) n=2 done, errors in 2 of 10 sorts.
Tests for batcher_sort (idx 8) n=4 done, errors in 10 of 10 sorts.
Tests for batcher_sort (idx 9) n=8 done, errors in 9 of 10 sorts.
Tests for batcher_sort (idx 10) n=16 done, errors in 10 of 10 sorts.
Tests for batcher_sort (idx 11) n=32 done, errors in 10 of 10 sorts.
Done with all tests, errors on 10 sorters.
```

The transcript shows the first five errors in detail, this is on lines starting with Mod. A tally of the total number of errors for a particular module is shown on a line starting Tests for.

Here is the output when the assignment is correctly solved:

ncsim> run Starting testbench. Tests for Batcher Merge (idx 1) n=2 done, errors in 0 of 10 sorts. Tests for Batcher Merge (idx 2) n=4 done, errors in 0 of 10 sorts. Tests for Batcher Merge (idx 3) n=8 done, errors in 0 of 10 sorts. Tests for Batcher Merge (idx 4) n=16 done, errors in 0 of 10 sorts. Tests for Batcher Merge (idx 5) n=32 done, errors in 0 of 10 sorts. Tests for Batcher Sort (idx 7) n=2 done, errors in 0 of 10 sorts. Tests for Batcher Sort (idx 8) n=4 done, errors in 0 of 10 sorts. Tests for Batcher Sort (idx 9) n=8 done, errors in 0 of 10 sorts. Tests for Batcher Sort (idx 10) n=16 done, errors in 0 of 10 sorts. Tests for Batcher Sort (idx 11) n=32 done, errors in 0 of 10 sorts. Done with all tests, errors on 0 sorters.

Debugging

To debug your code run SimVision: irun -gui hw05.v. Locate your module and copy symbols to the waveform viewer. See the SimVision instructions on the https://www.ece.lsu.edu/koppel/v/proc.html page.

Synthesis

The synthesis script, syn.tcl, will synthesize sort2 with two delay targets, an easy 10 ns and a unachievable 0.1 ns. If the module doesn't synthesize -.001 s is shown for the delay. The script is run using the shell command genus -files syn.tcl, which invokes Cadence Genus. In past semesters Cadence RTL Compiler (rc) was used, which would be invoked using rc -files syn.tcl, but that won't work on the 2018 homework assignments.

The synthesis script shows area (cost), delay, and the delay target in a neat table. Additional output of the synthesis program is written to file spew.log.

Problem 1: Complete module batcher_sort so that it implements a sorter as described below. The module has one input, an *n*-element array **a**, and one output, an *n*-element array **x**. Above some minimum value of **n** it should instantiate two copies of itself, each copy should sort half the the input array, **a**. A behav_merge module should be instantiated to merge the output of the two recursive implementations.

The behav_merge module, which is already written, has two inputs, a and b, each an *n*-element array, and one output, x, a 2*n*-element array, where *n* is the value of the first parameter. Output x contains the elements of a and b in sorted order.

Once Problem 2 is solved correctly replace behav_merge with batcher_merge.

The module must use structural code, be synthesizable, be reasonably efficient, clearly written, and of course pass the testbench. See other conditions on the solution and tips in the Verilog file.

The solution to this problem is straightforward and will be in the form of other tree-structured designs shown in class.

Warning: Do not search for a solution to this problem. Exam questions will be written under the assumption that each student has solved all homework problems.

Problem 2: Complete module batcher_merge so that it recursively implements a Batcher odd/ even merge module in which the number of elements of each input list is a power of 2. Use sort2 instantiations to combine the output of the recursively instantiated modules. Use either structural or behavioral code to separate each input sequence into odd and even parts.

The batcher_merge module should recursively instantiate two copies of itself, call them lo and hi. Input **a** of the lo module should connect to the even-numbered **a** elements of the enclosing module, input **b** of lo connects to odd-numbered **b** elements of the enclosing module. For the hi module switch odd and even. See the illustration below. The illustration also shows how the outputs should connect.



Warning: Do not search for a solution to this problem. Exam questions will be written under the assumption that each student has solved all homework problems.

The module must be synthesizable, reasonably efficient, clearly written, and of course pass the testbench.

Do not compare the cost and performance reported by genus for your module, batcher_merge, to those for behav_merge. That's because genus does not correctly infer hardware for behav_merge.

Homework 6

Due: 10 October 2018

Problem 1: Use the simple model to compute the cost and delay (critical path length) of the inferred hardware for module behav_merge from Homework 5. This module has two inputs, a and b, each of which is an *n*-element sorted sequence of *w*-bit unsigned integer values. Output x is a 2*n*-element array of *w*-bit quantities. The module assigns elements of a and b to x so that x itself is a sorted sequence of the elements from a and b.

Show the cost and delay of $behav_merge$ in terms of n and w. The Homework 5 module appears below. Use the tree implementation of multiplexors for cost and delay. (See the simple model notes.) Make reasonable optimizations, such as using the same multiplexor for a[ia] and a[ia++]. Avoid tedious optimizations such as varying the number of bits in ia and ib.

```
module behav_merge
```

```
#( int n = 4, int w = 8 )
  ( output logic [w-1:0] x[2*n], input uwire [w-1:0] a[n], b[n] );
logic [$clog2(n+1)-1:0] ia, ib;
always_comb begin
    ia = 0; ib = 0;
    for ( int i = 0; i < 2*n; i++ )
        x[i] = ib == n || ia < n && a[ia] <= b[ib] ? a[ia++] : b[ib++];
end
endmodule</pre>
```

Problem 2: As was probably mentioned, a proper *n*-element Batcher odd/even merge module is constructed from $\frac{n}{2} \lceil \lg n \rceil$ sort2 modules, and the critical path length through a merge module is $\lceil \lg n \rceil$ sort2 delays.

If the previous problem was solved correctly then the cost and critical path length of behav_merge should be much larger than a Batcher merge. But the behavioral code in behav_merge has a run time of O(2n) running as an ordinary program, and consumes O(2n) memory, both of which are optimal for an algorithm that must operate on all of 2n items. In fact, recursively applied code based on behav_merge can sort a sequence in $O(n \lg n)$ time, which is the best one can normally get in many cases.

What is it about the hardware realization of **behav_merge** that makes it so much less efficient than the software realization? Your answer should consider how much hardware is being used at each moment in time.

LSU EE 4755 Homework 7 Due: 10

ork 7 Due: 16 November 2018

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2018/hw07.v.html.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account, copy the assignment, and run the Verilog simulator and synthesis program on the unmodified homework file, hw07.v.

Homework Overview

Modules mult_seq_ds_prob_1 and mult_seq_d_prob_2 have similar sets of ports as the fast pipelined multiplier from 2017 Homework 7, but the code within this semester's modules implements a sequential rather than a pipelined multiplier. In this assignment these modules will be modified so they use handshaking to start and announce the availability of a product, and in mult_seq_d_prob_2, so that the latency (number of clock cycles) needed to compute a product depends upon the number and placement of zeros in the multiplicand. Unlike 2017 Homework 7, the solution to this problem will not be pipelined.

Initially the testbench should report errors for both modules, identified as Prob 1 and Prob 2, these errors are due to the modules ignoring the handshake signals (in_valid and out_avail). The testbench, however, should correctly synthesize both modules. The testbench will also synthesize an original copy of each module, for comparison.

A correct solution to Problem 1 will eliminate the testbench errors. A correct solution to Problem 2 will reduce the number of cycles needed to compute a correct result. A future assignment or possibly final exam questions will ask about the difference in performance between the Problem 1 and Problem 2 modules.

The testbench reports details of the first few errors encountered on each modules, and then a summary. If you would like to test your module on a specific multiplier/multiplicand pair search for values to try out and add those to the beginning of the list assigned to tests. The modules are instantiated with names prob1_m1, prob1_m2, etc. Look for these when using debugging tools such as SimVision.

The synthesis script for this assignment can be run with the command genus -files syn.tcl. It synthesizes modules mult_seq_ds_prob_1 and mult_seq_d_prob_2, as well as unmodified copies of these modules, mult_seq_ds_prob_1_orig and mult_seq_d_prob_2_orig. Each is synthesized at two sizes and three different values of m. The synthesis script assumes at latency of $\lceil w/m \rceil$ for these modules, which is an overestimate for Problem 2.

Problem 1: Module mult_seq_ds_prob_1 has two parameters, w and m, four input ports, clk, in_valid, plier, and cand, and two output ports, prod, and out_avail.

The unmodified module will set **prod** to the 2*w*-bit product of *w*-bit inputs **plier** and **cand**, which hold unsigned integers. It computes the product using *m*-bit partial products, similar to the method used by **mult_seq_dm** but using the streamlined code in **mult_seq_stream**. In **mult_seq_ds_prob_1** the product will be available with a latency of between $\lceil w/m \rceil + 1$ and $2\lceil w/m \rceil - 1$ cycles. The latency will be $\lceil w/m \rceil + 1$ when the multiplier and multiplicand arrive when **iter** is reset to zero, but if they arrive one cycle later the latency will be $2\lceil w/m \rceil - 1$. If that higher latency bothers you then this is your problem. (Even those that don't care need to solve this problem.)

The reason for this variation in latency in mult_seq_dm and friends is that those modules have no way of knowing when a new multiplier/multiplicand pair has arrived (other than continually comparing them to prior values which would require extra hardware). As the alert student

suspects, input in_valid in mult_seq_ds_prob_1 is used to indicate the arrival of a new pair. Modify mult_seq_ds_prob_1 so that it starts a new multiplication at the positive edge of clk when in_valid is 1, even if there's a multiplication in progress. When a new multiplication starts set out_avail to 0, and set it back to 1 when prod holds the correct product.

When this problem is correctly solved the testbench should not show errors on this module. The testbench instantiates the module for three sizes of m, and it has **Prob 1** in the name. See the checkboxes in hw07.v for additional requirements and tips. Don't forget synthesizability as well as clear and efficient code.

Problem 2: The unmodified module $mult_seq_d_prob_2$ computes a product in at best $\lceil w/m \rceil + 1$ cycles. For some multiplicands the value of cand_2d[iter] (see the code) will be zero for certain values of iter. An extreme case is when the multiplicand is zero, but there are many other situations where cand_2d[iter] will be zero. Currently iter is incremented by 1 each clock cycle. Modify $mult_seq_d_fast$ so that iter is incremented so that it points to the next non-zero value in cand_2d, or to $\lceil w/m \rceil$ if there are no more non-zero values. Doing so will reduce the number of clock cycles needed to compute a product. This should be reflected in the Avg Cyc shown for the Prob 2 module by the testbench.

Use the synthesis script syn.tcl to find the clock period of the module. The latency shown by the synthesis script assumes w cycles per multiply. To find the actual latency of your module multiply the clock period reported by the synthesis script with the average cycles reported by the testbench.

The goal is to reduce the average number of cycles, as reported by the testbench while also keeping clock period low (as reported by the synthesis script) so that the average latency, measured in seconds (or some fraction) is lower.

Homework 8

Due: 27 November 2018

Problem 1: Appearing below is the output of the simulator and synthesis script, showing data for the Homework 7 solution modules. Modules are simulated and synthesized for w = 32.

Module Name	Area	Period	Period				
		Target	Actual				
mult_seq_ds_prob_1_w32_m1	157813	1000	14926				
<pre>mult_seq_ds_prob_1_w32_m2</pre>	185493	1000	15431				
mult_seq_ds_prob_1_w32_m4	242568	1000	16296				
mult_seq_d_prob_2_w32_m1	288580	1000	31944				
<pre>mult_seq_d_prob_2_w32_m2</pre>	301203	1000	32204				
mult_seq_d_prob_2_w32_m4	329226	1000	32192				
For Prob 1 Deg 1 ran	400 tests, 0/	0/ 0	errors	found.	Avg	сус	33.0
For Prob 1 Deg 2 ran	400 tests, 0/	0/ 0	errors	found.	Avg	cyc	17.0
For Prob 1 Deg 4 ran	400 tests, 0/	0/ 0	errors	found.	Avg	сус	9.0
For Prob 2 Deg 1 ran	400 tests, 0/	0/ 0	errors	found.	Avg	сус	9.5
For Prob 2 Deg 2 ran	400 tests, 0/	0/ 0	errors	found.	Avg	cyc	7.3
For Prob 2 Deg 4 ran	400 tests, 0/	0/ 0	errors	found.	Avg	сус	5.0
Modules instantiated with w	= 32.						

The Problem 1 modules are based on the streamlined multiplier and so are faster. But the Problem 2 modules skip zeros. Based on the data above, indicate the ways, if any, that the Problem 2 modules are better than the Problem 1 modules. Explain using the numbers above.

There are more problems on the next pages.

Problem 2: Appearing below is a solution to Homework 7, Problem 1, the streamlined degree-m multiplier with handshaking. The complete solution is at https://www.ece.lsu.edu/koppel/v/2018/hw07-sol.v.html. For this problem assume that w and m are both powers of 2.

```
module mult seq ds prob 1 #( int w = 16, int m = 2 )
   ( output logic [2*w-1:0] prod, output logic out_avail,
     input uwire clk, in_valid,
                                  input uwire [w-1:0] plier, cand );
  localparam int iterations = ( w + m - 1 ) / m;
  localparam int iter_lg = $clog2(iterations);
  uwire [iterations-1:0] [m-1:0] cand_2d = cand;
  bit [iter_lg:0] iter;
  logic [2*w-1:0] accum;
  always_ff @( posedge clk ) begin
      if ( in_valid ) begin
         accum = cand;
         iter = 0;
         out_avail = 0;
      end else if ( !out_avail && iter == iterations ) begin
         out_avail = 1;
         prod = accum;
      end
      accum = { 0 + plier * accum[m-1:0] + accum[2*w-1:w], accum[w-1:m] };
      iter++;
   end
```

endmodule

(a) Show the hardware that will be inferred for this module. The Inkscape SVG format diagram of the hardware for the streamlined sequential module from the class demo notes can be used as a starting point. It is at https://www.ece.lsu.edu/koppel/v/2018/ill-mul-seq-str.svg.

(b) Compute the cost and delays for this module using the simple model. Show these in terms of w and m. Clearly show the critical path on your diagram.

There is a problem on the next page.

Problem 3: Appearing below is a solution to Homework 7, Problem 2, the streamlined degree-m multiplier with handshaking. The complete solution is at https://www.ece.lsu.edu/koppel/v/2018/hw07-sol.v.html. For this problem assume that w and m are both powers of 2.

```
module mult seq d prob 2 #( int w = 16, int m = 2 )
   ( output logic [2*w-1:0] prod,
                                    output logic out_avail,
     input uwire clk, in_valid,
                                    input uwire [w-1:0] plier, cand );
  localparam int iterations = ( w + m - 1 ) / m;
  localparam int iter_lg = $clog2(iterations);
  uwire [iterations-1:0] [m-1:0] cand_2d = cand;
  bit [iter_lg-1:0] iter;
  logic [2*w-1:0] accum;
  always_ff @( posedge clk ) begin
      logic [iter_lg-1:0] next_iter;
      if ( in_valid ) begin
         iter = 0;
         accum = 0;
         out_avail = 0;
      end else if ( !out_avail && iter == 0 ) begin
         prod = accum;
         out_avail = 1;
      end
      accum += plier * cand_2d[iter] << ( iter * m );</pre>
     next_iter = 0;
      for ( int i=iterations-1; i>0; i-- )
        if ( i>iter && cand_2d[i] ) next_iter = i;
      iter = next_iter;
   end
```

endmodule

(a) Show the hardware that will be inferred for this module.

(b) Compute the cost and delays for this module using the simple model. Show these in terms of w and m. Clearly show the critical path on your diagram.

8 Fall 2017

LSU EE 4755 Homework 1 Due: 8 September 2017

Start working on the solutions to the problems below on paper, but complete them using the computers in the lab. For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab visit https://www.ece.lsu.edu/koppel/v/2017/hw01.v.html.

Problem 1: Appearing below, and in hw01.v, is a Verilog description of a 2-input multiplexer, mux2, and a partially completed description of a 4-input mux, mux4, along with a diagram showing how a four-input mux can be made using three two-input multiplexers. Complete mux4 as described in the diagram.

It is important that mux4 instantiate three mux2 modules. Other correct 4-input multiplexer implementations will not receive credit. Also, don't forget to set the parameters correctly when instantiating modules.

```
select
module mux2
                                                                   0:0
                                                                                1:1
  #(int w = 16)
   ( output uwire [w-1:0] x,
                                                               a0
     input uwire s,
     input uwire [w-1:0] a, b );
                                                               a1
  assign x = s == 0? a : b;
                                                                                   х
endmodule
                                                               a2
module mux4
  #(int w = 6)
                                                               a3
   ( output uwire [w-1:0] x,
     input uwire [1:0] s,
```

endmodule

input uwire [w-1:0] a[3:0]);

Problem 2: Appearing below is a mux8 module. Complete mux8 so that it implements an 8-input multiplexer using two mux4 modules and one mux2 module. Notice that the data input to mux8 is an 8-element array of w-bit quantities. To see how to extract a subrange of an array (called a *part select* in Verilog) see the testbench module. Solve this problem by generalizing the technique appearing in the previous problem.

Credit will only be given for mux8 modules that *instantiate* two mux4 modules and a mux2 module. Yes, assign x = a[s]; is correct and the best way to do it in other situations, but the goal here is to learn about instantiation.

```
module mux8
```

```
#( int w = 5 )
( output uwire [w-1:0] x,
    input uwire [2:0] s,
    input uwire [w-1:0] a[7:0] );
```

endmodule

Appearing below is the start of the testbench code. To see the complete testbench and other modules follow https://www.ece.lsu.edu/koppel/v/2017/hw01.v.html.

module testbench();

```
localparam int w = 10;
localparam int n_in_max = 8;
localparam int n_mut = 3;
uwire [w-1:0] x[n_mut];
logic [2:0] s;
logic [w-1:0] a[n_in_max-1:0];
mux2 #(w) mm2(x[0], s[0], a[0], a[1]);
mux4 #(w) mm4(x[1], s[1:0], a[3:0]);
mux8 #(w) mm8(x[2], s[2:0], a[7:0]);
initial begin
automatic int n_test = 0;
```

```
automatic int n_err = 0;
```

Homework 2 Due: 25 September 2017

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab visit https://www.ece.lsu.edu/koppel/v/2017/hw02.v.html.

Problem 1: Let $f || \Re \to \Re$ be an approximately linear function, for example, f(x) might be the height of a tree that has been growing for x years. Suppose further that we have two pairs of values for the function, $a_1 = f(x_1)$ and $a_2 = f(x_2)$ with $x_1 < x_2$. (For example, $x_1 = 1$ year and $a_1 = 1$ m, and $x_2 = 2$ years and $a_2 = 1.5$ m.) To compute values of x between x_1 and x_2 we can use linear interpolation $a(x) = a_1 + (x - x_1) \frac{a_2 - a_1}{x_2 - x_1}$. Notice that $a(x_1) = a_1$ and $a(x_2) = a_2$. Module interp_behav has four 32-bit inputs x1, a1, x2, and a2. Each will hold a number in

Module interp_behav has four 32-bit inputs x1, a1, x2, and a2. Each will hold a number in shortreal representation, their values indicate the endpoints of a region to linearly interpolate, as described in the previous paragraph. Input j, jw bits, is expected to be $\lfloor x - x_1 \rfloor$, where x is a value to interpolate. (For example, suppose $x_1 = 20$. For $x = x_1 = 20$, input j would be 0, for x = 25.7, j=5.) Output aj is an 8-bit integer and is to be set to $\lfloor a(x_1 + j) \rfloor$. Though input j and output aj are integers, it's important that some of the calculation be done in floating-point to avoid rounding errors, such as the computation $\frac{a_2-a_1}{x_2-x_1}$. (Note: If you're having trouble following this, don't worry. All you really need to do is to look at what interp_behav is doing.) Finally, 1-bit output valid is set to 1 if $|x_1| + j \leq |x_2|$ and 0 otherwise.

```
module interp_behav
```

```
#(int jw = 12, amax = 255)
 ( output logic valid,
                                          output logic [7:0] aj,
   input uwire [31:0] x1, a1, x2, a2,
                                          input uwire [jw-1:0] j );
always_comb begin
    automatic shortreal x1r = $bitstoshortreal(x1);
    automatic shortreal x2r = $bitstoshortreal(x2);
    automatic shortreal a1r = $bitstoshortreal(a1);
    automatic shortreal a2r = $bitstoshortreal(a2);
    automatic int x1i = $floor(x1r);
    automatic int x2i = $floor(x2r);
    automatic int xj = x1i + j;
    shortreal dadx, ajr;
    valid = xj <= x2i;</pre>
    dadx = (a2r - a1r) / (x2r - x1r);
    ajr = a1r + j * dadx;
    aj = ajr < 0 ? 0 : ajr > amax ? amax : $floor(ajr);
```

end

endmodule

The code in interp_behav computes these values using behavioral code. It is not synthesiz-

able because it uses operators to perform floating-point arithmetic. Module interp has the same connections as inter_behav, and has some starter code. Modify module interp so it computes the same values and is synthesizable. To do so instantiate ChipWare modules to perform floating-point operations. Module interp already instantiates an adder and a float-to-int converter. Find additional modules in the ChipWare documentation, which can be found on the course references page. When using a ChipWare module put in an include directive at the end of the file. See the end of hw02.v for examples.

```
module interp
```

endmodule

The testbench will test module interp, it should initially report lots of errors. Of course, when you are done there should be zero errors.

Follow the synthesis steps on the course procedures page to determine if interp is synthesizable. If the elaborate step is successful then the module is synthesizable.

Problem 2: Floating-point hardware is relatively costly. Compare the cost of FP and integer arithmetic units by synthesizing equivalent FP and integer adders and dividers. Wrap the ChipWare modules in your own modules, (such as fp_add in hw02.v) and set parameters so the FP and integer units are comparable. Then modify the synthesis script, syn.tcl, so that it will synthesize these modules. The modules should be added to the list assigned on the set modules line.

Based on the data collected above, indicate how much less you think the cost would be of an interp module that used integer arithmetic.

LSU EE 4755 Homework 3 Due: 4 October 2017

Problem 1: Solve 2016 EE 4755 Final Exam Problem 2, in which timings are requested for individual units, such as a BFA and more complex circuits made from individual units.

In the simple timing model 2-input AND and OR gates each have a delay of 1 unit, and NOT gates have a delay of 0 units. AND and OR gates with more than two inputs have the delay obtained with a reduction tree of 2-input gates. That is, *n*-input AND and OR gates have a delay of $\lceil \lg n \rceil$ units.

Problem 2: Solve 2016 EE 4755 Final Exam Problem 4, in which the cost of some circuits is to be computed.

In the simple cost model NOT gates have a cost of 0 units and *n*-input AND and OR gates each have a cost of n-1 units. The cost of other gates is the cost of the AND, OR, and NOT gates needed to implement them.

Homework 4 Due: 1 No

Due: 1 November 2017

For instructions visit http://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab visit http://www.ece.lsu.edu/koppel/v/2017/hw04.v.html.

Problem 1: A run of characters in a sequence is a set of consecutive characters that are the same, the length of a run is the number of times the character is repeated in the run. For example, the string aabbbcaaaa contains four runs: a run of length 2 for character a, a run of length 3 for character b, a run of length 1 for character c, and a run of length 4 for character a. (Note that a has two runs.)

Module maxrun, when completed, will keep track of the maximum-length run in a sequence of characters appearing at its in_char input. In this assignment character refers to a c-bit value. The testbench (including the excerpt below) shows character values as two-digit hexadecimal numbers. For example, at cycle 2 the table shows c=8d for in_char, meaning that the character value is $8d_{16} = 141_{10}$. The fact that the character can be represented using two hexadecimal digits or three decimal digits does not change the fact that it is one character.

At the positive edge of input clk, maxrun will compare the character at in_char to the character seen at the previous positive edge. If they are the same it will increment a *current run counter*, if the characters are different it will set the current run counter to 1. If reset is 1 at the clock positive edge then the current run counter should be set to 1 (which is the same as setting it to 0 and then incrementing it). A second *max run counter* is also set to zero on the reset signal at the positive clock edge. If the current run counter is greater than the max run counter then the max run counter is set to the current run counter, and the character appearing in that run is remembered and used used for output mr_char.

If input mr is 1, then output len should be set to the value of the max run counter, otherwise it should be set to the value of the current run counter. This should be done asynchronously (len should be updated whenever mr changes, not just at a positive clock edge).

For example, look at the output of the testbench below. Column R shows the value of the reset signal and column in_char shows the input character, both appearing before and "during" the positive clock edge. The remaining columns show the value of the current run counter, max run counter, and the mr_char output after the positive clock edge. At cycle 1 the input character, 00, has a run of 2. At cycle 6 character 8d has reached a run of 5, etc. The testbench shows an ok if the output is correct, otherwise it shows what the correct output should be.

Cycle	R	in_char	current-	rur	ı	m	ax-run		mr_c	har	
	-					-					
0	r	c=00	cr_len	1	ok	m	r_len 1	ok	mr_c	00	ok
1		c=00	cr_len	2	ok	m	r_len 2	ok	mr_c	00	ok
2		c=8d	cr_len	1	ok	m	r_len 2	ok	mr_c	00	ok
3		c=8d	cr_len	2	ok	m	r_len 2	ok	mr_c	00	ok
4		c=8d	cr_len	3	ok	m	r_len 3	ok	mr_c	8d	ok
5		c=8d	cr_len	4	ok	m	r_len 4	ok	mr_c	8d	ok
6		c=8d	cr_len	5	ok	m	r_len 5	ok	mr_c	8d	ok
7		c=c5	cr_len	1	ok	m	r_len 5	ok	mr_c	8d	ok
8		c=77	cr_len	1	ok	m	r_len 5	ok	mr_c	8d	ok
9		c=f2	cr_len	1	ok	m	r_len 5	ok	mr_c	8d	ok
10	r	c=f2	cr_len	1	ok	m	r_len 1	ok	mr_c	f2	ok
11		c=f2	cr_len	2	ok	m	r_len 2	ok	mr_c	f2	ok
12		c=f2	cr_len	3	ok	m	r_len 3	ok	mr_c	f2	ok

3	c=f2	cr_len	4 ok	mr_len	4 ok	mr_c f2	ok
4 r	c=f2	cr_len	1 ok	mr_len	1 ok	mr_c f2	ok
5	c=9d	cr_len	1 ok	mr_len	1 ok	mr_c f2	ok
6	c=0d	cr_len	1 ok	mr_len	1 ok	mr_c f2	ok
7	c=d5	cr_len	1 ok	mr_len	1 ok	mr_c f2	ok
7	c=d5	cr_len	1 ok	mr_len	1 ok	mr.	_c f2

Complete the maxrun module so that it passes the testbench and is synthesizable. Please pay attention to the parameters, which indicate the size of a character and the number of bits in the counters. Use the parameters, not their default values.

Use simvision for debugging, which is explained in the course procedures page.

Problem 2: Run the synthesis script, using command rc -files syn.tcl. If it runs correctly, a file spew-file.log will be created which contains a timing report for a design. On paper or in comments in the submission file, indicate where the critical path is in your design.

Provide suggestions on making it faster, or explain what you actually did for a high clock frequency.

Homework 5 Due: 10 November 2017

For instructions visit http://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab visit http://www.ece.lsu.edu/koppel/v/2017/hw05.v.html.

Problem 1: Module lookup_char has a *w*-bit input char, and two outputs, found and idx. The module has parameter chars, which is an *n*-element array of *w*-bit characters. Complete lookup_char so that output found is logic 1 iff char is equal to one of the elements of chars. Set idx to the index of that character. (That is, if found is 1 then chars[idx] == char.) It does not matter what idx is if the character is not found. The module should synthesize into combinational logic.

See the Verilog Problem 1 code for details on the parameters and ports and review the comment checkboxes at the top of the problem for additional tips.

Module lookup_char will be used in the next problem and the testbench will be able to test lookup_char even if no other parts of nest are finished.

Note: There is a 2016 EE 4755 homework assignment in which a module a lot like lookup_char had to be designed. The major difference is that in 2016 the chars array was a port, here it is a parameter. Feel free to look at the solutions. It should go without saying that the chars array should remain a parameter in this assignment.

Problem 2: Module nest, when completed, will monitor a sequence of characters that includes bracketing characters (such as parentheses) and indicate whether these bracketing characters are properly nested. For example, sequence "a()[d()e[f]]" is properly nested but "a(]" is not.

The module has input parameters char_open and char_close, each of these is an *n*-element array of *w*-bit characters listing characters that are to be treated as opening and closing bracketing characters. See the Verilog code for details. The module has three inputs, clk, reset, and in_char. The module has five outputs, level, awaiting, is_open, is_close, and bad.

Output is_open should be set to 1 iff in_char is one of the characters in char_open, and is_close should be set to 1 iff in_char is one of the characters in char_close. These outputs should be generated by instantiations of lookup_char (the module from the first problem). The logic for computing is_open and is_close should be combinational.

(a) Complete the logic for is_open and is_close as described above. The testbench checks these outputs for correctness, look for op and cl in the trace. They are correct if er does not appear to the right of the 0 or 1. The module must be synthesizable.

The module has an output level which should operate as follows. On a positive clock edge if reset is 1, level is set to zero. Otherwise, if in_char is in char_open then level should be incremented and if in_char is in char_close then level should be decremented. If in_char is in neither list then level is left unchanged. (level provides the current nesting level. A value of 0 indicates the current character is not "inside" any bracketing characters, or put another way, that we are not awaiting something like a closing parenthesis.)

The module has an output bad which indicates whether the sequence seen since the last reset is improperly nested or if the nesting level exceeded d, a module parameter. Set bad to 0 when reset is 1 (at a positive clock edge). Set bad to 1 if a closing character is seen when level is 0 or if an opening character is seen when level is d.

Also set **bad** to 1 if the wrong closing character is seen. For example, for "(]" set **bad** to 1 when the "]" is seen because a ")" was expected.

Output awaiting should be set to the next valid closing character. For example, if the sequence so far is "()[" awaiting should be set to "]".

When **bad** is 1 outputs level and awaiting can be set to any value.

Note that bad, level, and awaiting should be updated at the positive clock edge.

(b) Complete **nest** so that it works as described above. The module must be synthesizable and show no errors.

The testbench checks **nest** for correctness and at the end of a run it shows the number of errors. As of this writing it will test **nest** on 1000 different sequences, see variable **num_groups** in the testbench. It will print details on up to 2 sequences with zero errors and up to 3 sequences with at least one error. Feel free to edit the testbench to change these numbers.

Consider the following sample of testbench output:

ncsim> run

сус	2	s.c	0.	0	i	op O	cl O	bad O	lev	0	0	await ')'
сус	3	s.c	0.	1	J	op O	cl O	bad O	lev	0	0	await ')'

The text cyc 2 indicates the cycle number. That can be used with SimVision or some other tool to locate the place in execution. The text s.c 0. 1 shows the sequence number, 0, and the number of previous characters in the sequence, 1. Next shown is the character at in_char, J in cycle 3. The text op 0 cl 0 bad 0 show the values of the is_open, is_close, and bad outputs that nest has produced. If these values are wrong then the text er appears to the right of the value. For example if the value at the is_open port were wrong the text would be op 0 er . Note that bad 1 is fine but bad 0 er indicates that the bad port value is wrong. The text lev 0 0 shows both the module level output (the first 0 here) and the known correct value (the second 0). Finally, await shows the module output followed by the correct value. They are between quotes to make spaces and other non-printable characters obvious.

Note that when level is zero the value of await is irrelevant. Also, when **bad** is 1, the values of level and await are both irrelevant.

The example below shows the trace output when there are errors:

		-									
cyc	54	s.c	5.0	L	op O	cl O	bad O	lev	0	0	await ')'
cyc	55	s.c	5.1	(op 1	cl O	bad O	lev	0	1 er	await ')'
cyc	56	s.c	5.2	(op 1	cl O	bad O	lev	0	2 er	await ')'
cyc	57	s.c	5.3	q	op O	cl O	bad O	lev	0	2 er	await ')'
cyc	58	s.c	5.4	Ζ	op O	cl O	bad O	lev	0	2 er	await ')'
cyc	59	s.c	5.5)	op O	cl 1	bad 1 er	lev	7	1	await ')'
cyc	60	s.c	5.6)	op O	cl 1	bad 1 er	lev	6	0	await ')'
	A	1 55	1 1 1	1	1 1 1	•	1 1 0 1 1	1/11			1 NT 1 1

At cycle 55 level should have been incremented for the "(", but it was not. Notice the **er** to the right of **lev**. Also, at cycle 59 the module set **bad** to 1 which is an error because the sequence has not violated any rules.

Problem 3: Run the synthesis script, using command rc -files syn.tcl. If it runs correctly, a file spew-file.log will be created which contains a timing report for a design. On paper or in comments in the submission file, indicate where the critical path is in your design.

Provide suggestions on making it faster, or explain what you actually did for a high clock frequency.

Homework 6

Due: 13 November 2017

Problem 1: The solution to Homework 4, http://www.ece.lsu.edu/koppel/v/2017/hw04-sol.v.html, includes two modules, maxrun and maxrun_opt.

(a) Show the hardware inferred for maxrun.

(b) Show the hardware inferred for maxrun_opt.

Problem 2: Compute the critical path for the maxrun and maxrun_opt modules using the simple model. The launch points (path starts) are at module inputs and register outputs, and the capture points (path ends) are at module outputs and register inputs. Note that with these definitions the critical path does not include the register itself. Show the critical path in terms of w, the number of bits in the len output and c the number of bits in a character.

Homework 7 Due: 29 November 2017

For instructions visit http://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab visit http://www.ece.lsu.edu/koppel/v/2017/hw07.v.html.

Problem 1: Module mult_pipe is a simple pipelined multiplier which multiplies two w-bit operands, computing m partial products per stage in $\lceil w/m \rceil$ stages. The latency of this multiplier is $\lceil w/m \rceil$ cycles regardless of what is being multiplied, which in many circumstances is just fine.

In contrast $\texttt{mult_fast}$ is designed for situations in which lower latency is beneficial. The goal is to compute the results for "easier" products in fewer cycles. For example, multiplying $abcd_{16} \times 9876_{16}$ in a 16-bit degree-4 (m=4) multiplier would take four cycles since all partial products are needed. But, $abcd_{16} \times 1_{16}$ requires one partial product and so the product should be available sooner.

Like the other multipliers mult_fast has w-bit inputs plier and cand and a 2w-bit output prod, and a 1-bit clk input. But it also has a 1-bit input in_valid and a 1-bit output out_avail.

At each positive clock edge if input in_valid is 1 mult_fast should start computing the product of the input values, plier×cand. If input in_valid is 0 then the external hardware does not need plier×cand. Though the module can start computing plier×cand when in_valid is 0, it should not set out_avail when the product is ready.

The outputs $\operatorname{out_avail}$ and prod should be set at each positive clock edge. If $\operatorname{out_avail}$ is 1 then prod is the product of values appearing earlier at the inputs at a time when $\operatorname{in_valid}$ was 1. The products should appear in the same order as the inputs. For example, suppose in cycle 10 the values $8765_{16} \times 53ab_{16}$ appear at the inputs and at cycle 11 the values 1×1 appear. Even though 1×1 can be computed in one cycle it cannot appear at the outputs until after $8765_{16} \times 53ab_{16}$ appears. If it takes four cycles to compute $8765_{16} \times 53ab_{16}$ then it will appear at the outputs in cycle 14, and so the product 1×1 will not appear at the outputs until four cycles after it arrives, at cycle 11 + 4 = 15.

A simple case is when in_valid is always equal to one. In that case after w/m cycles out_avail should always be set to one and the value at output prod is the product of inputs appearing w/m cycles earlier, which is how an ordinary pipelined multiplier, such as mult_pipe operates.

Next, consider the table below which shows inputs and possible outputs. In cycle 0 the values 1×11 arrive. Their product, 11 appears at the outputs in cycle 1. In cycle 1 values 98 and 99 appear at the inputs but since in_valid is 0 their product is not needed. At cycle 2 values 3 and 22 are at the inputs, the product $3 \times 22 = 66$ appears at the output in cycle 4. Note that at cycles 2 and 3 out_avail is 0. The product 4×14 appears at the outputs in cycle 5.

cycle	0	1	2	3	4	5
in_valid	1	0	1	1		
plier	1	98	3	4		
cand	11	99	22	14		
out_avail	0	1	0	0	1	1
prod		11			66	56

correctly the testbench should show that there are zero errors.

Note that it took two cycles to compute 3×22 but one cycle to compute the other products. (a) Modify mult_fast so that it sets out_avail when a product is ready. If this is completed

(b) Modify mult_fast so that the product is ready when all of the remaining multiplicand bits are zero. That is, suppose stage i examines bits mi to mi + m - 1 of the multiplicand. If multiplicand bits w - 1 to mi + m - 1 are all zero then the product is finished at stage i. If this is completed

correctly then the testbench should show that the average number of cycles for the degree-2 fast multiplier is about 5.1 and for degree 4 it should be about 2.7.

- Modules must be synthesizable.
- Modules must be reasonably efficient.
- Do not assume specific parameter values.
- Use SimVision for debugging.

9 Fall 2016

LSU EE 4755 Homework 1 Due: 9 September 2016

The questions below can be answered without using EDA software, paper and pencil will suffice. Please turn in the solution on paper. Homework 2 will require the use of Verilog implementations. Nevertheless, runnable SystemVerilog code for this assignment can be found at https://www.ece.lsu.edu/koppel/v/2016/hw01.v (plain Verilog) and

https://www.ece.lsu.edu/koppel/v/2016/hw01.v.html (syntax-highlighted HTML).

Those who are rusty about the correspondence between Verilog code and hardware might want to look at the solution to EE 3755 Fall 2013 Homework 1, at http://www.ece.lsu.edu/ee3755/2013f/hw01_sol.pdf.

Problem 1: Show a Verilog explicit structural description of the module illustrated below. In this assignment it is okay to use primitives (and, not,...), but don't get in the habit of using them.



- Base the names of ports, wires, and instances on labels in the illustration.
- Of course, use only primitives and wires. See Table 28-1 of IEEE Std 1800-2012 for a list of gates.

Problem 2: Answer the following questions about Verilog primitives as defined in IEEE Std 1800-2012. (See Chapter 28.) Indicate the exact section number where the answer is found.

(a) The standard provides a not primitive and a nor primitive, among others. One can easily argue that a 1-input nor gate is the same as a not gate. Does the standard actually allow Verilog code to instantiate a 1-input nor gate?

(b) Based on the standard, is there anything that can be done with a **not** primitive that can't be done with a 1-input **nor** primitive? (Don't try to answer this too deeply, just show an instantiation.)

Problem 3: Output match of module is_1133, shown below, is 1 iff its input d (digits) is 1133 in BCD (which has the same representation as 1133_16). The module instantiates BCD digit detection modules is_1 and is_3.

```
module is_1( output uwire match, input uwire [3:0] d );
  uwire z321;
  nor o0(z321,d[3],d[2],d[1]);
  and a1(match,z321,d[0]);
endmodule
module is_3( output uwire match, input uwire [3:0] d );
  uwire z32;
  nor o0(z32,d[3],d[2]);
  and a1(match,z32,d[1],d[0]);
endmodule
module is 1133( output uwire match, input uwire [15:0] d );
  uwire m1, m2, m3, m4;
  and a1(match, m1, m2, m3, m4);
  is_1 i0(m1, d[15:12]);
  is_1 i1(m2, d[11:8]);
  is_3 i2(m3, d[7:4]);
   is_3 i3(m4, d[3:0]);
endmodule
```

(a) Draw a diagram of is_1133 based on the explicit structural description above. Show the insides of the is_1 and is_3 modules. Label the diagram using the same wire and instance names used in the Verilog descriptions.

(b) Design a module is_1133_is that does the same thing as is_1133, but that uses implicit structural code. The correct solution requires adding only one short line to the shell shown below. Don't forget that the value in d is in BCD. Note: The word short was added after the original assignment.

module is_1133_is(output uwire match, input uwire [15:0] d);

endmodule

Problem 4: When completed the output of module is_1235 is 1 iff the input is 1235 in BCD.
module is_1235(output uwire match, input uwire [15:0] d);

endmodule

(a) Complete the module. The module must be explicitly structural except for the use of the concatenation operator (see Section 11.4.12). The module **must** use is_1 and is_3 to detect the digits. Do not assume or design an is_2 or is_5 and don't put in logic to detect those digits.

(b) Draw a diagram of the completed module, which should be very similar to the diagram from the previous problem.

Homework 2

Due: 22 September 2016

Problem 0: First, follow the instructions for account setup and homework workflow on the course procedures page, http://www.ece.lsu.edu/koppel/v/proc.html.

Look through the code in hw02.v. It contains partially completed modules for an ASCII-coded radix-R adder. An overview of ASCII-coded adders and the contents of hw02.v is given here in Problem 0, where there is nothing to answer. The problem problems start at Problem 1.

Consider first a hypothetical ASCII-coded radix-10 (decimal) adder with two 5-character ($5 \times 8 = 40$ bit) inputs, and a 5-character output. If the strings ___10 and __418 appeared at the inputs, the string __428 should appear at the output (the underscores are supposed to be blanks). The adder could be constructed from 5 ASCII full adders, which operate analogously to binary full adders. Each ASCII full adder has two 8-bit inputs, an 8-bit output, and a one-bit carry in and carry out. The value output is the sum of the values at the two inputs plus the carry in. The ASCII full adders should be connected to each other in the same way that binary full adders are connected to make a ripple adder.

BCD and ASCII adders have the following design detail that needs to be decided upon: what to do about input that's not a valid digit. For example, what should the radix-10, ASCII adder do for $__x10 + __234$? For the adders in this assignment, the decision is to end the number at the first non-digit character starting from the right. So $__x10$ would be 10 however $__10_$ and $_10y$ would both be treated as zero because there first digit character is after non-digit characters (starting from the right).

The modules in this assignment try to use inputs is_dig_in and is_dig_out to indicate whether there is still a run of digits. (There is a small problem in the implementation, a topic for a future assignment. Anyway, the testbench doesn't test for that.)

Here is a summary of the modules in hw02.v:

aa_decimal_digit_val: Is complete, don't touch. Determines the binary value and validity
of an ASCII decimal digit.

aa_digit_val: Incomplete, see Problem 1. Should determine the binary value and validity of a radix-R digit. Tested by the testbench.

aa_full_adder: Incomplete, see Problem 2. Should add two radix-R ASCII digits.

aa_width2: Is complete, don't touch. A two-digit ASCII-coded, radix-*R* adder. Instantiates two aa_full_adder modules. Tested by the testbench. Will not work correctly when aa_digit_val or aa_full_adder don't work correctly (which is the initial state of the file).

reference_adder: Complete, don't touch. A binary adder with the same range as a 2-digit, radix-R adder. It's purpose is to compare the cost and performance of synthesized hardware.

The modules below are used to implement the testbench. Only modify these to help debug your code.

radtos: Convert an integer into a radix-R ASCII string.

aa_test: Top-level module for the testbench. It instantiates testbenches for aa_digit_val
and aa_full_adder at each radix from 2 to 16.

aa_test_digit_val: Test aa_digit_val using every possible input.

aa_test_width2: Test aa_width2 using 100 randomly chosen numbers. These numbers only contain digits.

Run the testbench on the unmodified file. It should report errors for aa_digit_val and for aa_width2.

Note: There are no points for this problem.

Problem 1: Module aa_decimal_digit_val, below, has an 8-bit input char and two outputs. Output is_dig is 1 iff char (an ASCII character) is considered a decimal digit. Output val is the value of that digit (in binary), or zero if it's not a digit.

```
module aa_decimal_digit_val
```

```
( output wire [3:0] val, output wire is_dig, input wire [7:0] char );
assign is_dig = char >= "0" && char <= "9";
assign val = is_dig ? char - "0" : 0;
endmodule
```

Originally module aa_digit_val (see hw02.v) is the same as aa_decimal_digit_val. Modify aa_digit_val so that it honors the value of its radix parameter. That is, modify it so that is_dig is 1 iff char (an ASCII character) is considered a digit in radix radix and so that val is the value (in binary) of that digit. The module should work correctly for all radices from 2 to 16. For radices ≥ 10 only use lower-case letters for alphabetic digits. Please don't change the width of val.

Run the testbench (press F9) to check whether aa_digit_val is running correctly and make sure that it is synthesizable.

To check for synthesizability of a module follow the Verilog Synthesis steps given on the procedures page up to and including the elaborate command. There should be no warnings. The synthesis script can be run with the command rc -files syn.tcl, it's purpose will be described in the next homework.

Problem 2: When completed module aa_full_adder is supposed to add together two digits of a radix-R number represented in ASCII plus a carry in. Output sum of the module is the ASCII digit of the sum, and output carry_out is 1 iff there is a carry.

Complete module **aa_full_adder** so that it operates as described. The module should instantiate two **aa_digit_val** modules and use them to generate the sum digit. The module must be synthesizable, it can be written using implicit structural or behavioral code.

Run the testbench to verify correct functioning.

To check for synthesizability of a module follow the Verilog Synthesis steps given on the procedures page up to and including the elaborate command. There should be no warnings. The synthesis script can be run with the command rc -files syn.tcl, its purpose will be described in the next homework.

Homework 3 Due: 28 September 2016

Problem 1: Module aa_digit_val, below, is the solution to Homework 2 Problem 1. It has an 8-bit input char and two outputs. Output is_dig is 1 iff char (an ASCII character) is considered a radix-R digit, where $2 \le R \le 16$, is the value of parameter radix. Output val is the value of that digit (in binary), or zero if it's not a digit.

```
module aa_digit_val
```

```
#( int radix = 10 )
 ( output uwire [3:0] val, output uwire is_dig, input uwire [7:0] char );
uwire is_dig_09 = char >= "0" && char <= "9";
uwire is_dig_af = char >= "a" && char <= "f";
uwire [3:0] val_raw = is_dig_09 ? char - "0" : char - "a" + 10;
assign is_dig = ( is_dig_09 || is_dig_af ) && val_raw < radix;
assign val = is_dig ? val_raw : 0;</pre>
```

endmodule

Provide sketches of what you expect the inferred hardware to look like for aa_digit_val as described below. *Hint: Some problems in the EE 4755 2014 Final Exam dealt with numbers in ASCII representation. The optimizations requested below must go beyond those found in the exam solution.*

(a) Show a sketch of the inferred hardware before any optimization is done.

(b) Show a sketch of the inferred hardware after some optimization has been performed.

- The sketches must show the product of human thought (in particular, the human who's name is on the submission), not a synthesis program.
- When considering the optimizations for the logic generating is_dig (including the logic for is_dig_09 and is_dig_af) recall that in general the cost of logic computing a==b is less than the cost of logic computing a>b.
- When considering the optimizations for the logic generating val think about the subtraction operations and what they actually do when is_dig is true. If necessary, work out examples of the subtraction by hand in hexadecimal.

There is another problem on the next page!

Problem 2: Module aa_full_adder from Homework 2, Problem 2 adds together two digits of a radix-R number represented in ASCII plus a carry in. The module description from the solution appears below.

```
module aa full adder
  #( int radix = 10 )
   ( output uwire [7:0] sum, output uwire carry_out, output uwire is_dig_out,
     input uwire [7:0] a, b, input uwire carry_in, input uwire is_dig_in);
  uwire [3:0] val_a, val_b;
               is_dig_a, is_dig_b;
  uwire
  aa_digit_val #(radix) dva(val_a, is_dig_a, a);
  aa_digit_val #(radix) dvb(val_b, is_dig_b, b);
  assign is_dig_out = is_dig_in && ( carry_in || is_dig_a || is_dig_b );
  uwire [4:0] sum_val = carry_in + val_a + val_b;
              carry_out = sum_val >= radix;
   assign
  uwire [3:0] sum_dig_val = carry_out ? sum_val - radix : sum_val;
  assign sum = !is_dig_out ? " " :
          sum_dig_val < 10 ? "0" + sum_dig_val : "a" + sum_dig_val - 10;</pre>
```

endmodule

An obvious objection to an ASCII-coded radix-R adder is that it uses 8 bits to represent a digit that can be represented using only $\lceil \lg R \rceil$ bits.

(a) Show the hardware that might be synthesized for the module aa_full_adder based on the description above. This should be the inferred hardware with some optimizations applied. Take care to show the number of bits at the inputs and output of units like adders and comparison logic.

(b) Compare the cost of a *d*-digit ASCII-coded radix-16 adder to a 4*d*-bit ripple adder. (Note that both adders can add numbers in the range of 0 to $2^{4d} - 1$.) Do so by estimating the cost in terms of the number of gates, and state any assumptions, such as the number of gates needed for an *x*-bit comparison unit.

Homework 4

```
Due: 12 October 2016
```

Problem 0: First, follow the instructions for account setup and homework workflow on the course procedures page, http://www.ece.lsu.edu/koppel/v/proc.html.

Look through the code in hw04.v. Module lookup_behav in file hw04.v has a w-bit input char and an *n*-element array of w-bit quantities named chars. (Parameter nelts is n and parameter charsz is w.) The module also has a 1-bit output found which is logic 1 iff any element of chars is equal to char. Finally, the module has a $\lceil \lg n \rceil$ -bit output index which is set to the element number of chars that matches char, or 0 if found is 0. Assume that no two elements of chars are identical.

For example, suppose input char is set to 102 and that chars is $\{63,124,102,92\}$. Then output found will be 1 and index will be 2. If char were 7 index would be 0 and found would be 0, if char were 63 index would be 0 and found would be 1, etc. The alert student will have recognized that n = 4 and that $w \ge 7$ in these examples.

Module lookup is coded in synthesizable behavioral form that describes combinational logic. The hw04.v file contains two other modules which are to do the same thing, lookup_linear and lookup_tree, but those modules are not yet finished.

The testbench tests all of these modules. It tests them for sizes (n) of 4, 5, 10, 15, 16, 30, 40, and 64. To change which sizes are tested (or the order in which they are tested) edit the testbench module.

To have the testbench test only some of these modules (say, skip the lookup_tree tests until after lookup_linear is working) look for the for loop with mut=0 and modify it appropriately. (It should be easy to figure out the numbers.)

A synthesis script is provided that will synthesize all three modules at different sizes and both with and very lax timing constraint and a very strict timing constraint. The script can be run using the command rc -files syn.tcl. Initially it will stop with an error. To see it run to completion before starting the assignment have it only synthesize lookup_behav (see below). Pre-set synthesis options (in file .synth_init) were chosen to reject any design that is not combinational.

If there is an error when using the synthesis script then follow the manual synthesis steps on the procedures page and look for error messages.

To change which modules are synthesized edit the set modules line (near the bottom) in file syn.tcl. The values for nelts and other items can also be changed by editing the file.

Note: There are no points for this problem.

Problem 1: Complete lookup_linear so that it does the same thing as lookup_behavioral but by using as many copies of lookup_elt as it needs. That is, lookup_linear should use generate statements to instantiate lookup_elt and it should include whatever other code is needed to use these instances to compute the correct outputs.

- Behavioral or structural code can be used.
- The module must be synthesizable.
- Assume that all elements of chars are different.

Problem 2: Complete module lookup_tree so that it performs the lookup using recursive instantiations of itself. Take care so that index is computed efficiently. *Hint: think about how to compute index efficiently when n (nelts) is a power of 2, then get the same efficiency for any n.*

If completed correctly, the cost and especially the performance at larger sizes should be better than lookup_behavioral and (unless you did an unexpectedly good job) better than lookup_linear.

- Behavioral or structural code can be used.
- The module must be synthesizable.
- Assume that all elements of chars are different.

Problem 3: Run the synthesis script and characterize the strengths and weaknesses of each module. (For example, module X has lowest cost for low-speed designs.)

In a follow-on homework assignment additional questions will be asked about these modules.

Homework 5

Due: 7 November 2016

Problem 0: This first problem provides background on the module used in this assignment. Please read the background and then solve the problems further below. The Verilog source can be found in directory hw05, however for this assignment there is no need to do anything with it.

Module ortho has one input, v, a three-element vector of signed integers, and one output, u, also a three-element vector of signed integers. The output is computed so that u is orthogonal to v in the geometric sense. For those who are rusty on linear algebra, non-zero vectors u and v are orthogonal if $u \cdot v = 0$ or $u_x v_x + u_y v_y + u_z v_z = 0$. Using Verilog notation, u is computed so that u[0]*v[0]+u[1]*v[1]+u[2]*v[2]=0 and at least one element of u is not zero. It does so by finding the smallest element of v, setting the corresponding element in u to zero, swapping the to remaining two elements, and negating one of the two. For example, if v = (4, 7, 55) then the module would set u = (0, 55, -7).

```
module ortho #( int alternative = 1, int w = 32 )
   ( output logic signed [w-1:0] u [3],
                                          input wire signed [w-1:0] v [3] );
  logic [1:0] idx_min, idx_a, idx_b;
  always_comb begin
      idx_min = 0;
      for ( int i=1; i<3; i++ )
        if ( $abs(v[i]) < $abs(v[idx_min]) ) idx_min = i;</pre>
      idx_a = ( idx_min + 1 ) % 3;
      idx_b = (idx_min + 2) \% 3;
      if ( alternative == 1 ) begin
         // The loop below is needed as a hint to the synthesis program
         // Cadence Encounter 14.28.
         for ( int i=0; i<3; i++ ) u[i] = 0;
         u[idx_min] = 0;
         u[idx_a] = v[idx_b];
         u[idx_b] = -v[idx_a];
      end else if ( alternative == 2 ) begin
         for ( int i=0; i<3; i++ )
           u[i] = idx_min == i ? 0 : idx_a == i ? v[idx_b] : -v[idx_a];
      end else $fatal(1);
   end
```

endmodule

Important: For all problems below in which hardware is shown:

- Clearly show inputs and outputs of ortho.
- Try to draw diagrams showing all hardware for **ortho** and refer to parts of the diagram in your answers below.

Problem 1: Consider the following part of the module:

```
idx_min = 0;
for ( int i=1; i<3; i++ )
    if ( $abs(v[i]) < $abs(v[idx_min]) ) idx_min = i;</pre>
```

(a) Show the hardware that will be synthesized for this fragment. (Please refer to the entire module when determining what will be synthesized.) Make reasonable optimizations. (See the next subproblem.) In this subpart show abs as a box.

(b) The synthesis program synthesizes hardware that contains four absolute value units for this code, even with effort set to high. Explain why four is too many, perhaps by referring your own version that uses fewer absolute value units.

Problem 2: Consider the part of the module below: Show the hardware that will be synthesized for this code, taking into consideration that idx_min is two bits. *Hint: This is easy. Just consider all possible values of* idx_min.

idx_a = (idx_min + 1) % 3; idx_b = (idx_min + 2) % 3;

Problem 3: Show the hardware that will be synthesized for the alternative 2 code, below, after optimization. As with the other problems, take into account the rest of the module. Look for opportunities to optimize $-v[idx_a]$ taking advantage of hardware for abs.

for (int i=0; i<3; i++)
u[i] = idx_min == i ? 0 : idx_a == i ? v[idx_b] : -v[idx_a];</pre>

Problem 4: As directed below, estimate the critical path in ortho for a w-bit instantiation. Do so using ripple-adder like implementations for absolute value, comparison, and negation. Use the performance model in which n-input AND and OR gates have delay $\lceil \lg n \rceil$ units.

(a) Find the critical path using the assumption that in hardware for an expression like a + b < c the delay through the adder must be added to the delay through the comparison unit. The answer should be a function of w.

(b) Find the critical path accounting for the fact that in ripple-like hardware for an expression like a + b < c the low bits of the comparison can start as soon as the low bits of the sum are available. The answer should be a function of w.

(c) Show a sketch of the hardware with an arrow tracing the critical path through the hardware, from input to output. Annotating that arrow with intermediate delays will help in assigning partial credit.
LSU EE 4755

Homework 6

```
Due: 29 November 2016
```

Problem 0: Review the instructions for account setup and homework workflow on the course procedures page, http://www.ece.lsu.edu/koppel/v/proc.html.

Look through the code in hw06.v. These modules compute the floating-point sum of squares of their input, similar to the midterm exam problem but without the square root.

Module mag_functional is a non-synthesizable version of the module. It is not synthesizable by Cadence Encounter because it operates on floating-point values. The module is included to help in understanding the other modules.

Module mag_comb is a synthesizable combinational version of the module. The floating-point operations are implemented using modules from the ChipWare library. See the ChipWare documentation, linked to the course references page, for details.

Module mag_seq, when finished, computes mag sequentially. It contains some code, including floating-point module instantiations, but is not complete. It has an input start to initiate the computation and an output ready to signal that the computation is complete.

Module mag_pipe, when finished, computes mag in pipelined fashion. At each positive edge it reads a vector from its input and provides the mag of a prior vector at its output.

Module mag_comb should be fastest, but of high cost. Module mag_seq should be the lowest cost module and mag_pipe should be the highest cost but also the highest throughput.

The testbench provides test inputs to the three synthesizable modules. Initially, mag_comb should pass all tests and the others should fail all tests. To facilitate debugging the first eight tests are the vectors $[0, 0, 0], [0, 0, 1], [0, 1, 0], [0, 1, 1], \ldots$ After that the vector components are randomly chosen over the range [-10, 10].

Remember that the values are IEEE 754 single-precision floating point. A 0 in this FP representation is 32'h0 and a 1.0 is 32'h3f800000, a 2.0 is 32'h40000000, and a 3.0 is 32'h40400000.

To solve this assignment it is very important to use the waveform viewer for debugging. To do so start the simulator graphically using the command irun -gui hw06.v. From the Design Browser pane locate testbench and under it look for m2 (for mag_seq) or m3 (for mag_pipe). Select objects in the Objects pane and send them to the waveform window by pressing the waveform toolbar button (it looks like a logic analyzer display) or by selecting the sequence Windows \rightarrow Send To \rightarrow Waveform. Run the simulator by pressing the play toolbar icon. If you've made changes to the Verilog or otherwise want to re-run the simulation without exiting select Simulation \rightarrow Reinvoke Simulator.

For further documentation see the SimVision documentation on the course references page, http://www.ece.lsu.edu/koppel/v/ref.html.

There is a synthesis script that will synthesize each module at high (slow) and low (fast) clock period targets. To run it use the command rc -files syn.tcl. This will take a long time to run, so only run it to satisfy your curiosity. Check for synthesizability by manually running the synthesis using the instructions on the course procedures page, http://www.ece.lsu.edu/koppel/v/proc.html.

Note: There are no points for this problem.

Problem 1: Module mag_seq, when completed, will compute the magnitude sequentially. It should start when input start is logic 1 on a positive clock edge and it should signal completion by setting output ready to one several clock cycles later. The module should use one floating-point multiply and one FP add unit. The module already instantiates these, and contains some logic for performing the different steps, including setting ready (though not at the right time). Complete the module so that it works correctly. See the checklist in the Verilog source for hints and reminders.

Problem 2: Module mag_pipe, when completed, will compute the magnitude in pipelined fashion. That is, it will read a vector from its inputs at every clock cycle, and will present a magnitude at its output every cycle. The magnitude should be for the vector that was at input v nstages cycles in the past, where nstages is a constant in the module indicating the number of stages. The inputs to the module are available near the end of the clock cycle and the outputs are expected at the beginning of the clock cycle.

Choose the number of stages needed to maximize throughput. That is, minimize the delay in each stage. Of course, within that constraint minimize cost.

Pay close attention to where data is. Remember that at any one time the module will hold data for **nstages** different vectors. Use a pipeline diagram to make sure that data from the different vectors don't get mixed up. A common problem is a newly arriving vector overwriting data for an earlier vector. That's avoided by moving data long from stage to stage.

Be sure to use the waveform viewer for debugging. Remember that the first eight test vectors consists of 0 and 1 components, making debugging easy.

10 Fall 2015

LSU EE 4755 Homework 1 Due: 9 September 2015

The questions below can be answered without using EDA software, paper and pencil will suffice. Please turn in the solution on paper. Homework 2 will require the use of Verilog implementations. Those who are rusty about the correspondence between Verilog code and hardware might want

to look at the solution to EE 3755 Fall 2013 Homework 1, at http://www.ece.lsu.edu/ee3755/2013f/hw01_sol.pdf.

Problem 1: The routine shift_right_fixed_amt uses the >> operator to perform the right shift. Perhaps you are wondering if the operation is an arithmetic right shift or a logical right shift. (In a logical right shift the vacated bit positions are always set to zero, in an arithmetic shift they are set to the MSB of the input.) Look up the operation performed by this operator in the SystemVerilog 2012 documentation.

```
module shift_right_fixed_amt
#( int fsamt = 4 ) // Fixed shift amount.
  ( output wire [15:0] shifted,
    input wire [15:0] unshifted,
    input wire shift );
  // If shift is true shift by fsamt, otherwise don't shift.
  //
  assign shifted = shift ? unshifted >> fsamt : unshifted;
```

endmodule

(a) Indicate the section and page in which this information can be found.

(b) Show how the module can be modified to perform the other kind of shift (if it's currently arithmetic, make it logical, if it's currently logical make it arithmetic).

Problem 2: Appearing below are two variations on a min_4 module that finds the minimum of four unsigned integers. Both of these modules instantiate the following min_2 module.

(a) Draw a diagram of the hardware that will be synthesized for the min_4_t module below. Your diagram should include two-input multiplexors and a comparison module. To get an idea of what to draw, see the EE 3755 Homework solution mentioned at the top of this assignment.

```
module min_4_t
#( int elt_bits = 4 )
  ( output [elt_bits-1:0] elt_min,
      input [elt_bits-1:0] elts [4] );

  wire [elt_bits-1:0] im1, im2;
  min_2 #(elt_bits) m1( im1, elts[0], elts[1] );
  min_2 #(elt_bits) m2( im2, elts[2], elts[3] );
  min_2 #(elt_bits) m3( elt_min, im1, im2 );
endmodule
```

(b) Draw a diagram of the hardware that will be synthesized for the \min_4_1 module below. Your diagram should include two-input multiplexors and a comparison module.

```
module min_4_1
#( int elt_bits = 4 )
  ( output [elt_bits-1:0] elt_min,
      input [elt_bits-1:0] elts [4] );

wire [elt_bits-1:0] im1, im2;
min_2 #(elt_bits) m1( im1, elts[0], elts[1] );
min_2 #(elt_bits) m2( im2, im1, elts[2] );
min_2 #(elt_bits) m3( elt_min, im2, elts[3] );
endmodule
```

(c) Which of the two modules above would you expect to have lower cost? Which would you expect to be faster? Briefly explain.

Problem 3: The module min_4_err below is correct Verilog, but it won't do what we want.

```
module min_4_err
#( int elt_bits = 4 )
  ( output [elt_bits-1:0] elt_min,
      input [elt_bits-1:0] elts [4] );

wire [elt_bits-1:0] im;
min_2 #(elt_bits) m1( im, elts[0], elts[1] );
min_2 #(elt_bits) m2( im, im, elts[2] );
min_2 #(elt_bits) m3( elt_min, im, elts[3] );
```

endmodule

(a) Explain why it's correct Verilog yet provides the incorrect result.

(b) Look up uwire in the SystemVerilog standard and explain how that might help catching such errors.

Problem 4: Appearing below is yet another variation on min_4, this one attempting to take advantage of a special case by using generate statements. The module is correctly using generate statements to handle a special case. Do you think the synthesized hardware will be less expensive for the special case beyond the reduction in cost for using fewer bits. Hint: Think about what the comparison unit and mux would look like with 1-bit inputs and how such logic can be optimized.

Note: In the original assignment this problem had a typo, which made the Verilog illegal. Further, the phrase above starting "beyond the reduction" was not in the original question, making it difficult to see what was really being asked. The answer below is for the corrected question.

```
module min_4_special1
#( int elt_bits = 4 )
( output [elt_bits-1:0] elt_min,
    input [elt_bits-1:0] elts [4] );
if ( elt_bits == 1 ) begin
    assign elt_min = elts[0] && elts[1] && elts[2] && elts[3];
end else begin
    wire [elt_bits-1:0] im1, im2;
    min_2 #(elt_bits) m1( im1, elts[0], elts[1] );
    min_2 #(elt_bits) m2( im2, im1, elts[2] );
    min_2 #(elt_bits) m3( elt_min, im2, elts[3] );
end
```

Problem 5: The module below handles another special case, in this case the case where the first element is zero.

```
module min_4_special2
#( int elt_bits = 4 )
  ( output [elt_bits-1:0] elt_min,
    input [elt_bits-1:0] elts [4] );
wire [elt_bits-1:0] im1, im2;
if ( elts[0] == 0 )
    assign elt_min = 0;
else begin
    min_2 #(elt_bits) m1( im1, elts[0], elts[1] );
    min_2 #(elt_bits) m2( im2, im1, elts[2] );
    min_2 #(elt_bits) m3( elt_min, im2, elts[3] );
end
```

endmodule

(a) Explain why the module is illegal Verilog.

(b) Explain why what it's trying to do would be unlikely to help within a larger design. *Hint: Think about critical path.*

LSU EE 4755

Homework 2 Due: 16 September 2015

Problem 0: Follow the instructions for account setup and homework workflow on the course procedures page, http://www.ece.lsu.edu/koppel/v/proc.html. Run the testbench on the unmodified file. There should be errors on all but the min_4 (Four-element) module. Try modifying min_4 so that it simulates but produces the wrong answer. Re-run the simulator and verify that it's broken. Then fix it.

Note: There are no points for this problem.

Problem 1: Module min_n has an elt_bits-bit output elt_min and an elt_count-element array of elt_bits-bit elements, elts. Complete min_n so that elt_min is set to the minimum of the elements in elts, interpreting the elements as unsigned integers. Do so using a linear connection of min_2 modules instantiated with a genvar loop. (A linear connection means that the output of instance *i* is connected to the input of instance *i* + 1.)

Verify correct functioning using the testbench.

Problem 2: Module min_t is to have the same functionality as min_n. Complete min_t so that it recursively instantiates itself down to some minimum size. The actual comparison should be done by a min_2 module.

Verify correct functioning using the testbench.

Problem 3: By default the synthesis script will synthesize each module for two array sizes, four elements and eight elements.

(a) Run the synthesis script unmodified. Use the command rc -files syn.tcl. Explain the differences in performance between the different modules.

(b) Modify and re-run the synthesis script so that it synthesizes the modules with elt_bits set to 1.

The synthesis program should do a better job on the behavioral and linear models. Why do you think that is? *Hint: The 1-bit minimum module is equivalent to another common logic component that the synthesis program can handle well.*

LSU EE 4755

Homework 3

Due: 7 October 2015

Problem 1: Solve EE 4755 Fall 2014 Midterm Exam Problem 4 and Problem 5. The solutions are available, but please make an honest effort to solve them on your own.

Problem 2: The homework Verilog file, hw04.v contains two versions of the sequential shifter used in class, those modules are also reproduced below. Module shift_lt_seq_d_live, is based on the version written during class and module shift_lt_seq_d is the one prepared in advance. Though both work correctly their timing is not identical.

(a) Show the hardware that might be synthesized for each module using the default parameters. Include reasonable optimizations, the initially inferred hardware can be omitted. This should be a human-to-human diagram, don't show output of a synthesis program.

 $\left(b\right)$ The two modules differ in their timing. Using your hardware diagrams explain any differences in:

- The register-to-register delay within the module.
- How far in advance of the positive edge module inputs must become stable.
- How long after the positive edge module outputs will be available.

As with the previous part, this should be done by hand though synthesis tools can be used to help solve the problem.

An answer might look like this: "For register-to-register delay Module A is slower because its critical path has two multipliers, whereas in module B the two multiplications are split between cycles and so at most one multiplier is on the critical path. In module A inputs connect directly to a divider, and so they must arrive long before the positive edge, whereas in module B inputs can arrive just before the positive edge because" Of course, this question does not have a module A or B, nor does it really have multipliers and dividers.

Modules on next page.

```
module shift_lt_seq_d_live
  #( int wid_lg = 6,
     int num_shifters = 1,
     int wid = 1 << wid_lg )</pre>
   ( output logic [wid-1:0] shifted,
     output logic ready,
     input [wid-1:0] unshifted,
     input [wid_lg-1:0] amt,
     input start,
     input clk );
   localparam int bits_per_seg = wid_lg / num_shifters;
   logic [num_shifters-1:0] shift;
   wire [wid-1:0] shin[num_shifters-1:-1];
   assign shin[-1] = shifted;
   for ( genvar i=0; i<num_shifters; i++ ) begin</pre>
      localparam int fs_amt = 2 ** ( i * bits_per_seg );
      shift_fixed #( wid_lg, fs_amt ) sf( shin[i], shin[i-1], shift[i] );
   end
   logic [num_shifters-1:0][bits_per_seg-1:0] cnt;
   always_ff @( posedge clk ) begin
      if ( start == 1 ) begin
         ready = 0;
         cnt = amt;
         shift = 0;
         shifted = unshifted;
      end else begin
         if ( cnt == 0 ) ready = 1;
         for ( int i=0; i<num_shifters; i++ ) begin</pre>
            shift[i] = cnt[i] > 0;
            if ( cnt[i] != 0 ) cnt[i]--;
         end
         shifted = shin[num_shifters-1];
      end
   end
endmodule
```

Another module on next page.

```
module shift_lt_seq_d
  #( int wid_lg = 4,
     int num_shifters = 2,
     int wid = 1 << wid_lg )</pre>
   ( output logic [wid-1:0] shifted,
     output wire ready,
     input [wid-1:0] unshifted,
     input [wid_lg-1:0] amt,
     input start,
     input clk );
   localparam int cnt_bits = ( wid_lg + num_shifters - 1 ) / num_shifters;
   logic [num_shifters-1:0][cnt_bits-1:0] cnt;
   wire [wid-1:0] inter_sh[num_shifters-1:-1];
   assign inter_sh[-1] = shifted;
   for ( genvar i = 0; i < num_shifters; i++ ) begin</pre>
      localparam int shift_amt = 1 << i * cnt_bits;</pre>
                 shift = cnt[i] != 0;
      wire
      shift_fixed #(wid_lg,shift_amt) sf( inter_sh[i], inter_sh[i-1], shift );
   end
   always_ff @( posedge clk )
      if ( start == 1 ) begin
         shifted = unshifted;
         cnt = amt;
      end else if ( cnt > 0 ) begin
         shifted = inter_sh[num_shifters-1];
         for ( int i=0; i<num_shifters; i++ ) if ( cnt[i] ) cnt[i]--;</pre>
      end
   assign ready = cnt == 0;
endmodule
```

LSU EE 4755

Homework 4

```
Due: 12 October 2015
```

Problem 0: Follow the instructions for account setup and homework workflow on the course procedures page, http://www.ece.lsu.edu/koppel/v/proc.html. Run the testbench on the unmodified file. There should be errors on the shift_lt_seq_d_sol module, but the others should run correctly. Run the Note: There are no points for this problem.

Problem 1: The homework Verilog file, hw04.v, contains a module shift_lt_seq_d_sol which is based on shift_lt_seq_d. It contains an always_ff block that assigns the same variables that are assigned in shift_lt_seq_d, however it assigns them from variables of the same name with next_ prefixed:

```
always_ff @( posedge clk ) begin
  ready = next_ready;
  shifted = next_shifted;
  shift = next_shift;
  cnt = next_cnt;
end
```

Add code so that these next_ objects will be assigned values from combinational logic, and so that the resulting module describes the same hardware as shift_lt_seq_d. A hand-drawn diagram of synthesized hardware should be identical, though it's possible that there will be small differences in the actual output of a synthesis program.

The added code can be implicit structural or behavioral, but it must synthesize to combinational logic.

Problem 2: Module shift_lt_seq_d_live takes one more cycle to produce a result than module shift_lt_seq_d. Module shift_lt_seq_d_p2 initially is identical to shift_lt_seq_d_live.

(a) Modify shift_lt_seq_d_p2 so that it uses one less cycle to produce a result without changing the number of shifters per stage. There are two possible ways of doing this, performing some work in the same cycle that the start signal arrives, or doing work in the cycle when ready is set to 1. Either method is fine.

(b) Run syn.tcl and compare the cost and performance of your design and shift_lt_seq_d_live. Comment on the differences. An answer might start "The cost was about the same because the same hardware was used...".

LSU EE 4755 Homework 5 Due: 23 October 2015 17:00

Problem 1: The homework Verilog file, hw05.v, contains something similar to the streamlined multiplier presented in class, mult_seq_stream, and even more streamlined versions of the multiplier, mult_seq_stream_2, and mult_seq_stream_3. These modules are reproduced at the end of this assignment. For an HTML version visit

http://www.ece.lsu.edu/koppel/v/2015/hw05.v.html. See the 2014 midterm exam for similar problems.

 $\left(a\right)$ Show the hardware that will be synthesized for each module for the default parameters. Show the module after optimization.

(b) Estimate the clock frequency of each module based on the following assumptions:

Latch delay: 10 units. Multiplexor latency: 2 units. Latency of a *n*-bit adder: $5\lceil \lg n \rceil$ units. Latency of an *n*-input gate: $\lceil \lg n \rceil$ units.

(c) Why would module $mult_seq_stream_3$ provide a result in less time than the other two, even assuming that the clock frequency for all the modules was the same?

```
module mult_seq_stream #( int wid = 16 )
   ( output logic [2*wid-1:0] prod,
     input logic [wid-1:0] plier,
     input logic [wid-1:0] cand,
     input clk);
   localparam int wlog = $clog2(wid);
   logic [wlog-1:0] pos;
   logic [2*wid-1:0] accum;
   always @( posedge clk ) begin
      logic [wid:0] pp;
      if ( pos == 0 ) begin
         prod = accum;
         accum = cand;
         pos = wid - 1;
      end else begin
         pos--;
      end
      // Note: the multiplicand is in the lower bits of the accumulator.
      11
      pp = accum[0] ? { 1'b0, plier } : 0;
      // Add on the partial product and shift the accumulator.
      //
      accum = { { 1'b0, accum[2*wid-1:wid] } + pp, accum[wid-1:1] };
```

end

```
module mult_seq_stream_2 #( int wid = 16 )
   ( output logic [2*wid-1:0] prod,
     input logic [wid-1:0] plier,
     input logic [wid-1:0] cand,
     input clk);
   localparam int wlog = $clog2(wid);
   logic [wlog-1:0] pos;
   logic [2*wid-1:0] accum;
   always @( posedge clk ) begin
      if ( pos == 0 ) begin
         prod = accum;
         accum = { 1'b0, cand[0] ? plier : wid'(0), cand[wid-1:1] };
         pos = wid - 1;
      end else begin
         logic [wid:0] pp;
         // Note: the multiplicand is in the lower bits of the accumulator.
         11
         pp = accum[0] ? plier : 0;
         // Add on the partial product and shift the accumulator.
         11
         accum = { { 1'b0, accum[2*wid-1:wid] } + pp, accum[wid-1:1] };
         pos--;
      end
```

end

```
module mult_seq_stream_3 #( int wid = 16 )
   ( output logic [2*wid-1:0] prod,
     input logic [wid-1:0] plier,
     input logic [wid-1:0] cand,
     input clk);
   localparam int wlog = $clog2(wid);
   logic [wlog-1:0] pos;
   logic [2*wid-1:0] accum;
   always @( posedge clk ) begin
      if ( pos == 0 ) begin
         accum = { 1'b0, cand[0] ? plier : wid'(0), cand[wid-1:1] };
         pos = wid - 1;
      end else begin
         logic [wid:0] pp;
         /\!/ Note: the multiplicand is in the lower bits of the accumulator.
         11
         pp = accum[0] ? plier : 0;
         // Add on the partial product and shift the accumulator.
         11
         accum = { { 1'b0, accum[2*wid-1:wid] } + pp, accum[wid-1:1] };
         if ( pos == 1 ) prod = accum;
         pos--;
      end
   end
```

LSU EE 4755

Homework 6

Due: 2 December 2015

Problem 0: The homework Verilog file, hw06.v, contains something similar to the integer compression modules presented in class. (Follow the homework workflow instructions on the course procedures page to get a copy of the assignment package.) These modules compress an ASCII character stream by substituting a binary-encoded integer for a string of ASCII digits. These modules were based on 2014 Homework 4. Feel free to look at that assignment an solution for help.

Module icomp_none is a version of the module that does no compression at all. It does though implement the handshaking protocol so that characters can be passed from input to output. This module can be studied to help understand how the others work.

Module icomp_2cyc is one of the compression modules covered in class. It computes the encoded value in stage 0, and checks for overflow in stage 1. Don't modify this module, save if for reference. Module icomp_sol is initially identical to icomp_2cyc, but it should be modified as part of this assignment.

The testbench is set to simulate icomp_sol on a sample test string. At the end it will report the amount of compression and whether there was any errors. The testbench also prints out a trace showing some module inputs and outputs and the status of internal signals. Examine the testbench code to see how this is done and feel free to modify it to add signals of your own. A more detailed trace of execution can be obtained using the SimVision gui. To start that use the command irun hw06.v -gui. See http://www.ece.lsu.edu/koppel/v/v/s/SimVisionIntro.pdf for documentation. (On campus access only without password.)

The synthesis script will synthesize the modules icomp_2cyc and icomp_sol. Use the synthesis script to make sure that your designs are synthesizable and to determine their cost and performance.

(There is nothing to turn in for this assignment.)

Problem 1: In module icomp_sol there is a declaration of a variable named val_encode_size_1, but no uses of that variable. Add code to that module so that val_encode_size_1 is set to the number of bytes that are needed for the number currently in the register val_encode_1. For example, if val_encode_1 has a 0, then val_encode_size_1 should be 0. If val_encode_1 has a 123 then val_encode_size_1 should be 1 (one byte), if val_encode_1 has a 300 then val_encode_size_1 should be 2 (for 2 bytes), etc.

To help with your solution add code to the testbench to show the value of this variable.

Problem 2: Modify module icomp_sol so that a group of ASCII digits is compressed into the smallest number of bytes needed, up to max_chars. For example, if max_chars is 4 then just use one byte to compress 200, two bytes for 4000, and for 1234567890123 use a four-byte integer (for 1234567890) followed by a one byte integer (for 123).

Precede the compressed integer by the character 128 plus the number of bytes in the compressed number. For example, if the compressed value takes two bytes then where the first character of the uncompressed value would go emit a 130, then the next two characters should be the compressed number. (See how char_out is assigned in the unmodified code.)

To solve this problem you'll need to understand how the existing code works, how to interpret the trace output provided by the simulator, and how to use the SimVision waveform viewer. Random guesses based on a vague understanding will get you nowhere.

- The module should be written for arbitrary values of max_chars.
- Make sure that the testbench is not reporting errors.

 $\leftarrow \ \rightarrow \ \text{Homework} \ 6$

• Make sure that your module is compressing the string.

11 Fall 2014

LSU LSU EE 4755 Homework 1 Due: 15 September 2014

Follow the instructions for class account setup and Verilog Homework Workflow, which can be found on http://www.ece.lsu.edu/koppel/v/proc.html. Run the simulator code on the unmodified assignment. The output should show errors for two modules.

Problem 1: Module shift_right1 is supposed to perform a logical right shift on a 16-bit quantity, but it is not working properly, perhaps because the designer left for a vacation before finishing it and returned thinking that he or she had already finished it. Fix the problem.

Module shift_right1 is written in a behavioral style, and in a way which is not synthesizable. For this problem, **do not** try to make the code synthesiable, just get the module to perform the shift properly so that the testbench does not report an error. (The module for the next problem is synthesizable.)

Your solution should assign **shifted** one bit at a time, as does the existing code. (In other words, don't just use the right shift operator.) The testbench output might provide clues to what the problem is. *Hint: The problem can be fixed with one or two lines of code*.

Problem 2: Module shift_right2 is also supposed to perform a logical right shift. It's not working either, because it hasn't been finished. When finished shift_right2 will make use of four shift_right_fixed modules. A shift_right_fixed module can shift by two possible amounts, zero bits (which of course is no shift at all) or fsamt bits, where fsamt is the value of a parameter.

The shift_right2 module so far has instantiated one shift_right_fixed module and set the parameter to 8 (the #(8) indicates that the parameter is set to 8). The shift_right2 module should instantiate three more shift_right_fixed modules, one each for shifts of 4, 2, and 1 bit. Instantiate the modules and connect them together so that shift_right2 works correctly.

Hint: A correct answer will require no additional logic (beyond the three additional shifters) only declarations.

LSU EE 4755 Homework 2 Due: 26 September 2014

The Homework 2 code package contains four unsigned integer floating point modules and a testbench. The first two modules, mult_behav_1 and mult_behav_2 already work, the other two, mult_linear and mult_tree, are mostly empty and are to be completed as part of this assignment. The first two multipliers are synthesizable, though they were not written to be synthesized. If this assignment is completed correctly the other two multipliers will be synthesizable too.

Multiplier mult_behav_1 is a simple-as-possible implementation, the intent is to provide a correct result to use to check the other modules. Nevertheless it is synthesizable with Cadence RC, which will substitute an integer multiply library function from the ChipWare library.

Multiplier mult_behav_2 computes the multiplication itself by adding partial sums. (See http://www.ece.lsu.edu/ee3755/2013f/l07.v.html for a quick review of integer multiplication. Don't go beyond the long-hand procedure for this assignment.)

Warning: DO NOT attempt to find Verilog code for multipliers and use them for the solution. You will learn nothing by doing so and will be unprepared for the midterm exam.

Problem 0: Copy the code package from /home/faculty/koppel/pub/ee4755/hw/2014f/hw02. Verify that everything is working by running the simulation on the unmodified file. It should report a 0% error rate for mult_behav_2 and a 100% error rate for the linear and tree multipliers.

Problem 1: Synthesize mult_behav_1 and mult_behav_2 following the steps for synthesis on the course procedures page.

(a) Indicate the area and critical path delay for each module.

(b) Explain why one might be better than the other.

Problem 2: Complete mult_linear to that it performs a multiplication using wid instances of good_adder connected linearly. This module will be sort of a structural version of mult_behav_2. Use generate statements to instantiate the adders and make sure that the design is synthesiable.

Note that in this multiplier instance i of the adder cannot start until i - 1 finishes (that's an oversimplification, but it's true enough).

Problem 3: Complete mult_tree so that the adders are connected in a tree-like fashion. Let a and b be the two w-bit operands of the multiplier. There should be w/2 adders near the leaves which add two partial products. (There are w partial products, partial product $i \in [0, w-1]$ is $a2^i$ if b_i is 1, or 0 if b_i is 0, where b_i is the digit at bit position i.) At the next level there will be w/4 adders which each add the sum of two adders from the lower level, and so on.

First try to solve this using 2w-bit adders. If you are feeling clever optimize your solution by using (w + 2)-bit adders for the first row, (w + 4)-bit adders for the second row, etc.

As before, the design must be synthesiable.

Problem 4: Perform synthesis on your two modules.

(a) Indicate the area and delay of each module.

(b) Indicate which module you *expected* to be fastest and explain why. If that's different than the one that really is fastest, give a possible reason.

LSU LSU EE 4755

Homework 3

Due: 24 October 2014

The Homework 3 code package contains a simple behavioral multiplier and several sequential multipliers. It also contains a synthesis script in file syn.cmd.

Updated 18 October 2014, 18:00:29 CDT

Problem 0: Copy the code package from /home/faculty/koppel/pub/ee4755/hw/2014f/hw03. Verify that everything is working by running the simulation on the unmodified file. It should report a 0% error rate for all modules.

Problem 1: The module mult_seq_csa is a sequential multiplier that instantiates an adder, however unlike mult_seq_ga shown in class, mult_seq_csa instantiates a carry-save adder from the Chipware library, CW_csa. The carry save adder computes the sum of three integers, a, b, and c (those are the port names). It produces two sums, which we'll call sum_a and sum_b (the port names for these are carry and sum). All of these ports are w bits wide, where w is a parameter. The actual sum of a, b, and c is obtained by adding together outputs sum_a and sum_b using a conventional adder. Carry save adders are used when there many integers to be added. Some arrangement (linear, tree) of many carry-save adders will produce a sum_a and sum_b, which will be added by a single conventional (called carry-propagate) adder.

The advantage of a carry save adder is that it can compute a sum of w-bit numbers in O(1) time (the amount of time is not affected by w), which of course is much better than the O(w) time for a ripple adder or the $O(\log w)$ time for much more expensive carry look-ahead adders. The performance advantage of a CSA is lost for mult_seq_csa because the module only computes one partial product at a time.

(a) Sketch the hardware that will be synthesized for mult_seq_csa. Show the carry-save adder and other major units as boxes, but be sure to show registers, multiplexors, and other such components. Do not show the actual output produced by an actual synthesis program. (It's okay if you look at a synthesis program's output.)

(b) Based on this sketch of synthesized hardware, explain why the benefit of using a CSA is lost. Also explain how the module can be made a little faster (with a small change), but is still not a good way to use a CSA.

Problem 2: Module mult_seq_csa_m initially contains the *m*-partial-products-per-cycle module that we did in class. In this problem modify it to use CSA's, and avoid the issue identified in the previous problem.

(a) Modify mult_seq_csa_m so that it uses the carry-save adder to compute m partial products per cycle. Use generate statements to instantiate the CSA's, and of course, connect them appropriately. (In class we used generate statements for the pipelined adder to instantiate stages, that code is in mult_pipe_ia in the same file as the assignment.)

(b) Sketch the hardware that you expect to be synthesized for an m = 2 version. Make sure that your design does not do something foolish with the conventional adder.

Problem 3: Run the synthesis program to compare the cost and performance of mult_seq_csa_m to mult_seq_m. The synthesis script syn.cmd can be used to synthesize these modules at different sizes. To run it use the command rc -files syn.cmd. Feel free to modify the script. (It is written in TCL, it should be easy to find information on this language.)

(a) Show the cost and performance versus m for these modules.

(b) If you solved the previous problem correctly the total delay shown for mult_seq_csa_m should be wrong. Explain why, and (optional) if you like try modifying syn.cmd to fix it.

(c) Explain how you might expect the delay of $mult_seq_csa_m$ to change with increasing m? Explain your expectation and whether the synthesis results bear that out.

LSU EE 4755

Homework 4

Due: 24 November 2014

Problem 0: Copy the code package from /home/faculty/koppel/pub/ee4755/hw/2014f/hw04. Verify that everything is working by running the simulation on the unmodified file. It should report that there is correct output but no compression:

```
Correct output, strings match. But no compression!
In size 117 bytes, out size 117 bytes.
```

Problem 1: Module asc_to_bin is to filter a stream of ASCII characters so that ASCII decimal numbers are replaced by binary numbers preceded by an escape character. The idea is to reduce the size of data streams that contain lots of large numbers. For example, consider the sentence, "There are 31536000 seconds in a year." The module asc_to_bin should replace that sequence of eight ASCII characters 31536000 with an escape character and an integer encoding of the number.

The module has an 8-bit input and output for the character, char_in and char_out. There is a 1-bit input can_insert which is true when the module can read a character from char_in. If input insert_req is asserted when can_insert is true then the character on char_in will be read.

There is a 1-bit output can_remove which is true when the character on char_out is valid. (It would not be valid if the module does not contain any characters and for other reasons.) If input remove_req is set to 1 and can_remove is true then the character at char_out will change to the next character or, if that's the last available character, can_remove will go to zero.

There is also a 1-bit input reset. If reset is high at the positive edge of the clock then the module should reset itself.

Initially in the homework package, module asc_to_bin passes through characters unchanged. Modify it so that it converts ASCII decimal numbers to binary as described above.

At the end of the simulation the testbench will indicate whether the output string is correct, and the original and compressed sizes. For example, the output using the unmodified code package will be:

Correct output, strings match. But no compression!

```
In size 117 bytes, out size 117 bytes.
```

The testbench also provides a trace showing some information each time a character is removed. For the unmodified code,

```
ncsim> run
С
  79 = 0
            tail
                  1 head
                          0
c 110 = n
            tail
                  3 head
                          1
c 101 = e
            tail
                  4 head
                          2
  32 =
            tail 7 head 3
с
С
  49 = 1
            tail
                  8 head
                         4
```

The character removed is shown as a decimal number and as a character, for example 110 and "n" for the second line. Also shown are the values of two objects in the asc_to_int module, tail and head. Feel free to add your own variables to the list. Search for "Trace execution" to find the code that prints this trace.

The parameter max_chars indicates the maximum size of the integer that should be created. Currently the testbench expects all integers to be of this size.

Keep the following in mind:

- Do not convert a number to binary if it would take more space than the original.
- The module must be synthesizable.
- The synthesized hardware must be reasonably efficient.

For extra credit, modify both the asc_to_bin module and the testbench so that asc_to_bin can compress a string of ASCII digits to the smallest integer (in multiple of bytes) that can hold the integer. (The current behavior is to use one size integer, determined by parameter max_chars.)

Problem 2: Synthesize your module.

(a) Indicate the cost and performance with and without timing optimization. (With timing optimization means using define_clock.)

(b) Even if define_clock is used, the synthesis program won't optimize all paths, only those with both ends affected by the clock. Show how to use the Encounter external_delay command to get the proper timing optimization.

12 Spring 2001

EE 4702

Homework 1 Due: 12 February 2001

Solve this problem by modifying a copy of http://www.ee.lsu.edu/v/2001/hw01.html which can be found in /home/classes/ee4702/files/v/hw01.v. See

http://www.ee.lsu.edu/v/proc.html for instructions on running the simulator. Alternate instructions can be found in Lesson 7 of the ModelSim Tutorial, linked to the references web page, http://www.ee.lsu.edu/v/ref.html. The links are clickable when this assignment is viewed with Acrobat Reader. The ModelSim tutorial and other documentation can also be accessed from the Help menu on the ModelSim GUI (started by the command vsim -gui).

Problem 1: Copy the homework template, /home/classes/ee4702/files/v/hw01.v, into a subdirectory named hw in your class account. Simulate the welcome module in the homework template. If it works, a message should tell you to proceed to problem 2.

Problem 2: In Homework 2 (yes, this is Homework 1) a priority encoder will be designed which has an *n*-bit input and an *n*-bit output. Let bit positions be numbered from n - 1 to 0 and let bit zero be the least significant and the rightmost bit when written. Output bit $i, n - 1 \ge i \ge 1$, shall be 1 if input bit i is 1 and if input bits $i - 1, \ldots, 0$ are all 0, otherwise output bit i is zero. Output bit 0 is 1, otherwise it is 0. Therefore, at most one output bit is 1, corresponding to the first input bit that is 1. Some examples: $0011 \rightarrow 0001, 0110 \rightarrow 0010, 0111 \rightarrow 0001$, and $0000 \rightarrow 0000$, where foo \rightarrow bar indicates that output bar is expected for input foo.

The encoder will be constructed from n cells in the same way a ripple adder is constructed from binary full adder cells. These cells will be designed here, in Homework 1.

Complete module priority_encoder_1_es in the homework template so that it is a Verilog explicit structural description of the priority encoder cell. Do not rename the module or change any of its ports.

Problem 3: Complete module priority_encoder_1_is in the homework template so that it is a Verilog implicit structural description of the priority encoder cell. Do not rename the module or change any of its ports.

Problem 4: Complete module priority_encoder_1_b in the homework template so that it is a Verilog behavioral description of the priority encoder cell. Do not rename the module or change any of its ports.

Problem 5: Complete module $test_pe$ in the homework template so that it tests the three modules designed above. The test should be by exhaustion. That is, apply all possible combinations of inputs to each module and verify the outputs. (Consider only 0 and 1 for inputs, but watch for x or z at the outputs, which would indicate an error.)

Module test_pe has four one-bit outputs. Output done should be set to 1 when the tests are complete. When done is 1 outputs okay_b, okay_is, and okay_es shall be set to 1 if the respective module works correctly or set to 0 if the respective module does not work correctly.

As before, do not rename the module or change any of its ports.

EE 4702 Homework 2 Due: 22 Feb 2001, 23:59:59 CST

Solve this problem by modifying a copy of http://www.ee.lsu.edu/v/2001/hw02.html (or .v) which can also be found in /home/classes/ee4702/files/v/hw02.v. See

http://www.ee.lsu.edu/v/proc.html for instructions on running the simulator. Alternate instructions can be found in Lesson 7 of the ModelSim Tutorial, linked to the references web page, http://www.ee.lsu.edu/v/ref.html. The links are clickable when this assignment is viewed with Acrobat Reader. The ModelSim tutorial and other documentation can also be accessed from the Help menu on the ModelSim GUI (started by the command vsim -gui).

In this assignment a priority encoder will be designed which has an n-bit input, called request, and an n-bit output, called grant. Let bit positions be numbered from n - 1 to 0 and let bit zero be the least significant and the rightmost bit when written. Output bit i, $n - 1 \ge i \ge 1$, shall be 1 if input bit i is 1 and no lower-order bit, if any, is 1. Otherwise output bit i is zero. Therefore, at most one output bit is 1, corresponding to the first input bit that is 1. Some examples: $0011 \rightarrow 0001$, $0110 \rightarrow 0010$, $0111 \rightarrow 0001$, and $0000 \rightarrow 0000$, where foo \rightarrow bar indicates that output bar is expected for input foo.

Problem 1: Complete the module priority_encoder_8_b so that it is a behavioral description of an 8-bit priority encoder as described above (and in Homework 1). Just include behavioral code, **do not** instantiate other modules.

Problem 2: Modify the priority_encoder_1_es modules from Homework 1 so that each gate has a delay of one cycle.

Problem 3: Complete the module priority_encoder_8_es so that it is an explicit structural description of a priority encoder constructed using priority_encoder_1_es modules from the previous problem. They may be instantiated within priority_encoder_8_es or you can provide an intermediate module, say priority_encoder_4_es, which instantiates priority_encoder_1_es.

Problem 4: Complete the module test_pe_8 to that it tests priority_encoder_8_b and priority_encoder_8_es. Unlike the testbench in Homework 1, this testbench can be commanded to perform the test any number of times. Module test_pe_8 has one input, start, and three outputs, done, okay_b, and okay_es. Initially, done should be 0. When start is 1 output done should be set to zero. At this point, no other outputs should change until start goes to zero. After start goes to zero the modules should be tested. When the tests are complete set okay_b and okay_es based on the outcome of the test. After setting okay_b and okay_es set done to 1. At this point, wait for start to go to 1 and repeat the process.

Use module $\texttt{tests_pe_8}$ (two esses) to test the timing of your testbench. The testbench should be able to catch all errors, including undefined outputs.

EE 4702

Homework 3

Due: 4 April 2001.

Solve this problem by modifying a copy of http://www.ee.lsu.edu/v/2001/hw03.html (or .v) which can also be found in /home/classes/ee4702/files/v/hw03.v. See

http://www.ee.lsu.edu/v/proc.html for instructions on running the simulator. Alternate instructions can be found in Lesson 7 of the ModelSim Tutorial, linked to the references web page, http://www.ee.lsu.edu/v/ref.html. The links are clickable when this assignment is viewed with Acrobat Reader. The ModelSim tutorial and other documentation can also be accessed from the Help menu on the ModelSim GUI (started by the command vsim -gui).

Problem 1: Write a Verilog behavioral description of a microwave oven controller in module microwave_oven_controller. The module has two inputs, key_code and clk. The user operates the oven through a keypad, the keypad has a six-bit output which is connected to the controller through the port named key_code. Values for key_code are given in the template. As with the calculator described in class, when no key is pressed key_code is key_none (see the template). The keypad is de-bounced and a user must release one key before pressing another. One-bit input clk is a 64 Hz clock.

The controller has six outputs, beep, dmt dmu, dst, dsu, and mag_on. When one-bit output beep is 1 the oven will emit a tone. Four-bit output dmt (display minute tens) is connected to the tens digit of the oven minutes display, output dmu (display minute units) is connected to the unit digit of the minutes display, dst is connected to the tens digit of the seconds display, and dsu is connected to the unit digit of the seconds display. The display will properly render digit values 0-9 and will display nothing for a digit value of 10.

When controller output mag_on is 1 the magnetron is on (and so the oven is heating).

The keypad has keys for each digit key_0 - key_9, and keys key_power, key_start, and key_reset. There is no popcorn button. The oven operates as follows: When the oven is plugged in it should be placed in a reset state in which the magnetron is off and the display shows zero minutes and zero seconds. To cook at full power, the user enters 1 to 4 digits and presses start. (The digits indicate the cooking time in minutes and seconds. The number of seconds entered must be in [0, 59], so if the user wants to cook for 90 seconds 130 must be entered, not 90.) To cook at some other power the user presses a digit, power, then 1 to 4 digits for the time, then start. Digit 9 indicates 90% of full power, 8 indicates 80% of full power, etc.

Once commanded to start, the oven turns the magnetron on and off until the set time has elapsed. For full power the magnetron stays on over the entire interval. To cook at partial power the magnetron is turned on for a part of each 2.5-second interval. For example, to cook at 30% power the magnetron would be on for 0.75 seconds, off for 1.75 seconds, on for 0.75 seconds, and so on.

The controller must update the display as the user is entering the power and time and while the oven is heating.

If the user presses reset once while the oven is heating the magnetron is turned off but the display should show the remaining time. If the user presses reset again the oven should reset, if the user presses start cooking should resume.

If reset is pressed when the oven is not heating then it will go to the reset state and so any partially entered time or power will be lost.

When cooking is complete the oven should go into the reset state and sound a 2-second beep.

Whenever an invalid key is pressed, even when heating, the oven should emit a 250 ms beep. A key is invalid if it has no meaning when pressed, for example, pressing a digit while heating or pressing start with more than 59 seconds.

Resist the urge to gold plate your submission, for example, by adding outputs for a power indicator or using the display for a clock when not cooking. This will only confuse the TA-bot. Instead, discuss any such ideas with the instructor.

EE 4702

Homework 4

Due: 20 April 2001.

Solve this problem by modifying a copy of http://www.ee.lsu.edu/v/2001/hw04.html (or .v) which can also be found in /home/classes/ee4702/files/v/hw04.v. See

http://www.ee.lsu.edu/v/proc.html for instructions on running the simulator. Alternate instructions can be found in Lesson 7 of the ModelSim Tutorial, linked to the references web page, http://www.ee.lsu.edu/v/ref.html. This page also has links to manuals for the synthesis program, Leonardo. The links are clickable when this assignment is viewed with Acrobat Reader. The ModelSim tutorial and other documentation can also be accessed from the Help menu on the ModelSim GUI (started by the command vsim -gui).

Problem 1: Write a synthesizable Verilog behavioral description of a microwave oven controller in module microwave_oven_controller that passes the testbench in test_oven. The module is the same as the one assigned in Homework 3 with the following differences. There is a third input, reset. The oven should reset if reset is one at a positive edge of input clk. This is to be used for a power-on reset, it is not the front-panel reset button, and so the oven should reset regardless of what it is doing.

Input key_code should only be examined at positive clk edges. Input key_code will be set to a key's code as long as a key is pressed. Do not expect users to hold down keys for only $\frac{1}{64}$ of a second. As before key_code will be key_none when no key is pressed.

The module must be synthesizable using the provided synthesis script (see below) and the synthesized hardware must pass the testbench.

Follow these steps:

(1) Write an oven module that passes the testbench (without synthesis). This can be based on your submission to Homework 3, a classmate's submission to Homework 3, or the solution to Homework 3 (when that is posted). Note that the testbench tests the module needed for this homework, which is slightly different than the one designed for Homework 3.

(2) Synthesize the module. This can be done in three ways:

• In Emacs: press S-F9 (shift f9) while a buffer with the oven module is active. Lines containing error, warning, and information messages will be highlighted. If mouse-2 (the middle button) is pressed while the pointer is over a highlighted message Emacs will jump to the corresponding line in the Verilog description.

• From a shell: type syn.tcl hw04sol.v.

• Using the GUI: start Leonardo by selecting "Leonardo" from the slide-up menu over the Emacs kitchen-sink icon on the CDE control panel at the bottom of the screen. Select the SCL05u technology target, under ASIC and Sample. Load the homework solution and press Run Flow. Additional steps are needed to generate Verilog output. Use the first two methods when Verilog output is needed. (The GUI can be used, but the scripts are easier.)

Make sure the module synthesizes (look for a "Synthesis Complete" message), correct any problems if it does not.

(3) Run the testbench on the synthesized module. To do this, load or restart the testbench into Modelsim **without** recompiling it. (The synthesis script should have compiled the synthesized module for you.) If this is done correctly Modelsim should print many lines that look like "Loading work.OR4T2," the names of the technology modules. Run the testbench and correct any errors.

EE 4702

Homework 5

Due: 2 May 2001

Solve this problem by modifying a copy of http://www.ee.lsu.edu/v/2001/hw05.html (or .v) which can also be found in /home/classes/ee4702/files/v/hw05.v. See

http://www.ee.lsu.edu/v/proc.html for instructions on running the simulator. Alternate instructions can be found in Lesson 7 of the ModelSim Tutorial, linked to the references web page, http://www.ee.lsu.edu/v/ref.html. This page also has links to manuals for the synthesis program, Leonardo. The links are clickable when this assignment is viewed with Acrobat Reader. The ModelSim tutorial and other documentation can also be accessed from the Help menu on the ModelSim GUI (started by the command vsim -gui).

Module bsearch, in the homework template, stores numbers and can find whether a number had been seen before. The module has four inputs and an output. Input clk is a clock, input reset is a reset signal, op is a command, and din in the number to store or find. The module checks commands on a positive edge of the clock, unlike the calculator a command should be present for just one positive edge. (If it is present for two consecutive positive edges it may be performed twice.) Output result should be set by the negative edge following the command (though it can be set right after the positive edge). If the result is ready then result is set to the appropriate code, explained below, otherwise it is set to re_busy until the result is available. The module recognizes three commands, plus a nop.

When op = op_insert the module will attempt to store the number present at input din, if successful result will be set to re_i_inserted. If the module were full result is set to re_i_full. An inserted number must be strictly greater than the last one inserted, if not result is set to re_i_misordered. When op = op_find the module will set result to re_i_present if the number at din was inserted since the last reset, otherwise it is set to re_i_absent. When op = op_reset the module is emptied.

The homework template contains four copies of a behavioral description of this module, all named **bsearch** and each bracketed by an 'ifdef/'endif pair.

The module just below 'ifdef NOT_SYN is complete and does not have to be modified. (If would have been Problem 1 if there were more time left in the semester. :-)). The other bsearch modules are to be converted into synthesizable form as explained in the problems below.

Problem 1: Convert the module below 'ifdef FORM2 to a synthesizable module in Form 2 that does one iteration of the forever loop per cycle. (The original code does the entire loop in one cycle.) The synthesized module must pass the testbench. In the appropriate place in the comments indicate the clock frequency, area (number of gates), and worst-case time needed to find a number (time from positive edge when op = op_find to when result is set to re_f_present).

Problem 2: Convert the module below 'ifdef FORM3 to a synthesizable module in Form 3 that does no more than one iteration of the forever loop per cycle. The synthesized module must pass the testbench. Show how the critical path (as identified by the synthesis program) can be shortened by adding an event control **@(posedge clk)**. Include the line if that would improve performance, otherwise, include it and comment it out. (Remember that performance is more than just clock frequency.) Next to the line indicate the endpoints of the critical path that is, or would be, shortened.

In the appropriate place in the comments indicate the clock frequency, number of gates, and worst-case time needed to find a number.

Problem 3: Convert the module below 'ifdef FORM3_FAST to a synthesizable module in Form 3. The synthesized module must pass the testbench. Modify the description so that two iterations

of the original code is done by one iteration (and clock cycle) in the modified code. This module should take fewer clock cycles than the one in the previous problem (nearly half when the capacity is large). In the appropriate place in the comments indicate the clock frequency, number of gates, and worst-case time needed to find a number.

The modules must be synthesizable using the provided synthesis script (see below) and the synthesized hardware must pass the testbench.

Follow these steps:

(1) Modify the modules as needed. Be sure to include a 'define FOO when you are working on a module next to 'ifdef FOO.

(2) Synthesize the module. This can be done in two ways:

• In Emacs: press S-F9 (shift f9) while a buffer with the Verilog description is active. Lines containing error, warning, and information messages will be highlighted. If mouse-2 (the middle button) is pressed while the pointer is over a highlighted message Emacs will jump to the corresponding line in the Verilog description.

• From a shell: type syn.pl hw05sol.v.

The clock frequency, number of gates, and critical path information are written by the synthesis program and script.

Make sure the module synthesizes (look for a "Synthesis Complete" message), correct any problems if it does not.

(3) Run the testbench on the synthesized module. To do this, load or restart the testbench into Modelsim **without** recompiling it. (The synthesis script should have compiled the synthesized module for you.) If this is done correctly Modelsim should print many lines that look like "Loading work.OR4T2," the names of the technology modules. Run the testbench and correct any errors.

13 Spring 2000

EE 4702 Homework 1 Due: 14 February 2000

Solve this problem by modifying a copy of http://www.ee.lsu.edu/v/2000/hw01.v. Use Lesson 7 of the ModelSim tutorial for instructions on using the simulator as described in the references web page, http://www.ee.lsu.edu/v/ref.html. Instructions for submitting a solution will be given later.

Problem 1: Write two Verilog descriptions of the following circuit. The circuit has a four-bit input on which integers will appear. If the integer is equal to 2 or 9 the output should be 1, otherwise the output should be zero. One description, in a module named number_detect_es, should be explicit structural, and the other should be implicit structural in a module named number_detect_is.

Problem 2: Write a testbench for the descriptions above. Test all possible inputs. Name the testbench module test_number_detect.

Problem 3: The structural module below, when finished, is to produce a pulse of duration 3 ns on output o starting 4 ns after a positive edge on input i, but only if i is 1 for at least 2 ns. (The finished module will remain structural.) Correct operation is shown in the sample timing below where there are three pulses on input i. No output pulse appears at 14 ns because the input is 1 for only 1 ns. Pulses on o are produced for the next two positive edges on i. The testbench code used to generate the waveforms is in module test_pos_edge, already written.



Entity:test_pos_edge Architecture: Date: Wed Feb 02 17:54:43 CST 2000 Row: 1 Page: 1

```
module pos_edge_trigger(o,i);
input i;
output o;
wire noti;
wire preout;
assign o = preout;
not (noti,i);
and (preout,i,noti);
```

endmodule // pos_edge_trigger

Add delay specifications so that the module works as described. Add **only** delay specifications, nothing else. Don't add gates, don't add modules, and especially don't add behavioral code.

EE 4702

Homework 2

Due: 23 February 2000

Homework 2 and 3 are being assigned simultaneously. Homework 3 is really just homework 2a, but calling it that would ruin the numbering scheme. Solution templates can be found in /home/classes/ee4702/files/v and will be linked to the web page. Instructions for submission will be posted later.

Problem 1: A tachometer measures rotation rate by detecting marks on a disk using photodetectors as illustrated below.

In the illustration there are two rings of marks, in this assignment only the outer ring (the one with lots of marks) will be used.

As the disk spins the number of marks passing under the disk are counted. At fixed intervals a rotation rate is updated.

Write a Verilog behavioral description for hardware that determines the rotation rate using the photodetector output. The module has the following declaration:



```
parameter freq = 500; // Clock frequency.
parameter marks = 4; // Number of marks on ring.
parameter update_interval = 0.5; // Update every update_interval seconds.
parameter perwhat = 60; // Measure in revolutions per 60 seconds.
```

// Solution goes here.

module tach1(rpx,pd,clk); input pd, clk; output rpx;

reg [9:0] rpx;

pd, clk;

endmodule

wire

Input clk is a square wave for use by the module. Input pd is the photodetector output. It is 1 when a mark is under the photodetector. Output rpx is the rotation rate. Parameter freq is the frequency of clk and marks is the number of marks on a disk. Parameter update_interval is the number of seconds between updates of rpx. For example, if update_interval were 3 then rpx would have to be updated every 3 seconds. Parameter perwhat is the time unit for measuring revolutions, in seconds. If it is 60 then rpx should be in revolutions per minute, if it is 1 then rpx should be in revolutions per second, etc.

Consider the instantiation below:

tach1 #(200) s1(rpx,pd,clk);

This instantiates a tachometer which is to use a 200 MHz clock.

Call $\frac{\text{perwhat}}{\text{marks} \times \text{update_interval}}$ the precision, p. Let n_m denote the number of marks that have been counted in a time interval of duration update_interval. Then rpx should be set to $n_m \times p$.

In addition to generating **rpx** the module should also check to make sure its parameters are suitable. The parameters are not suitable if the precision is not an integer or if any registers would overflow in normal operation.

Use the testbenches provided in the solution template to test your circuit. Testbench module test_tach1_fast tests a single instance, while test_tach1_detailed tests several instances (using different parameters).

Follow the following rules when writing the hardware description. (The rules do not apply to testbench code.)

- Do not use multipliers or dividers.
- Do not use delays: #3 i=1;. You can use event controls: @(posedge clk).
- Use the initial block for parameter verification and register initialization only.

To be continued in homework $3 \ldots$
EE 4702Homework 3Due: 3 March 2000

Homework 3 is being split in to homework 3 and 4. Homework 4 is really just homework 2b, but calling it that would ruin the numbering scheme. Solution templates can be found in /home/classes/ee4702/files/v and will be linked to the web page. Instructions for submission can be found in the homework template.

Problem 1: Write an implicit structural description of the module designed in homework 2, either your design or the posted solution. Note: see the template for a workaround to a bug when using parameters.

Problem 2: Design a behavioral description of hardware similar to the one from homework 2, but that measures rotation speed by measuring the time between marks. The inputs and output are the same and the parameters are the same, except that update_interval is missing. In this module the output should be updated for each detected mark. (The update does not have to occur on the positive edge of pd, but it does have to be updated sometime.) The output must correctly indicate zero rotation rate. (You'll see why that needed to be specified.) Though the number of marks is known the width of the marks is not.

```
module tach2(rpx,pd,clk);
input pd, clk;
output rpx;
wire pd, clk;
reg [9:0] rpx;
parameter freq = 500; // Clock frequency.
parameter marks = 4; // Four pulses per revolution.
parameter perwhat = 60; // Measure in revolutions per 60 seconds.
// Code here.
```

endmodule

Follow the following rules when writing the hardware description. (The rules do not apply to testbench code.)

- You can use multipliers or dividers. (Just use the usual operators, no need to instantiate anything.)
- Do not use delays: #3 i=1;. You can use event controls: @(posedge clk).
- Use the initial block for parameter verification and register initialization only.

EE 4702

Homework 4 Due: 17 March 2000

Homework 4 is really just homework 2b, but calling it that would ruin the numbering scheme. Solution templates can be found in /home/classes/ee4702/files/v and will be linked to the web page.

Changes made to this assignment 13 March 2000, 10:02:54 CST. Changes are shown in a slanted (not italic) font.

Problem 1: Suppose the marks are glued on the disks used in the problems above and that sometimes they fall off. (Or maybe they're stolen, or painted over.) Design a behavioral Verilog module that can compute the correct rotation rate when as few as $\lceil \frac{m+1}{2} \rceil$ marks are still present, where *m* is the original number of marks. The angle subtended by the marks (their width, sort of) is not known.

Use the same design rules as for tach2. You may base the solution to this problem on your solution to homework 3 (perhaps corrected) or the posted solution to homework 3.

The module does **not** have to measure zero correctly, when the rotation rate is below the minimum measurable speed any output is acceptable.

```
module tach3(rpx,pd,clk);
input pd, clk;
output rpx;
wire pd, clk;
reg [9:0] rpx;
parameter freq = 500; // Clock frequency.
parameter marks = 12; // Four pulses per revolution, when new.
parameter perwhat = 60; // Measure in revolutions per 60 seconds.
// Code here.
```

endmodule

Problem 2: Design a testbench for the code above. The testbench should test the ability of tach3 to work with missing marks. The testbench can be based on the tach2 testbench provided with homework 3.

The testbench should be able to handle a disk with up to one hundred marks. Test at least these patterns: all marks present, one mark missing, the maximum number of marks missing and spread out as much as possible (so almost every other mark is missing), and the maximum number of marks missing where the missing marks are all adjacent (so there will be a big gap). Also, add a pattern of your own.

See the hint at http://www.ee.lsu.edu/v/2000/hw04hint.html.

EE 4702

Homework 5

Due: 19 April 2000

Solution templates can be found in /home/classes/ee4702/files/v and will be linked to the web page. Put your solution in a file named hw05sol.v. Soon after the time the assignment is due your directory tree will be searched for files named hw05sol.v and the most-recently modified one will be copied. If no such file is found an attempt will be made to copy a file using a guessed name, but this is not something to be relied on. Give the file the correct name.

Solutions to the problems below should be synthesized for the following technology: ASIC (type of target), Sample (manufacturer [usually]), XCL05U (technology family). Do not specify any optimization or other synthesis options. View the RTL schematic to check your solutions. (Under the Tools menu or using the toolbar button.) Leonardo is started by typing leonardo & in a shell. To work around a cosmetic stdout bug start Leonardo by typing leonardo > /dev/null & . Additional instructions on running Leonardo will be posted later.

The assignments will be graded under the assumption that the schematic was viewed; a substantial number of points will be deducted for solutions that do not synthesize correctly.

Problem 1: Complete the Leonardo-synthesizable Verilog description of an ALU module shown below. The module has three inputs, **a**, **b**, and **op**. Inputs **a** and **b** are each 8 bits and hold unsigned integers. Input **op** specifies an operation to perform; the coding is given by the parameters. The module has two outputs, **res** and **err**. Output **res** is 8 bits and is the result of performing the operation; output **err** is one bit and is 1 if **res** cannot hold the result of **op**. That is, **err** is one if the sum is more than eight bits or the difference is negative; it is zero otherwise.

Write the description using behavioral code and synthesize it for the target specified above. The synthesized module should be combinational—no latches allowed. The module should perform only the three operations indicated, **don't** add your own.

endmodule // alu

Problem 2: Complete the design of a Leonardo-synthesizable Verilog module with four 1-bit outputs and six one-bit inputs with the following behavior when synthesized:

- Output w is equal to the value input d had at the last negative edge of clk. (In other words, w is set to d at the negative edge of clk.)
- Output y is equal to the value input a had at the last positive edge of clk.
- Output z is equal to the last value input c had when both clk was high and d = b.
- Output x set to b at positive edge of clk if a=1. Output x is set to 1 if clk=1 and d=a.
- All outputs are set to zero when input r=1 (and will remain zero until set to a new value as described above).

If might be helpful to figure out what kinds of flip-flops are needed for each output and then check if Leonardo chooses the correct one (or something equivalent).

```
module latch_thing(w,x,y,z,a,b,c,d,r,clk);
input a, b, c, d, r, clk;
output w, x, y, z;
```

// Insert solution here. It's okay to delete this comment.

endmodule // latch_thing

EE 4702

Homework 6

Due: 28 April 2000

Solution templates can be found in /home/classes/ee4702/files/v and www.ee.lsu.edu/v/2000/hw06.html Put your solution in a file named hw06sol.v. Soon after the time the assignment is due your directory tree will be searched for files named hw06sol.v and the most-recently modified one will be copied. If no such file is found an attempt will be made to copy a file using a guessed name, but this is not something to be relied on. Give the file the correct name.

Solutions to the problems below should be synthesized for the following technology: ASIC (type of target), Sample (manufacturer [usually]), XCL05U (technology family). Do not specify any optimization or other synthesis options. View the RTL schematic to check your solutions. (Under the Tools menu or using the toolbar button.) Leonardo is started by typing leonardo & in a shell. To work around a cosmetic stdout bug start Leonardo by typing leonardo > /dev/null & . See the procedures and FAQ web pages for additional instructions on running Leonardo.

See the FAQ page for instructions on how to write Verilog code of the synthesized module for simulation using the Leonardo GUI, a TCL script, or Emacs. The process is particularly convenient using Emacs.

The assignments will be graded under the assumption that the synthesized code was simulated using the testbench provided; a substantial number of points will be deducted for solutions that do not pass the testbench correctly.

Problem 1: A Verilog behavioral description of a module similar to the one described in the first midterm problem appears in http://www.ee.lsu.edu/v/2000/hw06.v. The module cannot be synthesized by Leonardo (1999.1f). Modify the module so that it can be synthesized while retaining the benefits of behavioral code. (That is, do not convert it to a structural description.) The synthesized code must pass the testbench provided with the code.

The module, width_change, describes a FIFO in which data is inserted in 4-bit nibbles (the technical term for half a byte, no kidding) and removed in 8-bit bytes. The total storage capacity is 32 bits. In addition to the 4-bit input and 8-bit output there are two 1-bit inputs, inclk and outclk. On a positive edge of inclk data is read; on a positive edge of outclk data is removed in FIFO fashion. The low nibble of the output (bits 0-3) holds data that arrived earlier than the high nibble of the output full is one if the FIFO cannot accept another nibble, output empty is one if the FIFO is empty (in which case the output must be all zeros), and output complete is 1 if the output has eight bits of data. (Output complete is zero if the FIFO is empty or if it contains just 4 bits. If the FIFO contains four bits the high nibble of output should be zeros.)

Note that, unlike the test question, the sizes of the input, output, and storage capacity are digital-logic-friendly powers of two. However like the midterm exam, the input and output each have their own positive edge triggered clock. Getting this into synthesizable form will take some thought.

14 Fall 2024 Solutions

/// SOLUTION

```
11
/// LSU EE 4755 Fall 2024 Homework 1 -- SOLUTION
11
/// Assignment https://www.ece.lsu.edu/koppel/v/2024/hw01.pdf
`default_nettype none
/// Problem 1
11
 /// Complete the dot product modules as described below.
11
11
      [<] Complete dot2.</pre>
11
      [✓] Complete dot3.
      [<] Complete dot4.</pre>
11
      [...] None of your modules can use assign statements or procedural code.
11
11
11
      [~] Make sure that the testbench does not report errors.
      [<] Module must be synthesizable. Use command: genus -files syn.tcl</pre>
11
11
11
      [<] Don't assume any particular parameter values.</pre>
11
11
      [~] Code must be written clearly.
module mult
 #( int w = 5 ) ( output uwire [w-1:0] p, input uwire [w-1:0] a, b );
  // Do not modify this module.
  assign p = a * b;
endmodule
module add
 #( int w = 5 ) ( output uwire [w-1:0] s, input uwire [w-1:0] a, b );
  // Do not modify this module.
  assign s = a + b;
endmodule
module dot2
  #(int w = 5)
  ( output uwire [w-1:0] dp,
    input uwire [w-1:0] a[1:0], b[1:0] );
  // Compute
  11
  11
       dp = a[0] * b[0] + a[1] * b[1];
  11
  // [*] Use as many instantiations of mult and add as are needed, if any.
  // [<] Try to minimize the number of instantiations.</pre>
  // [*] DO NOT use assign, and DO NOT use procedural code (always, etc.).
  11
  // It will also be necessary to declare uwire objects to interconnect
  // the instantiations.
```

uwire [w-1:0] p0, p1;

Homework Sol Code

mult #(w) mO(p0, a[0], b[0]); mult #(w) m1(p1, a[1], b[1]); add #(w) ad(dp, p0, p1);

```
endmodule
```

```
module dot3
  #(int w = 5)
  ( output uwire [w-1:0] dp,
     input uwire [w-1:0] a[2:0], b[2:0] );
   // Compute
   11
   11
       dp = a[0] * b[0] + a[1] * b[1] + a[2] * b[2];
   11
  // [*] Use at least one instantiation of dot2.
   // [*] Use as many instantiations of mult and add as are needed, if any.
   // [*] Try to minimize the number of instantiations.
   // [*] D0 NOT use assign, and D0 NOT use procedural code (always, etc.).
   /// SOLUTION
   uwire [w-1:0] p0, p2;
   dot2 #(w) d0( p0, a[1:0], b[1:0] );
   mult #(w) m2( p2, a[2], b[2] );
   add #(w) a2(dp, p0, p2 );
endmodule
module dot4
 #(int w = 5)
   ( output uwire [w-1:0] dp,
     input uwire [w-1:0] a[3:0], b[3:0] );
  // Compute
   11
   11
       dp = a[0] * b[0] + a[1] * b[1] + a[2] * b[2] + a[3] * b[3];
  11
   // [*] Use as many instantiations of dot2 and dot3 as are needed, if any.
   // [*] Use as many instantiations of mult and add as are needed, if any.
  // [/] Try to minimize the number of instantiations.
   // [*] Try to minimize the time to compute the operation based on the
          longest path from inputs to outputs.
   11
   // [/] DO NOT use assign, and DO NOT use procedural code (always, etc.).
   /// SOLUTION
   uwire [w-1:0] p0, p1;
   dot2 #(w) d0( p0, a[1:0], b[1:0] );
   dot2 #(w) d1( p1, a[3:2], b[3:2] );
   add #(w) ad(dp, p0, p1 );
endmodule
```

```
/// Problem 2
11
 /// Complete the MADD Dot Product Modules
111
11
11
       [✓] Complete dot2m.
11
       [<] Complete dot4m.</pre>
11
       [✓] Complete dot6m.
11
11
       [...] Make sure that the testbench does not report errors.
11
       [ /] Module must be synthesizable. Use command: genus -files syn.tcl
11
11
       [<] Don't assume any particular parameter values.</pre>
11
11
       [ < ] Code must be written clearly.
module madd
 #(int w = 8)
  ( output uwire [w-1:0] s, input uwire [w-1:0] si, a, b );
   // Do not modify this module.
   assign s = si + a * b; // Perform a Multiply Add Operation.
endmodule
module dot2m
  #(int w = 5)
   ( output uwire [w-1:0] dp,
     input uwire [w-1:0] si, a[1:0], b[1:0] );
   // Compute
  11
  // dp = si + a[0] * b[0] + a[1] * b[1];
  11
  // [*] Use as many instantiations of madd as are needed, if any.
   // [*] Try to minimize the number of instantiations.
   // [*] D0 NOT use assign, and D0 NOT use procedural code (always, etc.).
  /// SOLUTION
   uwire [w-1:0] p0;
  madd #(w) mO(p0, si, a[0], b[0] );
   madd #(w) m1(dp, p0, a[1], b[1] );
endmodule
module dot4m
   #(int w = 6)
   ( output uwire [w-1:0] dp,
     input uwire [w-1:0] si, a[3:0], b[3:0] );
  // Compute
  11
   11
       dp = si + a[0] * b[0] + a[1] * b[1] + a[2] * b[2] + a[3] * b[3];
  11
   // [*] Use as many instantiations of dot2m and madd as are needed, if any.
   // [*] Try to minimize the number of instantiations.
   // [/] DO NOT use assign, and DO NOT use procedural code (always, etc.).
```

```
\leftarrow \rightarrow Fall 2024 \leftarrow \rightarrow Homework 1
```

```
/// SOLUTION
   uwire [w-1:0] p0;
   dot2m #(w) d0( p0, si, a[1:0], b[1:0] );
   dot2m #(w) d1( dp, p0, a[3:2], b[3:2] );
endmodule
module dot6m
   #(int w = 7)
   ( output uwire [w-1:0] dp,
    input uwire [w-1:0] si, a[5:0], b[5:0] );
  // Compute
  11
       dp = si+a[0]*b[0]+a[1]*b[1]+a[2]*b[2]+a[3]*b[3]+a[4]*b[4]+a[5]*b[5];
  11
   // Using the minimum number of instantiations of:
  // dot2m, dot4m, madd.
  11
   // [.] Use as many instantiations of dot2m,dot4m, and madd as needed, if any.
   // [~] Try to minimize the number of instantiations.
   // [*] D0 NOT use assign, and D0 NOT use procedural code (always, etc.).
   /// SOLUTION
   uwire [w-1:0] p0;
   dot4m #(w) d0( p0, si, a[3:0], b[3:0] );
   dot2m #(w) d1( dp, p0, a[5:4], b[5:4] );
endmodule
```



module multy

```
#( int wa = 1, wb = 2, wo = wa + wb )
  ( output uwire [wo-1:0] p,
    input uwire [wa-1:0] a,
    input uwire [wb-1:0] b );
```

```
\leftarrow \rightarrow \text{ Fall 2024} \qquad \leftarrow \rightarrow \text{ Homework 1}
```

/// SOLUTION 11 // Each port has its own size! // [r] Modify the connections to this module. (The stuff above this line.) assign p = a * b;endmodule module addy #(int wi = 1, wo = wi + 1) (output uwire [wo-1:0] s, input uwire [wi-1:0] a, b); /// SOLUTION 11 // The output can be a different size, wo, than the input, wi. // [~] Modify the connections to this module. (The stuff above this line.) assign s = a + b; endmodule module dot2y #(int wa = 5, wb = 6, wo = wa + wb + 1) (output uwire [wo-1:0] dp, input uwire [wa-1:0] a[1:0], input uwire [wb-1:0] b[1:0]); // Compute 11 // dp = a[0] * b[0] + a[1] * b[1]; 11 // Note: Product of a wa-bit and wb-bit unsigned integer needs wa+wb bits. 11 Sum of a wa-bit and wb-bit integer needs max(wa,wb)+1 bits. 11 // [~] Modify addy and multy so that in can be instantiated ... // .. with ports set to the needed size. // [*] Do not make the ports larger than are needed. // [*] Use as many instantiations of multy and addy as are needed, if any. // [*] D0 NOT use assign, and D0 NOT use procedural code (always, etc.). /// SOLUTION // Compute the size needed to hold the product a[i] * b[i]. 11 localparam int wr = wa + wb; 11 // Use that size for the dot product terms. 11 uwire [wr-1:0] p0, p1; multy #(wa,wb,wr) mO(p0, a[0], b[0]); multy #(wa,wb,wr) m1(p1, a[1], b[1]); addy #(wr,wr+1) ad(dp, p0, p1);

```
endmodule
```

```
module dot4y
 #( int wa = 5, wb = wa, wo = wa + wb + 2)
   ( output uwire [wo-1:0] dp,
     input uwire [wa-1:0] a[3:0],
     input uwire [wb-1:0] b[3:0] );
  // Compute
   11
  11
        dp = a[0] * b[0] + a[1] * b[1] + a[2] * b[2] + a[3] * b[3];
   11
   11
       addy, multy, dot2y
   // Note: Product of a wa-bit and wb-bit unsigned integer needs wa+wb bits.
   11
            Sum of a wa-bit and wb-bit integer needs max(wa,wb)+1 bits.
  11
  // [*] Use as many instantiations of multy,addy, and dot2y as needed, if any.
   // [*] D0 NOT create a new version of multy or addy just for dot4y.
   // [~] Do not make the ports larger than are needed.
   // [*] D0 NOT use assign, and D0 NOT use procedural code (always, etc.).
  /// SOLUTION
  11
   // Compute the size needed to hold the dot2 results.
   11
   localparam int wr = wa + wb + 1;
   uwire [wr-1:0] p0, p1;
   dot2y #(wa,wb) d0( p0, a[1:0], b[1:0] );
   dot2y #(wa,wb) d1( p1, a[3:2], b[3:2] );
   addy #(wr,wo) ad(dp, p0, p1 );
```

```
endmodule
```


11

// It is okay to modify the testbench code to facilitate the coding // and debugging of your modules. Keep in mind that your submission // will be tested using a different testbench, so on the one hand no // one will be accused of dishonesty for modifying the testbench // below. However be sure to restore any changes to make sure that // your code passes the original testbench.

```
// cadence translate_off
```

module testbench;

```
\leftarrow \rightarrow Fall 2024
                   \leftarrow \rightarrow Homework 1
                                                  Homework Sol Code
                     \{0, 2, 0, 0\},\
                     \{0, 8, 0, 0\},\
                     \{1, 3, 0, 0\},\
                     \{1, 7, 0, 0\},\
                     \{2, 5, 3, 0\},\
                     { 2, 8, 4, 0 }
                     };
       logic d[npsets:-1]; // Start / Done signals.
       int t_errs[npsets];
       int t_errs_mod[string];
       int t_n_tests_mod[string];
       int t_n_tests[npsets];
       string sname[] = { "Prob 1", "Prob 2", "Prob 3" };
       initial begin
          for ( int i=0; i<npsets; i++ ) begin</pre>
             t_{errs}[i] = 0;
             t_n_{tests[i]} = 0;
          end
          d[-1] = 1;
          wait( d[npsets-1] );
          $write("\n");
          for ( int p=0; p<0; p++ ) begin</pre>
             automatic string wline =
                pset[p][0] < 2 ? <u>$sformatf("w=%0d", pset[p][1])</u> :
                  $sformatf("wa=%0d,wb=%0d", pset[p][1],pset[p][2]);
            $write("End of tests %s, %s: %Od errors out of %Od tests.\n",
                    sname[ pset[p][0] ], wline, t_errs[p], t_n_tests[p]);
          end
          foreach ( t_errs_mod[mname] ) begin
             $write("End of tests. For %s: %Od errors out of %Od tests.\n",
                     mname, t_errs_mod[mname], t_n_tests_mod[mname] );
          end
       end
       for ( genvar p=0; p<npsets; p++ ) begin</pre>
          testbench n #( .idx(p), .variation(pset[p][0]), .wap(pset[p][1]), .wbp(pset[p][2]), .wo_delta(p) )
          tb( .done(d[p]), .tstart(d[p-1]) );
       end
    endmodule
    module testbench_n
      \#( int idx, variation = 0, wap = 2, wbp = 3, wo_delta = 1)
       ( output logic done, input uwire tstart );
```

```
localparam bit normal = variation == 0;
localparam bit ripple = variation == 1;
localparam bit hybrid = variation == 2;
localparam int wa = wap;
localparam int wb = hybrid ? wbp : wap;
```

localparam int wo = hybrid ? wa + wb + 2 : wap;

```
\leftarrow \rightarrow \text{ Fall 2024} \qquad \leftarrow \rightarrow \text{ Homework 1} \qquad \qquad \text{Homework Sol Code}
```

```
localparam int n_tests = 1000;
localparam int ms = 7; // Maximum array size
logic [wa-1:0] a[ms-1:0];
logic [wb-1:0] b[ms-1:0];
uwire [wo-1:0] dp[ms];
logic [wo-1:0] z;
int sizes[$];
string npre, npost;
localparam int wo2 = wa + wb + 1;
if (ripple) begin
   dot2m #(wa) d2( dp[2], z, a[1:0], b[1:0] );
   dot4m #(wa) d4( dp[4], z, a[3:0], b[3:0] );
   dot6m #(wa) d6( dp[6], z, a[5:0], b[5:0] );
   initial begin sizes = { 2, 4, 6 }; npre = "dot"; npost = "m"; end
end else if ( normal ) begin
   dot2 #(wa) d2( dp[2], a[1:0], b[1:0] );
   dot3 #(wa) d3( dp[3], a[2:0], b[2:0] );
   dot4 #(wa) d4( dp[4], a[3:0], b[3:0] );
   initial begin sizes = { 2, 3, 4 }; npre = "dot"; npost = ""; end
end else begin
   uwire [wo2-1:0] dp2o;
   dot2y #(wa,wb) d2( dp2o, a[1:0], b[1:0] );
   assign dp[2] = { 1'b0, dp2o };
   dot4y #(wa,wb) d4( dp[4], a[3:0], b[3:0] );
   initial begin sizes = { 2, 4 }; npre = "dot"; npost = "y"; end
end
string names[$];
initial begin
   automatic int n_err_dp[ms] = '{ms{0}};
   automatic string wline = hybrid
     ? <u>$sformatf</u>("wa=%0d,wb=%0d", wa, wb) : <u>$sformatf</u>("w=%0d", wa);
   wait( tstart );
   $write("Starting tests for %s %s.\n", testbench.sname[variation], wline);
   foreach ( sizes[sidx] )
     names.push_back( <u>$sformatf</u>("%s%0d%s",npre,sizes[sidx],npost) );
   foreach ( sizes[sidx] ) begin
      automatic int sz = sizes[sidx];
      for ( int t=0; t<n_tests; t++ ) begin</pre>
         automatic logic [wo-1:0] shadow_dp[ms-1:-1];
         z = \{\frac{\text{sndom}}{\text{sndom}}\};
         shadow_dp[0] = ripple ? z : 0;
         for ( int i=0; i<=sz; i++ ) begin</pre>
            automatic int bits = wa + wb + $clog2(i+1);
            // Test Patterns. Okay to Modify.
```

```
\leftarrow \rightarrow Fall 2024
                   \leftarrow \rightarrow Homework 1
                                                 Homework Sol Code
                   case (t)
                      0: begin a[i]=0; b[i]=0; end
                      1: begin a[i]=0; b[i]=1; end
                      2: begin a[i]=1; b[i]=0; end
                      3: begin a[i]=1; b[i]=1; end
                      4: begin a[i]=1; b[i]=i; end
                      5: begin a[i]=1; b[i]=(1<<wb)-1; end
                      6: begin a[i]=(1<<wa)-1; b[i]=1; end
                      default: begin a[i] = {$random}; b[i] = {$random}; end
                   endcase
                   shadow_dp[i+1] = ( shadow_dp[i] + a[i] * b[i] ) % 2**bits;
                end
                #1;
                if ( shadow_dp[sz] !== dp[sz] ) begin
                   n_err_dp[sz]++;
                   if ( n_err_dp[sz] < 6 ) begin</pre>
                       $write( "Error, %s, %s, %0d != %0d (correct)\n",
                               names[sidx], wline, dp[sz], shadow_dp[sz] );
                       for ( int j=0; j<sz; j++ )</pre>
                         $write(" %0d * %0d%s",
                                a[j], b[j], j == sz-1 ? "\n" : " +");
                       for ( int j=0; j<sz; j++ )</pre>
                         $write(" 0x%0x * 0x%0x%s",
                                a[j], b[j], j == sz-1 ? "\n" : " +");
                   end
                end
             end
          end
          testbench.t_errs[idx] = 0;
          $write("Tests complete %s %s: ",
                 testbench.sname[variation], wline);
          foreach ( sizes[sidx] ) begin
             automatic int sz = sizes[sidx];
             testbench.t_errs_mod[names[sidx]] += n_err_dp[sz];
             testbench.t_n_tests_mod[names[sidx]] += n_tests;
             testbench.t_errs[idx] += n_err_dp[sz];
             testbench.t_n_tests[idx] += n_tests;
             $write("%s %0d errors, ", names[sidx],n_err_dp[sidx]);
          end
          $write("\n");
          done = 1;
       end
```

endmodule

// cadence translate_on

LSU EE 4755

Homework 2 Solution Due: 4 October 2024

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow

https://www.ece.lsu.edu/koppel/v/2024/hw02.v.html. The solution Verilog is in the assignment directory.

For an htmlized version visit https://www.ece.lsu.edu/koppel/v/2024/hw02-sol.v.html.

Collaboration Rules

Each student is expected to complete his or her own assignment. It is okay to work with other students and to ask questions in order to get ideas on how to solve the problems or how to overcome some obstacle (be it a question of Verilog syntax, interpreting error messages, how a part of the problem might be solved, etc.) It is also acceptable to seek out digital design resources for help on Verilog, digital design, etc. It is okay to make use of AI LLM tools such as ChatGPT and Copilot to generate sample Verilog code. (Do not assume LLM output is correct. Treat LLM output the same way one might treat legal advice given by a lawyer character in a movie: it may sound impressive, but it can range from sage advice to utter nonsense.)

After availing oneself to these resources each student is expected to be able to complete the assignment alone. Test questions will be based on homework questions and the assumed time needed to complete the question will be for a student who had solved the homework assignment on which it was based.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account (if necessary), copy the assignment, and run the Verilog simulator on the unmodified homework file, hw02.v. Do this early enough so that minor problems (*e.g.*, password doesn't work) are minor problems.

Homework Overview

In this assignment modules will be completed that compute $a2^s + b > c$ where inputs a and b are real and inputs s and c are non-negative integers. Each module has an output gt, which should be set to 1 if the comparison is true and 0 otherwise. There is also an output ssum which should be set to $a2^s + b$. What makes this interesting is that the sizes of all inputs are parameters, and that in the instantiations tested the number of bits in the significands of a and b can be less than the number of bits in c.

The floating point calculations and conversion(s) are to be done using Chipware modules. Solving this assignment requires a straightforward application of Verilog techniques for instantiating modules and wiring them together. It also requires an understanding of when and how to convert numbers from floating-point to integer representations.

As of this writing two modules are to be completed, comp_fp and comp_int. In comp_fp the greater-than comparison is to be done in floating point (using a Chipware module) and in comp_int it is to be done using an integer comparison (using the > operator).

Testbench

To compile your code and run the testbench press [F9] in an Emacs buffer in a properly set up account. The testbench will apply inputs to several instantiation of modules comp_fp and comp_int. The instantiations differ on the number of bits used for the integer inputs and the format of the floating-point output. The instantiation parameters are shown at the end of the testbench along with a summary of the errors for that module. The end of the testbench output for an unmodified assignment appears below:

Total comp_int exp=7, sig=6, wc= 6, s=0: Errors: 50000 ss, 31394 gt.

```
Total comp_int exp=7, sig=6, wc= 6, s>0: Errors: 50000 ss, 28962 gt.

Total comp_int exp=7, sig=7, wc=10, s=0: Errors: 50000 ss, 33366 gt.

Total comp_int exp=7, sig=7, wc=10, s>0: Errors: 50000 ss, 31052 gt.

Total comp_int exp=8, sig=5, wc=12, s=0: Errors: 50000 ss, 35958 gt.

Total comp_int exp=8, sig=5, wc=12, s>0: Errors: 50000 ss, 33117 gt.

Total comp_fp exp=7, sig=6, wc= 6, s=0: Errors: 50000 ss, 31310 gt.

Total comp_fp exp=7, sig=6, wc= 6, s>0: Errors: 50000 ss, 29113 gt.

Total comp_fp exp=7, sig=7, wc=10, s=0: Errors: 50000 ss, 33478 gt.

Total comp_fp exp=7, sig=7, wc=10, s>0: Errors: 50000 ss, 30957 gt.

Total comp_fp exp=8, sig=5, wc=12, s=0: Errors: 50000 ss, 33073 gt.

Total comp_fp exp=8, sig=5, wc=12, s>0: Errors: 50000 ss, 33073 gt.

Total comp_fp exp=8, sig=5, wc=12, s>0: Errors: 50000 ss, 33073 gt.

TODL: xrun(64) 24.03-s005: Exiting on Sep 29, 2024 at 14:00:48 CDT (total: 00:00:02)
```

Compilation finished at Sun Sep 29 14:00:48, duration 2.14 s

Each line starting with Total shows a tally of results. After Total the line shows the module name, either comp_int or comp_fp, and three parameter values. The label exp shows the value of parameter w_exp, which is the size of the exponent of the FP numbers; label sig shows the value of parameter w_sig, which the size of the significand of inputs a and b, and wc shows the value of parameter w_c, the number of bits in input c. The lines with label s=0 show the results of tests in which module input s is set to zero, the lines with label s>0 show the results of tests in which module input s can be non-zero. Tallies of errors are shown after Errors:, first of the ssum output (scaled sum), and then for the gt output. In the unmodified assignment the ssum is unconnected, and so its output is always wrong. Output gt is set to 1, which is mostly but not always wrong.

Further up, the testbench shows some examples of incorrect output:

```
Starting comp_int tests iwth exp=7, sig=6, wc=6
Error in #(7,6,6) a=-17.50, s=0, b=0.04, c=3. ss 0.0000e+00 != -1.7464e+01 (correct)
Error in #(7,6,6) a=-17.50, s=0, b=0.04, c=3. gt 1 != 0 (correct) -20.4644
Error in #(7,6,6) a=-0.80, s=0, b=18.25, c=12. ss 0.0000e+00 != 1.7445e+01 (correct)
Error in #(7,6,6) a=12.62, s=0, b=13.62, c=0. ss 0.0000e+00 != 2.6250e+01 (correct)
Error in #(7,6,6) a=-3.62, s=0, b=3.72, c=0. ss 0.0000e+00 != 9.3750e-02 (correct)
```

In the sample above the first Error line indicates that the module output was 0.0000e+00 (that's what a z would look like) but $-1.7464 \times 10^1 = -17.464 = -1.7454e+01$ was expected. The second Error line indicates that the gt output was 1 but should have been 0. The -20.4544 is the correct difference between c = 3 and -17.5 + 0.04 = -17.46, indicating that it was not even close. Note that the number of digits past the decimal point is limited and so the full number is not shown. About the first five errors of each type will be shown.

Whether or not there are errors, at least one pair of lines is printed for each test. That output is preceded by the word **Sample** if the output is correct. Appearing below is the beginning and end of the output for correct modules:

Starting comp_int tests iwth exp=7, sig=6, wc=6 Sample in #(7,6,6) a=-17.50, s=0, b=0.04, c=3. ss -1.7500e+01 == -1.7464e+01 (correct) Sample in #(7,6,6) a=-17.50, s=0, b=0.04, c=3. gt 0 == 0 (correct) -20.4644 Finished comp_int tests exp=7, sig=6, wc=6, s=0. Errors: 0 ss, 0 gt Finished comp_int tests exp=7, sig=6, wc=6, s>0. Errors: 0 ss, 0 gt

[snip]

```
Total comp_int exp=7, sig=6, wc= 6, s=0: Errors: 0 ss, 0 gt.
Total comp_int exp=7, sig=6, wc= 6, s>0: Errors: 0 ss, 0 gt.
Total comp_int exp=7, sig=7, wc=10, s=0: Errors: 0 ss, 0 gt.
Total comp_int exp=7, sig=7, wc=10, s>0: Errors: 0 ss, 0 gt.
Total comp_int exp=8, sig=5, wc=12, s=0: Errors: 0 ss, 0 gt.
Total comp_int exp=8, sig=5, wc=12, s>0: Errors: 0 ss, 0 gt.
Total comp_fp exp=7, sig=6, wc= 6, s=0: Errors: 0 ss, 0 gt.
Total comp_fp exp=7, sig=6, wc= 6, s>0: Errors: 0 ss, 0 gt.
Total comp_fp exp=7, sig=7, wc=10, s=0: Errors: 0 ss, 0 gt.
Total comp_fp exp=7, sig=7, wc=10, s=0: Errors: 0 ss, 0 gt.
Total comp_fp exp=7, sig=7, wc=10, s>0: Errors: 0 ss, 0 gt.
Total comp_fp exp=8, sig=5, wc=12, s=0: Errors: 0 ss, 0 gt.
```

To add or change instantiation parameters search for the place where variable **pset** is assigned and edit the initialization of **pset** (and change **npsets** if needed):

The testbench will report on the correctness and accuracy of the output.

References and Helpful Examples

For this assignment Chipware modules are to be instantiated to perform floating-point computation and floating-point/integer conversion. A link to the Genus ChipWare IP Components Guide can be found on the course references page. The IEEE 754 floating point standard is described in the types lecture code, be sure to scroll down to reach it.

See 2023 Homework 2 for examples of how to instantiate these modules to perform a computation and for integer/floating-point conversion. A copy of the solution to the 2023 assignment is included in the 2024 assignment directory. As in this (2024) assignment the floating-point formats in the 2023 assignment vary and so parameters must be used when instantiating the Chipware modules to specify the exponent and significand length. In 2021 Homework 2 Chipware modules were instantiated with non-default exponent and significand lengths. Also see 2022 Homework 5. That assignment uses both combinational and sequential modules. (Sequential material has not yet been covered.) See ms_comb in 2022 Homework 5 for a straightforward connection of FP modules (but without format conversion). **Problem 1:** Module comp_fp has two floating-point (FP) inputs, a and b, two integer inputs s and c, one-bit output gt, and a FP output ssum; it also has integer parameters w_c, w_s, w_exp, w_sig and w_sig2. (The remaining parameters, w_fp and w_fp2, are set to the full size of the two FP formats used, don't change them.) Inputs a and b carry values in a custom IEEE 754 FP format with a w_exp-bit exponent and a w_sig-bit significand. The total size of each of these inputs is 1+w_exp+w_sig bits. (The custom format is recognized by the Chipware modules.) The value on input c is a w_c-bit unsigned integer. The value on output ssum is expected to be a IEEE-format FP number with a w_exp-bit exponent and w_sig2-bit significand.

The output ssum (scaled sum) is to be set to $a2^s + b$ and output gt is to be set to 1 if $a2^s + b > c$ and 0 otherwise.

For this problem one should review the IEEE 754 notes, plus the use of the Verilog concatenation (like {2'b11,a,4'd0}), shift (a<<2), and bit slice (a[6:1]) operators.

After each subproblem there is a description of how the part was solved. Then the complete solved module is shown.

(a) Modify comp_fp so that it computes $a2^s$ without using Chipware modules. The value does not have to be assigned to any particular object, but it should be used to compute $a2^s + b$. To solve this subproblem one must understand the IEEE 754 format. A correct solution requires just a line or two of Verilog code. (Just one line if overflow is ignored, which is okay.)

 \checkmark Compute $a2^s$ without Chipware modules.

To compute $a2^s$ for $a \neq 0$ all we need to do is add s to the exponent. For a = 0 we would leave the value unchanged. The significand is w_sig bits, so to add s to the exponent use expression: $a + (s << w_sig)$ if $a \neq 0$ and 0 otherwise.

Note that for the value $v = f \times 2^e$ with $1 \le f < 2$ in a representation with a w_e -bit exponent (w_exp using the module parameter names) the quantity in the exponent field is $e + e_{\text{bias}}$, where $e_{\text{bias}} = 2^{w_e - 1} - 1$. When s is added to the exponent field there is no need to subtract the bias first and then add it again. It is sufficient to just add s. The problem stated that overflow could be ignored.

The line performing the multiplication $a2^s$ appears below:

uwire [w_fp-1:0] a_sc = a ? a + (s << w_sig) : a;</pre>

(b) Modify comp_fp so that ssum is set to $a2^s + b$. (For partial credit, or to get started quickly set ssum to a + b. If this is done correctly the testbench s=0 tests should show zero ss errors.) Compute the sum using Chipware modules and the value of $a2^s$ from the previous part.

Note that a and b have a w_sig -bit significand, but the sum should have a w_sig2 -bit significand. So, the significands of $a2^s$ and b must be lengthened (assume that $w_sig2 > w_sig$). See the description of the IEEE 754 format. Please don't look for a module to do this for you.

 \checkmark Convert $a2^s$ and b into FP types with a w_sig2-bit significand.

Note that **a** and **b** carry values in a FP representation. All we need to do is widen the significand from w_sig bits to w_sig2 bits. These new bits will be in the least-significant position. The problem did not state what they should be, but a good bet is zero so that the representations of 1.5 and 1.25 don't change. A quick way to do the conversion is to just shift the quantities w_sig2-w_sig bits to the left.

uwire [w_fp2-1:0] a_cw = a_sc << w_sig2 - w_sig; uwire [w_fp2-1:0] b_cw = b << w_sig2 - w_sig;</pre>

 \bigvee Using the value from the previous part, set ssum to $a2^s + b$.

 $\leftarrow \rightarrow$ Homework 2

All one has to do is instantiate a ChipWare adder. Examples were shown in the reference assignment 2023 Homework 2. See the code following the parts below.

(c) Modify comp_fp so that gt is correctly set using a floating-point comparison. Don't forget that input c carries an unsigned integer so that to do a FP comparison c will need to be converted.

🗹 Set gt.

 \checkmark Use Chipware modules for floating-point computation and floating-point/integer conversion.

 \checkmark Use procedural or implicit structural (assign) code for any integer computation.

Pay attention to cost: don't use more bits than are needed.

The modules must be synthesizable.

One needs to first convert c to a floating point value, and then use a comparison unit to compare it to ssum. The comparison unit has many output ports, the only one we need is agtb, the others are left unconnected.

```
module comp fp
  #( int w_c = 5, w_s = 2, w_exp = 5, w_sig = 5, w_sig2 = 6,
     int w_fp = 1 + w_exp + w_sig, w_fp2 = 1 + w_exp + w_sig2 )
                                    output uwire [w_fp2-1:0] ssum,
   ( output uwire gt,
     input uwire [w_fp-1:0] a, b,
     input uwire [w_s-1:0] s,
                                  input uwire [w_c-1:0] c );
  // First, compute a2^s by just adding s to the exponent.
  uwire [w_fp-1:0] a_sc = a ? a + ( s << w_sig ) : a;</pre>
  // Convert a_sc and b from FP numbers with w_sig-bit significands to
  // FP numbers with w_sig2-bit significands by just shifting them over.
  uwire [w_fp2-1:0] a_cw = a_sc \ll w_sig2 - w_sig;
  uwire [w_fp2-1:0] b_cw = b << w_sig2 - w_sig;</pre>
   // Add the now-widened a2<sup>s</sup> to b.
  CW_fp_add #( .sig_width(w_sig2), .exp_width(w_exp) )
  d2(.z(ssum), .a(a_cw), .b(b_cw), .status(), .rnd(Rnd_to_near_up));
  // Convert c to FP
  uwire [w_fp2:1] cf;
  CW_fp_i2flt #( .sig_width(w_sig2), .exp_width(w_exp), .isize(w_c), .isign(0) )
  coa( .z(cf), .a(c), .status(), .rnd(Rnd_to_even) );
   // Compare ssum to c
  CW_fp_cmp #( .sig_width(w_sig2), .exp_width(w_exp) )
  cmp( .agtb(gt), .a(ssum), .b(cf),
        .zctr(1'b0), .altb(), .aeqb(), .unordered(),
        .z0(), .z1(), .status0(), .status1() );
  // Note that most of the outputs are unconnected. Hardware
   // for the unconnected outputs will be eliminated.
endmodule
```

Problem 2: Module comp_int has the same connections as comp_fp and its outputs should be set to the same values.

(a) Modify comp_int so that it computes ssum using an instantiation of comp_fp. The ssum output of the comp_fp instance should connect to the ssum output of comp_int. Don't use the gt output of comp_fp so that the synthesis program doesn't synthesize comp_fp hardware for gt.

 \checkmark Compute ssum using an instance of comp_fp $\boxed{}$ with the gt output unconnected.

That's just a straightforward instantiation. See the solution code further below.

(b) Modify comp_int so that gt is correctly set using an integer comparison. That is, instead of converting c, convert ssum. For maximum credit convert ssum into an integer of as few bits as possible. Don't forget that c is unsigned but ssum is signed.

Compute gt using an integer comparison.

Try to use as few bits as possible.

The value in c is w_c bits, so to do the comparison as integers one only really needs to convert ssum to a w_c -bit unsigned integer. The ChipWare CW_fp_flt2i however always converts to a signed integer, so we need to perform a w_c +1-bit conversion. The maximum representable value is then $2^{w_c} - 1$. What if ssum is larger than that, which is easily possible? No problem, just use the status output of CW_fp_flt2i to check for an overflow. If there's an overflow then $a2^s + b > c$. As can be determined by reading the ChipWare documentation, there is a overflow when status [6]=1. Another special case that needs to be checked is when ssum is negative. If it's negative then $a2^s + b > c$ is definitely false. The complete module is shown below.

```
module comp int
  #( int w_c = 5, w_s = 2, w_exp = 5, w_sig = 5, w_sig2 = 6,
     int w_{fp} = 1 + w_{exp} + w_{sig}, w_{fp2} = 1 + w_{exp} + w_{sig2})
                                   output uwire [w_fp2-1:0] ssum,
   ( output uwire gt,
     input uwire [w_fp-1:0] a, b,
     input uwire [w_s-1:0] s,
                                input uwire [w_c-1:0] c );
  // Instantiate comp_fp, but leave the gt output unconnected to anything.
  uwire gtx; // Don't connect this to anything!
  comp_fp #(.w_c(w_c),.w_s(w_s),.w_exp(w_exp),.w_sig(w_sig),.w_sig2(w_sig2))
   fp(gtx,ssum,a,b,s,c);
  // Since gtx is not used the hardware that would connect to gtx isn't synthesized.
  // Convert ssum to a (w_c+1)-bit number.
  uwire [w_c:0] sumi;
  uwire [7:0] sumi_status;
  CW_fp_flt2i #( .isize(w_c+1), .sig_width(w_sig2), .exp_width(w_exp) ) ftoi
     ( .status(sumi_status), .z(sumi), .a(ssum), .rnd(Rnd_to_plus_inf) );
  // Since c is w_c bits it is wasteful to use more than w_c bits for
  // ssumi, except for the one extra bit used for the sign.
  uwire ssum_positive = !ssum[w_fp2-1],
                                           ssum_overflow = sumi_status[6];
  assign gt = ssum_positive && ( ssum_overflow || sumi > c );
  // Note: If ssum_overflow is true then ssum can't fit in w_c bits and so ssum > c.
```

endmodule

 $| \mathbf{V} |$

Problem 3: Predict which version will be less expensive, comp_fp or comp_int. Then run the synthesis program to see which cost less.

Use the command genus -files syn.tcl to run synthesis. Be sure to correct any errors that prevent synthesis.

Predict which will be less costly.

Both modules have identical hardware for computing ssum, the only difference is in computing gt. Remember that in comp_int the gt output of the comp_fp instantiation is left unconnected. That means whatever hardware comp_fp would have used to compute gt is not synthesized when instantiated in comp_int.

So, in comp_fp the comparison hardware consists of: conversion of a w_c -bit integer to a float, and a floating-point comparison of two numbers with w_sig2 -bit significands.

In comp_int a FP value with a w_{sig2} -bit significand is converted into a w_{c} -bit value. The problem says nothing about the relative size of w_{c} and w_{sig2} (and nobody asked), but a look at the testbench reveals they are the same and so one might as well assume that. In comp_int the comparison is done as an integer.

The FP comparison in $comp_fp$ has to compare both the exponents and significands. That requires examining a total of $w_sig2 + w_exp$ bits. The corresponding comparison in $comp_int$ need only look at w_c bits, plus a sign bit and overflow bit. That favors $comp_int$.

What about the relative costs of conversion? Converting in either direction requires a shifter, which would be $3w \lceil \lg w \rceil u_c$. Here w is the significand or integer size, which is about the same in both cases. Converting to FP requires a count-leadingzeros operation to determine the exponent.

Based on this I'd call it a coin toss. It would be reasonable for a student to assume that it was not necessary to work out a tight estimate of the conversion units' cost in advance. And since it's a pre-synthesis guess there was no expectation of running experiments to see just how much those conversion units cost. So, based on all of this, I would say that comp_int should be less costly.

Run synthesis to find out which really is.

Appearing below are the synthesis results:

Module Name	Area	Delay	Delay	Synth
		Actual	Target	Time
comp_int_w_c6_w_s6_w_exp7_w_sig6_w_sig27				
	148989	23.33	900.0 ns	17 s
comp_fp_w_c6_w_s6_w_exp7_w_sig6_w_sig27				
	140689	20.42	900.0 ns	13 s
comp_int_w_c12_w_s6_w_exp7_w_sig6_w_sig213				
	244127	30.05	900.0 ns	19 s
comp_fp_w_c12_w_s6_w_exp7_w_sig6_w_sig213				
	210213	26.19	900.0 ns	17 s

Remember that the cost is shown under Area and the critical path length is under Delay Actual. The Synth Time column shows the amount of time it took to run synthesis for that module, which has no bearing on the synthesized hardware itself.

Looking at the data above I see that ooops, I was wrong. At both sizes the integer units were less costly. This is also true with the synthesis effort levels set to high. (They were medium in the synthesis script.)

The FP delay is also lower. I'm tempted to run further experiments to determine why. But perhaps I'll leave that for a future assignment.

```
//
/// LSU EE 4755 Fall 2024 Homework 2 -- SOLUTION
//
```

- /// Assignment https://www.ece.lsu.edu/koppel/v/2024/hw02.pdf
- /// Solution writeup https://www.ece.lsu.edu/koppel/v/2024/hw02_sol.pdf

```
`default_nettype none
```

```
/// Problem 1
11
 /// Complete scaled_comp_fp so the comparison is done in FP.
11
11
       [/] Use Chipware modules for floating-point operations and conversions.
//
//
       [...] Make sure that the testbench does not report errors.
       [/] Module must be synthesizable. Use command: genus -files syn.tcl
//
11
11
       [<] Don't assume any particular parameter values.</pre>
11
11
      [.] Code must be written clearly.
typedef enum logic [2:0]
  { Rnd to even = 0, Rnd to 0 = 1, Rnd to plus inf = 2,
    Rnd to minus inf = 3, Rnd to near up = 4, Rnd from 0 = 5 }
    Rnd:
module comp fp
  #( int w_c = 5, w_s = 2, w_exp = 5, w_sig = 5, w_sig2 = 6,
     int w_fp = 1 + w_exp + w_sig, w_fp2 = 1 + w_exp + w_sig2 )
   ( output uwire gt,
    output uwire [w_fp2-1:0] ssum,
     input uwire [w_fp-1:0] a, b,
     input uwire [w_s-1:0] s,
     input uwire [w_c-1:0] c );
  /// SOLUTION -- Problem 1
  // First, compute a2^s by just adding s to the exponent.
   //
  uwire [w_fp-1:0] \alpha_{sc} = a ? a + (s << w_{sig}) : a;
  11
  // Note that ( s << w_sig ) shifts s into the correct position.
  // Convert a_sc and b from FP numbers with w_sig-bit significands to
  // FP numbers with w_sig2-bit significands by just shifting them over.
  11
  uwire [w_fp2-1:0] α_cw = a_sc << w_sig2 - w_sig;</pre>
  uwire [w fp2-1:0] b cw = b << w sig2 - w sig;</pre>
  11
   // This just appends w_sig2-w_sig zeros to the LSB part.
  // Add the now-widened a2^s to b.
  11
  <u>CW_fp_add</u> #( .sig_width(w_sig2), .exp_width(w_exp) )
  d2(.z(ssum), .α(a_cw), .b(b_cw), .status(), .rnd(Rnd_to_near_up));
   // Convert c to FP
   11
```

```
Homework Solution Sol Code
```

 $\leftarrow \rightarrow$ Homework 2

```
/// Problem 2
11
 /// Complete scaled_comp_int so the comparison is done as an int.
11
11
       [v] Use Chipware modules for floating-point operations and conversions.
11
11
       [~] Make sure that the testbench does not report errors.
       [<] Module must be synthesizable. Use command: genus -files syn.tcl</pre>
11
11
//
       [<] Don't assume any particular parameter values.</pre>
11
11
       [.] Code must be written clearly.
```

module comp_int

 $\leftarrow \rightarrow$ Fall 2024

```
#( int w_c = 5, w_s = 2, w_exp = 5, w_sig = 5, w_sig = 6,
    int w_fp = 1 + w_exp + w_sig, w_fp2 = 1 + w_exp + w_sig2 )
    ( output uwire gt,
    output uwire [w_fp2-1:0] ssum,
    input uwire [w_fp-1:0] a, b,
    input uwire [w_s-1:0] s,
    input uwire [w_c-1:0] c );
```

/// SOLUTION -- Problem 2

```
// Instantiate comp_fp, but leave the gt output unconnected to anything.
11
uwire gtx; // Don't connect this to anything!
<u>comp fp</u> #(.w_c(w_c),.w_s(w_s),.w_exp(w_exp),.w_sig(w_sig),.w_sig2(w_sig2))
fp(gtx,ssum,a,b,s,c);
11
// Since gtx is not used the hardware that would connect to gtx
// will not be synthesized.
// Convert ssum to a (w_c+1)-bit number.
//
uwire [w_c:0] sumi;
uwire [7:0] sumi status;
<u>CW fp flt2i</u> #( .isize(w_c+1), .sig_width(w_sig2), .exp_width(w_exp) ) ftoi
  ( .status(sumi_status), .z(sumi), .a(ssum), .rnd(Rnd_to_plus_inf) );
11
// Since c is w_c bits it is wasteful to use more than w_c bits for
// ssumi, except for the one extra bit used for the sign.
uwire ssum_positive = !ssum[w_fp2-1];
uwire ssum_overflow = sumi_status[6];
```

```
\leftarrow \rightarrow Fall 2024 \leftarrow \rightarrow Homework 2
```

```
//
assign gt = ssum_positive && ( ssum_overflow || sumi > c );
//
// Note: If ssum_overflow is true then ssum can't fit in w_c
// bits and so ssum > c.
```

endmodule


```
// cadence translate off
virtual class CONV #(int wexp=6, wsig=10);
   // Convert between real and fp types using parameter-provided
   // exponent and significand sizes.
   localparam int w = 1 + wexp + wsig;
   localparam int bias_r = ( 1 << 11 - 1 ) - 1;</pre>
   localparam int w_sig_r = 52;
   localparam int w_exp_r = 11;
   localparam int bias_h = ( 1 << wexp - 1 ) - 1;</pre>
   static function logic [w-1:0] rtof( real r );
      logic [wsig-1:0] sig_f;
      logic [w_sig_r-wsig-2:0] sig_x;
      logic sig_x_msb;
      logic [w_exp_r-1:0] exp_r;
      logic sign_r;
      { sign_r, exp_r, sig_f, sig_x_msb, sig_x } = <u>$realtobits(r);</u>
      // So, what about a rounding mode? Not now!
      rtof = !r ? 0 : { sign_r, wexp'( exp_r + bias_h - bias_r ), sig_f };
   endfunction
   static function real ftor( logic [w-1:0] f );
      ftor = !f ? 0.0
        : <u>$bitstoreal</u>
          ( { f[w-1],
              w exp r' ( bias r + f[w-2:wsig] - bias h ),
              f[wsig-1:0], (w_sig_r-wsig)'(0) } );
   endfunction
   static function int err_bits( logic [w-1:0] a, b );
      logic [wsig-1:0] sig_a, sig_b;
      logic [wsig+2:0] frac_a, frac_b, frac_diff;
      logic [wexp-1:0] exp_a, exp_b;
      logic s_a, s_b;
      int delta_e;
      if ( <u>$isunknown(a) || $isunknown(b)</u> ) return 1 << wexp;</pre>
      if ( a == b ) return 0;
      { s_a, exp_a, sig_a } = a;
      { s_b, exp_b, sig_b } = b;
      if ( exp_a == 0 || exp_b == 0 ) begin
         logic [wsig-1:0] sig = ~ ( sig_a | sig_b );
         return 1 + wsig - \frac{\text{sclog2}}{\text{sig}} + 1 );
      end
```

```
\leftarrow \rightarrow Fall 2024 \leftarrow \rightarrow Homework 2 Homework Solution Sol Code
```

```
delta_e = $abs( 0 + exp_a - exp_b );
if ( delta_e > 1 ) return delta_e + wsig;
frac_a = exp_a > exp_b ? { 2'b1, sig_a, 1'b0 } : { 3'b1, sig_a };
frac_b = exp_b > exp_a ? { 2'b1, sig_b, 1'b0 } : { 3'b1, sig_b };
frac_diff =
    s_a != s_b ? frac_a + frac_b :
    frac_a > frac_b ? frac_a - frac_b : frac_b - frac_a;
return $clog2( frac_diff + 1 );
```

endfunction

endclass

```
module scaled_comp_1_behav
#( int w_c = 5, w_s = 2, w_exp = 5, w_sig = 5, wfp = 1 + w_exp + w_sig )
  ( output logic gt,
    input uwire [wfp-1:0] a, b,
    input uwire [w_s-1:0] s,
    input uwire [w_c-1:0] c );

logic [wfp-1:0] ssum;

always_comb begin
    real ra, rb, ssumr;
    ra = conv#(w_exp,w_sig)::ftor( a );
    rb = conv#(w_exp,w_sig)::ftor( b );
    ssumr = ra * 2.0 ** s + rb;
    ssum = conv#(w_exp,w_sig)::rtof( ssumr );
```

```
gt = ssumr > c;
end
```

```
endmodule
```

```
// cadence translate_on
```



```
// cadence translate_off
function automatic int unsigned rand_wid(int max_wid);
      automatic int wid = 1 + {<u>$random()</u>} % max_wid;
      return {<u>$random()</u>} & ( ( 1 << wid ) - 1 );</pre>
endfunction
function automatic real rand_fp(real min, real max);
      automatic real range = max - min;
      localparam real rmax_inv = real'(1) / ( ( longint'(1) << 32 ) - 1 );</pre>
      automatic real runit = {<u>$random()</u>} * rmax_inv;
      return runit * range + min;
endfunction
function automatic real fabs(real val);
      fabs = val < 0 ? -val : val;</pre>
endfunction
function int min( int a, b );
      min = a <= b ? a : b;</pre>
endfunction
function int max( int a, b );
      max = a >= b ? a : b;
endfunction
```

```
virtual class CONv2 #(int wexp=6, wsig=10);
   // Convert between real and fp types using parameter-provided
  // exponent and significand sizes.
  localparam int w = 1 + wexp + wsig;
  localparam int bias_r = (1 << 11 - 1) - 1;
  localparam int w_sig_r = 52;
  localparam int w_exp_r = 11;
  localparam int bias_h = ( 1 << wexp - 1 ) - 1;</pre>
  static function logic [w-1:0] rtof( real r );
     logic [wsig-1:0] sig_f;
      logic [w_sig_r-wsig-2:0] sig_x;
     logic sig_x_msb;
     logic [w_exp_r-1:0] exp_r;
     logic sign r;
      { sign_r, exp_r, sig_f, sig_x_msb, sig_x } = <u>$realtobits(r);</u>
      // So, what about a rounding mode? Not now!
      rtof = !r ? 0 : { sign_r, wexp'( exp_r + bias_h - bias_r ), sig_f };
  endfunction
  static function real ftor( logic [w-1:0] f );
      ftor = !f ? 0.0
        : <u>$bitstoreal</u>
          ( { f[w-1],
              w_exp_r'( bias_r + f[w-2:wsig] - bias_h ),
              f[wsig-1:0], (w_sig_r-wsig)'(0) } );
  endfunction
  static function int err_bits( logic [w-1:0] a, b );
      logic [wsig-1:0] sig_a, sig_b;
      logic [wsig+2:0] frac_a, frac_b, frac_diff;
      logic [wexp-1:0] exp_a, exp_b;
      logic s_a, s_b;
      int delta e;
      if ( <u>$isunknown(a) || $isunknown(b)</u> ) return 1 << wexp;</pre>
      if ( a == b ) return 0;
      { s_a, exp_a, sig_a } = a;
      { s_b, exp_b, sig_b } = b;
      if ( exp_a == 0 || exp_b == 0 ) begin
         logic [wsig-1:0] sig = ~ ( sig_a | sig_b );
         return 1 + wsig - <u>$clog2(</u> sig + 1 );
      end
      delta_e = \frac{abs}{0} + exp_a - exp_b ;
      if ( delta_e > 1 ) return delta_e + wsig;
      frac_a = exp_a > exp_b ? { 2'b1, sig_a, 1'b0 } : { 3'b1, sig_a };
      frac_b = exp_b > exp_a ? { 2'b1, sig_b, 1'b0 } : { 3'b1, sig_b };
      frac_diff =
        s_a != s_b ? frac_a + frac_b :
        frac_a > frac_b ? frac_a - frac_b : frac_b - frac_a;
      return <u>$clog2(</u> frac_diff + 1 );
```

endfunction

endclass

// cadence translate_on

```
// cadence translate_off
// Module names. (Used by the testbench.)
11
typedef enum { M_int, M_fp } M_Type;
module testbench;
   localparam int n_tests = 100000;
   localparam int npsets = 3; // This MUST be set to the size of pset.
   // { w_exp, w_sig, wc_int }
   localparam int pset[npsets][3] =
               '{
                {7, 6, 6},
                \{7, 7, 10\},\
                { 8, 5, 12 }
                };
   localparam int nmsets = 2;
   localparam M_Type mset[2] = '{ M_int, M_fp };
   string mtype_str[M_Type] = '{ M_int: "comp_int", M_fp: "comp_fp " };
   string mtype_abbr[M_Type] = '{ M_int: "in", M_fp: "fp" };
   int t_errs_mod[M_Type];
   int t_errs_each_gt[M_Type][int][2];
   int t_errs_each_ss[M_Type][int][2];
   int t_errs_size_gt[int][2];
   int t_errs_size_ss[int][2];
   int t_errs_each[M_Type][int];
   localparam int nsets = npsets * nmsets;
   logic d[nsets:-1]; // Start / Done signals.
                                        // Total number of errors.
   int t_errs_gt[2], t_errs_ss[2];
   initial begin
      t_errs_gt = '{0,0};
      t_errs_ss = '{0,0};
      for ( int m=0; m<nmsets; m++ )</pre>
        for ( int i=0; i<npsets; i++ ) begin</pre>
           t_errs_each_gt[mset[m]][i] = '{-1,-1};
           t_errs_each_ss[mset[m]][i] = '{-1,-1};
        end
      d[-1] = 1;
   end
   final begin
   `ifdef xxx
      $write("\nNumber of tests: %0d.\n", n_tests);
      for ( int i=0; i<npsets; i++ )</pre>
        <u>$write("Total for exp=%0d, sig=%0d, wc=%2d: Err (s=0): %0d ss, %0d gt. Err (s>0): %0d ss, %0d gt.\n",</u>
               pset[i][0], pset[i][1], pset[i][2],
               t_errs_size_ss[i][1], t_errs_size_gt[i][1],
               t_errs_size_ss[i][0], t_errs_size_gt[i][0]);
      for ( int i=0; i<nmsets; i++ )</pre>
        $write("Total for mod %4s: %5d errors.\n",
               mtype_str[mset[i]],
               t_errs_mod[mset[i]]
               );
      `endif
      for ( int mi=0; mi<nmsets; mi++ )</pre>
        for ( int i=0; i<npsets; i++ ) begin</pre>
```

 $\leftarrow \rightarrow$ Fall 2024

 $\leftarrow \rightarrow$ Homework 2

```
\leftarrow \ \rightarrow \ \text{Fall} \ 2024
                      \leftarrow \rightarrow Homework 2
                                                        Homework Solution Sol Code
                automatic M_Type m = mset[mi];
                for ( int j=1; j>=0; j-- )
                   <u>$write("Total %s exp=%0d, sig=%0d, wc=%2d, %s: Errors: %0d ss, %0d gt.\n",</u>
                          mtype_str[m],
                          pset[i][0], pset[i][1], pset[i][2], j == 0 ? "s>0" : "s=0",
                          t_errs_each_ss[m][i][j], t_errs_each_gt[m][i][j] );
             end
           // $write("Total number of errors (s=0): ss %0d, gt %0d. (s>0): ss %0d, gt %0d.\n",
                   // t_errs_ss[1], t_errs_gt[1], t_errs_ss[0], t_errs_gt[0]);
       end
       for ( genvar m=0; m<nmsets; m++ )</pre>
          for ( genvar i=0; i<npsets; i++ ) begin</pre>
             localparam int idx = m * npsets + i;
             testbench n
               #( .w_exp(pset[i][0]), .w_sig(pset[i][1]), .w_c(pset[i][2]),
                   .pset(i), .mtype(mset[m]) )
             t2( .done(d[idx]), .tstart(d[idx-1]) );
          end
```

endmodule

```
module testbench_n
  #(int w_exp = 5, w_sig = 8, w_c = 12,
     pset = 0, M_Type mtype = M_fp )
   ( output logic done, input uwire tstart );
   // Number of sample outputs to print (whether correct or not).
  localparam int n_samples = 1;
  localparam int w_s = w_exp-1;
  localparam int w_fp = 1 + w_sig + w_exp;
  localparam int bias = ( 1 << w_exp-1 ) - 1;</pre>
  localparam int w_sig2 = w_c + 1;
  localparam int w_fp2 = 1 + w_sig2 + w_exp;
  logic [w_c-1:0] c;
  logic [w_s-1:0] sl;
  logic [w_fp-1:0] a, b;
  uwire [w_fp2-1:0] ssum;
  uwire gt;
  localparam int c_max = ( 1 << w_c ) - 1;</pre>
  case ( mtype )
    M_fp:
       comp_fp #( w_c, w_s, w_exp, w_sig, w_sig2 )
     c1(gt, ssum, a, b, sl, c);
     M int:
       comp_int #( w_c, w_s, w_exp, w_sig, w_sig2 )
    c1(gt, ssum, a, b, sl, c);
   endcase
  initial begin
      automatic int n_tests = testbench.n_tests;
      automatic int n_err_gt[2] = '{0,0}, n_err_ss[2] = '{0,0};
      automatic int n_gt = 0;
     wait( tstart );
      $write("\nStarting %4s tests iwth exp=%0d, sig=%0d, wc=%0d\n",
             testbench.mtype_str[mtype], w_exp, w_sig, w_c);
```

```
    ← → Fall 2024    ← → Homework 2 Homework Solution Sol Code
    for (int i=0; i<n_tests; i++ ) begin
        automatic bit choose_close = $random() & 1'b1;
        automatic bit sl_zero = i < n_tests / 2;
        automatic bit ab_positive = 0;
        logic [w_fp2-1:0] shadow_ssumf;
        int eb_ssum, c_pre;
        real ar, br, shadow_ar, shadow_br, shadow_ssumr, delta, a_scr, ssumr;
    }
}
Homework Solution Sol Code
</pre>
```

```
real tol;
logic shadow_gt;
bit err_ss, err_gt, err;
c = $random() & 7 ? rand_wid(w_c) : c_max;
sl = sl_zero ? 0 : 1 + rand_wid(w_exp-2);
ar = ( ab_positive ? rand_fp(0,1):rand_fp(-0.5,0.5) )*rand_wid(w_c+2);
```

```
a_scr = ar * 2 ** sl;
```

```
br = choose_close
? c - a_scr + rand_fp(-1,1)
: ( ab_positive ? rand_fp(0,1):rand_fp(-0.5,0.5) ) * rand_wid(w_c+2);
```

```
if ( ab_positive \& br < 0 ) br = -br;
```

```
a = conv#(w_exp,w_sig)::rtof( ar );
b = conv#(w_exp,w_sig)::rtof( br );
```

```
shadow_ar = conv#(w_exp,w_sig)::ftor( a );
shadow_br = conv#(w_exp,w_sig)::ftor( b );
shadow_ssumr = shadow_ar * 2.0**sl + shadow_br;
shadow_ssumf = conv#(w_exp,w_sig2)::rtof(shadow_ssumr);
delta = shadow_ssumr - c;
tol = c / real'( 1 << w_sig2 + 1 );
shadow_gt = shadow_ssumr > c;
n_gt += shadow_gt;
```

#1;

```
ssumr = conv#(w_exp,w_sig2)::ftor(ssum);
err_gt = fabs(delta) > tol && gt !== shadow_gt;
eb_ssum = conv#(w_exp,w_sig2)::err_bits(ssum,shadow_ssumf);
err_ss = eb_ssum > 1;
err = err_gt || err_ss;
if ( i < n samples || err ) begin</pre>
   if ( err_gt ) n_err_gt[sl_zero]++;
   if ( err_ss ) n_err_ss[sl_zero]++;
   if ( i < n_samples || err_ss && n_err_ss[sl_zero] < 5 )</pre>
     <u>$write(</u> "%s %s #(%0d,%0d,%0d) a=%.2f, s=%0d, b=%.2f, c=%0d. ss %.4e %s %.4e (correct)\n",
             err_ss ? "Error " : "Sample",
             testbench.mtype_abbr[mtype],
             w_exp, w_sig, w_c,
             shadow_ar, sl, shadow_br, c,
             ssumr, err_ss ? "!=" : "==", shadow_ssumr );
   if ( i < n_samples || err_gt && n_err_gt[sl_zero] < 5 )</pre>
     <u>$write(</u> "%s %s #(%0d,%0d,%0d) a=%.2f, s=%0d, b=%.2f, c=%0d. gt %h %s %h (correct) %g\n",
             err_gt ? "Error " : "Sample",
             testbench.mtype_abbr[mtype],
             w_exp, w_sig, w_c,
             shadow ar, sl, shadow br, c,
```

gt, err_gt ? "!=" : "==", shadow_gt, delta);

```
end
```

```
for ( int i=1; i>=0; i-- )
    <u>$write</u>("Finished %4s tests exp=%0d, sig=%0d, wc=%0d, %s. Errors: %0d ss, %0d gt\n",
        testbench.mtype_str[mtype], w_exp, w_sig, w_c,
        i == 0 ? "s>0" : "s=0",
        n_err_ss[i], n_err_gt[i]);
// $write("Frac gt %.4f\n", real'(n_gt)/n_tests);
for ( int i=0; i<2; i++ ) begin
      testbench.t_errs_gt[i] += n_err_gt[i];
      testbench.t_errs_ss[i] += n_err_ss[i];
      testbench.t_errs_each_gt[mtype][pset][i] = n_err_gt[i];
      testbench.t_errs_each_ss[mtype][pset][i] = n_err_ss[i];
end
done = 1;
end</pre>
```

endmodule

```
// Define SIMULATION_ON in a translate_off region. Used to control
// whether simulation or synthesis versions of Chipware modules are
// included.
//
`define SIMULATION_ON
//
// cadence translate_on
```

`default_nettype wire

```
`ifdef SIMULATION_ON
```

`include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/sim/verilog/CW/CW_fp_mult.v" `include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/sim/verilog/CW/CW_fp_add.v" `include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/sim/verilog/CW/CW_fp_div.v" `include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/sim/verilog/CW/CW_fp_div.v" `include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/sim/verilog/CW/CW_fp_div.v" `include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/sim/verilog/CW/CW_fp_i2flt.v" `include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/sim/verilog/CW/CW_fp_i2flt.v" `include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/sim/verilog/CW/CW_fp_flt2i.v" `include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/sim/verilog/CW/CW_fp_flt2i.v" `include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/sim/verilog/CW/CW_fp_flt2i.v" `include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/sim/verilog/CW/CW_fp_cmp.v"

`include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/syn/CW/CW_fp_mult.v" `include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/syn/CW/CW_fp_add.v" `include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/syn/CW/CW_fp_sub.v" `include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/syn/CW/CW_fp_i2flt.v" `include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/syn/CW/CW_fp_i2flt.v" `include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/syn/CW/CW_fp_flt2i.v" `include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/syn/CW/CW_fp_flt2i.v" `include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/syn/CW/CW_fp_div.v"

`endif

/// Assignment https://www.ece.lsu.edu/koppel/v/2024/hw03.pdf

`default_nettype none

/// Convenient Character Names
//
typedef enum logic [3:0]
 { Char_Blank, Char_Dot,
 Char_Open, Char_Close,

Char_Open_Okay, Char_Close_Okay } Char;

/// Complete pmatch_base.

11 11 [<] The module can use procedural code.</pre> 11 [] The module must a recursive and describe tree-structured hardware. 11 11 $[\checkmark]$ Make sure that the testbench does not report errors. [/] Module must be synthesizable. Use command: genus -files syn.tcl 11 11 11 [Jon't assume any particular parameter values. 11 11 [<] As always, code must be written clearly.</pre> [.] As always, pay attention to cost and performance. 11

```
module pmatch_base
```

```
/// SOLUTION
```

if (n == 1) begin

// There is only one character, so if it's a parenthesis it must
// be unmatched.
//
assign left_out_n_unmat_close = str[0] == Char_Close ? 1 : 0;

```
assign right_out_n_unmat_open = str[0] == Char_Open ? 1 : 0;
```

```
end else begin
```

// Split the string between recursive instantiations.
//

```
localparam int n_left = n/2;
localparam int n_right = n - n_left;
localparam int wl = $clog2(n_left+1), wr = $clog2(n_right+1);
11
uwire [wl-1:0] lt_close, lt_open;
uwire [wr-1:0] rt_close, rt_open;
11
pmatch base #(n_left, wl) plt( lt_close, lt_open, str[0:n_left-1] );
pmatch_base #(n_right, wr) prt( rt_close, rt_open, str[n_left:n-1] );
// Compute the number of remaining unmatched opening parentheses
// when the lt_open unmatched parentheses from plt are matched
// with the rt_close closing parentheses from prt.
11
uwire logic signed [wn-1:0] delta = lt_open - rt_close;
11
// If delta is positive there are leftover unmatched opening
// parentheses that need to be added to output
// right_out_n_unmat_open, and if delta is negative there are
// leftover unmatched closing parentheses that need to be added
// to output left_out_n_unmat_close.
11
// Note: Declaring delta as a *signed* type is necessary so that
// the comparisons below, such as "delta >= 0" are correct. If
// delta were unsigned then "delta >= 0" would always be true!
11
assign right_out_n_unmat_open = delta >= 0 ? rt_open + delta : rt_open;
assign left_out_n_unmat_close = delta < 0 ? lt_close - delta : lt_close;</pre>
```

end

 $\leftarrow \rightarrow$ Fall 2024

 $\leftarrow \rightarrow$ Homework 3

endmodule

```
\leftarrow \rightarrow Fall 2024
                  \leftarrow \rightarrow Homework 3
                                              Homework Sol Code Sol Code
                                                                                         hw03-sol-p1.v.html
            if ( str[i] == Char_Close ) begin
                // We've found a closing parenthesis, ")".
                if ( right_out_n_unmat_open > 0 )
                  right_out_n_unmat_open--; // It matches an opening parenthesis.
                else
                  left_out_n_unmat_close++; // It's unmatched, update the count.
            end else if ( str[i] == Char_Open ) begin
                // We've found an opening parenthesis, "(".
                // Increment the count of unmatched open parentheses ...
                right_out_n_unmat_open++;
                // .. which might be decremented in a later iteration.
            end
```

e

end

endmodule

/// Problem 2 11 /// Complete pmatch_mark 11 [] The module can use procedural code. 11 [] The module must a recursive and describe tree-structured hardware. 11 11 11 [] Make sure that the testbench does not report errors. 11 [] Module must be synthesizable. Use command: genus -files syn.tcl 11 11 [] Don't assume any particular parameter values. 11 11 [] As always, code must be written clearly. 11 [] As always, pay attention to cost and performance.

module pmatch_mark

```
#( int n = 5, wn = <u>$clog2(n+1)</u>)
( output logic [wn-1:0] left_out_n_unmat_close, right_out_n_unmat_open,
    output uwire [3:0] str_marked [0:n-1],
    input uwire [wn-1:0] left_in_n_unmat_open, right_in_n_unmat_close,
    input uwire [3:0] str [0:n-1] );
```

endmodule

```
\#( int n = 5, wn = \frac{clog2}{n+1} )
 ( output logic [wn-1:0] left_out_n_unmat_close, right_out_n_unmat_open,
   output logic [3:0] str_marked [0:n-1],
   input uwire [wn-1:0] left_in_n_unmat_open, right_in_n_unmat_close,
   input uwire [3:0] str [0:n-1] );
 /// Reference Module
 11
 // Examine this module to help understand how to solve the problem.
 11
 // The solution should NOT BE placed in this module.
 always_comb begin
    automatic logic [wn-1:0] n_um_op = left_in_n_unmat_open;
    automatic logic [wn-1:0] n_um_cl = right_in_n_unmat_close;
    left_out_n_unmat_close = 0;
    right_out_n_unmat_open = 0;
    str_marked = str;
    // Scan string from left to right. (Leftmost character is at i=0.)
    11
    // The loop below is identical to the one in pmatch_comb_base.
    11
    for ( int i=0; i<n; i++ )</pre>
      if ( str[i] == Char_Close ) begin
         // We've found a closing parenthesis, ")".
         if ( right_out_n_unmat_open > 0 )
           right_out_n_unmat_open--; // It matches an opening parenthesis.
         else
           left_out_n_unmat_close++; // It's unmatched, update the count.
      end else if ( str[i] == Char_Open ) begin
         // We've found an opening parenthesis, "(".
         // Increment the count of unmatched open parentheses ...
         right_out_n_unmat_open++;
         // .. which might be decremented in a later iteration.
      end
    // Scan string forward and mark matched closing parentheses.
    11
    for ( int i=0; i<n; i++ )</pre>
      if ( str[i] == Char_Close && n_um_op > 0 ) begin
         n_um_op--;
         str_marked[i] = Char_Close_Okay;
      end else if ( str[i] == Char_Open ) begin
```

Homework Sol Code Sol Code

hw03-sol-p1.v.html

 $\leftarrow \rightarrow$ Fall 2024

 $\leftarrow \rightarrow$ Homework 3

```
n_um_op++;
```

```
end
```

```
// Scan string backward and mark matched opening parentheses.
//
for ( int i=n-1; i>=0; i-- )
    if ( str[i] == Char_Open && n_um_cl > 0 ) begin
        n_um_cl--;
        str_marked[i] = Char_Open_Okay;
end else if ( str[i] == Char_Close ) begin
        n_um_cl++;
end
end
```

endmodule


```
// cadence translate_off
// Module names. (Used by the testbench.)
11
typedef enum { M_base, M_mark } M_Type;
module testbench;
   localparam int n_tests = 100000;
   localparam int npsets = 6; // This MUST be set to the size of pset.
   localparam int pset[npsets][1] =
              '{{ 4 }, { 5 }, { 7 }, { 8 }, { 9 }, { 17 }};
   localparam int nmsets = 2;
   localparam M_Type mset[2] = '{ M_base, M_mark };
   string mtype_str[M_Type] =
          '{ M_base: "pmatch_base", M_mark: "pmatch_mark" };
   string mtype_abbr[M_Type] = '{ M_base: "base", M_mark: "mark" };
   int t_errs_each_cl[M_Type][int];
   int t_errs_each_op[M_Type][int];
   int t_errs_each_mk[M_Type][int];
   int t_errs_cl, t_errs_op, t_errs_mk;
```
```
\leftarrow \rightarrow Fall 2024
                  \leftarrow \rightarrow Homework 3
                                              Homework Sol Code Sol Code
       localparam int nsets = npsets * nmsets;
       logic d[nsets:-1]; // Start / Done signals.
       initial begin
          t_errs_cl = 0;
          t_errs_op = 0; t_errs_mk = 0;
          for ( int m=0; m<nmsets; m++ )</pre>
            for ( int i=0; i<npsets; i++ ) begin</pre>
                automatic int n = pset[i][0];
               t_errs_each_cl[mset[m]][n] = 0;
               t_errs_each_op[mset[m]][n] = 0;
                t_errs_each_mk[mset[m]][n] = 0;
            end
          d[-1] = 1;
       end
       final begin
          for ( int mi=0; mi<nmsets; mi++ )</pre>
            for ( int i=0; i<npsets; i++ ) begin</pre>
                automatic M_Type m = mset[mi];
               automatic int n = pset[i][0];
               $write("Total %s n=%0d: Errors: %0d cl, %0d op, %0d mk.\n",
                       mtype_str[m], n,
                       t_errs_each_cl[m][n],
                       t_errs_each_op[m][n],
                       t_errs_each_mk[m][n]);
            end
       end
       for ( genvar m=0; m<nmsets; m++ )</pre>
         for ( genvar i=0; i<npsets; i++ ) begin</pre>
            localparam int idx = m * npsets + i;
            testbench n
              #( .n(pset[i][0]), .mtype(mset[m]) )
            t2( .done(d[idx]), .tstart(d[idx-1]) );
         end
   endmodule
   module testbench n
      #( int n = 4, M_Type mtype = M_base )
       ( output logic done, input uwire tstart );
       localparam int wn = $clog2(n+1);
       localparam int n_tests = 2000;
       localparam int n samples show = 10;
```

```
localparam int n_errors_show = 5;
```

```
uwire [wn-1:0] n_cl_lt, n_op_rt;
logic [wn-1:0] n_u_op, n_u_cl;
logic [3:0] str[0:n-1];
uwire [3:0] str_marked[0:n-1];
string char_to_ascii[logic[3:0]] =
       '{ Char_Blank: " ",
          Char_Dot: ".",
          Char_Open: "(",
          Char_Open_Okay: "<",
          Char_Close: ")",
          Char_Close_Okay: ">" };
logic [3:0] ascii_to_char[string];
function automatic string char_to_string( logic [3:0] str[0:n-1] );
   automatic string str_txt = "";
   for ( int j=0; j<n; j++ ) str_txt = { str_txt, char_to_ascii[str[j]] };</pre>
   char_to_string = str_txt;
endfunction
case ( mtype )
 M_base:
    pmatch base #(n,wn) pm( n_cl_lt, n_op_rt, str );
    // pmatch_comb_base #(n,wn) pcomb( n_cl_lt, n_op_rt, str );
 M mark:
    pmatch_mark #(n,wn) pm(n_cl_lt,n_op_rt,str_marked,n_u_op,n_u_cl, str );
    // pmatch_comb_mark #(n,wn) pm( n_cl_lt, n_op_rt, str_marked, n_u_op, n_u_cl, str );
endcase
```

```
initial begin
```

```
automatic int n_errs_cl =0, n_errs_op = 0, n_errs_mk = 0;
automatic int n_samples = 0;
automatic string prefix_txt =
    <u>$sformatf</u>("%s n=%0d",testbench.mtype_str[mtype],n);
automatic string prefix_txt_str;
foreach ( char_to_ascii[c] ) ascii_to_char[char_to_ascii[c]] = c;
wait( tstart );
<u>$write</u>("Starting %s tests for n=%0d.\n",
    testbench.mtype_str[mtype], n);
```

```
for ( int i=0; i<n_tests; i++ ) begin</pre>
   automatic int shadow_n_close_lt, shadow_n_open_rt;
   automatic int n_unm_op, n_unm_cl;
   automatic string str_txt;
   automatic logic [3:0] shadow_str_e[0:n-1];
   automatic bit err_cl, err_op, err_mk, err;
   n_u_op = 0;
   n_u_c1 = 0;
   if ( i < str_special.size() ) begin</pre>
      automatic string spc = str_special[i];
      foreach ( spc[j] ) str[j] = ascii_to_char[spc[j]];
      for ( int j=spc.len(); j<n; j++ ) str[j] = Char_Blank;</pre>
   end else begin
      for ( int j=0; j<n; j++ ) str[j] = (4)'({<u>$random</u>} % 4);
   end
   str_txt = char_to_string( str );
   shadow n close lt = 0;
   shadow_n_open_rt = 0;
   for ( int j=0; j<n; j++ ) begin</pre>
      if ( str[j] == Char_Close ) begin
        if ( shadow_n_open_rt ) shadow_n_open_rt--;
        else shadow_n_close_lt++;
      end
      if ( str[j] == Char_Open ) shadow_n_open_rt++;
   end
   n_unm_op = n_u_op;
   shadow_str_e = str;
   for ( int j=0; j<n; j++ ) begin</pre>
      if ( str[j] == Char_Close ) begin
         if ( n_unm_op > 0 ) begin
            shadow_str_e[j] = Char_Close_Okay;
            n_unm_op--;
         end
      end
      if ( str[j] == Char_Open ) n_unm_op++;
   end
   n_unm_cl = n_u_cl;
   for ( int j=n-1; j>=0; j-- ) begin
      if ( str[j] == Char_Open ) begin
         if ( n_unm_cl > 0 ) begin
            shadow_str_e[j] = Char_Open_Okay;
            n_unm_cl--;
         end
      end
```

```
Homework Sol Code Sol Code
\leftarrow \rightarrow Fall 2024
                 \leftarrow \rightarrow Homework 3
                                                                                        hw03-sol-p1.v.html
                if ( str[j] == Char_Close ) n_unm_cl++;
             end
             #1;
             err_cl = n_cl_lt !== shadow_n_close_lt;
             err_op = n_op_rt !== shadow_n_open_rt;
             err_mk = mtype == M_mark && str_marked !== shadow_str_e;
             err = err_cl || err_op || err_mk;
             prefix_txt_str = <u>$sformatf("%s '%s'",prefix_txt,str_txt);</u>
             if ( !err && n_samples < n_samples_show ) begin</pre>
                n_samples++;
                $write("Sample %s: close = %0d, open = %0d (both correct)\n",
                        prefix_txt_str, n_cl_lt, n_op_rt);
                if ( mtype == M_mark )
                  $write("Sample %s '%s' (marked_outpuut)\n",
                          prefix_txt, char_to_string(shadow_str_e));
             end
             if ( err_cl ) begin
                n_errs_cl++;
                if ( n_errs_cl < n_errors_show )</pre>
                  $write("Error %s: close %0d != %0d (correct)\n",
                          prefix_txt_str, n_cl_lt, shadow_n_close_lt);
             end
             if ( err_op ) begin
                n_errs_op++;
                if ( n_errs_op < n_errors_show )</pre>
                  $write("Error %s: open %0d != %0d (correct)\n",
                          prefix_txt_str, n_op_rt, shadow_n_open_rt);
             end
             if ( err_mk ) begin
                n_errs_mk++;
                if ( n_errs_mk < n_errors_show ) begin</pre>
                   $write("Error %s: '%s' != '%s' (correct)\n",
                           prefix_txt,
                           char_to_string(str_marked), char_to_string(shadow_str_e));
                end
             end
          end
          <u>$write</u>("Done with tests %s. Errors: %0d cl, %0d op, %0d mark.\n",
                 prefix_txt,
                 n_errs_cl, n_errs_op, n_errs_mk);
          testbench.t_errs_each_cl[mtype][n] = n_errs_cl;
          testbench.t_errs_each_op[mtype][n] = n_errs_op;
          testbench.t_errs_each_mk[mtype][n] = n_errs_mk;
```

done = 1;

end

endmodule

// cadence translate_on

/// Assignment https://www.ece.lsu.edu/koppel/v/2024/hw03.pdf

`default_nettype none

/// Convenient Character Names
//
typedef enum logic [3:0]
 { Char_Blank, Char_Dot,
 Char_Close

Char_Open, Char_Close, Char_Open_Okay, Char_Close_Okay } Char;


```
/// Complete pmatch_base.
11
11
       [<] The module can use procedural code.</pre>
11
       [...] The module must a recursive and describe tree-structured hardware.
11
11
       [<] Make sure that the testbench does not report errors.</pre>
       [ / ] Module must be synthesizable. Use command: genus -files syn.tcl
11
11
11
       [ Jon't assume any particular parameter values.
11
11
       [<] As always, code must be written clearly.</pre>
       [...] As always, pay attention to cost and performance.
11
```

```
module pmatch_base
```

```
/// SOLUTION
```

if (n == 1) begin

assign left_out_n_unmat_close = str[0] == Char_Close; assign right_out_n_unmat_open = str[0] == Char_Open;

end else begin

```
localparam int n_left = n/2;
localparam int n_right = n - n_left;
localparam int wl = <u>$clog2(n_left+1)</u>, wr = <u>$clog2(n_right+1)</u>;
```

```
uwire [wl-1:0] lt_close, lt_open;
```

```
\leftarrow \rightarrow Fall 2024
                  \leftarrow \rightarrow Homework 3
                                             Homework Sol Code Sol Code
          uwire [wr-1:0] rt_close, rt_open;
          pmatch base #(n_left, wl) plt( lt_close, lt_open, str[0:n_left-1] );
          pmatch_base #(n_right, wr) prt( rt_close, rt_open, str[n_left:n-1] );
          uwire logic signed [wn-1:0] delta = lt_open - rt_close;
          assign left_out_n_unmat_close = delta >= 0 ? lt_close : lt_close - delta;
          assign right_out_n_unmat_open = delta < 0 ? rt_open : rt_open + delta;</pre>
       end
   endmodule
   module pmatch comb base
     \#( int n = 5, wn = \frac{clog2}{n})
       ( output logic [wn-1:0] left_out_n_unmat_close, right_out_n_unmat_open,
         input uwire [3:0] str[0:n-1] );
       /// Reference Module
       11
       // Examine this module to help understand how to solve the problem.
       11
       // The solution should NOT BE placed in this module.
       always_comb begin
          left_out_n_unmat_close = 0;
          right_out_n_unmat_open = 0;
          // Scan string from left to right. (Leftmost character is at i=0.)
          for ( int i=0; i<n; i++ )</pre>
            if ( str[i] == Char_Close ) begin
```

hw03-sol.v.html

// We've found a closing parenthesis, ")".

```
if ( right_out_n_unmat_open > 0 )
    right_out_n_unmat_open--; // It matches an opening parenthesis.
else
    left_out_n_unmat_close++; // It's unmatched, update the count.
```

```
end else if ( str[i] == Char_Open ) begin
```

```
// We've found an opening parenthesis, "(".
```

```
// Increment the count of unmatched open parentheses ..
right_out_n_unmat_open++;
// .. which might be decremented in a later iteration.
```

end

endmodule

//// Problem 2 // /// Complete pmatch_mark // // [~] The module can use procedural code. // [~] The module must a recursive and describe tree-structured hardware.

```
//
// [*] Make sure that the testbench does not report errors.
// [*] Module must be synthesizable. Use command: genus -files syn.tcl
//
// [*] Don't assume any particular parameter values.
//
// [*] As always, code must be written clearly.
// [*] As always, pay attention to cost and performance.
```

```
module pmatch_mark
```

```
#( int n = 5, wn = $clog2(n+1) )
  ( output logic [wn-1:0] left_out_n_unmat_close, right_out_n_unmat_open,
    output uwire [3:0] str_marked [0:n-1],
    input uwire [wn-1:0] left_in_n_unmat_open, right_in_n_unmat_close,
    input uwire [3:0] str [0:n-1] );
```

```
/// SOLUTION
```

```
if ( n == 1 ) begin
assign left_out_n_unmat_close = str[0] == Char_Close;
assign right_out_n_unmat_open = str[0] == Char_Open;
```

```
assign str_marked[0] =
    str[0] == Char_Close && left_in_n_unmat_open ? Char_Close_Okay :
    str[0] == Char_Open && right_in_n_unmat_close ? Char_Open_Okay :
    str[0];
```

```
end else begin
```

```
localparam int n_left = n/2;
localparam int n_right = n - n_left;
localparam int wl = $clog2( n_left+1 );
localparam int wr = $clog2( n_right+1 );
localparam logic [wl-1:0] nl_max = ~(wl)'(0); // All 1's.
localparam logic [wr-1:0] nr_max = ~(wr)'(0); // All 1's.
'define min(a,limit) ( unsigned'(a) <= (limit) ? a : limit )
// Recursive Instance Outputs
//
uwire [wl-1:0] lt_close, lt_open;
```

```
\leftarrow \rightarrow Fall 2024
                 \leftarrow \rightarrow Homework 3
                                            Homework Sol Code Sol Code
          uwire [wr-1:0] rt_close, rt_open;
          // Same as Problem 1
          11
          uwire signed [wn-1:0] delta = lt_open - rt_close;
          assign left_out_n_unmat_close = delta >= 0 ? lt_close : lt_close - delta;
          assign right_out_n_unmat_open = delta < 0 ? rt_open : rt_open + delta;</pre>
          /// Problem 2
          11
          // Pass the incoming number of matched parentheses to the
          // recursive instances. Use min in case their values are too
          // large.
          11
          uwire [wl-1:0] lt_matched_cl = `min( left_in_n_unmat_open,  nl_max );
          uwire [wr-1:0] rt_matched_op = `min( right_in_n_unmat_close, nr_max );
          /// Compute Right Recursive Instance Input rt_matched_cl
          11
          // Compute the number of closing parentheses that could be
          // matched in the right recursive instance (rt_matched_cl) using
          // the incoming unmatched opening parentheses and unmatched
          // opening parentheses found in the left instance.
          11
          // First, compute more_op: the number of unmatched incoming open
          // parentheses that were not matched by the portion of str
          // connected to the left recursive instance (plt).
          //
          uwire signed [wn:0] more_op = left_in_n_unmat_open - lt_close;
          11
          // Then, compute the number of unmatched opening parentheses to
          // the left of position str[n_left], accounting for the opening
          // parentheses found by the left recursive instance (lt_open)
          // and still unmatched incoming open parentheses (more_op).
          11
          uwire [wr-1:0] rt_matched_cl =
                 more_op < 0 ? lt_open : `min( lt_open + more_op, nr_max );</pre>
          /// Compute Left Recursive Instance Input It_matched_op
          11
          // Similar to the procedure above, compute the number of still
          // unmatched incoming closing parentheses (more_cl) and combine
          // it with the number of closing parentheses found in the right
          // recursive instance.
          11
          uwire signed [wn:0] more_cl = right_in_nunmat_close - rt_open;
          uwire [wl-1:0] lt_matched_op =
                 more_cl < 0 ? rt_close : `min( rt_close + more_cl, nl_max );</pre>
          /// Recursive Instantiations
          11
          pmatch mark #(n_left,wl)
          plt( lt_close, lt_open, str_marked[0:n_left-1],
               lt_matched_cl, lt_matched_op, str[0:n_left-1] );
```

hw03-sol.v.html

```
\leftarrow \rightarrow Fall 2024 \leftarrow \rightarrow Homework 3
```

```
pmatch mark #(n_right,wr)
      prt( rt_close, rt_open, str_marked[n_left:n-1],
           rt_matched_cl, rt_matched_op, str[n_left:n-1] );
   end
endmodule
module pmatch_comb_mark
  \#( int n = 5, wn = \frac{clog2}{n+1} )
   ( output logic [wn-1:0] left_out_n_unmat_close, right_out_n_unmat_open,
     output logic [3:0] str_marked [0:n-1],
     input uwire [wn-1:0] left_in_n_unmat_open, right_in_n_unmat_close,
     input uwire [3:0] str [0:n-1] );
   /// Reference Module
   11
   // Examine this module to help understand how to solve the problem.
   11
   // The solution should NOT BE placed in this module.
   always_comb begin
      automatic logic [wn-1:0] n_um_op = left_in_n_unmat_open;
      automatic logic [wn-1:0] n_um_cl = right_in_n_unmat_close;
      left_out_n_unmat_close = 0;
      right_out_n_unmat_open = 0;
      str_marked = str;
      // Scan string from left to right. (Leftmost character is at i=0.)
      11
      // The loop below is identical to the one in pmatch_comb_base.
      11
      for ( int i=0; i<n; i++ )</pre>
        if ( str[i] == Char_Close ) begin
           // We've found a closing parenthesis, ")".
           if ( right_out_n_unmat_open > 0 )
             right_out_n_unmat_open--; // It matches an opening parenthesis.
           else
             left_out_n_unmat_close++; // It's unmatched, update the count.
        end else if ( str[i] == Char_Open ) begin
           // We've found an opening parenthesis, "(".
           // Increment the count of unmatched open parentheses ...
           right_out_n_unmat_open++;
           // .. which might be decremented in a later iteration.
```

```
// Scan string forward and mark matched closing parentheses.
   11
   for ( int i=0; i<n; i++ )</pre>
     if ( str[i] == Char_Close && n_um_op > 0 ) begin
        n_um_op--;
        str_marked[i] = Char_Close_Okay;
     end else if ( str[i] == Char_Open ) begin
        n_um_op++;
     end
   // Scan string backward and mark matched opening parentheses.
   11
   for ( int i=n-1; i>=0; i-- )
     if ( str[i] == Char_Open && n_um_cl > 0 ) begin
        n_um_cl--;
        str_marked[i] = Char_Open_Okay;
     end else if ( str[i] == Char_Close ) begin
        n_um_cl++;
     end
end
```

endmodule


```
// cadence translate_off
```

```
// Module names. (Used by the testbench.)
//
typedef enum { M_base, M_mark } M_Type;
module testbench;
    localparam int n_tests = 100000;
    localparam int npsets = 6; // This MUST be set to the size of pset.
    localparam int pset[npsets][1] =
                              '{{{ 1}} {{ 4 } { 3 , { 5 } { 5 } { , { 5 } { 7 } { 3 , { 5 } { 8 } { 3 , { 5 } { 9 } { 3 , { 17 } { 3 } { ; } { 10calparam int nmsets = 2;
    }
}
```

```
\leftarrow \rightarrow Fall 2024
                  \leftarrow \rightarrow Homework 3
                                              Homework Sol Code Sol Code
       localparam M_Type mset[2] = '{ M_base, M_mark };
       string mtype_str[M_Type] =
               '{ M_base: "pmatch_base", M_mark: "pmatch_mark" };
       string mtype_abbr[M_Type] = '{ M_base: "base", M_mark: "mark" };
       int t_errs_each_cl[M_Type][int];
       int t_errs_each_op[M_Type][int];
       int t_errs_each_mk[M_Type][int];
       int t_errs_cl, t_errs_op, t_errs_mk;
       localparam int nsets = npsets * nmsets;
       logic d[nsets:-1]; // Start / Done signals.
       initial begin
          t_errs_cl = 0;
          t_errs_op = 0; t_errs_mk = 0;
          for ( int m=0; m<nmsets; m++ )</pre>
            for ( int i=0; i<npsets; i++ ) begin</pre>
               automatic int n = pset[i][0];
               t_errs_each_cl[mset[m]][n] = 0;
               t_errs_each_op[mset[m]][n] = 0;
               t_errs_each_mk[mset[m]][n] = 0;
            end
          d[-1] = 1;
       end
       final begin
          for ( int mi=0; mi<nmsets; mi++ )</pre>
            for ( int i=0; i<npsets; i++ ) begin</pre>
               automatic M_Type m = mset[mi];
               automatic int n = pset[i][0];
               $write("Total %s n=%0d: Errors: %0d cl, %0d op, %0d mk.\n",
                       mtype_str[m], n,
                       t_errs_each_cl[m][n],
                       t_errs_each_op[m][n],
                       t_errs_each_mk[m][n]);
            end
       end
       for ( genvar m=0; m<nmsets; m++ )</pre>
         for ( genvar i=0; i<npsets; i++ ) begin</pre>
            localparam int idx = m * npsets + i;
            testbench n
              #( .n(pset[i][0]), .mtype(mset[m]) )
            t2( .done(d[idx]), .tstart(d[idx-1]) );
         end
```

hw03-sol.v.html

endmodule

```
module testbench_n
  #( int n = 4, M_Type mtype = M_base )
   ( output logic done, input uwire tstart );
   localparam int wn = \frac{clog2}{n+1};
   localparam int n_tests = 2000;
   localparam int n_samples_show = 10;
   localparam int n_errors_show = 5;
   uwire [wn-1:0] n_cl_lt, n_op_rt;
   logic [wn-1:0] n_u_op, n_u_cl;
   logic [3:0] str[0:n-1];
   uwire [3:0] str_marked[0:n-1];
   string char_to_ascii[logic[3:0]] =
          '{ Char_Blank: " ",
             Char_Dot: ".",
             Char_Open: "(",
             Char_Open_Okay: "<",
             Char_Close: ")",
             Char_Close_Okay: ">" };
   logic [3:0] ascii_to_char[string];
   function automatic string char_to_string( logic [3:0] str[0:n-1] );
      automatic string str txt = "";
      for ( int j=0; j<n; j++ ) str_txt = { str_txt, char_to_ascii[str[j]] };</pre>
      char_to_string = str_txt;
   endfunction
   case ( mtype )
     M_base:
       pmatch_base #(n,wn) pm( n_cl_lt, n_op_rt, str );
       // pmatch_comb_base #(n,wn) pcomb( n_cl_lt, n_op_rt, str );
     M mark:
       pmatch_mark #(n,wn) pm(n_cl_lt,n_op_rt,str_marked,n_u_op,n_u_cl, str );
       // pmatch_comb_mark #(n,wn) pm( n_cl_lt, n_op_rt, str_marked, n_u_op, n_u_cl, str );
   endcase
```

initial begin

automatic int n_errs_cl =0, n_errs_op = 0, n_errs_mk = 0;

```
\leftarrow \rightarrow Fall 2024
                  \leftarrow \rightarrow Homework 3
                                              Homework Sol Code Sol Code
          automatic int n_samples = 0;
          automatic string prefix_txt =
            $sformatf("%s n=%0d",testbench.mtype_str[mtype],n);
          automatic string prefix_txt_str;
          foreach ( char_to_ascii[c] ) ascii_to_char[char_to_ascii[c]] = c;
          wait( tstart );
          $write("Starting %s tests for n=%0d.\n",
                 testbench.mtype_str[mtype], n);
          for ( int i=0; i<n_tests; i++ ) begin</pre>
             automatic int shadow_n_close_lt, shadow_n_open_rt;
             automatic int n_unm_op, n_unm_cl;
             automatic string str_txt;
             automatic logic [3:0] shadow_str_e[0:n-1];
             automatic bit err_cl, err_op, err_mk, err;
             n_u_op = 0;
             n_u_cl = 0;
             if ( i < str_special.size() ) begin</pre>
                automatic string spc = str_special[i];
                foreach ( spc[j] ) str[j] = ascii_to_char[spc[j]];
                for ( int j=spc.len(); j<n; j++ ) str[j] = Char_Blank;</pre>
             end else begin
                for ( int j=0; j<n; j++ ) str[j] = (4)'({<u>$random</u>} % 4);
             end
             str_txt = char_to_string( str );
             shadow_n_close_lt = 0;
             shadow_n_open_rt = 0;
             for ( int j=0; j<n; j++ ) begin</pre>
                if ( str[j] == Char_Close ) begin
                   if ( shadow_n_open_rt ) shadow_n_open_rt--;
                   else shadow_n_close_lt++;
                end
                if ( str[j] == Char_Open ) shadow_n_open_rt++;
             end
             n_unm_op = n_u_op;
             shadow_str_e = str;
             for ( int j=0; j<n; j++ ) begin</pre>
                 if ( str[j] == Char_Close ) begin
                    if ( n_unm_op > 0 ) begin
                       shadow_str_e[j] = Char_Close_Okay;
                       n_unm_op--;
                    end
```

```
\leftarrow \rightarrow \text{ Fall 2024} \qquad \leftarrow \rightarrow \text{ Homework 3}
```

```
end
   if ( str[j] == Char_Open ) n_unm_op++;
end
n_unm_cl = n_u_cl;
for ( int j=n-1; j>=0; j-- ) begin
   if ( str[j] == Char_Open ) begin
      if ( n_unm_cl > 0 ) begin
         shadow_str_e[j] = Char_Open_Okay;
         n_unm_cl--;
      end
   end
   if ( str[j] == Char_Close ) n_unm_cl++;
end
#1;
err_cl = n_cl_lt !== shadow_n_close_lt;
err_op = n_op_rt !== shadow_n_open_rt;
err_mk = mtype == M_mark && str_marked !== shadow_str_e;
err = err_cl || err_op || err_mk;
prefix_txt_str = <u>$sformatf("%s '%s'",prefix_txt,str_txt);</u>
if ( !err && n_samples < n_samples_show ) begin</pre>
   n_samples++;
   $write("Sample %s: close = %0d, open = %0d (both correct)\n",
          prefix_txt_str, n_cl_lt, n_op_rt);
   if ( mtype == M_mark )
     $write("Sample %s '%s' (marked_outpuut)\n",
            prefix_txt, char_to_string(shadow_str_e));
end
if ( err_cl ) begin
   n_errs_cl++;
   if ( n_errs_cl < n_errors_show )</pre>
     $write("Error %s: close %0d != %0d (correct)\n",
            prefix_txt_str, n_cl_lt, shadow_n_close_lt);
end
if ( err_op ) begin
   n_errs_op++;
   if ( n_errs_op < n_errors_show )</pre>
     $write("Error %s: open %0d != %0d (correct)\n",
            prefix_txt_str, n_op_rt, shadow_n_open_rt);
end
if ( err_mk ) begin
   n errs mk++;
   if ( n_errs_mk < n_errors_show ) begin</pre>
      $write("Error %s: '%s' != '%s' (correct)\n",
             prefix_txt,
             char_to_string(str_marked), char_to_string(shadow_str_e));
   end
```

end

```
end
```

```
testbench.t_errs_each_op[mtype][n] = n_errs_op;
testbench.t_errs_each_mk[mtype][n] = n_errs_mk;
```

done = 1;

end

endmodule

// cadence translate_on

LSU EE 4755

Homework 4 Solution

Due: 8 Nov 2024

Student Expectations

To solve this assignment students are expected to avail themselves of references provided in class and on the Web site, such as for Verilog programming and synthesis examples, and to seek out any additional help and resources that might be needed. (Of course this doesn't mean asking someone else to solve it for you.) It is the students' responsibility to resolve frustrations and roadblocks quickly. (If you get stuck *just ask for help!*)

This assignment cannot be solved by blindly pasting together parts of past assignments. Solving the assignment is a multi-step learning process that takes effort, but one that also provides the satisfaction of progress and of developing skills and understanding.

Collaboration Rules

Each student is expected to complete his or her own assignment. It is okay to work with other students and to ask questions in order to get ideas on how to solve the problems or how to overcome some obstacle (be it a question of Verilog syntax, interpreting error messages, how a part of the problem might be solved, etc.) It is also acceptable to seek out digital design resources for help on Verilog, digital design, etc. It is okay to make use of AI LLM tools such as ChatGPT and Copilot to generate sample Verilog code. (Do not assume LLM output is correct. Treat LLM output the same way one might treat legal advice given by a lawyer character in a movie: it may sound impressive, but it can range from sage advice to utter nonsense.)

After availing oneself to these resources each student is expected to be able to complete the assignment alone. Test questions will be based on homework questions and the assumed time needed to complete the question will be for a student who had solved the homework assignment on which it was based.

Problems start on next page.

Problem 1: Appearing below is the base case from module pmatch_mark in the solution to Homework 3 Problem 2.

```
typedef enum logic [3:0]
  \{ Char_Blank = 0, \}
                        Char_Dot = 1,
    Char_{Open} = 2,
                        Char_Close = 3,
    Char_Open_Okay = 4, Char_Close_Okay = 5 } Char;
module pmatch mark
  \#( int n = 5, wn = \frac{clog2(n+1)}{}
   ( output logic [wn-1:0] left_out_n_unmat_close, right_out_n_unmat_open,
     output uwire [3:0] str_marked [0:n-1],
     input uwire [wn-1:0] left_in_n_unmat_open, right_in_n_unmat_close,
     input uwire [3:0] str [0:n-1] );
  if (n == 1) begin
      assign left_out_n_unmat_close = str[0] == Char_Close;
      assign right_out_n_unmat_open = str[0] == Char_Open;
      assign str_marked[0] =
             str[0] == Char_Close && left_in_n_unmat_open
                                                             ? Char_Close_Okay :
             str[0] == Char_Open && right_in_n_unmat_close ? Char_Open_Okay :
             str[0];
```

Show the hardware that will be inferred for the base case (n==1) shown above.

Show the hardware after optimization and \checkmark for the default value of wn.

In the optimized hardware do not show comparison units, instead show the individual gates performing the comparison, \checkmark optimizing for constant values.

Solution appears to the right with some abbreviated connection names. As in the midterm exam the equality comparisons have been optimized into AND gates. Notice that because n = 1 input str has a single 4-bit element and so str[O] refers to all of str which is four bits and carries a single Char. Because the default value of wn is to be used and n=1 is given we know that $w_n = \lceil \lg(n+1) \rceil = \lceil \lg(2) \rceil = 1$. That means the left_in_un_open (a.k.a. left_in_n_unmat_open) is one bit and so it can be directly connected to an AND gate input. If $w_n > 1$ then an OR gate would be needed before the AND gate. Final exam short answer question?



Problem 2: Appearing below are three variations on a module that will set its output to either the input value, or a maximum value if the input is larger. The module will always be instantiated with wl < wn. All of them are functionally equivalent, but were synthesized to different costs (by Genus 23.12-s086.1 when similar code was used in the solution to Homework 3). Because they are functionally equivalent a perfect synthesis program would synthesize each to the same hardware (with equal costs).

module clamp_plan_a

```
#( int wl = 3, wn = 4 ) ( output uwire [wl-1:0] x, input uwire [wn-1:0] a );
localparam logic [wl-1:0] nl_max = ~(wl)'(0); // Sequence of wl 1s.
assign x = a <= nl_max ? a : nl_max;
endmodule
```

```
module clamp_plan_b
#( int wl = 3, wn = 4 )
```

```
#( int wl = 3, wn = 4 ) ( output uwire [wl-1:0] x, input uwire [wn-1:0] a );
localparam logic [wl-1:0] nl_max = ~(wl)'(0); // Sequence of wl 1s.
assign x = a < nl_max ? a : nl_max;
endmodule
```

```
module clamp_plan_c
```

```
#( int wl = 3, wn = 4 ) ( output uwire [wl-1:0] x, input uwire [wn-1:0] a );
localparam logic [wl-1:0] nl_max = ~(wl)'(0); // Sequence of wl 1s.
assign x = !a[wn-1:wl] ? a : nl_max;
endmodule
```

Show the optimized hardware for the low-cost version(s).

Solution appears to the right. Because nl_max is w_l bits and $w_l > w_n$ it is possible to determine that $a > nl_max$ by checking if any of the bits in positions wn-1:wl are 1. If so, $a > nl_max$, otherwise $a <= nl_max$. The Plan C hardware explicitly uses this optimization, and is shown to the right. For Plan A the solution is based on the assumption that the synthesis program figures out the optimization. The hardware is more complicated for Plan B because to compute $a < nl_max$ the hardware needs to compute $a <= nl_max$ (the AND gate) and $a!=nl_max$ (the OR gate). The Plan B solution is based on a synthesis program that can optimize the comparison this way, but one that can't figure out that there was no need to check for the $a!=nl_max$ case because if $a==nl_max$ either multiplexor input can be used.

Solution continued on next page.



 \checkmark Find the simple-model cost of each after optimization. The costs should be \checkmark in terms of wn and wl.

Plan A and Plan C: Multiplexor (one constant input): $w_l u_c$, OR gate $[w_n - w_l - 1] u_c$.

Plan B: Multiplexor (one constant input): $w_l u_c$, "big" AND gate $[w_n - w_l - 1] u_c$, OR gate $w_l u_c$, little AND gate 1 u_c . Note that the big AND gate might just have one input so not only would it not be big, but it would not be an AND gate at all, just a NOT gate.

Find the simple-model delay of each after optimization. The delays should be \checkmark in terms of wn and wl.

Plan A and Plan C: Delay of OR gate, $\lceil \lg(w_n - w_l) \rceil u_t$. Delay of mux, $1 u_t$. Critical path, shown in red on the diagram, is through both so the critical path delay is $\lceil \lg(w_n - w_l) \rceil + 1 \rceil u_t$.

Plan B: Delay of "big" AND gate, $\lceil \lg(w_n - w_l) \rceil u_t$. Delay of OR gate $\lceil \lg(w_l) \rceil u_t$. Delay of AND gate 1 u_t , delay of mux, 1 u_t . Assuming $w_l > w_n - w_l$ the critical path, shown on red in the diagram, is through the OR gate, little AND gate and mux for a total delay of $\lceil \lg(w_l) \rceil + 1 + 1 \rceil u_t$. Notice that the critical path length is much larger in Plan B under the reasonable assumption that $w_l > w_n - w_l$.

Problem 3: Appearing on the next page is a simplified solution to Homework 3, Problem 2. In this module the number of bits in the connections carrying parentheses counts is hardcoded to 8. Though the hardware is correct for n < 256 it is more costly and slower than it needs to be. But for this problem it's good enough.

Show the Homework 3, Problem 2 hardware that will be inferred for this module for n > 1 (the non-base case). That is, don't show the hardware computing left_out_n_unmat_close and right_out_n_unmat_open.

- Show the inferred hardware at one level for n > 1.
- Feel free to use abbreviations.
- Don't show the Homework 3 Problem 1 hardware (the last always_comb).
- Don't confuse elaboration-time computation with hardware.

Solution appears below. Note that the condition more_op<0 can be evaluated by just looking at the most-significant bit, 7 in this case.

To help understand the circuit try tracing the critical path. To do that consider two cases: the root (the top-level instantiation of pmatch_mark_big) and a lower-level instantiation (but not the base case). In the root assume that left_in_un_open and right_in_un_close are available at t = 0.



```
module pmatch_mark_big #( int n = 5, wn = 8 )
   ( output logic [wn-1:0] left_out_n_unmat_close, right_out_n_unmat_open,
     output uwire [3:0] str_marked [0:n-1],
     input uwire [wn-1:0] left_in_n_unmat_open, right_in_n_unmat_close,
     input uwire [3:0] str [0:n-1] );
   if (n == 1) begin
      assign left_out_n_unmat_close = str[0] == Char_Close;
      assign right_out_n_unmat_open = str[0] == Char_Open;
      assign str_marked[0] =
             str[0] == Char_Close && left_in_n_unmat_open ? Char_Close_Okay :
             str[0] == Char_Open && right_in_n_unmat_close ? Char_Open_Okay : str[0];
   end else begin
      localparam int n_left = n/2, n_right = n - n_left;
      localparam int wl = 8,
                                     wr = 8; // Note: this is wasteful.
      uwire [wl-1:0] lt_close, lt_open;
      uwire [wr-1:0] rt_close, rt_open;
      logic [wl-1:0] lt_matched_op, lt_matched_cl;
      logic [wr-1:0] rt_matched_op, rt_matched_cl;
      pmatch_mark_big #(n_left,wl) plt // Recursive Instantiation
        ( lt_close, lt_open, str_marked[0:n_left-1],
          lt_matched_cl, lt_matched_op, str[0:n_left-1] );
      pmatch_mark_big #(n_right,wr) prt // Recursive Instantiation
        ( rt_close, rt_open, str_marked[n_left:n-1],
          rt_matched_cl, rt_matched_op, str[n_left:n-1] );
      always_comb begin
         logic signed [wn-1:0] more_op, more_cl;
         lt_matched_cl = left_in_n_unmat_open;
         rt_matched_op = right_in_n_unmat_close;
         more_op = left_in_n_unmat_open - lt_close;
         rt_matched_cl = more_op < 0 ? lt_open : more_op + lt_open;</pre>
         more_cl = right_in_n_unmat_close - rt_open;
         lt_matched_op = more_cl < 0 ? rt_close : more_cl + rt_close;</pre>
     end
      always_comb begin
                                 // Same as Homework 3 Problem 1
         logic signed [wn-1:0] delta;
         delta = lt_open - rt_close;
         left_out_n_unmat_close = delta >= 0 ? lt_close : lt_close - delta;
         right_out_n_unmat_open = delta < 0 ? rt_open : rt_open + delta;</pre>
      end
   end
endmodule
```

11 /// LSU EE 4755 Fall 2024 Homework 5 -- SOLUTION 11 /// Assignment https://www.ece.lsu.edu/koppel/v/2024/hw05.pdf `default_nettype none /// Problem1 11 /// Complete dot_seq_2_base. 11 [<] The module can use procedural code.</pre> 11 11 11 [/] Make sure that the testbench does not report errors. 11 [...] Module must be synthesizable. Use command: genus -files syn.tcl 11 11 [/] Don't assume any particular parameter values. 11 11 [<] As always, code must be written clearly.</pre> 11 [...] As always, pay attention to cost and performance. module dot_seq_2 #(int w = 5, wi = 4) (output logic [w-1:0] dp, output logic [wi-1:0] first_id, last_id, input uwire [w-1:0] a[2], b[2], input uwire [wi-1:0] in_id, input uwire reset, first, last, input uwire clk); // [*] Critical path can't include more than one arithmetic operation. // [*] Don't change outputs until operation is complete. /// SOLUTION /// Declare Pipeline Latch Registers 11 // A pipeline latch is an edge-triggered register that carries // values passing from stage to stage. 11 // Index values in the first unpacked dimension indicate the // stage(s) for which a pipeline latch is declared. For example, // pl_a is only declared for stage 1, pl_prod is only declared for // stage 2, but pl id declares three registers, pl id[1] for stage // 1, pl_id[2] for stage 2, and pl_id[3] for stage 3. Note that // pl a[1] is a stage-1 register that holds two w-bit values. A // register declared for stage x is written by hardware in stage // x-1 and read by hardware in stage x. 11

```
\leftarrow \rightarrow Fall 2024
                \leftarrow \rightarrow Homework 5
                                             Homework Sol Code
       logic [w-1:0] pl_a[1:1][2], pl_b[1:1][2]; // Arriving vector elements.
      logic [w-1:0] pl_prod[2:2][2]; // Vector products.
                                                   // Dot prod of 2-element segment.
      logic [w-1:0] pl_sum[3:3];
       logic [wi-1:0] pl_id[1:3];
                                                   // ID.
       logic [1:0] pl_fl[1:3];
                                                    // The first and last signals.
       //
       // Note that ID, first, and last, move through the pipeline
       // unchanged, which is why there is a pipeline latch in each stage
       // to carry their values. In contrast, vector elements (arriving in
       // a and b) are transformed in each stage and so the names of the
       // pipeline latches carrying their values and values computed from
       // them change at each stage: a/b -> prod -> sum.
       /// Declare Accumulator Registers
       11
       // An accumulator holds values that don't move with the pipeline.
       // Here the accumulators are updated by values from stage 3.
       11
       logic [wi-1:0] acc_id;
       logic [w-1:0] acc_sum;
       always_ff @( posedge clk ) begin
          /// Stage 0
          11
          // Move arriving inputs into pipeline latches. Since the problem
          // states inputs arrive late in the cycle it is not possible to
          // do any calculations using their values until the next cycle.
          11
          pl_a[1] <= a; // This copies both elements of a.</pre>
          pl_b[1] <= b;
          pl_id[1] <= in_id;</pre>
          pl_fl[1] <= reset ? 2'b0 : {last,first};</pre>
          /// Stage1
          //
          // Compute products ..
          11
          for ( int i=0; i<2; i++ ) pl_prod[2][i] <= pl_a[1][i] * pl_b[1][i];</pre>
          11
          // .. and move everyone else along unchanged (except for reset).
          11
          pl_id[2] <= pl_id[1];</pre>
          pl_fl[2] <= reset ? 2'd0 : pl_fl[1];</pre>
          /// Stage 2
          //
          // Compute sum ..
          11
          pl_sum[3] <= pl_prod[2][0] + pl_prod[2][1];</pre>
          11
          // .. and move everyone else along unchanged (except for reset).
          11
          pl_id[3] <= pl_id[2];</pre>
```

hw05-sol.v.html

```
\leftarrow \rightarrow Fall 2024
                  \leftarrow \rightarrow Homework 5
                                              Homework Sol Code
          pl_f1[3] <= reset ? 2'h0 : pl_f1[2];</pre>
          /// Stage 3
          11
          begin
             // Declare intermediate values in this block.
             11
             automatic logic s3_first = pl_fl[3][0]; // For readability.
             automatic logic s3_last = pl_fl[3][1]; // For readability.
             // Add arriving value on to accumulated sum, unless this
             // is the first set of vector elements.
             11
             automatic logic [w-1:0] s3_sum =
               s3_first ? pl_sum[3] : pl_sum[3] + acc_sum;
             11
             // Write the sum to the accumulator register.
             //
             acc_sum <= s3_sum;</pre>
             11
             // Note that there is no need to check reset or last because
             // if they were true the value written to acc_sum would not
             // be used and so there is no need to waste hardware that
             // would avoid writing it.
             if ( reset ) begin
                // Set output IDs to zero on a reset.
                11
                first_id <= 0;</pre>
                last_id <= 0;</pre>
                11
                // Since the problem does not say to set dp to zero there
                // is no need to waste hardware doing so.
             end else begin
                // Hold on to the ID if this is the beginning of the
                // vector.
                11
                if ( s3_first ) acc_id <= pl_id[3];</pre>
                11
                // A beginner's mistake is to use the value of first
                // currently at the module inputs rather than the value
                // in pipeline latch pl_fs[3].
                if ( s3_last ) begin
                    // If this is the end of the vector, update the module
                    // outputs.
                    11
                    first_id <= s3_first ? pl_id[3] : acc_id;</pre>
                    last_id <= pl_id[3];</pre>
                    dp <= s3_sum;</pre>
```

```
end
end
end
```

```
end
```

endmodule

```
`ifdef xxxx
<u>Synthesizing</u> at effort level "high"
```

<u>Module</u> Name	Area	Delay	Delay		Synth	
		<u>Actual</u>	Target		Time	
dot_seq_2_w8_wi8	148802	3.58	900.0	ns	8	s
dot_seq_2_w8_wi8_17	<mark>219</mark> 405	2.02	0.1	ns	43	s
`endif						


```
/// Testbench Code
```

```
//
```

// It is okay to modify the testbench code to facilitate the coding // and debugging of your modules. Keep in mind that your submission // will be tested using a different testbench, so on the one hand no // one will be accused of dishonesty for modifying the testbench // below. However be sure to restore any changes to make sure that // your code passes the original testbench.

```
// cadence translate_off
```

```
program reactivate
```

```
(output uwire clk_reactive, output int cycle_reactive,
    input uwire clk, input var int cycle);
    assign clk_reactive = clk;
    assign cycle_reactive = cycle;
endprogram
```

```
module dot_seq_m
#( int n = 1, w = 5, wi = 4 )
  ( output logic [w-1:0] dp,
    output logic [wi-1:0] first_id, last_id,
    input uwire [w-1:0] a[n], b[n],
    input uwire [wi-1:0] in_id,
    input uwire reset, first, last,
    input uwire clk );

if ( n == 1 ) begin
    dot_seq #(w,wi) d(dp,first_id,last_id,a[0],b[0],in_id,reset,first,last,clk);
```

end else if (n == 2) begin

```
dot_seq_2 #(w,wi) d(dp,first_id,last_id,a,b,in_id,reset,first,last,clk);
   end
endmodule
module testbench;
   logic done;
   localparam int m = 2;
   localparam int n_tests = 10000;
   localparam int wi = 8;
   localparam int w = 8;
   // Maximum number of cycles from "last" signal to arrival of outputs.
   localparam int latency max = 5;
   // Minimum latency that will be considered correct.
   localparam int latency_min = 2 + <u>$clog2(m);</u>
   localparam int cyc_max = n_tests * 1000;
   int seed;
   initial seed = 475501;
   function automatic bit rand_bern( int period );
      rand_bern = <u>$dist uniform(seed,1,period) == 1;</u>
   endfunction
   bit clk;
   int cycle, cycle_limit;
   logic clk_reactive;
   int cycle_reactive;
   reactivate ra(clk_reactive,cycle_reactive,clk,cycle);
   string event_trace;
   string ev_trace[$];
   initial begin
      clk = 0;
      cycle = 0;
      event_trace = "";
      done = 0;
      cycle_limit = cyc_max;
      // wait( tstart );
      fork
         while ( !done ) #1 cycle += clk++;
         wait( cycle >= cycle_limit )
           <u>$write</u>("Exit from clock loop at cycle %0d, limit %0d. %s\n %s\n",
                  cycle, cycle_limit, "** CYCLE LIMIT EXCEEDED **",
                  event_trace);
      join_any;
```

```
done = 1;
end
typedef struct
  £
  logic [w-1:0] dp;
   logic [wi-1:0] first_id, last_id;
   int cyc; // Cycle that last input asserted.
   int latency; // Number of cycles from last to dp to appearing at output.
   bit correct;
   } Info;
uwire [w-1:0] dp;
uwire [wi-1:0] out_first_id, out_last_id;
logic [w-1:0] a[m], b[m];
logic [wi-1:0] in_id;
logic reset, first, last;
bit done_tests, start_check;
dot seq m #(m,w,wi)
ds(dp,out_first_id,out_last_id,a,b,in_id,reset,first,last,clk);
enum { S_reset, S_gap, S_continue } State;
Info exp_info[$];
int n_tests_completed;
Info info_null;
initial begin
   automatic int state = S_reset;
   logic [w-1:0] shadow_sum;
   logic [wi-1:0] shadow_id;
   n_tests_completed = 0;
   info_null.first_id = 0;
   info_null.last_id = 0;
   info_null.dp = 0;
   info_null.cyc = cycle;
   info_null.correct = 0;
   exp_info.push_back(info_null);
   start_check = 0;
   done_tests = 0;
   first = 0;
   last = 0;
   for ( int j=0; j<m; j++ ) begin a[j]=0; b[j]=0; end</pre>
   in_id = <u>$dist uniform</u>(seed,1,(1<<wi)-1);</pre>
   reset = 1;
   @( negedge clk ); @( negedge clk );
   start_check = 1;
   while ( n_tests_completed < n_tests ) begin</pre>
```

```
string tr_entry;
first = 0;
last = 0;
reset = 0;
for ( int j=0; j<m; j++ ) begin</pre>
   if ( n_tests_completed < 20 ) begin
      a[j] = 1;
                          b[j] = 1 << ( j * 4 );
   end else begin
      a[j] = {<u>$random</u>}; b[j]= {<u>$random</u>};
   end
end
// For error detection recent input IDs must be distinct.
in_id += $dist uniform(seed,1,3);
if ( in_id == 0 ) in_id = 1;
if ( state == S_reset ) state = S_gap;
if ( rand_bern(100) ) begin
   reset = 1;
   in_id = <u>$dist uniform</u>(seed,1,(1<<wi)-1);</pre>
   exp info.delete();
   info_null.cyc = cycle;
   exp_info.push_back(info_null);
   state = S_reset;
end
if ( state == S_gap ) begin
   first = rand_bern(3);
   if (first) begin
      state = S_continue;
      shadow_sum = 0;
      shadow_id = in_id;
   end
end
for ( int j=0; j<m; j++ )</pre>
  shadow_sum += a[j] * b[j];
if ( state == S_continue ) begin
   last = rand_bern(4);
   if (last) begin
      <u>Info</u> info;
      state = S_gap;
      n_tests_completed++;
      info.dp = shadow_sum;
      info.first_id = shadow_id;
      info.last_id = in_id;
      info.cyc = cycle;
      info.correct = 0;
      exp_info.push_back(info);
   end
end
```

```
if ( exp_info.size() > 1 && exp_info[1].cyc + latency_max < cycle )</pre>
        void'(exp_info.pop_front());
      @( negedge clk );
   end
   first = 0;
   last = 0;
   done_tests = 1;
   $write("Done with inputs.\n");
   begin
      automatic int cyc_limit = cycle + 20;
      wait ( cycle == cyc_limit );
      done = 1;
   end
end
initial begin
   automatic int sum_latency = 0;
   automatic int n_correct = 0;
   automatic int n_err_fid = 0;
   automatic int n_err_lid = 0;
   automatic int n_err_sum = 0;
   automatic int n_err_time = 0;
   automatic int n_err_early = 0;
   automatic int err_fid_cyc = 0;
   automatic int err_lid_cyc = 0;
   automatic int err_dp_cyc = 0;
   string tr_entry;
   #0;
   wait( start_check );
   while ( !done ) begin
      Info info, info_dp;
      automatic string err_text[$];
      string tr_entry;
      int fid_idx, lid_idx, dp_idx, age;
      bit err_time, err_fid, err_lid, err_early;
      @( posedge clk_reactive );
      if ( done ) break;
      fid_idx = -1; lid_idx = -1; dp_idx = -1;
```

```
\leftarrow \rightarrow Fall 2024
                  \leftarrow \rightarrow Homework 5
                                              Homework Sol Code
             info_dp = info_null; age = -1;
             err_early = 0;
             for ( int i=0; i<exp_info.size(); i++ ) begin</pre>
                 automatic Info info = exp info[i];
                 automatic int bi = exp_info.size() -1 -i;
                automatic int nm = 0;
                if ( info.first_id === out_first_id ) begin fid_idx = bi; nm++; end
                 if ( info.last_id === out_last_id ) begin lid_idx = bi; nm++; end
                 if ( info.dp === dp ||
                      info.first_id == 0 && out_first_id === 0 &&
                      info.last_id == 0 && out_last_id === 0 )
                   begin
                      dp idx = bi; nm++;
                      if ( !info.correct && info.first_id ) begin
                         automatic int latency = cycle - info.cyc;
                         exp_info[i].correct = 1;
                         exp_info[i].latency = latency;
                         sum_latency += latency;
                         err_early = latency < 3;</pre>
                         n_correct++;
                      end
                      info_dp = exp_info[i];
```

```
end
info = exp_info[$];
if ( dp_idx >= 0 ) age = cycle - info_dp.cyc;
err_fid = fid_idx == -1 || dp_idx >= 0 && fid_idx != dp_idx;
err_lid = lid_idx == -1 || dp_idx >= 0 && lid_idx != dp_idx;
if ( err_fid && info.cyc != err_fid_cyc ) begin
   n_err_fid++;
   err_fid_cyc = info.cyc;
   if (n_{err_fid} < 4)
     err_text.push_back
       ( <u>$sformatf</u>("Error first ID: %0h != %0h (correct)\n",
                  out_first_id, info_dp.first_id ) );
end
if ( err_lid && info.cyc != err_lid_cyc ) begin
   n_err_lid++;
   err_lid_cyc = info.cyc;
   if ( n_err_lid < 4 )</pre>
     err_text.push_back
       ( <u>$sformatf</u>("Error last ID: %0h != %0h (correct)\n",
                  out_last_id, info_dp.last_id ) );
end
```

```
if ( err_early ) begin
   n_err_early++;
   if ( n_err_early < 4 )</pre>
```

end

if (nm == 3) break;

```
\leftarrow \rightarrow Fall 2024
                  \leftarrow \rightarrow Homework 5
                                              Homework Sol Code
                                                                                            hw05-sol.v.html
                   err_text.push_back
                     ( <u>$sformatf</u>("Error dp timing: latency %Od cyc < 3 cyc (minimum)\n",</pre>
                                  info_dp.latency) );
             end
             if ( dp_idx == -1 && info.cyc != err_dp_cyc ) begin
                n_err_sum++;
                err_dp_cyc = info.cyc;
                if (n_err_sum < 4)
                   err_text.push_back
                   ( <u>$sformatf</u>("Error dp: %h != %h (correct)\n", dp, info.dp ) );
             end
             err_time = 0 && fid_idx >= 0 && lid_idx >= 0 && dp_idx >= 0
               && ( fid_idx != lid_idx || lid_idx != dp_idx );
             if ( err_time ) begin
                n_err_time++;
                if ( n_err_time < 4 )</pre>
                   err_text.push_back
                   (<u>$sformatf</u>("Error timing: %0d %0d (should all be same)\n",
                          fid_idx, lid_idx, dp_idx) );
             end
             begin
                 automatic string a_str, b_str;
                for ( int j=0; j<m; j++ ) begin</pre>
                    a_str = { a_str, j?",":"", <u>$sformatf("%h",a[j]) };</u>
                    b_str = { b_str, j?", ":"", <u>$sformatf("%h",b[j]) };</u>
                 end
             tr entry =
               { <u>$sformatf</u>("%4d %s%s%s ID %h A %s B %s",
                             cycle,
                             reset ? "R" : "_",
                             first ? "F" : "_"
                            last ? "L" : "_"
                             in_id, a_str, b_str ),
                  " ",
                  $sformatf("exp: fid %h lid %h dp %h",
                             exp_info[$].first_id, exp_info[$].last_id,
                             exp_info[$].dp),
                  ",
                  $sformatf("MOD: %s %h %s %h %s %h",
                             err_fid ? "ERR" : err_time ? "err" : "FID",
                             out_first_id,
                             err_lid ? "ERR" : err_time ? "err" : "LID",
                             out_last_id,
                             dp idx == -1 ? "ER" : age < 3 ? "EY" : err time ? "er" : "DP",
                            dp )
                  };
             end
             ev_trace.push_back(tr_entry);
```

```
\leftarrow \rightarrow Fall 2024
                 \leftarrow \rightarrow Homework 5
                                              Homework Sol Code
                                                                                           hw05-sol.v.html
             while ( ev_trace.size() > 10 ) tr_entry = ev_trace.pop_front();
             if ( err_text.size() || cycle < 20 ) begin</pre>
                while ( ev_trace.size() ) <u>$write("%s\n",ev_trace.pop_front());</u>
                 // foreach ( ev_trace[i] ) $write("%s\n",ev_trace[i]);
                 foreach ( err_text[i] ) <u>$write("%s",err_text[i]);</u>
             end
          end
          begin
             automatic real avg_latency =
               n_correct ? sum_latency / real'(n_correct) : 0;
             $write("Done with %0d tests. %0d dp errs ( %0d correct )\n",
                     n_tests_completed, n_err_sum, n_correct);
             // $write("Done with %Od tests. %Od ID errs, %Od FID errs, %Od LID errs.\n",
             $write("Done with %0d tests. %0d FID errs, %0d LID errs.\n",
                     n_tests_completed, n_err_fid, n_err_lid);
             <u>$write</u>("Done with %0d tests. Correct %0d, avg latency %.1f cyc %0s\n",
                     n_tests_completed, n_correct, avg_latency,
                     avg_latency < latency_min ?</pre>
                     $sformatf("Error, too low, %0d cyc minimum.",latency_min) : "Okay");
```

end

end

endmodule

// cadence translate_on

LSU EE 4755

Homework 6 Solution

Due: 1 Dec 2024

Student Expectations

To solve this assignment students are expected to avail themselves of references provided in class and on the Web site, such as for Verilog programming and synthesis examples, and to seek out any additional help and resources that might be needed. (Of course this doesn't mean asking someone else to solve it for you.) It is each student's duty to himself or herself to resolve frustrations and roadblocks quickly. (If you get stuck *just ask for help!*)

This assignment cannot be solved by blindly pasting together parts of past assignments. Solving the assignment is a multi-step learning process that takes effort, but one that also provides the satisfaction of progress and of developing skills and understanding.

Collaboration Rules

Each student is expected to complete his or her own assignment. It is okay to work with other students and to ask questions in order to get ideas on how to solve the problems or how to overcome some obstacle (be it a question of Verilog syntax, interpreting error messages, how a part of the problem might be solved, etc.) It is also acceptable to seek out digital design resources for help on Verilog, digital design, etc. It is okay to make use of AI LLM tools such as ChatGPT and Copilot to generate sample Verilog code. (Do not assume LLM output is correct. Treat LLM output the same way one might treat legal advice given by a lawyer character in a movie: it may sound impressive, but it can range from sage advice to utter nonsense.)

After availing oneself to these resources each student is expected to be able to complete the assignment alone. Test questions will be based on homework questions and the assumed time needed to complete the question will be for a student who had solved the homework assignment on which it was based.

Problems start on next page.

Problem 1: Show the hardware that will be synthesized for the posted solution to Homework 5. The solution (with fewer comments than the posted version) is shown below.

Solution appears on the page after the module.

```
module dot_seq_2 #( int w = 5, wi = 4 )
   ( output logic [w-1:0] dp, output logic [wi-1:0] first_id, last_id,
     input uwire [w-1:0] a[2], b[2], input uwire [wi-1:0] in_id,
     input uwire reset, first, last, input uwire clk );
   logic [w-1:0] pl_a[1:1][2], pl_b[1:1][2]; // Arriving vector elements.
                                        // Vector products.
   logic [w-1:0] pl_prod[2:2][2];
                                               // Dot prod of 2-element segment.
   logic [w-1:0] pl_sum[3:3];
   logic [wi-1:0] pl_id[1:3];
                                               // ID.
   logic [1:0] pl_fl[1:3];
                                              // The first and last signals.
   logic [wi-1:0] acc_id;
   logic [w-1:0] acc_sum;
   always_ff @( posedge clk ) begin
      /// Stage 0
      pl_a[1] <= a; // This copies both elements of a.</pre>
      pl_b[1] <= b;
      pl_id[1] <= in_id;</pre>
      pl_fl[1] <= reset ? 2'b0 : {last,first};</pre>
      /// Stage 1
      for ( int i=0; i<2; i++ ) pl_prod[2][i] <= pl_a[1][i] * pl_b[1][i];</pre>
      pl_id[2] <= pl_id[1];</pre>
      pl_f1[2] <= reset ? 2'd0 : pl_f1[1];</pre>
      /// Stage 2
      pl_sum[3] <= pl_prod[2][0] + pl_prod[2][1];</pre>
      pl_id[3] <= pl_id[2];</pre>
      pl_f1[3] <= reset ? 2'h0 : pl_f1[2];</pre>
      /// Stage 3
      begin
         automatic logic s3_first = pl_f1[3][0]; // For readability.
         automatic logic s3_last = pl_fl[3][1]; // For readability.
         automatic logic [w-1:0] s3_sum = s3_first ? pl_sum[3] : pl_sum[3] + acc_sum;
         acc_sum <= s3_sum;</pre>
         if (reset ) begin
            first_id <= 0;</pre>
            last_id <= 0;</pre>
         end else begin
            if ( s3_first ) acc_id <= pl_id[3];</pre>
            if ( s3_last ) begin
               first_id <= s3_first ? pl_id[3] : acc_id;</pre>
               last_id <= pl_id[3];</pre>
               dp <= s3_sum;
            end
         end
      end
   end
endmodule
```

Solution to Problem 1 appears below.



Problem 2: Solve 2023 Final Exam Problem 2, which asks for a cost and delay analysis of a word count module.

See the posted final exam solution.
15 Fall 2023 Solutions

```
11
/// LSU EE 4755 Fall 2023 Homework 1 -- SOLUTION
11
 /// Assignment https://www.ece.lsu.edu/koppel/v/2023/hw01.pdf
`default_nettype none
/// Problem 1
11
 /// Complete minmax2p1 using a compare_It and mux2 instantiations.
///
11
      [.] Only modify minmax2p1. Use minmax2 for reference.
11
11
11
      [/] minmax2p1 must instantiate a compare_lt module and mux2 modules.
11
      [*] minmax2p1 must NOT use assign statements or procedural code.
11
      [~] Make sure that the testbench does not report errors.
11
11
      [ / ] Module must be synthesizable. Use command: genus -files syn.tcl
11
      [/] Don't assume any particular parameter values.
11
11
      [.] Code must be written clearly.
11
module minmax2p1
 #(int w = 4)
   ( output uwire [w-1:0] min, max,
    input uwire [w-1:0] a0, a1 );
  // Put solution here.
  /// SOLUTION
  uwire lt;
  compare lt #(w) clt(lt, a0, a1);
  mux2 #(w) mn(max,lt,a0,a1);
  mux2 #(w) mx(min,lt,a1,a0);
endmodule
module compare_lt
 #(int w = 31)
   ( output uwire lt,
    input uwire [w-1:0] a0, a1 );
  // DO NOT modify this module.
  // Set lt to 0 if a1 < a0, set lt to 1 otherwise.</pre>
  11
```

```
assign lt = a0 <= a1;
```

```
endmodule
```

```
module mux2
#( int w = 3 )
  ( output uwire [w-1:0] x,
    input uwire s,
    input uwire [w-1:0] a0, a1 );

// D0 NOT modify this module either.
  assign x = s ? a1 : a0;
endmodule
module minmax2
#( int w = 10 )
  ( output uwire [w-1:0] min, max,
    input uwire [w-1:0] a0, a1 );

// D0 NOT modify this module either.
```

```
// Assign min to the smaller of a0 and a1, and max to the larger.
assign { min, max } = a0 <= a1 ? { a0, a1 } : { a1, a0 };
```

Homework Sol Code

```
/// Problem 2
11
 /// Complete minmax4 and minmax8.
11
11
      [.] In minmax4, instantiate minmax2.
11
      [.] In minmax8, instantiate minmax4.
      [ ] In minmax4 and minmax8, instantiate min2 and max2, as necessary.
11
11
11
      [ ] Do not use assign statements or procedural code.
11
11
      [...] Make sure that the testbench does not report errors.
      [...] Module must be synthesizable. Use command: genus -files syn.tcl
11
11
11
      [ ] Don't assume any particular parameter values.
11
11
      [ / ] Pay attention to cost.
      [...] Assume cost of min2 + max2 in more than minmax2.
11
      [.] Code must be written clearly.
11
module minmax4
```

```
#( int w = 20 )
  ( output uwire [w-1:0] min, max,
     input uwire [w-1:0] a[4] );
```

```
// Put solution here.
```

```
/// SOLUTION
```

uwire [w-1:0] lomin, lomax, himin, himax; minmax2 #(w) mlo(lomin, lomax, a[0], a[1]); minmax2 #(w) mhi(himin, himax, a[2], a[3]); min2 #(w) m1(min, lomin, himin); max2 #(w) m2(max, lomax, himax);

```
module minmax8
  #(int w = 12)
   ( output uwire [w-1:0] min, max,
     input uwire [w-1:0] a[8] );
   // Put solution here.
   /// SOLUTION
   uwire [w-1:0] lomin, lomax, himin, himax;
   minmax4 #(w) mlo( lomin, lomax, a[0:3] );
   minmax4 #(w) mhi( himin, himax, a[4:7] );
   min2 #(w) m1( min, lomin, himin );
   max2 #(w) m2( max, lomax, himax );
endmodule
module min2
  #(int w = 10)
   ( output uwire [w-1:0] min,
     input uwire [w-1:0] a0, a1 );
   assign min = a0 < a1 ? a0 : a1;</pre>
```

```
endmodule
```

```
module max2
  #( int w = 10 )
   ( output uwire [w-1:0] max,
        input uwire [w-1:0] a0, a1 );
   assign max = a0 < a1 ? a1 : a0;
endmodule</pre>
```

// cadence translate_off

module testbench;

```
int t_errs; // Total number of errors.
initial begin t_errs = 0; end
final <u>$write</u>("Total number of errors: %0d\n",t_errs);
```

```
uwire d[npsets:-1]; // Start / Done signals.
assign d[-1] = 1; // Initialize first at true.
```

```
// Instantiate a testbench at each size.
//
for ( genvar i=0; i<npsets; i++ )
   testbench_n #(pset[i]) t2( .done(d[i]), .tstart(d[i-1]) );</pre>
```

```
module testbench_n
  #(int n = 5)
   ( output logic done, input uwire tstart );
   localparam int w = 13;
   localparam int ntests = 100;
   logic [w-1:0] a[n], sa[n];
   uwire [w-1:0] min, max;
   if (n == 2)
     minmax2p1 #(w) mm( min, max, a[0], a[1] );
   else if (n == 4)
     minmax4 #(w) mm( min, max, a );
   else if (n == 8)
     minmax8 #(w) mm( min, max, a );
   int n_err_min, n_err_max;
   initial begin
      done = 0;
      wait( tstart );
      n_{err_min} = 0;
      n_err_max = 0;
      for ( int i=0; i<ntests; i++ ) begin</pre>
         logic [w-1:0] shadow_min, shadow_max;
```

```
for ( int i=0; i<n; i++ ) a[i] = {<u>$random</u>};
   sa = a; sa.sort();
   shadow_min = sa[0];
   shadow_max = sa[n-1];
   #1;
   if ( min !== shadow_min ) begin
      n_err_min++;
      if (n_{err} - min < 5)
        $write("Error n=%0d min %d != %d (correct)\n",
                 n, min, shadow_min);
   end
   if ( max !== shadow_max ) begin
      n_err_max++;
      if (n_err_max < 5)
        $write("Error n=%0d max %d != %d (correct)\n",
                 n, max, shadow_max);
   end
end
testbench.t_errs += n_err_min + n_err_max;
done = 1;
$write("Done with n=%0d, tests, %0d min %0d max errors found.\n",
         n, n_err_min, n_err_max );
```

end endmodule

// cadence translate_on

11 /// LSU EE 4755 Fall 2023 Homework 2 -- SOLUTION 11 /// Assignment https://www.ece.lsu.edu/koppel/v/2023/hw02.pdf *`default nettupe* none /// Problem 1 11 /// Complete comp_p1 so that it computes (1-b/c)/a. See writeup. /// 11 11 [/] Perform computation in order given by expression (1-b/c)/a. [.] Only modify comp_p1. 11 11 11 [/] Use Chipware modules for floating point arithmetic and conversions. 11 [...] Do not perform FP arithmetic with procedural code. 11 11 [...] Make sure that the testbench does not report errors. [/] Module must be synthesizable. Use command: genus -files syn.tcl 11 11 [<] Don't assume any particular parameter values.</pre> 11 11 [/] Pay attention to cost. Don't grossly oversize things. 11 [<] Code must be written clearly.</pre> 11 module fp_one #(int w_exp=5, w_sig=9, w_fp=1+w_exp+w_sig)(output uwire [w_fp-1:0] one); // Output is the constant 1. This module is synthesizable. assign one = { 1'b0, $(w_exp)'((1 << w_exp-1) - 1)$, $(w_sig)'(0)$ }; endmodule typedef enum logic [2:0] { Rnd_to_even = 0, Rnd_to_0 = 1, Rnd_to_plus_if = 2, Rnd to minus inf = 3, Rnd to plus inf = 4, Rnd from 0 = 5 } Rnd; module comp_p1 #(int w = 5, w_exp = 5, w_sig = 5, wfp = 1 + w_exp + w_sig) (output uwire [wfp-1:0] h, input uwire [w-1:0] a, b, c); localparam Rnd rnd = Rnd_to_even; uwire logic [wfp-1:0] one; fp one #(w_exp,w_sig) o(one); /// SOLUTION uwire logic [wfp-1:0] One; fp one #(w_exp,w_sig) 0(One);

```
\leftarrow \rightarrow Fall 2023
                   \leftarrow \rightarrow Homework 2
                                                 Homework Sol Code
       uwire [wfp-1:0] af, bf, cf, boc, numer;
       uwire [7:0] sa, sb, sc, sboc, snumer, sh;
       // Convert inputs to floating-point.
       //
       <u>CW fp i2flt</u> #( .sig_width(w_sig), .exp_width(w_exp), .isize(w), .isign(0) )
       coa( .z(af), .a(a), .rnd(rnd), .status(sa) );
       <u>CW fp i2flt</u> #( .sig_width(w_sig), .exp_width(w_exp), .isize(w), .isign(0) )
       cob( .z(bf), .a(b), .rnd(rnd), .status(sb) );
       <u>CW fp i2flt \#(.sig_width(w_sig), .exp_width(w_exp), .isize(w), .isign(0)</u>)
       coc( .z(cf), .a(c), .rnd(rnd), .status(sc) );
       // Compute (1-b/c)/a
       11
       <u>CW fp div</u> #( .sig_width(w_sig), .exp_width(w_exp) )
                                            .status(sboc), .rnd(rnd) );
       d1( .z(boc), .a(bf), .b(cf),
       CW_fp_sub #( .sig_width(w_sig), .exp_width(w_exp) )
       d2( .z(numer), .a(One), .b(boc), .status(snumer), .rnd(rnd) );
       CW fp div #( .sig_width(w_sig), .exp_width(w_exp) )
       d3( .z(h), .a(numer), .b(af), .status(sh), .rnd(rnd) );
```

endmodule


```
/// Complete comp_p2 so that it computes (1-b/c)/a efficiently. See writeup.
///
11
11
       [ ] Transform (1-b/c)/a for computation efficiency; implement that.
11
       [.] Only modify comp_p2.
11
       [/] Use Chipware modules for floating point arithmetic and conversions.
11
11
       [~] Do not perform FP arithmetic with procedural code.
11
       [~] Make sure that the testbench does not report errors.
11
       [/] Module must be synthesizable. Use command: genus -files syn.tcl
11
11
       [...] Don't assume any particular parameter values.
11
11
11
       [...] Pay attention to cost. Don't grossly oversize things.
       [...] Pay attention to performance (delay).
11
11
       [✓] Code must be written clearly.
```

```
module comp_p2
    #( int w = 5, w_exp = 5, w_sig = 5, wfp = 1 + w_exp + w_sig )
    ( output uwire [wfp-1:0] h,
        input uwire [w-1:0] a, b, c );
    localparam logic [2:0] rnd = Rnd_to_0;
```

```
/// SOLUTION
//
// Summary:
//
```

```
\leftarrow \rightarrow Fall 2023
                  \leftarrow \rightarrow Homework 2
                                               Homework Sol Code
       // - Transform (1-b/c)/a into (c - b) / (ac).
       11
       // - Use integer arithmetic for c - b and for ac.
       11
             Take care to use enough bits in each expression.
       //
       // - Convert c-b and ac to floating point.
       11
       // - Compute (c-b)/ac with one extra bit of precision.
       // Perform integer computations.
       // Note: Width (bits) of integer product is sum of width of operands.
       11
       localparam int wac = 2 * w;
       11
       uwire [wac-1:0] ac = a * c;
       // Use an extra bit for difference because result can be negative.
       11
       uwire [w:0] cmb = c - b;
       // Use one extra bit of precision when doing division.
       11
       localparam int w_Sig = w_sig + 1;
       localparam int wFp = 1 + w_exp + w_Sig;
       uwire [wFp-1:0] acf, cmbf, H;
       uwire [7:0] sa, sb, sboc;
       // Convert to floating point.
       11
       CW fp i2flt #( .sig_width(w_Sig), .exp_width(w_exp), .isize(wac), .isign(0) )
       coa( .z(acf), .a(ac), .rnd(rnd), .status(sa) );
       CW_fp_i2flt #( .sig_width(w_Sig), .exp_width(w_exp), .isize(w+1), .isign(1) )
       cob( .z(cmbf), .a(cmb), .rnd(rnd), .status(sb) );
       // Compute quotient.
       11
       <u>CW fp div</u> #( .sig_width(w_Sig), .exp_width(w_exp) )
       di1( .z(H), .a(cmbf), .b(acf), .status(sboc), .rnd(rnd) );
       // Remove the extra bit.
       11
       assign h = H[wFp-1:wFp-wfp];
```

hw02-sol.v.html

endmodule

// cadence translate_off

```
\leftarrow \rightarrow Fall 2023
                  \leftarrow \rightarrow Homework 2
                                                Homework Sol Code
          return {$random()} & ( ( 1 << wid ) - 1 );</pre>
    endfunction
   function automatic real fabs(real val);
          fabs = val < 0 ? -val : val;
   endfunction
   function int min( int a, b );
          min = a \le b ? a : b;
   endfunction
    function int max( int a, b );
          max = a >= b ? a : b;
    endfunction
   virtual class CONV #(int wexp=6, wsig=10);
       // Convert between real and fp types using parameter-provided
       // exponent and significand sizes.
       localparam int w = 1 + wexp + wsig;
       localparam int bias_r = (1 \ll 11 - 1) - 1;
       localparam int w_sig_r = 52;
       localparam int w_exp_r = 11;
       localparam int bias_h = ( 1 << wexp - 1 ) - 1;</pre>
       static function logic [w-1:0] rtof( real r );
          logic [wsig-1:0] sig_f;
          logic [w_sig_r-wsig-2:0] sig_x;
          logic sig_x_msb;
          logic [w_exp_r-1:0] exp_r;
          logic sign_r;
          { sign_r, exp_r, sig_f, sig_x_msb, sig_x } = <u>$realtobits(r);</u>
          // So, what about a rounding mode? Not now!
          rtof = !r ? 0 : { sign_r, wexp'( exp_r + bias_h - bias_r ), sig_f };
       endfunction
       static function real ftor( logic [w-1:0] f );
          ftor = !f ? 0.0
            : $bitstoreal
              ( { f[w-1],
                  w_exp_r'( bias_r + f[w-2:wsig] - bias_h ),
                  f[wsig-1:0], (w sig r-wsig)'(0) } );
       endfunction
       static function int err_bits( logic [w-1:0] a, b );
          logic [wsig-1:0] sig_a, sig_b;
          logic [wsig+2:0] frac_a, frac_b, frac_diff;
          logic [wexp-1:0] exp_a, exp_b;
          logic s_a, s_b;
          int delta_e;
          if ( <u>$isunknown(a) || $isunknown(b)</u> ) return 1 << wexp;</pre>
          if ( a == b ) return 0;
          { s_a, exp_a, sig_a } = a;
          { s_b, exp_b, sig_b } = b;
```

```
if ( exp_a == 0 || exp_b == 0 ) begin
         logic [wsig-1:0] sig = ~ ( sig_a | sig_b );
         return 1 + wsig - <u>$clog2( sig + 1 );</u>
      end
      delta_e = \frac{\text{sabs}}{0} + exp_a - exp_b );
      if ( delta_e > 1 ) return delta_e + wsig;
      frac_a = exp_a > exp_b ? { 2'b1, sig_a, 1'b0 } : { 3'b1, sig_a };
      frac_b = exp_b > exp_a ? \{ 2'b1, sig_b, 1'b0 \} : \{ 3'b1, sig_b \};
      frac_diff =
        s_a != s_b ? frac_a + frac_b :
        frac_a > frac_b ? frac_a - frac_b : frac_b - frac_a;
      return <u>$clog2( frac_diff + 1 );</u>
   endfunction
endclass
// cadence translate_on
// cadence translate_off
// Module names. (Used by the testbench.)
11
typedef enum { M_p1, M_p2 } M_Type;
module testbench;
   localparam int n_tests = 10000;
   localparam int npsets = 5; // This MUST be set to the size of pset.
   // { w_exp, w_sig, w_int }
   localparam int pset[npsets][3] =
               ١Ş
                {7, 6, 4},
                {7, 8, 4},
                \{8, 10, 5\},\
                \{ 8, 10, 10 \},\
                { 8, 12, 10 }
                };
   localparam int nmsets = 2;
   localparam M_Type mset[nmsets] = '{ M_p1, M_p2 };
   string mtype_str[M_Type] = '{ M_p1: "comp_p1", M_p2: "comp_p2" };
   string mtype_abbr[M_Type] = '{ M_p1: "p1", M_p2: "p2" };
   int t_errs_mod[M_Type];
   int t_errs_size[int];
   int t_errs_each[M_Type][int];
   int t_mub_each[M_Type][int];
   real t_aub_each[M_Type][int];
   localparam int nsets = npsets * nmsets;
   logic d[nsets:-1]; // Start / Done signals.
```

```
// Total number of errors.
   int t_errs;
   initial begin
      t_{errs} = 0;
      for ( int m=0; m<nmsets; m++ )</pre>
        for ( int i=0; i<npsets; i++ ) begin</pre>
           t_errs_each[mset[m]][i] = -1;
           t_mub_each[mset[m]][i] = -1;
            t_aub_each[mset[m]][i] = -1;
        end
      d[-1] = 1;
   end
   final begin
      $write("\nNumber of tests: %0d.\n", n_tests);
      for ( int i=0; i<npsets; i++ )</pre>
        $write("Total for exp=%2d, sig=%2d, w=%2d: %5d errors.\n",
                pset[i][0], pset[i][1], pset[i][2],
                t errs size[i]);
      for ( int i=0; i<nmsets; i++ )</pre>
        $write("Total for mod %4s: %5d errors.\n",
                mtype_str[mset[i]], t_errs_mod[mset[i]]);
      for ( int m=0; m<nmsets; m++ )</pre>
        for ( int i=0; i<npsets; i++ )</pre>
          <u>$write("Total %4s exp=%2d, sig=%2d, w=%2d: %5d errors. Err bits: avg %6.2f, max %3d\n",</u>
                  mtype str[mset[m]],
                  pset[i][0], pset[i][1], pset[i][2],
                  t_errs_each[mset[m]][i],
                  t_aub_each[mset[m]][i], t_mub_each[mset[m]][i]);
      $write("Total number of errors: %Od\n",t errs);
   end
   for ( genvar m=0; m<nmsets; m++ )</pre>
     for ( genvar i=0; i<npsets; i++ ) begin</pre>
        localparam int idx = m * npsets + i;
        testbench n
          #( .w_exp(pset[i][0]), .w_sig(pset[i][1]), .w_int(pset[i][2]),
              .pset(i), .mtype(mset[m]) )
        t2( .done(d[idx]), .tstart(d[idx-1]) );
     end
endmodule
module testbench_n
  #( int w_exp = 5, w_sig = 8, w_int = 12, pset = 0, M_Type mtype = M_p1 )
   ( output logic done, input uwire tstart );
   localparam int w_fp = 1 + w_sig + w_exp;
   localparam int bias = ( 1 << w_exp-1 ) - 1;</pre>
   logic [w_int-1:0] a, b, c;
   uwire [w_fp-1:0] h;
   case ( mtype )
     M_p1: comp_p1 #( w_int, w_exp, w_sig ) c1(h, a, b, c);
```

```
\leftarrow \rightarrow Fall 2023
                 \leftarrow \rightarrow Homework 2
                                               Homework Sol Code
                                                                                             hw02-sol.v.html
         M_p2: comp_p2 #( w_int, w_exp, w_sig ) c2(h, a, b, c);
       endcase
       initial begin
          automatic int n_tests = testbench.n_tests;
          automatic int n_err = 0;
          automatic int ub_max = 0, ub_emax = 0, ub_sum = 0;
          wait( tstart );
          $write("Starting tests for mod %4s exp=%2d, sig=%2d, w=%2d\n",
                 testbench.mtype_str[mtype], w_exp, w_sig, w_int);
          for (int i=0; i<n_tests; i++ ) begin</pre>
             automatic bit choose_close_bc = $random() & 1'b1;
             real mut_h, shadow_h, shadow_hr, boc;
             logic [w_fp-1:0] shadow_hf;
             int ub, bit_loss, tol;
             a = rand_wid(w_int);
             if ( a == 0 ) a = 1;
             b = choose_close_bc ? <u>$random()</u> : rand_wid(w_int);
             c = choose_close_bc ? <u>$random()</u> : rand_wid(w_int);
             if (c == 0) c = 1;
             bit_loss = mtype == M_p2 || b == c ? 0
               : <u>$clog2(1 + int'($ceil(1 / fabs(1 - real'(b)/c)))</u>;
             tol = 1 + bit_loss;
             shadow_hr = (1 - real'(b)/c) / a;
             shadow_hf = conv#(w_exp,w_sig)::rtof( shadow_hr );
             shadow_h = conv#(w_exp,w_sig)::ftor( shadow_hf );
             #1;
             mut_h = conv#(w_exp,w_sig)::ftor(h);
             ub = conv#(w_exp,w_sig)::err_bits( shadow_hf, h );
             if ( ub > 0 ) ub_sum += ub;
             if ( ub > tol ) begin
                n_err++;
                if ( ub > ub_emax ) begin
                   ub_emax = ub;
                   $write( "Error %s #(%0d,%0d,%0d) a=%d b=%d c=%d: Err bits %0d (tol %0d)\n",
                            testbench.mtype_abbr[mtype],
                            w_exp, w_sig, w_int,
                            a, b, c, ub, tol );
                   $write( " Output %.4e != %.4e (correct).\n",
                            mut_h, shadow_h );
                   $write( " Output 'h%h * 2^(%d-%Od) != 'h%h * 2^(%d-%Od) (correct)\n",
                            h[w_sig-1:0], h[w_sig+w_exp-1:w_sig], bias,
                            shadow_hf[w_sig-1:0], shadow_hf[w_sig+w_exp-1:w_sig],
                            bias );
```

end

```
end
```

if (ub > ub_max) ub_max = ub;

end

```
$write("Finished tests for mod %4s exp=%2d, sig=%2d, w=%2d. %0d errors.\n",
testbench.mtype_str[mtype], w_exp, w_sig, w_int, n_err);
```

```
testbench.t_errs += n_err;
testbench.t_errs_each[mtype][pset] = n_err;
testbench.t_mub_each[mtype][pset] = ub_max;
testbench.t_aub_each[mtype][pset] = real'(ub_sum) / n_tests;
testbench.t_errs_mod[mtype] += n_err;
testbench.t_errs_size[pset] += n_err;
```

done = 1;

end

endmodule

`define SIMULATION_ON

// cadence translate_on

`default_nettype wire

`*ifdef* SIMULATION_ON

```
`include "/apps/linux/cadence/GENUS211/share/synth/lib/chipware/sim/verilog/CW/CW_fp_mult.v"
`include "/apps/linux/cadence/GENUS211/share/synth/lib/chipware/sim/verilog/CW/CW_fp_add.v"
`include "/apps/linux/cadence/GENUS211/share/synth/lib/chipware/sim/verilog/CW/CW_fp_sub.v"
`include "/apps/linux/cadence/GENUS211/share/synth/lib/chipware/sim/verilog/CW/CW_fp_div.v"
`include "/apps/linux/cadence/GENUS211/share/synth/lib/chipware/sim/verilog/CW/CW_fp_div.v"
```

`else

```
`include "/apps/linux/cadence/GENUS211/share/synth/lib/chipware/syn/CW/CW_fp_mult.v"
`include "/apps/linux/cadence/GENUS211/share/synth/lib/chipware/syn/CW/CW_fp_add.v"
`include "/apps/linux/cadence/GENUS211/share/synth/lib/chipware/syn/CW/CW_fp_sub.v"
`include "/apps/linux/cadence/GENUS211/share/synth/lib/chipware/syn/CW/CW_fp_i2flt.v"
`include "/apps/linux/cadence/GENUS211/share/synth/lib/chipware/syn/CW/CW_fp_i2flt.v"
```

`endif

```
11
/// LSU EE 4755 Fall 2023 Homework 3 -- SOLUTION
11
/// Assignment https://www.ece.lsu.edu/koppel/v/2023/hw03.pdf
`default_nettype none
 /// Problem 1
11
 /// Complete perm so that it permutes its inputs and computes the next perm num.
111
11
11
      [ ] Only modify perm.
11
      [<] perm must be recursive.</pre>
11
11
      [...] Make sure that the testbench does not report errors.
11
      [ / ] Module must be synthesizable. Use command: genus -files syn.tcl
11
11
      [<] Don't assume any particular parameter values.</pre>
11
11
      [~] Pay attention to cost. Don't grossly oversize things.
      [.] Code must be written clearly.
11
module perm
 \#( int w = 8, n = 20, dw = \frac{\text{sclog2}(n)}{\text{sclog2}(n)}
   ( output uwire [w-1:0] pdata_out[n],
    output uwire [dw-1:0] pnum_out[n],
    output uwire carry_out,
    input uwire [w-1:0] pdata_in[n],
    input uwire [dw-1:0] pnum_in[n] );
  /// SOLUTION
  if (n == 1) begin
     /// SOLUTION -- Problem 1a
     11
     // For n=1 the permutation is always identity ...
     // .. so the pdata out is set to pdata in ..
     // .. the permutation number remains zero (it always is 0 at n=1) ..
     // .. and the carry_out is set to 1.
     11
     assign pdata_out[0] = pdata_in[0];
     assign carry_out = 1;
     assign pnum_out[0] = 0;
  end else begin
     /// SOLUTION -- Problem 1a
```

```
\leftarrow \rightarrow Fall 2023 \leftarrow \rightarrow Homework 3
```

Homework Sol Code

```
11
// Set pos to the position of the element to be moved.
11
uwire [dw-1:0] pos = n - 1 - pnum_in[n-1];
11
// Copy the element at position pos to position n-1 in the output.
11
assign pdata_out[n-1] = pdata_in[pos];
11
// Prepare an array of n-1 elements and set to ..
// .. the elements of pdata_in except for the element at pos.
11
uwire [w-1:0] prdata_in[n-1];
for ( genvar i=0; i<n-1; i++ )</pre>
  assign prdata_in[i] = i < pos ? pdata_in[i] : pdata_in[i+1];</pre>
uwire co;
perm #(w,n-1,dw) rp( pdata_out[0:n-2], pnum_out[0:n-2], co,
                     prdata_in, pnum_in[0:n-2] );
/// SOLUTION -- Problem 1b
11
// Compute a tentative next value of digit n-1.
11
uwire [dw-1:0] dnext = pnum_in[n-1] + co;
11
// Determine whether there is a carry.
//
assign carry_out = dnext >= n;
11
// Set the next value of digit n-1 based on whether there is a carry.
11
assign pnum_out[n-1] = carry_out ? 0 : dnext;
```

end

```
endmodule
```

```
module perm_behavioral
#( int w = 8, n = 20, dw = <u>$clog2(n)</u>)
( output logic [w-1:0] pdata_out[n],
    output logic [dw-1:0] pnum_out[n],
    output logic carry_out,
    input uwire [w-1:0] pdata_in[n],
    input uwire [dw-1:0] pnum_in[n] );
```

/// DO NOT modify this module. The testbench uses it.

```
always_comb begin
// Permute values
```

pdata_out = pdata_in;

```
\leftarrow \rightarrow Fall 2023
                   \leftarrow \rightarrow Homework 3
                                                Homework Sol Code
          for ( int i=n-1; i>0; i-- ) begin
              automatic logic [dw-1:0] pos = i-pnum_in[i];
              automatic logic [w-1:0] x = pdata_out[pos];
              for ( int j=pos; j<i; j++ ) pdata_out[j] = pdata_out[j+1];</pre>
              pdata out[i] = x;
          end
       end
       /// DO NOT modify this module. The testbench uses it.
       always_comb begin
          // Compute next permutation number.
          carry out = 1;
          for ( int i=0; i<n; i++ ) begin</pre>
              automatic int radix = i + 1;
              automatic logic [dw:0] next_val = pnum_in[i] + carry_out;
              if ( next_val < radix ) begin</pre>
                 pnum_out[i] = next_val;
                 carry_out = 0;
              end else begin
                 pnum_out[i] = 0;
              end
          end
       end
```

 $///\ \,$ DO NOT modify this module. The testbench uses it.

```
int t_errs_i[npsets];
   int t_n_tests[npsets];
   int t_errs; // Total number of errors.
   initial begin
      t_{errs} = 0;
      for ( int i=0; i<npsets; i++ ) begin</pre>
         t_{errs_v[i]} = -1;
         t_errs_i[i] = -1;
         t_n_{tests[i]} = -1;
      end
      d[-1] = 1;
      wait( d[npsets-1] );
      for ( int p=0; p<npsets; p++ )</pre>
        <u>$write</u>("End of tests n=%2d, %0d perm errors, %0d next idx errors for %0d tests.\n",
                pset[p][1], t_errs_v[p], t_errs_i[p], t_n_tests[p]);
   end
   for ( genvar p=0; p<npsets; p++ ) begin</pre>
      <u>testbench_n</u> #( .w(pset[p][0]), .n(pset[p][1]), .idx(p) )
      tb( .done(d[p]), .tstart(d[p-1]) );
   end
endmodule
module testbench n
  #( int w=8, n=3, idx=0 )
   ( output logic done, input uwire tstart );
   localparam int dw = \frac{clog2}{n};
   localparam int max_tests = 1000;
   uwire [w-1:0] p_out[n], pb_out[n];
   uwire [dw-1:0] i_out[n], ib_out[n];
   uwire co, cob;
   logic [w-1:0] p_in[n];
   logic [dw-1:0] i_in[n];
   perm behavioral #(w,n,dw) pb( pb_out, ib_out, cob, p_in, i_in );
   perm #(w,n,dw) pmut( p_out, i_out, co, p_in, i_in );
   initial begin
      automatic int n_v_err = 0, n_i_err = 0;
      automatic longint nfact = 1;
      automatic int run_curr = 0;
      int n_tests;
      int run_length; // Number of consecutive permutations.
      for ( int i=2; i<=n; i++ ) nfact *= i;</pre>
      n_tests = nfact <= max_tests ? nfact : max_tests;</pre>
```

```
\leftarrow \rightarrow Fall 2023
                 \leftarrow \rightarrow Homework 3
                                               Homework Sol Code
          run_length = n_tests >= nfact ? n_tests : 4;
          for ( int i=0; i<n; i++ ) p_in[i] = "a" + n - i - 1;</pre>
          for ( int i=0; i<n; i++ ) i_in[i] = 0;</pre>
          wait( tstart );
          $write("Starting tests for w=%0d, n=%0d\n",w,n);
          for ( int i=0; i<n_tests; i++ ) begin</pre>
              automatic int tn_v_err = 0, tn_i_err = 0;
              bit show_v_err, show_i_err, show_trace;
              #1;
              for ( int j=0; j<n; j++ ) if ( p_out[j] !== pb_out[j] ) tn_v_err++;</pre>
              for ( int j=0; j<n; j++ ) if ( i_out[j] !== ib_out[j] ) tn_i_err++;</pre>
              if ( tn_v_err ) n_v_err++;
              if ( tn_i_err ) n_i_err++;
              show_trace = i < 10;
              show_v_err = tn_v_err && n_v_err < 5;</pre>
              show_i_err = tn_i_err && n_i_err < 5;</pre>
              if ( show_v_err || show_i_err || show_trace ) begin
                 if ( tn_v_err ) <u>$write("Error in permutation: ");</u>
                 else <u>$write("Trace of permutation: ");</u>
                 for ( int j=n-1; j>=0; j-- ) <u>$write("%1d ", i_in[j]);</u>
                 $write(" -> ");
                 for ( int j=n-1; j>=0; j-- ) <u>$write("%c ", char_or_q(p_out[j]));</u>
                 if ( tn_v_err ) begin
                     $write( " != ");
                    for ( int j=n-1; j>=0; j-- ) <u>$write("%c ", pb_out[j]);</u>
                    $write( " (correct)");
                 end
                 $write("\n");
                 if ( show_i_err ) begin
                 if ( tn_i_err ) <u>$write</u>("Error in next index: ");
                 else <u>$write("Trace of next index: ");</u>
                 for ( int j=n-1; j>=0; j-- ) <u>$write("%1d ", i_in[j]);</u>
                 $write(" -> ");
                 for ( int j=n-1; j>=0; j-- ) <u>$write("%h ", i_out[j]);</u>
                 if ( tn_i_err ) begin
                    $write( " != ");
                    for ( int j=n-1; j>=0; j-- ) <u>$write("%h ", ib_out[j]);</u>
                    $write( " (correct)");
                 end
                 $write("\n");
                 end
```

hw03-sol.v.html

```
\leftarrow \rightarrow Homework 3
\leftarrow \rightarrow \text{ Fall } 2023
```

```
end
```

```
if ( run_curr >= run_length ) begin
   run_curr = 0;
   for ( int j=1; j<n; j++ ) i_in[j] = {<u>$random()</u>} % (j+1);
```

end else begin

```
run_curr++;
i_in = ib_out;
```

end

end

```
$write("Finished with n=%0d, %0d perm errors, %0d next idx errors in %0d tests.\n",
          n, n_v_err, n_i_err, n_tests);
   testbench.t_errs_v[idx] = n_v_err;
   testbench.t_errs_i[idx] = n_i_err;
   testbench.t_n_tests[idx] = n_tests;
   done = 1;
end
```

endmodule

// cadence translate_on

LSU EE 4755 Homework 4 solution Due: 6 November 2023

Collaboration Rules

Each student is expected to complete his or her own assignment. It is okay to work with other students and to ask questions in order to get ideas on how to solve the problems or how to overcome some obstacle (be it a question of Verilog syntax, how a part of the problem might be solved, etc.) It is also acceptable to seek out digital design resources for help on Verilog, digital design, etc. It is okay to make use of AI LLM tools such as ChatGPT to answer these questions. Just don't trust the answers. (Do not assume LLM output is correct. Treat LLM output the same way one might treat legal advice given by a lawyer character in a movie: it may sound impressive, but it can range from sage advice to utter nonsense.)

After availing oneself to these resources each student is expected to be able to complete the assignment alone. Test questions will be based on homework questions and the assumed time needed to complete the question will be for a student who had solved the homework assignment on which it was based.

Helpful Examples

See the simple model slides for material on computing cost and delay, and also for a list of some sample problems. Also see 2022 Homework 3.

 $\leftarrow \rightarrow$ Fall 2023

Permutation Module

This assignment is based on the solution to Homework 3, the recursive permutation module perm, and the solution to Midterm Exam Problem 1, the inferred hardware for the permutation module. See Homework 3 for details on what the permutation module does. Appearing below is the Homework 3 solution with some comments removed. For the unabridged version visit https://www.ece.lsu.edu/koppel/v/2023/hw03-sol.v.html.

```
module perm
```

```
#( int w = 8, n = 20, wd = (100) )
 ( output uwire [w-1:0] pdata_out[n],
                                         output uwire [wd-1:0] pnum_out[n],
  output uwire carry_out,
  input uwire [w-1:0] pdata_in[n],
                                    input uwire [wd-1:0] pnum_in[n] );
if ( n == 1 ) begin
   assign pdata_out[0] = pdata_in[0];
   assign carry_out = 1;
   assign pnum_out[0] = 0;
 end else begin
   // Set pos to the position of the element to be moved.
   uwire [wd-1:0] pos = n - 1 - pnum_in[n-1];
   // Copy the element at position pos to position n-1 in the output.
    assign pdata_out[n-1] = pdata_in[pos];
   // Prepare an array of n-1 elements and set to ...
   // .. the elements of pdata_in except for the element at pos.
   uwire [w-1:0] prdata_in[n-1];
   for ( genvar i=0; i<n-1; i++ )</pre>
     assign prdata_in[i] = i < pos ? pdata_in[i] : pdata_in[i+1];</pre>
   // Recursively instantiate perm.
    uwire co;
    perm #(w,n-1,wd) rp( pdata_out[0:n-2], pnum_out[0:n-2], co,
                        prdata_in, pnum_in[0:n-2] );
   // Compute a tentative next value of digit n-1.
   uwire [wd-1:0] dnext = pnum_in[n-1] + co;
   // Determine whether there is a carry.
   assign carry_out = dnext >= n;
   // Set the next value of digit n-1 based on whether there is a carry.
   assign pnum_out[n-1] = carry_out ? 0 : dnext;
```

end

Permutation Module Inferred Hardware

Midterm Exam Problem 1 asked for the inferred hardware for the perm module instantiated with n=4. The solution appears below on the left. For this assignment the inferred hardware for a non-specific value of n will be needed, that is shown on the right.



There's no need to squint, the diagrams appear again in larger size at the end of this assignment. Also, SVG source for these modules are at https://www.ece.lsu.edu/koppel/v/2023/mt-p1-sol.svg and https://www.ece.lsu.edu/koppel/v/2023/hw04-perm-gen.svg. **Problem 1:** Compute the cost and delay of the following arithmetic hardware from the perm module. Assume that ripple units are used for addition, subtraction, and comparison.

(a) Compute the cost and delay of the hardware computing $pos = n - 1 - pnum_in[n-1]$ in terms of w_d , the value of parameter wd. Optimize for constants, including n.

Cost of hardware in terms of w_d . \bigtriangledown Delay of hardware in terms of w_d .

Optimize for constants, don't confuse elaboration-time computation with computation hardware.

The hardware is a subtractor with constant input n-1 and non-constant input $pnum_in[n-1]$. The exact cost of an adder would depend on the value of n-1, for example if n-1=0 the cost would be zero. But for a subtractor we set the carry in to 1 and so with a constant input the cost is the cost of w_d BHAs. So the cost is $4w_d u_c$ (see the midterm exam solution for details). (The cost can be reduced to $3w_d u_c$ by splitting the XOR gate in each BHA.)

The delay is one unit per bit (because the delay from ci to co of a BHA is just one gate delay), for a total delay of $w_d \, \mathrm{u_t}$.

(b) Compute the cost and delay of the hardware computing $dnext = pnum_in[n-1] + co$ in terms of w_d , the value of parameter wd. Optimize for constants and for the size of co. Assume in this problem that pnum_in and co arrive at t = 0.

Cost of hardware in terms of w_d . \checkmark Delay of hardware in terms of w_d .

Optimize considering the size of co. 🗹 Optimize for constants, don't confuse elaboration-time computation with computation hardware.

The dnext value is computed by adding a 1-bit value, co to pnum_in[n-1]. So this is equivalent to an adder with a constant input, 0, with the carry-in connected to co. The cost then will be $4w_d u_c$ (or $3w_d u_c$) and the delay $w_d u_t$].

 $\left(c\right)$ Compute the cost and delay of the hardware described by these lines:

```
uwire [wd-1:0] dnext = pnum_in[n-1] + co;
assign carry_out = dnext >= n;
```

Assume in this problem that co and pnum_in arrive at t = 0. The cost, of course, includes the cost of computing dnext in the previous part. The delay must be computed taking both lines into account.

Cost of hardware in terms of w_d . \checkmark Delay of co in terms of w_d .

Optimize considering the size of co. 🗹 Optimize for constants, don't confuse elaboration-time computation with computation hardware.

The cost of the hardware to compute carry_out is the cost of the hardware to compute dnext, $4w_d u_c$, plus the cost of the comparison module. A comparison module can be constructed from a subtractor with the difference bits eliminated. For two non-constant *w*-bit inputs the cost would be $4w u_c$, but in this case one input is constant dropping the cost to just $w_d u_c$. The total cost is $[4w_d + w_d] u_c$. As with the subtractor, the carry chain delay is one gate per bit so the delay of the comparison built using a ripple circuit is $w_d u_t$. Because the adder and the ripple circuit are cascadable the total delay is $[2 + w_d] u_t$, where the $2 u_t$ is the time for the adder to compute the first bit of the sum.

There are more problems on the next page.

Problem 2: In this problem consider the multiplexors with inputs connecting to pdata_in. (In the diagram they are the multiplexors on the upper-left including the 2-input muxes the *n*-input mux.) Call these the pdata multiplexors. In the solutions to the parts below use w for the value of parameter w and w_d for the value of parameter w_d .

(a) Compute the cost of the pdata multiplexors for a module instantiated at size n = N including only the hardware in the n=N instantiation, not in the recursive instantiations. The answer should be in terms of N and w. *Hint: this is easy.*

Cost of the pdata multiplexors at one level in terms of N, w, and (if needed) w_d .

In all of the multiplexors the inputs are w bits each. There are N-1 2-input multiplexors and one N-input mux. The cost of a 2-input mux is $3w u_c$, and there are N-1 of them so their cost is $3w(N-1) u_c$. The cost of an N-input, w-bit mux is $3w(N-1) u_c$, which interestingly is the same as the total cost of the 2-input multiplexors. The total cost is $6w(N-1) u_c$.

(b) This is important. Expect to expend brain energy. Don't skip. Compute the total cost of the pdata multiplexors for an instantiation at size n = N including the recursive instantiations all the way down. The answer should be in terms of N and w.

Cost of the pdata multiplexors including recursive instantiations in terms of N, w, and (if needed) w_d .

The cost at level n, based on the previous part (but using lower-case n) is $6w(n-1)u_c$. The cost of the n = 1 instantiation is zero because all that module does is connect its inputs to its outputs. So the total cost of instantiations from N to 2, which we'll call C(N), is $\sum_{n=2}^{N} 6w(n-1)u_c$. Proceeding step by step for the benefit of those who are rusty, even on one of the more storied finite sums

$$C(N) = \sum_{n=2}^{N} 6w(n-1) u_{c}$$
$$= 6w u_{c} \sum_{n=2}^{N} (n-1)$$
$$= 6w u_{c} \sum_{n=1}^{N-1} n$$
$$= 6w u_{c} \frac{N(N-1)}{2}$$
$$= 3wN(N-1) u_{c}$$

For those scanning for boxes, the total $\left| \, \cos t \, \mathrm{is} \, \, 3w N (N-1) \, \mathrm{u_c} \, \right|$

Problem 3: In this problem compute delays for pdata_out and pnum_out. In the solutions use d for the value of parameter wd. This is also important and even more interesting. Expect to expend brain energy. Don't skip.

(a) Assume that the delay of the subtractors computing **pos** is $\lg w_d$, where w_d is the value of parameter wd. (Note that $\lg w_d$ is not an answer to Problem 1.) Further, suppose the delay of the less-than units providing a select signal to the 2-input pdata multiplexors is zero. Using these assumptions compute the delay of the first and last elements of pdata_out for an instantiation at n=N and show the critical path. The delay should be in terms of N and w_d . To solve this problem it might be helpful to draw two instantiation levels to help find the critical path.

 \checkmark Delay of pdata_out[0] in terms of N and w_d accounting for recursive instantiations. \checkmark Show critical path.

] Delay of pdata_out[N-1] in terms of N and w_d accounting for recursive instantiations. \checkmark Show critical path.

The easier of these to solve is $pdata_out[N-1]$ because its value is computed without using data from a recursive instance. As everyone reading this should know or at least learn now and not forget, the delay of an N-input multiplexor is $2\lceil \lg N \rceil u_t$. For this problem we were to assume that the subtractor computing pos has a delay of $\lg w_d$. We can safely assume that the inputs to the n = N instance arrive at t = 0, and so pos (the output of the subtractor) arrives

at $t = \lg w_d$. Therefore the delay of $\lfloor \text{pdata_out[N-1]} \text{ is } \lfloor \lg(w_d) + 2\lceil \lg N \rceil \rfloor u_t \rfloor$. The delays, arrival times, and critical path are shown in the diagram below.



To compute the delay of output pdata_out [0] we need to find the path it will take through the recursive instantiations. The illustration below shows the top-level instantiation, for n=N and one level down, for n=N-1. To understand the solution it is important that you pay attention to the arrival times of signals, shown in circled purple numbers and expressions. For the top-level instantiation the arrival time of all inputs is at t=0. But, for the n=N-1 instantiation notice that some signals arrive at t = 0, such as pnum_in, while pdata_in arrives later, at $t = [\lg(w_d) + 2] u_t$. (The time unit, $\mathbf{u}_{t,i}$ is not shown on the illustrations.) The fact that **pnum_in** to the n = N - 1 instantiation arrives at t = 0 means that the select signals to the 2-input multiplexors arrives at $t = \lg w_d$ at all instantiations. The pdata_in inputs are different. At n = N they arrive at t = 0, while for n = N - 1 they arrive at $[\lg(w_d) + 2] u_t$. In the n = N - 1 instance consider the 2-input multiplexors. Whereas at n = N the data inputs arrived before the select signal, at n = N - 1 the data inputs arrive after the select signal. That means that the arrival time at the outputs of the 2-input multiplexors at n = N - 1 is at $[\lg(w_d) + 2 + 2] u_t = [\lg(w_d) + 4] u_t$. Each further level down adds just 2 units of delay. At level n input pdata_in[n-1] does not go through the recursive instantiation. But input $pdata_in[0]$ goes all the way down to n = 1, and at each level before n = 1 another 2 units are added. (The delay, remember, at n = 1 is zero.) Therefore the total delay down to n = 1 is $[\lg(w_d) + 2(N-1)] u_t$. The pdata_out output of the recursive instance connects directly to the pdata_out of the containing instance, and so no further delay is added. Therefore | the total delay is $\left[\lg(w_d) + 2(N-1)
ight] \mathrm{u_t}$



SVG source for the module below is at https://www.ece.lsu.edu/koppel/v/2023/mt-p1-sol.svg.



SVG source for the module below is at https://www.ece.lsu.edu/koppel/v/2023/hw04-perm-gen.svg.



```
11
/// LSU EE 4755 Fall 2023 Homework 5 -- SOLUTION
11
/// Assignment https://www.ece.lsu.edu/koppel/v/2023/hw05.pdf
`default_nettype none
/// Problem1
11
 /// Complete uniq_vector_seq as described in the handout.
111
11
11
      [ / ] Only modify uniq_vector_seq
      [...] Remove the uniq vector comb instantiation.
11
11
11
      [~] Make sure that the testbench does not report errors.
      [/] Module must be synthesizable. Use command: genus -files syn.tcl
11
11
      [...] Don't assume any particular parameter values.
11
11
11
      [.] Code must be written clearly.
11
      [.] Pay attention to cost.
      [\checkmark] Make sure that cost is not proportional to n^2.
11
module uniq_vector_seq
  #( int we = 10, n = 5, wc = $clog2(n+1) )
  ( output logic [n-1:0] uniq_bvec,
    output logic [wc-1:0] n_match,
    input uwire [we-1:0] element,
    input uwire start, clk );
  /// SOLUTION
  logic [we-1:0] elements [n-1:0];
  logic [n-1:0] occ_bvec;
  logic [wc-1:0] uniq_at [n-1:0];
  always ff @( posedge clk ) begin
     // Find minimum match_pos for which elements[match_pos] == element.
     11
     automatic logic [wc-1:0] match_pos = 0;
     // Number of existing elements matching element.
     n match = 1;
     for ( int i=n-1; i>=1; i-- ) begin
        automatic logic next_occ_bvec = !start && occ_bvec[i-1];
        11
        // If next_occ_bvec == 0, this element had been reset.
        // Check whether element matches elements[i-1]
        11
```

```
\leftarrow \rightarrow Fall 2023
                   \leftarrow \rightarrow Homework 5
                                                 Homework Sol Code
             automatic logic match = next_occ_bvec && element == elements[i-1];
              11
              // There is no match if this elt had been reset.
             n_match += match;
             if ( match ) match_pos = n - i;
             elements[i] <= elements[i-1];</pre>
             occ_bvec[i] <= next_occ_bvec;</pre>
             // If match is true then elements[i-1] will never be unique. :-(
              11
             uniq_at[i] <= match ? n : uniq_at[i-1];</pre>
             // Update uniqueness
              11
             uniq_bvec[i] <= !next_occ_bvec || !match && i >= uniq_at[i-1];
             //
             // Future elements[i] is unique if:
              // - It had been reset.
              // - It is beyond its unique-at position (uniq_at).
          end
          elements[0] <= element;</pre>
          occ_bvec[0] <= 1;</pre>
          uniq_at[0] <= match_pos;</pre>
          uniq bvec[0] <= match pos == 0;</pre>
       end
   endmodule
   module uniq_vector_comb
      \#( int we = 10, n = 5, wc = \frac{clog2}{n+1})
       ( output logic [n-1:0] uniq_bvec,
         output logic [wc-1:0] n_match,
         input uwire [we-1:0] element [n-1:0] );
       /// This module is for reference. It should not be part of your solution.
       // Modify this module only for experimentation.
       // Combinational version.
       always_comb
         for ( int i=0; i<n; i++ ) begin</pre>
             automatic logic [wc-1:0] occ = 0;
             for ( int j=0; j<n; j++ ) if ( element[i] == element[j] ) occ++;</pre>
            if ( i == 0 ) n_match = occ;
            uniq bvec[i] = occ == 1;
         end
```

/// Testbench Code

```
11
// It is okay to modify the testbench code to facilitate the coding
// and debugging of your modules. Keep in mind that your submission
// will be tested using a different testbench, so on the one hand no
// one will be accused of dishonesty for modifying the testbench
// below. However be sure to restore any changes to make sure that
// your code passes the original testbench.
// cadence translate_off
program reactivate
   (output uwire clk_reactive, output int cycle_reactive,
    input uwire clk, input var int cycle);
   assign clk_reactive = clk;
   assign cycle_reactive = cycle;
endprogram
module testbench;
   localparam int npsets = 4; // This MUST be set to the size of pset.
   // { n we s }
   localparam int pset[npsets][3] =
              '₹
                \{4, 4, 0\},\
                \{4, 4, 1\},\
                \{7, 6, 0\},\
                \{7, 6, 1\}
                };
   logic d[npsets:-1]; // Start / Done signals.
   int t_errs_bvec[npsets];
   int t_errs_n_match[npsets];
   int t_n_tests[npsets];
   int t_errs;
                   // Total number of errors.
   initial begin
      t_{errs} = 0;
      for ( int i=0; i<npsets; i++ ) begin</pre>
         t_errs_bvec[i] = -1;
         t_errs_n_match[i] = -1;
         t_n_{tests[i]} = -1;
      end
      d[-1] = 1;
      wait( d[npsets-1] );
      for ( int p=0; p<npsets; p++ )</pre>
        $write("End of tests n=%2d, s=%0d: %0d bvec errors, %0d n_match errors for %0d tests.\n",
               pset[p][1], pset[p][2],
               t_errs_bvec[p], t_errs_n_match[p], t_n_tests[p]);
```

end

```
for ( genvar p=0; p<npsets; p++ ) begin
    testbench_n #( .we(pset[p][0]), .n(pset[p][1]), .s(pset[p][2]), .idx(p) )</pre>
```

```
\leftarrow \ \rightarrow \ \text{Fall} \ 2023
                   \leftarrow \rightarrow Homework 5
                                                Homework Sol Code
          tb( .done(d[p]), .tstart(d[p-1]) );
       end
   endmodule
   module testbench_n
      #( int n = 12, we = 6, idx = 1, s = 1 )
       ( output logic done, input uwire tstart );
       localparam int wc = $clog2(n+1);
       localparam int n_tests = 100000;
       localparam int cyc_max = n_tests * 2 + 3*n;
       int seed;
       initial seed = 475501;
       function string sample( input string str );
          sample = str[ <u>$dist uniform( seed, 0, str.len()-1 ) ];</u>
       endfunction
       bit clk;
       int cycle, cycle_limit;
       logic clk_reactive;
       int cycle_reactive;
       reactivate ra(clk_reactive,cycle_reactive,clk,cycle);
       string event_trace;
       initial begin
          clk = 0;
          cycle = 0;
          event_trace = "";
          done = 0;
          cycle_limit = cyc_max;
          wait( tstart );
          fork
             while ( !done ) #1 cycle += clk++;
             wait( cycle >= cycle_limit )
               $write("Exit from clock loop at cycle %0d, limit %0d. %s\n %s\n",
                       cycle, cycle_limit, "** CYCLE LIMIT EXCEEDED **",
                       event_trace);
          join_any;
          done = 1;
       end
       typedef logic [we-1:0] Digit;
       Digit element_stream[$];
       bit start_stream[$];
       logic [we-1:0] element_stream_x[$];
       int element_most_recent_t[int];
       logic [n-1:0] shadow_uniq_bvec;
```

int element_occ[int];

hw05-sol.v.html

```
uwire [n-1:0] uniq_bvec;
uwire [wc-1:0] n_match;
<u>Digit</u> element;
logic start;
uniq_vector seg #(we,n) uvs( uniq_bvec, n_match, element, start, clk );
int n_err_bvec, n_err_n_match;
localparam int pre n = 2;
localparam int trace_len = 5;
localparam int n_pre_check = 2 * n; // Number of inputs before testing.
localparam int start_dups = 5 * n + n_pre_check;
initial begin
   automatic int n_tests_done = 0;
   int tnum_last_start;
   bit err_bvec_here, err_n_match_here, show_trace;
   n_err_bvec = 0;
   n_err_n_match = 0;
   element = 1;
   start = 1;
   @( negedge clk );
   @( negedge clk );
   start = 0;
   wait( cycle > 2 );
   @( negedge clk );
   <u>$write</u>("\n** Starting tests for n=%0d, input start used = %0s **\n",
          n, s ? "Yes" : "No");
   for ( int tnum=0; tnum<n_tests; tnum++ ) begin</pre>
      automatic bit want_match =
        tnum > start_dups && <u>$dist_uniform(seed,0,2) == 0;</u>
      automatic bit want_reset =
        tnum == 0 || s && <u>$dist_uniform(seed,0,1*n) == 0;</u>
      automatic logic [we-1:0] next_element =
        want_match ? element_stream[ {<u>$random</u>} % (n-1) ] : {<u>$random</u>} % 100;
      automatic int n_starts_recent = 0;
      automatic int shadow_n_match = 0;
      bit err_here;
      @( negedge clk );
      if ( element_stream.size() >= n + pre_n ) begin
         automatic int old_element = element_stream.pop_back();
         automatic bit old_start = start_stream.pop_back();
      end
      if ( element_stream.size() >= n
```

```
\leftarrow \rightarrow Fall 2023
                  \leftarrow \rightarrow Homework 5
                                               Homework Sol Code
                  && tnum_last_start + n <= tnum )
               element_occ[element_stream[n-1]]--;
             if ( want_reset ) tnum_last_start = tnum;
             element = next_element;
             start = want_reset;
             if ( want_reset ) element_occ.delete();
             element occ[element]++;
             element_stream.push_front(element);
             start_stream.push_front(start);
             for ( int i=0; i<n; i++ ) begin</pre>
                if ( element_stream[i] == element && !n_starts_recent )
                  shadow n match++;
                shadow_uniq_bvec[i] =
                  n_starts_recent || element_occ[element_stream[i]] == 1;
                n_starts_recent += start_stream[i];
             end
             @( posedge clk_reactive );
             if ( tnum < n_pre_check ) continue;</pre>
             err_n_match_here = n_match !== shadow_n_match;
             if ( err_n_match_here ) n_err_n_match++;
             err bvec here = unig bvec !== shadow unig bvec;
             if ( err_bvec_here ) n_err_bvec++;
             err_here = err_bvec_here || err_n_match_here;
             show trace = tnum > start dups + n && tnum < start dups + n + trace len
               || err_here && n_err_bvec < 5 && n_err_n_match < 5;</pre>
             n_tests_done++;
             if ( show_trace ) begin
                $write( "%s, uniq_bvec: t=%0d, %b",
                         err_bvec_here ? "Error" : "Trace", tnum,
                         uniq_bvec);
                if ( err_bvec_here )
                  $write( "!= %b ( correct )", shadow_uniq_bvec );
                if ( err_n_match_here )
                  $write("\nError: n_match: %0d != %0d (correct)",
                          n_match, shadow_n_match);
                $write("\n[");
                for ( int i=n+pre_n-1; i>=n; i-- )
                  $write( "%2s%0s%0s ", "", i == n ? "]" : "", i ? "," : "" );
                for ( int i=n-1; i>=0; i-- )
                  $write( "%1s%1h%0s%0s ",
                           uniq bvec[i]===shadow uniq bvec[i] ? " " : "E",
                           uniq_bvec[i],
                           i == n ? "]" : "", i ? "," : "" );
                $write(" <-- uniq_bvec\n[");</pre>
```

hw05-sol.v.html

```
Homework Sol Code
\leftarrow \rightarrow Fall 2023
                  \leftarrow \rightarrow Homework 5
                 for ( int i=n+pre_n-1; i>=0; i-- )
                   $write( "%2d%0s%0s ",
                           element_stream[i], i == n ? "]" : "", i ? "," : "" );
                 $write(" <-- Element\n[");</pre>
                 for ( int i=n+pre_n-1; i>=0; i-- )
                   $write( "%2d%0s%0s ",
                            start_stream[i], i == n ? "]" : "", i ? "," : "" );
                 $write(" <-- Start\n");</pre>
              end
          end
          <u>$write</u>
             ("For n=%0d, s=%0d: done with %0d tests. Errors: %0d bvec, %0d n_match.\n",
              n, s, n_tests, n_err_bvec, n_err_n_match);
          testbench.t_errs_bvec[idx] = n_err_bvec;
          testbench.t_errs_n_match[idx] = n_err_n_match;
          testbench.t_n_tests[idx] = n_tests_done;
          done = 1;
```

end

endmodule

// cadence translate_on
16 Fall 2022 Solutions

11

```
/// LSU EE 4755 Fall 2022 Homework 1 -- SOLUTION
11
/// Assignment https://www.ece.lsu.edu/koppel/v/2022/hw01.pdf
`default_nettype none
/// Problem 0
11
/// Look over the modules and enum below.
11
11
/// Declare Useful Enumeration Constants.
11
typedef enum
 { Char_space = 32, Char_0 = 48, Char_9 = 57,
   Char_A = 65, Char_Z = 90, Char_a = 97, Char_z = 122 }
 Chars_Special;
11
// See digit_valid_09 to see how these constants can be used.
/// An ordinary two-input multiplexor.
11
module mux2
 #(int w = 3)
  ( output uwire [w-1:0] x,
    input uwire s,
    input uwire [w-1:0] a0, a1 );
  assign x = s? a1 : a0;
endmodule
/// Problem 1
11
111
     Replace procedural code in atoi1 with modules as described in handout.
111
11
11
      [<] atoi1 must instantiate and use a digit_valid_az module.</pre>
11
      [<] atoi1 must instantiate and use a char_to_uc module.</pre>
11
      [/] atoi1 must instantiate and use mux2 modules.
      [...] The completed atoi1 must not have procedural code (always_comb, etc.)
11
11
```

```
\leftarrow \rightarrow Fall 2022
                  \leftarrow \rightarrow Homework 1
                                              Homework Sol Code
   11
           [<] Complete module digit_valid_az.</pre>
   11
           [ 	 Complete module char_to_uc.
   11
   11
           [<] Make sure that the testbench does not report errors.</pre>
   11
           [/] Module must be synthesizable. Use command: genus -files syn.tcl
   11
   11
           [<] Don't assume any particular parameter value.</pre>
   11
           [<] Code must be written clearly.</pre>
   11
           [ ] Pay attention to cost and performance.
   11
   module char_to_uc( output uwire [7:0] uc, input uwire [7:0] c );
       uwire is_lc = c >= Char_a && c <= Char_z;</pre>
       uwire [7:0] uc_if_lc = c - Char_a + Char_A;
       /// SOLUTION
       mux2 #(8) m( uc, is_lc, c, uc_if_lc );
   endmodule
   module digit_valid_az
     #( int r = 11, vw = \frac{clog2}{r} (r) )
       ( output uwire valid, output uwire [vw-1:0] val, input uwire [7:0] char );
       /// SOLUTION
       assign val = 10 + char - Char_A;
       assign valid = char >= Char_A && char < Char_A + r - 10;
   endmodule
   module atoi1
     #(int r = 32, w = \frac{clog2}{r})
       ( output logic [w-1:0] val,
         output logic is_digit,
         input uwire [7:0] char );
       /// SOLUTION
       logic [w-1:0] val_09, val_az, val_n;
       logic is_09, is_az;
       digit valid 09 #(r,w) v09( is_09, val_09, char );
       uwire [7:0] char uc;
       char to uc tuc(char_uc,char);
       digit valid az #(r,w) vaz( is_az, val_az, char_uc );
       uwire [w-1:0] z = 0;
       mux2 #(w) mval(val_n,is_09,val_az,val_09);
       mux2 #(w) mval0(val,is_digit,z,val_n);
       assign is_digit = is_09 || is_az;
   endmodule
   module digit_valid_09
```

```
#( int r = 9, vw = <u>$clog2(r)</u> )
  ( output uwire valid, output uwire [vw-1:0] val, input uwire [7:0] char );
```

```
hw01-sol.v.html
```

```
\leftarrow \rightarrow Fall 2022
                  \leftarrow \rightarrow Homework 1
                                               Homework Sol Code
       assign val = char - Char_0;
       assign valid = char >= Char_0 && char <= Char_9 && char < Char_0 + r;
   endmodule
    /// Reference Module -- Do Not Modify
    11
   module atoi1_behavioral
      \#( int r = 32, w = \frac{\text{sclog2}(r)}{r} )
       ( output logic [w-1:0] val,
         output logic is_digit,
         input uwire [7:0] char );
       logic [7:0] char_uc;
       logic [w-1:0] val_09, val_az;
       logic is_09, is_az;
       always_comb begin
          char_uc = char >= Char_a && char <= Char_z</pre>
             ? char - Char_a + Char_A : char;
          val_09 = char - Char_0;
          val_az = 10 + char_uc - Char_A;
          is_09 = char >= Char_0 && char <= Char_9 && char < Char_0 + r;</pre>
          is_az = char_uc >= Char_A && char_uc < Char_A + r - 10;</pre>
          is_digit = is_09 || is_az;
          if ( is_09 ) val = val_09;
          else if ( is_az ) val = val_az;
          else
                              val = 0;
       end
```



```
// cadence translate_off
```

```
module testbench;
```

```
\leftarrow \rightarrow Fall 2022
                  \leftarrow \rightarrow Homework 1
                                              Homework Sol Code
       assign d[-1] = 1; // Initialize first at true.
       // Instantiate a testbench at each size.
       11
       for ( genvar i=0; i<nradices; i++ )</pre>
         testbench r #(radices[i]) t2( .done(d[i]), .tstart(d[i-1]) );
    endmodule
   module testbench_r
      #(int r = 16)
       ( output logic done, input uwire tstart );
       localparam int wd = 8;
       localparam int w = <u>$clog2(r**wd);</u>
       localparam int w1 = 2 * \frac{\text{sclog2}(r)}{r};
       localparam int ntests = 500;
       logic [1:0][7:0] str;
       uwire [w1-1:0] val1;
       uwire is_digit1;
       atoi1 #(r,w1) a1( val1, is_digit1, str[0] );
       logic [7:0] non_digit[256];
       function string to_string(input logic [w1-1:0] val);
          automatic string result = "";
          if ( val == 0 ) result = "0";
          while (val) begin
             automatic int d = val % r;
             automatic int v = d < 10 ? d + Char_0 : d - 10 + Char_A;</pre>
             val = val / r;
             result = { string'(v), result };
          end
          to_string = result;
       endfunction
       initial begin
          automatic int nd_size = 0;
          automatic int rm10 = r > 10 ? 10 : r;
          automatic bit err_silent = 0;
          for ( int i=32; i<128; i++ ) begin</pre>
             if ( i >= Char_0 && i < Char_0 + rm10 ) continue;</pre>
             if ( i >= Char_A && i < Char_A + r - 10 ) continue;</pre>
             if ( i >= Char_a && i < Char_a + r - 10 ) continue;</pre>
             non_digit[nd_size++] = i;
          end
          str[1] = Char_space;
```

```
\leftarrow \rightarrow Fall 2022
                 \leftarrow \rightarrow Homework 1
                                             Homework Sol Code
                                                                                          hw01-sol.v.html
          wait( tstart );
          for ( int tt=0; tt<1; tt++ ) begin</pre>
             automatic bit single char = tt == 0;
             automatic bit space_pad = single_char || tt == 1;
             automatic int nttests = single_char ? 256 : ntests;
             automatic int n_err = 0, n_lerr = 0;
             automatic string ttype =
               single_char ? "Single_Char (SC)"
                 : space_pad ? "Space_Pad (SP)" : "General (GE)";
             automatic string abbrev =
               single_char ? "SC" : space_pad ? "SP" : "GE";
          for ( int i=0; i<nttests; i++ ) begin</pre>
             automatic int len = single_char ? 1 : 1 + {$random} % wd;
             automatic logic [w1-1:0] sval = 0;
             automatic bit is_09 = i >= Char_0 && i <= Char_9 && i < Char_0 + r;
             automatic int iuc =
               i >= Char_a && i <= Char_z ? i - Char_a + Char_A : i;
             automatic bit is_az = iuc >= Char_A && iuc < Char_A + r - 10;
             automatic bit sis_digit = is_09 || is_az;
             str[0] = i;
             sval = is_09 ? i - Char_0 : is_az ? 10 + iuc - Char_A : 0;
             #1;
             if ( sval !== val1 ) begin
                n err++;
                if ( !err silent && n err < 5 )</pre>
                  <u>$write</u>("R %2d Error val 'h%h or %s != %s (correct) for string \"%s\"\n",
                          r, val1, to_string(val1), to_string(sval),
                          string'(str));
             end
             if ( sis_digit !== is_digit1 ) begin
                n lerr++;
                if ( !err silent && n lerr < 5 )</pre>
                  $write("R %2d Error is_digit %h != %0d (correct) for string \"%s\"\n",
                          r, is_digit1, sis_digit, string'(str) );
             end
             #1;
          end
             <u>$write</u>("Radix %2d, done with %0d tests, %0d val errors, %0d is_digit errors.\n",
                 r, nttests, n_err, n_lerr);
                testbench.t_errs += n_err + n_lerr;
             if ( n_err + n_lerr ) err_silent = 1;
          end
          done = 1;
       end
```

```
11
/// LSU EE 4755 Fall 2022 Homework 2 -- SOLUTION
11
/// Assignment https://www.ece.lsu.edu/koppel/v/2022/hw02.pdf
/// Problem 0
11
/// Look over the modules and enum below.
11
11
// Ensure that an omitted type results in an error message.
`default nettype none
// Module names. (Used by the testbench.)
11
typedef enum { M_proc, M_iter, M_tree, M_iter_sol, M_tree_sol } M_Type;
// Hide the fact that we've memorized ASCII codes.
11
typedef enum
 { Char_0 = 48, Char_9 = 57,
   Char_A = 65, Char_Z = 90, Char_a = 97, Char_z = 122 }
 Chars_Special;
// A function version of atoi1 -- Convert ASCII character to a value.
11
function int atoi1_func( input logic [7:0] char, input int r );
     automatic int char_uc =
       char >= Char_a && char <= Char_z ? char - Char_a + Char_A : char;</pre>
     automatic int val_09 = char - Char_0;
     automatic int val_az = 10 + char_uc - Char_A;
     automatic bit is_09 = char>=Char_0 && char <= Char_9 && char < Char_0 + r;</pre>
     automatic bit is_az = char_uc >= Char_A && char_uc < Char_A + r - 10;</pre>
     atoi1_func = is_09 ? val_09 : is_az ? val_az : -1;
endfunction
module atoi1
 #(int r = 32, w = 10)
  ( output logic [w-1:0] val,
    output logic is_digit,
    input uwire [7:0] char );
  always_comb begin
     automatic int valr = atoi1_func(char,r);
     is_digit = valr >= 0;
     val = is_digit ? valr : 0;
  end
endmodule
module mux2
 #(int w = 3)
  ( output uwire [w-1:0] x,
    input uwire s,
    input uwire [w-1:0] a0, a1 );
```

```
\begin{array}{ll} \leftarrow \rightarrow \mbox{Fall 2022} & \leftarrow \rightarrow \mbox{Homework 2} & \mbox{Homework Sol Code} \\ & \mbox{assign } x = \mbox{s ? al : a0;} \\ & \mbox{endmodule} \\ & \mbox{module mult_by_c} \\ & \mbox{\#( int w_in = 8, int c = 16, int w_out = w_in+\mbox{$sclog2(c) })} \end{array}
```

```
( output uwire [w_out-1:0] prod, input uwire [w_in-1:0] a );
assign prod = a * c;
endmodule
module add
  #( int w = 5 )
  ( output uwire [w-1:0] s, input uwire [w-1:0] a, b );
  assign s = a + b;
endmodule
```

```
/// Problem1
11
/// Complete atoi_it so that it computes the string value as follows.
///
11
11
      [/] atoi_it must instantiate and use n atoi modules.
11
      [<] atoi_it must instantiate and use mult_by_c modules.</pre>
      [<] atoi_it must instantiate and use add modules.</pre>
11
11
      [*] Procedural code can be used, but not in place of atoi and mult_by_c.
11
11
      [ ] DO NOT use atoi1_func in your solution.
11
11
      [...] Make sure that the testbench does not report errors.
11
      [v] Module must be synthesizable. Use command: genus -files syn.tcl
11
      [.] Don't assume any particular parameter value.
11
```

```
//
// [•] Code must be written clearly.
// [•] Pay attention to cost and performance.
```

```
module atoi_it
```

```
#( int r = 11, n = 5, wv = <u>$clog2(</u> r**n ), wd = <u>$clog2(n+1)</u> )
  ( output logic [wv-1:0] val,
    output logic [wd-1:0] nd,
    input uwire [7:0] str [n-1:0] );
```

```
/// SOLUTION
```

```
\leftarrow \rightarrow \text{ Fall 2022} \qquad \leftarrow \rightarrow \text{ Homework 2}
```

Homework Sol Code

```
11
uwire [wcv-1:0] valdr;
uwire is_digit;
atoi1 #(r,wcv) a( valdr, is_digit, str[i] );
// Determine if this digit continues a sequence of valid digits
// starting at str[0].
11
assign is_valid[i] = is_digit && is_valid[i-1];
// Replace value with zero if str[i] is not a digit, or if the
// string of valid digits has already ended.
11
uwire [wcv-1:0] vald = is_valid[i] ? valdr : 0;
// Multiply (scale) the digit value based on its position in the number.
11
uwire [wv-1:0] vals;
mult by c #( .w_in(wcv), .c(r**i), .w_out(wv) ) mc( vals, vald );
// Add the scaled digit to the value accumulated so far.
11
add #(wv) a1( vali[i], vali[i-1], vals );
// Update the number of digits so far.
11
assign ndi[i] = is_valid[i] ? i+1 : ndi[i-1];
```

```
end
```

```
endmodule
```

```
module atoi_pr
#( int r = 11, n = 5, wv = <u>$clog2(</u> r**n ), wd = <u>$clog2(n+1)</u> )
  ( output logic [wv-1:0] val,
     output logic [wd-1:0] nd,
     input uwire [7:0] str [n-1:0] );
```

/// DO NOT Modify the module. Use it for reference.

```
always_comb begin
  val = 0; nd = 0;
  for ( int i=0; i<n; i++ ) begin
      // Get val of current char. If val is < 0 then char is not a digit.
      automatic int dval = atoi1_func(str[i],r);
      if ( dval < 0 ) break;
      val += dval * r**i;
      nd++;
    end
end
```

```
endmodule
```

11 11 [<] atoi_tr must recurisvely instantiate two instances of itself.</pre> [<] atoi_tr must instantiate and use atoi modules.</pre> 11 11 [*] atoi_tr must instantiate and use mult_by_c modules. 11 [<] Procedural code can be used, but not in place of atoi and mult_by_c.</pre> 11 [✓] DO NOT use atoi1_func in your solution. 11 11 11 [...] Make sure that the testbench does not report errors. [.] Module must be synthesizable. Use command: genus -files syn.tcl 11 11 [/] Don't assume any particular parameter value. 11 11 11 [✓] Code must be written clearly. [<] Pay attention to cost and performance.</pre> 11 module atoi_tr #(int r = 11, n = 5, wv = <u>\$clog2(</u> r**n), wd = <u>\$clog2(</u>n+1)) (output uwire [wv-1:0] val, output var logic [wd-1:0] nd, input uwire [7:0] str [n-1:0]); /// SOLUTION if (n == 1) begin uwire is dd; uwire [wv-1:0] valr; atoi1 #(r,wv) a(valr, is_dd, str[0]); assign val = is_dd ? valr : 0; assign nd = is_dd; // Note: nd may be more than one bit. end else begin // Prepare to split the input string into two halves. Note that // the hi half may be larger, and so we use nhi to compute the // number of bits needed in the value output (vwh) and the // number of digits output (dwh). 11 localparam int nlo = n/2; localparam int nhi = n - nlo; localparam int vwh = \$clog2(r**nhi); localparam int dwh = \$clog2(nhi+1); 11 uwire [vwh-1:0] vallo, valhi; uwire [dwh-1:0] ndlo, ndhi; // Split input string between two recursive instantiations 11 atoi tr #(r,nlo,vwh,dwh) alo(vallo, ndlo, str[nlo-1:0]); atoi tr #(r,nhi,vwh,dwh) ahi(valhi, ndhi, str[n-1:nlo]); // Determine whether the hi half of the string may be part // of the number. 11 uwire hitoo = ndlo == nlo; uwire [vwh-1:0] valhid = hitoo ? valhi : 0; // Scale the upper half. 11 uwire [wv-1:0] valhis; // VALue HIgh Scaled

```
\leftarrow \rightarrow \text{ Fall 2022} \qquad \leftarrow \rightarrow \text{ Homework 2} \qquad \qquad \text{Homework Sol Code}
```

```
mult by c #(vwh,r**nlo,wv) mc( valhis, valhid );
assign val = vallo + valhis;
assign nd = hitoo ? nlo + ndhi : ndlo;
```

```
end
```



```
// cadence translate_off
module testbench;
   localparam int nnsets = 7;
   localparam int nset[nnsets] = '{ 1, 2, 3, 4, 7, 8, 9 };
   localparam int npsets = 2;
   localparam int pset[npsets] = '{ 10, 16 };
   localparam int nmsets = 2;
   localparam M_Type mset[nmsets] = '{ M_tree, M_iter };
   string mtype_str[M_Type] =
          '{ M_proc: "atoi_pr", M_tree: "atoi_tr", M_iter: "atoi_it",
             M_tree_sol:"a_tr_sol", M_iter_sol:"a_it_sol" };
   int t_errs_len_mod[M_Type];
   int t_errs_val_mod[M_Type];
   int t_errs_len_r[int];
   int t_errs_val_r[int];
   int t_errs_len_n[int];
   int t_errs_val_n[int];
                  // Total number of errors.
   int t_errs;
   initial t_errs = 0;
   final begin
      for ( int i=0; i<npsets; i++ )</pre>
        $write("Total errors for radix %2d: %5d len, %5d val\n",
               pset[i], t_errs_len_r[pset[i]],
               t_errs_val_r[pset[i]]);
      for ( int i=0; i<nnsets; i++ )</pre>
        $write("Total errors for string length %2d: %5d len, %5d val\n",
               nset[i], t_errs_len_n[nset[i]],
               t_errs_val_n[nset[i]]);
      for ( int i=0; i<nmsets; i++ )</pre>
        $write("Total errors for mod %4s: %5d len, %5d val\n",
               mtype_str[mset[i]], t_errs_len_mod[mset[i]],
               t_errs_val_mod[mset[i]]);
      $write("Total number of errors: %0d\n",t errs);
   end
   localparam int nsets = nnsets * npsets * nmsets;
   uwire d[nsets:-1]; // Start / Done signals.
   assign d[-1] = 1; // Initialize first at true.
```

```
// Instantiate a testbench at each size.
   11
   for ( genvar m=0; m<nmsets; m++ )</pre>
     for ( genvar n=0; n<nnsets; n++ )</pre>
       for ( genvar i=0; i<npsets; i++ )</pre>
         begin
            localparam int idx = m * npsets * nnsets + n * npsets + i;
            testbench r #(pset[i],nset[n],mset[m])
            t2( .done(d[idx]), .tstart(d[idx-1]) );
       end
endmodule
module testbench_r
  #( int r = 16, n = 3,
     M_Type mtype = M_proc )
   ( output logic done, input uwire tstart );
   localparam int w = $clog2(r**n);
   localparam int ntests = 500;
   localparam int wd = $clog2(n+1);
   uwire [wd-1:0] nd;
   uwire [w-1:0] val;
   logic [7:0] str[n-1:0];
   string mtype_str[M_Type] =
          '{ M_proc:"atoi_pr", M_tree:"atoi_tr", M_iter:"atoi_it",
                M_tree_sol:"a_tr_sol", M_iter_sol:"a_it_sol" };
   case ( mtype )
     M_proc: atoi_pr #(r,n,w) a8( val, nd, str );
     M_tree: atoi_tr #(r,n,w) a8( val, nd, str );
     M_iter: atoi_it #(r,n,w) a8( val, nd, str );
     M_tree_sol: atoi_tr_sol #(r,n,w) a8( val, nd, str );
     M_iter_sol: atoi_it_sol #(r,n,w) a8( val, nd, str );
   endcase
```

```
logic [7:0] non_digit[256];
```

```
function string to_string(input logic [w-1:0] val);
```

for (int i=32; i<128; i++) begin</pre>

```
automatic string result = "";
if ( val == 0 ) result = "0";
while ( val ) begin
    automatic int d = val % r;
    automatic int v = d < 10 ? d + Char_0 : d - 10 + Char_A;
    val = val / r;
    result = { string'(v), result };
end
to_string = result;
endfunction
initial begin
automatic int nd_size = 0;
automatic int rm10 = r > 10 ? 10 : r;
automatic bit err_silent = testbench.t_errs > 10;
```

```
\leftarrow \rightarrow Fall 2022
                    \leftarrow \rightarrow Homework 2
                                                   Homework Sol Code
              if ( i >= Char_0 && i < Char_0 + rm10 ) continue;</pre>
              if ( i >= Char_A && i < Char_A + r - 10 ) continue;</pre>
              if ( i >= Char_a && i < Char_a + r - 10 ) continue;</pre>
              non_digit[nd_size++] = i;
          end
          wait( tstart );
          for ( int tt=0; tt<3; tt++ ) begin</pre>
              automatic bit single_char = tt == 0;
              automatic bit space_pad = single_char || tt == 1;
              automatic int nttests = single_char ? r : ntests;
              automatic int n_err = 0, n_lerr = 0;
              automatic string ttype =
                single_char ? "Single_Char (SC)"
                  : space_pad ? "Space_Pad (SP)" : "General (GE)";
              automatic string abbrev =
                single_char ? "SC" : space_pad ? "SP" : "GE";
              // $write("Radix %2d, starting %s tests.\n", r, ttype);
          for ( int i=0; i<nttests; i++ ) begin</pre>
              automatic int len = single_char ? 1 : 1 + {$random} % n;
              automatic logic [w-1:0] sval = 0;
              for ( int j=0; j<len; j++ ) begin</pre>
                 automatic int d = {<u>$random</u>} % r;
                 automatic int char_a = {$random} % 1 ? Char_A : Char_a;
                 if ( d == 0 && j == len - 1 ) d = 1;
                 if ( single_char ) d = i;
                 str[j] = d < 10 ? Char_0 + d : char_a + d - 10;</pre>
                 sval += d * r ** j;
              end
              str[len] = space_pad ? " " : non_digit[{<u>$random</u>}%nd_size];
              for ( int j=len+1; j<n; j++ )</pre>
                str[j] = space_pad ? 32 : 32 + {<u>$random</u>}%(128-32);
              #1;
              if ( sval !== val ) begin
                 n err++;
                 if ( !err_silent && n_err < 5 )</pre>
                   $write("Mod-%s R-%2d n-%2d Ty-%s Error val %s != %s (correct) for string \"%s\"\n",
                           mtype_str[mtype], r, n, abbrev, to_string(val), to_string(sval), string'(str));
              end
              if ( !single_char && len !== nd ) begin
                 n_lerr++;
                 if ( !err_silent && n_lerr < 10 )</pre>
                   $write("Mod-%s R-%2d n-%2d Ty-%s Error len %0d != %0d (correct) for string \"%s\"\n",
                          mtype_str[mtype],
                           r, n, abbrev, nd, len, string'(str) );
              end
```

#1;

```
\leftarrow \ \rightarrow \ \text{Fall} \ 2022
                     \leftarrow \ \rightarrow \ \text{Homework} \ 2
                                                       Homework Sol Code
                      mtype_str[mtype],
                   r, n, abbrev, nttests, n_err, n_lerr);
                  testbench.t_errs += n_err + n_lerr;
              testbench.t_errs_len_mod[mtype] += n_lerr;
              testbench.t_errs_val_mod[mtype] += n_err;
              testbench.t_errs_len_r[r] += n_lerr;
              testbench.t_errs_val_r[r] += n_err;
              testbench.t_errs_len_n[n] += n_lerr;
              testbench.t_errs_val_n[n] += n_err;
              if ( n_err + n_lerr ) err_silent = 1;
           end
           done = 1;
       end
```

// cadence translate_on

LSU EE 4755

Homework 3 soluDule: 17 Oct 2022, 11:30 CDT

Resources

To help with this assignment review the simple cost model slides and the material in generate statement demo code.

The following problems ask for both inferred hardware and a cost/performance analysis: 2019 Midterm Exam Problem 3c (equality module with shifted inputs), 2021 Midterm Exam Problem 2 (a concentrator for neural network hardware reading sparse weights).

The following are good cost and performance analysis questions (these are the same ones mentioned in the simple model slides): The "find oldest" (big mux) problem covered in class can be found in 2017 Final Exam Problem 3, the knapsack problem hardware covered in class can be found in 2016 Final Exam Problem 2 and 4.

The following are good inferred hardware and optimization problems. Start with 2019 Midterm Exam Problem 1 (a recursively described clz [count leading zeros] module). A problem combining both recursive and iterative generate statements can be found in 202 Midterm Exam Problem 4.

A sequential version of the ASCII-to-value hardware was also assigned in this course. The hardware was described by procedural code and it operated sequentially, so I don't suggest that it specifically be studied for clues on how to solve this assignment.

Problem 1: Compute the cost and delay, using the simple model, of the atoi1 module (from the solution to Homework 1) instantiated with r=12. Base this on a module with reasonable optimizations applied and be sure to account for constants when computing cost and delay.

- Base your analysis of ripple implementations of the adder and magnitude comparison units.
- Show cost.
- Show delay of each output and identify the critical path.
- Account for constants when computing cost and delay.

```
module atoi1
```

```
#( int r = 32, w = $clog2(r) )
 ( output logic [w-1:0] val, output logic is_digit,
    input uwire [7:0] char );
logic [w-1:0] val_09, val_az, val_n;
logic is_09, is_az;
digit_valid_09 #(r,w) v09( is_09, val_09, char );
uwire [7:0] char_uc;
char_to_uc tuc(char_uc,char);
digit_valid_az #(r,w) vaz( is_az, val_az, char_uc );
uwire [w-1:0] z = 0;
mux2 #(w) mval(val_n,is_09,val_az,val_09);
mux2 #(w) mval0(val,is_digit,z,val_n);
```

```
assign is_digit = is_09 || is_az;
endmodule
typedef enum
  { Char_0 = 48, Char_9 = 57, Char_A = 65, Char_Z = 90, Char_a = 97, Char_z = 122 }
  Chars_Special;
module digit valid 09
  \#( int r = 9, vw = \frac{1}{2}(r) )
   ( output uwire valid, output uwire [vw-1:0] val, input uwire [7:0] char );
   assign val = char - Char_0;
   assign valid = char >= Char_0 && char <= Char_9 && char < Char_0 + r;
endmodule
module char to uc( output uwire [7:0] uc, input uwire [7:0] c );
   uwire is_lc = c >= Char_a && c <= Char_z;</pre>
   uwire [7:0] uc_if_lc = c - Char_a + Char_A;
   mux2 #(8) m( uc, is_lc, c, uc_if_lc );
endmodule
module digit_valid_az
  \#( int r = 11, vw = \frac{1}{clog2(r)}
   ( output uwire valid, output uwire [vw-1:0] val, input uwire [7:0] char );
   assign val = 10 + char - Char_A;
   assign valid = char >= Char_A && char < Char_A + r - 10;</pre>
endmodule
module mux2
  #(int w = 3)
   ( output uwire [w-1:0] x,
     input uwire s, input uwire [w-1:0] a0, a1 );
   assign x = s ? a1 : a0;
```

To start the solution, lets review the cost and delay of common components using the simple model. Those are shown below using symbols u_c for unit of cost and u_t for unit of time. For brevity those symbols are omitted in most of the analysis.

A w-Bit Ripple Adder. Cost: $9w u_c$. Delay: $4 u_t$ (ISD), $2(w+1) u_t$ (MSD).

A w-Bit Ripple Adder with One Constant Input. Cost: $4w u_c$. Delay: $2 u_t$ (ISD), $w u_t$ (MSD).

A w-Bit Integer Magnitude Unit (Computes a > b, a < b.) Cost: $4w u_c$. Delay: $2w + 1 u_t$.

A w-Bit Integer Magnitude Unit with One Constant Input Cost: w uc. Delay: w ut.

In the pages that follow the Verilog descriptions of **atoi** and the modules that it instantiates include comments that show the cost and delay analysis. The words **Cost** and **Delay** are prefixed with abbreviations that indicate the degree of optimization applied. Those abbreviations are:

N, No Optimization.

c0, Use constant-input cost or delay formulae for the particular device, but make no further optimizations.

B, Apply basic optimizations. This includes using the constant-input formulae and making further obvious optimizations.
 G, Apply good optimizations. These may require careful examination of the computation being performed on that line of Verilog code or an understanding of how the result of the computation is used elsewhere.



```
module char_to_uc( output uwire [7:0] uc, input uwire [7:0] c );
  uwire is_lc = c >= Char_a && c <= Char_z;</pre>
  // n Cost: 4*8
                            1
                                4*8
                                                          = 65
  // B Cost: 1*8
                            1 1*8
                                                          = 17
  // B Delay: 1*8
                           1 {1*8}
                                                          = 9
  uwire [7:0] uc_if_lc = c - Char_a + Char_A;
  // n Cost:
                        9*8
  // c0 Cost:
                        4*8
  // B Cost:
                       4*3
                               // Five LSB of (-Char_a+Char_A) are zero.
  // B Delay:
                        1*3
  mux2 #(8) m( uc, is_lc, c, uc_if_lc );
  // B Cost: 3*8
  // B Delay: 2
  /// Module, Basic Optimization
  // B Cost 17+12+24 = 53 u_c
  // B Critical path: is_lc -> mux : 9 + 2 = 11 u_t
  /// Good Optimization
  11
  uwire is_lc = c[7:5] == 3'b011 && c[4:0] >= 5'b1 && c[4:0] <= 5'b11010;
  // G Cost:
                      3
                               1 1*5 1 1*5 = 15
  // G Delay:
                      {2}
                                1
                                         3
                                                1
                                                     {3} = 5
  assign uc = { char[7:6], char[5] && !is_lc, char[4:0] };
  // G Cost:
              0
                                 1
                                       0
  // G Delay:
                                  1
  /// Module, Good Optimization
  // G Cost = 15 u_{\rm c}
  // G Delay = 5 u_t
```

```
endmodule
```

```
module digit_valid_09
 #( int r = 9, vw = \frac{clog2(r)}{r} )
  ( output uwire valid, output uwire [vw-1:0] val, input uwire [7:0] char );
  assign val = char - Char_0;
  // N Cost: 9*8
  // c0 Cost:
               1*8
  // B Cost: 1*4 (Note: -Char_0 = 8'b11010000, so only adding 4 bits.)
  // B Delay: 1*4
  assign valid = char >= Char_0 && char <= Char_9 && char < Char_0 + r;</pre>
  // N Cost: 4*8
                       1 4*8
                                         1 4*8
                                                           = 98
                             1 1*8
  // B Cost:
                                               1 1*8
                                                           = 26
                1*8
  // B Delay: 1*8
                             1 {1*8}
                                               1 \{1*8\} = 10
 /// Module, Basic Optimization
 // B Cost: 4+26 = 30 u<sub>c</sub>
 // B Delay: = 10 u_t (Valid output)
                = 4 u_t (Val output)
 // B Delay:
 /// Good Optimizations
 11
 assign val = char[3:0]; // val can be anything if char isn't 0-9
 // G Cost:
                0
 // G Delay:
                 0
 assign valid = char[7:4] == 4'h3 & & char[3:0] < 10;
 // Cost:
                3
                                 1
                                     1*4
                                                           = 8
 11
      Delay
                {2}
                                                           = 5
                                 1
                                     4
 assign valid = char[7:4] == 4'h3 && ( !char[3] || !char[2] && !char[1] );
 // G Cost:
                                                        1 = 6
                 3
                                 1
                                              1
               {2}
 // G Delay:
                                 1
                                               1
                                                         1 = 3
```

/// Module, Good Optimization

// G Cost: = 6 $u_{\rm c}$ // G Delay: = 3 $u_{\rm t}$ (Valid output) // G Delay: = 0 $u_{\rm t}$ (Val output) endmodule

```
module digit_valid_az
  #( int r = 11, vw = (clog2(r))
   ( output uwire valid, output uwire [vw-1:0] val, input uwire [7:0] char );
   assign val = 10 + char - Char_A;
  // N Cost:
                  9*8
   // B Cost:
                  4*8
                                             = 32
   // B Delay:
                  1*8
                                             = 8
  assign valid = char >= Char_A && char < Char_A + r - 10;</pre>
   // N Cost:
                  4*8
                                 1 4*8
  // B Cost:
                  1*8
                                 1 1*8
                                             = 17
   // B Delay:
                  1*8
                                 1
                                      \{1*8\} = 9
  /// Module, Basic Optimization
   // B Cost = 48 u_c
  // B Delay = 9 u_t
   /// Good Optimizations (Optimized for r = 12).
   assign valid = char[7:2] == 6'b010000 && ( char[1:0] == 2'b1 || char[1:0] == 2'b2 )
  // G Cost:
                  6
                                          1
                                                1
                                                                 1 1 = 10
   // G Delay:
                                                {1}
                                                                 \{1\}\ \{1\}\ =\ 4
                  3
                                          1
   assign val = { (vw-1)'b101, char[0] };
   // G Cost:
                  0
   // G Delay:
                  0
```

```
/// Module, Good Optimization
```

// G Cost = 10 u_c // G Delay = 4 u_t (Valid output) // G Delay = 0 u_t (Val output)

endmodule

```
atoi1
                                                               Timing for basic optimization
module atoi1
                                                     11
                                                                      8
                                                                                         21
  #(int r = 32,
                                                                               val az
                                                                                              22
                                                char to uc
                                                                  d val az
     int w = (clog2(r))
                                                                              is_az 19
   ( output uwire [w-1:0] val,
                                                                                               ۲a
                                     char
     output uwire is_digit,
                                                                      Q
                                                     4
                                      <del>'8</del>''
     input uwire [7:0] char );
                                                                     4
                                                              val 09
                                                 d val 09
                                                                                        1
                                                              is 09
   // Analysis for r = 12 ...
                                                                     10
   // ... therefore w = 4
                                                     10
                                                                                               digit
                                                                                20
   uwire is_09, is_az;
                                                                                               S
   uwire [w-1:0] val_09, val_az, val_n;
   digit_valid_09 #(r,w) v09( is_09, val_09, char );
   // B Cost: 30 Delay: 10 (is_09), 4 (val_09)
   uwire [7:0] char_uc;
   char_to_uc tuc(char_uc,char);
   // B Cost: 53 Delay: 11
   digit_valid_az #(r,w) vaz( is_az, val_az, char_uc );
   // B Cost: 48 Delay: 9 (is_az), 8 (val_az)
   uwire [w-1:0] = 0;
   mux2 #(w) mval( val_n, is_09, val_az, val_09 );
   // B Cost: 3*w = 3*4 = 12
   // B Delay: 2
   mux2 #(w) mval0( val, is_digit, z, val_n );
   // N Cost: 3*w = 3*4 = 12
   // B Cost: 1*w = 1*4 = 4
                                   (One input is zero.)
   // B Delay: 1
   assign is_digit = is_09 || is_az;
   // B Cost 1, Delay 1
   /// Module, Basic Optimization
   // B Cost: 30 + 53 + 48 + 12 + 12 + 1 = 156 u_c
   // B A Critical Path: char 
ightarrow char_uc 
ightarrow is_az 
ightarrow is_digit 
ightarrow val
   // B Delay: 11 + 9 + 1 + 1 = 22 u<sub>t</sub>
   // B A Critical Path: char \rightarrow char_uc \rightarrow val_az \rightarrow val_n \rightarrow val
   // B Delay: 11 + 8 + 2 + 1 = 22 \mathrm{u_t}
```

Problem 2: Appearing further below is the atoi_it from the solution to Homework 2. (a) Show the hardware inferred for an atoi_it module instantiated with r=14 (yes, radix 14) and n=3.

- Show atoi1, mult_by_c, and add instances as modules, do not show what is inside.
- Show the hardware inferred for the operators, such as && and ?:.
- Do not confuse parameters and ports.
- Omit hardware that does not belong, such as "hardware" to compute values needed at elaboration time.
- Be sure to show the inferred logic. Remember that generate statements describe what happens at elaboration time, not what happens at simulation time nor does it describe operations performed by the hardware.

Solution on the next page.

Solution appears below. The first diagram shows the inferred logic and shows hardware that can easily be removed by optimization in gray. The hardware corresponding to each iteration of the generate loop is shown within a green dotted outline.

In the second diagram the easy optimizations are applied. One easy optimization is the $mult_by_c$ module instantiated with c=1. Since it would be multiplying by one the output would match the input, and so no hardware is needed. One input to the add module on the upper left is zero, so that adder isn't needed. An AND gate is also optimized out.





(b) Show the hardware inferred for an atoi_it module instantiated with r=16 (hexadecimal this time) and n=3, and show the hardware after optimization. Consider the impact of optimization on the mult_by_c and add modules, which should be considerable since r is a power of 2.

The solution appears below. The first diagram shows the inferred logic before optimization. The second diagram shows the optimized hardware, which is substantially less costly since both the mult_by_c and add modules can be eliminated.

The $mult_by_c$ modules can be eliminated because they are multiplying by a power of 2, which can be accomplished simply by re-labeling bit positions. The add modules can be eliminated because the two adder inputs will never have a 1 in the same bit position.

For example, consider ASCII input 24'h393635 which should decode to value 12'h965, in binary 12'b1001_0110_0101. For this input vali[0] = 0000_0000_0101 and for i=1, vald=0000_0110_0000. So all the i=1 adder really has to do is concatenate the high 8 bits of vald with the low 8 bits of vali[0]. No addition is necessary. That is shown in the optimized hardware, where each vald output is connected directly to their four bit positions in the module output.





```
module atoi it
 #( int r = 11, n = 5, wv = $clog2( r**n ), wd = $clog2(n+1) )
   ( output logic [wv-1:0] val,
     output logic [wd-1:0] nd,
    input uwire [7:0] str [n-1:0] );
   uwire [wv-1:0] vali[n-1:-1];
   uwire is_valid[n-1:-1];
   uwire [wd-1:0] ndi[n-1:-1];
   assign is_valid[-1] = 1;
   assign ndi[-1] = 0;
   assign vali[-1] = 0;
   assign nd = ndi[n-1];
   assign val = vali[n-1];
   localparam int wcv = $clog2(r);
   for ( genvar i=0; i<n; i++ ) begin</pre>
      // Find Value of Digit i
      11
      uwire [wcv-1:0] valdr;
      uwire is_digit;
      atoi1 #(r,wcv) a( valdr, is_digit, str[i] );
      // Determine if this digit continues a sequence of valid digits
      // starting at str[0].
      11
      assign is_valid[i] = is_digit && is_valid[i-1];
      // Replace value with zero if str[i] is not a digit, or if the
      // string of valid digits has already ended.
      11
      uwire [wcv-1:0] vald = is_valid[i] ? valdr : 0;
      // Multiply (scale) the digit value based on its position in the number.
      11
      uwire [wv-1:0] vals;
      mult_by_c #( .w_in(wcv), .c(r**i), .w_out(wv) ) mc( vals, vald );
      // Add the scaled digit to the value accumulated so far.
      11
      add #(wv) a1( vali[i], vali[i-1], vals );
      // Update the number of digits so far.
      11
      assign ndi[i] = is_valid[i] ? i+1 : ndi[i-1];
   end
endmodule
```

Problem 3: Appearing further below is the atoi_tr from the solution to Homework 2. Show the inferred logic for an instantiation with r=10 and n=9.

- Show the logic for one level. That is, show the two instantiations of atoi_tr, alo and ahi, but don't show what is inside of alo nor ahi.
- Show the mult_by_c instantiations as modules, do not show what is inside.
- Show the hardware inferred for the operators, such as && and ?:.
- Omit hardware that does not belong, such as "hardware" to compute values needed at elaboration time.
- Do not confuse parameters and ports.
- Be sure to show the inferred logic. Remember that generate statements describe what happens at elaboration time, not what happens at simulation time nor does it describe activities performed by the hardware.

Solution appears below. Note that the equality module and adder that operate on the nd outputs each have one constant input ndlo, which will result in lower-cost and faster hardware. Also note that the value of nlo here is 4, and that no hardware is shown computing it. The value is computed by the synthesis (or simulation) program at elaboration time and used to create the module.



```
module atoi_tr
 #( int r = 11, n = 5, wv = \frac{c\log^2(r**n)}{wd} = \frac{c\log^2(n+1)}{r})
   ( output uwire [wv-1:0] val, output var logic [wd-1:0] nd,
     input uwire [7:0] str [n-1:0] );
   if (n == 1) begin
      uwire is_dd;
      uwire [wv-1:0] valr;
      atoi1 #(r,wv) a( valr, is_dd, str[0] );
      assign val = is_dd ? valr : 0;
      assign nd = is_dd; // Note: nd may be more than one bit.
   end else begin
      // Prepare to split the input string into two halves. Note that
      // the hi half may be larger, and so we use nhi to compute the
      // number of bits needed in the value output (vwh) and the
      // number of digits output (dwh).
      11
      localparam int nlo = n/2;
      localparam int nhi = n - nlo;
      localparam int vwh = $clog2( r**nhi );
      localparam int dwh = $clog2( nhi+1 );
      //
      uwire [vwh-1:0] vallo, valhi;
      uwire [dwh-1:0] ndlo, ndhi;
      // Split input string between two recursive instantiations
      11
      atoi_tr #(r,nlo,vwh,dwh) alo( vallo, ndlo, str[nlo-1:0] );
      atoi_tr #(r,nhi,vwh,dwh) ahi( valhi, ndhi, str[n-1:nlo] );
      // Determine whether the hi half of the string may be part
      // of the number.
      11
      uwire hitoo = ndlo == nlo;
      uwire [vwh-1:0] valhid = hitoo ? valhi : 0;
      // Scale the upper half.
      11
      uwire [wv-1:0] valhis; // Value High Scaled
      mult_by_c #(vwh,r**nlo,wv) mc( valhis, valhid );
      assign val = vallo + valhis;
      assign nd = hitoo ? nlo + ndhi : ndlo;
   end
endmodule
```

```
//
/// LSU EE 4755 Fall 2022 Homework 4 -- SOLUTION
//
```

```
/// Assignment https://www.ece.lsu.edu/koppel/v/2022/hw04.pdf
```

```
typedef enum
{ Char_escape = 128, Char_escape_stop = 200, Char_EOS = 255,
    Char_A = 65, Char_Z = 90, Char_a = 97, Char_z = 122,
    Char_0 = 48, Char_9 = 57,
    Char_space = 32, Char_underscore = 95, Char_cr = 13
    } Chars_Special;
```

`default_nettype none

```
/// Problem1
11
/// Complete word_count as described in the handout.
///
11
11
      [*] Do not use more adders than are necessary, especially for len_avg.
11
11
      [<] Make sure that the testbench does not report errors.</pre>
      [ Module must be synthesizable. Use command: genus -files syn.tcl
11
11
11
      [<] Don't assume any particular parameter value.</pre>
11
      [✓] Code must be written clearly.
11
```

// [/] Pay attention to cost and performance.

module word_count

```
#( int wl = 5, wn = 6, n_avg_of = 10 )
( output logic word_start, word_part, word_ended,
    output logic [wl-1:0] len_word,
    output logic [wn-1:0] num_words,
    output logic [wl-1:0] len_avg,
    input uwire [7:0] char,
    input uwire reset, clk );

uwire char_az = char >= Char_a && char <= Char_z
    || char >= char_A && char <= Char_2;
uwire char_09 = char >= Char_0 && char <= Char_9;
uwire char_wd_start = char_az;
uwire char_wd_part = char_wd_start || char_09 || char == Char_underscore;</pre>
```

/// SOLUTION

```
logic prev_char_wd_part;
```

```
uwire next_word_start = char_wd_start && !prev_char_wd_part;
uwire next_word_part = word_part && char_wd_part || next_word_start;
uwire next_word_ended = word_part && !char_wd_part;
```

```
always_ff @( posedge clk ) begin
    prev_char_wd_part <= reset ? 0 : char_wd_part;
    word_start <= reset ? 0 : next_word_start;
    word_part <= reset ? 0 : next_word_part;
    word_ended <= reset ? 0 : next_word_ended;</pre>
```

end

```
logic [wl-1:0] len_recent[n_avg_of];
   logic [wl+<u>$clog2(n_avg_of):0] len_sum;</u>
   assign len_avg = len_recent[n_avg_of-1] ? len_sum / n_avg_of : 0;
   always_ff @ ( posedge clk ) if ( reset ) begin
      num_words <= 0;</pre>
      len_word <= 0;</pre>
      for ( int i=0; i<n_avg_of; i++ ) len_recent[i] = 0;</pre>
      len sum = 0;
   end else begin
      len_word <= next_word_start ? 1 : next_word_part ? len_word+1 : len_word;</pre>
      num_words <= next_word_ended ? num_words + 1 : num_words;</pre>
      if ( next_word_ended ) begin
         len_sum -= len_recent[n_avg_of-1];
         len_sum += len_word;
         for ( int i=n_avg_of-1; i>0; i-- ) len_recent[i] = len_recent[i-1];
         len recent[0] = len word;
      end
   end
endmodule
module word_count_blank
  #( int wl = 5, wn = 6, n_avg_of = 10 )
   ( output logic word_start, word_part, word_ended,
     output logic [wl-1:0] len word,
     output logic [wn-1:0] num_words,
     output logic [wl-1:0] len_avg,
     input uwire [7:0] char,
     input uwire reset, clk );
   uwire char_az = char >= Char_a && char <= Char_z</pre>
         || char >= Char_A && char <= Char_Z;</pre>
   uwire char_09 = char >= Char_0 && char <= Char_9;</pre>
```

endmodule

uwire char_wd_part = char_wd_start || char_09 || char == Char_underscore;

11

// It is okay to modify the testbench code to facilitate the coding

// and debugging of your modules. Keep in mind that your submission

// will be tested using a different testbench, so on the one hand no

// one will be accused of dishonesty for modifying the testbench

 $//\ensuremath{\left|}$ below. However be sure to restore any changes to make sure that

// your code passes the original testbench.

uwire char_wd_start = char_az;

// cadence translate_off

program reactivate

(output uwire clk_reactive, output int cycle_reactive,

```
input uwire clk, input var int cycle);
   assign clk_reactive = clk;
   assign cycle_reactive = cycle;
endprogram
module testbench;
   localparam int npsets = 3;
   localparam int pset[npsets][2] =
              \{ \{ 2, 5 \}, \{ 1, 6 \}, \{ 9, 7 \} \};
   int n_err_shown; // Number of times error info printed to console.
   int n_err_sh_nc, n_err_sh_nw, n_err_sh_avg, n_err_sh_state;
   initial begin
      n_err_sh_nc = 0;
      n_{err_sh_nw} = 0;
      n_err_sh_avg = 0;
      n_err_sh_state = 0;
   end
   int t_errs;
                    // Total number of errors.
   initial begin t_errs = 0; n_err_shown = 0; end
   final <u>$write("Total number of errors: %0d\n",t_errs);</u>
   uwire d[npsets:-1];
                          // Start / Done signals.
   assign d[-1] = 1; // Initialize first at true.
   // Instantiate a testbench at each size.
   11
   for ( genvar i=0; i<npsets; i++ )</pre>
     testbench n #(pset[i][0],pset[i][1]) t2( .done(d[i]), .tstart(d[i-1]) );
endmodule
module testbench_n
  #( int win_sz = 10, wd_len_max = 5 )
   ( output logic done, input uwire tstart );
   localparam int wl = <u>$clog2</u>(wd_len_max+1);
   localparam int wn = <u>$clog2(win_sz) + 5;</u>
   localparam int n_tests = 10000;
   localparam int cyc_max = n_tests * 2;
   // Number of starting trace lines shown.
   localparam int tr_initial_lines = 12;
   // Number of trace lines to show when there is an error.
   localparam int tr_err_context = 5;
   int seed;
   initial seed = 4755;
   function string sample( input string str );
      sample = str[ <u>$dist uniform( seed, 0, str.len()-1 ) ];</u>
   endfunction
   function string fbit( input logic b, input string s );
      fbit = b === 1 ? s : b === 0 ? "_" : b === 1'bx ? "x" : "z";
   endfunction
  bit clk;
   int cycle, cycle_limit;
   logic clk_reactive;
   int cycle_reactive;
```

```
reactivate ra(clk_reactive,cycle_reactive,clk,cycle);
string event_trace;
initial begin
   clk = 0;
   cycle = 0;
   event_trace = "";
   done = 0;
   cycle_limit = cyc_max;
   wait( tstart );
   fork
      while ( !done ) #1 cycle += clk++;
      wait( cycle >= cycle limit )
        <u>$write</u>("Exit from clock loop at cycle %0d, limit %0d. %s\n %s\n",
               cycle, cycle_limit, "** CYCLE LIMIT EXCEEDED **",
               event_trace);
   join_any;
   done = 1;
end
uwire [wl-1:0] len, lavg;
uwire [wn-1:0] nw;
uwire w_start, w_part, w_ended;
logic [7:0] char;
logic reset;
string test_one = "I II III 2not o_wd four cinco a b c d ";
// string test_one = "A or bee
                                    ";
word_count #(wl,wn,win_sz) wd_cnt
  (w_start, w_part, w_ended, len, nw, lavg, char, reset, clk);
bit char_wd_start[256];
bit char_wd_part[256];
string str_wd_start, str_wd_part, str_wd_notstart;
localparam string str_wd_not = " ,!.-";
int lens[$];
initial begin
   automatic logic [wl-1:0] shadow_nc = 0;
   automatic logic [wn-1:0] shadow_nw = 0;
   automatic logic [wl-1:0] shadow avg = 0;
   automatic int len_sum = 0;
   automatic int n_err_nc = 0, n_err_w_st=0, n_err_w_pa=0, n_err_w_en=0;
   automatic logic shadow_w_st, shadow_w_pa, shadow_w_en;
   automatic int n_err = 0, n_err_lavg = 0, n_err_nw = 0;
   automatic int str_idx = 0;
   automatic string str_win = {10{" "}};
   automatic string test_str_buffer;
   automatic int n_err_pre;
   automatic logic pw_start, pw_part, pw_ended; // State before + edge.
   automatic string tr_recent[$];
   automatic bit need reset = 0;
   bit in_word, was_in_word, was_word_char;
   for ( int i=0; i<256; i++ )</pre>
     begin char_wd_start[i] = 0; char_wd_part[i] = 0; end
   for ( int i=Char_a; i<=Char_z; i++ )</pre>
     begin
```

char_wd_start[i] = 1; char_wd_part[i] = 1;

```
end
for ( int i=Char_A; i<=Char_Z; i++ )</pre>
  begin
     char_wd_start[i] = 1; char_wd_part[i] = 1;
  end
for ( int i=Char_0; i<=Char_9; i++ ) char_wd_part[i] = 1;</pre>
char_wd_part[Char_underscore] = 1;
for ( int i=0; i<256; i++ ) begin</pre>
   if ( !char_wd_start[i] && char_wd_part[i] )
     str_wd_notstart = { str_wd_notstart, string'(byte'(i)) };
   if ( char_wd_start[i] )
     str_wd_start = { str_wd_start, string'(byte'(i)) };
   if ( char_wd_part[i] )
     str_wd_part = { str_wd_part, string'(byte'(i)) };
end
test_str_buffer = { test_one, test_one };
str_idx = 0;
in_word = 0;
was_in_word = 0;
was_word_char = 0;
char = Char A;
reset = 1;
@( posedge clk_reactive ); @( posedge clk_reactive );
reset = 0;
for ( int i=0; i<n_tests; i++ ) begin</pre>
   automatic int round = i / test_one.len();
   automatic bit do_reset =
     round == 1 && <u>$dist_uniform</u>(seed,1,7) == 1
       || round > 1 && <u>$dist uniform(seed,1,(wd_len_max+4)/2*win_sz*2)==1;</u>
   automatic bit show_err = 0;
   @( negedge clk );
   if ( str_idx >= test_str_buffer.len() ) begin
      automatic int wd_sz = <u>$dist uniform(seed,1,wd_len_max);</u>
      automatic int wd_ws = <u>$dist uniform</u>(seed,1,4);
      automatic bit fake_word = <u>$dist_uniform(seed,1,10) == 1;</u>
      test_str_buffer = "";
      str_idx = 0;
      if ( fake_word )
        test_str_buffer = { test_str_buffer, sample( str_wd_notstart ) };
      else
        test_str_buffer = { test_str_buffer, sample( str_wd_start ) };
      for ( int j=1; j<wd_sz; j++ )</pre>
        test_str_buffer = { test_str_buffer, sample( str_wd_part ) };
      for ( int j=0; j<wd_ws; j++ )</pre>
        test_str_buffer = { test_str_buffer, sample( str_wd_not ) };
   end
   reset = do_reset;
   char = test_str_buffer[str_idx++];
   if ( round < 1 ) begin
   end else begin
```

```
end
str_win = { str_win.substr(1,9), char };
pw_start = w_start;
pw_part = w_part;
pw_ended = w_ended;
@( posedge clk_reactive );
if ( do_reset ) begin
   was_in_word = 0;
   was_word_char = 0;
   in_word = 0;
   shadow_w_en = 0;
   shadow_w_pa = 0;
   shadow_w_st = 0;
end else begin
   was_in_word = in_word;
   shadow_w_st = !was_word_char && char_wd_start[char];
   in_word =
     was_in_word && char_wd_part[char] || shadow_w_st;
   shadow_w_pa = in_word;
   shadow_w_en = was_in_word && !in_word;
   was_word_char = char_wd_part[char];
end
if ( do_reset ) begin
   shadow_nc = 0;
   shadow_nw = 0;
   shadow_avg = 0;
   lens.delete();
   len_sum = 0;
end else if ( was_in_word && in_word ) begin
   shadow_nc++;
end else if ( shadow_w_en ) begin
   shadow_nw++;
   len_sum += shadow_nc;
   lens.push_front(shadow_nc);
   if ( lens.size() > win_sz )
     len_sum -= lens.pop_back();
   if ( lens.size() == win_sz )
     shadow_avg = len_sum / win_sz;
end else if ( shadow_w_st ) begin
   shadow_nc = 1;
end
n_err_pre = n_err;
if ( w_start !== shadow_w_st ) begin
   n_err_w_st++;
   n_err++;
end
if ( w_part !== shadow_w_pa ) begin
   n_err_w_pa++;
   n_err++;
end
```

```
if ( w_ended !== shadow_w_en ) begin
     n_err_w_en++;
     n_err++;
   end
   if ( n_err_pre != n_err ) begin
      if ( testbench.n_err_sh_state++ < 4 ) show_err = 1;</pre>
  end
  if ( shadow_nw !== nw )
    begin
        n_err_nw++; n_err++; need_reset = 1;
        if ( testbench.n_err_sh_nw++ < 4 ) show_err = 1;</pre>
    end
   if ( shadow_avg !== lavg )
    begin
        n_err_lavg++; n_err++; need_reset = 1;
        if ( testbench.n_err_sh_avg++ < 4 ) show_err = 1;</pre>
    end
  if ( shadow_nc !== len ) begin
      n_err_nc++; n_err++;
      if ( testbench.n_err_sh_nc++ < 4 ) show_err = 1;</pre>
  end
  begin
      automatic string hd =
       " W-M I Text--->|
                                        SPELNA {D}";
      automatic string item =
        $sformatf
          ("Trace %2d-%1d %4d \"%10s\" %s %s%s%s %s%s%s %1d %2d %1d {%1d}",
          win_sz, wd_len_max, i, str_win,
           do_reset ? "R" : " "
           fbit(pw_start,"s"), fbit(pw_part,"p"), fbit(pw_ended,"e"),
           fbit(w_start,"S"), fbit(w_part,"P"), fbit(w_ended,"E"),
           len, nw, lavg,
           wd_cnt.char_az
           );
      if ( n_err != n_err_pre )
        item =
          { item,
            $sformatf(" <-Error Correct-> %s%s%s %1d %2d %1d",
                      shadow_w_st ? "S" : "_", shadow_w_pa ? "P" : "_",
                      shadow_w_en ? "E" : "_",
                      shadow_nc, shadow_nw, shadow_avg) };
      if ( i == 0 ) <u>$write("%s\n",hd);</u>
      if ( i 
        $write("%s\n",item);
      else begin
         if ( tr_recent.size() > tr_err_context ) tr_recent.delete(0);
         tr_recent.push_back(item);
      end
  end
   if ( n_err != n_err_pre && show_err ) begin
     while ( tr_recent.size() > 0 )
        $write("%s\n",tr_recent.pop_front());
  end
end
```

\$write
("Done with n_avg_of=%0d, max wd len=%0d. Errors: st %0d, pa %0d, en %0d, nc %0d, nw %0d, av %0d\n",
win_sz, wd_len_max,

```
n_err_w_st, n_err_w_pa, n_err_w_en,
```

```
n_err_nc, n_err_nw, n_err_lavg);
```

```
testbench.t_errs += n_err;
done = 1;
```

end

endmodule

// cadence translate_on

Homework 5 solution Due: 22 November 2022

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2022/hw05.v.html.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account, copy the assignment, and run the Verilog simulator and synthesis program on the unmodified homework file, hw05.v. Do this early enough so that minor problems (*e.g.*, password doesn't work) are minor problems.

Assignment Background

LSU EE 4755

As we should know the synthesis program, given a Verilog description of a module, writes a design file with an optimized version of the module mapped to the chosen technology. For this assignment the chosen technology is the same Oklahoma University ASIC process we've been using throughout the semester.

An important skill for those writing Verilog descriptions is to estimate the cost and performance of those synthesized modules. In this assignment we'll look at how well the synthesis program handles the different modules we considered for computing the floating-point expression $v_0^2 + v_0 v_1 + v_1^2$. We will consider the combinational, sequential, and pipelined modules covered in class.

A synthesis script will be used to synthesize these modules, plus three arithmetic unit modules, plus additional modules created for the solution to this problem. To complete the assignment the output of the script must be understood and the synthesis script must be modified. The output of the synthesis script is similar to the output of the scripts used in prior assignments, so it should be familiar. Modifying the script will be something new, and might be a challenge for some of you. It is okay to seek help modifying the script from classmates and others, though the solutions to the problems themselves must be completed individually.

Modules

This assignment includes modules for the combinational, sequential, and pipelined implementations of the multi-step computation. They are named ms_comb, ms_seq, and ms_pipe. For comparison the assignment also includes modules containing a single floating-point unit, they are named try_mult, try_add, and try_sq (square).

Four additional modules are provided for experimentation, $m1_func$, $m1_comb$, $m1_seq$, and $m1_pipe$. These modules initially perform the computation $v_0 + v_0v_1 + v_1^2$, but they can be modified to perform other computations. Module $m1_func$ is used by the testbench to obtain a correct value, so modify it first so that it computes the desired computation. Then modify the others that you want to synthesize. (The synthesis program does not care whether a module passes the testbench, but no conclusion can be drawn from the area and delay of module that does not work correctly.)

All of these modules have the same parameters and ports, though not every module uses every port. For example, only ms_seq and ms_pipe are sequential so that the clk and reset ports on the others serve no function. These unused ports will be eliminated during optimization so they won't affect cost or timing.

Module Parameters and Floating Point Format

The modules used in this assignment all have the same parameters, these parameters specify the floating-point number format to be used. The first parameter, wsig, specifies the number of bits in the significand (fractional part) of the floating point number. The default value is 23, which is the same as an IEEE 754 single (C float). The second parameter, wexp, is the number of bits in the exponent. The default value is 8, which matches an IEEE single. The third parameter, ieee, specifies whether the IEEE floating-point format should be strictly followed. The default value
is 1, which means yes; a 0 means that special cases do not have to be handled correctly. These include NaN (not a number) and subnormal values. The size of the floating point number using these parameters is 1+wexp+wsig, the extra 1 is for the sign bit.

For this assignment all modules are instantiated with ieee=0. This is done to explore the fuller range of optimization possibilities and also to reduce the time needed for synthesis.

The sample synthesis runs consider two formats, IEEE single in which wsig=23 and wexp=8, and the ML-friendly BF16 (informally known as brain float) in which wsig=7 and wexp=8. The advantage of BF16 for machine learning is that it is half the size of a single, and with a 7-bit significand, requires half the energy for multiplication than the older 16-bit FP16 format. For us the big advantage is that it takes less time to synthesize than a single.

Testbench

The testbench exercises the six modules, ms_comb, ms_seq, ms_pipe, m1_comb, m1_seq, and m1_pipe instantiated with a significand size of 7 and 23. They should all initially pass. As with other testbenchs in this class, a line will be printed for the first few module errors, and a tally will be provided for each module and size. The testbench uses ms_func to determine the correct output of the ms modules and m1_func to determine the correct output of the m1 modules. When modifying the m1 modules be sure to also modify m1_func so that the testbench can show you whether your modified modules do what you think they are doing.

The Synthesis Script

As with past assignments, the modules in the assignment file should be synthesized using the script syn.tcl. Unlike other assignments, this script will have to be modified.

The synthesis script itself is written in TCL (Tool Control Language, the abbreviation is pronounced tickle) a scripting language chosen by Cadence for scripting their EDA software. (Nowadays Python would be used. If it were up to me it would be Perl. But it's TCL.) Documentation for TCL can be found at https://tmml.sourceforge.net/doc/tcl/. This describes TCL, not the functionality needed to run Genus or other tools. For Genus-specific commands see the synthesis documentation linked to https://www.ece.lsu.edu/koppel/v/ref.html.

For this assignment it should not be necessary to use new Genus commands, just to change which modules are synthesized and which parameters to instantiate with. For that, one needs only a rudimentary knowledge of TCL, perhaps what can be learned just by looking at syn.tcl.

The synthesis script starts by setting some script variables, using the TCL set command, and by setting Genus attributes, using the Genus set_db command:

```
set verilog_source hw05.v
set syn_level "high"
set spew_file "spew.log"
set report_file "syn-report.log"
set_db syn_global_effort $syn_level
set rpt_chan [open $report_file w]
puts "Synthesizing at effort level \"$syn_level\"\n"
```

As one might guess syn_level is the amount of effort used for synthesis. Possible values are none, low, medium, and high. These initial lines are followed by the definition of a TCL procedure syn_mod, which emits the commands needed to synthesize a module, followed by commands to retrieve the area and delay of the synthesized module. A line of text is written showing the area and delay. It should not be necessary to modify syn_mod for this assignment.

Module syn_mod is called in a loop nest near the end of the file:

[#] List of combinational modules.

```
set mods_comb { ms_comb try_mult try_add try_sq }
set delay_targets { 100 0.1 }
set mods { try_mult try_add try_sq }
set mods { ms_comb ms_seq ms_pipe try_mult try_add try_sq }
set wsigs { 7 14 23 }
foreach delay_target $delay_targets {
    foreach ws $wsigs {
        foreach mod $mods {
            syn_mod $mods {
            syn_mod $mod $delay_target " $ws 8 0 "
            }
      }
}
```

The loop nest above synthesizes each of the modules listed in mods (that's the inner loop). Each of these six modules is synthesized for each significand size found in wsigs. These modules are synthesized with each delay constraint in delay_target. For the code above there would be a total of $2 \times 6 \times 3$ synthesis runs. That would probably take hours.

The first set line writes variable mods_comb with a list of combinational modules. This variable must be updated with any new combinational modules that you use. Variable mods is set twice, first to a list of the arithmetic modules, then those are replaced with a list of the arithmetic modules and our multi-step modules. (Because of the second assignment the first assignment has no effect.) If one wanted to only synthesize the arithmetic modules one would comment out the second mods line. There is no need to use a loop nest. It is possible to write a syn_mod call for each synthesis, for example:

```
set delay_targets { 100 }
set wsigs { 7 14 23 }
syn_mod try_mult 5 "7 8 0"
syn_mod try_mult 5 "7 6 0"
# Exit before the loop nest.
close $rpt_chan
quit
foreach delay_target $delay_targets {}
```

The example above does two synthesis runs. The 5 is the delay target and the quoted part are the parameters. (The parameters must be quoted so that they are read as a single argument to syn_mod.) In the example above, try_mult is synthesized with two exponent sizes, 8 bits and 6 bits, both are synthesized with a delay target of 5 ns.

To synthesize a new module (for example, one you wrote) add the name to one of the mod lists, or just use the name on a direct call to syn_mod as in the example above. Iff the module is combinational add the module to mods_comb. Not adding a combinational module to mods_comb will result in an error. Adding a sequential module to mods_comb will result in incorrect timing.

Synthesis Script Output

The synthesis script syn.tcl is run using the command genus -files syn.tcl. The run starts with a substantial amount of header output, including warnings, copyright information, and system information. Some is shown below:

[cyc.ece.lsu.edu] % genus -files syn.tcl

2022/11/13 16:52:05 WARNING This OS does not appear to be a Cadence supported Linux configuration. 2022/11/13 16:52:05 For more info, please run CheckSysConf in <cdsRoot/tools.lnx86/bin/checkSysConf <productId> TMPDIR is being set to /tmp/genus_temp_566634_cyc.ece.lsu.edu_koppel_nvftYI Cadence Genus(TM) Synthesis Solution. Copyright 2022 Cadence Design Systems, Inc. All rights reserved worldwide. Cadence and the Cadence logo are registered trademarks and Genus is a trademark of Cadence Design Systems, Inc. in the United States and other countries.

[16:52:12.338826] Configured Lic search path (21.01-s002): /apps/linux/cadence/share/license/license.dat:/opt/pgi/license.dat

The output of the script proper (as opposed to Genus, the synthesis program) starts with an announcement of the synthesis effort level followed by a table of synthesis results:

Synthesizing at effort level "high"

Module Name	Area	Delay	Delay	Synth
		Actual	Target	Time
ms_comb_wsig7_wexp8_ieee0	600190	12.219	0.1 ns	423 s
ms_seq_wsig7_wexp8_ieee0	445400	5.754	0.1 ns	236 s
ms_pipe_wsig7_wexp8_ieee0	797327	5.678	0.1 ns	309 s
ms_comb_wsig14_wexp8_ieee0	1363980	14.391	0.1 ns	707 s

Each line of the table shows the result of one synthesis run. The Module Name column shows the name of the module followed by the parameter values used in its instantiation. In the sample above three different modules are synthesized, ms_comb, ms_seq, and ms_pipe. Module ms_comb is synthesized once with significand of 7 bits and once with a significand of 14 bits.

The Area column shows the area given by the Genus report area command. The units are relative to the OSU technology. The Delay Actual column shows the length of critical path through the module in units of nanoseconds. The Delay Target column shows the delay constraint that the synthesis program was set to meet. In the example above the constraint is 0.1 ns, which means the critical path can be no longer than 0.1 ns. This constraint was intentionally set to an impossibly low value, to determine the minimum delay that the synthesis program could achieve. Normally the delay constraint is set to something achievable, perhaps 4 ns in the example above, and the synthesis program would generate the least expensive design that meets the delay constraint. The Synth Time column shows the wall-clock (elapsed) time needed to perform the synthesis. The wall-clock time is shown to help plan the synthesis runs, it does not directly affect or describe the design itself.

Problem 1: In class we considered three ways of implementing multi_step, the modules that computed $v_0^2 + v_0v_1 + v_1^2$: A combinational version, a sequential version, and a pipelined version. Appearing below are the results from synthesizing these three modules, named ms_comb, ms_seq, and ms_pipe, followed by results of synthesizing modules consisting only of the Chipware floating-point multiplier, adder, and a multiplier with the same value used for both operands. These are synthesized with a large delay constraint, meaning that the cost has been minimized.

Module Name	Area	Delay	Delay	Synth
		Actual	Target	Time
ms_comb_wsig23_wexp8_ieee0	1597692	75.142	100.0 n	s 229 s
ms_seq_wsig23_wexp8_ieee0	<mark>94</mark> 5919	29.324	100.0 n	s 111 s
ms_pipe_wsig23_wexp8_ieee0	1866509	28.273	100.0 n	s 205 s
try_mult_wsig23_wexp8_ieee0	525991	28.231	100.0 n	s 62 s
try_add_wsig23_wexp8_ieee0	339036	27.396	100.0 n	s 53 s
try_sq_wsig23_wexp8_ieee0	297753	25.504	100.0 n	s 38 s
ms_comb_wsig7_wexp8_ieee0	375767	34.708	100.0 n	s 75 s
ms_seq_wsig7_wexp8_ieee0	275858	15.305	100.0 n	s 34 s
ms_pipe_wsig7_wexp8_ieee0	526000	14.466	100.0 n	s 62 s
try_mult_wsig7_wexp8_ieee0	94274	9.346	100.0 n	s 13 s
try_add_wsig7_wexp8_ieee0	140221	14.196	100.0 n	s 21 s
try_sq_wsig7_wexp8_ieee0	57802	6.085	100.0 n	s 8s

(a) Based on the data above, show the latency and throughput of each module for the 23-bit significand. It might be necessary to look at the module descriptions (Verilog code) to answer this question.

In the discussion below call the value in the **Delay Actual** column of the synthesis results table the *clock* period and let t_c denote its value. For example, for ms_comb with the 23-bit significand the clock period is $t_c = 75.142 \text{ ns.}$ Also, let L denote latency and θ denote throughput.

Combinational Module, ms_comb: Latency: $L = t_c = 75.142 \text{ ns}$ and throughput $\theta = \frac{1}{t_c} = \frac{1}{75.142 \text{ ns}}$. The combinational module computes the entire result in one cycle and so the clock period is the latency. It can compute a new result every cycle and so the throughout is the reciprocal of the latency.

Sequential Module, ms_seq: Latency: $L = n_c t_c = 5 \times 29.324 \,\mathrm{ns} = 146.62 \,\mathrm{ns}$, where n_c is the number of cycles needed to compute a result. Throughput: $\theta = \frac{1}{n_c t_c} = \frac{1}{146.62 \,\mathrm{ns}}$. The sequential module needs five cycles $(n_c = 5)$ to compute a result, so its latency is five times its clock period. Because a new computation cannot start while a computation is in progress the throughput is one over the latency.

Pipelined Module, ms_pipe: Latency $L = n_s t_c = 4 \times 28.273$ ns, where n_s is the number of stages. Throughput $\theta = \frac{1}{t_c} = \frac{1}{28.273 \text{ ns}}$. Like the sequential circuit, the latency of the pipelined unit is the clock period times the number of cycles needed to compute a result. Unlike the sequential circuit, the pipelined circuit can start a new computation every cycle, and so the throughput is the reciprocal of the clock period.

(b) For each of the two significand sizes, show that the delay of the three ms modules are what one would expect given the delays of the three arithmetic modules.

Combinational Module, ms_comb: To solve this problem one needs to find the critical path through the module. Refer to the Verilog description and the diagram of the inferred hardware below.

```
ms_comb
                                                     m00
                                         v0
                                                                  a1
module ms comb
                                                    .w_fp_mult
                                                                                    result
                                                                              a2
                                                                cw_fp_add
                                        Ŧ
  #( int wsig = 23, wexp = 8,
                                                                            cw_fp_add
                                                     rnd
     int ieee = 1,
                                                                  rnd
                                                      Τ
                                                3'b0-
                                                                              rnd
     int wf = 1 + wexp + wsig )
                                                     m01
                                                                 3'b0
                                                                              3'b0
   ( output uwire [wf-1:0] result,
                                                    cw_fp_mult
                                         v1
     output uwire ready,
                                       -
                                                     rnd
     input uwire [wf-1:0] v0, v1,
                                                      3'b0-
     input uwire start, clk);
                                                     m11
                                                                                     ready
                                         start
                                                    .w_fp_mult
                                                                              1'd1
   localparam logic [2:0] rm = 0;
                                         clk 5
                                                     rnd
   assign ready = 1;
                                                      J
                                                3'b0
   uwire [7:0] mul_s1, mul_s2, mul_s3;
   uwire [7:0] a_s1, a_s2;
   uwire [wf-1:0] v00, v01, v11, s1;
   CW_fp_mult #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     m00( .a(v0), .b(v0), .rnd(rm), .z(v00), .status(mul_s1));
   CW_fp_mult #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     m01( .a(v0), .b(v1), .rnd(rm), .z(v01), .status(mul_s2));
   CW_fp_mult #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     m11( .a(v1), .b(v1), .rnd(rm), .z(v11), .status(mul_s3));
   CW_fp_add #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     a1(.a(v00), .b(v11), .rnd(rm), .z(s1), .status(a_s1));
   CW_fp_add #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     a2(.a(s1), .b(v01), .rnd(rm), .z(result), .status(a_s2));
endmodule
```

Based on the timings given in the synthesis results table the critical path goes through m00, a1, and a2. Both mOO and m11 compute the square of their inputs, and based on the data in the synthesis results table computing a square takes slightly less time than computing a product, $25.504 \,\mathrm{ns}$ versus $28.321 \,\mathrm{ns}$.

Using the timings from the synthesis table, the delay (critical path) through ms_comb is $t_{sq}+2t_{add}=25.504$ ns+ $2 \times 27.396 \,\mathrm{ns} = 80.296 \,\mathrm{ns}$. This is about 5 ns longer than the delay for ms_comb reported in the synthesis table, $75.142 \,\mathrm{ns}$, a difference of only about 6%.



Sequential Module, ms_seq : The inferred hardware is shown above, taken from the solution to the 2020 final exam (the module name was prob1_seq in the exam). For ms_seq the critical path cannot pass through both the multiplier and adder, it must pass through one or the other. In addition to these arithmetic units there is also one multiplexor delay and some logic gates. Assuming that the multiplexor and logic gates' delays are small compared to the arithmetic unit, the critical path will be the larger of the two delays, 28.231 ns for the multiplier and 27.396 ns for the adder. So the clock period would be a bit over 28.231 ns. This is very close to the results from the table, 29.324 ns.

Pipelined Module, ms_pipe: As with the sequential module, the critical path will be through the arithmetic unit that takes the most time, the multiplier. Unlike the sequential version, there are no multiplexors or logic between the arithmetic units and the pipeline latches, and so we would expect the delay to be even closer to the multiplier delay, 28.231 ns. The reported delay, 28.273 ns is indeed very close.

(c) Using the cost of the arithmetic units, show that the cost of ms_comb is lower than expected, but the cost of ms_seq and ms_pipe are about or perhaps a little more than what one would expect.

Combinational Module, ms_comb : This consists of one multiplier, two square units and two adders. The expected cost is $525991 + 2 \times 339036 + 2 \times 297753 = 1799569$. The reported cost is 1597692, which is lower by 11.2%. Sequential Module, ms_seq : This module has one multipler and one adder. Their costs are 525991 + 297753 = 823744. This estimated cost ignores the cost of registers, multiplexors, and miscellaneous logic. The reported cost is 945919, which is higher, perhaps due to the ignored hardware.

Pipelined Module, ms_pipe: This module has the same arithmetic units as the combinational module, and so the estimated cost, ignoring registers, would be the same, $525991 + 2 \times 339036 + 2 \times 297753 = 1799569$. The reported cost is 1866509 which is higher. The higher cost is probably due to ignoring the cost of registers.

Problem 2: It is welcome that the cost of ms_comb is lower than what one would expect based on the cost of the arithmetic units. There are several possible reasons for this, for example the synthesis program may be simplifying the two adders used in computations such as a + b + c or it may be sharing hardware used to process the common b operand in expressions like $a \times b$ and $b \times c$, or perhaps it may even be transforming $v_0^2 + v_0v_1 + v_1^2$ into $(v_0 + v_1)^2 - v_0v_1$. Or maybe the costs for the arithmetic units shown in the table are higher than they should be.

Perform a set of synthesis runs to provide evidence for a reason that ms_comb cost less than its constituent parts. Consider the possible reasons given above, or one of your own. These synthesis runs can operate on one of the existing modules, a slightly modified version of the modules, or something wholly different. The modules m1_comb, m1_seq, m1_pipe can be used for experimentation. See the Modules section above.

Describe the results of these experiments and how they convincingly support a particular reason for the lower cost. Data from a single synthesis run, or a series of very similar runs will not be considered convincing.

The Verilog file for this assignment will be collected, but submit the answers to this question on paper or by E-mail. Please E-mail PDF files. Sending word processor source files as a final product is unprofessional, even if they are T_{FX} files.

In your writeup:

- Indicate how you believe the synthesis program is optimizing ms_comb.
- Describe the modules you synthesized to come to this conclusion, and the results of synthesis. Most credit will be given for this part of the assignment.
- Explain why your experiments show that the lower cost was not due to other optimizations.

Based on the experiments described below, it appears that the synthesis program can significantly reduce the cost of computations of the form $a^2 + b^2$ computed using the ChipWare FP arithmetic modules. The optimization is not applied to similar computations such as $(a + c)^2 + b^2$.

To determine why the cost of ms_comb was more than 11% less than the estimated cost, a number of new modules were simulated. The modules were designed to test various hypotheses, including those suggested in the problem. The modules' names all start with $m1_$, followed by an abbreviation that may suggest what it does. (In the table of synthesis results the name is appended with the parameter values used.) For example, $m1_a3$ is a module that computes a+b+c. Each module was tested for correctness by updating $m1_functional$ so that it computes the same value as the test module. A wrapper module, $m1_comb$, provides a third input for modules that take three data inputs, such as $m1_a3$. The third input value is just v0*v1, so $m1_functional$ uses v0*v1 in places where v2 might go. All of the tested modules were combinational. The synthesis script output shown below (near the end of the solution) is for runs using these modules.

The Verilog code used for these experiments can be found at https://www.ece.lsu.edu/koppel/v/2022/hw05-sol.v.html and the synthesis script is at https://www.ece.lsu.edu/koppel/v/2022/syn-sol.tcl.html.

Appearing below (on the next page) is the m1_a3 module, its wrapper, and m1_functional.

```
/// This module is synthesized.
module m1 a3
  #( int wsig = 23, wexp = 8, ieee = 1, wf = 1 + wexp + wsig )
  ( output uwire [wf-1:0] result, output uwire ready,
     input uwire [wf-1:0] v0, v1, v2, input uwire start, clk);
  localparam logic [2:0] rm = 0; // Rounding Mode
  uwire [7:0] mul_s1, mul_s2, mul_s3, a_s1, a_s2;
  uwire [wf-1:0] v00, v01, v11, s1;
  CW_fp_add #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     a1(.a(v0), .b(v1), .rnd(rm), .z(s1), .status(a_s1));
  CW_fp_add #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
    a2(.a(s1), .b(v2), .rnd(rm), .z(result), .status(a_s2));
  assign ready = 1;
endmodule
/// This module is simulated
module m1 comb
```

```
#( int wsig = 23, wexp = 8, ieee = 1, wf = 1 + wexp + wsig )
   ( output uwire [wf-1:0] result, output uwire ready,
    input uwire [wf-1:0] v0, v1,
                                     input uwire start, clk);
  localparam logic [2:0] rm = 0; // Rounding Mode
  uwire [wf-1:0] v01;
  uwire [7:0] mul_s2;
  // Generate a third input for m1_a3.
  CW_fp_mult #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
    m01( .a(v0), .b(v1), .rnd(rm), .z(v01), .status(mul_s2));
  m1_a3 #( .wsig(wsig), .wexp(wexp), .ieee(ieee) )
  a3( result, ready, v0, v1, v01, start, clk );
endmodule
// cadence translate_off
module m1_functional
  ( output real mag, input real v0, v1 );
  // The testbench uses this module to test the others, so set
  // the computation to match the others.
  localparam string name = "A3 Func";
  // Note: The third value is v0*v1.
  always_comb mag = v0 + v1 + v0 * v1;
endmodule
// cadence translate_on
```

The results of each experiment are described below. The value inputs to the modules are called v_0 , v_1 , and v_2 . The original multi-step modules only had two data inputs, v_0 and v_1 . The third input, v_2 , is set to v_0v_1 by the wrapper module, m1_comb, for testing purposes. The synthesis program operates on modules such as m1_a3 and so to it the value on third input, v_2 , is unrelated to the other two values.

In the discussion below let c_a , c_m , and c_s denote the cost of the adder, multiplier, and square unit. Those costs are $c_m = 525991$, $c_a = 339036$, and $c_s = 297753$ for the 23-bit significand and $c_m = 94274$, $c_a = 140221$, and $c_s = 57802$ for the 7-bit significand.

Module m1_a3: Computes $v_0 + v_1 + v_2$

To test for any benefit of computing a + b + c use a module that computes this sum, m1_a3. The expected cost is two adders, $3c_a$, which is 280442 for 7 bits and 678072 for 23 bits. The synthesized costs are 278532 and 668518, respectively or .68% and 1.41% lower than estimated. So there is not much optimization benefit from combining two adders.

Module m1_mad: Computes $v_0 * v_1 + v_2$

To test whether adder and multiplier hardware is shared, try a module that computes $v_0 \times v_1 + v - 2$, called m1_mad. The expected cost is $c_m + c + a$ or 234495 for 7 bits and 865027 for 23 bits. The synthesized hardware is just 2.58% and 1.48% less costly than the estimate, not enough to explain ms_comb.

Module m1_mm: Computes $v_0 * v_1$ and $v_0 * v_2$

Perhaps two multipliers that have a common multiplier can share some hardware. Module $m1_mm$ tests that by using v_0 in both multiplies. This module has two outputs, one for each product. So the estimated cost is $2c_m$: 188548 and 1051982 for the 7- and 23-bit versions. The synthesized cost is just 1.76% and .59% less than the estimates.

Module m1_comb_v3: Computes $v_0^2 + v_0v_2 + v_1^2$

To rule out whether the cost reduction is due to an algebraic transformation, a version of ms_comb which has three value inputs was tried. The new value, v_2 , replaces v_1 in the v_0v_1 term. The estimated cost is $2c_s + c_m + 2c_a$, the same as the ms_comb estimate. The synthesized costs are 22.24% and 10.79% lower than the estimated costs, which means that the synthesis program is not doing an algebraic transformation that depends on the middle term, v_0v_1 , sharing a variable with the other two.

Module m1_comb_sos: Computes $v_0^2 + v_1^2$

Perhaps there's something special about a sum of squares. The estimated cost is $2c_s + c_a$, or 255825 and 934542 for the 7- and 23-bit versions. The synthesized costs are substantially lower, 38.3% and 8.61%. The fact that the benefit is larger for the smaller significand suggests that the savings is with the handling of the exponents, which are eight bits in both versions.

Module m1_comb_sop: Computes $v_0v_2 + v_1v_3$

Are squares special? To rule that out a module computing a sum of two products was tried. This module has four value inputs. The estimated cost is $2c_m + c_1$ or 328769 and 1391018. The synthesized costs are 1.99% and 1.58% less, suggesting that there is something special about a sum of squares.

Module m1_comb_ssp: Computes $v_0^2 + v_1 v_2$

Perhaps one square can be optimized, m1_comb_ssp tests that. The expected cost is $c_m + c_s + c + a$ or 292297 and 1162780. The synthesized costs are 7.48% and 2.31% less, so there is some benefit to one square, but not nearly as much as the benefit from both adder inputs being squares.

Module m1_comb_alt: Computes $(v_0^2 + v_0v_1) + v_1^2$

Finally, just to be sure, re-do ms_comb so the two squares are not operands of the same adder. The expected cost is $2c_s + c_m + 2c_a$ or 441037 and 1726894. The synthesized costs are lower, 10.05% and 4.04%, suggesting that there is some benefit of using a square input to an adder, but that the benefit is substantially larger when both inputs are a square.

Synthesis Data on Next Page

Module Name	Area	Delay	Delay	Synth
	070500	Actual	larget	lime
m1_a3_wsig/_wexp8_ieee0	278532	28.162	100.0 ns	s 54 s
m1_a3_wsig23_wexp8_ieee0	668518	54.005	100.0 ns	s 117 s
m1_mad_wsig7_wexp8_ieee0	228453	23.283	100.0 ns	s 36 s
m1_mad_wsig23_wexp8_ieee0	852191	53.147	100.0 ns	s 114 s
m1_mm_wsig7_wexp8_ieee0	185236	9.346	100.0 ns	s 20 s
m1_mm_wsig23_wexp8_ieee0	1045808	28.231	100.0 ns	s 80 s
m1 comb v3 wsig7 wexp8 ieee0	381271	34.077	100.0 ns	s 79 s
m1 comb v3 wsig 2 woxpolicecc	1605/66	7/ 753	100.0 m	276 s
m1_comp_v3_w31g23_wexb0_1eeeo	1000400	14.100	100.0 11	5 210 5
m1_comb_sos_wsig7_wexp8_ieee0	157807	19.544	100.0 ns	s 34 s
m1_comb_sos_wsig23_wexp8_ieee0	854120	48.375	100.0 ns	s 128 s
m1_comb_sop_wsig7_wexp8_ieee0	322223	23.763	100.0 ns	s 48 s
m1_comb_sop_wsig23_wexp8_ieee0	1369003	53.049	100.0 ns	s 169 s
m1 comb sep usig7 wayn8 ieee0	270427	23 781	100 0 ng	a 44 a
m1_comb_ssp_wsig?_wexpe_iccco	1125020	E2 206	100.0 m	150 a
mr_comp_psh_wpr859_werho_16660	1133920	53.300	100.0 11	5 102 8
m1_comb_alt_wsig7_wexp8_ieee0	441037	38.112	100.0 ns	s 103 s
m1_comb_alt_wsig23_wexp8_ieee0	1726894	80.177	100.0 ns	s 281 s
<u> </u>				

```
11
/// LSU EE 4755 Fall 2022 Homework 5 -- SOLUTION
11
 /// Assignment https://www.ece.lsu.edu/koppel/v/2022/hw05.pdf
/// Solution writeup https://www.ece.lsu.edu/koppel/v/2022/hw05_sol.pdf
`default_nettype none
/// All Problems
11
/// Arithmetic-Unit-Only Modules
11
11
     These modules have a single arithmetic module.
11
11
     Use these to estimate the cost of the multi-step complex modules.
11
11
     The ports and parameters match the multi-step for convenience.
module try_mult
 #( int wsig = 23, wexp = 8, ieee = 1, wf = 1 + wexp + wsig )
  ( output uwire [wf-1:0] result,
    output uwire ready,
    input uwire [wf-1:0] v0, v1,
    input uwire start, clk);
  localparam logic [2:0] rm = 0; // Rounding Mode
  uwire [7:0] mul s1;
  <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
    m00( .a(v0), .b(v1), .rnd(rm), .z(result), .status(mul_s1));
  assign ready = 1;
endmodule
module try sq
 #( int wsig = 23, wexp = 8, ieee = 1, wf = 1 + wexp + wsig )
  ( output uwire [wf-1:0] result,
    output uwire ready,
    input uwire [wf-1:0] v0,
    input uwire start, clk);
  try mult #(wsig,wexp,ieee) tm( result, ready, v0, v0, start, clk);
endmodule
module try_add
 #( int wsig = 23, wexp = 8, ieee = 1, wf = 1 + wexp + wsig )
  ( output uwire [wf-1:0] result,
    output uwire ready,
    input uwire [wf-1:0] v0, v1,
    input uwire start, clk );
  localparam logic [2:0] rm = 0; // Rounding Mode
  uwire [7:0] add_s1;
```

```
\leftarrow \rightarrow Fall 2022 \leftarrow \rightarrow Homework 5
```

assign ready = 1;

```
<u>CW fp add</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     a00( .a(v0), .b(v1), .rnd(rm), .z(result), .status(add_s1));
   assign ready = 1;
endmodule
111
     Multi-Step Modules
11
11
      These compute the function in three different ways.
11
11
      Do not modify these modules.
11
      Modify the m1 modules instead.
// cadence translate_off
module ms_functional
  ( output real mag, input real v0, v1 );
   localparam string name = "Func";
   always_comb mag = v0 * v0 + v0 * v1 + v1 * v1;
endmodule
// cadence translate_on
module ms_comb
  #( int wsig = 23, wexp = 8, ieee = 1, wf = 1 + wexp + wsig )
   ( output uwire [wf-1:0] result,
     output uwire ready,
     input uwire [wf-1:0] v0, v1,
     input uwire start, clk);
   // cadence translate_off
   localparam string name = "Comb";
   // cadence translate_on
   localparam int nstages = 1;
   localparam logic [2:0] rm = 0; // Rounding Mode
   uwire [7:0] mul_s1, mul_s2, mul_s3, a_s1, a_s2;
   uwire [wf-1:0] v00, v01, v11, s1;
   <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     m00( .a(v0), .b(v0), .rnd(rm), .z(v00), .status(mul_s1));
   <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     m01( .a(v0), .b(v1), .rnd(rm), .z(v01), .status(mul_s2));
   <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     m11(.a(v1), .b(v1), .rnd(rm), .z(v11), .status(mul_s3));
   <u>CW_fp_add</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     a1(.a(v00), .b(v11), .rnd(rm), .z(s1), .status(a_s1));
   <u>CW fp add</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     a2(.a(s1), .b(v01), .rnd(rm), .z(result), .status(a_s2));
```

endmodule

```
module ms seq
  #( int wsig = 23, wexp = 8, ieee = 1, wf = 1 + wexp + wsig )
   ( output logic [wf-1:0] result, output logic ready,
     input uwire [wf-1:0] v0, v1,
                                     input uwire start, clk );
   // cadence translate_off
   localparam string name = "Seq";
   // cadence translate_on
   uwire [7:0] mul_s, add_s; // Operation status. Ignored.
   uwire [wf-1:0] mul_a, mul_b, add_a, add_b, prod, sum;
   logic [2:0] step;
   logic [wf-1:0] ac0, ac1;
   localparam int last_step = 4;
   always_ff @( posedge clk )
     if ( start ) step <= 0;</pre>
     else if ( step < last_step ) step <= step + 1;</pre>
   localparam logic [2:0] rm = 0; // Rounding Mode
   <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     m1( .z(prod), .a(mul_a), .b(mul_b), .rnd(rm), .status(mul_s));
   <u>CW fp add</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     a1(.z(sum), .α(add_a), .b(add_b), .rnd(rm), .status(add_s));
   assign mul_a = step < 2 ? v0 : v1;
   assign mul_b = step == 0 ? v0 : v1;
   assign add_a = ac0, add_b = ac1;
   always_ff @( posedge clk )
     begin
        ac0 <= prod;</pre>
        if ( step < 3 ) ac1 <= step ? sum : 0;
        if ( start ) ready <= 0; else if ( step == last_step-1 ) ready <= 1;</pre>
     end
   assign result = sum;
endmodule
module ms_pipe
  #( int wsig = 23, wexp = 8, ieee = 1, wf = 1 + wexp + wsig )
   ( output uwire [wf-1:0] result,
     output uwire ready,
     input uwire [wf-1:0] v0, v1,
     input uwire start, clk);
   // cadence translate_off
   localparam string name = "Pipe";
   // cadence translate_on
   localparam int nstages = 4;
   localparam logic [2:0] rm = 0; // Rounding Mode
```

```
uwire [7:0] mul_s1, mul_s2, mul_s3, a_s1, a_s2;
   uwire [wf-1:0] v00, v01, v11, s1, s2;
   logic [wf-1:0] pl_1_v00, pl_1_v01, pl_1_v11;
   logic [wf-1:0] pl_2_v0001, pl_2_v11;
   logic [wf-1:0] pl_3_sum;
   logic pl_1_occ, pl_2_occ, pl_3_occ;
   <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     mOO( .z(v00), .a(v0), .b(v0), .rnd(rm), .status(mul_s1));
   <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     m01( .z(v01), .a(v0), .b(v1), .rnd(rm), .status(mul_s2));
   <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     m11( .z(v11), .a(v1), .b(v1), .rnd(rm), .status(mul_s3));
   <u>CW fp add</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     a1(.z(s1), .α(pl_1_v00), .b(pl_1_v01), .rnd(rm), .status(a_s1));
   <u>CW fp add</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     a2(.z(s2), .a(pl_2_v0001), .b(pl_2_v11), .rnd(rm), .status(a_s2));
   assign ready = pl_3_occ;
   assign result = pl_3_sum;
   always_ff @( posedge clk ) begin
      pl_1_v00 <= v00;
      pl_1_v01 <= v01;
      pl_1_v11 <= v11;
      pl_1_occ <= start;</pre>
      pl_2_v0001 <= s1;
      pl_2_v11 <= pl_1_v11;
      pl_2_occ <= pl_1_occ;</pre>
      pl_3_sum <= s2;
      pl_3_occ <= pl_2_occ;</pre>
   end
endmodule
```

```
/// Experimentation Modules
//
// These compute a different function in three different ways.
//
// Modify these modules.
//
```

```
// cadence translate_off
module m1_functional
  ( output real mag,
     input real v0, v1 );
   // The testbench uses this module to test the others, so set
   // the computation to match the others.
```

```
\leftarrow \rightarrow Fall 2022
                   \leftarrow \rightarrow Homework 5
                                                 Homework Solution Sol Code
       localparam string name = "A3 Func";
       // always_comb mag = v0 + v0 * v1 + v1 * v1;
       // always_comb mag = v0 * v1 + v1 + v0;
       // always_comb mag = v0 * v1 + v0 * v1 * v0 ;
       // always_comb mag = v0 * v0 + v0 * v1 * v0 + v1 * v1;
       // always_comb mag = v0 * v0 + v0 * v1;
       always_comb mag = v0 * v0 + v0 * v1 + v1 * v1;
   endmodule
   // cadence translate_on
   module m1_comb_alt
      #( int wsig = 23, wexp = 8, ieee = 1, wf = 1 + wexp + wsig )
       ( output uwire [wf-1:0] result,
         output uwire ready,
         input uwire [wf-1:0] v0, v1,
         input uwire start, clk);
       // cadence translate_off
       localparam string name = "Alt Comb";
       // cadence translate_on
       localparam int nstages = 1;
       localparam logic [2:0] rm = 0; // Rounding Mode
       uwire [7:0] mul_s1, mul_s2, mul_s3, a_s1, a_s2;
       uwire [wf-1:0] v00, v01, v11, s1;
       <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
         m00( .a(v0), .b(v0), .rnd(rm), .z(v00), .status(mul_s1));
       <u>CW_fp_mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
         m01( .a(v0), .b(v1), .rnd(rm), .z(v01), .status(mul_s2));
       <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
         m11( .a(v1), .b(v1), .rnd(rm), .z(v11), .status(mul_s3));
       <u>CW_fp_add</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
         a1(.a(v00), .b(v01), .rnd(rm), .z(s1), .status(a_s1));
       <u>CW fp add</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
         a2(.a(s1), .b(v11), .rnd(rm), .z(result), .status(a_s2));
       assign ready = 1;
   endmodule
   module m1_comb_ssp
      #( int wsig = 23, wexp = 8, ieee = 1, wf = 1 + wexp + wsig )
       ( output uwire [wf-1:0] result,
         output uwire ready,
         input uwire [wf-1:0] v0, v1, v2,
         input uwire start, clk);
       // cadence translate_off
       localparam string name = "Comb";
       // cadence translate_on
       localparam int nstages = 1;
       localparam logic [2:0] rm = 0; // Rounding Mode
```

```
uwire [7:0] mul_s1, mul_s2, mul_s3, a_s1, a_s2;
   uwire [wf-1:0] v00, v01, v11, s1;
   <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     m00( .a(v0), .b(v0), .rnd(rm), .z(v00), .status(mul_s1));
   <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     m11( .a(v1), .b(v2), .rnd(rm), .z(v11), .status(mul_s3));
   <u>CW fp add</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     a1(.a(v00), .b(v11), .rnd(rm), .z(result), .status(a_s1));
   assign ready = 1;
endmodule
module m1_comb_sop
  #( int wsig = 23, wexp = 8, ieee = 1, wf = 1 + wexp + wsig )
   ( output uwire [wf-1:0] result,
     output uwire ready,
     input uwire [wf-1:0] v0, v1, v2, v3,
     input uwire start, clk);
   // cadence translate_off
   localparam string name = "Comb";
   // cadence translate_on
   localparam int nstages = 1;
   localparam logic [2:0] rm = 0; // Rounding Mode
   uwire [7:0] mul_s1, mul_s2, mul_s3, a_s1, a_s2;
   uwire [wf-1:0] v00, v01, v11, s1;
   <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     m00( .a(v0), .b(v2), .rnd(rm), .z(v00), .status(mul_s1));
   <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     m11( .a(v1), .b(v3), .rnd(rm), .z(v11), .status(mul_s3));
   <u>CW fp add</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     a1(.a(v00), .b(v11), .rnd(rm), .z(result), .status(a_s1));
   assign ready = 1;
endmodule
module m1_comb_sos
  \#( int wsig = 23, wexp = 8, ieee = 1, wf = 1 + wexp + wsig )
   ( output uwire [wf-1:0] result,
     output uwire ready,
     input uwire [wf-1:0] v0, v1,
     input uwire start, clk);
   // cadence translate_off
   localparam string name = "Comb";
   // cadence translate_on
   localparam int nstages = 1;
   localparam logic [2:0] rm = 0; // Rounding Mode
```

```
\leftarrow \rightarrow Fall 2022
                    \leftarrow \rightarrow Homework 5
                                                  Homework Solution Sol Code
       uwire [7:0] mul_s1, mul_s2, mul_s3, a_s1, a_s2;
       uwire [wf-1:0] v00, v01, v11, s1;
       <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
         m00( .a(v0), .b(v0), .rnd(rm), .z(v00), .status(mul_s1));
       <u>CW_fp_mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
         m11( .a(v1), .b(v1), .rnd(rm), .z(v11), .status(mul_s3));
       <u>CW fp add</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
         a1(.a(v00), .b(v11), .rnd(rm), .z(result), .status(a_s1));
       assign ready = 1;
    endmodule
    module m1_comb_v3
      #( int wsig = 23, wexp = 8, ieee = 1, wf = 1 + wexp + wsig )
       ( output uwire [wf-1:0] result,
         output uwire ready,
         input uwire [wf-1:0] v0, v1, v2,
         input uwire start, clk);
       // cadence translate_off
       localparam string name = "Comb";
       // cadence translate_on
       localparam int nstages = 1;
       localparam logic [2:0] rm = 0; // Rounding Mode
       uwire [7:0] mul_s1, mul_s2, mul_s3, a_s1, a_s2;
       uwire [wf-1:0] v00, v01, v11, s1;
       <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
         mOO( .a(v0), .b(v0), .rnd(rm), .z(v00), .status(mul_s1));
       <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
         m01( .a(v0), .b(v2), .rnd(rm), .z(v01), .status(mul_s2));
       <u>CW_fp_mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
         m11( .a(v1), .b(v1), .rnd(rm), .z(v11), .status(mul_s3));
       <u>CW fp add</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
         a1(.a(v00), .b(v11), .rnd(rm), .z(s1), .status(a_s1));
       <u>CW_fp_add</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
         a2(.a(s1), .b(v01), .rnd(rm), .z(result), .status(a_s2));
       assign ready = 1;
    endmodule
    module m1 a3
      #( int wsig = 23, wexp = 8, ieee = 1, wf = 1 + wexp + wsig )
       ( output uwire [wf-1:0] result,
         output uwire ready,
         input uwire [wf-1:0] v0, v1, v2,
         input uwire start, clk);
       // cadence translate_off
       localparam string name = "One Comb";
       // cadence translate_on
```

```
\leftarrow \rightarrow Fall 2022
                   \leftarrow \rightarrow Homework 5
                                                  Homework Solution Sol Code
       localparam int nstages = 1;
       localparam logic [2:0] rm = 0; // Rounding Mode
       uwire [7:0] mul_s1, mul_s2, mul_s3, a_s1, a_s2;
       uwire [wf-1:0] v00, v01, v11, s1;
       <u>CW fp add</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
         a1(.a(v0), .b(v1), .rnd(rm), .z(s1), .status(a_s1));
       <u>CW fp add</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
         a2(.a(s1), .b(v2), .rnd(rm), .z(result), .status(a_s2));
       assign ready = 1;
    endmodule
    module m1_mad
      #( int wsig = 23, wexp = 8, ieee = 1, wf = 1 + wexp + wsig )
       ( output uwire [wf-1:0] result,
         output uwire ready,
         input uwire [wf-1:0] v0, v1, v2,
         input uwire start, clk);
       // cadence translate_off
       localparam string name = "One Comb";
       // cadence translate_on
       localparam int nstages = 1;
       localparam logic [2:0] rm = 0; // Rounding Mode
       uwire [7:0] mul_s1, mul_s2, mul_s3, a_s1, a_s2;
       uwire [wf-1:0] v00, v01, v11, s1;
       <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
         a1(.a(v0), .b(v1), .rnd(rm), .z(s1), .status(a_s1));
       <u>CW fp add</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
         a2(.a(s1), .b(v2), .rnd(rm), .z(result), .status(a_s2));
       assign ready = 1;
    endmodule
    module m1_mm
      #( int wsig = 23, wexp = 8, ieee = 1, wf = 1 + wexp + wsig )
       ( output uwire [wf-1:0] p1, p2,
         output uwire ready,
         input uwire [wf-1:0] v0, v1, v2,
         input uwire start, clk);
       // cadence translate_off
       localparam string name = "One Comb";
       // cadence translate_on
       localparam int nstages = 1;
       localparam logic [2:0] rm = 0; // Rounding Mode
       uwire [7:0] mul_s1, mul_s2, mul_s3, a_s1, a_s2;
       uwire [wf-1:0] v00, v01, v11, s1;
       <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
```

```
\leftarrow \rightarrow Fall 2022
                   \leftarrow \rightarrow Homework 5
                                                 Homework Solution Sol Code
         a1(.α(v0), .b(v1), .rnd(rm), .z(p1), .status(a_s1));
       <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
         a2(.a(v0), .b(v2), .rnd(rm), .z(p2), .status(a_s2));
       assign ready = 1;
   endmodule
   module m1_comb
      #( int wsig = 23, wexp = 8, ieee = 1, wf = 1 + wexp + wsig )
       ( output uwire [wf-1:0] result,
         output uwire ready,
         input uwire [wf-1:0] v0, v1,
         input uwire start, clk);
       // cadence translate_off
       localparam string name = "MM Comb";
       // cadence translate_on
       localparam int nstages = 1;
       localparam logic [2:0] rm = 0; // Rounding Mode
       uwire [wf-1:0] v01, p1, p2;
       uwire [7:0] mul_s2, a_s3;
       <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
         m01( .a(v0), .b(v1), .rnd(rm), .z(v01), .status(mul_s2));
       m1_comb_ssp #( .wsig(wsig), .wexp(wexp), .ieee(ieee) )
       a3( result, ready, v0, v1, v0, start, clk );
       // assign ready = 1;
   endmodule
   module m1_v3
      #( int wsig = 23, wexp = 8, ieee = 1, wf = 1 + wexp + wsig )
       ( output uwire [wf-1:0] result,
         output uwire ready,
         input uwire [wf-1:0] v0, v1,
         input uwire start, clk);
       // cadence translate_off
       localparam string name = "MM Comb";
       // cadence translate_on
       localparam int nstages = 1;
       localparam logic [2:0] rm = 0; // Rounding Mode
       uwire [wf-1:0] v01, p1, p2;
       uwire [7:0] mul_s2, a_s3;
       <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
         m01( .a(v0), .b(v1), .rnd(rm), .z(v01), .status(mul_s2));
       m1_comb_v3 #( .wsig(wsig), .wexp(wexp), .ieee(ieee) )
       a3( result, ready, v0, v1, v01, start, clk );
       // assign ready = 1;
```

```
module m1_comb_mm
  #( int wsig = 23, wexp = 8, ieee = 1, wf = 1 + wexp + wsig )
   ( output uwire [wf-1:0] result,
     output uwire ready,
     input uwire [wf-1:0] v0, v1,
     input uwire start, clk);
   // cadence translate_off
   localparam string name = "MM Comb";
   // cadence translate_on
   localparam int nstages = 1;
   localparam logic [2:0] rm = 0; // Rounding Mode
   uwire [wf-1:0] v01, p1, p2;
   uwire [7:0] mul_s2, a_s3;
   <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     m01( .a(v0), .b(v1), .rnd(rm), .z(v01), .status(mul_s2));
   m1 mm #( .wsig(wsig), .wexp(wexp), .ieee(ieee) )
   a3( p1, p2, ready, v0, v1, v01, start, clk );
   <u>CW fp add</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
   a2(.a(p1), .b(p2), .rnd(rm), .z(result), .status(a_s3));
   // assign ready = 1;
endmodule
module m1_comb_a3
  #( int wsig = 23, wexp = 8, ieee = 1, wf = 1 + wexp + wsig )
   ( output uwire [wf-1:0] result,
     output uwire ready,
     input uwire [wf-1:0] v0, v1,
     input uwire start, clk);
   // cadence translate_off
   localparam string name = "A3 Comb";
   // cadence translate_on
   localparam int nstages = 1;
   localparam logic [2:0] rm = 0; // Rounding Mode
   uwire [wf-1:0] v01;
   uwire [7:0] mul_s2;
   <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     m01( .a(v0), .b(v1), .rnd(rm), .z(v01), .status(mul_s2));
   m1 a3 #( .wsig(wsig), .wexp(wexp), .ieee(ieee) )
   a3( result, ready, v0, v1, v01, start, clk );
   // assign ready = 1;
endmodule
module m1_comb_orig
  \#( int wsig = 23, wexp = 8, ieee = 1, wf = 1 + wexp + wsig )
```

```
( output uwire [wf-1:0] result,
     output uwire ready,
     input uwire [wf-1:0] v0, v1,
     input uwire start, clk);
   // cadence translate_off
   localparam string name = "One Comb";
   // cadence translate_on
   localparam int nstages = 1;
   localparam logic [2:0] rm = 0; // Rounding Mode
   uwire [7:0] mul_s1, mul_s2, mul_s3, a_s1, a_s2;
   uwire [wf-1:0] v00, v01, v11, s1;
   <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     m01( .a(v0), .b(v1), .rnd(rm), .z(v01), .status(mul_s2));
   <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     m11( .a(v1), .b(v1), .rnd(rm), .z(v11), .status(mul_s3));
   <u>CW fp add</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     a1(.a(v0), .b(v11), .rnd(rm), .z(s1), .status(a_s1));
   <u>CW fp add</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     a2(.a(s1), .b(v01), .rnd(rm), .z(result), .status(a_s2));
   assign ready = 1;
endmodule
module m1 seq
  #( int wsig = 23, wexp = 8, ieee = 1, wf = 1 + wexp + wsig )
   ( output logic [wf-1:0] result, output logic ready,
     input uwire [wf-1:0] v0, v1, input uwire start, clk );
   // cadence translate_off
   localparam string name = "One Seq";
   // cadence translate_on
   uwire [7:0] mul_s, add_s; // Operation status. Ignored.
   uwire [wf-1:0] mul_a, mul_b, add_a, add_b, prod, sum;
   logic [2:0] step;
   logic [wf-1:0] ac0, ac1;
   localparam int last_step = 4;
   always_ff @( posedge clk )
     if ( start ) step <= 0;</pre>
     else if ( step < last_step ) step <= step + 1;</pre>
   localparam logic [2:0] rm = 0; // Rounding Mode
   <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     m1( .z(prod), .a(mul_a), .b(mul_b), .rnd(rm), .status(mul_s));
   <u>CW_fp_add</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
     a1( .z(sum), .a(add_a), .b(add_b), .rnd(rm), .status(add_s));
   localparam logic [wf-1:0] one = { ( 1 << wexp - 1 ) - 1, wsig'(0) };</pre>
   assign mul_a = step < 2 ? v0 : v1;
```

 $\leftarrow \rightarrow$ Fall 2022

 $\leftarrow \rightarrow$ Homework 5

```
Homework Solution Sol Code
```

```
hw05-sol.v.html
```

```
\leftarrow \rightarrow Fall 2022
                    \leftarrow \rightarrow Homework 5
       assign mul b = step == 0 ? one : v1;
       assign add_a = ac0, add_b = ac1;
       always_ff @( posedge clk )
         begin
            ac0 <= prod;
            if ( step < 3 ) ac1 <= step ? sum : 0;</pre>
            if ( start ) ready <= 0; else if ( step == last_step-1 ) ready <= 1;</pre>
         end
       assign result = sum;
    endmodule
    module m1_pipe
      #( int wsig = 23, wexp = 8, ieee = 1, wf = 1 + wexp + wsig )
       ( output uwire [wf-1:0] result,
         output uwire ready,
         input uwire [wf-1:0] v0, v1,
         input uwire start, clk);
       // cadence translate off
       localparam string name = "One Pipe";
       // cadence translate_on
       localparam int nstages = 4;
       localparam logic [2:0] rm = 0; // Rounding Mode
       uwire [7:0] mul_s1, mul_s2, mul_s3, a_s1, a_s2;
       uwire [wf-1:0] v00, v01, v11, s1, s2;
       logic [wf-1:0] pl_1_v00, pl_1_v01, pl_1_v11;
       logic [wf-1:0] pl_2_v0001, pl_2_v11;
       logic [wf-1:0] pl_3_sum;
       logic pl_1_occ, pl_2_occ, pl_3_occ;
       <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
         m01( .z(v01), .a(v0), .b(v1), .rnd(rm), .status(mul_s2));
       <u>CW fp mult</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
         m11( .z(v11), .a(v1), .b(v1), .rnd(rm), .status(mul_s3));
       <u>CW_fp_add</u> #( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(ieee) )
         a1(.z(s1), .α(pl_1_v00), .b(pl_1_v01), .rnd(rm), .status(a_s1));
       CW fp add #( .sig width(wsig), .exp width(wexp), .ieee compliance(ieee) )
         a2(.z(s2), .α(pl_2_v0001), .b(pl_2_v11), .rnd(rm), .status(a_s2));
       assign ready = pl_3_occ;
       assign result = pl_3_sum;
       always_ff @( posedge clk ) begin
          pl_1_v00 <= v0;
          pl_1_v01 <= v01;
          pl_1_v11 <= v11;
          pl_1_occ <= start;</pre>
          pl_2_v0001 <= s1;
          pl_2_v11 <= pl_1_v11;
          pl_2_occ <= pl_1_occ;</pre>
```

pl_3_sum <= s2; pl_3_occ <= pl_2_occ;

end

endmodule

```
/// Testbench Code
11
// It is okay to modify the testbench code to facilitate the coding
// and debugging of your modules.
// cadence translate_off
function automatic real rand_real(real minv, real maxv);
     rand_real = minv + ( maxv - minv ) * ( real'({<u>$random</u>}) ) / 2.0**32;
endfunction
function automatic real fabs(real val);
     fabs = val < 0 ? -val : val;</pre>
endfunction
virtual class CONV #(int wexp=6, wsig=10);
  // Convert between real and fp types using parameter-provided
  // exponent and significand sizes.
  localparam int w = 1 + wexp + wsig;
  localparam int bias_r = (1 << 11 - 1) - 1;
  localparam int w_sig_r = 52;
  localparam int w_exp_r = 11;
  localparam int bias_h = ( 1 << wexp - 1 ) - 1;</pre>
  static function logic [w-1:0] rtof( real r );
     logic [wsig-1:0] sig_f;
     logic [w_sig_r-wsig-1:0] sig_x;
     logic [w_exp_r-1:0] exp_r;
     logic sign_r;
     { sign_r, exp_r, sig_f, sig_x } = <u>$realtobits(r);</u>
     rtof = !r ? 0 : { sign_r, wexp'( exp_r + bias_h - bias_r ), sig_f };
  endfunction
  static function real ftor( logic [w-1:0] f );
     ftor = !f ? 0.0
       : $bitstoreal
         ( { f[w-1],
             w_exp_r'( bias_r + f[w-2:wsig] - bias_h ),
             f[wsig-1:0], (w_sig_r-wsig)'(0) } );
  endfunction
endclass
```

```
program reactivate
  (output uwire clk_reactive, output int cycle_reactive,
    input uwire clk, input var int cycle);
   assign clk_reactive = clk;
```

```
assign cycle_reactive = cycle;
endprogram
```

module testbench;

```
localparam int npsets = 4; // Number of instantiations.
localparam int pset[npsets][2] =
           \{ \{ 7, 0 \}, \{ 23, 0 \}, \{ 7, 1 \}, \{ 23, 1 \} \};
11
// Above: First number in each pair is value of n_avg_of,
// second number is maximum word length.
int n_err_shown; // Number of times error info printed to console.
int n_err_sh_nc, n_err_sh_nw, n_err_sh_avg, n_err_sh_state;
initial begin
   n_err_sh_nc = 0;
   n_{err_sh_nw} = 0;
   n_{err_sh_avg} = 0;
   n_err_sh_state = 0;
end
int t_errs;
                  // Total number of errors.
initial begin t_errs = 0; n_err_shown = 0; end
final <u>$write("Total number of errors: %0d\n",t_errs);</u>
uwire d[npsets:-1];
                      // Start / Done signals.
assign d[-1] = 1; // Initialize first at true.
// Instantiate a testbench at each size.
11
for ( genvar i=0; i<npsets; i++ )</pre>
  testbench n #(pset[i][0], pset[i][1]) t2( .done(d[i]), .tstart(d[i-1]) );
```

endmodule

```
module testbench_n
  #( int w_sig = 7, use_one = 0 )
   ( output logic done, input uwire tstart );
   typedef enum { MT_comb, MT_seq, MT_pipe } Module_Type;
   localparam int w_exp = 8;
   localparam int wid = w_sig + w_exp + 1;
   localparam int max_latency = 10;
   localparam int num_tests = 16;
   localparam int nmuts = 10;
   int err[nmuts];
   uwire [wid-1:0] mag[nmuts];
   uwire
                 ready[nmuts];
   real
        magr;
   real vr[2];
   logic [wid-1:0] v[2], vp[2];
   logic
               start;
   typedef struct
     £
      int idx;
```

```
int err count = 0;
   int ncyc = 0;
   Module Type mt = MT_comb;
   logic [wid-1:0] sout = 'h111;
   int cyc_tot = 0;
   } Info;
Info pi[string];
localparam int cycle_limit = num_tests * max_latency * 4;
int cycle, cyc_start;
logic clock;
bit use_others;
logic clk_reactive;
int cycle_reactive;
reactivate ra(clk_reactive,cycle_reactive,clock,cycle);
task pi_seq(input int idx, input string name);
   automatic string m = <u>$sformatf("%s", name</u>);
   pi[m].idx = idx; pi[m].mt = MT_seq;
endtask
task pi_comb(input int idx, input string name);
   automatic string m = <u>$sformatf("%s", name</u>);
   pi[m].idx = idx; pi[m].mt = MT_comb;
endtask
task pi_pipe(input int idx, input string name, input int ncyc);
   automatic string m = <u>$sformatf("%s", name);</u>
   pi[m].idx = idx; pi[m].mt = MT_pipe;
   pi[m].ncyc = ncyc;
endtask
initial begin
   clock = 0;
   cycle = 0;
   done = 0;
   wait( tstart );
   fork
      while ( !done ) #10 cycle += clock++;
      wait( done );
      wait( cycle >= cycle_limit )
        $write("*** Cycle limit exceeded, ending.\n");
   join_any;
   done = 1;
end
if ( use_one ) begin
   m1 functional mf( magr, vr[0], vr[1] );
   m1 seq #( .wsig(w_sig), .wexp(w_exp), .ieee(0) )
     m2( mag[1], ready[1], v[0],v[1], start, clock );
   initial begin pi_seq(1,m2.name); end
   m1 comb_alt #( .wsig(w_sig), .wexp(w_exp), .ieee(0) )
     m5r( mag[5], ready[5], v[0],v[1], start, clock );
```

 $\leftarrow \rightarrow$ Fall 2022

 $\leftarrow \rightarrow$ Homework 5

```
\leftarrow \ \rightarrow \ \text{Fall} \ 2022
                   \leftarrow \rightarrow Homework 5
                                                  Homework Solution Sol Code
          initial begin pi_comb(5,m5r.name); end
          m1 pipe #( .wsig(w_sig), .wexp(w_exp), .ieee(0) )
            m3( mag[3], ready[3], vp[0],vp[1], start, clock );
          initial begin pi_pipe(3,m3.name,m3.nstages); end
       end else begin
          ms functional mf( magr, vr[0], vr[1] );
          ms_seq #( .wsig(w_sig), .wexp(w_exp), .ieee(0) )
            m2( mag[1], ready[1], v[0],v[1], start, clock );
          initial begin pi_seq(1,m2.name); end
          ms comb #( .wsig(w_sig), .wexp(w_exp), .ieee(0) )
            m5r( mag[5], ready[5], v[0],v[1], start, clock );
          initial begin pi_comb(5,m5r.name); end
          ms pipe #( .wsig(w_sig), .wexp(w_exp), .ieee(0) )
            m3( mag[3], ready[3], vp[0],vp[1], start, clock );
          initial begin pi_pipe(3,m3.name,m3.nstages); end
       end
       initial begin
          while ( !done ) @( posedge clk_reactive ) #2
             if ( use_others ) begin
                vp = v;
                use_others = 0;
                start = 1;
             end else begin
                vp[0] = conv#(w_exp,w_sig)::rtof( real'(cycle-cyc_start) );
                vp[1] = cycle - cyc_start;
                start = 0;
             end
       end
       initial begin
          automatic int n_err = 0;
          use_others = 0;
          start = 0;
          @( posedge clk_reactive );
```

```
for ( int i=0; i<num_tests; i++ ) begin
  automatic int awaiting = pi.num();
  cyc_start = cycle;</pre>
```

if (i < 4) begin

```
// In first eight test vector components are zero or one.
   11
   for ( int j=0; j<2; j++ ) vr[j] = i & 1 << j ? 1.0 : 0.0;</pre>
end else begin
   // In other tests vector components are randomly chosen.
   11
   for ( int j=0; j<2; j++ ) vr[j] = rand_real(-10,+10);</pre>
end
for ( int j=0; j<2; j++ ) v[j] = conv#(w_exp,w_sig)::rtof(vr[j]);</pre>
vp = v;
use_others = 1;
/// Collect Result (mag) From Each Module Under Test (mut)
11
foreach ( pi[muti] ) begin
   // Note: need to make a local copy of muti because of the
   // fork below.
   automatic string mut = muti;
   // Create a child thread to get response from current mut.
   // The parent thread, without delay, proceeds to join_none.
   11
   fork begin
      if ( pi[mut].mt == MT_seq ) begin
         wait ( !ready[pi[mut].idx] );
         wait ( ready[pi[mut].idx] );
      end else begin
         // Compute time at which result should be ready or
         // when to start examining a READY output.
         11
         automatic int latency =
           pi[mut].mt == MT_comb ? 1 : pi[mut].ncyc;
         automatic int eta = cyc_start + latency;
         wait ( cycle_reactive == eta );
      end
      // Decrement count of the number of modules we are waiting for.
      11
      awaiting--;
      // Store the module MAG output, it will be checked later
      // for correctness.
      11
      pi[mut].sout = mag[pi[mut].idx];
      pi[mut].cyc_tot += cycle - cyc_start;
```

// This thread ends execution here.

```
end join_none;
   end
   // Wait until data collected from all modules under test.
   11
   wait ( awaiting == 0 );
   // Check the output of each Module Under Test.
  11
   foreach ( pi[ mut ] ) begin
      // Assign module output to a real.
      11
      automatic real mmagr = conv#(w_exp,w_sig)::ftor(pi[mut].sout);
      11
      // Note: pi[mut].sout is type logic which is assumed to be
      // an unsigned integer. However, the contents is really an
      // float.
      // Compute difference between module output and expected
      // output. With FP small differences can be okay, they might
      // occur, for example, due to differences in the order of
      // operations.
      11
      automatic real err_mag =
        fabs( mmagr - magr ) / fabs( magr ? magr : 1 );
      localparam real tol = real'(4) / ( 1 << w_sig );</pre>
      automatic bit okay = err_mag < tol;</pre>
      if ( !okay ) begin
        pi[mut].err_count++;
         n_err++;
        if ( pi[mut].err_count < 5 )</pre>
          $write("%s (%0d) test #%0d vec (%.1f,%.1f) error: h'%8h %7.4f != %7.4f (correct)\n",
             mut, w_sig, i, vr[1], vr[0],
                 pi[mut].sout, mmagr, magr);
     end
   end
  while ( {$random} & 1 == 1 ) @( posedge clk_reactive );
   11
   // Note: By waiting for reactive clock we can be sure that
   // modules under test have completed all work due to the
   // positive edge of the regular clk. Wait a random amount of
   // time in case any modules are only correct at some stride.
end
foreach ( pi[ mut ] )
 $write("Ran %4d tests for (%0d) %-0s, %4d errors found. Avg cyc %.1f\n",
         num_tests, w_sig, mut,
         pi[mut].err_count,
         pi[mut].mt == MT_comb ? 1 : real'(pi[mut].cyc_tot) / num_tests);
done = 1;
testbench.t_errs += n_err;
```

end

endmodule

`define SIMULATION_ON

// cadence translate_on

`default_nettype wire

`*ifdef* SIMULATION_ON

`include "/apps/linux/cadence/GENUS211/share/synth/lib/chipware/sim/verilog/CW/CW_fp_mult.v"

`*include* "/apps/linux/cadence/GENUS211/share/synth/lib/chipware/sim/verilog/CW/CW_fp_add.v"

`else

```
`include "/apps/linux/cadence/GENUS211/share/synth/lib/chipware/syn/CW/CW_fp_mult.v"
`include "/apps/linux/cadence/GENUS211/share/synth/lib/chipware/syn/CW/CW_fp_add.v"
```

`endif

17 Fall 2021 Solutions

LSU EE 4755 Homework 1 solution Due: 24 September 2021

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2021/hw01.v.html.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account, copy the assignment, and run the Verilog simulator and synthesis program on the unmodified homework file, hw01.v. Do this early enough so that minor problems (*e.g.*, password doesn't work) are minor problems.

Problem 1: The partially completed insert_at module below and in the homework assignment file has three inputs, a wa-bit input ia, a wb-bit input ib, and a $\lceil lg(wa+1) \rceil$ -bit input pos, and there is one output, a wa+wb-bit output o. Complete the module following the coding requirements given further below so that o consists of the bits of ia with ib inserted at pos. That is, o[pos-1:0] should be set to ia[pos-1:0], o[wb+pos-1:pos] should be set to ib, and o[wa+wb-1:wb+pos] should be set to ia[wa-1:pos].

For example, let wa=6 and wb=2, ia=111111, ib=00, and pos = 2. Then o=11110011. For pos=5, o=10011111. For those still not 100% sure of what o should be set to should look at how o_shadow is computed in the testbench module. Also, the testbench will show what the output should be when it isn't.

```
module insert_at
#( int wa = 20, wb = 10, wo = wa+wb, walg = $clog2(wa+1) )
( output logic [wo-1:0] o,
    input uwire [wa-1:0] ia, input uwire [wb-1:0] ib,
    input uwire [walg-1:0] pos );
// The line assigning mask_low must be replaced with a mask module.
uwire [wo-1:0] mask_low = ( 1 << pos ) - 1; // REPLACE ME!
uwire [wo-1:0] ib_at_pos;
shift_left #(wb,wo,walg) sl1( ib_at_pos, ib, pos );
assign o = ia & mask_low | ib_at_pos;
endmodule</pre>
```

The insert_at module must be synthesizable and must not use procedural code and must not use shift operators. (That includes the line assigning mask_low, it must be replaced.) Instead, rely on instantiations of the provided shift and mask modules.

The testbench will test your module and report the first few errors. For example, here is the testbench output for the unmodified module:

```
Error for ia=11111111 ib=000
                              pos= 0
                                      00000000000 != 11111111000 (correct)
                                      0000000001 != 11111110001 (correct)
Error for ia=11111111
                      ib=000
                              pos= 1
Error for ia=11111111 ib=000
                                      0000000011 != 11111100011 (correct)
                              pos= 2
Error for ia=11111111 ib=000 pos= 3
                                      00000000111 != 11111000111 (correct)
Error for ia=11111111
                      ib=000
                                      00000001111 != 11110001111 (correct)
                              pos= 4
Done with 27 tests, 15 errors found.
```

The text 00000001111 != 11110001111 (correct) shows the output of insert_at to the left of the != and the correct answer to the right. So in this case 00000001111 is the module output

and 11110001111 is what the module output should have been. Only the first few errors are shown, but the total number of errors is reported at the end, 15 in this case.

Synthesizability can be checked by running the synthesis script using the command genus -files syn.tcl. If the module is synthesizable (though not necessarily correct) a table of area and delay will be shown, for example:

Module Name	Area	Delay	Delay
		Actual	Target
insert_at	51832	0.987	1.000 ns
insert_at_1	97968	0.616	0.100 ns
Normal exit.			

One common problem encountered by beginners is setting the correct port sizes. For example, the shift_left module the port sizes are wi, wo, and wolg:

```
module insert_at #( int wa = 20, wb = 10, wo = wa+wb, walg = $clog2(wa+1) )
  ( output logic [wo-1:0] o,
    input uwire [wa-1:0] ia, input uwire [wb-1:0] ib,
    input uwire [walg-1:0] pos );
    uwire [wo-1:0] ib_at_pos;
    shift_left #(wb,wo,walg) sl1( ib_at_pos, ib, pos );
```

So the first connection to a shift_left instantiation must be wi bits, the second must be wo bits, and the third wolg bits. In the unmodified insert_at these parameters to insert_at were set explicitly to match the connection sizes. Sometimes it may be necessary to use an intermediate object or to cast in order to get the correct connection size. For example, if we wanted to shift by pos+1 the following would not work:

shift_left #(wb,wo,walg) sl1(ib_at_pos, ib, pos + 1); because the 1 in the pos+1 expression implicitly expands it to 32 bits. (This results in a warning, but it's not good to clutter compiler output with ignorable warnings.) The problem can be solved using a cast:

```
shift_left #(wb,wo,walg) sl1( ib_at_pos, ib, walg'(pos + 1) );
```

Solution starts on the next page.

The solution appears below, and can be found in the assignment directory, and on the course Web pages at https://www.ece.lsu.edu/koppel/v/2021/hw01-sol.v.html. Immediately below is the solution without extensive comments. On the following pages is the same solution, but with sample values shown in the comments.

```
module insert at
  #( int wa = 20, wb = 10, wo = wa+wb, walg = $clog2(wa+1) )
   ( output logic [wo-1:0] o,
     input uwire [wa-1:0] ia,
    input uwire [wb-1:0] ib,
     input uwire [walg-1:0] pos );
                                SOLUTION
  ///
  uwire [wa-1:0] mask_low;
  mask_lsb #(wa) ml(mask_low, pos);
  uwire [wa-1:0] ia_low = ia & mask_low;
  uwire [wa-1:0] ia_high_low = ia & ~mask_low;
  localparam int wblg = $clog2(wb);
  uwire [wo-1:0] ia_high;
  shift_left #(wa,wo,wblg) slc( ia_high, ia_high_low, wblg'(wb) );
  uwire [wo-1:0] ib_at_pos;
  shift_left #(wb,wo,walg) slb( ib_at_pos, ib, pos );
  assign o = ia_high | ib_at_pos | ia_low;
endmodule
```

The challenge in this assignment was refreshing your knowledge of Verilog and digital logic. If you can't follow the module above, look at the one on the following pages and in particular use the sample values to figure out what is going one.

The solution here makes use of a single mask unit (named ml) creating mask mask_low. This mask is used twice, in its original form to extract the lowest pos bits of ia into ia_low and in inverted form to extract the high bits of ia into ia_high_low. Note that both ia_low and ia_high_low are wa-bit quantities. The "shifter" slc writes a shifted value of ia_high_low into ia_high. Notice that the shift-amount input to slc (the last port) is wb, a constant (since it's a module parameter). That brings the cost of slc to zero.

A real shifter, slb, is used to move ib into the correct position in its output ib_at_pos. The assign statement puts all of these together.

Common Mistakes: In a few solutions the shift amounts or mask sizes were set assuming that wa=8 and wb=3. That is not correct because insert_at can be instantiated with other possible values of wa and wb.

Another common mistake was to set the width of the shift amount port to a value much larger than needed. For example, consider:

shift_left #(wb,wa+wb,wo) slb(ib_at_pos, ib, phat_pos);

The third parameter of the $shift_left$ module has been set to wo, which is overkill. (The shift amount input has been renamed $phat_pos$ to emphasize its new size.) For this use of $shift_left$ the most by which we would shift is in bits, so at most the position would take $\lceil \log_2 2wa \rceil$ (or as a Verilog expression, sclog2(wa)) bits. Setting a parameter like this to too large a value will not affect correctness (in cases like this) but it can increase the cost of the synthesized hardware. That depends on the synthesis programs ability to recognize that high-order bits will always be zero. So for that reason it is best to set parameters to appropriate values. That does mean taking the time to learn what each parameter is for and to set it properly, but that is what you would be paid for.

Solution with sample values appearing in the comments:

```
module insert at
  #( int wa = 20, wb = 10, wo = wa+wb, walg = $clog2(wa+1) )
   ( output logic [wo-1:0] o,
    input uwire [wa-1:0] ia,
    input uwire [wb-1:0] ib,
    input uwire [walg-1:0] pos );
  /// SOLUTION
  /// :Example: Input Values:
  11
  // ia =
                                   (Each a is a bit of ia, it can be 0 or 1 .)
                        aaaaaaaa
  // ib =
                                   (Each b is a bit of ib, it can be 0 or 1 .)
                             bbb
  // pos = 2
  11
  /// Desired Output Value
  11
  // 0
                     aaaaaabbbaa (Notice that ib is insert at pos 2)
  uwire [wa-1:0] mask_low;
  mask_lsb #(wa) ml(mask_low, pos);
  uwire [wa-1:0] ia_low = ia & mask_low;
  uwire [wa-1:0] ia_high_low = ia & ~mask_low;
  // ia =
                        aaaaaaaa
  // mask_low =
                      00000011 (Two low bits are 1 because pos=2.)
  // ia_low =
                        000000aa (ia_low has the bits to the right of pos.)
  // ia_high_low =
                      aaaaaa00 (ia_high_low: the bits to the left of pos.)
  localparam int wblg = $clog2(wb);
  uwire [wo-1:0] ia_high;
  shift_left #(wa,wo,wblg) slc( ia_high, ia_high_low, wblg'(wb) );
  // ia_high_low =
                        aaaaaa00
  // ia_high =
                     aaaaaa00000 (Shift wb bits to make room for ib.)
  uwire [wo-1:0] ib_at_pos;
  shift_left #(wb,wo,walg) slb( ib_at_pos, ib, pos );
  // ib =
                             bbb
  // ib_at_pos = 000000bbb00 (Shifted pos bits, and widened to wo bits.)
  assign o = ia_high | ib_at_pos | ia_low;
                     aaaaa00000
  // ia_high =
  // ib_at_pos =
                     000000bbb00
  // ia_low =
                        000000aa
  // 0
                     aaaaaabbbaa
            =
endmodule
```

//////////////////////////////////////
/// LSU EE 4755 Fall 2021 Homework 1 /// SOLUTION
/// Assignment <u>https://www.ece.lsu.edu/koppel/v/2021/hw01.pdf</u> /// Solution Discussion <u>https://www.ece.lsu.edu/koppel/v/2021/hw01_sol.pdf</u>
` <i>default_nettype</i> none
//////////////////////////////////////
<pre>/// Complete insert_at so that output o is set to ia with ib inserted at pos. ///</pre>
<pre>// // [•] Make sure that the testbench does not report errors. // [•] Module must be synthesizable. Use command: genus -files syn.tcl //</pre>
<pre>// [*] Do not use procedural code. // [*] Do not use the << or >> operators (or anything similar). // [*] Use the shift and mask modules to provide shifted values and bitmasks. //</pre>
<pre>// [*] Don't assume any particular parameter value. // // [*] Code must be written clearly. // [*] Pay attention to cost and performance.</pre>
<pre>module insert_at #(int wa = 20, wb = 10, wo = wa+wb, walg = \$clog2(wa+1)) (output logic [wo-1:0] o, input uwire [wa-1:0] ia, input uwire [wb-1:0] ib, input uwire [walg-1:0] pos);</pre>
/// SOLUTION
/// :Example: Input Values: //
<pre>// ia = aaaaaaaa (Each a is a bit of ia, it can be 0 or 1.) // ib = bbb (Each b is a bit of ib, it can be 0 or 1.) // pos = 2 //</pre>
/// Desired Output Value //
<pre>// o = aaaaaabbbaa (Notice that ib is inserted at pos 2.)</pre>
uwire [wa-1:0] mask_low; <u>mask_lsb</u> #(wa) ml (mask_low, pos);

```
Homework Solution Sol Code
\leftarrow \rightarrow Fall 2021
                 \leftarrow \rightarrow Homework 1
      uwire [wa-1:0] ia_low = ia & mask_low;
      uwire [wa-1:0] ia_high_low = ia & ~mask_low;
      // ia =
                             aaaaaaaa
      // mask_low =
                             00000011 (Two low bits are 1 because pos=2.)
      // ia low =
                             000000aa (ia_low has the bits to the right of pos.)
      // ia_high_low = aaaaaa00 (ia_high_low: the bits to the left of pos.)
      localparam int wblg = <u>$clog2(wb);</u>
      uwire [wo-1:0] ia_high;
      shift left #(wa,wo,wblg) slc( ia_high, ia_high_low, wblg'(wb) );
      // ia_high_low =
                             aaaaaa00
      // ia_high = aaaaaa00000 (Shift wb bits to make room for ib.)
      uwire [wo-1:0] ib_at_pos;
      shift left #(wb,wo,walg) slb( ib_at_pos, ib, pos );
      // ib =
                                   bbb
                          000000bbb00 (Shifted pos bits, and widened to wo bits.)
      // ib_at_pos =
      assign o = ia_high | ib_at_pos | ia_low;
      // ia_high =
                          aaaaaa00000
      // ib_at_pos =
                          000000bbb00
      // ia_low =
                             000000aa
               =
                          aaaaaabbbaa
      // 0
   endmodule
   module shift_left
     #( int wi = 4, wo = wi, wolg = $clog2(wo) )
       ( output uwire [wo-1:0] o,
        input uwire [wi-1:0] i,
        input uwire [wolg-1:0] amt );
      assign o = i << amt;</pre>
   endmodule
   module shift_right
     #( int wi = 4, wo = wi, wolg = $clog2(wo) )
       ( output uwire [wo-1:0] o,
        input uwire [wi-1:0] i,
        input uwire [wolg-1:0] amt );
      assign o = i >> amt;
   endmodule
   module mask lsb
     #( int wo = 6, wp = \frac{clog2}{wo+1} )
       ( output logic [wo-1:0] o, input uwire [wp-1:0] n1 );
      always_comb for ( int i=0; i<wo; i++ ) o[i] = i < n1;
   endmodule
```

module mask_msb
```
\leftarrow \rightarrow Fall 2021 \leftarrow \rightarrow Homework 1
```

```
#( int wo = 6, wp = <u>$clog2(wo+1)</u>)
  ( output logic [wo-1:0] o, input uwire [wp-1:0] n1 );
  always_comb for ( int i=0; i<wo; i++ ) o[wo-i-1] = i < n1;
endmodule</pre>
```



```
// cadence translate_off
```

module testbench;

```
logic done [1:-1];
initial done[-1] = 1;
<u>testbench size</u> #(8,3, "Set 1") tb1(done[0],done[-1]);
<u>testbench size</u> #(4,5, "Set 2") tb2(done[1],done[0]);
```

endmodule

```
module testbench_size
  #( int wa = 8, int wb = 3, string label = "set me" )
   ( output logic done_me,
     input uwire logic done_pred );
   localparam int wo = wa+wb;
   localparam int walg = $clog2(wa+1);
   localparam int n_tests = (wa+1) * 3;
   logic [wa-1:0] ia;
   logic [wb-1:0] ib;
   uwire [wo-1:0] o;
   logic [walg-1:0] pos;
   insert at #(wa,wb) iat(o, ia, ib, pos);
   initial begin
      automatic int n_err = 0;
      wait ( done_pred === 1 );
      for ( int tn = 0; tn < n_tests; tn++ ) begin</pre>
         automatic int rnd = tn / (wa+1);
         logic [wo-1:0] o_shadow;
         pos = tn % (wa+1);
         case ( rnd )
```

```
\leftarrow \rightarrow Homework 1
                                               Homework Solution Sol Code
\leftarrow \rightarrow Fall 2021
                 0: begin ia = -1; ib = 0; end
                 1: begin ia = 0; ib = -1; end
                 default: {ia,ib} = {<u>$random</u>};
              endcase
              #1;
              for ( int i=0; i<pos; i++ ) o_shadow[i] = ia[i];</pre>
              for ( int i=0; i<wb; i++ ) o_shadow[i+pos] = ib[i];</pre>
              for ( int i=pos; i<wa; i++ ) o_shadow[i+wb] = ia[i];</pre>
              if ( o_shadow !== o ) begin
                 n_err++;
                 if (n_err < 6)
                   $write("Error %s for ia=%b ib=%b pos=%d %b != %b (correct)\n",
                           label,
                           ia, ib, pos, o, o_shadow);
              end
          end
          $write("For %s, done with %0d tests, %0d errors found.\n",
                  label, n_tests, n_err);
```

endmodule

// cadence translate_on

done_me = 1;

```
11
/// LSU EE 4755 Fall 2021 Homework 2
11
 /// SOLUTION
 /// Assignment https://www.ece.lsu.edu/koppel/v/2021/hw02.pdf
`default_nettype none
/// Problem1
11
111
     Complete nn_sparse so that it computes both dense (fmt=4'b1111)
     and sparse (fmt= 4'b1100, 4'b0110, 4'b1010, etc.) products.
111
111
11
11
      [*] Make sure that the testbench does not report errors.
11
      [ / ] Module must be synthesizable. Use command: genus -files syn.tcl
11
11
      [<] To achieve the fastest speed a sparse product computation</pre>
          should not go through two adders.
11
11
11
      [ Jon't assume any particular parameter value.
11
11
      [.] Code must be written clearly.
11
      [~] Pay attention to cost and performance.
module nn_sparse
 #( int nn = 4, wexp = 6, wsig_ac = 15, wsig_in = 10, wsig_wd = 6,
    wo = 1 + wexp + wsig_ac,
    wi = 1 + wexp + wsig_in,
    ww = nn * (1 + wexp + wsig_wd))
   ( output logic [wo-1:0] o,
    input uwire [wi-1:0] i[nn],
    input uwire [ww-1:0] w,
    input uwire [nn-1:0] fmt );
  // Compute size of significand of sparse weights.
  localparam int wsig_ws = 2 * wsig_wd + wexp + 1;
  // Separate w into dense weights.
  11
  localparam int wwd = ww / nn;
  uwire [3:0][wwd-1:0] wd;
  assign wd = w;
  // SOLUTION
  11
  // Separate w into sparse weights
  11
```

```
hw02-sol.v.html
```

```
localparam int wws = wwd * 2;
   uwire [1:0][wws-1:0] ws = w;
   // Dense
   uwire [wo-1:0] acc1, acc2, od, os;
   nn2 #(wexp,wsig_in,wsig_wd,wsig_ac) nn2d1(acc1, i[0], i[1], wd[0], wd[1]);
   nn2 #(wexp,wsig_in,wsig_wd,wsig_ac) nn2d2(acc2, i[2], i[3], wd[2], wd[3]);
   <u>fp add</u> #(wexp,wsig_ac) add(od,acc1,acc2);
   // SOLUTION
   11
   // Select the two inputs that will participate in the sparse
   // computation ..
   11
   uwire [wi-1:0] is0 = fmt[0] ? i[0] : fmt[1] ? i[1] : i[2];
   uwire [wi-1:0] is1 = fmt[3] ? i[3] : fmt[2] ? i[2] : i[1];
   11
   // .. and connect them to an nn2 instantiation in which the weight
   // input size parameters are wsig_ws instead of wsig_wd.
   11
   nn2 #(wexp,wsig_in,wsig_ws,wsig_ac) nn2s(os, is0, is1, ws[0], ws[1]);
   // SOLUTION
   11
   // Route the appropriate value to the output.
   11
   assign o = fmt[2:0] == 3'b111 ? od : os;
endmodule
module nn_sparse_cheap
  #( int nn = 4, wexp = 6, wsig_ac = 15, wsig_in = 10, wsig_wd = 6,
    wo = 1 + wexp + wsig_ac,
    wi = 1 + wexp + wsig_in,
    ww = nn * (1 + wexp + wsig_wd))
   ( output logic [wo-1:0] o,
     input uwire [wi-1:0] i[nn],
     input uwire [ww-1:0] w,
    input uwire [nn-1:0] fmt );
   // This module is less expensive than nn_sparse because it
   // instantiates only two nn2 modules, but it has a longer
   // critical path.
   localparam int wwd = ww / nn;
   localparam int wsig_ws = 2 * wsig_wd + wexp + 1;
   localparam int wws = 1 + wexp + wsig_ws;
   uwire sparse = &fmt[2:0] == 0;
   uwire [3:0] [wwd-1:0] wd; // Xcelium bug?: can't assign on decl line.
   assign wd = w;
   uwire [1:0][wws-1:0] ws = w;
```

Homework Sol Code

 $\leftarrow \rightarrow$ Fall 2021

 $\leftarrow \rightarrow$ Homework 2

```
// Dense
   uwire [wo-1:0] acc1, acc2, od, os;
   nn2 #(wexp,wsig_in,wsig_wd,wsig_ac) nn2d2(acc2, i[2], i[3], wd[2], wd[3]);
   <u>fp_add</u> #(wexp,wsig_ac) add(od,acc1,acc2);
   uwire [wi-1:0] is0 = fmt[0] ? i[0] : fmt[1] ? i[1] : i[2];
   uwire [wi-1:0] is1 = !sparse ? i[1] : fmt[3] ? i[3] : fmt[2] ? i[2] : i[1];
   uwire [wws-1:0] ws0 = sparse ? ws[0] : wd[0] << wsig_ws - wsig_wd;</pre>
   uwire [wws-1:0] ws1 = sparse ? ws[1] : wd[1] << wsig_ws - wsig_wd;</pre>
   // Sparse
   <u>nn2</u> #(wexp,wsig_in,wsig_ws,wsig_ac) nn2s(acc1, is0, is1, ws0, ws1);
   assign o = sparse ? acc1 : od;
endmodule
module nn2
  #( int wexp = 9, wsig_in = 10, wsig_w = 5, wsig_ac = 12,
     wi = 1 + wexp + wsig_in,
     ww = 1 + wexp + wsig_w,
     wo = 1 + wexp + wsig_ac)
   ( output uwire [wo-1:0] o,
     input uwire [wi-1:0] i0, i1,
     input uwire [ww-1:0] w0, w1 );
   uwire [wo-1:0] p0, p1;
   hy_mult #(wexp, wsig_in, wsig_w, wsig_ac) m0(p0,i0,w0);
   hy_mult #(wexp, wsig_in, wsig_w, wsig_ac) m1(p1,i1,w1);
   fp add #(wexp,wsig_ac) a(o,p0,p1);
endmodule
module fp_add
  #( int wexp = 3, wsig = 50, w = 1 + wexp + wsig )
   ( output uwire [w-1:0] sum,
     input uwire [w-1:0] i0, i1 );
   uwire [7:0] s;
   localparam logic [2:0] rnd_to_0 = 3'b1;
   <u>CW fp add</u> \#( .sig_width(wsig), .exp_width(wexp), .ieee_compliance(0))
   a(.a(i0),.b(i1), .rnd(rnd_to_0), .z(sum), .status(s));
```

endmodule

module hy_mult

```
\leftarrow \rightarrow Fall 2021
                  \leftarrow \rightarrow Homework 2
                                              Homework Sol Code
      #( int wexp = 5, int wsig_a = 6, int wsig_b = 7,
         int wsig_p = wsig_a + wsig_b )
       ( output uwire [wexp+wsig p:0] prod,
         input uwire [wexp+wsig_a:0] a,
         input uwire [wexp+wsig b:0] b );
       uwire [7:0] s;
       localparam logic [2:0] rnd_to_0 = 3'b1;
       localparam logic [2:0] rnd_to_plus_inf = 3'b10;
       localparam logic [2:0] rnd_to_minus_inf = 3'b11;
       localparam int wm = 1 + wexp + wsig_p;
       localparam int wsig_diff_a = wsig_p - wsig_a;
       localparam int wsig_diff_b = wsig_p - wsig_b;
       uwire [wm-1:0] ea = wsig_diff_a >= 0
                       ? a << wsig_diff_a : a[wexp+wsig_a:-wsig_diff_a];</pre>
       uwire [wm-1:0] eb = wsig_diff_b >= 0
                       ? b << wsig_diff_b : b[wexp+wsig_b:-wsig_diff_b];</pre>
```

```
<u>CW fp_mult</u> #( .sig_width(wsig_p), .exp_width(wexp), .ieee_compliance(0))
U1(.a(ea),.b (eb), .rnd (rnd_to_0), .z (prod), .status (s) );
```

endmodule


```
// cadence translate_off
```

```
virtual class CONV #(int wexp=6, wsig=10);
   // Convert between real and fp types using parameter-provided
   // exponent and significand sizes.
   localparam int w = 1 + wexp + wsig;
   localparam int bias_r = ( 1 << 11 - 1 ) - 1;</pre>
   localparam int w_sig_r = 52;
   localparam int w_exp_r = 11;
   localparam int bias_h = ( 1 << wexp - 1 ) - 1;</pre>
   static function logic [w-1:0] rtof( real r );
      logic [wsig-1:0] sig f;
      logic [w_sig_r-wsig-1:0] sig_x;
      logic [w_exp_r-1:0] exp_r;
      logic sign_r;
      { sign_r, exp_r, sig_f, sig_x } = <u>$realtobits(r);</u>
      rtof = !r ? 0 : { sign_r, wexp'( exp_r + bias_h - bias_r ), sig_f };
   endfunction
   static function real ftor( logic [w-1:0] f );
      ftor = !f ? 0.0
        : <u>$bitstoreal</u>
          ( { f[w-1],
```

```
hw02-sol.v.html
```

```
Homework Sol Code
\leftarrow \rightarrow Fall 2021
                 \leftarrow \rightarrow Homework 2
                  w_exp_r'( bias_r + f[w-2:wsig] - bias_h ),
                  f[wsig-1:0], (w_sig_r-wsig)'(0) } );
       endfunction
   endclass
   function real fabs(real a);
          fabs = a < 0 ? -a : a;
   endfunction
   function int min( int a, b );
          min = a < b ? a : b;
   endfunction
   function int min3( int a, b, c );
          automatic int ab = a < b ? a : b;</pre>
          min3 = ab < c ? ab : c;
   endfunction
   module testbench_nn_sparse;
      localparam int npsets = 3;
      localparam int pset[npsets][4] =
                   '{ {5, 20, 15, 4}, {6, 18, 10, 5}, {6, 18, 12, 3} };
      // wexp, wsig_ac, wsig_in, wsig_wd
      logic done[npsets:0];
      initial done[0] = 1;
      for ( genvar i = 0; i<npsets; i++ )</pre>
          testbench nn sparse p
            #(pset[i][0],pset[i][1],pset[i][2],pset[i][3])
            tb(done[i+1],done[i]);
   endmodule
   module testbench_nn_sparse_p
     #( int wexp = 5, wsig_ac = 10, wsig_in = 6, wsig_wd = 4 )
       ( output logic done, input uwire start );
      localparam int ni = 4;
      localparam int wo = 1 + wexp + wsig_ac;
      localparam int wi = 1 + wexp + wsig_in;
      localparam int ww = ni * ( 1 + wexp + wsig_wd );
```

localparam int wsig_ws = 2 * wsig_wd + wexp + 1;

localparam real tol_d = real'(2) / (1 << wsig_wd);</pre>

localparam real tol_s = real'(2) / (1 << min(wsig_in,wsig_ws));</pre>

localparam int ws = 1 + wexp + wsig_ws; localparam int wd = 1 + wexp + wsig_wd;

```
localparam int n_tests = 5000;
localparam real hot_val[] = { 1, 2, 0.1, 10.1 };
localparam int n_one_hot = 4;
localparam int n two hot = n one hot;
initial if ( n one hot != hot val.size() )
  $fatal(1,"Fix n_one_hot and file a Cadence bug.");
logic [wo-1:0] o;
logic [wi-1:0] ia[ni];
logic [ww-1:0] wht;
logic [ni-1:0] fmt;
localparam logic [5:0][3:0] fmts =
           { 4'b11, 4'b110, 4'b1100, 4'b101, 4'b1010, 4'b1001 };
nn sparse #(ni, wexp, wsig_ac, wsig_in, wsig_wd) nnsp(o, ia, wht, fmt);
initial begin
   automatic int n_errd = 0, n_errs = 0;
   automatic real max_diffs = 0, max_diffd = 0;
   automatic string abbrev =
          $sformatf("ex%0d,ac%0d,in%0d,wd%0d",wexp,wsig_ac,wsig_in,wsig_wd);
   wait ( start );
   $write("Testing %s: wexp=%0d, wsig_ac=%0d, wsig_in=%0d, wsig_wd=%0d\n",
          abbrev, wexp, wsig_ac, wsig_in, wsig_wd);
   for (int tn = 0; tn < n_tests; tn++ ) begin</pre>
      automatic int sidx = 0;
      automatic int hot = tn % 4;
      automatic int rnd = tn / 4;
      automatic int one_hot = rnd < n_one_hot;</pre>
      automatic int two_hot = !one_hot && rnd - n_one_hot < n_two_hot;</pre>
      automatic int sparse = one_hot || two_hot || {$random} & 1;
      automatic int h2 = ( hot + 1 + {<u>$random</u>}%3 ) % 4;
      real shadow_ia[4], shadow_w[4], shadow_o, diff, oreal, tol;
      real max diff;
      logic [3:0][wd-1:0] wht4;
      logic [1:0][ws-1:0] wht2;
      fmt = one_hot || two_hot ? ( 1<<hot ) | ( 1<<h2 )</pre>
      : sparse ? fmts[{$random}%6] : 4'hf;
      tol = sparse ? tol_s : tol_d;
      shadow_o = 0;
      for ( int i=0; i<4; i++ ) begin</pre>
         automatic real iav = real'({$random}) / ( 1 << 30 );</pre>
         automatic real w = real'({$random}) / (1 << 30);</pre>
         if ( one_hot || two_hot )
           begin
              iav = 1.0 + real'(i)/10;
              w = i == hot || two_hot && i == h2 ? hot_val[rnd] : 0;
```

```
\leftarrow \rightarrow \text{ Fall 2021} \qquad \leftarrow \rightarrow \text{ Homework 2}
```

```
end
      shadow_w[i] = w;
     shadow ia[i] = iav;
     wht4[i] = conv#(wexp,wsig_wd)::rtof(w);
      ia[i] = conv#(wexp,wsig in)::rtof(iav);
      if ( sparse && fmt[i] ) wht2[sidx++] = conv#(wexp,wsig_ws)::rtof(w);
     if ( fmt[i] ) shadow_o += iav * w;
   end
   wht = sparse ? wht2 : wht4;
   #1;
   oreal = conv#(wexp,wsig_ac)::ftor(o);
   diff = fabs( shadow_o - oreal ) / fabs( shadow_o ? shadow_o : 1 );
   max_diff = sparse ? max_diffs : max_diffd;
   if (! (diff < tol)) begin
      automatic int n_err = sparse ? ++n_errs : ++n_errd;
      if ( n_err < 5 || 0 && diff > max_diff ) begin
         automatic int ilast = fmt[3] ? 3 : fmt[2] ? 2 : 1;
         $write( "Error tn=%0d for fmt %4b %h = %7.4f != %7.4f (correct)\n",
                 tn, fmt, o, oreal, shadow_o );
                     ");
         $write( "
         for ( int i=0; i<4; i++ )</pre>
           if ( fmt[i] )
             $write( "%.4f %.4f%s", shadow_ia[i], shadow_w[i],
                     i < ilast ? " + " : "\n");
                     ");
         <u>$write(</u>"
         for ( int i=0; i<4; i++ )</pre>
          if ( fmt[i] )
           $write( "%.4f %s", shadow_ia[i] * shadow_w[i],
                   i < ilast ? " + " : "\n");
         if (0)
                        diff %.8f, tol %.8f\n",diff,tol);
           $write( "
         // Feel free to modify or add to this to help with your solution.
         $write( " acc1 = %h = %.4f\n",
                  nnsp.acc1, conv#(wexp,wsig_ac)::ftor(nnsp.acc1));
      end
   end
   if ( diff > max diff ) begin
      if ( sparse ) max_diffs = diff; else max_diffd = diff;
   end
end
<u>$write</u>("Done with %s %0d tests, %0d, %0d sp, den errors found.\n",
       abbrev, n_tests, n_errs, n_errd);
$write("For %s max diff %f, %f sp, den.\n",
      abbrev, max_diffs, max_diffd);
done = 1;
```

endmodule

```
module testbench_hy;
   localparam int n_tests = 5;
   localparam int w_sig_a = 10;
   localparam int w_sig_b = 20;
   localparam int w_sig_p = 25;
   localparam int w_exp = 5;
   localparam int wa = 1 + w_exp + w_sig_a;
   localparam int wb = 1 + w_exp + w_sig_b;
   localparam int wp = 1 + w_exp + w_sig_p;
   localparam int bias_hy = ( 1 << w_exp - 1 ) - 1;</pre>
   localparam int bias_sr = ( 1 << 8 - 1 ) - 1;</pre>
   localparam int bias_r = ( 1 << 11 - 1 ) - 1;</pre>
   localparam int w_sig_r = 52;
   localparam int w_exp_r = 11;
   localparam int w_sig_min = min3( w_sig_a, w_sig_b, w_sig_p );
   localparam real tol = 1.0 / ( longint'(1) << w_sig_min );</pre>
   logic [wa-1:0] a;
   logic [wb-1:0] b;
   uwire [wp-1:0] prod;
   hy_mult #(w_exp,w_sig_a,w_sig_b,w_sig_p) hm1(prod,a,b);
   initial begin
      automatic int n_err = 0;
      automatic real diff_max = 0;
      for (int i=0; i<n_tests; i++ ) begin</pre>
         automatic real a_shadow = real'(<u>$random()</u>) / (1<<31);</pre>
         automatic real b_shadow = real'(<u>$random()</u>) / (1<<31);</pre>
         automatic real prod_correct = a_shadow * b_shadow;
         real prodf, diff;
         a = conv#(w_exp,w_sig_a)::rtof(a_shadow);
         b = conv#(w_exp,w_sig_b)::rtof(b_shadow);
         #1;
         prodf = conv#(w_exp,w_sig_p)::ftor( prod );
         diff = fabs( prodf - prod_correct );
         if ( diff > diff_max ) diff_max = diff;
         if ( ! ( diff < tol ) ) begin</pre>
            n_err++;
            if (n_err < 4)
               $write( "Error for %.3f * %.3f: %.4f != %.4f (correct)\n",
                       a_shadow, b_shadow, prodf, prod_correct);
```

end

end

endmodule

// cadence translate_on

`default_nettype wire

`include "/apps/linux/cadence/GENUS211/share/synth/lib/chipware/sim/verilog/CW/CW_fp_mult.v" `include "/apps/linux/cadence/GENUS211/share/synth/lib/chipware/sim/verilog/CW/CW_fp_add.v"

LSU EE 4755

Homework 3 solution Due: 18 October 2021

To help solve the problems below, look at problems listed in the simple model slides, 2020 Homework 4, 2019 Midterm Exam Problem 2b and c, and especially 2018 Final Exam problems 1 and 2.

Problem 1: As requested in the subproblems below use the simple model to determine the cost and delay of the insert_at module from the solution to Homework 1 (see last page) instantiated with $wa = w_a$ and $wb = w_b$, and using $C_{lsb}(w_a)$ for the cost of the mask_lsb module and $D_{lsb}(w_a)$ for the delay of the mask_lsb module. The wo and walg parameters are not set so you can use their default values, $w_o = w_a + w_b$, $l_a = \lceil \lg(w_a + 1) \rceil$, and $l_b = \lceil \lg w_b \rceil$, in your answers.

For partial credit, and to help you solve the problems provide a sketch of the inferred hardware. It may help to first solve the problem for specific values of w_a and w_b , and then to generalize for arbitrary w_a and w_b .

(a) Find the cost and delay of the hardware inferred for the line of Verilog from insert_at shown below. Just for the hardware described on the line. There's no trick, this part is easy. Just remember to express your answers in terms of w_a , w_b , and w_o .

```
assign o = ia_high | ib_at_pos | ia_low;
```

Suppose for a moment that each of the quantities being ORd, ia_high, ib_at_pos, and ia_low, are w_o bits. Then for each of the w_o bit positions in o there will be a 3-input OR gate (or possibly two 2-input OR gates) and the total cost would be $2w_o u_c$. But while ia_high and ib_at_pos are w_o bits, ia_low is only w_a bits. So the cost of the hardware computing the low w_a bits of o will be $2w_a u_c$. Each of the remaining $w_o - w_a = w_b$ bits will just be an OR of a bit of ia_high with a bit of ib_at_pos, for a cost of $w_b u_c$. So the total cost will be $[2w_a + w_b] u_c$ or equivalently $[w_o + w_a] u_c$.

The low w_a bits are computed using either two 2-input OR gates or a 3-input OR gate, either way the delay is $2 u_t$. Note that the delay should be based on the critical path, and in this case it is one of the low w_a bits. I suppose it's nice that those other bits are computed in just $1 u_t$ but the important number is when all bits are done.

Grading Note: Many gave the delay as $\lceil \lg 3 \rceil u_t$. Normally I don't expect numbers to be computed for arithmetic expressions, but that's for complex ones. In this case, please just give the answer as 2, lest I assume you don't know what $\lceil \lg 3 \rceil u_t$ means.

Common Mistake: A common mistake was to OR together all $2w_o + w_a$ bits in one big OR gate, or perhaps two large OR gates. That's wrong because that's not what a bitwise OR does.

(b) Find the cost and delay of the shift_left module instances slc and slb taking into account any constant inputs and assuming that the synthesis program infers a logarithmic shifter. Don't forget that your answer must be in terms of w_a , w_b , w_o , l_a , and l_b , and that these denote the parameters of insert_at, not the parameters of the shifters. For more information on the logarithmic shifter see the additional material provided for the Set 1 lectures on the course lectures page.

Before cutting-and-pasting simple-model cost and delay expressions for a logarithmic shifter, take a close look at the parameters set for **slc** and **slb** and be sure to optimize for them. Notice that unlike typical shifters, the shift-out and shift-in ports are not the same size and that the shift amount is not necessarily ceiling-log-two of the input width.

Hint: The cost and delay for one of these shifters will be really easy to compute.

Notice that the shift amount connection (amt) to slc is an elaboration-time constant, wb. Therefore, the cost of slc is zero. A bit in the output ia_high is either connected to a bit of input ia_high_low or to the constant zero.

 $\leftarrow \rightarrow$ Homework 3

Grading Note: Most people did not see that the shifter required no hardware at all (other than something to generate a constant zero which would be optimized away). A few that did notice that the shift amount was zero did not properly optimize the multiplexors to which the shift amount is connected. If one of the data inputs of a mux is constant the cost drops from $3 u_c$ to $1 u_c$ per bits. But if the select input is constant the cost goes to zero. If that's not obvious please review what a mux does.

Next, consider slb, in which none of inputs are constant. The width of the input is w_b , the width of the output is w_o , and the input can be shifted by at most $2^{\lceil \lg(w_a+1) \rceil}$ bits. Let $l_a = \lceil \lg(w_a+1) \rceil$, that's the number of bits used to represent the shift amount. The value of the shift amount is at most $2^{l_a} - 1$.

A logarithmic shifter with an l_a -bit shift amount consists of l_a multiplexors, one multiplexor for each bit in the shift amount. Multiplexor 0 shifts by either 0 or $2^0 = 1$ bit, mux 1 shifts by either 1 or $2^1 = 2$ bits, mux *i* shifts by either 0 or 2^i bits, and mux $l_a - 1$ shifts by 0 or 2^{l_a-1} bits. In a conventional logarithmic shifter with $l_a = 4$, the input and output would each be $2^4 = 16$ bits, and as a whole the shifter could shift by an amount ranging from 0 bits to 15 bits (but not by 16 bits). (Why not 16 bits? That's a convention, but why not allow a shift amount that would shift away all of the bits. Good question, I'm sure it was debated.)

Lets consider the shifter needed for slb. Let the first multiplexor making up this shifter shift by 0 or 1 bits. In a conventional shifter the mux has two w-bit inputs and a w-bit output. But in slb the output will be larger than the input, w_o bits. So we need to make the mux large enough to handle the largest value produced at that stage. For the first stage, since it can shift by one bit, we need to make the mux $w_b + 1$ bits (remembering that input is w_b bits). The second mux can shift by 0 or 2 bits, and to it needs to be $w_b + 1 + 2 = w_b + 3$ bits. Because the output is w_o bits the maximum mux size is w_o bits, which will be the last mux. That last mux can shift by 0 or 2^{l_a-1} bits. (Because w_a and w_b are not constrained, it is not always true that $2^{l_a-1} = w_a/2$.) The diagram below shows such a shifter in which wi would be used for w_b and wamt would be used for l_a .



A general w-bit 2-input mux has cost $3w u_c$. But in a shifter some mux input bits are zero, and at those positions the cost is $1 u_t$ each. First lets assume that all bits have cost $w u_t$. Also, lets restrict ourselves to the case where $w_o = w_b + 2^{l_a - 1}$.

The cost under that assumption and restriction is

$$C_{\text{sl-noopt}}(w_b, w_o, l_a) = \sum_{i=0}^{l_a - 1} 3\left(w_b + \sum_{j=0}^{i} 2^j\right) u_c$$
$$= \sum_{i=0}^{l_a - 1} 3(w_b + 2^{i+1} - 1) u_c$$
$$= \left[3(w_b - 1)l_a + \frac{3}{2}(2^{l_a} - 1)\right] u_c$$

 $\leftarrow \rightarrow$ Homework 3

For a tighter cost estimate, consider the number of zero bits in stage i. Stage i shifts by 2^i bits and so 2^i zeros must be appended to the most-significant side of the unshifted input and 2^i zeros are appended to the least-significant side of the shifted input. So there are 2×2^i mux bits with a zero at either input, and so the cost is

 $[3(w_b + 2^{i+1} - 1) - 2 \times 2 \times 2^i] u_c \text{ or } [3(w_b + 2^{i+1} - 1) - 2 \times 2^{i+1}] u_c \text{ or } [3(w_b - 1) + (3 - 2)2^{i+1}] u_c \text{ or } [3(w_b - 1) + 2^{i+1}] u_c.$

The total cost is

$$C_{\text{sl-opt}}(w_b, w_o, l_a) = \sum_{i=0}^{l_a - 1} [3(w_b - 1) + 2^{i+1}] u_c$$
$$= [3(w_b - 1)l_a + \frac{1}{2}(2^{l_a} - 1)] u_c$$

Grading Note: No one computed the cost completely correctly. A small deduction, 0.5, was given for a cost of $w_o l_a u_c$ since that overstates the cost of all but the last mux. A much larger deduction was given if the cost was based on muxen that were too small.

The delay is far less tedious to compute because regardless of the size of each multiplexor, the critical path through a mux passes through two 2-input gates. Under the simple model their delay is $2 u_t$, and so the total delay is $2l_a u_t$. That's it.

(c) Find the cost and delay of insert_at. Use the answers above and work out cost and delay for the remaining hardware in the module. Don't forget to use $C_{lsb}(w_a)$ for the cost of the mask_lsb module and $D_{lsb}(w_a)$ for the delay of the mask_lsb module.

For this discussion refer to the insert_at module below which includes labels such as Line 1 in the comments. In the sub-problems above the cost and delay of hardware described by Lines 7, 5, and 6 has been found. The cost and delay of the ml instance, Line 1, are given in this problem as $C_{\rm lsb}(w_a)$ and $D_{\rm lsb}(w_a)$. The Verilog on Line 4 is executed at elaboration time and so does not describe hardware. All that remains to work out is the hardware described on Lines 2 and 3.

Each of these lines is a bitwise AND of two w_a -bit quantities, for a cost of $w_a u_c$ each. Their delay is $1 u_t$. Combining all of these yields the total cost,

$$C_{\text{insertat}}(w_a, w_b) = \begin{bmatrix} C_{\text{lsb}}(w_a) + 2w_a + 0 \end{bmatrix} + 3(w_b - 1)l_a + \frac{1}{2}(2^{l_a} - 1) + 2w_a + w_b \end{bmatrix} u_c$$

Collecting terms and using $C_{\rm lsb}$ from the problem below:

$$\begin{split} C_{\text{insertat}}(w_a, w_b) &= \left[C_{\text{lsb}}(w_a) + 2w_a + 0 + 3(w_b - 1)l_a + \frac{1}{2}(2^{l_a} - 1) + 2w_a + w_b \right] \, \mathbf{u}_{\mathbf{c}} \\ &= \left[w_a + 2^{l_a} - 4 + 2w_a + 0 + 3(w_b - 1)l_a + \frac{1}{2}(2^{l_a} - 1) + 2w_a + w_b \right] \mathbf{u}_{\mathbf{c}} \\ &= \left[w_a + w_a - 4 + 2w_a + 0 + 3(w_b - 1)l_a + \frac{1}{2}(w_a - 1) + 2w_a + w_b \right] \mathbf{u}_{\mathbf{c}} \\ &= \left[6.5w_a - 4.5 + 3(w_b - 1)l_a + w_b \right] \mathbf{u}_{\mathbf{c}} \\ &= \left[3(w_b - 1)l_a + w_b + 6.5w_a - 4.5 \right] \mathbf{u}_{\mathbf{c}} \end{split}$$

The dominant term is $3w_b l_a$, which isn't so bad.

```
// SOLUTION -- Line numbers are referenced in the solution discussion.
module insert_at #( int wa = 20, wb = 10, wo = wa+wb, walg = $clog2(wa+1) )
   ( output logic [wo-1:0] o,
    input uwire [wa-1:0] ia, input uwire [wb-1:0] ib,
    input uwire [walg-1:0] pos );
  uwire [wa-1:0] mask_low;
  mask_lsb #(wa) ml(mask_low, pos);
                                             // Line 1.
  uwire [wa-1:0] ia_low = ia & mask_low;
                                             // Line 2.
  uwire [wa-1:0] ia_high_low = ia & ~mask_low; // Line 3.
  localparam int wblg = $clog2(wb); // Line 4. No Hardware. (Computed during elaboration.)
  uwire [wo-1:0] ia_high;
  shift_left #(wa,wo,wblg) slc( ia_high, ia_high_low, wblg'(wb) ); // Line 5
  uwire [wo-1:0] ib_at_pos;
  shift_left #(wb,wo,walg) slb( ib_at_pos, ib, pos ); // Line 6
  assign o = ia_high | ib_at_pos | ia_low;
                                                                  // Line 7
```

endmodule

To find the total delay we need to find the critical path. Note: Emphasis added after grading. The critical path is easy to find because the parts taking a substantial amount of time, ml (the mask_lsb instance) and slb, connect only to insert_at module inputs. The default assumption for timing analysis is that module inputs arrive at t = 0, and so the output of ml is available at $D_{lsb}(w)$ and the output of slb is available at $2l_a$ ut. Peeking ahead to the solution of the next problem, we know that ml has a delay of l_a ut.

The output of both ml and slb each connect only to the o expression, Line 7, and so the critical path is from slb to Line 7. That would add a delay of 1 (if connected intelligently), and so the delay is $D_{\text{insertat}}(w_a, w_b) = [2l_a+1] u_t$, where $l_a = \lceil \lg(w_a + 1) \rceil$.

Problem 2: Some of you may have seen this coming: Find expressions for $C_{lsb}(w)$, the cost of the mask_lsb module and $D_{lsb}(w)$, the delay of the mask_lsb module, in both cases wo = w, where wo is the parameter used in the mask_lsb definition. Assume a well-optimized design, not something that uses $w [\lg w]$ -bit magnitude comparison units.

Hint: Think about the problem for about 30 minutes, then look at 2018 Final Exam Problems 1 and 2.

The gtd_rec module from the 2018 final exam is similar to mask_lsb but has three differences. In mask_lsb the input value, n1, specifies that there should be n1 ones followed by Zeros. In gtd the input value, iter, specifies that there should be iter+1 zeros followed by ones. The second difference (or a consequence of the first) is that while the output of mask_lsb can be all zeros or all ones, the output of gtd_rec must have at least one zero. Finally, gtd_rec can only be instantiated at power-of-two sizes.

Those minor differences are easy to fix. For example, inverting the output (change each zero to a one) will fix the first difference. The non-power-of-two issue can be fixed by making sure that the size of the recursive instantiation is always a power of two. The initial instantiation does not have to be a power of two. Also a special case can be added to the initial instantiation to handle the all ones case.

I'm tempted to show the recursive version of mask_lsb, but I might make it a midterm exam problem. (Not the whole thing, just a small part.) If I do I'll provide a warning in class on Monday, 25 October 2021.

 $\leftarrow \rightarrow$ Homework 3

For cost, the easiest thing to do is assume that w is a power of 2 and then just use the expressions from the exam. Using this assumption: $C_{\rm lsb}(w) = [2w - 4] u_c$. For arbitrary positive w the cost of the initial instantiation is $w u_c$ and the cost of the recursive instantiation (one level down) is $2^{\lceil \lg w \rceil - 1} u_c$. The terminal case for recursion is for w = 2, and the cost of that hardware is zero under the simple model. So the summation will end at w = 4 (which is i = 2 in the summation). The total cost is

$$C_{\rm lsb}(w) = [w + \sum_{i=l_w-1}^{2} 2^i] u_{\rm c}$$
$$= [w + 2^{l_w} - 4] u_{\rm c}$$

where $l_w = \lceil \lg w \rceil$.

Each level has a delay of 1, and so the total delay is $[\lceil \lg w \rceil - 1] u_t$ for $w \ge 4$.

An uncommented Homework 1 solution appears below. For the full version visit https://www.ece.lsu.edu/koppel/v/2021/hw01-sol.v.html.

```
module insert at
  #( int wa = 20, wb = 10, wo = wa+wb, walg = clog2(wa+1) )
   ( output logic [wo-1:0] o,
     input uwire [wa-1:0] ia,
     input uwire [wb-1:0] ib,
     input uwire [walg-1:0] pos );
   uwire [wa-1:0] mask_low;
   mask_lsb #(wa) ml(mask_low, pos);
   uwire [wa-1:0] ia_low = ia & mask_low;
   uwire [wa-1:0] ia_high_low = ia & ~mask_low;
   localparam int wblg = $clog2(wb);
   uwire [wo-1:0] ia_high;
   shift_left #(wa,wo,wblg) slc( ia_high, ia_high_low, wblg'(wb) );
   uwire [wo-1:0] ib_at_pos;
   shift_left #(wb,wo,walg) slb( ib_at_pos, ib, pos );
   assign o = ia_high | ib_at_pos | ia_low;
endmodule
module shift left
  #( int wi = 4, wo = wi, wolg = $clog2(wo) )
   ( output uwire [wo-1:0] o,
     input uwire [wi-1:0] i,
     input uwire [wolg-1:0] amt );
   assign o = i << amt;</pre>
endmodule
module mask lsb
  #(int wo = 6, wp = (clog2(wo+1)))
   ( output logic [wo-1:0] o, input uwire [wp-1:0] n1 );
   always_comb for ( int i=0; i<wo; i++ ) o[i] = i < n1;</pre>
endmodule
```

LSU EE 4755 Homework 4 solution Due: 11 November 2021

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2021/hw04.v.html.

Problem 0: If necessary, follow the instructions at https://www.ece.lsu.edu/koppel/v/proc.html to set up your class account, copy the assignment, and run the Verilog simulator and synthesis program on the unmodified homework file, hw04.v. Do this early enough so that minor problems (*e.g.*, password doesn't work) are minor problems.

Teamwork

Students can work on this assignment in teams. Each student should submit his or her own assignment but list team members. It is recommended that one team member be responsible for learning SimVision.

Every member of a team that has completed a project, must be capable of re-solving the problem. It is recommended that all team members re-solve the problem on their own for their own pedagogical benefit.

Problem 1: Module bit_keeper has a w_b -bit output bits ($_b$ is for width of buffer) and a 1-bit output ready. Think of output bits as a long bit vector (w_b bits long) that is edited using the module's inputs. Commands to edit bits are given using four-bit input cmd (command), w_i -bit input din (data in), and w_s -bit input pos (position). The module is to operate sequentially using input clk.

Complete bit_keeper as described below, and make sure that it is synthesizable. As always, code should be written clearly, and designs should not be costly or slow.

When completed bit_keeper should operate as follows. On a positive edge of clk action is taken based on the value of cmd. The possible values of cmd are: Cmd_Reset, Cmd_None, Cmd_Write, and Cmd_Rot_To. (These can be used as constants in your code. The constants are defined by enum Command.) Some commands will be complete in one cycle (the cycle in which the cmd is set up to the positive edge of clk). Other commands will take multiple cycles.

Be sure to understand the details of how multi-cycle commands execute. When a multi-cycle command starts the ready output must be set to zero and must be held at zero until the command completes. The command and its arguments will only be held at the inputs for one cycle, and so at the next positive clock edge they will be gone. The cmd input will be set to Cmd_Nop, and the pos and din inputs will be set to random values. This means that the inputs of multi-cycle commands that will be needed in subsequent cycles must be saved in registers.

The testbench can emit a trace of commands and their effects. This trace is used below to illustrate what the module is supposed to do. The trace is collected after the command completes. A trace entry starts with the word Cycle. The cycle number is shown, followed by command details, followed by the state of bits.

For Cmd_Reset output bits should be set to zero. Also, any internal registers should be set to zero. The command should complete at the positive edge. This should set ready to 1. In the trace below the reset command set bits back to zero. Notice that the command completes in one cycle (based on the cycle numbers).

Cycle	307	 test	73:	Cmd_Nop	:	bits = 01	401f4
Cycle	308	 test	74:	Cmd_Reset	:	bits = 00	00000

For Cmd_Rot_To the value in bits must be rotated so that the contents of bits[0] is moved to bits[pos], bits[1] is moved to bits[(pos+1)%wb], and so on. This is like a left shift of pos bits, except that the most significant pos bits of bits are rotated into the the pos least significant bits. In the trace below the rotate command rotates four bits (one hexadecimal digit). Notice that the most-significant digit on the first line is rotated to the least significant digit after the rotation command.

Cycle 301 test 7	1: Cmd_Nop	: bits = 401401f
Cycle 306 test 7	2: Cmd_Rot_To pos 4	: bits = 01401f4

This rotation **must be performed** using two instances of module **rot_left**. One instance should rotate by 1, the other rotates by a larger value, call it r_b , of your choosing. Each clock cycle the value of **bits** is rotated using one of these, but never both in the same clock cycle. Use the r_b -bit rotate instance until the number of bit positions to shift is $\leq r_b$, then use the 1-bit rotate instance.

Command Cmd_Write has two forms based on the value of input pos. If pos is zero then the least significant w_b bits of **bits** should be written with **din**. This should complete at the positive edge. Otherwise, bits pos through pos+wi-1 of bits should be written with dim—but not directly. Instead, bits should be rotated so that bit pos is at the least-significant position, then the data should be written, then **bits** should be rotated back to its original position. Use only the two rot_left instances.

The trace below shows a write with pos=0:

Cycle	417		test	86:	Cmd_Nop				:	bits	=	0000240000
Cycle	418		test	87:	Cmd_Write	pos O,	data	7	:	bits	=	0000240007
W	hen j	pos	is nor	n-zero	the writes t	take long	er:					
Cycle	96		test	20:	Cmd_Nop				:	bits	=	0a000003c
Cycle	107		test	21:	Cmd_Write	pos 27	, data	4	:	bits	=	0a2000003c

No action is needed for command Cmd_Nop. In fact, this is the command that will be present while the external hardware, including the testbench, is waiting for other commands to complete.

The testbench will test **bit_keeper** at two sizes. At each size detailed information is given for the first few errors. That includes a trace of commands leading up to the error, followed by the erroneous command, and what the bits should have been. After each error the testbench sets its shadow value of **bits** to the erroneous output so that subsequent tests can pass. Here is in example of the output:

```
Cycle 22 -- test
                  0: Cmd_Rot_To pos 20
                                               : bits = 000000000
Cycle 54 -- test
                  1: Cmd_Rot_To pos 31
                                               : bits = 000000000
Cycle 55 -- test
                  2: Cmd_Nop
                                               : bits = 000000000
                  3: Cmd_Write pos 37, data 2 : bits = 4000000000
Cycle 96 -- test
                  4: Cmd_Nop
Cycle 97 -- test
                                               : bits = 400000000
                  5: Cmd_Rot_To pos 5
                                               : bits = 000000008
Cycle 103 -- test
                  6: Cmd_Write pos 0, data 3
                                              : bits = 000000003
Cycle 104 -- test
Error in test 7: Cmd_Write pos 1, data 2 : 0000000c04 != 0000000005 (correct)
```

For multi-cycle commands the testbench will wait for ready to go to zero and then back to one. If that does not happen after a certain number of cycles the testbench will *timeout*, meaning that it will give up waiting and print a CYCLE LIMIT EXCEEDED message. If there is a timeout while a command is in progress (meaning that **ready** did go to zero, but did not return to one) the testbench will show a trace of recent history, followed by an indication of what it was waiting for: Exit from clock loop at cycle 16000, limit 16000, ** CYCLE LIMIT EXCEEDED **

```
** Preceding Commands **
Cycle 7 -- test 0: Cmd_Rot_To pos 20 : bits = 000000000
Cycle 14 -- test 1: Cmd_Rot_To pos 31 : bits = 0000000000
Cycle 15 -- test 2: Cmd_Nop : bits = 0000000000
** In-Progress Command **
test 3: Cmd_Write pos 37, data 2
-- Awaiting ready = 1.
```

If the testbench does not timeout then it will print a tally of the number of errors after testing each bit_keeper instance. Also, as a measure of quality, the testbench reports the average number of cycles to perform Cmd_Rot_To and Cmd_Write (with non-zero pos). For example,

```
Starting tests for (wb=40,wi=4)
Finished 200 tests for (wb=40,wi=4), 0 errors.
Avg cyc Cmd_Rot_To 5.5 (67) Cmd_Write 10.6 (35)
```

```
Starting tests for (wb=28,wi=8)
Finished 140 tests for (wb=28,wi=8), 0 errors.
Avg cyc Cmd_Rot_To 4.2 (57) Cmd_Write 8.2 (18)
```

The lines starting Avg cyc report timing. The number in parentheses is the number of times the command was issued. So for the first set of tests Cmd_Rot_To was tried 67 times, and the average number of cycles taken to complete it was 5.5.

A lower number for Avg cyc can indicate a good design, or that certain rules were not followed.

It is very important that debugging tools are used. Take advantage of the testbench messages to see what is going wrong. Run SimVision to get a detailed look at what your module is doing.

The solution has been copied to the homework directory, and an htmlized version has been posted at https://www.ece.lsu.edu/koppel/v/2021/hw04-sol.v.html. For the discussion below the solution is shown in pieces, shorn of most comments. Following that is the complete solution. The solution starts by specifying rotate amounts for the two rotation modules, followed by their instantiation.

```
localparam int rot_amt_a = 1;
localparam int rot_amt_b = 1 << ( ws >> 1 );
uwire [wb-1:0] ra, rb;
rot_left #(wb,rot_amt_a) rl1(ra,bits);
rot_left #(wb,rot_amt_b) rl8(rb,bits);
```

The rotate amount of the first module is set to 1, but a localparam is used for its value. To minimize the number of rotations the rotate amount for the second module, **rot_amt_b**, should be set to the square root of **wb**. To minimize delay it should be set to a power of 2. Here it is set to a power of 2 close to the square root of **wb**.

Rotations are to be done over several cycles. As stated in the problem commands are presented at the inputs for just for one cycle, and are then replaced with a Cmd_Nop until the ready returns to 1. To remember what needs to be done three registers will be used, rot_to_do, rot_to_return, and wval. Register rot_to_do is set to the number of bits of rotation that still need to be done. For Cmd_Rot_To it is initialized to pos and for Cmd_Write with pos!=O it is initialized to wb - pos. Register rot_to_return is set to the amount of rotation needed after the write is performed. Register wval is the value to write.

The ready output is set to 1 when both rot_to_do and rot_to_return are both Zero.

```
logic [ws-1:0] rot_to_do; // Remaining amount of rotation to do.
logic [ws-1:0] rot_to_return; // Amount of rotation needed after write.
```

```
logic [wi-1:0] wval;
                            // Value to write.
assign ready = rot_to_do == 0 && rot_to_return == 0;
```

The main always_ff has just a single case statement. Cmd_Reset is straightforward:

```
always_ff @( posedge clk ) begin
   case ( cmd )
    Cmd_Reset: begin
        bits = 0;
        rot_to_do = 0;
       rot_to_return = 0;
     end
```

For Cmd_Rot_To the rotate amount is saved in rot_to_do. The work of rotating is done when cmd is Cmd_Nop.

Cmd_Rot_To: begin rot_to_do = pos; end

What Cmd_Write does depends on pos. If it's zero the write is done immediately. Otherwise rot_to_do is set to an amount that will bring bit **pos** to the least-significant position. Variable **rot_to_return** is set to the rotation to use after the write completes, one which moves the least-significant bit back to where it was. Also, the write value is saved.

```
Cmd_Write:
  if ( pos == 0 ) begin
    bits[wi-1:0] = din;
  end else begin
    rot_to_do = wb - pos;
     wval = din;
    rot_to_return = pos;
  end
```

The work of rotating is done when cmd is set to Cmd_Nop. If rot_to_do is non-zero (which means \geq rot_amt_a) then **bits** is set to the output of the appropriate rotation module and **rot_to_do** is decremented. Note that the rotation being performed can be for one of three purposes: a Cmd_Rot_To, the rotation before a write, or the rotation after a write.

```
Cmd_Nop: begin
  if ( rot_to_do >= rot_amt_b ) begin
     bits = rb; // Use output of larger rot module.
     rot_to_do -= rot_amt_b; // Decrement remaining rot amt.
  end else if ( rot_to_do >= rot_amt_a ) begin
     bits = ra; // Use output of smaller rot module.
     rot_to_do -= rot_amt_a; // Decrement remaining rot amt.
  end
 // More Cmd_Nop code below
```

Next, Cmd_Nop needs to check whether a write needs to be done now. (A write needs to be done if rot_to_return is non-zero and it needs to be done now if also rot_to_do is zero.) If so, the write is performed and rot_to_do is set so that **bits** is rotated back to its original position.

```
if ( rot_to_do == 0 && rot_to_return !=0 ) begin
  bits[wi-1:0] = wval;
  rot_to_do = rot_to_return;
  rot_to_return = 0;
```

The entire solution with more comments appears below.

Grading Notes: In many solutions there were three separate pieces of code to perform rotate: one used for Cmd_Rot_To, one used before a write, and one used after a write. That code duplication makes it harder for humans to read, and could also lead to more costly and slower designs.

```
module bit_keeper
```

```
#( int wb = 64, wi = 8, ws = $clog2(wb) )
( output logic [wb-1:0] bits,
   output uwire ready,
   input uwire [3:0] cmd,
   input uwire [wi-1:0] din,
   input uwire [ws-1:0] pos,
   input uwire clk );
```

```
/// SOLUTION
```

```
// Specify Rotation Amounts
11
localparam int rot_amt_a = 1;
localparam int rot_amt_b = 1 << ( ws >> 1 );
11
// To minimize the number of rotations, rot_amt_b should be set to
// the square root of wb. But, to minimize delay it should be set
// to a power of 2. Here it is set to a power of 2 close to the
// square root of wb.
// Instantiate Rotation Modules
11
uwire [wb-1:0] ra, rb;
rot_left #(wb,rot_amt_a) rl1(ra,bits);
rot_left #(wb,rot_amt_b) rl8(rb,bits);
logic [ws-1:0] rot_to_do; // Remaining amount of rotation to do.
logic [ws-1:0] rot_to_return; // Amount of rotation needed after write.
                              // Value to write.
logic [wi-1:0] wval;
// The module is ready if there is no remaining rotation to do.
11
assign ready = rot_to_do == 0 && rot_to_return == 0;
```

```
always_ff @( posedge clk ) begin
   case ( cmd )
     Cmd_Reset: begin
        11
        // Perform Reset
        bits = 0;
        rot_to_do = 0;
        rot_to_return = 0;
     end
     Cmd_Rot_To: begin
        11
        // Set Amount of Rotation
        11
        // The rotation will be performed in subsequent cycles.
        rot_to_do = pos;
     \operatorname{end}
     Cmd_Write:
       if ( pos == 0 ) begin
          11
          // Perform Write Immediately
          bits[wi-1:0] = din;
       end else begin
          11
          // Perform Write Later
          // Set amount of rotation needed before the write, ...
          11
          rot_to_do = wb - pos;
          11
          // .. save the value that will be written, ..
          11
          wval = din;
          11
          /\!/ .. and save the amount of rotation needed after the write.
          11
          rot_to_return = pos;
```

```
Cmd_Nop: begin
   11
  // Continue Executing a Cmd_Rot_To or Cmd_Write.
   // If necessary, set bits to a rotated value.
   11
   if ( rot_to_do >= rot_amt_b ) begin
      11
      // Still need to rotate by at least rot_amt_b bits.
                                // Use output of larger rot module.
      bits = rb;
      rot_to_do -= rot_amt_b; // Decrement remaining rot amt.
   end else if ( rot_to_do >= rot_amt_a ) begin
      11
      // Still need to rotate by at least rot_amt_a (1) bit.
                                // Use output of smaller rot module.
      bits = ra;
      rot_to_do -= rot_amt_a; // Decrement remaining rot amt.
   end
   // Check whether a write is pending and can now be performed.
   11
   if ( rot_to_do == 0 && rot_to_return !=0 ) begin
      11
      // Write value, and set amount of rotation to return to
      // original positioning.
      bits[wi-1:0] = wval;
      rot_to_do = rot_to_return;
      rot_to_return = 0;
   end
```

endcase

end

endmodule

```
11
/// LSU EE 4755 Fall 2021 Homework 4
11
/// SOLUTION
 /// Assignment https://www.ece.lsu.edu/koppel/v/2021/hw04.pdf
 /// Solution Discussion https://www.ece.lsu.edu/koppel/v/2021/hw04_sol.pdf
`default_nettype none
/// Problem1
11
     Complete bit_keeper so that it applies input commands as described
111
111
    in the handout.
111
11
11
      [.] Only modify module bit_keeper.
11
      [...] Instantiate two rot_left instances two rotate bits.
      [✓] APPLY AT MOST ONE rotate per cycle.
11
      [~] ONLY WRITE DATA to the least-significant w bits.
11
11
      [...] Use SimVision to debug. Use command: xrun -gui hw04.v
11
11
      [...] Make sure that the testbench does not report errors.
11
11
      [/] Module must be synthesizable. Use command: genus -files syn.tcl
11
      [<] Don't assume any particular parameter values.</pre>
11
11
      [<] Code must be written clearly.</pre>
11
      [.] Pay attention to cost and performance.
11
11
11
      [] Students can work in teams. List team members in this file
typedef enum
  { Cmd Reset = 0, Cmd Nop, Cmd Write, Cmd Rot To, Cmd SIZE } Command;
module rot_left
 #(int w = 10, amt = 1)
   ( output uwire [w-1:0] r, input uwire [w-1:0] a);
  assign r = \{ a[w-amt-1:0], a[w-1:w-amt] \};
endmodule
module bit_keeper
 \#( int wb = 64, wi = 8, ws = \frac{clog2}{wb} )
  ( output logic [wb-1:0] bits,
    output uwire ready,
    input uwire [3:0] cmd,
    input uwire [wi-1:0] din,
    input uwire [ws-1:0] pos,
```

```
input uwire clk );
```

/// SOLUTION

```
// Specify Rotation Amounts
11
localparam int rot_amt_a = 1;
localparam int rot_amt_b = 1 << ( ws >> 1 );
11
// To minimize the number of rotations, rot amt b should be set to
// the square root of wb. But, to minimize delay it should be set
// to a power of 2. Here it is set to a power of 2 close to the
// square root of wb.
// Instantiate Rotation Modules
11
uwire [wb-1:0] ra, rb;
rot_left #(wb,rot_amt_a) rl1(ra,bits);
rot left #(wb,rot_amt_b) rl8(rb,bits);
logic [ws-1:0] rot_to_do;
                            // Remaining amount of rotation to do.
logic [ws-1:0] rot_to_return; // Amount of rotation needed after write.
logic [wi-1:0] wval;
                               // Value to write.
// The module is ready if there is no remaining rotation to do.
11
assign ready = rot_to_do == 0 && rot_to_return == 0;
always_ff @( posedge clk ) begin
   case ( cmd )
     Cmd_Reset: begin
        11
        // Perform Reset
        bits = 0;
        rot_to_do = 0;
        rot_to_return = 0;
     end
     Cmd_Rot_To: begin
        11
        // Set Amount of Rotation
        11
        // The rotation will be performed in subsequent cycles.
        rot_to_do = pos;
     end
     Cmd_Write:
       if ( pos == 0 ) begin
          11
          // Perform Write Immediately
          bits[wi-1:0] = din;
```

```
end else begin
    11
     // Perform Write Later
     // Set amount of rotation needed before the write, ...
     11
    rot_to_do = wb - pos;
     11
    // .. save the value that will be written, ..
     11
    wval = din;
     11
     // .. and save the amount of rotation needed after the write.
    11
     rot_to_return = pos;
  end
Cmd_Nop: begin
   11
   // Continue Executing a Cmd_Rot_To or Cmd_Write.
   // If necessary, set bits to a rotated value.
   11
   if ( rot_to_do >= rot_amt_b ) begin
     11
      // Still need to rotate by at least rot_amt_b bits.
      bits = rb;
                                // Use output of larger rot module.
      rot_to_do -= rot_amt_b; // Decrement remaining rot amt.
   end else if ( rot_to_do >= rot_amt_a ) begin
      11
      // Still need to rotate by at least rot_amt_a (1) bit.
      bits = ra;
                                // Use output of smaller rot module.
      rot_to_do -= rot_amt_a; // Decrement remaining rot amt.
   end
   // Check whether a write is pending and can now be performed.
   //
   if ( rot_to_do == 0 && rot_to_return !=0 ) begin
      11
      // Write value, and set amount of rotation to return to
      // original positioning.
      bits[wi-1:0] = wval;
      rot_to_do = rot_to_return;
      rot_to_return = 0;
   end
end
```

endcase

endmodule


```
// cadence translate_off
```

```
program reactivate
  (output uwire clk_reactive, output int cycle_reactive,
    input uwire clk, input var int cycle);
   assign clk_reactive = clk;
   assign cycle_reactive = cycle;
endprogram
```

module testbench;

```
localparam int npsets = 2;
localparam int pset[npsets][2] =
                     '{ { 40, 4 }, { 28, 8 } };
int t_errs; // Total number of errors.
initial t_errs = 0;
final $write("Total number of errors: %0d\n",t_errs);
uwire d[npsets:-1]; // Start / Done signals.
assign d[-1] = 1; // Initialize first at true.
// Instantiate a testbench at each size.
//
for ( genvar i=0; i<npsets; i++ )
        testbench_n #(pset[i][0],pset[i][1]) t2( .done(d[i]), .tstart(d[i-1]) );
```

endmodule

```
module testbench_n
#( int bsize = 40, isize = 5 )
  ( output logic done, input uwire tstart );

  localparam int bslg = $clog2(bsize);
  localparam int n_tests = bsize * 5;
  localparam int cyc_max = n_tests * bsize * 2;
  bit clk;
  int cycle, cycle_limit;
  logic clk_reactive;
  int cycle_reactive;
  int cycle_reactive;
```

```
\leftarrow \rightarrow Fall 2021
                   \leftarrow \rightarrow Homework 4
                                               Homework Solution Sol Code
          cmd_str[Cmd_Nop] = "Cmd_Nop";
          cmd_str[Cmd_Write] = "Cmd_Write";
          cmd_str[Cmd_Rot_To] = "Cmd_Rot_To";
       end
       string event_trace, history_trace;
       initial begin
          clk = 0;
          cycle = 0;
          done = 0;
          cycle_limit = cyc_max;
          wait( tstart );
          fork
             while ( !done ) #1 cycle += clk++;
             wait( cycle >= cycle_limit ) begin
                $write("Exit from clock loop at cycle %0d, limit %0d, %s\n",
                        cycle, cycle_limit, "** CYCLE LIMIT EXCEEDED **");
                $write("** Preceding Commands **\n%s", history_trace);
                $write("** In-Progress Command **\n%s\n", event_trace);
             end
          join_any;
          done = 1;
       end
       uwire [bsize-1:0] bits;
       uwire rdy;
       bit [bsize-1:0] bits_shadow, bcpy;
      logic [bslg-1:0] pos;
       logic [3:0] cmd;
       logic [isize-1:0] din;
       bit keeper #(bsize,isize) bk1(bits, rdy, cmd, din, pos, clk);
       typedef struct {int pos; int lat_cnt[int];} Lat_Range;
       Lat_Range lat_range[Cmd_SIZE][int];
       Lat_Range pos_range[Cmd_SIZE][int];
       initial begin
          automatic int n_err = 0;
          int n_cmd[Cmd_SIZE], n_cyc[Cmd_SIZE];
          int n_cycles;
          string cmd_info;
          for ( int i=0; i<Cmd_SIZE; i++ ) begin n_cmd[i] = 0; n_cmd[i] = 0; end</pre>
          cmd = Cmd_Reset;
          bits_shadow = bsize'(0);
          wait( tstart );
```

```
\leftarrow \rightarrow Fall 2021
                   \leftarrow \rightarrow Homework 4
                                                 Homework Solution Sol Code
          $write("\nStarting tests for (wb=%0d,wi=%0d)\n",bsize,isize);
          @( negedge clk_reactive );
          @( negedge clk_reactive );
          cmd = Cmd_Nop;
          while ( rdy !== 1'b1 ) @( negedge clk_reactive );
          for ( int tn = 0; tn < n_tests; tn++ ) begin</pre>
             bit expect rdy 0;
             logic [bslg-1:0] pos_given;
             logic [3:0] cmd_given;
             event_trace = <u>$sformatf</u>("test %2d: ",tn);
              cmd = {<u>$random</u>} % ( Cmd_SIZE - 1 ) + 1;
              if ( ( {$random} & 15 ) == 0 ) cmd = Cmd_Reset;
             pos = {<u>$random</u>} % (bsize-1) + 1;
             if ( cmd == Cmd_Write && ( {<u>$random</u>} & 1 ) == 0 ) pos = 0;
             din = {<u>$random</u>};
              cmd_given = cmd;
             pos_given = pos;
             event_trace = { event_trace, <u>$sformatf("%-10s ",cmd_str[cmd]) };</u>
              case ( cmd )
                Cmd_Reset: begin
                   bits_shadow = 0; expect_rdy_0 = 0;
                end
                Cmd_Write: begin
                   event_trace =
                     { event_trace,
                       $sformatf("pos %0d, data %h", pos_given, din) };
                   expect_rdy_0 = pos != 0;
                   for ( int i=0; i<isize; i++ )</pre>
                     bits_shadow[(i+pos)%bsize] = din[i];
                end
                Cmd_Rot_To: begin
                   event_trace =
                     { event_trace,
                       $sformatf("pos %0d", pos_given) };
                   expect_rdy_0 = pos != 0;
                   bcpy = bits_shadow;
                   for ( int i=0; i<bsize; i++ )</pre>
                     bits_shadow[(i+pos)%bsize] = bcpy[i];
                end
                Cmd_Nop: begin
                   expect_rdy_0 = 0;
                end
                default begin
                   $write("This can't happen.\n");
                   $fatal(1);
                end
              endcase
```

```
cmd_info = event_trace;
```

```
\leftarrow \rightarrow Fall 2021
                  \leftarrow \rightarrow Homework 4
                                                Homework Solution Sol Code
             event_trace = { event_trace, "\n" };
             @( negedge clk_reactive );
             // Wait for rdy to go to zero.
             if ( expect_rdy_0 )
               begin
                  automatic int cyc_start = cycle;
                  event_trace = { cmd_info, "\n -- Awaiting ready = 0.\n" };
                  while ( rdy !== 1'b0 ) @( negedge clk reactive );
                  event_trace = { cmd_info, "\n -- Awaiting ready = 1.\n" };
                  cmd = Cmd_Nop;
                  pos = {<u>$random</u>};
                  din = {<u>$random</u>};
                  while ( rdy !== 1'b1 ) @( negedge clk_reactive );
                  event_trace = { cmd_info, "\n -- About to check outputs.\n" };
                  n_cycles = cycle - cyc_start;
               end else begin
                  n_cycles = 0;
               end
             if ( bits_shadow === bits ) begin
                if ( expect_rdy_0 ) begin
                   n_cmd[cmd_given]++;
                   n_cyc[cmd_given] += n_cycles;
                   lat_range[cmd_given][pos_given].lat_cnt[n_cycles]++;
                   pos_range[cmd_given][n_cycles].lat_cnt[pos_given]++;
                end
             end else begin
                n_err++;
                if ( n_err < 5 ) begin</pre>
                   $write("%s",history_trace);
                    $write("Error in %-35s: %h != %h (correct)\n",
                           cmd_info, bits, bits_shadow);
                end
                history_trace = "";
                bits_shadow = bits;
             end
             if ( cmd_given == Cmd_Reset ) history_trace = "";
             history_trace =
               { history_trace,
                 $sformatf("Cycle %3d -- %-35s: bits = %h\n",
                            cycle, cmd_info, bits) };
          end
          <u>$write</u>("Finished %0d tests for (wb=%0d,wi=%0d), %0d data errors.\n",
                 n_tests, bsize, isize, n_err );
          begin
             automatic bit double_check = 0;
             automatic Command mcc[] = '{ Cmd_Rot_To, Cmd_Write };
             automatic string err_str =
               $sformatf("Error: (wb=%0d,wi=%0d)",bsize,isize);
```

```
<u>$write</u>("Avg cyc");
```

```
foreach ( mcc[i] )
     $write(" %s %.1f (%0d)",
            cmd_str[mcc[i]],
            n_cmd[mcc[i]] ? real'(n_cyc[mcc[i]])/n_cmd[mcc[i]] : 0.0,
            n_cmd[mcc[i]]);
   $write("\n");
   if ( double_check ) begin
   $write("Avg cyc");
   foreach ( mcc[i] ) begin
      automatic Command c = mcc[i];
      automatic int tot_cyc = 0, tot_cmd = 0;
      foreach ( lat_range[c][pos] ) begin
         foreach ( lat_range[c][pos].lat_cnt[nc] ) begin
            automatic int ncmd = lat_range[c][pos].lat_cnt[nc];
            tot_cyc += nc * ncmd;
            tot_cmd += ncmd;
         end
      end
      $write(" %s %.1f (%0d)",
             cmd_str[mcc[i]],
             real'(tot_cyc)/tot_cmd, tot_cmd);
   end
   end
   $write("\n");
   foreach ( mcc[i] ) begin
      automatic Command c = mcc[i];
      automatic int n_one = 0, n_zero = 0;
      string n_z_str, n_o_str;
      n_o_str = <u>$sformatf</u>(" %s 1-cyc pos ",cmd_str[c]);
      foreach ( pos_range[c][1].lat_cnt[pos] ) begin
         n_o_str = { n_o_str, <u>$sformatf</u>("%0d ",pos) };
         n_one++;
      end
      n_z_str = <u>$sformatf(" %s 1-cyc pos ",cmd_str[c]);</u>
      foreach ( pos_range[c][0].lat_cnt[pos] ) begin
         n_z_str = { n_z_str, <u>$sformatf</u>("%0d ",pos) };
         n_zero++;
      end
      if ( n_one ) <u>$write("%s\n",n_o_str);</u>
      if ( n_zero )
        <u>$write</u>("%s\n%s Zero-Cycle %s. Should never be zero when pos!=0\n",
               n_z_str,err_str,cmd_str[c]);
      if ( c == Cmd_Rot_To && n_one > 2 )
        $write("%s One-Cycle Cmd_Rot_To for more than 2 pos values.\n",
               err_str);
      if ( c == Cmd_Write && n_one > 0 )
        $write("%s One-Cycle Cmd_Write at least one time. Should never happen.\n",err_str);
   end
end
testbench.t_errs += n_err;
done = 1;
```

```
end
```

 $\leftarrow \rightarrow$ Fall 2021

 $\leftarrow \rightarrow$ Homework 4

endmodule

// cadence translate_on

LSU EE 4755 Homework 5 solution Due: 17 November 2021

Problem 1: Solve 2020 Solve-Home Final Exam Problem 1, which asks for the inferred hardware for the $v_0^2 + v_0v_1 + v_1^2$ module that we covered in class. For those who may have forgotten how to use a pencil, or never learned, an SVG version of the illustration is available at https://www.ece.lsu.edu/koppel/v/2020/fe-ms.svg. Use Inkscape or your favorite SVG editor on the file.

See the 2020 Final Exam Solution.

Problem 2: This assignment does not have a Problem 2. I know that's confusing but the alternative is also confusing.

Problem 3: Solve 2020 Solve-Home Final Exam Problem 3, which asks for a timing analysis of the $v_0^2 + v_0v_1 + v_1^2$ module. An SVG version of the diagram is at

https://www.ece.lsu.edu/koppel/v/2020/fe-ms-t.svg.

See the 2020 Final Exam Solution for this problem too.

// /// LSU EE 4755 Fall 2021 Homework 6

// /// SOLUTION

/// Assignment https://www.ece.lsu.edu/koppel/v/2021/hw06.pdf

```
/// Additional Resources
11
// Verilog Documentation
       The Verilog Standard
11
        https://ieeexplore.ieee.org/document/8299595/
11
11
       Introductory Treatment (Warning: Does not include SystemVerilog)
11
         Brown & Vranesic, Fundamentals of Digital Logic with Verilog, 3rd Ed.
11
// Account Setup and Emacs (Text Editor) Instructions
11
         https://www.ece.lsu.edu/koppel/v/proc.html
11
         To learn Emacs look for Emacs tutorial.
11
```

`default_nettype none

```
/// Problem1
11
/// Complete multi_step_pipe so that it computes the same value as
     ms_functional, but does so in a pipelined fashion.
111
111
//
11
       [.] Only modify module multi_step_pipe.
11
       [/] Module must operate in pipelined fashion ..
11
       [*] .. meaning it should accept a new set of inputs each cycle ..
;;
;;
;;
       [<] .. and provide the result several cycles later.</pre>
       [\ensuremath{\,\checkmark}] Be sure to pass the start signal from input to output.
11
//
//
       [.] Instantiate as many Chipware mult and add units as needed.
       [<] The critical path can go through at most one Chipware module.</pre>
//
//
       [~] Use SimVision to debug. Use command: xrun -gui hw06.v
||
||
       \left[ \boldsymbol{\prime} \right] Make sure that the testbench does not report errors.
11
       [*] Module must be synthesizable. Use command: genus -files syn.tcl
//
//
       [.] Code must be written clearly.
11
       [.] Pay attention to cost and performance.
//
11
       [ ] Students can work in teams. List team members in this file
module multi_step_pipe
  ( output logic [31:0] result,
    output logic ready,
    input uwire [31:0] v0, v1,
    input uwire start, clk);
   /// SOLUTION
   11
   // Part of the solution is changing the object kind of the result
   // and ready outputs from uwire to var (logic).
   localparam int nstages = 3;
   localparam logic [2:0] rm = 0; // Rounding Mode
   // Wires for fp unit outputs.
   11
   uwire [7:0] mul_s1, mul_s2, mul_s3, a_s1, a_s2;
   uwire [31:0] v00, v01, v11, s1, s2;
   /// Pipeline Latch Declarations
   11
```

logic [31:0] pl_1_v00, pl_1_v01, pl_1_v11; logic [31:0] pl_2_v0001, pl_2_v11; logic pl_1_occ, pl_2_occ; // // By convention pipeline latch names start with "pl_" followed by // the stage in which their value is used (read). So pl_1_v00 holds

// a value that will be used in stage 1. The value of pl_1_v00 $\,$ // would have to have been written in stage 0. /// Floating-Point Functional Unit Instantiations 11 // Instantiate one functional unit for each operation: v0 * v0 + v0 * v1 + v1 * v1 11 Three multiplications, two additions. 11 11 // The multipliers' operands come directly from the module inputs .. // .. and so the multipliers are in stage 0. 11 <u>CW fp mult</u> m00(.z(v00), .a(v0), .b(v0), .rnd(rm), .status(mul_s1)); $\underline{CW \ fp \ mult} \ mO1(\ .z(vO1), \ .a(vO), \ .b(v1), \ .rnd(rm), \ .status(mul_s2) \);$ <u>CW fp mult</u> m11(.z(v11), .a(v1), .b(v1), .rnd(rm), .status(mul_s3)); 11 // The adders' operands come from the pipeline latches. 11 // Adder a1 is in stage 1. <u>CW fp add</u> **a1**(.*z*(s1), .*a*(pl_1_v00), .*b*(pl_1_v01), .*rnd*(rm), .*status*(a_s1)); 11 // Adder a2 is in stage 2. <u>CW fp add</u> a2(.z(s2), .a(pl_2_v0001), .b(pl_2_v11), .rnd(rm), .status(a_s2)); always_ff @(posedge clk) begin /// Stage 0 11 // Stage 0 computes: 11 v00 <- v0 * v0 (Instance m00) 11 v01 <- v0 * v1 (Instance m01) 11 11 v11 <- v1 * v1 (Instance m11) 11 // Write values from stage 0 into pipeline latches. 11 pl_1_v00 <= v00; pl_1_v01 <= v01; pl_1_v11 <= v11; pl_1_occ <= start; // Note that start is passed down pipeline.</pre> /// Stage1 11 // Stage 1 computes: s1 <- pl_1_v00 + pl_1_v01</pre> 11 pl_2_v0001 <= s1; pl_2_v11 <= pl_1_v11; pl_2_occ <= pl_1_occ;</pre> /// Stage 2 11 // Stage 2 computes: s2 <- pl_2_v0001 + pl_2_v11</pre> 11 result <= s2: ready <= pl_2_occ;</pre> 11 // Note: result and ready could have been named pl_3_result and // pl_3_ready. end endmodule /// Non-Synthesizable Mag Module --- Complete, Don't Edit // cadence translate_off module multi_step_functional (output shortreal mag,

input shortreal v0, v1); always_comb mag = v0 * v0 + v0 * v1 + v1 * v1;

endmodule
// cadence translate_on

```
/// Non-Synthesizable Mag Module --- Complete, Don't Edit
//
// This is provided for reference.
//
```

```
module multi_step_seq
  ( output logic [31:0] result,
    output logic ready,
    input uwire [31:0] v0, v1,
    input uwire start,
    input uwire clk );
   localparam logic [2:0] rnd = 0; // 1 is round towards zero.
   uwire [7:0] mul_s, add_s;
   logic [2:0] step;
   uwire [31:0] mul_a, mul_b;
   uwire [31:0] add_a, add_b;
   uwire [31:0] prod, sum;
  logic [31:0] ac0, ac1;
   localparam int last_step = 4;
   always_ff @( posedge clk )
     if ( start ) step <= 0;</pre>
     else if ( step < last_step ) step <= step + 1;</pre>
   <u>CW fp mult</u> m1( .a(mul_a), .b(mul_b), .rnd(rnd), .z(prod), .status(mul_s));
   <u>CW fp add</u> a1( .a(add_a), .b(add_b), .rnd(rnd), .z(sum), .status(add_s));
   assign mul_a = step < 2 ? v0 : v1;</pre>
   assign mul_b = step == 0 ? v0 : v1;
   assign add_a = ac0, add_b = ac1;
   always_ff @( posedge clk )
     begin
        ac0 <= prod;</pre>
        case ( step )
           0: ac1 <= 0;
           1: ac1 <= sum;
           2: ac1 <= sum;
        endcase
        if ( start ) ready <= 0; else if ( step == last_step-1 ) ready <= 1;</pre>
     end
   assign result = sum;
endmodule
```


// cadence translate_off

```
function automatic real rand_real(real minv, real maxv);
    rand_real = minv + ( maxv - minv ) * ( real'(<u>{</u><u>srandom</u>}) ) / 2.0**32;
endfunction
function automatic shortreal fabs(shortreal val);
    fabs = val < 0 ? -val : val;
endfunction
program reactivate
    (output uwire clk_reactive, output int cycle_reactive,
    input uwire clk, input var int cycle);
    assign clk_reactive = clk;
    assign cycle_reactive = cycle;
endprogram
module testbench;</pre>
```

typedef enum { MT_comb, MT_seq, MT_pipe } Module_Type;

localparam int num_tests = 400; localparam int NUM_MUT = 4;
```
localparam int err_limit = 7;
localparam int trace_max_lines = 10;
shortreal magr, vr[2];
logic [31:0] vp[NUM_MUT][2];
uwire [31:0] mag[NUM_MUT];
uwire availn[NUM_MUT];
logic avail[NUM_MUT];
logic in_valid[NUM_MUT];
typedef struct { int tidx; int cycle_start; int eta; } Test_Vector;
typedef struct { int idx;
                 int err_count = 0;
                 int err_timing = 0;
                 Module Type mt = MT_comb;
                 Test Vector tests_active[$];
                 string trace_lines[$];
                 int eta_to_test[int];
                 bit all_tests_started = 0;
                 bit seq = 0; bit pipe = 0;
                 bit bpipe = 0;
                 int ncyc = 0;
                 int ncompleted = 0;
                 int cyc_tot = 0;
                 int latency = 0;
                 } Info;
Info pi[string];
localparam int cycle_limit = num_tests * 10;
int cycle;
bit done;
logic clock;
logic clk_reactive;
int cycle_reactive;
reactivate ra(clk_reactive,cycle_reactive,clock,cycle);
initial begin
   clock = 0;
   cycle = 0;
   fork
      forever #10 cycle += ++clock;
      wait( done );
      wait( cycle >= cycle_limit )
       $write("*** Cycle limit exceeded, ending.\n");
   join_any;
   $finish();
end
task pi_seq(input int idx, input string name);
   automatic string m = <u>$sformatf("%s", name);</u>
   pi[m].idx = idx; pi[m].mt = MT_seq;
   pi[m].seq = 1; pi[m].bpipe = 0; pi[m].pipe = 0;
endtask
task pi_pipe(input int idx, input string name, input int ncyc);
   automatic string m = <u>$sformatf("%s", name);</u>
   pi[m].idx = idx; pi[m].mt = MT_pipe;
   pi[m].ncyc = ncyc;
   pi[m].seq = 1; pi[m].pipe = 1; pi[m].bpipe = 0;
endtask
multi step pipe m3( mag[3], availn[3], vp[3][0],vp[3][1], in_valid[3], clock );
initial begin pi_pipe(3,"MS Pipe",m3.nstages); end
always @*
  foreach ( availn[i] ) if ( availn[i] !== 1'bz ) avail[i] = availn[i];
initial begin
   automatic int awaiting = pi.size();
   logic [31:0] vs[num_tests][2];
   shortreal vrs[num_tests][2];
   done = 0;
```

```
foreach ( pi[mut] ) begin
   automatic int midx = pi[mut].idx;
   automatic int steps = pi[mut].ncyc;
   automatic int latency =
     !pi[mut].seq ? 1 : !pi[mut].pipe ? 2 * steps : steps;
   pi[mut].latency = latency;
   in_valid[midx] = 0;
end
for ( int i=0; i<num_tests; i++ ) begin</pre>
   if (i < 4) begin
      // In first eight tests vector components are zero or one.
      for ( int j=0; j<2; j++ ) vrs[i][j] = i & 1 << j ? 1.0 : 0.0;</pre>
   end else begin
      // In other tests vector components are randomly chosen.
      11
      for ( int j=0; j<2; j++ ) vrs[i][j] = rand_real(-10,+10);</pre>
   end
   for ( int j=0; j<2; j++ ) vs[i][j] = <u>$shortrealtobits(vrs[i][j]);</u>
end
fork forever @( negedge clk_reactive ) foreach ( pi[mut] ) begin
   automatic int midx = pi[mut].idx;
   if ( !in_valid[midx] && pi[mut].pipe ) begin
      vp[midx][0] = cycle;
      vp[midx][1] = 1;
   end
end join_none;
repeat ( 2 * 10 ) @( negedge clock );
foreach ( pi[mutii] ) begin
   automatic string muti = mutii;
   fork begin
      automatic string mut = muti;
      automatic int midx = pi[mut].idx;
      for ( int i=0; i<num_tests; i++ ) begin</pre>
         automatic int gap_cyc =
           ( {<u>$random</u>} % 2 ) ? {<u>$random</u>} % ( 5 ) : 0;
         automatic Test_Vector tv;
         repeat ( gap_cyc ) @( negedge clock );
         vp[midx] = vs[i];
         in_valid[midx] = 1;
         tv.tidx = i:
         tv.cycle_start = cycle;
         tv.eta = tv.cycle_start + pi[mut].latency;
         pi[mut].eta_to_test[tv.eta] = i;
         pi[mut].tests_active.push_back( tv );
         @( negedge clock );
         in_valid[midx] = 0;
      end
      pi[mut].all_tests_started = 1;
   end join_none;
   fork begin
      automatic string mut = muti;
      automatic int midx = pi[mut].idx;
      automatic int n_timing_errs = 0;
      automatic int n_correct_val = 0; // Reset when test over.
      while ( !pi[mut].all_tests_started || pi[mut].tests_active.size() )
        @( negedge clk_reactive ) begin
           automatic shortreal v0 = <u>$bitstoshortreal(vp[midx][0]);</u>
           automatic shortreal v1 = <u>$bitstoshortreal(vp[midx][1]);</u>
           automatic shortreal r_future = v0*v0+v0*v1+v1*v1;
           automatic shortreal r = <u>$bitstoshortreal(mag[midx]);</u>
           automatic Test_Vector tv = pi[mut].tests_active[0];
           automatic bit avail_sh = pi[mut].eta_to_test.exists(cycle);
           automatic int ita = tv.tidx;
           automatic int ieta =
             avail_sh ? pi[mut].eta_to_test[cycle] : -1;
           automatic int i = ita > ieta ? ita : ieta;
```

```
automatic shortreal v0p = vrs[i][0], v1p = vrs[i][1];
           automatic shortreal shadow_magr = v0p*v0p+v0p*v1p+v1p*v1p;
           automatic string in_txt = in_valid[midx]
             ? <u>$sformatf</u>("In: %5.1f,%5.1f -> %5.1f", v0, v1, r_future)
             : "start=0";
           automatic shortreal err_mag = fabs( r - shadow_magr );
           automatic bit okay = err_mag < 1e-4;</pre>
           automatic bit err_rdy = avail_sh !== avail[midx];
           automatic bit err_val = avail_sh && !okay;
           automatic string tr_txt =
             $sformatf
               ("%-8s Cyc %3d %-24s Rdy %1d%s, Res: %5.1f %0s\n",
                mut, cycle, in_txt,
                avail[midx],
                err_rdy ? "X" : " ",
                r.
                okay && avail[midx] && avail_sh ? "Good" :
                okay && !avail[midx] && avail_sh ? "XX: Need Rdy" :
                okay && avail[midx] && !avail_sh ? "XX: Early" :
                !okay && avail_sh ? "XX: Wrong" :
                avail[midx] && !avail_sh ? "XX: Unexpected" : ""
                );
           if ( err_rdy ) n_timing_errs++;
           if ( okay ) n_correct_val++;
           if ( pi[mut].ncompleted < 3 )</pre>
             <u>$write("%s",tr_txt);</u>
           else
             pi[mut].trace_lines.push_back( tr_txt );
           if ( pi[mut].err_count < err_limit</pre>
                && pi[mut].err_timing < err_limit
                && ( err_rdy || err_val ) )
             while ( pi[mut].trace_lines.size() )
               $write("%s", pi[mut].trace_lines.pop_front() );
           if ( avail_sh ) begin
              pi[mut].tests_active.delete(0);
              pi[mut].ncompleted++;
              if ( n_timing_errs ) begin
                 pi[mut].err_timing++;
                 n_timing_errs = 0;
              end
              if ( n_correct_val == 0 ) begin
                 pi[mut].err_count++;
                 if ( pi[mut].err_count <= err_limit ) begin</pre>
                    <u>$write</u>
                       ("%-8s test %0d: Inputs at cyc %0d, result expected at cyc %0d. Wrong val: h'%8h %7.4f != %7.4f (correct)\n",
                       mut, i, tv.cycle_start, tv.eta,
                       mag[midx], r, shadow_magr);
                 end
              end
              n_correct_val = 0;
           end
           if ( pi[mut].trace_lines.size() > trace_max_lines )
             pi[mut].trace_lines.delete(0);
        end
      awaiting--;
   end join_none
end
wait( awaiting == 0 || cycle > cycle_limit );
foreach ( pi[ mut ] )
 $write("For %0s ran %0d tests: Errors: %0d wrong val, %0d bad timing\n",
         mut, num_tests,
         pi[mut].err_count, pi[mut].err_timing);
done = 1;
$finish(2);
```

end

// cadence translate_on

`default_nettype wire

`*include* "/apps/linux/cadence/GENUS211/share/synth/lib/chipware/sim/verilog/CW/CW_fp_mult.v" `*include* "/apps/linux/cadence/GENUS211/share/synth/lib/chipware/sim/verilog/CW/CW_fp_add.v"

18 Fall 2020 Solutions

LSU EE 4755 Homework 1 solution Due: 16 September 2020

 $\textcircled{Paper copies will not be accepted. E-mail your solution to koppel@ece.lsu.edu. A single PDF file is preferred.$

Problem 1: In the Module-Port-versus-Module-Parameter section of lecture code

https://www.ece.lsu.edu/koppel/v/2020/1005-review.v.html there are several module designs for computing $c_1x + c_2y$, where c_1 and c_2 are constants and x and y are module inputs. The point of that section and of the modules was to illustrate the SystemVerilog differences between module parameters and ports (syntax issues, for example) and also how they relate to the hardware being modeled.

(a) Draw a diagram of module c1x_c2y_good, shown below, using its default parameter values (which are different than the ones in the lecture code). Show the contents of all instantiated modules and appropriately label ports and wires. (See 2016 Homework 1 Problem 3 for a diagram showing instantiated modules. Also see module arb_exp and the illustration that follows in https://www.ece.lsu.edu/koppel/v/2020/l015-syn-comb-str.v.html.)

- Use the default parameter values of the module $c1x_c2y_good$ shown below.
- Use the appropriate parameter values for the mult_by_c instances. *Hint: appropriate is not a synonym for default.*
- Show the ports for all modules.
- Show the number of bits in each wire.
- Label wires with the symbols used below (such as p1 and prod) and take care to place the label on the correct side of a module boundary. (In the two_pie illustration from https://www.ece.lsu.edu/koppel/v/2020/1005-review.v.html look at the wire carrying labels x, i1, and a.).

Continued on next page.

```
module mult_by_c
  #( int w = 8, int c = 16, int w2 = w+$clog2(c) )
  ( output uwire signed [w2-1:0] prod, input uwire signed [w-1:0] a );
  assign prod = a * c;
endmodule
module c1x_c2y_good
  #( int c1 = 4, int c2 = 7, int w = 15,
      int w2 = w + $clog2(c1) + $clog2(c2) )
  ( output logic signed [w2-1:0] s, input uwire signed [w-1:0] x, y );
  uwire [w2-1:0] p1, p2;
  mult_by_c #(w,c1,w2) m1(p1,x);
  mult_by_c #(w,c2,w2) m2(p2,y);
  assign s = p1 + p2;
```

endmodule

Solution appears below. Notice that parameters are not shown as module inputs. For example, c1 is not shown as an input to m1.



(b) Draw a diagram of module $c1x_c2y_okay$ below using its default parameter values (which are different than the defaults used in the lecture code). Show the same details, such as ports, as was requested for the previous part.

```
module mult
#( int w = 8, int w2 = 2 * w )
  ( output uwire signed [w2-1:0] prod, input uwire signed [w-1:0] a, b );
  assign prod = a * b;
endmodule
module c1x_c2y_okay
#( int c1 = 4, int c2 = 7, int w = 15,
        int w2 = w + $clog2(c1) + $clog2(c2) )
   ( output logic signed [w2-1:0] s, input uwire signed [w-1:0] x, y );
   uwire [w2-1:0] p1, p2;
   uwire [w:1] C1 = c1, C2 = c2; // Convert constants to desired size.
   mult #(w,w2) m1(p1, x, C1);
   mult #(w,w2) m2(p2, y, C2);
   assign s = p1 + p2;
```

endmodule

Solution appears below. Here, C1 and C2 are inputs to m1 and m2. A lazy synthesis program, or less judgmentally, a synthesis program set to optimize at a low effort level might not take advantage of the fact that in m1 the b input is 4. That would result in much more expensive hardware.



Problem 2: Synthesis programs optimize a design to minimize cost while meeting timing constraints. The illustration below for the mult and mult_by_c modules (used in the slides) show how the multiplier can be simplified when one of the inputs is a convenient constant, 1.

Show how the $c1x_c2y_good$ module from the first problem can be optimized based on the default c1=4 and c2=7 values. To do so show the multiplier replaced by much simpler hardware, such as adder(s). A correct solution uses only one adder for both multipliers, bit relabeling, *plus the adder used to combine* p1 *and* p2.

Note: As originally assigned, and until Tuesday, 15 September 2020 at about 16:15, the problem stated that a correct solution uses only one adder, implying but not specifically stating that the one adder was the replacement for the multipliers and that there would also be and adder computing p1+p2, for a total of two adders.

Before instantiation and optimization.



1

Solution on next page.

Two solutions appear below. The first is easier to understand, but uses two adders for m2. The second uses one adder for m2.

Both solutions take advantage of the fact that multiplication by a power of 2, such as 4, can be achieved by leftshifting. To compute 4x the value of x is left-shifted by two positions. The hardware for achieving that is trivial: relabel bit position i to i + 2 and set bits at positions 0 and 1 to the constant 0. Both solutions do this in m1. Make sure that the notation for re-labeling bits used in m1 is understood.

The solution below computes 7y using two adders: 4y + 2y + y = 7y.

Both solutions use adders that have unequal port sizes. For example in the first solution the adder computing s has one 17-bit input and one 20-bit input. That's not an unreasonable assumption to make.



Better one-adder-m2 solution on next page.

The solution using one adder for m2 appears below. Recall that m2 computes 7y. That can be done with one adder by computing 8y + (-y) = 7y. But to compute a 2's complement representation of -y one needs to negate each bit and then add 1. Negating each bit is easy. A wasteful solution would use an adder just to compute (-y-1)+1. There's no need for that here, instead the solution computes (8y + 1) + (-y - 1) = 7y. The quantity 8y + 1 is obtained by left-shifting by 3 bits and then putting a 1 in the least-significant bit position. Negating the bits of 2's complement number y results in -y - 1, which is what we need. Notice that the hardware computing -y - 1 produces an 18-bit quantity by sign-extending the 15-bit quantity. The need to do sign extension in the diagram below could have been eliminated by using an adder with an 18- and 15-bit input. The adder would do the sign-extension internally.



```
11
/// LSU EE 4755 Fall 2020 Homework 2 -- SOLUTION
11
/// Assignment https://www.ece.lsu.edu/koppel/v/2020/hw02.pdf
`default_nettype none
/// Problem1
11
/// Modify
///
11
      [...] nn4x4b must instantiate exactly four nn1x4b modules.
11
11
      [...] nn1x4b must instantiate exactly two nn1x2 modules.
11
      [~] Make sure that the testbench does not report errors.
11
11
      [/] Module must be synthesizable. Use command: genus -files syn.tcl
11
11
      [<] Don't assume any particular parameter value.</pre>
11
      [ ] Pay attention to port widths. Do not make them larger than needed.
11
11
      [.] Code must be written clearly.
module nn4x4
 #( int wa = 10, ww = 5 )
  ( output uwire [wa-1:0] ao[4],
    input uwire [wa-1:0] ai[4],
    input uwire [ww-1:0] wht[4][4] );
  /// DO NOT MODIFY THIS ROUTINE.
  assign \alpha o[0] = ai[0] * wht[0][0] + ai[1] * wht[0][1]
         + ai[2] * wht[0][2] + ai[3] * wht[0][3];
  assign \alpha o[1] = ai[0] * wht[1][0] + ai[1] * wht[1][1]
         + ai[2] * wht[1][2] + ai[3] * wht[1][3];
  assign αo[2] = ai[0] * wht[2][0] + ai[1] * wht[2][1]
         + ai[2] * wht[2][2] + ai[3] * wht[2][3];
  assign \alpha o[3] = ai[0] * wht[3][0] + ai[1] * wht[3][1]
         + ai[2] * wht[3][2] + ai[3] * wht[3][3];
endmodule
```

module nn4x4b
 #(int wa = 10, ww = 5)

```
( output uwire [wa-1:0] ao[4],
    input uwire [wa-1:0] ai[4],
    input uwire [ww-1:0] wht[4][4] );
```

/// SOLUTION

```
nn1x4b #(wa,ww) n0( ao[0], ai, wht[0] );
nn1x4b #(wa,ww) n1( ao[1], ai, wht[1] );
nn1x4b #(wa,ww) n2( ao[2], ai, wht[2] );
nn1x4b #(wa,ww) n3( ao[3], ai, wht[3] );
```

endmodule

module nn1x4b

```
#( int wa = 10, ww = 5 )
  ( output uwire [wa-1:0] ao,
    input uwire [wa-1:0] ai[4],
    input uwire [ww-1:0] wht[4] );
```

/// SOLUTION

```
uwire [wa-1:0] aoa, aob;
nn1x2b #(wa,ww) n0(aoa, ai[0:1], wht[0:1]);
nn1x2b #(wa,ww) n1(aob, ai[2:3], wht[2:3]);
assign αo = aoa + aob;
```

endmodule

/// SOLUTION

assign αo = ai[0] * wht[0] + ai[1] * wht[1];

endmodule


```
module nnOxl
  #( int no = 4, ni = 4, wa = 10, ww = 5 )
  ( output logic [wa-1:0] ao[no],
    input uwire [wa-1:0] ai[ni],
    input uwire [ww-1:0] wht[no][ni] );
```

/// DO NOT MODIFY THIS ROUTINE.

```
\leftarrow \rightarrow Fall 2020
                 \leftarrow \rightarrow Homework 2
                                             Homework Sol Code
           for (int o = 0; o < no; o++) begin
              ao[o] = 0;
              for ( int i=0; i<ni; i++ ) ao[o] += ai[i] * wht[o][i];</pre>
           end
   endmodule
   // cadence translate_off
   module testbench;
       localparam int wa = 16;
       localparam int ww = 8;
       localparam int ni = 4; // Number of input neurons.
       localparam int no = 4; // Number of output neurons.
       localparam int nmut = 3;
       localparam int ntests = 10;
       logic [wa-1:0] ai[ni];
       uwire [wa-1:0] ao[nmut][no];
       logic [ww-1:0] wht[no][ni];
       string mname[] = { "Behav", "Flat", "Sol" };
       typedef struct { string name; int no, ni; } Test_Set;
       Test Set ts[] = '{ '{ "n12", 1, 2 }, '{ "n14", 1, 4 }, '{ "n44", 4, 4 } };
       nnOxI #(no,ni,wa,ww) nn1i(ao[0],ai,wht);
       nn4x4 #(wa,ww) nn2i(ao[1],ai,wht);
       nn4x4b #(wa,ww) nn3i(ao[2],ai,wht);
       initial begin
          automatic int mut = 2;
          automatic string test_summary = "";
          $write("Testing module %s\n", mname[mut]);
          foreach ( ts[ti] ) begin
             automatic Test_Set tinfo = ts[ti];
             automatic int n_err = 0;
             <u>$write</u>("\n** Starting test set %s (%0d outputs, %0d inputs) **\n",
                    tinfo.name, tinfo.no, tinfo.ni );
             for ( int tnum=0; tnum < ntests; tnum++ ) begin</pre>
                for ( int io=0; io<no; io++ )</pre>
                  for ( int ii=0; ii<ni; ii++ )</pre>
                    wht[io][ii] = io < tinfo.no && ii < tinfo.ni ? {$random} : 0;</pre>
                for ( int ii=0; ii<ni; ii++ )</pre>
```

hw02-sol.v.html

```
Homework Sol Code
\leftarrow \rightarrow Fall 2020
                   \leftarrow \rightarrow Homework 2
                                                                                                hw02-sol.v.html
                    ai[ii] = ii < tinfo.ni ? {<u>$random</u>} : 0;
                 #1;
                 for ( int io=0; io<tinfo.no; io++ ) begin</pre>
                     if ( ao[0][io] !== ao[mut][io] ) begin
                        n_err++;
                        if (n_err < 4)
                          <u>$write</u>
                             ("Error test # %0d, output %0d: %0d != %0d (correct)\n",
                              tnum, io, ao[mut][io], ao[0][io] );
                     end
                 end
              end
              begin
                 automatic string msg =
                    $sformatf("%0d %s tests on %s: %0d errors found.",
                               ntests, tinfo.name, mname[mut], n_err);
                 $write("Done with %s\n",msg);
                 test_summary = { test_summary, <u>$sformatf</u>("Results of %s\n", msg) };
              end
          end
```

\$write("\n** Summary of Results **\n%s", test_summary);

end

endmodule

// cadence translate_on

//////////////////////////////////////
/// LSU EE 4755 Fall 2020 Homework 3 SOLUTION //
/// Assignment https://www.ece.lsu.edu/koppel/v/2020/hw03.pdf
`default_nettype none
//////////////////////////////////////
// /// Modify nnOxI and nn1xI so they compute same output as nnOxIbe. ///
<pre>// // [*] Make sure that the testbench does not report errors. // [*] Module must be synthesizable. Use command: genus -files syn.tcl //</pre>
<pre>// [•] Don't assume any particular parameter value. // [•] Don't make ports wider than necessary. //</pre>
// [/] Code must be written clearly.
/// Module Connection Names //
<pre>// no: Number of elements in Output array. // ni: Number of elements in Input array. // wo: Width (number of bits) in each element of output array. // wi: Width (number of bits) in each element of weight array. // ww: Width (number of bits) in each element of weight array. // sat: If 0, on overflow use low wo bits of result. // If 1, on overflow set result to maximum possible value, // do this where overflow occurs. // If 2, on overflow set result to maximum possible value, // do this in nn0xI (not in nn1xI nor in nnAdd, nnMult, etc.) // tr: If 0, generate a linear connection of nnMADD modules in nn1xI. // If 1, generate a tree connection of arithmetic units by // recursively defining nn1xI. // ao: Activation (neuron) Output array. // wht: Weights.</pre>
<pre>module nnOxl #(int no = 4, ni = 2, wo = 10, wi = 4, ww = 5, tr = 0, sat = 0) (output uwire [wo-1:0] ao[no], input uwire [wi-1:0] ai[ni], input uwire [ww-1:0] wht[no][ni]);</pre>
<pre>// [•] Instantiate nn1xI modules here. // [•] If sat == 2 replace overflow values with max possible value.</pre>

```
\leftarrow \rightarrow Fall 2020
```

```
\leftarrow \rightarrow Homework 3
                                     Homework Sol Code
   [ Jon't forget to set appropriate parameter values.
11
/// SOLUTION
// Compute number of bits to represent largest possible value that
// can appear on an ao.
11
localparam int wr = $clog2( ( 2**wi - 1 ) * ( 2**ww - 1 ) * ni );
if ( sat < 2 || wr <= wo ) begin
   // If overflow is not possible turn off check for saturation.
   11
   localparam int satp = wr <= wo ? 0 : sat;</pre>
   for (genvar i = 0; i < no; i++)
     nn1xI #(wo,wi,ww,ni,tr,satp) row( ao[i], ai, wht[i] );
end else begin
   for ( genvar i = 0; i < no; i++ ) begin</pre>
      uwire [wr-1:0] ar;
      nn1xI #(wr,wi,ww,ni,tr,0) row( ar, ai, wht[i] );
      // If there is an overflow substitute maximum value.
      11
      assign αo[i] = ar[wr-1:wo] ? ~wo'(0) : ar[wo-1:0];
   end
end
```

```
endmodule
```

```
module nn1xl
  #( int wo = 10, wi = 4, ww = 5, ni = 2, tr = 0, sat = 0 )
   ( output uwire [wo-1:0] ao,
     input uwire [wi-1:0] ai[ni],
     input uwire [ww-1:0] wht[ni] );
        [/] If tr == 0 use generate loop to instantiate nnMADD modules.
   11
   11
        [/] If tr == 1 use recursion to describe a tree structure ...
        [ < ] .. and use nnMADD, nnMult, and nnAdd where appropriate.
   11
        [ Jon't forget to set appropriate parameter values.
   //
   /// SOLUTION
   11
   if (tr) begin
      if ( ni == 1 ) begin
         nnMult #(wi,ww,wo,sat) mult(ao, ai[0], wht[0]);
```

```
end else begin
localparam int nlo = ni / 2;
localparam int nhi = ni - nlo;
uwire [wo-1:0] aolo, aohi;
nn1xI #(wo,wi,ww,nlo,1,sat) nnlo(aolo, ai[0:nlo-1], wht[0:nlo-1]);
nn1xI #(wo,wi,ww,nhi,1,sat) nnhi(aohi, ai[nlo:ni-1], wht[nlo:ni-1]);
nnAdd #(wo,sat) add(ao,aolo,aohi);
```

end

```
end else begin
```

```
uwire [wo-1:0] s[ni-1:-1];
assign s[-1] = 0;
assign ao = s[ni-1];
for ( genvar i = 0; i < ni; i++ )
    nnMADD #(ww,wi,wo,sat) madd( s[i], wht[i], ai[i], s[i-1] );
```

end

endmodule

module nnMADD

```
#( int wa = 10, wb = 5, ws = wa + wb, sat = 0 )
  ( output uwire [ws-1:0] so,
      input uwire [wa-1:0] a, input uwire [wb-1:0] b, input uwire [ws-1:0] si);
```

/// DO NOT MODIFY THIS MODULE.

uwire [ws-1:0] p; nnMult #(wa,wb,ws,sat) mu(p, a, b); nnAdd #(ws,sat) ad(so, si, p);

endmodule

```
module nnAdd
  #( int w = 5, sat = 0 )
   ( output uwire [w-1:0] so,
        input uwire [w-1:0] a, b );
```

/// DO NOT MODIFY THIS MODULE.

uwire [w:0] s = a + b; localparam logic [w-1:0] smax = ~w'(0); assign so = sat && s[w] ? smax : s[w-1:0];

endmodule

```
module nnMult
  #( int wa = 5, wb = 6, wp = wa + wb, sat = 0 )
  ( output uwire [wp-1:0] p,
```

```
Homework Sol Code
\leftarrow \rightarrow Fall 2020
                 \leftarrow \rightarrow Homework 3
                                                                                       hw03-sol.v.html
        input uwire [wa-1:0] a, input uwire [wb-1:0] b );
      /// DO NOT MODIFY THIS MODULE.
      localparam logic [wp-1:0] pmax = ~wp'(0);
      localparam int wmx = wp > wa+wb ? wp : wa+wb;
      uwire [wmx-wp:0] phi;
      uwire [wp-1:0] plo;
      assign {phi,plo} = a * b;
      assign p = sat && wp < wa + wb && phi ? pmax : plo;</pre>
   endmodule
   // Synthesizing at effort level "medium"
   // Module Name
                                                  Area
                                                         Delay
                                                                 Delay
   11
                                                        Actual Target
   // nn0xI_no2_ni16_wo12_wi5_ww4_sat0_tr0
                                                588304
                                                         6.972 90.000 ns
   // nn0xI_no2_ni16_wo12_wi5_ww4_sat0_tr1
                                                         6.972 90.000 ns
                                                588304
   // nn0xI_no2_ni16_wo12_wi5_ww4_sat1_tr0
                                                753136 63.864 90.000 ns
   // nn0xI_no2_ni16_wo12_wi5_ww4_sat1_tr1
                                                631611
                                                         7.043
                                                                90.000 ns
   // nn0xI_no2_ni16_wo12_wi5_ww4_sat2_tr0
                                                594261
                                                         7.450 90.000 ns
   // nn0xI_no2_ni16_wo12_wi5_ww4_sat2_tr1
                                                594261
                                                         7.450 90.000 ns
   // nn0xI_no2_ni16_wo12_wi5_ww4_sat0_tr0
                                                         4.828
                                                783094
                                                                  1.000 ns
   // nn0xI_no2_ni16_wo12_wi5_ww4_sat0_tr1
                                                         4.852
                                                779386
                                                                 1.000 ns
   // nn0xI no2 ni16 wo12 wi5 ww4 sat1 tr0
                                                         9.503
                                                951332
                                                                 1.000 ns
   // nn0xI_no2_ni16_wo12_wi5_ww4_sat1_tr1
                                                916787
                                                         5.136
                                                                  1.000 ns
   // nn0xI_no2_ni16_wo12_wi5_ww4_sat2_tr0
                                                800554
                                                         4.980
                                                                 1.000 ns
   // nn0xI_no2_ni16_wo12_wi5_ww4_sat2_tr1
                                                771789
                                                         4.981
                                                                 1.000 ns
   // Normal exit.
   module nnOxlbe
     #( int no = 4, ni = 4, wo = 10, wi = 4, ww = 5, sat = 0 )
       ( output logic [wo-1:0] ao[no],
        input uwire [wi-1:0] ai[ni], input uwire [ww-1:0] wht[no][ni] );
      /// DO NOT MODIFY THIS MODULE
      11
      // Study the code in this module to get a better understanding
      // of what the output of nn0xI should be.
      // Determine the maximum possible value of each element of ao.
      11
      localparam logic [wo-1:0] smax = ~wo'(0);
      always_comb
        for ( int o = 0; o < no; o++ ) begin</pre>
```

```
\leftarrow \rightarrow Fall 2020 \leftarrow \rightarrow Homework 3
```

```
automatic int unsigned acc = 0;
for ( int i=0; i<ni; i++ ) acc += ai[i] * wht[o][i];
ao[o] = sat && acc > smax ? smax : acc;
end
```

endmodule


```
// cadence translate_off
```

typedef struct { int ni, no, wa, ww; } Config;

```
module testbench;
```

```
final begin
```

```
\quad \text{end} \quad
```

```
localparam int maxsat = 3;
uwire d[maxsat*nc:-1]; // Start / Done signals.
assign d[-1] = 1; // Initialize first at true.
// Instantiate a testbench at each size.
//
for ( genvar i=0; i<nc; i++ ) begin
localparam int c[4] = configs[i];
```

```
\leftarrow \rightarrow Fall 2020
                 \leftarrow \rightarrow Homework 3
                                             Homework Sol Code
          for ( genvar sat=0; sat<maxsat; sat++ ) begin</pre>
             localparam int idx = maxsat*i + sat;
             testbench x #(c[0],c[1],c[2],c[3],sat)
             t2( .done(d[idx]), .start(d[idx-1]) );
          end
      end
   endmodule
   module testbench_x
     \#( int ni = 4, no = 4, wo = 16, ww = 8, sat = 0 )
       ( output logic done, input uwire start );
      localparam int wi = ww + 1;
      localparam int nmut = 3;
      localparam int ntests = 10;
      logic [wi-1:0] ai[ni];
       uwire [wo-1:0] ao[nmut][no];
      logic [ww-1:0] wht[no][ni];
      string mname[] = { "Behav", "Linear", "Tree" };
      typedef struct { string name; int no, ni; } Test_Set;
      <u>Test Set</u> ts[] = '{ '{ "n12", 1, 2 }, '{ "n1*", 1, ni }, '{ "n**", no, ni } };
      nn0xIbe #(no,ni,wo,wi,ww,sat) nn0(ao[0],ai,wht);
      nn0x1 #(no,ni,wo,wi,ww,0,sat) nn1(ao[1],ai,wht);
      nn0x1 #(no,ni,wo,wi,ww,1,sat) nn2(ao[2],ai,wht);
       initial begin
          automatic string config_label =
            $sformatf("no=%0d, ni=%0d, wo=%0d, wi=%0d, ww=%0d, sat=%0d",
                       no, ni, wo, wi, ww, sat );
          wait( start );
          $write("\n** Starting tests for %s\n", config_label);
          testbench.test_summary =
            { testbench.test_summary, <u>$sformatf</u>("Results from %s\n",config_label) };
          for ( int mut = 1; mut < nmut; mut++ ) begin</pre>
             $write("Testing module %s\n", mname[mut]);
             foreach ( ts[ti] ) begin
                automatic Test_Set tinfo = ts[ti];
                automatic int n_err = 0;
```

\$write("\n** Starting test set %s (%0d outputs, %0d inputs) for %s **\n",

```
\leftarrow \rightarrow Fall 2020
                  \leftarrow \rightarrow Homework 3
                                               Homework Sol Code
                                                                                             hw03-sol.v.html
                         tinfo.name, tinfo.no, tinfo.ni, mname[mut] );
                 for ( int tnum=0; tnum < ntests; tnum++ ) begin</pre>
                    for ( int io=0; io<no; io++ )</pre>
                      for ( int ii=0; ii<ni; ii++ )</pre>
                         wht[io][ii] = io < tinfo.no && ii < tinfo.ni ? <u>$random</u> : 0;
                    for ( int ii=0; ii<ni; ii++ )</pre>
                      ai[ii] = ii < tinfo.ni ? <u>$random</u> : 0;
                    #1;
                    for ( int io=0; io<tinfo.no; io++ ) begin</pre>
                       if ( ao[0][io] !== ao[mut][io] ) begin
                           n_err++;
                           if (n_err < 4)
                             <u>$write</u>
                               ("Error test # %0d, output %0d: %0d != %0d (correct)\n",
                                tnum, io, ao[mut][io], ao[0][io] );
                        end
                    end
                 end
                 begin
                    automatic string sat_key =
                      $sformatf("Sat %0d",sat);
                    automatic string long_key =
                      $sformatf("%s %s",mname[mut],sat_key);
                    automatic string msg =
                      $sformatf("%0d %s tests on %s: %0d errors found.",
                                 ntests, tinfo.name, mname[mut], n_err);
                    $write("Done with %s\n",msg);
                    testbench.test_summary =
                      { testbench.test_summary, <u>$sformatf</u>("Results of %s\n", msg) };
                    testbench.t errs += n err;
                    testbench.t_errs_cat[{"All ",sat_key}] += n_err;
                    testbench.t_errs_cat[long_key] += n_err;
                    testbench.t_errs_cat[mname[mut]] += n_err;
                 end
              end
          end
          done = 1;
       end
    endmodule
```

// cadence translate_on

LSU EE 4755 Homework 4 solution Due: 28 October 2020

Dependence of the second secon

This assignment refers to the solution to Homework 3. Pieces are shown below, the complete solution can be found at https://www.ece.lsu.edu/koppel/v/2020/hw03-sol.v.html and in the directory where the original assignment was copied from.

This solution was prepared 3 Nov 2020 at 16:23. A more detailed solution may be posted later.

Problem 1: Using the simple model compute the cost and delay of the nnAdd module from Homework 3 (shown below) for both sat=0 and sat=1. Do so after applying optimizations for constants. Show the cost and delay in terms of w. Hint: See the simple model notes, https://www.ece.lsu.edu/koppel/v/2020/lsli-simple-model.pdf, for the cost of a ripple adder.

- Show cost and delay in terms of w.
- Don't forget to optimize for constant values.
- Assume that the adder will be implemented using a ripple circuit.
- Indicate both the delay of the least-significant bit of the sum and the delay of the most significant bit of the sum. Answering this part correctly and applying it to the other problems in this assignment will reveal something important about the impact of detecting overflow and of the different methods of doing so.

Under the simple model the cost of a w-bit ripple adder is $9w u_c$, the delay of the least-significant bit is $4 u_t$ and the delay of the entire sum is $2(w+1) u_t$.

For sat=0 the cost and delay are those of the w-bit adder described above: | The cost of the sat=0 module is $9w \, \mathrm{u_c}$

the delay of the LSB in the sat=0 module is $4 u_t$, and the delay of the MSB in the sat=0 module is $2(w + 1) u_t$. When sat=1 the overflow logic must be taken into account too. That overflow logic synthesizes into a multiplexor with the select signal connected to s[w], the zero input connected to smax, and the one input connected to the sum, s[w-1:0]. Because smax is a constant, the cost of the multiplexor is w and the added delay is 1. So, the cost with sat=1 is $10w u_c$.

Because the multiplexor control signal is connected to the carry out of the adder (which would be bit position w of the sum), all bits of the sum must wait for the MSB to arrive. That means that

the delay for all bits in the sat=1 module is $[2(w + 1) + 1] u_t$. Sure, if all you cared about was the MSB this would be no big deal. But it precludes getting a faster result with cascaded ripple adders.

There are more problems on the next pages.

Problem 2: Using the simple model compute the cost and delay of the nnMult module from Homework 3 for sat=1. Let w denote the setting of both wa and wb (they are to be set to the same value), and let y denote the setting of wp. Solve this for y < 2w. Do so after applying optimizations for constants.

Solve this using the following cost for an unsigned integer multiplier with two w-bit inputs and a 2w-bit output: the cost using the simple model is $10w^2 u_c$ and the delay is $[8w + 2] u_t$ for the complete product and $[4i + 2] u_t$ for bit position *i*. (The LSB is at position i = 0.) (For more details on how those were derived see the comments after the Linear Multiplier in https://www.ece.lsu.edu/koppel/v/2020/mult-seq.v.html.)

- Show the cost and delay in terms of w and y.
- Solve this for y < 2w.
- Don't forget to optimize for constant values.

```
module nnMult #( int wa = 5, wb = 6, wp = wa + wb, sat = 0 )
  ( output uwire [wp-1:0] p, input uwire [wa-1:0] a, input uwire [wb-1:0] b );
```

```
localparam logic [wp-1:0] pmax = ~wp'(0);
localparam int wmx = wp > wa+wb ? wp : wa+wb;
uwire [wmx-wp:0] phi;
uwire [wp-1:0] plo;
assign {phi,plo} = a * b;
assign p = sat && wp < wa + wb && phi ? pmax : plo;</pre>
```

endmodule

In order to detect overflow the multiplier must compute a 2w-bit product. The problem statement helpfully gives the cost of such hardware as $10w^2 u_c$ and the delay as $[8w + 2] u_t$.

The only difference with the saturation logic is that it must examine 2w - y bits of the product. If any of those 2w - y bits are 1 then there is overflow. As in the previous problem there is a multiplexor with the result (product in this case) at the zero input and **pmax** at the one input. The select signal is generated by ORing the 2w - y high bits of the product together. The cost of the multiplexor is $y u_c$, and the cost of the OR gate is $[2w - y - 1] u_c$. Ordinarily under the simple model the delay for an *a*-input OR gate would be $\lceil \lg a \rceil$. But in this case we know the less significant bits of the product arrive earlier than the more significant bits. To implement an *a*-input OR gate for such a situation the OR gates can be connected linearly (rather than using a reduction tree). The MSB of the product would connect to the last OR gate, and so the delay for checking whether any of the 2w - y bits is 1 would just be $1 u_t$.

```
The total cost of nnMult is [10w^2 + y] u_c and the delay of all bits is [8w + 2 + 1] u_t
```

There are more problems on the next pages.

Problem 3: Using the simple model determine the cost and performance of module nn1xI (shown on the next page) for the configurations described below. In all cases, let *n* denote the value of ni, *w* denote the value of ww and wi (which are the same) and *y* denote the value of wo. Assume the same hardware costs as the first two problems (modifying sizes and accounting for cascading where appropriate).

(a) Find the cost (not delay in this part) for sat=0, tr=0, and y > 2w (that's one configuration) and for sat=0, tr=1, and y > 2w (that's a second configuration). The two costs will be very similar.

• Show the costs in terms of n, w, and y.

Short answer: The cost for tr=0 and tr=1 is $[10nw^2 + 9(n-1)y] u_c$ (or lower, see detailed answer).

Detailed Answer: The y > 2w condition means that the multiplier will not overflow and that all bits of the product are needed. (If y were smaller, say y = w, then some of the adders used to implement the multiplier would be less than w bits and so would cost less.)

The nnMADD module consists of both an nnAdd and nnMult module. So the cost of the tr=O solution will be discussed in terms of the nnAdd and nnMult modules.

For both the tr=0 and tr=1 cases there will be n multipliers each having two w-bit inputs. The total cost of these multipliers is $10nw^2 u_c$.

For the tr=0 case there are n nnAdd units but the input to the first adder is zero (because s[-1]=0), so after optimization there are n - 1 adders. When n is a power of 2, the number of adders for the tr=1 case is $\sum_{l=0}^{(\log n)-1} 2^l = n - 1$. So the number of adders is the same in both cases.

The code instantiates y-bit adders, but good synthesis programs—and good students—will have noticed that not all adders need y bits to avoid overflow. For the tr=0 case the i=1 adder has two 2w-bit inputs and so only needs to compute a sum of 2w + 1 bits to avoid overflow. So if y > 2w + 1 the cost can be reduced by using a 2w + 1 bit adder rather than a y bit adder. Call this a trim optimization.

First, compute the cost without the trim optimization. The cost of each of these adders is $9y u_c$. The total cost of the adders for both tr=0 and tr=1 is $9y(n-1)u_c$.

The total cost of the nn1xI module without the trim optimization is $[10nw^2 + 9(n-1)y]u_c$.

The cost with the trim optimization will be computed for tr=1. Let l indicate a level in the recursion tree with l corresponding to a level in which $n = 2^l$. The base case is l = 0, for which there are no adders. For l > 0 there are $n/2^l$ adders each need 2w + l bits, so the cost at level l is $\left[\frac{n}{2^l}9(2w+l)\right] u_c$. The total adder cost is $\sum_{l=1}^{(\lg n)} \left[\frac{n}{2^l}9(2w+l)\right] u_c = \left[9(2w+2)(n-1) - 9\lg n\right] u_c$.

(b) Find the delay (not cost in this part) for sat=0, tr=0, and y > 2w (that's one configuration) and for sat=0, tr=1, and y > 2w (that's a second configuration). The two delays will be very different.

- Show the delays in terms of n, w, and y.
- When computing the total delay don't forget to take into account the time that inputs arrive at each port, especially for the multiplier.
- When computing total delay account for cascading of ripple units.

At launch time (t=0) inputs are available at all of the multipliers. As stated in the problem, bit i is correct at time [4i+2] \mathbf{u}_{t} .

First consider tr=0. For i=1 (the *i* from the generate loop) the two inputs to the adder are from multipliers (because for i=0 there is no need for an adder), and so bit *i* arrives at 4i + 2. Because the inputs to the adder aren't all available at the same time we can't rely on the ripple adder formula for when bit *i* of the sum is available. We know that each BFA requires 4 units of time to compute both the sum and carry output from its inputs when those inputs are available at the same time. Therefore, bit *i* of that first adder is available at 4i + 2 + 4 = 4i + 6. Accounting for

n-1 adders, bit i is available at 4i + 2 + 4(n-1) = 4(i+n) - 2 and the most-significant bit, y-1 is available at $[4(y-1) + 4n - 2] u_t = [4(y+n) - 6] u_t$.

So, the delay for the LSB when tr=0 is $[4n-2] u_t$ and the delay for the MSB when tr=0 is $[4(y+n)-6] u_t$. For tr=1 the computation is similar, except that the critical path passes through $\lg n$ adders rather than n-1.

adders. Therefore the delay for bit i is $[4i + 2 + 4 \lg n] \operatorname{u}_{t}$ and the MSB is available at $[4(y - 1) + 2 + 4 \lg n] \operatorname{u}_{t}$.

So, the delay for the LSB when tr=1 is $[2+4\lg n]\,\mathrm{u_t}$ and the

delay for the MSB when tr=1 is $[4(y-1)+2+4\lg n]\,\mathrm{u_t}\,|$

(c) Find the delay for sat=1, tr=0, and y > 2w (that's one configuration) and for sat=1, tr=1, and y > 2w (that's a second configuration). The two delays should be very different from each other and from the delays from the previous problem.

Since y > 2w there will be no saturation penalty for the multiplier. Therefore bit i of the product is stable at 4i + 2.

Because of the multiplexor, the delay though one saturating adder (an nnAdd module with sat=1) is the same for all bits. That delay is $[2(y+1)+1] u_t$.

First consider tr=0. For i=1 (the genvar, not a bit position) bit *i* of the sum (before saturation, and accounting for the multiplier delay) is ready at time 4i + 2 + 4 = 4i + 6. The MSB, y - 1, is available at 4y + 2, and the output of the mux is available at $[4y + 3] u_t$. The delay computation is different for the remaining n - 2 adders. Consider the i=2 (the genvar) adder. One input is from the i=1 adder and the other is from a multiplier. The input from the i=1 adder arrives at $[4y + 3] u_t$ (which we just calculated). By then all bits from the multiplier will have arrived. So the time at which the LSB can be computed is 4y + 3, there is no early start. The sum will be computed 2(y + 1) later, or at a total delay of $[4y + 3 + 2(y + 1) + 1] u_t = [6y + 5 + 1] u_t$ including the mux. The complete sum is available at $[4y + 3 + (n - 2)(2(y + 1) + 1)] u_t$ of $[n(2y + 3) - 3] u_t$.

Notice that with without saturation the time is O(n+y) and that with saturation the time is O(ny), much worse! The computation is similar for the tr=1 case. The critical path starts with a multiply, add, saturate (same as for tr=0) with a delay of [4y+3] ut. After that the critical path passed through $(\lg n) - 1$ additional adders, so the total time is $[4y+3+(\lg n-1)(2(y+1)+1)]$ ut or $[(2y+3)\lg n+2y]$ ut. Here the time is order $O(y\lg n)$ which is better than O(ny) but not nearly as good as O(n+y).

```
module nn1x1 #( int wo = 10, wi = 4, ww = 5, ni = 2, tr = 0, sat = 0 )
   ( output uwire [wo-1:0] ao,
     input uwire [wi-1:0] ai[ni],
     input uwire [ww-1:0] wht[ni] );
  if ( tr ) begin
      if ( ni == 1 ) begin
         nnMult #(wi,ww,wo,sat) mult(ao, ai[0], wht[0]);
      end else begin
         localparam int nlo = ni / 2;
         localparam int nhi = ni - nlo;
         uwire [wo-1:0] aolo, aohi;
         nn1xI #(wo,wi,ww,nlo,1,sat) nnlo(aolo, ai[0:nlo-1], wht[0:nlo-1]);
         nn1xI #(wo,wi,ww,nhi,1,sat) nnhi(aohi, ai[nlo:ni-1], wht[nlo:ni-1]);
         nnAdd #(wo,sat) add(ao,aolo,aohi);
      end
  end else begin
      uwire [wo-1:0] s[ni-1:-1];
      assign s[-1] = 0;
      assign ao = s[ni-1];
      for ( genvar i = 0; i < ni; i++ )</pre>
        nnMADD #(ww,wi,wo,sat) madd( s[i], wht[i], ai[i], s[i-1] );
   end
endmodule
module nnMADD #( int wa = 10, wb = 5, ws = wa + wb, sat = 0 )
   ( output uwire [ws-1:0] so,
     input uwire [wa-1:0] a, input uwire [wb-1:0] b, input uwire [ws-1:0] si);
  uwire [ws-1:0] p;
  nnMult #(wa,wb,ws,sat) mu(p, a, b);
  nnAdd #(ws,sat) ad(so, si, p);
endmodule
```

There are even more problems on the next pages.

Problem 4: Consider module nn0xI instantiated with no=1, tr=0, for both sat=1 and sat=2. (A slightly simplified version appears below.) Let n denote the value of ni, w denote the value of wi and ww (which are the same), and let y denote the value of wo.

Assume that $2w < y < \lceil \lg n(2^w - 1)^2 \rceil$. That is, y is large enough so that the multipliers can't overflow but not so large that the adders can't overflow.

(a) Compute the cost and delay for both the sat=1 and sat=2 cases. For sat=1 just re-use answers from the previous problems.

- Show answers in terms of n, w, and y.
- Don't forget that the value of wo in the nn1xI instantiations depends upon sat.

When sat=1 and no=1 the hardware for nnOxI is the same as that of nn1xI.

The cost of the sat=0 instantiation based on the answer to Problem 3 is $[10nw^2 + 9(n-1)y] u_c$. The cost of the saturation hardware is that of n-1 2-input, y-bit multiplexors in which one input is a constant. The cost of these is $[(n-1)y] u_c$. So the total cost for nnOxI with sat=1 is $[10nw^2 + 9(n-1)y + (n-1)y] u_c = [10nw^2 + 10(n-1)y] u_c$.

The delay has been computed in Problem 3, it is $[n(2y+3)-3]\,\mathrm{u_t}.$

When sat=2 the nn1xI modules are instantiated with sat=0, and so their cost and delay are $[10nw^2 + 9(n-1)r]u_c$ and $[4(r+n) - 6]u_t$ where r is the value of wr for which they were instantiated. Note that $r = \lceil \lg n(2^w - 1)^2 \rceil$.

Module nnOxI checks for saturation by checking whether the high r-y bits of ar are non-zero. That can be done using an OR gate, with a cost of $[r-y-1] u_c$. If the OR used a tree reduction the delay would be $\lg(r-y) u_t$, but if we expect bit i + 1 to arrive at least one u_t later than bit i a linear connection of OR gates would be faster, and have a net delay of just 1. So the total delay is $[4(r+n)-6+1] u_t$.

The total cost includes a 2-input, y-bit multiplexor and the (r - y)-input OR gate. One input to the mux is constant, so its cost is y. The total cost with this hardware is $[10nw^2 + 9(n-1)r + y + (r - y - 1)]u_c$ or $[10nw^2 + 9(n-1)r + r - 1]u_c$ where $r = \lceil \lg n(2^w - 1)^2 \rceil$.

(b) In terms of the costs computed above is **sat=2** always better, always worse, or sometimes better than **sat=1**? Be specific of course.

Recall that for sat=1 the cost is $C(1, n, w, y) = [10nw^2 + 10(n-1)y]$ u_c and for sat=2 the is $c(2, n, w, y) = [10nw^2 + 9(n-1)r + r - 1]$ u_c.

To solve this compute C(1, n, w, y) - C(2, n, w, y). If the result is always positive then sat=2 always costs less, etc.

C(1, n, w, y) - C(2, n, w, y) = 10(n - 1)y - 9(n - 1)r - r + 1

Recall $r = \lceil \lg n(2^w - 1)^2 \rceil$ and that the assumption is that 2w < y < r. We can approximate $r \approx 2w + \lg n$. The cost benefit for sat=2 is less favorable larger when y is smaller. Consider one minus the smallest value of y, which is y = 2w Then $C(1, n, w, y) - C(2, n, w, y) = 10(n-1)2w - 9(n-1)(2w + \lg n) - (2w + \lg n) + 1 = (n-1)2w - 9(n-1)\lg n - 2w - \lg n + 1 \approx (n-1)2w - 9(n-1)\lg n$. This expression is positive when $w > 2.25 \lg n$. Generally when w is large sat=2 works better, when n is large sat=1 works better.

module nnOxl #(int no = 4, ni = 2, wo = 10, wi = 4, ww = 5, tr = 0, sat = 0)
 (output uwire [wo-1:0] ao[no],
 input uwire [wi-1:0] ai[ni], input uwire [ww-1:0] wht[no][ni]);
 // Compute number of bits to represent largest possible value that
 // can appear on an ao.
 localparam int wr = \$clog2((2**wi - 1) * (2**ww - 1) * ni);
 if (sat < 2) begin</pre>

```
for ( genvar i = 0; i < no; i++ )
    nn1xI #(wo,wi,ww,ni,tr,sat) row( ao[i], ai, wht[i] );
end else begin
for ( genvar i = 0; i < no; i++ ) begin
    uwire [wr-1:0] ar;
    nn1xI #(wr,wi,ww,ni,tr,0) row( ar, ai, wht[i] );
    assign ao[i] = ar[wr-1:wo] ? ~wo'(0) : ar[wo-1:0];
end
end</pre>
```

endmodule

Problem 5: Zero points will be given for the answer to this question, but please try your very best to answer it. Suggest a method of saturating ao that avoids the extra wo bits needed (for nn1xI) when sat=2 but also avoids the critical-path-killing saturation logic used when sat=1. Your solution could add extra ports to all modules except nn0xI. A correct solution would detect overflow under the same conditions as nn0xI does with sat=1.

19 Fall 2019 Solutions

LSU EE 4755 Homework 1 solution Due: 18 September 2019

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2019/hw01.v.html.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account, copy the assignment, and run the Verilog simulator and synthesis program on the unmodified homework file, hw01.v. Do this early enough so that minor problems (*e.g.*, password doesn't work) are minor problems.

Homework Overview

In class you were told that for common operations, such as shifting, addition, and multiplication, it's better to use Verilog operators in procedural code than to re-invent the wheel by writing Verilog to implement those operations. This point was made when covering the shift module in the introductory lectures. For example, if you need a shifter it's better to just use the shift operator: module shift_right_operator

```
( output uwire [15:0] shifted,
    input uwire [15:0] unshifted, input uwire [3:0] amt );
    assign shifted = unshifted >> amt;
    dredule
```

endmodule

than to write code for your own shifter:

module shift_right_logarithmic

endmodule

The reason for showing the implementation of shifters, and other common operations, was to teach general design concepts using operations that you should be familiar with. That will be the approach in this homework, in which a multiplier is to be implemented.

Testbench Code

The testbench for this assignment, which can be run when visiting the file in Emacs in a properly set-up account by pressing F9, tests the multiply modules. Modules mult_operator and mult16 should pass, mult16_tree awaits your solution. A sample of the end of the testbench output appears below:

```
Starting testbench...
Error in mult16_tree test 0: xxxxxxxx != 00000001 (correct)
Error in mult16_tree test 1: xxxxxxxx != 00000002 (correct)
Error in mult16_tree test 2: xxxxxxxx != 00000020 (correct)
Error in mult16_tree test 3: xxxxxxxx != 00000020 (correct)
```

```
Error in mult16_tree test
                                 xxxxxxxx != 139dff24 (correct)
                             4:
Error in mult16_tree test
                                 xxxxxxxx != 4839cb7b (correct)
                             5:
Mut mult_operator ,
                        0 errors (0.0% of tests)
Mut mult16_flat
                        0 errors (0.0% of tests)
Mut mult16_tree
                   , 1000 errors (100.0% of tests)
Memory Usage - 38.6M program + 154.6M data = 193.2M total
CPU Usage - 0.0s system + 0.0s user = 0.1s total (70.4% cpu)
Simulation complete via $finish(2) at time 10 US + 0
./hw01.v:218
                   $finish(2);
```

ncsim> exit

A count of the number of tests and errors is shown for three modules. The testbench shows the first six errors it finds on each module. To see more than six modify the testbench (search for err_limit). In the output above the testbench is showing that the module outputs are x (uninitialized) which of course don't match the expected outputs.

Use Simvision to debug your modules. Feel free to modify the testbench so that it presents inputs that facilitate debugging.

Synthesis

The synthesis script, syn.tcl, will synthesize the three modules each with two delay targets, an easy 10 ns and a un-achievable 0.1 ns. If the module doesn't synthesize -.001 s is shown for the delay. The script is run using the shell command genus -files syn.tcl, which invokes Cadence Genus.

The synthesis script shows area (cost), delay, and the delay target in a neat table. Additional output of the synthesis program is written to file **spew.log**. Sample synthesis script output appears below:

Problem 1 on next page.

 $\leftarrow \rightarrow$ Homework 1

Problem 1: The illustration to the right shows a sketch of a multiplier, mult16, with two 16-bit inputs and a 32-bit output. The multiplier is constructed from mult2 modules, shifters (<<), and adders. The illustrated module is similar to the multiplier in mult16_flat in hw01.v. The mult2 modules have two inputs, one is two bits, the other is 16 bits. Each input holds an unsigned integer. The output, 18 bits, is the product of the two inputs. Notice that each mult2 module is connected to two bits of a and all bits of b. The outputs of the mult2 modules are shifted and added together in such a way that **prod** is the correct product of **a** and **b**.

There are two parts of mult16 surrounded by green boxes. The upper one, labeled 16b by 4b, contains two mult2 modules. The label is explaining that the boxed material multiplies a 16-bit number by a 4-bit number. A similar box could have been put around the next pair of mult2 modules, etc.



The hardware within each of these four boxes would be identical. (The bit slices at the upper mult2 inputs, such as 1:0 and 5:4 are different, but that can be taken care of outside the green box.) Think about the poor soul who might have just typed in all the Verilog for mult16 and then suddenly realizes this. All that person would have had to do would be to code one module, call it mult4_tree, and just instantiate it four times. Here is an almost empty version of mult4_tree:

module mult4_tree

```
( output uwire [0:0] prod, // Need to change output size.
input uwire [3:0] a, input uwire [15:0] b );
mult2 mlo( /* finish */ );
mult2 mhi( /* finish */ );
```

endmodule

Alert students might suspect that we don't actually instantiate mult4_tree four times because the 16b by 8b section itself could be a module which would contain only two instantiations of mult4_tree. That would be correct.

Modify modules mult16_tree, mult8_tree, and mult4_tree found in hw01.v so that they implement the multiplier described above. Module mult16_tree must instantiate exactly two mult8_tree modules, module mult8_tree must instantiate exactly two mult4_tree modules, and

mult4_tree must use the two mult2 modules that are already instantiated (but with the ports missing).

In each module use implicit structural code or behavioral code to combine the outputs of that module's two instantiated modules. It might be helpful to look at mult16_flat for examples of instantiation and implicit procedural code.

Start with module mult16_tree. You can test your changes to mult16_tree by putting placeholder code in mult8_tree, such as assign prod = a*b;. Don't forget to change the port sizes on mult8_tree to what they should be based on the diagram.

Once the testbench reports zero errors move the placeholder to mult4_tree and complete mult8_tree. Continue until the three modules are finished.

Some of the port sizes are set to 1 bit, [0:0]. Those are placeholders, change those to the correct sizes, but no larger. Credit will be deducted for oversized ports, especially if all ports are made 32 bits.

Pay attention to port-size warnings when running the simulator.

The solution Verilog code has been placed in the assignment directory, and on the Web at

https://www.ece.lsu.edu/koppel/v/2019/hw01-sol.v.html.

To solve the problem one needed to see that a was split between the two modules, mlo and mhi, but that a complete version of b was used in each. Another important element to work out was the size of the product. When an x-bit unsigned integer is multiplied by a y-bit unsigned integer, the maximum sized product is x + y bits. So the mult8_tree output, and the wire that connects to it, must be 8 + 16 = 24 bits. Therefore in the solution (shown below) prod_lo and prod_hi are 24 bits, as is the output of the mult8_tree module.

module mult16_tree

```
#( int wa = 16, int wb = 16, int wp = wa + wb )
  ( output uwire [31:0] prod, input uwire [15:0] a, input uwire [15:0] b );
```

/// SOLUTION

```
// Declare properly-sized connections to mult8_tree outputs.
uwire [23:0] prod_lo, prod_hi;
```

// Instantiate two mult8_tree multipliers, each handles 8 bits of a.
mult8_tree mlo(prod_lo, a[7:0], b);
mult8_tree mhi(prod_hi, a[15:8], b);

// Compute the full product using the two partial products.
assign prod = prod_lo + (prod_hi << 8);</pre>

endmodule

```
module mult8_tree
( output uwire [23:0] prod,
    input uwire [7:0] a, input uwire [15:0] b );
/// SOLUTION
    uwire [19:0] prod_lo, prod_hi;
    mult4_tree mlo( prod_lo, a[3:0], b);
    mult4_tree mhi( prod_hi, a[7:4], b);
    assign prod = prod_lo + ( prod_hi << 4 );
endmodule</pre>
```

```
module mult4_tree
```

```
( output uwire [19:0] prod,
    input uwire [3:0] a, input uwire [15:0] b );
/// SOLUTION
    uwire [17:0] prod_lo, prod_hi;
    mult2 mlo( prod_lo, a[1:0], b);
    mult2 mhi( prod_hi, a[3:2], b);
    assign prod = prod_lo + ( prod_hi << 2 );
endmodule
```

Problem 2: The synthesis script will synthesize mult16_tree from Problem 1, plus two already working modules, mult16_flat and mult_operator, which just uses the multiply operator.

If the synthesis program were perfect then all three modules would have the same cost and delay because they each do exactly the same thing (multiply) and so the optimization algorithms would have found the same lowest-cost circuit from each one. Spoiler alert: Genus is not perfect.

Guess which module you think will be the fastest or least expensive, and explain why. Then run the synthesis script and comment on whether the results met your expectations.

Solution on next page.
I would expect that mult_operator would be fastest with the 0.1 ns delay target and least expensive with the 10 ns target because integer multiplication is a common operation and so the synthesis program should have a well-tuned multiply module in its library for situations such as these.

If optimization was not very good, then I'd expect mult16_flat to have a longer delay than mult16_tree because of the expression adding together the partial products:

```
assign prod = prod00 + ( prod02 << 2 ) + ( prod04 << 4 ) + ( prod06 << 6 ) + ( prod08 <<
8 ) + ( prod10 << 10 ) + ( prod12 << 12 ) + ( prod14 << 14 );</pre>
```

This expression has seven additions. If the order of additions follows the expression above then each addition after the first will not have its operands ready until the previous addition finishes. Therefore the critical path passes through seven additions. In the tree version the critical pass passes through just three additions, and so would be faster.

Modern optimizers, however, should be able to *re-associate* the expression to reduce the critical path. For example, internally the optimizer might convert the expression into:

```
assign prod =
    (
        ( ( prod00 ) + ( prod02 << 2 ) )
        +
        ( ( prod04 << 4 ) + ( prod06 << 6 ) )
    )
    +
        (
        ( prod08 << 8 ) + ( prod10 << 10 ) )
        +
        ( ( prod12 << 12 ) + ( prod14 << 14 ) )
        );
</pre>
```

In the expression above the four inner additions (the ones where the plus sign is in the middle of the line) can start at the same time, when they finish two more additions can start and proceed in parallel, followed by the last addition in the center of the expression.

Below is the actual synthesis output:

Module Name	Area	Delay	Delay
		Actual	Target
mult_operator	235272	9.266	10.000 ns
mult16_flat	403519	9.982	10.000 ns
mult16_tree	294419	8.861	10.000 ns
mult_tree	240616	7.934	10.000 ns
mult_operator_1	491053	3.103	0.100 ns
mult16_flat_1	817229	4.502	0.100 ns
mult16_tree_1	590500	3.360	0.100 ns
mult_tree_3	510150	3.150	0.100 ns

The results indicate that optimizers are not as good as I thought. As expected, the library routine, and so mult_operator was least expensive. But mult_tree was almost as good, and for some reason was better than mult16_tree, perhaps because it does not use a multiplier in its terminal case. For delay the library routine also wins out and our tree-structured modules outperform the flat ones.

mult4 tree mlo(prod_lo, a[3:0], b); mult4 tree mhi(prod_hi, a[7:4], b); assign prod = prod_lo + (prod_hi << 4);</pre>

endmodule

module mult4_tree

(output uwire [19:0] prod, input uwire [3:0] a,

11 /// LSU EE 4755 Fall 2019 Homework 1 -- SOLUTION 11 /// Assignment https://www.ece.lsu.edu/koppel/v/2019/hw01.pdf `default_nettype none /// Problem 1 -- SOLUTION 11 /// Modify mult16_tree, mult8_tree, and mult4_tree to implement multiplier. 111 11 11 [~] Make sure that the testbench does not report errors. 11 [...] mult16_tree must use exactly two mult8_tree modules, etc. $\left[\boldsymbol{\prime} \right]$ Pay attention to port widths. Do not make them larger than needed. 11 11 [*] Module must be synthesizable. Use command: genus -files syn.tcl module mult16_tree #(int wa = 16, int wb = 16, int wp = wa + wb) (output uwire [31:0] prod, input uwire [15:0] a, input uwire [15:0] b); /// Problem 1 solution goes here, and in other modules. // [*] Instantiate two mult8_tree's. // [/] Use implicit structural or behavioral code to combine their outputs. /// SOLUTION // Declare properly-sized connections to mult8_tree outputs. 11 uwire [23:0] prod_lo, prod_hi; 11 // They are 24 bits wide because that's the maximum size of the // product of an 8-bit unsigned integer (such as a[7:0]) and a // 16-bit unsigned integer (b): 8+16 =24. // Instantiate two mult8_tree multipliers, each handles 8 bits of a. 11 mult8 tree mlo(prod_lo, a[7:0], b); mult8 tree mhi(prod_hi, a[15:8], b); // Compute the full product using the two partial products. 11 assign prod = prod_lo + (prod_hi << 8);</pre> 11 // Because prod is 32-bits wide the right-hand side computation // will be computed with a 32-bit precision. endmodule module mult8_tree (output uwire [23:0] prod, input uwire [7:0] a, input uwire [15:0] b); // $\circ{[$\textbf{\prime}$]}$ Pay attention to port widths. Do not make them larger than needed. /// Problem 1 solution goes here, and in other modules. // [<] Instantiate two mult4_tree's.</pre> // $\left[{\boldsymbol{\prime}} \right]$ Use implicit structural or behavioral code to combine their outputs. /// SOLUTION 11 // See the solution comments description in mult16_tree. uwire [19:0] prod_lo, prod_hi;

input uwire [15:0] b);
// [Pay attention to port widths. Do not make them larger than needed.

/// Problem 1 solution goes here, and in other modules.
// [*] Use implicit structural or behavioral code to combine their outputs.
/// SOLUTION

// See the solution comments description in mult16_tree.

uwire [17:0] prod_lo, prod_hi;

mult2 mlo(prod_lo, a[1:0], b); mult2 mhi(prod_hi, a[3:2], b); assign prod = prod_lo + (prod_hi << 2);</pre>

endmodule

11

```
/// Bonus Solution:
module mult_tree
 #( int wa = 16, int wb = 16, int wp = wa + wb )
  ( output uwire [wp:1] prod,
    input uwire [wa:1] a,
    input uwire [wb:1] b );
  /// BONUS SOLUTION
  11
  // This answers a question that was almost but not quite asked:
  11
       Using generate statements design a single module that can be
        instantiated into a module equivalent to mult16_tree,
  11
        mult8_tree, mult4_tree, and mult2, and also mult32_tree, etc.
  11
  if ( wa == 1 ) begin
     // Terminal case: 1 bit partial product.
     11
     assign prod = a ? b : 0;
     11
     // Equivalent to: prod = a * b;
  end else begin
     // Split a in half and recursively instantiate a module for each
     // half.
     localparam int wn = wa / 2;
     localparam int wx = wb + wn;
     uwire [wx:1] prod_lo, prod_hi;
     mult tree #(wn,wb) mlo( prod_lo, a[wn:1], b);
     mult tree #(wn,wb) mhi( prod_hi, a[wa:wn+1], b);
     // Combine the partial products.
     11
     assign prod = prod_lo + ( prod_hi << wn );</pre>
  end
```

endmodule

/// Do not modify the code below this point.

```
module mult2
```

(output uwire [17:0] prod, input uwire [1:0] a, input uwire [15:0] b);

/// DO NOT MODIFY THIS ROUTINE.

assign prod = a * b;

endmodule

```
module mult16_flat
```

#(int wa = 16, int wb = 16, int wp = wa + wb)
 (output uwire [31:0] prod, input uwire [15:0] a, b);

/// DO NOT MODIFY THIS ROUTINE.

```
`ifdef NEVER_DEFINE_ME
   // Emacs Lisp code to generate Verilog code for mult16_flat.
  (cl-loop for i from 0 to 14 by 2
   concat (if (= i 0) " assign prod = prod00"
            (format " + ( prod%02d << %d )" i i)) into prod
   concat (format "%s prod%02d" (if (= i 0) "" ",") i) into decl
   concat (format " mult2 m%d( prod%02d, a[%d:%d], b);\n" i i (+ i 1) i)
   into inst
   finally (insert (concat "\n uwire [17:0]" decl ";\n" inst "\n" prod ";\n")))
`endif
  uwire [17:0] prod00, prod02, prod04, prod06, prod08, prod10, prod12, prod14;
  mult2 m0( prod00, a[1:0], b);
  mult2 m2( prod02, a[3:2], b);
  mult2 m4( prod04, a[5:4], b);
  mult2 m6( prod06, a[7:6], b);
  mult2 m8( prod08, a[9:8], b);
  mult2 m10( prod10, a[11:10], b);
  mult2 m12( prod12, a[13:12], b);
  mult2 m14( prod14, a[15:14], b);
  assign prod = prod00 + ( prod02 << 2 ) + ( prod04 << 4 ) + ( prod06 << 6 ) + ( prod08 << 8 ) + ( prod10 << 10 ) + ( prod12 << 12 ) + ( ]
endmodule
module mult_operator
 #( int wa = 16, int wb = 16, int wp = wa + wb )
  ( output uwire [wp:1] prod, input uwire [wa:1] a, input uwire [wb:1] b );
  /// DO NOT MODIFY THIS ROUTINE.
  assign prod = a * b;
endmodule
/// Testbench Code
// cadence translate_off
```

module testbench;

```
localparam int wid = 16;
localparam int num_tests = 1000;
localparam int NUM_MULT = 4;
localparam int err_limit = 7;
logic [wid-1:0] plier, cand;
logic [2*wid-1:0] prod[NUM_MULT], shadow_prod;
mult operator mb0(prod[0], plier, cand);
mult16 flat mb1(prod[1], plier, cand);
mult16 tree mb2(prod[2], plier, cand);
multw tree #(wid,wid) mb3(prod[3], plier, cand);
string names[] = '{ "mult_operator", "mult16", "tree16", "treep" };
int err_cnt[NUM_MULT];
// Array of multiplier/multiplicand values to try out.
// After these values are used a random number generator will be used.
11
int tests[$] = {1,1, 1,2, 1,32, 32, 1};
initial begin
   $display("Starting testbench.\n");
   for ( int i=0; i<num_tests; i++ ) begin</pre>
      // Set multiplier and multiplicand values.
      11
      plier = tests.size() ? tests.pop_front() : <u>$random();</u>
      cand = tests.size() ? tests.pop_front() : <u>$random();</u>
      shadow_prod = plier * cand;
```

// Make sure each module's output is correct. 11 for (int mut=0; mut<NUM_MULT; mut++) begin</pre> if (shadow_prod !== prod[mut]) begin err_cnt[mut]++; if (err_cnt[mut] < err_limit)</pre> \$display("Error in %s test %4d: %x != %x (correct)\n", names[mut], i, prod[mut], shadow_prod); end end end $\ensuremath{{//}}$ Tests completed, report error count for each device. 11 for (int mut=0; mut<NUM_MULT; mut++) begin</pre> \$display("Mut %s, %d errors (%.1f%% of tests)\n", names[mut], err_cnt[mut], 100.0 * err_cnt[mut]/real'(num_tests)); end

\$finish(2);

end

endmodule

// cadence translate_on

LSU EE 4755

Homework 2 solution Due: 8 October 2019

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2019/hw02.v.html.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account, copy the assignment, and run the Verilog simulator and synthesis program on the unmodified homework file, hw02.v. Do this early enough so that minor problems (*e.g.*, password doesn't work) are minor problems.

Homework Correction (December 2019)

When assigned in October 2019 this assignment defined clz backward, starting at the least-significant bit. That has been corrected in this version and in the posted code.

Homework Overview

A count leading zeros (clz) operation returns the number of consecutive zeros starting at the most significant bit of an integer's binary representation. For example, the clz of 00101_2 is 2, the clz of 101_2 is 0, and the clz of 32-bit number 0_2 is 32. The Verilog module below computes the clz of its input:

```
module Clz
```

```
#( int w = 19, int ww = $clog2(w+1) )
  ( output var logic [ww-1:0] nlz, input uwire logic [w-1:0] a );
  uwire [w:0] aa = { a, 1'b1 };
  always_comb for ( int i=0; i<=w; i++ ) if ( aa[i] ) nlz = w-i;
endmodule</pre>
```

The module was written as behavioral code, but it does turn out to be synthesizable. Nevertheless, one may wonder if the synthesis program will do a good job with this. (Later in the semester we will learn what kind of hardware will be inferred for the description above.) One way to find out is to design a module which *should* be efficient and see how well it compares to what the synthesis program does with the module above. That, and the use of generate statements, is the subject of this assignment.

Testbench Code

The testbench for this assignment, which can be run when visiting the file in Emacs in a properly set-up account by pressing F9, tests the clz_tree module at several different widths. All should initially fail. A shortened sample of the testbench output appears below:

```
ncsim> run
** Starting tests for width 1.
Error for width 1: input 1: z != 0 (correct).
Error for width 1: input 0: z != 1 (correct).
Error for width 1: input 1: z != 0 (correct).
Error for width 1: input 0: z != 1 (correct).
Width 1, done with 10 tests, 10 errors.
** Starting tests for width 2.
Error for width 2: input 3: z != 0 (correct).
Width 2, done with 20 tests, 20 errors.
** Starting tests for width 5.
```

```
[snip]
Error for width 17: input 08959: z != 0 (correct).
Width 17, done with 170 tests, 170 errors.
ncsim: *W,RNQUIE: Simulation is complete.
ncsim> exit
Total number of errors: 610
```

The testbench prints the details of the first four errors it finds, and after that prints just one detail time per width. A total for each width and a grand total are printed, see the transcript above.

Use Simvision to debug your modules. Feel free to modify the testbench so that it presents inputs that facilitate debugging.

Synthesis

The synthesis script, syn.tcl, will synthesize clz (for reference) and clz_tree (your solution). Each module will be synthesized at three widths, and with two delay targets, an easy 10 ns and a un-achievable 0.1 ns. If a module doesn't synthesize -.001 s is shown for its delay. The script is run using the shell command genus -files syn.tcl, which invokes Cadence Genus. If you would like to synthesize additional modules or sizes edit syn.tcl near the bottom.

The synthesis script shows area (cost), delay, and the delay target in a neat table. Additional output of the synthesis program is written to file spew.log.

Problem 1 on next page.

Problem 1: Complete module clz_tree so that it computes the clz of its input in a tree-like fashion. For the non-terminal case it should instantiate two clz_tree modules and each should operate on part of the input, a. The outputs of these two modules should be appropriately combined. To help you get started, a recursive solution to Homework 1, mult_tree, is in hw02.v.

An easy mistake to make is using the wrong sized variable in a module port connection. Previously the Verilog software (ncelab to be precise) would issue a warning which was easy to miss. Now a port size mismatch is a fatal error.

For maximum credit do not use adders in your design. Adders can be avoided if the size of the low module is always a power of 2.

See the Verilog code check boxes for additional items to check for.

The solution appears below. The partial-credit solution, using an adder, appears first.

```
/// SOLUTION – With Adder. Two points would be deducted.
module clz tree fat
  \#( int w = 19, int ww = \frac{clog2(w+1)}{}
   ( output uwire [ww:1] nlz, input uwire [w:1] a );
   if (w == 1) begin
      assign nlz = ~a;
   end else begin
      localparam int wlo = w/2;
      localparam int whi = w - wlo;
      localparam int wwlo = $clog2(wlo+1);
      localparam int wwhi = $clog2(whi+1);
      uwire [wwlo:1] lz_lo;
      uwire [wwhi:1] lz_hi;
      clz_tree_fat #(wlo) clo( lz_lo, a[wlo:1]
                                                   );
      clz_tree_fat #(whi) chi( lz_hi, a[w:wlo+1] );
      assign nlz = lz_hi < whi ? lz_hi : whi + lz_lo;</pre>
   end
```

endmodule

The better solution, without the adder, is on the next page.

The solution below avoids an adder by setting the size of the hi module to a power of 2. If all of the high bits are zero, then the clz is the count of the number of low bits, plus a power of 2. The power of 2 to add is parameter **lhi** (see the code).

```
/// SOLUTION – Without Adder
module clz_tree #( int w = 19, int ww = $clog2(w+1) )
               ( output uwire [ww-1:0] nlz, input uwire [w-1:0] a );
  if (w == 1) begin
     assign nlz = !a[0];
  end else if ( w == 2 ) begin
     assign nlz = { !a[0] && !a[1], !a[1] && a[0] };
  end else begin
     // Set whi to the largest power of 2 strictly less than w.
     11
     localparam int lhi = $clog2(w) - 1;
     localparam int whi = 1 << lhi;</pre>
     localparam int wwhi = lhi + 1;
     // Then set wlo to the number of remaining bits.
     11
     localparam int wlo = w - whi;
     uwire [wwhi-1:0] nlz_lo, nlz_hi; // Note: nlz_lo may be 1 bit wider than needed.
     // Instantiate recursive modules.
     11
     clz_tree #(wlo,wwhi) clo( nlz_lo, a[wlo-1:0] );
     clz_tree #(whi,wwhi) chi( nlz_hi, a[w-1:wlo] );
     // Split the nlz_lo and nlz_hi outputs into "overflow" (MSB) bits,
     // ov_lo and ov_hi, and the remaining bits lz_lo and lz_hi.
     11
     uwire ov_lo, ov_hi;
     uwire [lhi-1:0] lz_lo, lz_hi;
     assign { ov_lo, lz_lo } = nlz_lo;
     assign { ov_hi, lz_hi } = nlz_hi;
     assign nlz = !ov_hi ? { 2'b00, lz_hi } : // Case 0
                   !ov_lo ? { 2'b01, lz_lo } : // Case 1
                            { 2'b10, lz_lo }; // Case 2
     // Case 0:
      // Input to chi has a 1, so just use nlz_hi.
     11
         This case occurs when the MSB of nlz_hi is 0.
     // For this case just set nlz to nlz_hi.
     11
     // Case 1:
     // Input to chi is all zeros, and wlo < whi or nlz_lo < whi.</pre>
     // For this case set nlz = whi + nlz_lo = { 2'b01, lz_lo }.
     11
     // Case 2:
     // Input to chi is all zeros, and nlz_lo == whi.
     // If this condition is true then ov_lo = 1
     // For this case set
      11
            nlz = whi + nlz_lo = { 2'b1 + ov_lo, lz_lo } = { 2'b10, lz_lo }
```

 $\quad \text{end} \quad$

 ${\tt endmodule}$

Problem 2: Run the synthesis program and indicate how your module compares to the behavioral module, clz. Indicate which results are expected, and which are not expected, and explain why.

Attention students studying for exams: A good practice problem would be to show the synthesized hardware for these modules.

The behavioral model looks at bits sequentially, starting at the most-significant bit. The hardware as initially inferred would have a chain of multiplexors either selecting i if aa[i] were 1, or the prior value of nlz otherwise. The nlz output would pass through w multiplexors, for a delay of $w u_t$ after optimizing for the fact that i is constant.

In contrast the critical path through the tree modules passes through $\lceil \lg w \rceil$ units, and so that should be faster. In the 0.1 ns delay target results, shown below, the behavioral model is fastest at w = 30 bits and the adder-less clz_tree module is only fastest at w = 32 bits. At best, clz_tree never does poorly when delay is a priority. The behavioral module however is consistently more costly than clz_tree.

Module Name	Area	Delay	Delay	
		Actual	Target	
clz_w30	18540	1.653	10.000	ns
clz_tree_w30	17977	1.653	10.000	ns
clz_tree_fat_w30	17977	1.653	10.000	ns
clz_w32	26290	3.110	10.000	ns
clz_tree_w32	21706	1.425	10.000	ns
clz_tree_fat_w32	21401	1.296	10.000	ns
clz_w35	23140	1.300	10.000	ns
clz_tree_w35	22578	1.300	10.000	ns
clz_tree_fat_w35	26073	2.094	10.000	ns
clz_w30_1	30053	0.504	0.100	ns
clz_tree_w30_4	38532	0.650	0.100	ns
clz_tree_fat_w30_1	37798	0.861	0.100	ns
clz_w32_1	36476	1.007	0.100	ns
clz_tree_w32_5	37356	0.577	0.100	ns
clz_tree_fat_w32_2	32254	0.634	0.100	ns
clz_w35_1	37008	0.606	0.100	ns
clz_tree_w35_6	37008	0.606	0.100	ns
clz_tree_fat_w35_1	37008	0.606	0.100	ns

/// LSU EE 4755 Fall 2019 Homework 2 -- SOLUTION
// Assignment <u>https://www.ece.lsu.edu/koppel/v/2019/hw02.pdf</u>
/// Solution Problem 2: <u>https://www.ece.lsu.edu/koppel/v/2019/hw02_sol.pdf</u>
`default_nettype none

```
/// Problem 1
11
///
      Complete clz_tree so that it computes the clz of its input recursively.
11
11
      [...] Split the input between two recursive instantiations ...
          .. and properly combine the results.
11
       [.] Don't forget the terminal case, maybe for w == 1.
11
      [<] For maximum credit, avoid any use of adders ...</pre>
11
11
          .. by making the width of the "hi" module a power of 2.
11
11
      [.] Make sure that port connections are the correct size ...
          .. mismatched ports are Verilog errors in this assignment.
11
11
      [...] Do not make port widths larger than needed.
11
      [~] Make sure that the testbench does not report errors.
      [/] Module must be synthesizable. Use command: genus -files syn.tcl
11
11
      [<] As always, avoid costly, slow, and confusing code.</pre>
11
/// Solution Discussion
11
// Two solutions appear below.
11
// The clz_tree_fat module is much simpler, but it uses an adder.
// Two points would be deducted if this were given as a solution
11
// The clz_tree module does not use an adder. It would get full credit.
```

```
/// SOLUTION -- With Adder. Two points would be deducted.
module clz_tree_fat
  #( int w = 19,
    int ww = <u>$clog2(w+1)</u>)
  ( output uwire [ww:1] nlz,
    input uwire [w:1] a );
  if ( w == 1 ) begin
    assign nlz = ~ a;
  end else begin
```

```
\leftarrow \rightarrow Fall 2019
                  \leftarrow \rightarrow Homework 2
          localparam int wlo = w/2;
          localparam int whi = w - wlo;
          localparam int wwlo = $clog2(wlo+1);
          localparam int wwhi = $clog2(whi+1);
          uwire [wwlo:1] lz_lo;
          uwire [wwhi:1] lz_hi;
          clz tree fat #(wlo) clo( lz_lo, a[wlo:1]
                                                      );
          clz tree fat #(whi) chi( lz_hi, a[w:wlo+1] );
          assign nlz = lz_hi < whi ? lz_hi : whi + lz_lo;</pre>
       end
    endmodule
    /// SOLUTION -- Without Adder
   module clz_tree
      #(int w = 19,
         int ww = \frac{clog2}{w+1})
       ( output uwire [ww-1:0] nlz,
         input uwire [w-1:0] a );
       if ( w == 1 ) begin
          assign nlz = !a[0];
       end else if ( w == 2 ) begin
          assign nlz = { !a[0] && !a[1], !a[1] && a[0] };
       end else begin
          // Set whi to the largest power of 2 strictly less than w.
          11
          localparam int lhi = \frac{clog2}{w} - 1;
          localparam int whi = 1 << lhi;</pre>
          localparam int wwhi = lhi + 1;
          // Then set wlo to the number of remaining bits.
          11
          localparam int wlo = w - whi;
          uwire [wwhi-1:0] nlz_lo, nlz_hi;
          // Note: nlz_lo may be one bit wider than needed.
          // Instantiate recursive modules.
          //
          clz tree #(wlo,wwhi) clz_lo( nlz_lo, a[wlo-1:0] );
          clz tree #(whi,wwhi) clz_hi( nlz_hi, a[w-1:wlo] );
          // Split the nlz_lo and nlz_hi outputs into "overflow" (MSB) bits,
```

```
Homework Solution Sol Code Sol Code hw02-sol-try.v.html
```

```
// ov_lo and ov_hi, and the remaining bits lz_lo and lz_hi.
  11
  uwire ov lo, ov hi;
  uwire [lhi-1:0] lz_lo, lz_hi;
  11
  assign { ov_lo, lz_lo } = nlz_lo;
  assign { ov_hi, lz_hi } = nlz_hi;
  // Assemble nlz in one of three ways (Case 0, Case 1, Case 1)
  11
  assign nlz = !ov_hi ? { 2'b00, lz_hi } : // Case 0
                !ov_lo ? { 2'b01, lz_lo } : // Case 1
                         { 2'b10, lz_lo }; // Case 2
  11
  // Case 0:
        Input to clz_hi has a 1, so just use nlz_hi.
  11
       This case occurs when the MSB of nlz_hi is 0.
  //
       For this case just set nlz to nlz_hi.
  11
  11
  // Case 1:
  11
        Input to clz_hi is all zeros, and wlo < whi or nlz_lo < whi.
  11
        For this case set nlz = whi + nlz_{lo} = \{ 2'b01, lz_{lo} \}.
  11
  // Case 2:
  11
       Input to clz_hi is all zeros, and nlz_lo == whi.
  11
       If this condition is true then ov_lo = 1
   11
       For this case set
  11
         nlz = whi + nlz_{lo} = \{ 2'b1 + ov_{lo}, lz_{lo} \} = \{ 2'b10, lz_{lo} \}
end
```

```
endmodule
```

 $\leftarrow \rightarrow$ Fall 2019

 $\leftarrow \rightarrow$ Homework 2

```
/// A Behavioral CLZ Description
module ClZ
#( int w = 19,
    int ww = <u>$clog2(w+1)</u>)
( output var logic [ww-1:0] nlz,
    input uwire logic [w-1:0] a );
uwire [w:0] aa = { a, 1'b1 };
always_comb for ( int i=0; i<=w; i++ ) if ( aa[i] ) nlz = w-i;</pre>
```

endmodule

// cadence translate_off

module testbench;

```
// The widths (values of w) at which the modules will be instantiated. //
```

```
\leftarrow \rightarrow Fall 2019
                  \leftarrow \rightarrow Homework 2
                                              Homework Solution Sol Code Sol Code
       localparam int widths[] = { 1, 2, 5, 8, 13, 15, 17 };
       // localparam int nw = widths.size();
       localparam int nw = 7; // Cadence, please fix this.
       initial if ( nw != widths.size() )
         $fatal(1,"Constant nw should be %Od.\n",widths.size() );
       int t errs;
                     // Total number of errors.
       initial t_errs = 0;
       final <u>$write("Total number of errors: %0d\n",t_errs);</u>
       uwire d[nw:-1]; // Start / Done signals.
       assign d[-1] = 1; // Initialize first at true.
       // Instantiate a testbench at each size.
       11
       for ( genvar i=0; i<nw; i++ )</pre>
         testbench_n #(widths[i]) t2( .done(d[i]), .start(d[i-1]) );
```

```
endmodule
```

```
module testbench n
  #(int w = 20)
   ( output logic done, input uwire start );
   localparam int ww = <u>$clog2(w+1);</u>
   localparam int n_tests = w * 10;
   uwire [ww:1] nlz;
   logic [w-1:0] a;
   clz_tree #(w) cO(nlz,a);
   // clz #(w) c0(nlz,a);
   initial begin
      automatic int n_errs = 0;
      wait( start );
      $write("** Starting tests for width %0d.\n",w);
      for ( int t=0; t<n_tests; t++ ) begin</pre>
         automatic int lz = {t} % ( w + 1 );
         a = { 1'b1, (w)'({<u>$random</u>}) } >> ( lz + 1 );
         #1;
         if ( nlz !== lz ) begin
            n_errs++; testbench.t_errs++;
            if ( testbench.t_errs < 5 || n_errs < 2 )</pre>
              $write("Error for width %2d: input %h: %d != %0d (correct).\n",
                      w, a, nlz, lz);
```

end

end

<u>\$write</u>("Width %0d, done with %0d tests, %0d errors.\n",w,n_tests,n_errs);

done = 1;

end

endmodule

// cadence translate_on

11 /// LSU EE 4755 Fall 2019 Homework 2 -- SOLUTION 11 /// Assignment https://www.ece.lsu.edu/koppel/v/2019/hw02.pdf /// Solution Problem 2: https://www.ece.lsu.edu/koppel/v/2019/hw02_sol.pdf `default_nettype none /// Problem 1 11 111 Complete clz_tree so that it computes the clz of its input recursively. 11 11 [/] Split the input between two recursive instantiations and properly combine the results. 11 11 [~] Don't forget the terminal case, maybe for w == 1. [<] For maximum credit, avoid any use of adders ...</pre> 11 11 .. by making the width of the "hi" module a power of 2. 11 11 [] Make sure that port connections are the correct size mismatched ports are Verilog errors in this assignment. 11 [~] Do not make port widths larger than needed. 11 [...] Make sure that the testbench does not report errors. 11 11 [/] Module must be synthesizable. Use command: genus -files syn.tcl 11 11 [<] As always, avoid costly, slow, and confusing code.</pre> /// Solution Discussion 11 // Two solutions appear below. 11 // The clz_tree_fat module is much simpler, but it uses an adder. // Two points would be deducted if this were given as a solution 11 // The clz_tree module does not use an adder. It would get full credit.

/// SOLUTION -- With Adder. Two points would be deducted.
module clz_tree_fat
 #(int w = 19,
 int ww = <u>\$clog2(w+1)</u>)
 (output uwire [ww:1] nlz,
 input uwire [w:1] a);
 if (w == 1) begin
 assign nlz = ~ a;

```
end else begin
```

```
\leftarrow \ \rightarrow \ \text{Homework} \ 2
\leftarrow \rightarrow Fall 2019
          localparam int wlo = w/2;
          localparam int whi = w - wlo;
          localparam int wwlo = $clog2(wlo+1);
          localparam int wwhi = $clog2(whi+1);
          uwire [wwlo:1] lz_lo;
          uwire [wwhi:1] lz_hi;
          clz tree fat #(wlo) clo( lz_lo, a[wlo:1]
                                                       );
          clz tree fat #(whi) chi( lz_hi, a[w:wlo+1] );
          assign nlz = lz_hi < whi ? lz_hi : whi + lz_lo;</pre>
       end
    endmodule
     /// SOLUTION -- Without Adder
   module clz_tree
      #(int w = 19,
         int ww = \frac{clog2}{w+1}
       ( output uwire [ww-1:0] nlz,
         input uwire [w-1:0] a );
       if (w == 1) begin
          assign nlz = !a[0];
       end else if ( w == 2 ) begin
          assign nlz = { !a[0] && !a[1], !a[1] && a[0] };
       end else begin
          // Set whi to the largest power of 2 strictly less than w.
          11
          localparam int lhi = <u>$clog2(w)</u> - 1;
          localparam int whi = 1 << lhi;</pre>
          localparam int wwhi = lhi + 1;
          // Then set wlo to the number of remaining bits.
          11
          localparam int wlo = w - whi;
          uwire [wwhi-1:0] nlz_lo, nlz_hi;
          // Note: nlz_lo may be one bit wider than needed.
          // Instantiate recursive modules.
          11
          clz tree #(wlo,wwhi) clz_lo( nlz_lo, a[wlo-1:0] );
          clz tree #(whi,wwhi) clz_hi( nlz_hi, a[w-1:wlo] );
          // Split the nlz_lo and nlz_hi outputs into "overflow" (MSB) bits,
```

```
\leftarrow \rightarrow Fall 2019
                 \leftarrow \rightarrow Homework 2
                                             Homework Solution Sol Code Sol Code
          // ov_lo and ov_hi, and the remaining bits lz_lo and lz_hi.
          11
          uwire ov lo, ov hi;
          uwire [lhi-1:0] lz_lo, lz_hi;
          11
          assign { ov_lo, lz_lo } = nlz_lo;
          assign { ov_hi, lz_hi } = nlz_hi;
          // Assemble nlz in one of three ways (Case 0, Case 1, Case 1)
          11
          assign nlz = !ov_hi ? { 2'b00, lz_hi } : // Case 0
                        !ov_lo ? { 2'b01, lz_lo } : // Case 1
                                 { 2'b10, lz_lo }; // Case 2
          11
          // Case 0:
               Input to clz_hi has a 1, so just use nlz_hi.
          11
               This case occurs when the MSB of nlz_hi is 0.
          //
               For this case just set nlz to nlz_hi.
          11
          11
          // Case 1:
          11
               Input to clz_hi is all zeros, and wlo < whi or nlz_lo < whi.
               For this case set nlz = whi + nlz_lo = { 2'b01, lz_lo }.
          11
          11
          // Case 2:
          11
               Input to clz_hi is all zeros, and nlz_lo == whi.
          11
               If this condition is true then ov_lo = 1
          11
               For this case set
          11
                 nlz = whi + nlz_{lo} = \{ 2'b1 + ov_{lo}, lz_{lo} \} = \{ 2'b10, lz_{lo} \}
```

```
end
```

endmodule

```
/// A Behavioral CLZ Description
module ClZ
#( int w = 19,
    int ww = <u>$clog2(w+1)</u>)
( output var logic [ww-1:0] nlz,
    input uwire logic [w-1:0] a );
uwire [w:0] aa = { a, 1'b1 };
always_comb for ( int i=0; i<=w; i++ ) if ( aa[i] ) nlz = w-i;</pre>
```

endmodule

// cadence translate_off

module testbench;

```
// The widths (values of w) at which the modules will be instantiated. //
```

```
\leftarrow \rightarrow Fall 2019
                  \leftarrow \rightarrow Homework 2
                                              Homework Solution Sol Code Sol Code
       localparam int widths[] = { 1, 2, 5, 8, 13, 15, 17 };
       // localparam int nw = widths.size();
       localparam int nw = 7; // Cadence, please fix this.
       initial if ( nw != widths.size() )
         $fatal(1,"Constant nw should be %Od.\n",widths.size() );
       int t errs;
                     // Total number of errors.
       initial t_errs = 0;
       final <u>$write("Total number of errors: %0d\n",t_errs);</u>
       uwire d[nw:-1]; // Start / Done signals.
       assign d[-1] = 1; // Initialize first at true.
       // Instantiate a testbench at each size.
       11
       for ( genvar i=0; i<nw; i++ )</pre>
         testbench_n #(widths[i]) t2( .done(d[i]), .start(d[i-1]) );
```

```
endmodule
```

```
module testbench_n
  #(int w = 20)
   ( output logic done, input uwire start );
   localparam int ww = <u>$clog2(w+1);</u>
   localparam int n_tests = w * 10;
   uwire [ww:1] nlz;
   logic [w-1:0] a;
   clz_tree #(w) cO(nlz,a);
   // clz #(w) c0(nlz,a);
   initial begin
      automatic int n_errs = 0;
      wait( start );
      $write("** Starting tests for width %0d.\n",w);
      for ( int t=0; t<n_tests; t++ ) begin</pre>
         automatic int lz = \{t\} \% (w + 1);
         a = { 1'b1, (w)'({<u>$random</u>}) } >> ( lz + 1 );
         #1;
         if ( nlz !== lz ) begin
            n_errs++; testbench.t_errs++;
            if ( testbench.t_errs < 5 || n_errs < 2 )</pre>
               $write("Error for width %2d: input %h: %d != %0d (correct).\n",
                      w, a, nlz, lz);
```

end

end

<u>\$write</u>("Width %0d, done with %0d tests, %0d errors.\n",w,n_tests,n_errs);

done = 1;

end

endmodule

// cadence translate_on

LSU EE 4755

Homework 3 solution Due: 23 October 2019

Problem 1: Appearing below is a module excerpted from the solution to Homework 1. Compute the cost and delay of this module using the simple model under the following assumptions:

- The inputs arrive at t = 0. Don't assume that any bit is early or late, they all arrive at exactly t = 0.
- A ripple adder will be used to implement addition.
- Apply obvious optimizations. In particular, don't use a BFA if a BHA would suffice. And only use a BHA if that is needed.
- Don't overlook the fact that one of the shifter inputs is a constant.

Show the cost and delay in terms of wa and wb, but use symbol a for wa and b for wb. For example, "The cost is $(a + b)9 u_c$ and the delay is $(a + b)2 u_t$." (Those answers assume that BFAs are used for the entire module, which is wrong.)

The simple model slides (AOTW) don't show the cost and delay of a BHA, so work that out yourselves.

```
assign prod = prod_lo + ( prod_hi << wn );</pre>
```

endmodule

Short answer: Cost: $[9b + 3\frac{a}{2}] \mathbf{u}_c$, Delay: $[2 + 2b + \frac{a}{2}] \mathbf{u}_t$

Long answer: Because prod_hi is shifted and because prod_lo and prod_hi are the same width the adder can be broken into three regions: an a/2-bit low region consisting of the low a/2 bits of prod_lo, a b-bit middle region consisting of the high b bits of prod_lo and the low b bits of prod_hi, and an a/2-bit region consisting of the high a/2 bits of prod_hi.

There is no hardware at all for the low region. The middle region consists of b binary full adders, and the high region consists of a/2 binary half adders. (The high region has to handle the carry out from the middle region.)

Under the simple model a BFA cost $9 u_c$ and in a *w*-bit ripple configuration has a delay of $[2 + 2w] u_t$. A BHA can be derived from a BFA by setting the **a** or **b** input to logic zero and then simplifying. Such a BHA would have a cost of $3 u_c$ per bit and a delay of $1 u_t$ per bit in a ripple configuration.

The total cost is then $[9b + 3\frac{a}{2}] \mathbf{u}_c$ and the delay is $[2 + 2b + \frac{a}{2}] \mathbf{u}_t$.

There's another problem on the next page!

Problem 2: A *w*-bit multiplier needs to add together *w* partial products using w - 1 adders. A naïve timing analysis of a non-tree ripple adder implementation would compute a delay of $w(2 \times 2w + 2) = (4w^2 + w) u_t$ for the 2*w*-bit product using the simple model and ignoring ripple-unit cascading. As we should know $4w^2$ is not a good term to have in an expression for time. The goal of this problem is to see how the tree multiplier compares to this naïve timing analysis.

Appearing below is the Bonus Solution to Homework 1 in which a single mult_tree module is used rather than separate modules mult16_tree, mult8_tree, etc. Also shown is a module, my_module, that instantiates the mult_tree. Also shown a page or two ahead is the diagram from Homework 1. You may want to use this to help work out the solution to this problem.

Analyze the cost and performance of my_module as described below. When computing the cost and performance don't forget to account for the full elaboration, not just the top level. For example, my_module with w=4 consists of one mult_tree at w=4 and two mult_tree modules at w=2, and four mult_tree modules at w=1.

```
module mult tree
  #( int wa = 16, int wb = 16, int wp = wa + wb )
   ( output logic [wp:1] prod,
     input uwire [wa:1] a,
     input uwire [wb:1] b );
  if (wa == 1) begin
      assign prod = a ? b : 0;
      // Equivalent to: prod = a * b;
  end else begin
      // Split a in half and recursively instantiate a module for each half.
      localparam int wn = wa / 2;
      localparam int wx = wb + wn;
      uwire [wx:1] prod_lo, prod_hi;
      mult_tree #(wn,wb) mlo( prod_lo, a[wn:1], b );
      mult_tree #(wn,wb) mhi( prod_hi, a[wa:wn+1], b );
      // Combine the partial products.
      always_comb prod = prod_lo + ( prod_hi << wn );</pre>
   end
endmodule
module my module
  \#( int w = 8, int wp = 2 * w )
   ( output uwire [wp-1:0] p,
     input uwire [w-1:0] x, y );
  mult_tree #(w,w) mt1(p,x,y);
```

```
endmodule
```

(a) Compute the cost of my_module using the same assumptions as in Problem 1. The cost must

be in terms of w. It's okay, indeed encouraged, to use sample values like w = 16 when working out the problem, but once you have it figured out give the answer in terms of w. (If you have not solved Problem 1 then use the incorrect sample answers provided in Problem 1.)

The following identity may be helpful: $\sum_{i=0}^{m-1} 2^i = 2^m - 1$. In such a summation *i* might indicate the level of recursion and 2^i might indicate the number of modules at that recursion level. For the top level of the recursion i = 0.

Let j denote the recursion level such that $a = 2^j$, and note that j starts at $\lg w$ with the initial instantiation of **mult-tree** (the one made by **my-module**) and ends at j = 0, the terminal case. At level j there are a total of $w/2^j$ instances. For the terminal case, j = 0 and a = 1, **mult-tree** produces just a mux, which itself will be optimized to b AND gates. There will be $w/2^0$ instances for j = 0, so their total cost will be $w^2 u_c$, after setting b = w.

The j > 0 levels consist of binary full and half adders. Each instance has about w BFAs and $a/2 = 2^{j-1}$ BHAs. Let c_f denote the per-bit cost of a BFA and c_h denote the per-bit cost of a BHA. By the simple model $c_f = 9 u_c$ and $c_h = 3 u_t$. (In the BHA the carry out can be used to compute the sum, reducing the number of additional gates for the XOR to 2.) Then the total cost of the adders is

$$\sum_{j=1}^{\lg w} \frac{w}{2^{j}} \left(wc_{f} + 2^{j-1}c_{h} \right)$$
$$= w \sum_{j=1}^{\lg w} \left(\frac{wc_{f}}{2^{j}} + \frac{c_{h}}{2} \right)$$
$$= w^{2} \sum_{j=1}^{\lg w} \frac{c_{f}}{2^{j}} + \frac{w}{2} \sum_{j=1}^{\lg w} c_{h}$$
$$= w^{2} \left(1 - \frac{1}{w} \right) c_{f} + \frac{w}{2} (\lg w) c_{h}$$

(Note that $\sum_{j=1}^{\lg w} 2^{-j} = (1-1/w)$.) The total overall cost is

$$w^2 \mathbf{u}_{c} + w^2 \left(1 - \frac{1}{w}\right) c_f + \frac{w}{2} (\lg w) c_h$$
$$= \left[10w^2 - 9w + \frac{3w}{2} (\lg w)\right] \mathbf{u}_{c}$$

An important point to note is that the cost is proportional to w^2 . That should not be surprising because we know that to multiply two w-bit quantities we need w - 1 adders, each costing about wc_f .

(b) Compute the delay of the multiplier using a simplifying assumption similar to the one used in Problem 1: when computing the delay of prod = prod_lo + (prod_hi << wn) assume that all bits for prod_lo and prod_hi arrive at the same time and that all bits of prod are sent to the outputs at the same time. (Don't like simplifying assumptions? The next subproblem is for you!)

Show your answer for w=8 and as an expression in terms of w. Don't forget to consider the entire elaboration, not just the top-level module.

The launch point starts at j = 0 (the terminal case), which depends only on the inputs to my-module, a and b. The delay is just 1 u_t .

Level j > 0 has an adder consisting of w BFAs and 2^{j-1} BHAs. The total delay through that is $[2(w-1) + 2^{j-1}] u_t$, where the delay through a 2^{j-1} -bit BHA is $2^{j-1} u_t$. The total delay including the AND gates is

$$\begin{bmatrix} 1 + \sum_{j=1}^{\lg w} \left(2(w-1) + 2^{j-1} \right) \end{bmatrix} u_{t}$$

= $[1 + 2(w-1)(\lg w) + w - 1] u_{t}$
= $[w + 2(w-1)(\lg w)] u_{t}$
 $\approx 2w \lg w u_{t}$

The dominant term is $2w \lg w$ which is not as bad as a linear connection of adders which would have a delay of $\approx 2w^2 u_t$ under similar assumptions.

(c) Compute the delay of the multiplier without the simplifying assumption. That is, account for the fact that the less-significant bits of $mult_tree$ will be ready before the more-significant bits.

Show your answer for w=8 and as an expression in terms of w. Don't forget to consider the entire elaboration, not just the top-level module.

At level j the least significant BFA (which could actually be a BHA, but we'll keep it simple) is connected to bit 2^{j-1} of prod-lo and bit zero of prod-hi. Since level j is waiting for 2^{j-1} to be ready, the next level, j + 1, must be waiting for bit 2^j . Therefore for level j we need to compute the delay though $2^{j-1} + 1$ BFAs: stating at the least significant BFA (bit position 2^{j-1}) and ending at the BFA computing bit 2^j . The delay for w bits for a ripple adder under the simple model is 2(w+1) ut, so the delay at level j before j+1 can start is $2((2^{j-1}+1)+1) = 2^j + 4$.

For level j = 0 the delay is $1 u_t$ (an AND gate). For level $j = \lg w$ we need to add on the remaining bits in the ripple adder: w/2 - 1 BFA delays and w/2 BHA delays.

The total delay is:

$$\left[1 + \left(\sum_{j=1}^{\lg w} 2^j + 4\right) + \left(\frac{w}{2} - 1\right)2 + \frac{w}{2}\right] u_t$$
$$= \left[1 + 2(2w - 1) + 4(\lg w) + \left(\frac{w}{2} - 1\right)2 + \frac{w}{2}\right] u_t$$
$$= \left[5.5w + 4(\lg w) - 1\right] u_t$$

Useful diagram on next page.



Use the diagram below to help work out solutions.

LSU EE 4755 Homework 4 solution Due: 11 November 2019

For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab follow https://www.ece.lsu.edu/koppel/v/2019/hw04.v.html.

Problem 0: Following instructions at https://www.ece.lsu.edu/koppel/v/proc.html, set up your class account (if for whatever reason you haven't done so or neeed to do it again), copy the assignment, and run the Verilog simulator and synthesis program on the unmodified homework file, hw04.v. Do this early enough so that minor problems (*e.g.*, password doesn't work) are minor problems.

Homework Overview

Module best_match_behavioral has two inputs, a longer vector, val, and a short vector, k. It sets pos to the start of a subvector of val that best matches k and sets err to the number of bit positions that don't match. For example, suppose val = 8'b11110000 and k=4'b1100. Then pos would be set to 2 and err to 0 because there is an exact match at position 2 in val. If k=4'b1101 then there isn't an exact match for k in val, but at position 2 there is a match with one error. If k=2'b00 then there are matches at positions 0, 1, and 2, all with zero errors.

Module **best_match_behavioral** is combinational (and was written as a behavioral module). In this assignment a sequential version will be written and analyzed.

Testbench Code

The testbench for this assignment, which can be run when visiting the file in Emacs in a properly set-up account by pressing [F9], tests the modules. Initially, the testbench will exit because module best_match has not responded in sufficient time. When that happens one of the last lines of the testbench output shows that the final cycle count is the same as the cycle limit (128 below), and "CYCLE LIMIT EXCEEDED" is shown.

```
ncsim> run
Exit from clock loop at cycle 128, limit 128. ** CYCLE LIMIT EXCEEDED **
ncsim: *W,RNQUIE: Simulation is complete.
ncsim> exit
```

Compilation finished at Mon Nov 4 17:56:24

To get rid of this message best_match must handshake correctly, see Problem 1. If best_match responds in time, the testbench will check to see if pos is in the right range. The output below shows errors when pos is out of range: Error in best_match, test # 3, pos out of range: 0xff

```
Error in best_match, test # 4, pos out of range: 0xff
Done with best_match_behavioral tests, 0 errors found.
Done with best_match tests, 1000 errors found.
Exit from clock loop at cycle 59001, limit 59069.
ncsim: *W,RNQUIE: Simulation is complete.
ncsim> exit
```

The output err is supposed to be the number of non-matching bits at pos. If not, the testbench shows output like:

```
Error in best_match, test #2, err wrong 1 != 3 (correct) pos284 ^ 01Error in best_match, test #3, err wrong 1 != 2 (correct) pos131f ^ 3dError in best_match, test #4, err wrong 1 != 2 (correct) pos478 ^ f9Done with best_match_behavioral tests,0errors found.
```

Done with best_match tests, 972 errors found. Exit from clock loop at cycle 59001, limit 59069. ncsim: *W,RNQUIE: Simulation is complete. ncsim> exit

For test # 4, the testbench reports that err was 1 but should have been 2. The line also shows that pos was set to 4, and that val at that position was 78 (in hexadecimal) and that k=f9.

The testbench also checks whether the $\tt err$ returned is the minimum error for that value of <code>val</code> and <code>k</code>.

The testbench prints the details of the first few errors it finds. A grand total is printed at the end, see the transcript above.

Use Simvision to debug your modules. Feel free to modify the testbench so that it presents inputs that facilitate debugging.

Synthesis

The synthesis script, syn.tcl, will synthesize best_match_behavioral (for reference) and best_match (your solution). Each module will be synthesized at three widths, and with two delay targets, an easy 90 ns and a un-achievable 0.1 ns. If a module doesn't synthesize -.001 s is shown for its delay. The script is run using the shell command genus -files syn.tcl, which invokes Cadence Genus. If you would like to synthesize additional modules or sizes edit syn.tcl near the bottom.

The synthesis script shows area (cost), delay, and the delay target in a neat table. Additional output of the synthesis program is written to file spew-file.log.

Problem 1 on next page.

Problem 1: Complete module best_match so that it computes the best match sequentially as described below. In addition to val and k, the module has 1-bit inputs start and clk and 1-bit output ready.

Handshaking works as follows: When start=1 at a positive edge the module should set ready to zero. It should then start scanning for the best match, checking one shifted position per cycle. The maximum number of cycles needed should be wv-wk plus one or two more needed for handshaking. (The testbench will wait 2*wv cycles before giving up.) The module should set err and pos to their correct values and ready to 1.

The inputs, val and k will be held steady at least until ready is set to 1.

The module must use the pop (population) module (in hw04.v) to compute possible values for err. That is, don't use something like the b loop in best_match_behavioral to accumulate the sum e. Instead compute the XOR of the appropriate bit range and provide that to the pop module as an input.

For maximum credit avoid the use of large (such as wv-input) multiplexors in your design, or the use of a non-constant shifter.

The module must be synthesizable and correct.

The behavioral best match module is shown below for reference.

```
module best_match_behavioral
```

```
#( int wv = 32, int wk = 10, int wvb = $clog2(wv), int wkb = $clog2(wk+1) )
  ( output logic [wvb:1] pos, // Position of best match.
    output logic [wkb:1] err, // Number of non-matching bits.
    input uwire [wv-1:0] val, input uwire [wk-1:0] k );
```

always_comb begin

```
automatic int best_err = wk + 1;
automatic int best_pos = -1;
for ( int p=0; p<=wv-wk; p++ ) begin
    automatic int e = 0;
    for ( int b=0; b<wk; b++ ) e += k[b] !== val[p+b];
    if ( e < best_err ) begin
        best_err = e;
        best_pos = p;
    end
end
err = best_err;
pos = best_pos;
```

end

endmodule

Solution on next page.

The solution appears below. The biggest difference between best_match_behavioral and best_match is that the p-loop has been eliminated, and the iteration variable, p, has been declared as a variable. The variable p is initialized to zero when start is asserted and then incremented each cycle until it points to the last position of a possible match, wv-wp.

Another difference is that the \mathbf{b} loop, used to total the number of incorrect bit positions, has been replaced by the pop module. The input to the pop module is a bit vector, e_vec , which is constructed by exclusive-or'ing k with the low bits of sh_val. Bit i of e_vec is 1 if the bit i of k is different than bit i of sh_val, bit i is 0 if the bits are the same. Equivalently, e_vec[i] = k[i] !== sh_val[i], or e_vec[i] = k[i] ^ sh_val[i]. Rather than iterating over i the entire value is computed using the bitwise exclusive OR operator: $e_vec = k \circ sh_val$.

The register sh_val is initialized to val and then shifted right by one bit each iteration. This avoids the need for a shifter. For example, if the error vector were computed using $e_vec = k \cap val[p + : wk]$; a shifter would be needed for val [p +: wk], to extract wk bits starting at position p.

```
module best match
```

```
#( int wv = 32, int wk = 10, int wvb = $clog2(wv), int wkb = $clog2(wk+1) )
( output logic [wvb:1] pos, output logic [wkb:1] err, output logic ready,
  input uwire [wv-1:0] val, input uwire [wk-1:0] k, input uwire start, clk );
logic [wv-1:0] sh_val;
logic [wvb-1:0] p;
uwire [wk-1:0] e_vec = k ^ sh_val[wk-1:0];
uwire [wkb-1:0] e;
pop #(wk,wkb) p1( e, e_vec );
always_ff @( posedge clk )
  if ( start == 1 ) begin
     ready = 0;
     sh_val = val;
     p = 0;
     err = wk; // wk+1 might overflow err.
   end else if ( !ready ) begin
     if ( e < err ) begin err = e; pos = p; end</pre>
     ready = p == wv - wk;
     p++;
     sh_val >>= 1;
   end
```

```
endmodule
```

Problem 2: Run the synthesis program and indicate how your module compares to the behavioral module.

Synthesis results appear below.

Module Name	Area	Delay Actual	Delay Target
			0
best_match_wv16	47923	3.786	90.000 ns
best_match_mux_wv16	46566	5.181	90.000 ns
best_match_behavioral_wv16	87155	10.862	90.000 ns
best_match_wv24	60757	3.675	90.000 ns
best_match_mux_wv24	60566	5.503	90.000 ns
best_match_behavioral_wv24	192546	21.535	90.000 ns
best_match_wv16_2	63287	2.413	0.100 ns
best_match_mux_wv16_3	77134	3.398	0.100 ns
best_match_behavioral_wv16_137	231102	3.504	0.100 ns
best_match_wv24_1	79273	2.652	0.100 ns
best_match_mux_wv24_2	89081	3.590	0.100 ns
<pre>best_match_behavioral_wv24_297</pre>	563769	6.667	0.100 ns

(a) Compare the amount of time needed for your module compared to the behavioral one. The answer to this question requires some manipulation of the values in the Delay Actual column. Indicate which results are expected, and which are not expected, and explain why.

The manipulation alluded to in the question is the multiplying of the delay by the number of cycles needed to compute the result (the position and error of the best match). The behavioral module is combinational, and so only one "cycle" is needed. (It's not really a cycle because the module isn't clocked.) The **best_match** module, in contrast, requires wv-wk cycles and so the delay must be multiplied by that number of cycles, 24 - 10 = 14 for the 24-bit module and 16 - 10 = 6 for the 16-bit module, in order to compute the time needed to find the best match.

Since we are comparing time we should look at the results for a delay target of 0.1 ns because it is in those runs that the synthesis program is optimizing delay. For the 24-bit module the behavioral module requires 6.667 ns to compute the best match. For wv=24 and wk=10 the best_match module in this solution requires at least 24 - 10 = 14 cycles, for a total time of $14 \times 2.652 \text{ ns} = 37.128 \text{ ns}$. So the behavioral module will compute the error and position in much less time.

Some students submitted solutions that used fewer than wv-wk cycles when a perfect match (err==0) was found before bit wv-wk was reached. A student eager to showcase this clever shortcut could answer this question by describing a favorable situation: "For situations in which a perfect match occurs half the time and is uniformly distributed,

The question also asks for a discussion of whether the synthesis delay results were expected. That means we need to make some kind of a delay estimate for each module and compare it to the delays provided by the synthesis program. A starting point for the delay comparison is to recognize a key difference between the two modules: the behavioral module computes the error for each of 24 - 10 = 14 positions (for the 24-bit module) in one cycle while the **best_match** module computes just one position per cycle. This factor of 14 (or v - k) difference would seem to put the behavioral module at a disadvantage. An important question to answer is whether the behavioral module's delay should be 14 times larger, $\lceil \lg 14 \rceil$ times larger, or something else. In the module generated by the synthesis program the behavioral delay is $6.667/2.652 \approx 2.5$ times larger.

The question did not explicitly ask us to compute the delay (say using the simple model), so that gives us some latitude for approximation. Full credit would have been given for all of the key points made so far in this solution. But having gotten this far, how can we not proceed further into the delay analysis? (Warning: EE 4755 Fall 2019 students are

expected to read the entire solution. Exam questions will be based on homework assignments and the posted solutions, even the excessively wordy ones.)

First, consider the **b** loop in the behavioral module. It is doing the same thing as the assignment to **e_vec** and the hardware in **pop** module are doing in **best_match**. Let's assume that both will be synthesized to the same hardware after optimization (though in the case of the behavioral module there will be **wv-wk** copies of the hardware).

An important thing to remember is that the p loop and the b loop describe how synthesized hardware will be interconnected. They **do not execute** and don't even exist in the synthesized hardware. (The Verilog simulator does execute the loops as procedural code, but in this part we're considering synthesis.) The expression $\mathbf{k}[\mathbf{b}] !== \mathbf{val}[\mathbf{p}+\mathbf{b}]$ is synthesized into (v - k)k pieces of hardware, one for each possible value of $\mathbf{p}((v - k))$ possible values) and $\mathbf{b}(k)$ possible values). Since the values of \mathbf{k} and \mathbf{val} are available the beginning of a clock cycle all (v - k)k comparisons are done simultaneously. The b loop describes a series of adders, computing the same sum as the **pop** module though describing the sum as a linear sequence of additions. If the synthesis program does its job well, meaning that it can re-associate the linear sequence of additions into a reduction tree, the delay for this will be $2 \lg k$ BFAs. Because of the way the BFAs are connected (possible final exam question?) we'll set the adder delay to 4 per BFA, for a total of $8 \lg k u_t$. The input to each b loop is the same \mathbf{val} and \mathbf{k} , which are available at the start of a clock cycle. So taking into account the XOR delay each sum will be available at $[2 + 8 \lg k] u_t$.

So far it looks like the time for the behavioral model to compute v - k values of e is the same as the time needed by best_match to compute one. The difference in timing between the two is due to the code starting at if (e < best_err) begin. The problem is best_err. The value at iteration p depends on iteration p-1 for p>0. Variable best_err is a live-in and live-out for an iteration. It's critical path passes through a comparison, e < best_err, and a mux (selecting the old or new best_err). If the comparison has delay $2 \lg k$ and the mux 2, the delay for v - kiterations will be $[2 + 8 \lg k + (2(\lg k) + 2)(v - k)] u_t$. The delay for best_match is roughly the of one iteration, $[2 + 8 \lg k + (2(\lg k) + 2)] u_t$.

When v - k is large the behavioral module would take (v - k) times longer based on this analysis. For for v - k = 24 - 10 = 14 and $\lg k = 4$ the delays are much closer. For the behavioral delay $2 + 8 \times 4 + (2 \times 8 + 2)(14) = 316 u_t$ and for best_match delay $2 + 8 \times 4 + (2 \times 8 + 2) = 82 u_t$, the modules have less than factor of 4 difference in delay. The synthesis program gives a difference of 2.5. Perhaps the synthesis program used a reduction tree for the if (e < best_err) code. In that case the critical path would be through $\lceil \lg(v - k) \rceil = \lceil \lg 14 \rceil = 4$ layers, in which case delay would be $2 + 8 \times 4 + (2 \times 8 + 2)(4) = 136 u_t$, which works out to 136/82 = 1.66 times longer than best_match. The difference in delays obtained from the synthesis program, 2.5, is somewhere between these two possibilities.

(b) Compare the area of your design to the behavioral one. Indicate which results are expected, and which are not expected, and explain why.

For the area comparison the 90 ns delay target runs should be used. For wv=24 and wk=10 the p loop iterates 14 times and so we would expect the behavioral code to have $14 \times$ as much addition (including the pop module) and comparison hardware. The best_match module though needs a register for sh_val, something which the behavioral module does not need. Assume that the pop module and the expression totaling e use 2k BFAs each. (Approximated using $\sum_{i=1}^{\lg k} ik/2^i = 2(k-1) - \lg k$.) At a cost of $9 u_c$ per BFA, the cost of just the adders would be $18k u_c$. For best_match there would be only one set of such adders, but for the behavioral module there would be v-k such adders. For v = 24 and k = 10 the costs would be $180 u_c$ versus $2520 u_c$ for the behavioral module. Using $7 u_c$ per bit for sh_val, pos, and err, best_match would also require $7(v + \lg v + \lg(k+1)) = 7(24 + 5 + 4) = 231 u_c$ that the behavioral module lacks. The total so far is $411 u_c$ versus $2520 u_c$, a factor of 6 difference. The actual difference is closer to a factor of 3 when optimizing for area.

LSU EE 4755

Homework 5 solution Due: 20 November 2019

Problem 1: Solve 2018 Final Exam Problem 3, in which the inferred hardware for a misc module is to be found (a) and the state of the event queue over time simulating misc (b) is to be found. See the final exam solution at https://www.ece.lsu.edu/koppel/v/2018/fe_sol.pdf.

Problem 2 on next page.

Problem 2: Appearing below is a solution to Homework 4 Problem 1. Show the hardware that will be inferred for this module after some optimization. Show the pop module as a box.

- Clearly show all input and output ports.
- Please don't get parameters and ports confused.

Solution appears below. The solution uses enable signals on the registers, but it would also be correct to use an extra mux instead. Because optimization is applied the wv-wk term is shown as a constant, not as a subtraction unit. The >>=1 is shown as a bit renumbering instead of has a shift unit.

```
module best match
  #( int wv = 32, int wk = 10, int wvb = $clog2(wv),
                                                                       int wkb = $clog2(wk+1) )
   ( output logic [wvb:1] pos, output logic [wkb:1] err, output logic ready,
    input uwire [wv-1:0] val, input uwire [wk-1:0] k, input uwire start,
                                                                       input uwire start, clk );
   logic [wvb-1:0] curr_pos;
   logic [wv-1:0] sh_val;
   uwire [wkb-1:0] e;
   pop #(wk,wkb) p( e, k ^ sh_val[wk-1:0] );
                                                                                                       best match
                                              start
   always_ff @( posedge clk )
                                                                                                         wv,wk,wvb,wkb
                                                                                               ready
                                                                                         en
                                                                 w-wk
                                                                                                                 ready
     if ( start == 1 ) begin
                                                                                               curr
         ready = 0;
         curr_pos = 0;
                                                                                               sod<sup>-</sup>
         sh_val = val;
                                                                                         en
         err = ~0;
                                                                                                                    pos
                                                                                              wvb
                                                                                                                    wvb
                                              clk
     end else if ( !ready ) begin
                                                           start
                                                                                        en
                                              val
         if ( e < err ) begin
                                                                                               Š
            err = e;
                                               ŵv
                                                                1'b0
                                                                                               <a
           pos = curr_pos;
                                                                                0
                                                                         lsb
         end
                                                                      wv-1:1
                                                     sh val
         ready = curr_pos == wv-wk;
                                                           start
         curr_pos++;
         sh_val >>= 1;
                                                                                       <
                                                   wk-1:0
      end
                                                                                  start
                                                                     р
                                                                   pop
                                                                                                             en
endmodule
                                                                                                                     err
                                                                             е
                                                                                                                     wkb
                                               k
                                                                              -0
                                              wk
```


// /// LSU EE 4755 Fall 2019 Homework 6 -- SOLUTION //

/// Assignment https://www.ece.lsu.edu/koppel/v/2019/hw06.pdf

`default_nettype none

```
/// Problem1
11
      Complete add_accum so that it accumulates a sum.
///
//
//
       [\ensuremath{\, {\rm 	extsf{v}}}] Put your solution in add_accum. No other modules should
11
           be modified. (Except the testbench, to help debug.)
11
//
       [\boldsymbol{\,\prime\,}] add_accum must use an add_pipe module to compute the sum.
//
11
       [...] Make sure that the testbench does not report errors.
11
       [.] Module must be synthesizable. Use command: genus -files syn.tcl
11
//
       [\checkmark] As always, avoid costly, slow, and confusing code.
       [<] As always, don't assume parameters will be at their default values.</pre>
11
module add_accum
  #( int w = 21, n_stages = 3 )
   ( output logic [w-1:0] sum,
    output logic sum_valid,
    input uwire [w-1:0] ai,
    input uwire ai_valid, reset, clk );
   /// SOLUTION
   // Register to keep track of which stage of add pipeline is occupied.
   11
  logic [n_stages:0] st_occ;
   11
   // If st_occ[i] == 1 then stage i of pipelined adder is occupied.
   // If none of the adder stages is occupied the value in sum must be valid.
   11
```

```
assign sum_valid = !st_occ;
```

// If true, there is a useful result at the adder output. //

uwire aout_valid = st_occ[n_stages-1];

```
// Connections to adder.
//
uwire [w-1:0] aout;
uwire [w-1:0] a0 = ai_valid ? ai : sum;
uwire [w-1:0] a1 = aout_valid ? aout : sum;
```

add_pipe #(w,n_stages) add_p0(aout, a0, a1, clk);

```
// If true, the value in sum is needed.
//
logic sum_occupied;
```

```
// Number of values ready to be added together.
//
uwire [1:0] n_values = ai_valid + sum_occupied + aout_valid;
//
// If n_values == 0: Nothing to do.
// If n_values == 1: Put or keep the value in sum.
// If n_values == 2: Put the two values into the adder.
// If n_values == 3: Put ai and aout into the adder and leave sum unchanged.
```

// uwire start_an_addition = n_values >= 2; // If true, write sum with either ai or aout. 11 uwire write_sum = !sum_occupied && n_values == 1; always_ff @(posedge clk) if (reset) begin sum <= 0; sum_occupied <= 0;</pre> st_occ <= 0;</pre> // Set occupied bit of every stage to 0. end else begin if (write_sum) sum <= aout_valid ? aout : ai;</pre> // sum will be occupied if there are an odd number (1 or 3) values \ldots 11 sum_occupied <= n_values[0];</pre> //

// .. because if there were 2 values they both would go into the adder.

Area

Delay Delay

```
// Advance occupied bit by one stage.
//
st_occ <= { st_occ[n_stages-1:0], start_an_addition };</pre>
```

end

endmodule

```
`ifdef xxx
<u>Synthesizing</u> at effort level "high"
```

<u>Module</u>	Name	

		<u>Actual</u>	Target
add_pipe_w24_n_stages1	<mark>29</mark> 928	10.174	90.000 ns
add_pipe_w24_n_stages2	47043	5.428	90.000 ns
add_pipe_w24_n_stages3	64159	3.701	90.000 ns
add_pipe_w24_n_stages4	<mark>81</mark> 275	2.837	90.000 ns
add_pipe_w24_n_stages6	115 506	1.973	90.000 ns
add_accum_w24_n_stages1	87556	11.449	90.000 ns
add_accum_w24_n_stages2	105305	6.349	90.000 ns
add_accum_w24_n_stages3	123530	4.560	90.000 ns
add_accum_w24_n_stages4	141598	3.696	90.000 ns
add_accum_w24_n_stages6	177545	3.061	90.000 ns
add_pipe_w24_n_stages1	84351	1.114	0.100 ns
add_pipe_w24_n_stages2	83959	1.249	0.100 ns
add_pipe_w24_n_stages3	103383	1.105	0.100 ns
add_pipe_w24_n_stages4	117 358	1.001	0.100 ns
add_pipe_w24_n_stages6	150854	0.896	0.100 ns
add accum w24 p stages1	150738	2 023	0 100 pc
add_accum_w24_n_stages1	140544	2.023	0.100 hs
add_accull_w24_II_stages2	149544	1./5/	0.100 ms
add_accum_w24_n_stages3	183994	1.514	0.100 ns
add_accum_w24_n_stages4	191611	1.444	0.100 ns
add_accum_w24_n_stages6	224175	1.332	0.100 ns
<u>Normal</u> exit.			

`endif

module add_pipe

```
#( int w = 21, n_stages = 3 )
  ( output uwire [w-1:0] sum,
    input uwire [w-1:0] a, b,
    input uwire clk );
```

localparam int bits_per_stage = (w + n_stages - 1) / n_stages; localparam int wr = n_stages * bits_per_stage; // w rounded.

logic [wr-1:0] pl_a[n_stages+1], pl_b[n_stages+1], pl_sum[n_stages+1]; logic pl_carry[n_stages+1];
```
always_ff @( posedge clk ) begin

pl_a[0] = a;

pl_b[0] = b;

pl_carry[0] = 0;

for ( int s=0; s<n_stages; s++ ) begin

    automatic logic [bits_per_stage:0] sumi =

    pl_a[s][bits_per_stage-1:0] +

    pl_b[s][bits_per_stage-1:0] + pl_carry[s];

    pl_carry[s+1] <= sumi[bits_per_stage];

    pl_sum[s+1] <=

        { sumi[bits_per_stage-1:0], pl_sum[s] } >> bits_per_stage;

    pl_a[s+1] <= pl_a[s] >> bits_per_stage;

    pl_b[s+1] <= pl_b[s] >> bits_per_stage;

    }
```

end

```
end
```

assign sum = pl_sum[n_stages][w-1:0];

endmodule

// cadence translate_off

program reactivate

```
(output uwire clk_reactive, output int cycle_reactive,
    input uwire clk, input var int cycle);
    assign clk_reactive = clk;
    assign cycle_reactive = cycle;
endprogram
```

module testbench;

localparam int n_stages[] = { 1, 2, 3, 5, 6 };

```
localparam int nw = 5; // Cadence, please fix this.
initial if ( nw != n_stages.size() )
<u>$fatal</u>(1,"Constant nw should be %Od.\n",n_stages.size() );
```

```
int t_errs; // Total number of errors.
initial t_errs = 0;
final <u>$write</u>("Total number of errors: %Od\n",t_errs);
```

```
uwire d[nw:-1]; // Start / Done signals.
assign d[-1] = 1; // Initialize first at true.
// Instantiate a testbench at each size.
```

```
//
for ( genvar i=0; i<nw; i++ )
    testbench_n #(n_stages[i]) t2( .done(d[i]), .tstart(d[i-1]) );</pre>
```

```
endmodule
```

```
module testbench_n
  #( int n_stages = 3 )
  ( output logic done, input uwire tstart );
  localparam int n_tests = 10000;
  localparam int w = 30;
  localparam int a_in_max = 42;
  localparam int cyc_max = 1 << 30;
  localparam int lat_limit_empty = n_stages + 2;
</pre>
```

```
localparam int lat_min_empty = n_stages;
localparam int lat_limit_full = 2 + (1+<u>$clog2</u>(n_stages)) * ( n_stages + 1 );
bit clk;
int cycle, cycle_limit;
logic clk_reactive;
int cycle_reactive;
reactivate ra(clk_reactive,cycle_reactive,clk,cycle);
string event_trace;
initial begin
  clk = 0;
  cycle = 0;
  done = 0;
  cycle_limit = cyc_max;
  wait( tstart );
  fork
     while ( !done ) #1 cycle += clk++;
     wait( cycle >= cycle_limit )
        $write("Exit from clock loop at cycle %0d, limit %0d. %s\n %s\n",
               cycle, cycle_limit, "** CYCLE LIMIT EXCEEDED **",
               event_trace);
   join_any;
   done = 1;
end
uwire [w-1:0] sum;
uwire sum_valid;
logic [w-1:0] a;
logic a_valid, reset;
add accum #(w,n_stages) fpa(sum, sum_valid, a, a_valid, reset, clk);
int rsum;
bit tests_start;
int series_idx, value_idx, series_n_vals;
int n_errs, n_underdue_errs, n_overdue_errs, n_tests_done;
int sum_due_cyc_earliest, sum_due_cyc, n_correct;
int last_a_cyc;
int latency_sum, latency_sum_n;
bit error_val_issued, error_late_issued;
initial wait ( done ) begin
   automatic int not_done = n_tests - series_idx;
  $write("Done with %0d-stage tests, %0d series.\n Correct, %0d. Errors: %0d not done, %0d val, %0d/%0d early/late.\n",
          n_stages, series_idx,
          n_correct, not_done, n_errs, n_underdue_errs, n_overdue_errs );
   $write("For %0d stages average latency %.2f cycles.\n",
          n_stages,
          real'(latency_sum) / ( latency_sum_n ? latency_sum_n : 1 ) );
   testbench.t errs += n_errs + n_underdue errs + n_overdue errs + not_done;
end
initial begin
  wait( tests_start );
  while ( !done ) @( posedge clk_reactive ) begin
      if ( sum_valid ) begin
         automatic bit pending = sum_due_cyc < cyc_max;</pre>
         if ( pending ) begin
            n_tests_done++;
            sum_due_cyc = cyc_max;
            if ( sum === rsum ) n_correct++;
            latency_sum += cycle - last_a_cyc;
            latency_sum_n++;
            if ( cycle < sum_due_cyc_earliest ) begin</pre>
```

tests_start = 1; reset = 0; @(negedge clk);

```
n_underdue_errs++;
               if ( n_underdue_errs < 5 ) begin</pre>
                   <u>$write</u>
                     ("At cyc %Od, value ready too soon, %Od, cyc. (Min cyc %Od.)\n",
                      cycle, last_a_cyc - cycle, lat_limit_empty
                      );
                   if ( event_trace != "" ) <u>$write</u>(" %s\n",event_trace);
               end
            end
         end
         if ( !error_val_issued && sum !== rsum ) begin
            error_val_issued = 1;
            n_errs++;
            if ( n_errs < 5 ) begin</pre>
               $write("At cyc %0d, wrong sum, %0d != %g (correct)\n",
                       cycle, sum, rsum);
               if ( event_trace != "" ) <u>$write(" %s\n",event_trace</u>);
            end
         end
      end else if ( sum_due_cyc <= cycle ) begin</pre>
         if ( !error_late_issued ) begin
            error_late_issued = 1;
            n_overdue_errs++;
            sum_due_cyc = cyc_max;
            if ( n_overdue_errs < 5 ) begin</pre>
                $write("At cycle %0d, sum overdue.\n",cycle);
               if ( event_trace != "" ) <u>$write</u>(" %s\n",event_trace);
            end
         end
      end
   end
end
initial begin
   automatic int seed = 4755;
   automatic int series_sparsity = 0;
   rsum = 0;
  n errs = 0;
   latency_sum_n = 0;
  latency_sum = 0;
   error_val_issued = 0;
  error_late_issued = 1;
  series_idx = 0;
  value_idx = 0;
  series_n_vals = 0;
  n_overdue_errs = 0;
  n_underdue_errs = 0;
   sum_due_cyc = cyc_max;
   sum_due_cyc_earliest = 0;
  n_tests_done = 0;
  n_correct = 0;
   event_trace = "";
   wait( tstart );
   $write("Starting tests for %Od-stage pipeline.\n",n_stages);
   @( negedge clk );
  reset = 1;
   event_trace = <u>$sformatf("R(%0d)",cycle</u>);
   a_valid = 0;
  a = 0;
   @( negedge clk );
   cycle_limit = cycle + n_stages * 2;
```

```
wait( sum_valid );
   while ( series_idx < n_tests ) begin</pre>
      @( negedge clk );
      a = <u>$dist_uniform( seed, 1, a_in_max );</u>
      if ( value_idx >= series_n_vals ) begin
         a_valid = 0;
         if ( sum_valid ) begin
            series_idx++;
            value_idx = 0;
            event_trace = <u>$sformatf("R(%0d)", cycle);</u>
            reset = 1;
            a_valid = 0;
            rsum = 0;
            series_n_vals = <u>$dist_uniform(</u> seed, 1, 10 );
            series_sparsity = series_idx % 6;
            sum_due_cyc = cycle + 1;
            sum_due_cyc_earliest = cycle;
            error_val_issued = 0;
            error_late_issued = 0;
            cycle_limit = cycle + 1;
         end
      end else begin
         reset = 0;
         a_valid = series_sparsity == 0
          || <u>$dist uniform(</u> seed, 0, series_sparsity ) == 0;
         cycle_limit = cycle + lat_limit_full;
      end
      if ( a_valid ) begin
        value_idx++;
         event_trace = {event_trace, $sformatf("+%Od(%Od)",a,cycle)};
         error_val_issued = 0;
         error_late_issued = 0;
         rsum += a;
         last_a_cyc = cycle;
         sum_due_cyc = cycle +
           ( sum_valid ? lat_limit_empty : lat_limit_full );
         sum_due_cyc_earliest =
           cycle + ( value_idx > 1 ? lat_min_empty : 0 );
      end
   end
   done = 1;
end
```

endmodule

// cadence translate_on

20 Fall 2018 Solutions

endmodule

```
11
/// LSU EE 4755 Fall 2018 Homework 1 -- SOLUTION
11
/// Assignment https://www.ece.lsu.edu/koppel/v/2018/hw01.pdf
`default nettype none
/// Problem 1
11
/// Modify sort2 so that it implements a 2-input sorting network ..
/// .. using explicity structural code only.
11
11
      [<] Make sure that the testbench does not report errors.</pre>
      [.] Use structural code only: including mux2 and compare le.
11
      [ / ] Pay attention to bit widths.
11
11
      [...] Module must be synthesizable.
module sort2
 #(int w = 8)
   ( output uwire [w-1:0] x0, x1,
    input uwire [w-1:0] a0, a1 );
  /// SOLUTION
  11
   // The only common problem was forgetting to specify the width.
  uwire c;
  compare le #(w) comp(c, a0, a1);
  mux2 #(w) m0(x1,c,a0,a1);
  mux2 #(w) m1(x0,c,a1,a0);
endmodule
module mux2
 #(int w = 4)
   ( output uwire [w-1:0] x,
    input uwire select,
    input uwire [w-1:0] a0, a1 );
   assign x = select ? a1 : a0;
endmodule
module compare le
 #(int w = 2)
   ( output uwire c,
     input uwire [w-1:0] a, b );
   assign c = a \ll b;
endmodule
module sort2 is
 #(int w = 8)
   ( output uwire [w-1:0] x0, x1,
     input uwire [w-1:0] a0, a1 );
   assign {x0, x1} = a0 <= a1 ? { a0, a1 } : { a1, a0 };</pre>
```

/// Problem 2 11 /// Modify sort4 so that it implements a 4-input sorting network ... /// .. using explicitly structural code only. // [~] Make sure that the testbench does not report errors. 11 11 [~] Use structural code only: including sort2 and sort3 modules. 11 [/] Pay attention to bit widths. [<] Module must be synthesizable.</pre> 11 $[\cdot]$ The critical path length should be 4 or fewer sort2 modules. 11 module sort4 #(int w = 8)(output uwire [w-1:0] x0, x1, x2, x3, input uwire [w-1:0] a0, a1, a2, a3); /// SOLUTION uwire [w-1:0] s10, s11, s12, s13, s20; // Connect sort2 modules into a tree, so that the longest path // is through 2 sort2 modules. 11 sort2 #(w) s2(s10, s11, a0, a1); sort2 #(w) s3(s12, s13, a2, a3); sort2 #(w) s4(s20, x3, s11, s13); // Note that s20 will be available later than s10 and s12 because // the path from a0 - a3 to s20 go through two sort2 modules, // whereas the paths from a0 - a3 to s10 and s12 only pass through // one sort2 module. Since s20 will be available later connect it // to sort3 port a2, which is closer to the outputs. 11 sort3 #(w) s1(x0, x1, x2, s10, s12, s20); 11 // Note that module would be slower if s12 and s20 connections above // were reversed: // sort3 #(w) s1(x0, x1, x2, s10, s20, s12); endmodule module sort3 #(int w = 8)(output uwire [w-1:0] x0, x1, x2, input uwire [w-1:0] a0, a1, a2); uwire [w-1:0] i10, i11, i21; sort2 #(w) s0_01(i10, i11, a0, a1); sort2 #(w) s1_12(i21, x2, i11, a2);

endmodule

// provides test inputs, and verifies the outputs.

sort2 #(w) s2_01(x0, x1, i10, i21);

```
//
11
    The testbench may be modified to facilitate your solution. For
11
    example, one might modify the testbench so that the first tests it
11
    performs are those which make it easier to determine what the
11
    problem is, for example, test inputs that are all 0's or all 1's.
11
11
    Of course, the removal of tests which your module fails is not a
    method of fixing a broken module. The TA-bot will test your
//
11
    code using a fresh copy of the testbench, not the one below.
// cadence translate_off
module sortx
  #( int max size = 5,
     int modnum = 0,
     int w = 8,
     int max muts = 3)
   ( output uwire [w-1:0] xlong[max_muts][max_size],
     input uwire [w-1:0] a[max size] );
   uwire [w-1:0] x[max_size];
   assign xlong[modnum] = x;
   if ( modnum == 0 ) begin:A
      localparam int s_size = 2;
      localparam string name = "sort2";
      sort2 #(w) s(x[0],x[1],a[0],a[1]);
   end else if ( modnum == 1 ) begin:A
      localparam int s size = 2;
      localparam string name = "sort2 is";
      sort2 is #(w) s(x[0],x[1],a[0],a[1]);
   end else if ( modnum == 2 ) begin:A
      localparam int s size = 3;
      localparam string name = "sort3";
      sort3 #(w) s(x[0],x[1],x[2],a[0],a[1],a[2]);
   end else begin:A
      localparam int s_size = 4;
      localparam string name = "sort4";
      sort4 #(w) s(x[0],x[1],x[2],x[3],a[0],a[1],a[2],a[3]);
   end
endmodule
module testbench;
   localparam int w = 8;
   localparam int n_tests = 100;
   localparam int max_size = 4;
   localparam int max_muts = 4;
   logic [w-1:0] a[max_size];
   uwire [w-1:0] x[max_muts][max_size];
   typedef struct { int idx; string name; int s_size; } Info;
   <u>Info</u> pi[$];
```

```
for ( genvar i=0; i<4; i++ ) begin</pre>
   sortx #(max size,i,w,max muts) s(x,a);
   initial pi.push back( '{ i, s.A.name, s.A.s size} );
end
initial begin
   automatic int g elt err count = 0;
   automatic int g_sort_err_count = 0;
   swrite("Starting testbench.");
   // Initialize the input to a recognizable pattern, which should
   // be overwritten but if not, we can tell. If we print the value in
   // hex.
   for ( int e = 0; e < max_size; e++ ) a[e] = 'haaaaaaaaa;</pre>
   foreach ( pi[idx] ) begin
      automatic Info p = pi[idx];
      automatic string mut = p.name;
      automatic int s size = p.s size;
      automatic logic [w-1:0] shadow[] = new[s size];
      for ( int i = 0; i < n tests; i++ ) begin</pre>
         automatic int this elt err count = 0;
         // To make sure that the comparison is correct restrict the
         // key to a subset of bits.
         automatic int n_bits = {<u>$random</u>} % w + 1;
         automatic int mask = ( 1 << n bits ) - 1;</pre>
         for ( int i=0; i<w; i++ ) begin</pre>
            automatic int b = {<u>$random</u>} % w;
            {mask[b],mask[i]} = {mask[i],mask[b]};
         end
         for ( int e = 0; e < s_size; e++ )</pre>
           begin a[e] = {<u>$random</u>} & mask; shadow[e] = a[e]; end
         #1;
         shadow.sort();
         for ( int e = 0; e < s size; e++ ) begin
            automatic logic [w-1:0] elt = x[p.idx][e];
            if ( shadow[e] === elt ) continue;
            this elt err count++;
            g_elt_err_count++;
            if ( g elt err count > 5 ) continue;
            $write
               ("Mod %s, sort %2d index %2d, wrong elt %d != %d (correct)\n",
               mut,i, e, elt, shadow[e]);
         end
         if ( this_elt_err_count ) g_sort_err_count++;
      end
      <u>$write("Tests for %s done, errors in %d of %d sorts.\n",</u>
```

 $\quad \text{end} \quad$

endmodule

// cadence translate_on

LSU EE 4755

Homework 2 solution Due: 12 September 2018

Problem 1: The Verilog code below is the sort3 module from Homework 1. Draw a diagram of the hardware as described by sort3, showing the sort2 modules as boxes. Be sure to label the input and output ports with the same symbols used in the module.

```
module sort3
#( int w = 8 )
```

```
( output uwire [w-1:0] x0, x1, x2,
    input uwire [w-1:0] a0, a1, a2 );
uwire [w-1:0] i10, i11, i21;
sort2 #(w) s0_01( i10, i11, a0, a1 );
sort2 #(w) s1_12( i21, x2, i11, a2 );
sort2 #(w) s2_01( x0, x1, i10, i21 );
```

endmodule

Solution appears below.



Problem 2: It is possible to build an *n*-element sorting network using $\frac{n}{2} \lg^2 n$ two-element sorting networks in such a way that the *n*-element sorting network has a critical path of $\lg^2 n$. (Note: $\lg n \equiv \log_2 n$.) But this assignment is concerned with *n*-element sorting networks using n(n-1)/2 two-element sorting networks, which we will call *n*-element bad sorting networks or bad sorters for short.

An *n*-element bad sorter has inputs $a_0, a_1, \ldots, a_{n-1}$ and outputs $x_0, x_1, \ldots, x_{n-1}$. The largest value is routed to x_{n-1} .

A 2-element bad sorter is a single **sort2** module. An *n*-element bad sorter, n > 2, can be constructed using an (n-1)-element bad sorter and n-1 **sort2** modules as follows. The n-1 **sort2** modules are connected to the *n* inputs and to each other in such a way that the largest value is routed to a specific output of one of the **sort2** modules. That specific **sort2** output is connected to output x_{n-1} of the *n*-element sorter. The other values connect to the (n-1)-element bad sorter, and the (n-1)-element bad sorter outputs connect to outputs $x_0, x_1, \ldots, x_{n-2}$ of the *n*-element bad sorter that we are constructing. Note that this generalizes the solution to Homework 1 Problem 2.

The description above is recursive. At level *i* (the same as *n* above) another i - 1 sort2 modules are used. For a 4-element sorter we need (4 - 1) + (3 - 1) + 1 = 6 sort2 modules. The

cost of an *n*-element bad sorter is found by solving the summation $\sum_{i=2}^{n} i - 1$, which is n(n-1)/2. That's $O(n^2)$, which is how the bad sorter got its name.

It gets worse. The critical path through the bad sorter can range from bad to awful. That depends on two things: How the **sort2** modules are used to find the largest value, and how the **sort2** modules connect to the (n-1)-element bad sorter.

(a) Show the worst way that sort2 modules can be connected to find the largest value. *Hint: the critical path should be* n-1 sort2 *modules.* Provide a sketch for the general case, and an example for n = 4.

Call the sort2 modules s_0 to s_{n-2} . Connecting output x1 of s_i to input a0 of s_{i+1} for $0 \le i < n-1$ is the worst way to connect n-1 modules. See the illustration below. The critical path starts at a0 or a1 and ends at either output of sorter s_{n-2} .



(b) Show the worst way that the sort2 modules, as connected above, can connect to the (n-1)-element sorter. Provide a sketch.

Notice that the critical path through the sort2 modules starts at a[0] and ends at j[n-2]. So when connecting j[n-2] to the smaller sort module the worst ports that it can be connected to are a[0] and a[1]. That's shown below. Note that n inside the smaller sort_awful is equal to n-1 in the larger one.



(c) Determine the critical path for an *n*-element bad sorter constructed in the way described in the last two parts. *Hint: The math part should be familiar.*

In an *n*-input awful bad sorter the path from a0 to j[n-2] is of length n-1. Signal j[n-2] connects to a0 of an n-1 element bad sorter where it goes through n-2 sort2 modules. The total length of the path is $\sum_{i=n}^{2} i-1 = n(n-2)/2$ sort2 modules.

(d) Show a much better way of connecting the sort2 modules to find the largest value. It should be easy to show that the critical path is the lowest that is possible. Provide a sketch for n = 8.

Connect the sort2 modules in a tree, the solution appears below for n=8, and showing the recursive connection.



The problem with the approach to building the bad sorters described in this assignment is that each level in the recursion reduces the size by 1 (that is, from n to n - 1), and so the critical path must be at least O(n). As some students may have realized, a better approach would be to use recursion in which the n inputs were split between two $\frac{n}{2}$ -element networks and then somehow combined. But how? The key insight, described by K. E. Batcher in a landmark 1968 paper, is not to try to recursively describe a sorting network, but to instead recursively describe a network that merges two already sorted sequences. The input to a 2-element merge network would be two 1-element sorted sequences. (Of course, every 1-element sequence is sorted.) Pairs of 2-element merge networks feed a 4-element merge network, and so on. This will be further described later in the semester.

```
11
/// LSU EE 4755 Fall 2018 Homework 3 -- SOLUTION
11
 /// Assignment https://www.ece.lsu.edu/koppel/v/2018/hw03.pdf
`default nettype none
/// All Problems
11
/// Modify sort2 so that it implements a 2-input sorting network ...
/// .. using explicit and implicit structural code only.
11
11
       [✓] Easy:
                  Modify to compare keys, not data.
                  Modify to sort pairs of signed integer keys.
11
       [✓] Easy:
11
       [<] Medium: Modify to sort pairs of floating-point keys.</pre>
       [~] Medium: Modify to sort one signed int and one FP key.
11
11
       [✓] Hard:
                  Keep cost and critical path low.
11
11
       [ Juse implicit and explicit structural code only.
       [\checkmark] Use mux2 to swap the values.
11
11
       [v] Add ChipWare Verilog modules to includes at the end of this file.
11
       [v] Module must be synthesizable. Use command: genus -files syn.tcl
11
       [<] Make sure that the testbench does not report errors.</pre>
11
11
       [✓] Use SimVision for debugging.
11
11
           DMK: Yes, I used SimVision.
       [<] Modify testbench to facilitate solution ...</pre>
//
           .. but code must pass original testbench.
//
module sort2
  #(int w = 30,
     int k = 16,
     int exp = 5,
     int sig = k - exp - 1)
   ( output uwire [w-1:0] x0, x1,
     input uwire [w-1:0] a0, a1 );
   /// Encoding of a0 and a1
   11
   // Bits
                 Contents
   // -----
                  // w-1 : k+1
                 Data
   // k
                 Key type: 0, integer; 1, floating point.
                 Key, a signed integer; if Key type = 0.
   // k-1 : 0
                  Sign bit, if key type = 1.
   // k-1
   // k-2 : sig
                  Exponent, if key type = 1.
                 Significand, if key type = 1.
   // sig-1 : 0
   /// SOLUTION OVERVIEW
   11
   11
       Compare integer/integer keys using <= operator.</pre>
   11
       Compare fp/fp and fp/integer keys using ChipWare comparison operator.
      For fp/integer keys that are reported equal use the inexact
   11
   // status bit.
   // Extract key portion of inputs and assign to a logic signed type.
   11
   uwire signed [k-1:0] k0 = a0[k-1:0];
   uwire signed [k-1:0] k1 = a1[k-1:0];
   // Integer / Integer Comparison
   11
   uwire ci = k0 \ll k1;
```

```
\leftarrow \rightarrow Fall 2018 \leftarrow \rightarrow Homework 3
```

```
//
// Note that ci is ignored if either input is FP.
11
/// Convert Keys to FP
11
// Floating-point version of keys. Only valid if key is an integer.
11
uwire [k-1:0] kif0, kif1; // Key Integer converted to Float.
uwire [7:0] si0, si1; // Status output of integer-to-FP modules.
localparam logic [2:0] rnd_to_0 = 3'b1;
// Convert using ChipWare integer two floating-point modules.
11
<u>CW_fp_i2flt</u> #( .sig_width(sig), .exp_width(exp), .isize(k), .isign(1) )
  itof0( .z(kif0), .status(si0), .a(k0), .rnd(rnd_to_0) );
<u>CW_fp_i2flt</u> #( .sig_width(sig), .exp_width(exp), .isize(k), .isign(1) )
  itof1( .z(kif1), .status(si1), .a(k1), .rnd(rnd_to_0) );
// Extract the inexact bit.
11
uwire inexact0 = si0[5], inexact1 = si1[5];
11
// If this bit is 1 the converted value is slightly less in
// magnitude than the original integer value. Less because the
// round-towards-zero (rnd_to_0) rounding option was selected.
// Select the FP version of the key.
11
uwire [k-1:0] fk0 = a0[k] ? k0 : kif0;
uwire [k-1:0] fk1 = a1[k] ? k1 : kif1;
11
// Note that k0 is selected if the key in a is already FP,
// otherwise use the output of the conversion module.
11
/// Floating Point Comparison
11
uwire gt, lt, eq, un;
uwire [k-1:0] z0, z1; // Unused
uwire [7:0] s0, s1;
<u>CW_fp_cmp</u> #( .sig_width(sig), .exp_width(exp), .ieee_compliance(0) )
fp_comp(.a(fk0),.b(fk1),.agtb(gt),.altb(lt),.aeqb(eq),
        .zctr(1'b0), .unordered(un), .z0(z0), .z1(z1),
        .status0(s0), .status1(s1));
/// Check whether kif0 <= kif1.
11
11
   Approximate method:
11
uwire cf approx = |t| |eq; // Unused, shown to explain solution.
11
// cf_approx can be wrong when eq is true because of rounding
// errors when converting an integer to FP. Wire inexact0 is 1 when
// there was a rounding error converting k0, etc. If eq is 1 then
// a0 <= a1 iff one of the two cases below is true:</pre>
11
// Case 1:
11
     k0 is negative
       k0 is FP (so no rounding)
11
       or k0 is an integer and no rounding error in the conversion.
11
       -- otherwise kif0 is larger than the value in a0
11
11
// Case 2:
     k0 is positive
11
```

```
\leftarrow \rightarrow Fall 2018
                                                 Homework Sol Code
                   \leftarrow \rightarrow Homework 3
       11
               k1 is FP (so no rounding)
               or k1 is an integer and no rounding error in the conversion.
       11
       11
               -- otherwise kifl is smaller than the value in al.
       // Determine whether a0 \leq al accounting for rounding errors, as
       // described above.
       11
       uwire cf = lt || eq \&\&
                !kif0[k-1] && ( a0[k] || !inexact0 ) // Case 1
              (
                || kif0[k-1] && ( a1[k] || !inexact1 ) // Case 2
                  );
       // If at least one input is FP use FP comparison result, else int result.
       11
       uwire c = a0[k] || a1[k] ? cf : ci;
       mux2 #(w) m0(x0,c,a1,a0);
       mux2 #(w) ml(x1,c,a0,a1);
   endmodule
   module mux2
```

```
#( int w = 4 )
  ( output uwire [w-1:0] x,
     input uwire select,
     input uwire [w-1:0] a0, a1 );
   assign x = select ? a1 : a0;
endmodule
```

```
/// Testbench Code
11
11
   The code below instantiates some of the modules above,
11
   provides test inputs, and verifies the outputs.
11
11
   The testbench may be modified to facilitate your solution. For
11
   example, one might modify the testbench so that the first tests it
   performs are those which make it easier to determine what the
11
11
   problem is, for example, test inputs that are all 0's or all 1's.
11
11
   Of course, the removal of tests which your module fails is not a
11
   method of fixing a broken module. The TA-bot will test your
   code using a fresh copy of the testbench, not the one below.
11
```

// cadence translate_off

module testbench;

```
var bit s[3];
testbench_size #(32,16,6) tl(s[1],s[0]);
testbench_size #(24,14,5) t2(s[2],s[1]);
initial begin
   s[0] = 1;
   wait( s[2] );
    <u>$write("\nAll done.\n");</u>
end
```

endmodule

```
int exp = 6,
  int sig_width = k - exp - 1 )
( output var bit done, input var bit start );
localparam int s_pos = k - 1;
localparam int exp_hi = s_pos - 1;
localparam int exp_lo = s_pos - exp;
localparam int sig_hi = exp_lo - 1;
localparam int bias = ( 1 << exp - 1 ) - 1;</pre>
localparam int exp_i_max = bias + k - 1;
localparam int exp_max = ( 1 << exp ) - 2;</pre>
localparam int exp_range_ini = exp_i_max - bias;
localparam int exp_range_gti = exp_max - exp_i_max - 1;
function real fp_to_val(input logic [k-1:0] a);
   fp_to_val =
     a[exp_hi:0] == 0 ? 0.0 :
       ((1.0 + a[sig_hi:0] / real'(1 << sig_width))
         * 2 ** ( 0.0 + a[exp_hi:exp_lo]-bias )
         * ( a[s_pos] ? -1 : 1 ) );
endfunction
localparam int num tests = 3000000;
localparam int test ff start = num tests / 3;
localparam int test_if_start = test_ff_start * 2;
uwire [w-1:0] x0, x1;
logic [w-1:0] a[2];
sort2 #(w,k,exp,sig_width) s2(x0,x1, a[0], a[1]);
initial begin
   automatic int err_count[string] = '{"ii":0, "ff":0, "if":0 };
   automatic logic [1:0][w-1:0] tests[$];
   /// Add tests below by copying output of testbench.
   // Note: Tests only work at a particular value of exp, k.
   // Put in correct place.
   case (k)
     14: begin
        tests.push back('h2a823); tests.push back('h77b7e);
     end
     16: begin
        tests.push back('hdc641209); tests.push back('ha0935641);
     end
   endcase
   wait( start );
   $write("Starting testbench for w=%0d, k=%0d, exp=%0d sig width=%0d...\n",
          w, k, exp, exp lo);
   for ( int i=0; i<num_tests; i++ ) begin</pre>
      automatic logic [k-1:0] i 1 mask = 1 << {$random} % k;</pre>
      automatic string test_type =
        i < test_ff_start ? "ii" :</pre>
          i < test_if_start ? "ff" : "if";</pre>
      bit fp[2];
      real val[2];
      bit swap;
      logic [w-1:0] shadow x0, shadow x1;
      for ( int j=0; j<2; j++ )</pre>
        fp[j] = test_type == "ff" || test_type == "if" && ( (i+j) & 1 );
      // FP Options: 0, (0,1), int range, > int range, int, int, int, int
      for ( int j=0; j<2; j++ ) begin</pre>
```

```
automatic int fp_sz = fp[j] ? {<u>$random</u>} % 4 : 4;
   a[j][w-1:0] = {\underline{\$random}};
   a[j][k] = fp[j];
   case ( fp_sz )
     0: a[j][exp_hi:0] = 0;
     1: a[j][exp_hi:exp_lo] = 1 + {<u>$random</u>} % bias;
     2: a[j][exp_hi:exp_lo] = bias + {<u>$random</u>} % exp_range_ini;
     3: a[j][exp_hi:exp_lo] = exp_i_max + {<u>$random</u>} % exp_range_gti;
     default:; // For int leave random value.
   endcase
end
// Test cases for floating-point pairs.
if ( a[0][k] && a[1][k] && a[1][exp_hi:0] ) begin
   // Generate fp numbers with matching exponents
   if ( {<u>$random</u>} & 1 ) a[0][exp_hi:exp_lo] = a[1][exp_hi:exp_lo];
   // Generate fp numbers with matching significands.
   if ( {<u>$random</u>} & 1 ) a[0][sig_hi:0] = a[1][sig_hi:0];
end
// Test cases for integer pairs.
if ( !a[0][k] && !a[1][k] ) begin
   case ( {<u>$random</u>} % 6 )
     // Differ by 1
     0: a[1][k-1:0] = a[0][k-1:0] - 1;
     1: a[1][k-1:0] = a[0][k-1:0] + 1;
     // Differ by 2
     2: a[1][k-1:0] = a[0][k-1:0] - 2;
     3: a[1][k-1:0] = a[0][k-1:0] + 2;
     // Sort key in only 1 bit.
     4: begin a[0][k-1:0] &= i_1_mask; a[1][k-1:0] &= i_1_mask; end
     default:;
   endcase
end
// Test cases for int/fp keys.
if ( a[0][k] != a[1][k] ) begin
   automatic int opt = {<u>$random</u>} % 32;
   casex ( opt )
     'h0xxx: if ( a[0][k] ) a[1][k-1:0] = fp_to_val(a[0])+opt[2:0]-4;
     'hlxxx: if ( a[1][k] ) a[0][k-1:0] = fp_to_val(a[1])+opt[2:0]-4;
   endcase
end
// Replace the keys found above with user-defined keys, if any.
if ( tests.size() ) begin
   a[0] = tests.pop_front();
   a[1] = tests.pop front();
end
case ( {a[0][k], a[1][k] } )
  'b00: test_type = "ii";
'b11: test_type = "ff";
  default: test type = "if";
endcase
for ( int j=0; j<2; j++ )</pre>
  val[j] = a[j][k] ? fp_to_val(a[j]) : signed'(a[j][s_pos:0]);
swap = val[0] > val[1];
{ shadow_x0, shadow_x1 } = { a[swap], a[1-swap] };
```

```
\leftarrow \rightarrow Fall 2018
                    \leftarrow \rightarrow Homework 3
                                                   Homework Sol Code
                                                                                                     hw03-sol.v.html
              if ( shadow_x0 !== x0 || shadow_x1 !== x1 ) begin
                 err_count[test_type]++;
                 if ( err_count[test_type] > 5 ) continue;
                 <u>$write</u>
                    ("Test %s %4d, error (x0,x1): (%h,%h) != (%h,%h) correct.\n",
                     test_type, i,
                     x0, x1, shadow_x0, shadow_x1);
                 for ( int j=0; j<\overline{2}; j++ )
                    $write('
                                         a%ld: data %h, key %12.5f = %s %s\n",
                           j, a[j][w-1:k], val[j], a[j][k] ? "FP " : "INT",
                           a[j][k] ?
                           $sformatf("s %b exp %0d-%0d=%0d sig 'h%h",
                                       a[j][s_pos],
                                       a[j][exp_hi:exp_lo], bias,
                                       signed'({1'b0,a[j][exp_hi:exp_lo]}) - bias,
                                       a[j][sig_hi:0])
                            : <u>$sformatf</u>("'h%h",a[j][k-1:0]));
                 <u>$writ</u>e("
                                       To re-run paste: tests.push_back('h%h); tests.push_back('h%h);\n",
                         a[0],a[1]);
              end
```

```
end
```

done = 1;

end

endmodule

// cadence translate_on

`*default_nettype* wire

```
`include "/apps/linux/cadence/GENUS171/share/synth/lib/chipware/sim/verilog/CW/CW_fp_cmp.v"
`include "/apps/linux/cadence/GENUS171/share/synth/lib/chipware/sim/verilog/CW/CW_fp_i2flt.v"
```

LSU EE 4755

Homework 4 Solution

Due: 3 October 2018

Problem 1: Solve 2017 Final Exam Problem 3, in which the cost and delay of two alternative designs are to be compared.

See posted final exam solution on the previous work page at https://www.ece.lsu.edu/koppel/v/prev.html.

11 /// LSU EE 4755 Fall 2018 Homework 5 -- SOLUTION 11 /// Assignment https://www.ece.lsu.edu/koppel/v/2018/hw05.pdf `default nettype none /// Problem 1 11 /// Complete batcher_sort so that it recursively implements a Batcher /// sorter using a merge module. 11 11 [✓] Assume that n is a power of 2. [...] Use implicit and explicit structural code only. 11 [<] Use recursion as described in the handout.</pre> 11 [...] Use behav merge initially and when it's done, batcher merge. 11 11 11 [~] Make sure that the testbench does not report errors. 11 [v] Module must be synthesizable. Use command: genus -files syn.tcl 11 [<] Use SimVision for debugging.</pre> 11 [...] Modify testbench to facilitate solution ... 11 11 .. but code must pass original testbench. 11 11 [~] As always, code should be efficient and clearly written. module batcher sort #(int n = 4, int w = 8)(output uwire [w-1:0] x[n], input uwire [w-1:0] a[n]); /// SOLUTION if (n == 1) begin // Set the terminal case at n==1 ... // .. because sorting is easy when there's just one element! 11 assign x = a;end else begin localparam int nh = n/2;uwire [w-1:0] xlo[nh], xhi[nh]; // Recursively instantiate two sorters, slo and shi, ... // .. slo will sort elements 0 to nh-1, and .. // .. shi will sort elements nh to n-1. 11 batcher sort #(nh,w) slo(xlo, a[0:nh-1]); batcher sort #(nh,w) shi(xhi, a[nh:n-1]); // Use a merge module to combine the two sorted sequences. 11 batcher merge #(nh,w) m(x, xlo, xhi);

end

endmodule

```
module behav_merge
#( int n = 4, int w = 8 )
  ( output logic [w-1:0] x[2*n], input uwire [w-1:0] a[n], b[n] );
logic [$clog2(n+1)-1:0] ia, ib;
  always_comb begin
    ia = 0; ib = 0;
    for ( int i = 0; i < 2*n; i++ )
        x[i] = ib == n || ia < n && a[ia] <= b[ib] ? a[ia++] : b[ib++];
end</pre>
```

endmodule


```
11
/// Modify batcher_merge so that it recursively implements a Batcher
/// odd/even merge module.
11
11
       [~] Recursively implement a Batcher Odd / Even merge module.
11
11
       [\checkmark] Assume that n is a power of 2.
11
       [...] Use sort2 to swap the values.
11
11
       [v] Make sure that the testbench does not report errors.
11
       [...] Module must be synthesizable. Use command: genus -files syn.tcl
17
11
       [~] Use SimVision for debugging.
       [<] Modify testbench to facilitate solution ...</pre>
//
```

```
.. but code must pass original testbench.
```

```
module batcher merge
```

//

```
#( int n = 4, int w = 8 )
  ( output uwire [w-1:0] x[2*n], input uwire [w-1:0] a[n], b[n] );
```

/// SOLUTION

```
// Note: Input a and input b are each sorted.
```

```
// Declare the outputs of the recursively instantiated merge modules.
//
uwire [w-1:0] xlo[n], xhi[n];
if ( n == 1 ) begin
    // No need for recursion when each sorted sequence is one element.
    //
    assign xlo[0] = a[0];
    assign xhi[0] = b[0];
```

end else begin

```
localparam int nh = n/2;
// Put even elements of a into ae ..
// .. odd elements of a into ao ..
// .. and likewise for b.
uwire [w-1:0] ae[nh], ao[nh], be[nh], bo[nh];
for ( genvar i=0; i<nh; i++ )</pre>
```

// and the other to merge sorted sequences ao and be. //

```
batcher_merge #(nh,w) mhi( xhi, ao, be );
```

```
//
// This ensures that one of the two smallest elements is xlo[0] ..
// .. and the other is xhi[0].
```

 end

```
// Use 2-input sorters to complete the merge.
//
for ( genvar i=0; i<n; i++ )
    sort2 #(w) s2( x[2*i], x[2*i+1], xlo[i], xhi[i] );</pre>
```

endmodule

```
// Correctly functioning 2-input sorter.
module sort2
    #( int w = 8 )( output uwire [w-1:0] x0, x1, input uwire [w-1:0] a0, a1 );
    assign {x0, x1} = a0 <= a1 ? { a0, a1 } : { a1, a0 };
endmodule</pre>
```


11 11 The code below instantiates some of the modules above, provides test inputs, and verifies the outputs. 11 // The testbench may be modified to facilitate your solution. For // example, one might modify the testbench so that the first tests it // performs are those which make it easier to determine what the 11 problem is, for example, test inputs that are all 0's or all 1's. 11 11 Of course, the removal of tests which your module fails is not a 11 method of fixing a broken module. The TA-bot will test your 11 code using a fresh copy of the testbench, not the one below. //

// cadence translate_off

```
module Sortx
#( int n = 5,
    int modnum = 0,
    int mut_idx = 0,
    int w = 10,
    int max_muts = 3,
    int max_n = n)
  ( output uwire [w-1:0] xlong[max_muts][max_n],
    input uwire [w-1:0] a[n] );
```

```
localparam string name = "Batcher Merge";
      localparam bit merge = 1;
      batcher_merge #(nlo,w) s(x,alo,ahi);
   end else if ( modnum == 1 ) begin:A
      localparam string name = "Batcher Sort";
      localparam bit merge = 0;
      batcher_sort #(n,w) s(x,a);
   end else if ( modnum == 2 ) begin:A
      localparam string name = "sort3";
      localparam bit merge = 0;
   end else begin:A
      localparam string name = "sort4";
      localparam bit merge = 0;
   end
endmodule
module testbench;
   localparam int w = 8;
   localparam int n tests = 10;
   localparam int max n = 32;
   localparam int max muts = 12;
   logic [w-1:0] a[max n];
   uwire [w-1:0] x[max muts][max n];
   typedef struct { int idx; string name; bit merge; int n; } Info;
   <u>Info</u> pi[$];
   for ( genvar i=0; i<2; i++ ) begin</pre>
      for ( genvar nlg = 1; nlg < \tilde{6}; nlg++ ) begin
         localparam int n = 1 << nlg;</pre>
         localparam int idx = i * 6 + nlg;
         sortx #(n,i,idx,w,max_muts,max_n) s(x,a[0:n-1]);
         initial pi.push_back( '{ idx, s.A.name, s.A.merge, s.n } );
      end
   end
   initial begin
      automatic int g_elt_err_count = 0;
      automatic int g_sort_err_count = 0;
      $write("Starting testbench.\n");
```

// Initialize the input to a recognizable pattern, which should
// be overwritten but if not, we can tell. If we print the value in

```
\leftarrow \rightarrow Fall 2018 \leftarrow \rightarrow Homework 5
```

```
// hex.
for ( int e = 0; e < max n; e++ ) a[e] = 'haaaaaaaaa;
foreach ( pi[idx] ) begin
   automatic Info p = pi[idx];
   automatic string mut = p.name;
   automatic int n = p.n;
   automatic int s size = n;
   automatic int nlo = n/2;
   automatic int nhi = n - nlo;
   automatic logic [w-1:0] shadow[] = new[s_size];
   automatic logic [w-1:0] alo[] = new[nlo];
   automatic logic [w-1:0] ahi[] = new[nhi];
   automatic int this_sort_err_count = 0;
   for ( int i = 0; i < n_tests; i++ ) begin</pre>
      automatic int this_elt_err_count = 0;
      // To make sure that the comparison is correct restrict the
      // key to a subset of bits.
      automatic int n_bits = {<u>$random</u>} % w + 1;
      automatic int mask = ( 1 << n bits ) - 1;</pre>
      for ( int i=0; i<w; i++ ) begin</pre>
         automatic int b = {<u>$random</u>} % w;
         {mask[b],mask[i]} = {mask[i],mask[b]};
      end
      for ( int e = 0; e < s size; e++ )
        begin
           a[e] = {<u>$random</u>} & mask;
           shadow[e] = a[e];
           if ( e < nlo ) alo[e] = a[e]; else ahi[e-nlo] = a[e];</pre>
        end
      if ( p.merge ) begin
         alo.sort();
         ahi.sort();
         for ( int e=0; e<nlo; e++ ) a[e] = alo[e];</pre>
         for ( int e=nlo; e<n; e++ ) a[e] = ahi[e-nlo];</pre>
      end
      #1;
      shadow.sort();
      for ( int e = 0; e < s size; e++ ) begin</pre>
         automatic logic [w-1:0] elt = x[p.idx][e];
         if ( shadow[e] === elt ) continue;
         this elt err count++;
         g elt err count++;
         if ( g elt err count > 5 ) continue;
         $write
           ("Mod %s, n=%0d, sort %2d idx %2d, wrong elt %d != %d (correct)\n",
            mut, n, i, e, elt, shadow[e]);
      end
      if ( this_elt_err_count ) this_sort_err_count++;
   end
   if ( this sort err count ) g sort err count++;
```

\$write("Tests for %s (idx %0d) n=%0d done, errors in %0d of %0d sorts.\n",
mut, p.idx, n, this_sort_err_count, n_tests);

end

end

endmodule

// cadence translate_on

LSU EE 4755

Homework 6 solution Due: 10 October 2018

Problem 1: Use the simple model to compute the cost and delay (critical path length) of the inferred hardware for module behav_merge from Homework 5. This module has two inputs, a and b, each of which is an *n*-element sorted sequence of *w*-bit unsigned integer values. Output x is a 2n-element array of *w*-bit quantities. The module assigns elements of a and b to x so that x itself is a sorted sequence of the elements from a and b.

Show the cost and delay of $behav_merge$ in terms of n and w. The Homework 5 module appears below. Use the tree implementation of multiplexors for cost and delay. (See the simple model notes.) Make reasonable optimizations, such as using the same multiplexor for a[ia] and a[ia++]. Avoid tedious optimizations such as varying the number of bits in ia and ib.

Solution on next page.

```
module behav_merge
  #(int n = 4, int w = 8)
   ( output logic [w-1:0] x[2*n], input uwire [w-1:0] a[n], b[n] );
   logic [$clog2(n+1)-1:0] ia, ib;
   always_comb begin
       ia = 0; ib = 0;
       for ( int i = 0; i < 2*n; i++ )</pre>
         x[i] = ib == n || ia < n && a[ia] <= b[ib] ? a[ia++] : b[ib++];
   end
endmodule
                                   behav_merge, n, w
                          а
                                   lg n.↓ ↓lg n
                                    ia
                                       ib
                          b
                                 a[0]
                                 a[1]
                                 000
                                                               x[i]
                                 b[0]
                                 b[1]
                                 ŝ
                                 +
                                          +
                                    0
                                         0
                                                                      ×
                                         ib
                                    lia
                                        <u>_(=</u>
                                 a[0]
                                 a[1]
                                 000
                                          \leq
                                 b[0]
                                 b[1]
                                 ŝ
                                    ia
                                         ih
                                                                    ž
```

The inferred hardware appears above. The problem did not explicitly ask for the inferred hardware, but cost and delay could not be found without it. The diagram shows the hardware resulting from two for loop iterations, for outputs i and i+1. The cost is dominated by the cost of the multiplexors implementing a[ia] and b[ib]. Each of these muxen, before optimization, has n inputs of w bits, for a cost of 3w(n-1) u_c each. Since there are 2n iterations, the total cost of the a and b multiplexors will be $2n \times 2 \times 3w(n-1)$ u_c $\approx 12wn^2$ u_c. That's expensive. The cost will be less than that because the muxen for iteration i < n only need i inputs. But accounting for that would not even cut the cost in half.

The muxen producing the value of x[i] cost $3w u_c$ each for a total cost of $6wn u_c$. The muxen passing ia and ib (incremented or not) cost $3 \lg n u_c$ each for a total cost of $12n \lg n u_c$.

Magnitude comparison units (\leq) of w bits have a cost of $4w u_c$ and a delay of $2w + 1 u_t$, so the total cost of these units is $8wn u_c$. The = n limit units test whether is and ib have reached their maximum value, n. In general an ω -bit comparison unit cost $4\omega - 1 u_c$ but in this case one input is a constant, and so the first column of

XOR gates is converted into either NOT gates or wire, and so the cost is reduced to $\omega - 1 u_c$. For behav_merge $\omega \rightarrow \lceil \lg(n+1) \rceil \approx \lg n$. There are two limit units per iteration, for a total of 4n units and so their total cost is $4n \lg n u_c$.

The adders to increment ia and ib operate on $\lg n$ -bit quantities. Unoptimized and based on a ripple implementation they would cost $9 \lg n u_c$. But since one input is the constant 1 the ripple adder can be built using binary half-adders, at a cost of $3 u_c$ per bit, for a cost of $3 \lg n u_c$. There are 4n adders for a total cost of $12n \lg n u_c$.

The cost of everything is:

$$2 \times \underset{n}{\text{big mux}} \underset{1}{\underset{n}{\text{big mux}}} x \underset{n}{\underset{n}{\text{mux}}} + \underset{1}{\underset{n}{\text{big mux}}} \underset{n}{\underset{n}{\text{big mux}}} x \underset{n}{\underset{n}{\text{big mux}}} = 2 \times \underbrace{= n}_{2 \times \underbrace{= n}} 2 \times \underbrace{+1}_{2 \text{lg } n}$$

 $= 2n \left[6wn + w + 14 \lg n \right] \mathbf{u}_{\mathbf{c}}$

The critical path is shown as a red dashed line. (The critical path also passes through ib, that's omitted for clarity and because those two paths are the same length.) Assuming a tree implementation for the mux and a ripple implementation for the comparison, each section has a critical path length of $((2 \lg n) + 2w + 1 + 1 + 2) u_t$. The total critical path length is $2n[(2 \lg n) + 2w + 1 + 1 + 2] u_t \approx (4n \lg n + 4nw) u_t$. That's long. Even if the comparison used a tree-like design with a $\lg w$ delay the critical path through the merge unit would still be very long, at least compared to the Batcher odd/even merger.

Problem 2: As was probably mentioned, a proper *n*-element Batcher odd/even merge module is constructed from $\frac{n}{2} \lceil \lg n \rceil$ sort2 modules, and the critical path length through a merge module is $\lceil \lg n \rceil$ sort2 delays.

If the previous problem was solved correctly then the cost and critical path length of **be-hav_merge** should be much larger than a Batcher merge. But the behavioral code in **behav_merge** has a run time of O(2n) running as an ordinary program, and consumes O(2n) memory, both of which are optimal for an algorithm that must operate on all of 2n items. In fact, recursively applied code based on **behav_merge** can sort a sequence in $O(n \lg n)$ time, which is the best one can normally get in many cases.

What is it about the hardware realization of **behav_merge** that makes it so much less efficient than the software realization? Your answer should consider how much hardware is being used at each moment in time.

In the hardware version a piece of hardware is needed for each of the 2n outputs. That can't be avoided because this is combinational logic. So, for example, there are $2n \leq comparison$ units, whereas in the execution of the software version there might be one ALU with just one comparison unit which gets used 2n times. This kind of efficiency could be realized with sequential logic.

```
11
/// LSU EE 4755 Fall 2018 Homework 7 -- SOLUTION
11
 /// Assignment https://www.ece.lsu.edu/koppel/v/2018/hw07.pdf
`default_nettype none
/// Problem 1
11
 /// Complete mult_seq_ds_prob_1 as described in the handout and below.
//
//
       [*] Start multiplying when in_valid is 1 at a positive clock edge ...
11
       [v] .. even if that means abandoning a multiplication in progress.
[...] Set out_avail to 1 when prod holds the result for
           most recent plier*cand.
       [✓] The module must pass the testbench.
           Average cycles should be w/m+1
       [...] The module must be synthesizable.
       [...] Make sure that synthesized hardware is reasonably fast.
       [~] Code must be reasonably efficient.
       [<] Do not change module parameters.</pre>
//
       [v] Do not change ports, EXCEPT changing between var and net kinds.

    [~] Don't assume that parameter values will match those used here.
    [~] USE DEBUGGING TOOLS LIKE SimVision.

11
module mult_seq_ds_prob_1
  input var logic out_avail,
input uwire clk, in_valid,
input uwire [w-1:0] plier, cand );
   localparam int iterations = ( w + m - 1 ) / m;
   localparam int iter_lg = <u>$clog2</u>(iterations);
localparam logic [w+m-1:0] zero = 0; // Used to set precision to w+m bits.
   uwire [iterations-1:0][m-1:0] cand 2d = cand;
   bit [iter_lg:0] iter;
logic [2*w-1:0] accum;
   always_ff @( posedge clk ) begin
      /// SOLUTION, Problem 1
      11
      // - Start a new multiplication whenever in valid is 1.
         - When multiplication is finished set out_avail to 1.
      11
      11
      if ( in valid ) begin
         // If in valid is 1 start a multiplication.
         accum = cand:
         iter = 0;
         out avail = 0;
      end else if ( !out_avail && iter == iterations ) begin
         // If a multiplication is in progress (!out_avail) ...
         // .. and we just finished the last iteration of a multiplication ..
// .. make the result available.
         out_avail = 1;
         prod = accum;
      end
      // Add on a partial product.
      // Do this whether or not a multiplication is in progress.
      accum = { zero + plier * accum[m-1:0] + accum[2*w-1:w], accum[w-1:m] };
      iter++;
   end
```

endmodule

/// Problem 2 // /// Complete mult_seq_d_prob_2 as described in the handout and below. 11 11 [~] Skip over multiplicand digits that are zero. 11 [*] Start multiplying when in_valid is 1 at a positive clock edge ... || || || || || || || .. even if that means abandoning a multiplication in progress. [•] [.] Set out_avail to 1 when prod holds the result for most recent plier*cand. $\left[\boldsymbol{\prime} \right]$ The module must pass the testbench. Average cycles should be less than w/m+1 [~] The module must be synthesizable. The period should not be too much longer than the original module. [~] Make sure that synthesized hardware is reasonably fast. [...] The module must be synthesizable. [...] Code must be reasonably efficient. ;; ;; [~] Do not change module parameters.
 [~] Do not change ports, EXCEPT changing between var and net kinds. // [<] Don't assume that parameter values will match those used here.</pre> 11 [✓] USE DEBUGGING TOOLS LIKE SimVision. module mult_seq_d_prob_2 output logic out_avail input uwire clk, in_valid, input uwire [w-1:0] plier, cand); localparam int iterations = (w + m - 1) / m; localparam int iter_lg = <u>\$clog2</u>(iterations); uwire [iterations-1:0][m-1:0] cand 2d = cand; bit [iter_lg-1:0] iter; logic [2*w-1:0] accum; always_ff @(posedge clk) begin logic [iter_lg-1:0] next_iter; /// SOLUTION -- Problem 2 // Implement handshaking. // Computation is completed when iter is zero. (See below.) 11 if (in_valid) begin iter = 0;accum = 0;out avail = 0; end else if (!out_avail && iter == 0) begin prod = accum; out avail = 1; end accum += plier * cand_2d[iter] << (iter * m);</pre> /// SOLUTION -- Problem 2 11 11 Set iter to . 11 .. index of next non-zero multiplicand digit or to zero if multiplication is complete. 11 11 11 Scan multiplicand digits starting at most significant digit. // Update next_iter whenever . (meaning that that partial product not yet use) .. 11 i > iter 11 and digit, cand_2d[i], is non-zero. 11 next iter = 0;for (int i=iterations-1; i>0; i--) if (i>iter && cand_2d[i]) next_iter = i; iter = next_iter;

end

endmodule

/// Comparison Modules

/// The modules below are for reference.

```
module mult_seq_ds_prob_1_orig
  #( int w = 16, int m = 2 )
  ( output logic [2*w-1:0] prod,
     output uwire out_avail,
input uwire clk, in_valid,
      input uwire [w-1:0] plier, cand );
   /// DO NOT MODIFY THIS MODULE.
   // It is to be used for comparison when performing synthesis.
   localparam int iterations = ( w + m - 1 ) / m;
localparam int iter_lg = <u>$clog2</u>(iterations);
localparam logic [w+m-1:0] zero = 0; // Used to set precision to w+m bits.
   uwire [iterations-1:0][m-1:0] cand_2d = cand;
   bit [iter_lg:0] iter;
logic [2*w-1:0] accum;
   always_ff @( posedge clk ) begin
       if ( iter == iterations ) begin
           prod = accum;
           accum = cand;
           iter = 0;
       end
       // Note: accum[m-1:0] is the same as cand_2d[iter];
       accum = { zero + plier * accum[m-1:0] + accum[2*w-1:w], accum[w-1:m] };
       iter++;
   end
endmodule
module mult_seq_d_prob_2_orig
  #( int w = 16, int m = 2 )
  ( output logic [2*w-1:0] prod,
     output uwire out_avail,
input uwire clk, in_valid,
      input uwire [w-1:0] plier, cand );
   /// DO NOT MODIFY THIS MODULE.
// It is to be used for comparison when performing synthesis.
   localparam int iterations = ( w + m - 1 ) / m;
   localparam int iter_lg = <u>$clog2</u>(iterations);
   uwire [iterations-1:0][m-1:0] cand_2d = cand;
   bit [iter_lg:0] iter;
   logic [2*w-1:0] accum;
   always ff @( posedge clk ) begin
       if ( iter == iterations ) begin
           prod = accum;
           accum = 0;
           iter = 0:
       end
       accum += plier * cand_2d[iter] << ( iter * m );</pre>
       iter++;
   end
endmodule
```

```
program reactivate
   (output uwire clk_reactive, output int cycle_reactive,
    input uwire clk, input var int cycle);
   assign clk_reactive = clk;
   assign cycle_reactive = cycle;
endprogram
module testbench;
   localparam int w = 20;
   localparam int num_tests = 400;
localparam int NUM_MULT = 20;
   localparam int err_limit = 7;
   bit use others;
   logic [w-1:0] plier, cand;
logic [w-1:0] plierp[NUM_MULT], candp[NUM_MULT];
   logic [2*w-1:0] prod[NUM_MULT];
   uwire availn[NUM MULT];
   logic avail[NUM MULT];
   logic in_valid[NUM_MULT];
   typedef struct { int tidx; int cycle_start; } Test_Vector;
   typedef struct { int idx;
                       int err_count = 0;
int err_timing = 0;
                       Test Vector tests_active[$];
                       bit all_tests_started = 0;
                       bit seq = 0; bit pipe = 0;
                       bit bpipe = 0;
                       int deg = 1;
                       int ncompleted = 0;
                       int cyc_tot = 0;
int latency = 0;
                       } Info;
   Info pi[string];
   localparam int cycle_limit = num_tests * w * 4;
   int cycle;
   bit done;
   logic clock;
   logic clk_reactive;
   int cycle_reactive;
   reactivate ra(clk_reactive,cycle_reactive,clock,cycle);
   initial begin
       clock = 0;
       cycle = 0;
       fork
          forever #10 cycle += clock++;
          wait( done );
          wait( cycle >= cycle limit )
    <u>$write</u>("*** Cycle limit exceeded, ending.\n");
       join_any;
       $finish();
   end
   task pi_seq(input int idx, input string name, input int deg);
       automatic string m = <u>$sformatf</u>("%s Deg %0d", name, deg);
       pi[m].deg = deg;
       pi[m].idx = idx; pi[m].seq = 1; pi[m].bpipe = 0;
   endtask
   task pi_bseq(input int idx, input string name, input int deg);
    automatic string m = <u>$sformatf</u>("%s Deg %0d", name, deg);
       pi[m].deg = deg;
       pi[m].idx = idx; pi[m].seq = 1; pi[m].bpipe = 1;
   endtask
   task pi_pipe(input int idx, input string name, input int deg);
    automatic string m = <u>$sformatf</u>("%s Deg %0d", name, deg);
       pi[m].deg = deg;
       pi[m].idx = idx; pi[m].seq = 1; pi[m].pipe = 1; pi[m].bpipe = 0;
   endtask
   task pi bpipe(input int idx, input string name, input int deg);
       automatic string m = <u>$sformatf(</u>"%s Deg %0d", name, deg);
       pi[m].deg = deg;
       pi[m].idx = idx; pi[m].seq = 1; pi[m].pipe = 1; pi[m].bpipe = 1;
   endtask
   mult_seq_ds_prob_1 #(w,1) prob1_m1(prod[6], availn[6], clock,
```

```
\leftarrow \rightarrow Fall 2018
                         \leftarrow \rightarrow Homework 7
                                                                 Homework Sol Code
                                     in_valid[6], plierp[6], candp[6]);
        initial pi_bseq(6,"Prob 1",prob1_m1.m);
        mult seq ds prob 1 #(w,2) prob1_m2(prod[7], availn[7], clock,
                                     in_valid[7], plierp[7], candp[7]);
        initial pi_bseq(7,"Prob 1", prob1_m2.m);
        in_valid[14], plierp[14], candp[14]);
initial pi_seq(14,"Seq",ms14.m);
        mult_seq_ds_prob_1_orig #(w,1) ms14(prod[14], availn[14], clock,
        mult_seq_ds_prob_1_orig #(w,2) ms4(prod[4], availn[4], clock,
                                    in_valid[4], plierp[4], candp[4]);
        initial pi seq(4, "Seq", ms4.m);
        mult_seq_ds_prob_1_orig #(w,4) ms5(prod[5], availn[5], clock,
                                    in_valid[5], plierp[5], candp[5]);
        initial pi seq(5, "Seq", ms5.m);
        mult_seq_d_prob_2 #(w,1) prob2_m1(prod[17], availn[17], clock,
                                     in_valid[17], plierp[17], candp[17]);
        initial pi bseq(17, "Prob 2", prob2 m1.m);
        mult_seq_d_prob_2 #(w,2) prob2_m2(prod[16], availn[16], clock,
        in_valid[16], plierp[16], candp[16]);
initial pi_bseq(16,"Prob 2",prob2_m2.m);
        mult_seq_d_prob_2 #(w,4) prob2_m4(prod[15], availn[15], clock,
                                     in_valid[15], plierp[15], candp[15]);
        initial pi_bseq(15,"Prob 2",prob2_m4.m);
        always @* begin
            foreach ( availn[i] ) begin
               if ( availn[i] !== 1'bz ) avail[i] = availn[i];
            end
        end
        // Array of multiplier/multiplicand values to try out.
        // After these values are used a random number generator will be used.
        11
        int tests[$] = {1,1, 1,2, 1,3, 1,4, 1,5, 1,32, 32, 1};
        initial begin
           automatic int awaiting = pi.size();
           logic [w-1:0] pliers[num_tests], cands[num_tests];
           done = 0;
            foreach ( pi[mut] ) begin
               automatic int midx = pi[mut].idx;
               automatic int steps = ( w + pi[mut].deg - 1 ) / pi[mut].deg;
               automatic int latency =
               !pi[mut].seq ? 1 : !pi[mut].pipe ? 2 * steps : steps;
pi[mut].latency = latency;
               if ( pi[mut].bpipe == 0 ) begin
                  avail[midx] = 1;
               end
               in_valid[midx] = 0;
           end
            for ( int i=0; i<num_tests; i++ ) begin</pre>
               automatic int num_bits_c = {$random()}%w + 1;
automatic logic [w-1:0] mask_c = ( (w+1)'(1) << num_bits_c ) - 1;
automatic int num_bits_p = {$random()}%w + 1;
automatic logic [w-1:0] mask_p = ( (w+1)'(1) << num_bits_p ) - 1;</pre>
               pliers[i] = tests.size() ? tests.pop_front() : {$random()}&mask_p;
cands[i] = tests.size() ? tests.pop_front() : {$random()}&mask_c;
```

```
end
```

```
fork begin
   forever @( negedge clk_reactive ) begin
      foreach ( pi[mut] ) begin
          automatic int midx = pi[mut].idx;
          if ( !in_valid[midx] && pi[mut].pipe ) begin
                plierp[midx] = cycle;
```

candp[midx] = 1;end end end end join_none; repeat (2 * w) @(negedge clock); foreach (pi[mutii]) begin automatic string muti = mutii; fork begin automatic string mut = muti; automatic int midx = pi[mut].idx; for (int i=0; i<num_tests; i++) begin</pre> (int int gap_cyc = !pi[mut].pipe ? w * 2 : ({<u>\$random</u>} % 2) ? {<u>\$random</u>} % (w + 2) : 0; automatic Test Vector tv; automatic (rest Vector tv; repeat (gap_cyc) @(negedge clock); plierp[midx] = pliers[i]; candp[midx] = cands[i]; in valid[midx] = 1; tv.tidx = i; tv.cycle_start = cycle; pi[mut].tests_active.push_back(tv); @(negedge clock); in_valid[midx] = 0; end pi[mut].all_tests_started = 1; end join_none; fork begin automatic string mut = muti; automatic int midx = pi[mut].idx; while (1) begin @(negedge clock); while (pi[mut].tests_active.size() == 0 && !pi[mut].all_tests_started) @(negedge clock); if (pi[mut].tests_active.size() == 0) break; begin automatic Test_Vector tv = pi[mut].tests_active.pop_front(); automatic int \overline{i} = tv.tidx; automatic logic [2*w-1:0] shadow_prod = pliers[i] * cands[i]; automatic int eta = tv.cycle_start + pi[mut].latency; automatic bit timing_err = 0; automatic int delta t; if (pi[mut].bpipe) begin if (!pi[mut].pipe && cycle == tv.cycle_start) @(negedge clock); while (!avail[midx] && cycle < eta) @(negedge clock);</pre> if (!avail[midx] || cycle > eta) begin timing err = 1;if (pi[mut].err_timing++ < err_limit)</pre> <u>\$write</u>("At cyc_%4d (eta %0d) avail not set for %s (idx %0d) after %0d cycles for 0x%0h*0x%0h.\n", cycle, eta, mut, midx, cycle - tv.cycle_start, pliers[i], cands[i]); end end else begin wait (cycle >= eta); end delta_t = cycle - tv.cycle_start; if (!timing_err) begin pi[mut].ncompleted++; pi[mut].cyc_tot += delta_t; end if (!timing_err && shadow_prod !== prod[midx]) begin pi[mut].err_count++; if (pi[mut].err_count < err_limit) begin</pre> \$write ("%-15s test %5d cyc %0d+%0d (%0d) wrong: 0x%0h * 0x%0h: 0x%0h != 0x%0h (correct)\n", mut, i, tv.cycle_start, delta_t, pi[mut].latency, pliers[i], cands[i], prod[midx], shadow_prod); end end end end awaiting--; end join none; end

wait(awaiting == 0 || cycle > cycle_limit);

```
$write("At cycle %0d. Error types: couldn't test / wrong result / timing\n",cycle);
foreach ( pi[ mut ] )
    $write("For %-18s ran %4d tests, %4d/%4d/%4d errors found. Avg cyc %.lf\n",
    mut, num_tests,
    num_tests - pi[mut].ncompleted,
    pi[mut].err_count, pi[mut].err_timing,
    pi[mut].seq ? real'(pi[mut].cyc_tot) / pi[mut].ncompleted : 1);
done = 1;
$write("Modules instantiated with w = %0d.\n",w);
$finish(2);
```

end

endmodule

// cadence translate_on
LSU EE 4755

Homework 8 Solution Due: 27 November 2018

Problem 1: Appearing below is the output of the simulator and synthesis script, showing data for the Homework 7 solution modules. Modules are simulated and synthesized for w = 32.

Module Name	Area	Period	Period				
		Target	Actual				
mult_seq_ds_prob_1_w32_m1	157813	1000	14926				
<pre>mult_seq_ds_prob_1_w32_m2</pre>	185493	1000	15431				
mult_seq_ds_prob_1_w32_m4	242568	1000 1629					
mult_seq_d_prob_2_w32_m1	288580	1000	31944				
mult_seq_d_prob_2_w32_m2	301203	1000	32204				
<pre>mult_seq_d_prob_2_w32_m4</pre>	329226	1000	32192				
For Prob 1 Deg 1 ran	400 tests, 0/	0/ 0	errors	found.	Avg	сус	33.0
For Prob 1 Deg 2 ran	400 tests, 0/	0/ 0	errors	found.	Avg	cyc	17.0
For Prob 1 Deg 4 ran	400 tests, 0/	0/ 0	errors	found.	Avg	сус	9.0
For Prob 2 Deg 1 ran	400 tests, 0/	0/ 0	errors	found.	Avg	сус	9.5
For Prob 2 Deg 2 ran	400 tests, 0/	0/ 0	errors	found.	Avg	сус	7.3
For Prob 2 Deg 4 ran	400 tests, 0/	0/ 0	errors	found.	Avg	сус	5.0
Modules instantiated with w	= 32.						

The Problem 1 modules are based on the streamlined multiplier and so are faster. But the Problem 2 modules skip zeros. Based on the data above, indicate the ways, if any, that the Problem 2 modules are better than the Problem 1 modules. Explain using the numbers above.

By skipping zeros the Problem 2 modules should compute a result with lower latency (in less time) than the Problem 1 modules, which require $\lceil w/m \rceil + 1$ cycles regardless of the numbers being multiplied. The latency for a multiplication is the product of the clock period and the average number of cycles required. For the Problem 1 modules that works out to

 $33 \times 14.926 \,\mathrm{ns} = 492.6 \,\mathrm{ns}, \quad 17 \times 15.431 \,\mathrm{ns} = 262.3 \,\mathrm{ns}, \text{ and } \quad 9 \times 16.296 \,\mathrm{ns} = 146.7 \,\mathrm{ns}$

for the degree (m) 1, 2, and 4 modules respectively. Though the clock periods for the Problem 2 modules are larger, fewer cycles are needed to produce an answer according to the data collected by the testbench. (See the number to the right of Avg cyc.) The Problem 2 module latencies are

 $9.5 \times 31.944 \,\mathrm{ns} = 303.5 \,\mathrm{ns}, \quad 7.3 \times 32.204 \,\mathrm{ns} = 235.1 \,\mathrm{ns}, \text{ and } \quad 5.0 \times 32.192 \,\mathrm{ns} = 161.0 \,\mathrm{ns}.$

In all but the m=4 case the Problem 2 module has a lower latency than the respective Problem 1 module.

There are more problems on the next pages.

Problem 2: Appearing below is a solution to Homework 7, Problem 1, the streamlined degree-m multiplier with handshaking. The complete solution is at https://www.ece.lsu.edu/koppel/v/2018/hw07-sol.v.html. For this problem assume that w and m are both powers of 2.

```
module mult_seq_ds_prob_1 #( int w = 16, int m = 2 )
   ( output logic [2*w-1:0] prod, output logic out_avail,
                                input uwire [w-1:0] plier, cand );
     input uwire clk, in_valid,
  localparam int iterations = ( w + m - 1 ) / m;
  localparam int iter_lg = $clog2(iterations);
  uwire [iterations-1:0] [m-1:0] cand_2d = cand;
  bit [iter_lg:0] iter;
  logic [2*w-1:0] accum;
  always_ff @( posedge clk ) begin
      if ( in_valid ) begin
         accum = cand;
         iter = 0;
         out_avail = 0;
      end else if ( !out_avail && iter == iterations ) begin
         out_avail = 1;
         prod = accum;
      end
      accum = { 0 + plier * accum[m-1:0] + accum[2*w-1:w], accum[w-1:m] };
      iter++;
  end
```

endmodule

(a) Show the hardware that will be inferred for this module. The Inkscape SVG format diagram of the hardware for the streamlined sequential module from the class demo notes can be used as a starting point. It is at https://www.ece.lsu.edu/koppel/v/2018/ill-mul-seq-str.svg.



Solution appears above with the critical path shown in red. The hardware is un-optimized. Optimization opportunities include the logic for computing out_avail.

(b) Compute the cost and delays for this module using the simple model. Show these in terms of w and m. Clearly show the critical path on your diagram.

See the solution to Problem 3 for a complete delay and timing analysis. In this (Problem 2) module the cost of the adder is less because it is w + m bits, rather than 2w bits for the Problem 3 adder. Also, this module does not use a shifter or a mux to extract the multiplicand bits.

There is a problem on the next page.

Problem 3: Appearing below is a solution to Homework 7, Problem 2, the streamlined degree-m multiplier with handshaking. The complete solution is at https://www.ece.lsu.edu/koppel/v/2018/hw07-sol.v.html. For this problem assume that w and m are both powers of 2.

```
module mult seq d prob 2 #( int w = 16, int m = 2 )
   ( output logic [2*w-1:0] prod, output logic out_avail,
     input uwire clk, in_valid,
                                    input uwire [w-1:0] plier, cand );
  localparam int iterations = ( w + m - 1 ) / m;
  localparam int iter_lg = $clog2(iterations);
  uwire [iterations-1:0] [m-1:0] cand_2d = cand;
  bit [iter_lg-1:0] iter;
  logic [2*w-1:0] accum;
  always_ff @( posedge clk ) begin
      logic [iter_lg-1:0] next_iter;
      if ( in_valid ) begin
         iter = 0;
         accum = 0;
         out_avail = 0;
      end else if ( !out_avail && iter == 0 ) begin
        prod = accum;
         out_avail = 1;
      end
      accum += plier * cand_2d[iter] << ( iter * m );</pre>
     next_iter = 0;
      for ( int i=iterations-1; i>0; i-- )
        if ( i>iter && cand_2d[i] ) next_iter = i;
      iter = next_iter;
   end
```

```
endmodule
```

(a) Show the hardware that will be inferred for this module.



Hardware shown above with the critical path shown in red.

(b) Compute the cost and delays for this module using the simple model. Show these in terms of w and m. Clearly show the critical path on your diagram.



The costs and delay of each component are shown in the diagram above. The path delay for selected paths is shown in the circled orange numbers. Note that one input to all of the comparison units (for example, the zero in $\neq 0$), is a constant, reducing their costs and delays. Many of the multiplexors also have one constant data input.

The interesting thing to compare is the time needed to compute the updated accum value versus the time needed to find the next non-zero digit. The i > iter comparison, because i is a constant, takes time $\lg w/m u_t = \lg n u_t$ and

the $\neq 0$ takes less, especially if w/m > m. The mux delay is $1 u_t$ because one data input is a constant. The time to generate the new iter signal is $(1 + n + \lg n) u_t$.

The updated accum value consumes most of the time. Inputs arrive at the multiplier at time $1 + 2 \lg n$. For an unoptimized *m*-bit by w + m-bit multiplier, the least significant bit takes $(4(m-2) + 4) u_t$ to compute. Since the shifter can shift by *n* possible amounts its delay is $2 \lg n$. The least significant bit arrives at the adder at time $1 + 2 \lg n + 4(m-2) + 4 + 2 \lg n = (4 \lg n + 4m - 3) u_t$ (see the diagram). The adder requires $(4w + 4) u_t$ to finish and so the adder output is ready at time $(4 \lg n + 4m - 3 + 4w + 4) u_t$.

The clock period would include six more cycles for the latch setup time.

21 Fall 2017 Solutions

LSU EE 4755 Homework 1 solution Due: 8 September 2017

Start working on the solutions to the problems below on paper, but complete them using the computers in the lab. For instructions visit https://www.ece.lsu.edu/koppel/v/proc.html. For the complete Verilog for this assignment without visiting the lab visit https://www.ece.lsu.edu/koppel/v/2017/hw01.v.html.

Problem 1: Appearing below, and in hw01.v, is a Verilog description of a 2-input multiplexer, mux2, and a partially completed description of a 4-input mux, mux4, along with a diagram showing how a four-input mux can be made using three two-input multiplexers. Complete mux4 as described in the diagram.

It is important that mux4 instantiate three mux2 modules. Other correct 4-input multiplexer implementations will not receive credit. Also, don't forget to set the parameters correctly when instantiating modules.

```
select
module mux2
                                                                  0:0
                                                                               1:1
  #(int w = 16)
   ( output uwire [w-1:0] x,
                                                              a0
     input uwire s,
     input uwire [w-1:0] a, b );
                                                              a1
  assign x = s == 0? a : b;
                                                                                  х
endmodule
                                                              a2
module mux4
                                                              aЗ
  #(int w = 6)
   ( output uwire [w-1:0] x,
     input uwire [1:0] s,
     input uwire [w-1:0] a[3:0] );
  /// SOLUTION
  11
  // Notice that wires and modules are named based upon the select
  // bits for which they connect to the output.
  11
  uwire [w-1:0] x0x, x1x;
  mux2 #(w) m0x(x0x, s[0], a[0], a[1]);
  mux2 #(w) m1x(x1x, s[0], a[2], a[3]);
  mux2 #(w) mxx(x, s[1], x0x, x1x);
endmodule
```

Problem 2: Appearing below is a mux8 module. Complete mux8 so that it implements an 8-input multiplexer using two mux4 modules and one mux2 module. Notice that the data input to mux8 is an 8-element array of w-bit quantities. To see how to extract a subrange of an array (called a *part select* in Verilog) see the testbench module. Solve this problem by generalizing the technique appearing in the previous problem.

Credit will only be given for mux8 modules that *instantiate* two mux4 modules and a mux2 module. Yes, assign x = a[s]; is correct and the best way to do it in other situations, but the goal here is to learn about instantiation.

module mux8

```
#( int w = 5 )
( output uwire [w-1:0] x,
    input uwire [2:0] s,
    input uwire [w-1:0] a[7:0] );
```

/// SOLUTION

uwire [w-1:0] x0xx, x1xx;

mux4 #(w) m0xx(x0xx, s[1:0], a[3:0]); mux4 #(w) m1xx(x1xx, s[1:0], a[7:4]); mux2 #(w) m(x, s[2], x0xx, x1xx);

endmodule

Appearing below is the start of the testbench code. To see the complete testbench and other modules follow https://www.ece.lsu.edu/koppel/v/2017/hw01.v.html.

module testbench();

```
localparam int w = 10;
localparam int n_in_max = 8;
localparam int n_mut = 3;
uwire [w-1:0] x[n_mut];
logic [2:0] s;
logic [w-1:0] a[n_in_max-1:0];
mux2 #(w) mm2(x[0], s[0], a[0], a[1]);
mux4 #(w) mm4(x[1], s[1:0], a[3:0]);
mux8 #(w) mm8(x[2], s[2:0], a[7:0]);
initial begin
    automatic int n_test = 0;
```

automatic int n_err = 0;

```
11
/// LSU EE 4755 Fall 2017 Homework 1
11
/// SOLUTION
`default nettype none
/// Problem 1
11
/// Modify mux4 so that it implements a 4-input mux as described in handout.
11
11
      [...] Make sure that the testbench does not report errors.
      [~] Code must instantiate three mux2 modules as shown in hw01.pdf.
11
      [...] Make sure that parameters set correctly in instantiation.
11
module mux4
 #(int w = 6)
  ( output uwire [w-1:0] x,
    input uwire [1:0] s,
    input uwire [w-1:0] a[3:0] );
  /// SOLUTION
  11
     Notice that wires and modules are named based upon the select
  11
     bits for which they connect to the output.
  11
  11
  uwire [w-1:0] x0x, x1x;
  mux2 #(w) m0x(x0x, s[0], a[0], a[1]);
  mux2 #(w) mlx(x1x, s[0], a[2], a[3]);
  mux2 #(w) mxx(x, s[1], x0x, x1x);
endmodule
module mux2
 #(int w = 16)
  ( output uwire [w-1:0] x,
    input uwire s,
    input uwire [w-1:0] a, b );
  assign x = s == 0? a : b;
endmodule
/// Problem 2
11
/// Modify mux8 so that it implements an 8-input mux as described in handout.
11
      [<] Make sure that the testbench does not report errors.</pre>
11
      [...] Code must instantiate two mux4 and one mux2 modules.
11
```

// [/] Make sure that parameters set correctly in instantiation.

module mux8
#(int w = 5)

```
( output uwire [w-1:0] x,
    input uwire [2:0] s,
    input uwire [w-1:0] a[7:0] );
```

/// SOLUTION

uwire [w-1:0] x0xx, x1xx; mux4 #(w) m0xx(x0xx, s[1:0], a[3:0]); mux4 #(w) m1xx(x1xx, s[1:0], a[7:4]); mux2 #(w) m(x, s[2], x0xx, x1xx);

endmodule

/// Testbench Code 11 11 The code below instantiates some of the modules above, provides test inputs, and verifies the outputs. 11 11 11 The testbench may be modified to facilitate your solution. Of course, the removal of tests which your module fails is not a 11 method of fixing a broken module. (One might modify the testbench 11 // so that the first tests it performs are those which make it easier // to determine what the problem is, for example, test inputs that // are all 0's or all 1's.)

// cadence translate_off

```
module testbench();
   localparam int w = 10;
   localparam int n_in_max = 8;
   localparam int n mut = 3;
   uwire [w-1:0] x[n mut];
   logic [2:0] s;
   logic [w-1:0] a[n_in_max-1:0];
   mux2 #(w) mm2(x[0], s[0], a[0], a[1]);
   mux4 #(w) mm4(x[1], s[1:0], a[3:0]);
   mux8 #(w) mm8(x[2], s[2:0], a[7:0]);
   initial begin
      automatic int n test = 0;
      automatic int n_err = 0;
      for ( int i=0; i < n in max; i++ ) begin</pre>
         n test++;
         s = i;
         for ( int j=0; j<n_in_max; j++ ) a[j] = <u>$random;</u>
         #1;
         for ( int m=0; m<n mut; m++ ) begin</pre>
            automatic int n_in = 2 << m;</pre>
            automatic int sm = i & ( n in - 1 );
```

endmodule

// cadence translate_on

```
11
/// LSU EE 4755 Fall 2017 Homework 2 -- SOLUTION
11
/// Assignment http://www.ece.lsu.edu/koppel/v/2017/hw02.pdf
/// Problem 1 -- SOLUTION
11
/// Modify interp so that it performs linear interpolation. See the handout
/// and module interp_behav.
11
11
      [...] Make sure that the testbench does not report errors.
11
      [.] Module must be synthesizable.
11
      [<] Module must do some FP arithmetic.</pre>
11
      [...] Modify include statements (at end) for any new ChipWare modules.
`default_nettype none
module interp
 #( int jw = 12, int amax = 255 )
  ( output uwire valid,
    output uwire [7:0] aj,
    input uwire [31:0] x1, a1, x2, a2,
    input uwire [jw-1:0] j );
  /// Port Data Representations
  //
  // Inputs:
  11
        x1,a1,x2,a2: shortreal.
  11
        j:
                    Unsigned integer.
  11
  // Outputs:
  11
        valid:
                    Boolean, 0 = no, 1 = yes.
  11
                    Unsigned integer.
        aj:
  11
  localparam logic [2:0] rnd_even = 3'b000; // Round to closest. Default.
  uwire [jw:0] x1i, x2i;
  /// SOLUTION
  /// First, generate the valid signal.
  // Convert x1 and x2 to integers.
  //
  fp_ftoi #( jw+1 ) ftoi1(x1i, x1);
  fp ftoi #( jw+1 ) ftoi2(x2i, x2);
  11
  // Note: Since the ChipWare float-to-int module can only convert to
  // a signed integer and x is unsigned need to make the integer one
  // bit wider to accommodate the sign bit that we won't need.
  // Otherwise, values >= 2^{jw-1}, for the default, 2^{11} = 2048,
  // will be clamped to the maximum 12-bit signed representation,
  // 2047.
  // Check whether j is between x1 and x2.
  //
```

```
hw02-sol.v.html
```

```
\leftarrow \rightarrow Fall 2017
                    \leftarrow \rightarrow Homework 2
                                                     Homework Sol Code
       assign valid = x1i + j <= x2i;</pre>
       11
       /// Perform the interpolation: a_j = a_1 + j * (a_2 - a_1) / (x_2 - x_1)
       11
       uwire [31:0] delta_x, delta_a, dadx, jr, jdadx, ajr;
       uwire [7:0] status[2]; // Unused status connections for CW modules.
       fp_sub sdx(delta_x, x2, x1);
       fp sub sda(delta_a, a2, a1);
       <u>CW fp div</u> div
         ( .status(status[0]), .z(dadx), .a(delta_a), .b(delta_x), .rnd(rnd_even) );
       fp itof #(jw) itof(jr,j);
       //
       // Note: Module performs an unsigned conversion, so we don't need to
       // widen j by one bit. See ftoi3 below and ftoi1 and ftoi2 above.
       <u>CW fp mult</u> mul
         ( .status(status[1]), .z(jdadx), .a(jr), .b(dadx), .rnd(rnd_even) );
       fp add add(ajr,a1,jdadx);
       /// Convert the interpolated value to an integer and clamp it between
       // 0 and amax.
       // Declare aji signed so that the comparison operator works correctly
       // for aji < 0.
       //
       uwire signed [8:0] aji;
       fp ftoi #( 9 ) ftoi3( aji, ajr );
                   αj = aji < 0 ? 0 : aji > amax ? amax : aji[7:0];
       assign
       11
       // Note that when amax is 255 the clamp isn't necessary
       // because the float-to-int module clamps to the maximum representable
       // value, which is 255 for a 9-bit signed integer.
    endmodule
    module fp_itof
      #( int wid = 10, logic i_is_signed = 0 )
       ( output uwire [31:0] f, input uwire [wid-1:0] i);
       uwire [7:0] status;
       localparam logic [2:0] rnd_even = 3'b000;
       <u>CW_fp_i2flt</u> #( .isize(wid), .isign(i_is_signed) )
         itof ( .status(status), .a(i), .z(f), .rnd(rnd_even) );
    endmodule
```

```
\leftarrow \rightarrow Fall 2017
                     \leftarrow \rightarrow Homework 2
                                                     Homework Sol Code
   // See <a href="http://www.ece.lsu.edu/v/ref.html">http://www.ece.lsu.edu/v/ref.html</a> for ChipWare documentation.
    module fp_add(output uwire [31:0] x, input uwire [31:0] a, b );
       uwire [7:0] status;
       localparam logic [2:0] rnd_even = 3'b000; // Round to closest. Default.
       <u>CW fp add</u> add( .status(status), .z(x), .a(a), .b(b), .rnd(rnd_even) );
    endmodule
    module fp_sub(output uwire [31:0] x, input uwire [31:0] a, b );
       uwire [7:0] status;
       localparam logic [2:0] rnd_even = 3'b000; // Round to closest. Default.
       CW fp sub sub( .status(status), .z(x), .a(a), .b(b), .rnd(rnd_even) );
    endmodule
    module fp ftoi
      #( int wid = 10 )
       ( output uwire [wid-1:0] i, input uwire [31:0] f);
       uwire [7:0] status;
       localparam logic [2:0] rnd_even = 3'b000; // Round to closer integer.
       localparam logic [2:0] rnd trun = 3'b001; // Round towards zero. (truncate)
       localparam logic [2:0] rnd_minf = 3'b011; // Round towards -infinity.
       CW fp flt2i #( .isize(wid) ) ftoi
         ( .status(status), .z(i), .a(f), .rnd(rnd_trun) );
    endmodule
```

```
// cadence translate_off
```

```
module interp_behav
#( int jw = 12,
    int amax = 255 )
  ( output logic valid,
    output logic [7:0] aj,
    input uwire [31:0] x1, a1, x2, a2,
    input uwire [jw-1:0] j );
```

```
always_comb begin
```

```
automatic shortreal x1r = $bitstoshortreal(x1);
automatic shortreal x2r = $bitstoshortreal(x2);
automatic shortreal a1r = $bitstoshortreal(a1);
automatic shortreal a2r = $bitstoshortreal(a2);
automatic int x1i = $floor(x1r);
automatic int x2i = $floor(x2r);
automatic int xj = x1i + j;
shortreal dadx, ajr;
valid = xj <= x2i;
dadx = ( a2r - a1r ) / ( x2r - x1r );
ajr = a1r + j * dadx;
aj = ajr < 0 ? 0 : ajr > amax ? amax : $floor(ajr);
```

endmodule

// The code below instantiates some of the modules above, // provides test inputs, and verifies the outputs. //

// The testbench may be modified to facilitate your solution. Of // course, the removal of tests which your module fails is not a // method of fixing a broken module. (One might modify the testbench // so that the first tests it performs are those which make it easier // to determine what the problem is, for example, test inputs that // are all 0's or all 1's.)

```
module testbench();
```

```
localparam bit trunc x1 = 1;
localparam int err_max_display = 20;
localparam shortreal tolerance = 0.0001;
localparam int num_tests = 2000;
localparam int xmin = 0;
localparam int xmax = 3839;
localparam longint rand max = longint'(1) << 32;</pre>
localparam shortreal xscale = shortreal'(xmax) / rand_max;
localparam shortreal short_len = 5;
localparam shortreal short_scale = short_len / rand_max;
localparam int amax = 255;
localparam shortreal ascale = shortreal'(amax) / rand_max;
localparam int jw = 12;
typedef struct
  Ł
  string name;
  int err valid = 0;
   int err_aj = 0;
  } Info;
Info muts[int];
task new_interp(input int idx, input string name);
  muts[idx].name = name;
endtask
localparam int mut_n_max = 5;
logic [jw-1:0] mj;
             mvalid[mut_n_max];
uwire
uwire [7:0] maj[mut n max];
logic [31:0] mx1, mx2, ma1, ma2;
<u>interp_behav</u> #(jw) iO(mvalid[0], maj[0], mx1, ma1, mx2, ma2, mj);
initial new_interp(0,"interp_behav");
interp #(jw) i1(mvalid[1], maj[1], mx1, ma1, mx2, ma2, mj);
```

```
\leftarrow \rightarrow Fall 2017 \leftarrow \rightarrow Homework 2
```

```
initial new_interp(1,"interp");
initial begin
   for ( int i=0; i<num_tests; i++ ) begin</pre>
      automatic bit short_line = $random & 1;
      automatic shortreal x[] = { {$random} * xscale, {$random} * xscale };
      shortreal len1;
      shortreal x1, x2, a1, a2, dadx;
      int x1i, x2i;
      int npts;
      x.sort();
      len1 = x[1] - x[0];
      if ( short_line && len1 > short_len )
        x[1] = x[0] + {<u>$random</u>} * short_scale;
      if (trunc_x1) x[0] = \frac{floor}{x[0]};
      x1 = x[0]; x2 = x[1];
      mx1 = <u>$shortrealtobits</u>(x1);
      mx2 = <u>$shortrealtobits</u>(x2);
      a1 = {<u>$random</u>} * ascale;
      a2 = {<u>$random</u>} * ascale;
      ma1 = <u>$shortrealtobits</u>(a1);
      ma2 = <u>$shortrealtobits</u>(a2);
      dadx = (a2 - a1) / (x2 - x1);
      x1i = <u>$floor</u>(x1);
      x2i = \frac{floor}{x2};
      npts = x2i - x1i + 1;
      for ( int j=0; j<npts+10; j++ ) begin</pre>
         automatic shortreal aj = a1 + ( x1i + j - x1 ) * dadx;
         automatic int aji = aj < 0 ? 0 : aj > amax ? amax : <u>$floor(aj</u>);
         automatic shortreal ajfrac = aj - aji;
         automatic int tol =
           ajfrac < tolerance ? -1 : ajfrac > 1 - tolerance ? 1 : 0;
         automatic int ajalt = aji + tol;
         automatic logic valid = j < npts;</pre>
         mj = j;
         #1;
         foreach ( muts[m] ) begin
             if ( mvalid[m] !== valid ) begin
                if ( muts[m].err_valid < err_max_display )</pre>
                  <u>$write</u>("Err in %s for %4.1f, %4.1f, j=%0d, valid %0d != %0d (correct)\n",
                          muts[m].name, x1, x2, j, mvalid[m], valid );
                muts[m].err_valid++;
            end
             if ( valid && mvalid[m] && maj[m] !== aji && maj[m] !== ajalt )
               begin
                  if ( muts[m].err_aj < err_max_display )</pre>
                    $write("Err in %s for %4.1f, %4.1f, j=%0d, aj=%.4f %0d != %0d (correct)\n",
                            muts[m].name, a1, a2, j, aj, maj[m], aji );
                  muts[m].err_aj++;
               end
```

```
end
```

```
. . .
```

```
end
foreach ( muts[m] )
    <u>$write</u>("Done with tests for %s, %0d + %0d errors.\n",
        muts[m].name,muts[m].err_valid, muts[m].err_aj);
```

endmodule

`define SIMULATION_ON

// cadence translate_on

`default_nettype wire

`*ifdef* SIMULATION_ON

`include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/sim/verilog/CW/CW_fp_mult.v"
`include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/sim/verilog/CW/CW_fp_add.v"
`include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/sim/verilog/CW/CW_fp_sub.v"
`include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/sim/verilog/CW/CW_fp_div.v"
`include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/sim/verilog/CW/CW_fp_div.v"
`include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/sim/verilog/CW/CW_fp_div.v"
`include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/sim/verilog/CW/CW_fp_div.v"

`else

`include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/syn/CW/CW_fp_mult.v"
`include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/syn/CW/CW_fp_add.v"
`include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/syn/CW/CW_fp_sub.v"
`include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/syn/CW/CW_fp_i2flt.v"
`include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/syn/CW/CW_fp_i2flt.v"
`include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/syn/CW/CW_fp_i2flt.v"
`include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/syn/CW/CW_fp_i2flt.v"
`include "/apps/linux/cadence/DDIEXPORT23/GENUS231/share/synth/lib/chipware/syn/CW/CW_fp_flt2i.v"

`endif

```
11
/// LSU EE 4755 Fall 2017 Homework 4
11
/// SOLUTION
/// Assignment http://www.ece.lsu.edu/koppel/v/2017/hw04.pdf
/// Additional Resources
 11
 // Verilog Documentation
        The Verilog Standard
 11
          http://standards.ieee.org/getieee/1800/download/1800-2012.pdf
 11
 11
        Introductory Treatment (Warning: Does not include SystemVerilog)
 11
          Brown & Vranesic, Fundamentals of Digital Logic with Verilog, 3rd Ed.
 11
 // Account Setup and Emacs (Text Editor) Instructions
          http://www.ece.lsu.edu/koppel/v/proc.html
 11
```

// To learn Emacs look for Emacs tutorial.

`*default_nettype* none

```
/// Problem 1
11
/// Modify maxrun so that it keeps track of the current and maximum runs.
11
11
      [~] Make sure that the testbench does not report errors.
11
      [<] Module must be synthesizable.</pre>
11
      [<] Code must be reasonably efficient.</pre>
/// Solution 1: Written for maximum code clarity.
11
module maxrun
 #(int w = 2,
    int c = 4)
   ( output uwire [w-1:0] len,
```

```
output logic [c-1:0] mr char,
  input uwire clk, reset, mr,
  input uwire [c-1:0] in char );
logic [w-1:0] cr_len, mr_len;
logic [c-1:0] prev_char;
assign len = mr ? mr len : cr len;
always ff @( posedge clk ) begin
   if (reset) mr len = 0;
   if ( !reset && in char == prev char )
     cr_len++;
   else
     cr_len = 1;
   if ( cr_len > mr_len )
     begin
        mr len = cr len;
        mr char = in char;
     end
```

```
prev char = in char;
```

endmodule

11

```
/// Solution 2: Written for high performance.
module maxrun opt
  #(int w = 2,
     int c = 4)
   ( output uwire [w-1:0] len,
     output logic [c-1:0] mr_char,
     input uwire clk, reset, mr,
     input uwire [c-1:0] in char );
   logic [w-1:0] cr_len, mr_len;
   logic [c-1:0] prev_char;
   assign len = mr ? mr_len : cr_len;
   always_ff @( posedge clk ) begin
      logic match;
      match = in_char == prev_char;
      /// Approach to Reducing Critical Path
      11
      11
           To keep addition off the critical path ...
           .. check cr_len >= mr_len && match ..
      11
           .. rather than using incremented cr_len for: cr len > mr len.
      11
      11
      11
           Based on experimentation, use ...
           .. cr len >= mr_len ..
      11
      11
           .. instead of ..
           .. cr_len == mr_len ..
      11
           .. even though cr len == mr len is easier to compute.
      11
      if ( reset ) begin
         mr_len = 1;
         mr char = in char;
      end else if ( cr len >= mr_len && match ) begin
         mr len = cr len + 1;
         mr char = in char;
      end
      if ( !reset && match )
        cr_len = cr_len + 1;
      else
        cr_len = 1;
      prev_char = in_char;
   end
```

endmodule

/// Testbench Code 11 The code below instantiates some of the modules above, 11 11 provides test inputs, and verifies the outputs. 11

```
\leftarrow \rightarrow Fall 2017
                  \leftarrow \rightarrow Homework 4
                                              Homework Sol Code
   // The testbench may be modified to facilitate your solution. Of
   11
        course, the removal of tests which your module fails is not a
   11
        method of fixing a broken module. (One might modify the testbench
   // so that the first tests it performs are those which make it easier
// to determine what the problem is, for example, test inputs that
   // are all 0's or all 1's.)
   // cadence translate off
   program reactivate
       (output uwire clk_reactive, output int cycle_reactive,
        input uwire clk, input var int cycle);
       assign clk reactive = clk;
       assign cycle reactive = cycle;
   endprogram
   module testbench;
       localparam int char_wid = 8;
       localparam int count_wid = 10;
       localparam int test_num_chars = 100;
       localparam int cycle_limit = test_num_chars + 20;
       localparam int nmuts = 1;
       localparam int char mask = ( 1 << char wid ) - 1;</pre>
       uwire [count_wid-1:0] len[nmuts];
       uwire [char wid-1:0] mr char[nmuts];
       logic [char wid-1:0] char, shadow last char;
       logic mr;
       logic clock, reset;
       bit done;
       int cycle;
       logic clk reactive;
       int cycle reactive;
       reactivate ra(clk reactive,cycle reactive,clock,cycle);
       initial begin
          clock = 0;
          cycle = 0;
          fork
             forever #10 cycle += clock++;
             wait( done );
             wait( cycle >= cycle limit )
                $write("*** Cycle limit exceeded, ending.\n");
          join any;
          $finish();
       end
       maxrun_opt #(count_wid, char_wid) mr1 (len[0],mr_char[0], clock, reset, mr, char);
       initial begin
          automatic int n_err_cr_len = 0, n_err_mr_len = 0, n_err_mr_char = 0;
          int shadow_mr_len, shadow_mr_char, shadow_cr_len;
          bit is_err_cr_len, is_err_mr_len, is_err_mr_char;
```

```
done = 0;
```

```
\leftarrow \rightarrow Fall 2017 \leftarrow \rightarrow Homework 4
```

```
reset = 0;
char = 0;
mr = 0;
@( posedge clk reactive );
for ( int i=0; i<test_num_chars; i++ ) begin</pre>
   automatic bit do reset = i == 0 || {<u>$random</u>} % 10 == 0;
   automatic bit do_new_char = {<u>$random</u>} % 3 == 0;
   logic [count_wid-1:0] mr_len, cr_len;
   @( negedge clock );
   shadow_last_char = char;
   if ( do_new_char ) char = {<u>$random</u>} & char_mask;
   reset = do_reset;
   if ( !do_reset && char === shadow_last_char )
     shadow_cr_len++;
   else
     shadow cr len = 1;
   if ( do reset )
      shadow_mr_len = 0;
   if ( shadow_cr_len > shadow_mr_len ) begin
      shadow_mr_len = shadow_cr_len;
      shadow_mr_char = char;
   end
   @( posedge clk reactive );
   repeat (2) begin
      if ( mr ) mr_len = len[0]; else cr_len = len[0];
      mr = !mr;
      #0; #0;
   end
   is err cr len = shadow cr len !== cr len;
   is_err_mr_len = shadow_mr_len !== mr_len;
   is err mr char = shadow mr char !== mr char[0];
   $write
     ("%5d %1s c=%2x
                      cr len %3d %s
                                          mr len %3d %s
                                                          mr c %2x %s\n",
      i, do reset ? "r" : " ", char,
      cr len,
      is err cr len ? <u>$sformatf("!= %3d", shadow cr len) : "ok</u>
      mr len,
                                                                     ۳,
      is err mr len ? <u>$sformatf("!= %3d", shadow mr len) : "ok</u>
      mr char[0],
      is err mr char ? <u>$sformatf("!= %2x"</u>, shadow mr char) : "ok
                                                                      ");
   if ( shadow cr len !== cr len ) n err cr len++;
   if ( shadow_mr_len !== mr_len ) n_err_mr_len++;
   if ( shadow_mr_char !== mr_char[0] ) n_err_mr_char++;
end
```

```
$write("Done with %0d tests, %0d %0d %0d errors found.\n",
    test_num_chars,
    n_err_cr_len,
    n_err_mr_len,
    n_err_mr_char);
```

done = 1;

end

endmodule

// cadence translate_on

bad = 0;

```
11
/// LSU EE 4755 Fall 2017 Homework 5 -- SOLUTION
11
 /// Assignment http://www.ece.lsu.edu/koppel/v/2017/hw05.pdf
`default_nettype none
/// Problem 1
11
 /// Complete so that lookup_char finds index of character.
11
//
       [~] Module must be synthesizable.
       [...] Code must be reasonably efficient.
//
11
       [~] Do not change module parameters.
//
       [<] Do not change ports, EXCEPT changing between var and net kinds.</pre>
       [/] The module must synthesize into combinational logic (no latches).
11
       [.] Don't assume that parameter values will match those used here.
11
       [...] See a 2016 homework assignment.
11
module lookup char
  #(int w = 4,
     int n = 3,
     logic [w-1:0] chars[n] = '{ "a", "2", "g" },
     int c = \frac{clog2}{n}
   ( output logic found,
     output logic [c-1:0] idx,
     input uwire [w-1:0] char );
   always comb begin
      found = 0;
      idx = 0;
      for ( int i=0; i<n; i++ )</pre>
        if ( chars[i] == char ) begin found = 1; idx = i; end
   end
endmodule
/// Problem 2
11
 /// Complete so that nest checks for properly nested characters.
//
11
       [.] Use lookup_char in nest.
//
        [<] Module must be synthesizable.</pre>
11
       [~] Code must be reasonably efficient.
11
       [<] Do not change module parameters.</pre>

    [v] Do not change ports, EXCEPT changing between var and net kinds.
    [v] Outputs bad, level, and awaiting should change on positive clk edge.

11
11
       [<] Don't assume that parameter values will match those used here.</pre>
11
module nest
  #(int d = 8,
     int w = 8,
     int n = 2,
     logic [w-1:0] char_open[n] = { 1, 2 },
logic [w-1:0] char_close[n] = { 3, 4 },
     int dw = \frac{clog2}{d+1}
  ( output logic [dw-1:0] level,
  output uwire [w-1:0] awaiting,
    output uwire is_open, is_close,
    output logic bad,
input uwire clk, reset,
input uwire [w-1:0] in_char );
   localparam int nw = <u>$clog2(n);</u>
   uwire [nw-1:0] loidx, lcidx;
   lookup_char #(w,n,char_open) l1(is_open,loidx,in_char);
   lookup_char #(w,n,char_close) l2(is_close,lcidx,in_char);
   logic [nw-1:0] stack [1:d];
   assign awaiting = char_close[stack[level]];
   always_ff @( posedge clk ) begin
      if ( reset ) begin
         level = 0;
```

end else begin

if (is open) begin if (level == d) bad = 1; level++; stack[level] = loidx: end else if (is_close) begin if (awaiting != in_char || !level) bad = 1; level--; end end end endmodule /// Testbench Code 11 // The code below instantiates some of the modules above, 11 provides test inputs, and verifies the outputs. 11 // The testbench may be modified to facilitate your solution. Of course, the removal of tests which your module fails is not a 11 11 method of fixing a broken module. (One might modify the testbench so that the first tests it performs are those which make it easier 11 11 to determine what the problem is, for example, test inputs that // are all 0's or all 1's.) // cadence translate_off program reactivate (output uwire clk_reactive, output int cycle_reactive, input uwire clk, input var int cycle); assign *clk reactive* = clk; assign cycle_reactive = cycle; endprogram module testbench; localparam int w = 8; localparam int max_depth = 6; localparam int dw = <u>\$clog2</u>(max_depth); // Maximum number of groups for which to show traces. 11 localparam int show_groups_bad = 3; localparam int show_groups_good = 2; localparam int num_seq = 1000; localparam int cycle_limit = num_seq * 1000; localparam logic [w-1:0] char_open[] = { "(", "[", "{", "<" }; localparam logic [w-1:0] char_close[] = { ")", "]", "}", ">" }; localparam int num_pairs = 4; initial begin if (num_pairs != char_open.size())
 <u>\$error("Size of char_open, %0d, different than num_pairs., %0d",</u> char_open.size(), num_pairs); end uwire is_op, is_cl, bad; logic [w-1:0] in_char; uwire [w-1:0] await; logic [dw-1:0] lev; logic clock, reset; bit done: int cycle; logic clk_reactive; int cycle reactive; reactivate ra(clk_reactive,cycle_reactive,clock,cycle);

int num_tests, errs_bad, errs_op, errs_cl, errs_lv, errs_await;

```
initial begin
    clock = 0;
    cycle = 0;
    fork
        forever #10 cycle += clock++;
        wait( done );
       wait( cycle >= cycle_limit )
<u>$write</u>("*** Cycle limit exceeded, ending.\n");
    join_any;
    <u>$write</u>
      ("End of %0d tests, errors: %0d + %0d + %0d + %0d + %0d = %0d\n",
        num_tests,
        errs_op, errs_cl, errs_bad, errs_lv, errs_await,
        errs_op + errs_cl + errs_bad + errs_lv + errs_await );
    $finish();
end
nest #(max_depth,w,num_pairs,char_open,char_close)
n1(lev, await, is_op, is_cl, bad, clock, reset, in_char );
localparam string oe[] = '{" ","er"};
logic [w-1:0] chars_plain[$];
bit chars_br[int];
int nchars_plain;
initial begin
    automatic int groups_good_count = 0;
automatic int groups_bad_count = 0;
    num_tests = 0;
    errs_bad = 0;
    errs_{op} = 0;
   errs_cl = 0;
errs_lv = 0;
    errs_await = 0;
    foreach ( char_open[c] ) chars_br[c] = 1;
foreach ( char_close[c] ) chars_br[c] = 1;
for ( int i=0; i<26; i++ ) begin</pre>
       chars_plain.push_back("A" + i);
chars_plain.push_back("a" + i);
    end
    nchars_plain = chars_plain.size();
    done = 0;
    reset = 0:
    in_char = 0;
    @( negedge clk_reactive );
    for ( int s=0; s<num_seq; s++ ) begin</pre>
       automatic int targ_depth = {$random} % max_depth;
automatic int curr_depth = 0;
automatic int stack[$];
       automatic bit hit_target = 0;
automatic bit back_to_0 = 0;
        automatic int c = \overline{0};
       automatic bit shadow_bad = 0;
automatic bit botch_close = {$random} % 2;
        automatic int bad_cyc = 0;
        automatic byte shadow_await;
        automatic string trace text[$];
        automatic int some err = 0;
       automatic bit err_op;
automatic bit err_cl;
        trace_text.push_back("\n");
        reset = 1;
        @( negedge clock );
        @( negedge clock );
        reset = 0:
        while ( !back_to_0 && c < 100 && bad_cyc < 3 ) begin
            automatic bit plain = {<u>$random</u>} & 1;
            automatic bit b_open
    = {<u>$random</u>} & 'hff > ( hit_target ? 'hc0 : 'h40 );
```

if (plain) begin in_char = chars_plain[{<u>\$random</u>} % nchars_plain]; end else begin automatic int idx = {\$random} % num pairs; if (b_open) begin in_char = char_open[idx]; curr_depth++; stack.push back(idx); if (curr_depth == targ_depth) hit_target = 1; if (curr_depth > max_depth) shadow_bad = 1; end else begin automatic bit botch_this_close = botch_close && {<u>\$random</u>} & 'hff > 'h40; automatic int tos = curr_depth > 0 ? stack.pop_back() : idx; in_char = char_close[botch_this_close ? (tos+1)%num_pairs : tos]; if (curr_depth == 0 || botch_this_close) shadow_bad = 1; curr_depth--; if (curr depth == 0 && hit target) back to 0 = 1; end end shadow await = char close[stack.size() ? stack[stack.size()-1] : 0]; #1; err_op = is_op !== (!plain && b_open); err_cl = is_cl !== (!plain && !b_open); @(posedge clk_reactive); begin automatic bit checkable = !bad && !shadow_bad; automatic bit err_bad = bad !== shadow_bad; automatic bit err_lv = checkable && lev !== curr_depth; automatic bit err_await = checkable && lev && await !== shadow await; string tr_txt; if (err_op || err_cl || err_bad || err_lv || err_await) some err++; num_tests++; errs_op += err_op; errs_cl += err_cl; errs_bad += err_bad; errs lv += err lv; errs await += err await; if (!checkable) bad_cyc++; tr_txt \$sformatf ("cyc %4d s.c %2d.%2d %1s op %1h %2s cl %1h %2s bad %1h %2s lev %2d %2d %2s await '%1s%1s' %2s\n", cycle, s, c, in_char, is_op, oe[err_op], is_cl, oe[err_cl], bad, oe[err_bad], lev, curr_depth, oe[err_lv], await, shadow await, oe[err await]); trace_text.push_back(tr_txt); if (some_err && groups_bad_count < show_groups_bad)</pre> while (trace_text.size()) <u>\$write(trace_text.pop_front());</u> end C++: @(negedge clock); end if (!some_err && groups_good_count < show_groups_good) while (trace_text.size()) <u>\$write(</u> trace_text.pop_front()); if (some_err) groups_bad_count++; else groups_good_count++;

done = 1;

end

endmodule

// cadence translate_on

LSU EE 4755

Homework 6 Solution Due: 13 November 2017

Problem 1: The solution to Homework 4, http://www.ece.lsu.edu/koppel/v/2017/hw04-sol.v.html, includes two modules, maxrun and maxrun_opt.

(a) Show the hardware inferred for maxrun. The Verilog code appears below.

```
module maxrun #( int w = 2, int c = 4 )
   ( output uwire [w-1:0] len,
                                     output logic [c-1:0] mr_char,
                                     input uwire [c-1:0] in_char );
     input uwire clk, reset, mr,
  logic [w-1:0] cr_len, mr_len;
  logic [c-1:0] prev_char;
  assign len = mr ? mr_len : cr_len;
  always_ff @( posedge clk ) begin
      if ( reset ) mr_len = 0;
      if ( !reset && in_char == prev_char )
        cr_len++;
      else
        cr_len = 1;
      if ( cr_len > mr_len )
        begin
           mr_len = cr_len;
           mr_char = in_char;
        end
      prev_char = in_char;
   end
endmodule
```

The solution appears below.

A common difficulty was properly accounting for order of assignments to mr_len and cr_len. The last assignment in the always block creates the value that is written to a register. The first illustration below shows the inferred hardware, the one below it shows the inferred hardware labeled with the Verilog code from which it was inferred.





(b) Show the hardware inferred for $\verb"maxrun_opt".$

The solution appears below.

Note that there is no register for match. That is because it is not a live-out variable. That's obvious in this case because it is declared within the block.



Problem 2: Compute the critical path for the maxrun and maxrun_opt modules using the simple model. The launch points (path starts) are at module inputs and register outputs, and the capture points (path ends) are at module outputs and register inputs. Note that with these definitions the critical path does not include the register itself. Show the critical path in terms of w, the number of bits in the len output and c, the number of bits in a character.

Short Answer: The critical path length is $(\lg c) + 2w + 3$ and its route is marked with a red dashed line in the illustration below. Grading Note: In too many submissions the critical path was not marked on the diagram, instead relying on a prose description or just hints such as the modules the path passes through. Please show the path in the diagram.

Explanation: The critical path starts at the in_char input and prev_char register output and follows the course shown. An interesting part of the critical path is the first mux on the path. The LSB of the lower data input arrives at t = 2 and the MSB arrives at t = w, which is later than the select signal, which arrives at $(\lg c) + 1$. Normally that would mean the lower data input is on the critical path. However, because the comparison unit can start when the LSB is ready the LSB arrival time determines criticality, and since $2 < (\lg c) + 1$ the select signal, not the data input, is on the critical path.

The maxrun module is slowed because the > comparison must wait for the equality test.

Also note that multiplexors with constant inputs have a delay of 1 and that a w-bit ripple adder with a constant input has a delay of about w.



Short Answer: Assuming that $2w > \lg c$ the critical path length is 2w + 4. The route of the path is shown with a red dashed line in the diagram.

Explanation: The critical path starts at the outputs of mr_len and cr_len and ends at the mr_len input. Unlike maxrun, the magnitude comparison and the equality test both start at t = 0, reducing the critical path.



1//////////////////////////////////////												
// /// LSU EE 475 //	5 Fall 2	2017	Hom	ework	7 S(OLUTI	ON					
/// Assignment http://www.ece.lsu.edu/koppel/v/2017/hw07.pdf												
//////////////////////////////////////		()	//////		///////	//////	///////////////////////////////////////	(//////	/////			
// // Complete so that mult_fast sets out_avail as described in the handout.												
<pre>// [~] The module must be synthesizable. // [~] Code must be reasonably efficient. // [~] Do not change module parameters. // [~] Do not change ports, EXCEPT changing between var and net kinds. // [~] Don't assume that parameter values will match those used here. // [~] USE DEBUGGING TOOLS LIKE SimVision. // [~] Make sure that Avg cyc shown in testbench for Fast is lower // than Pipelined module of same degree (when all tests pass).</pre>												
/// SOLUTION - Pro	blem 1a											
// // A new pipeline // value of in_val // last stage will	latch w: id throu connect	ill be ugh th t to t	e creat he pipe the out	ed, pl line. T put por	occ, wh he pl_o t out_a	ich wil cc regi: vail.	l carry ster fou	the r the				
<pre>// The timing diag // multiplier is a // multiplicands a // 'h123 = 'h246, // outputs three o // pipeline is hig //</pre>	gram belo always so arrive, 2 * 'h4 cycles la ghlighteo	ow is et to 'h123 = 'h8 ater. d in l	for a 2 (not , 'h4, 8, and The pr blue.	w=12, m shown) and 'h5 2 * 'h5 ogress	=4 mult: . Three 6, thei 6 = 'ha of 'h12	iplier differ r produ c, appe 3 throu	in which ent cts, 2 * ar at th gh the	n the ∗ ne				
<pre>// // The timing diagram does not show the plier and cand inputs. As // stated above, the plier is always 2 (for the sample execution shown // in the diagram). The value of input cand appearing at a positive // edge can be seen in pl_cand[0] just after the positive edge. For // example, at the positive edge between cycle 0 and 1 input cand must // be 'h123.</pre>												
cycle	0	7 6	1	2	3	4	5	6	7	8		
L± clk												
⊡— in_valid												
pl_occ[0]												
pl_cand[0]		X	'h 123	X	X ^h 4	(h56	_X					
pl_accum[0]	'h0											
pl_occ[1]				X								
pl_cand[1]				('h 12	χ	(h0	('h5	_X				
pl_accum[1]				('h6	X	X 'h 8	(hc	_X			_	
pl_occ[2]					X	 						
pl_cand[2]					('h1	Χ	(h0	X'h0	_X			
pl_accum[2]					('h46	X	(h8	Thac	_X			
pl_occ[3]						A	-			-		
pl_cand[3]						('h0	X	X'h0	X'h0			
pl_accum[3]						('h 246	X	Xh8	X'hac			
- out avail							_					
prod						('h246		X'h8	(hac			
//					:	L	!		:			
/// SOLUTION Pr //	oblem 1a											
<pre>module mult_tast_1a #(int w = 16, int m = 4) (output uwire [2*w-1:0] prod, output uwire out avail</pre>												
input uwire o	:lk, in_v	valid	,									

input uwire [w-1:0] plier, cand); localparam int nstages = (w + m - 1) / m; logic [2*w-1:0] pl_accum[0:nstages]; logic [w-1:0] pl_plier[0:nstages]; logic [w-1:0] pl_cand[0:nstages]; assign prod = pl_accum[nstages]; /// SOLUTION -- Problem 1a // logic pl_occ[0:nstages]; assign out_avail = pl_occ[nstages]; 11 // Provide a pipeline latch for the in valid signal to pass through // the pipeline and connect the last stage's latch to the out_avail // port. always_ff @(posedge clk) begin /// SOLUTION -- Problem 1a 11 pl_occ[0] = in_valid; // Connect in valid port to the first stage. pl accum[0] = 0;pl_plier[0] = plier; pl_cand[0] = cand; for (int stage=0; stage<nstages; stage++) begin</pre> pl_accum[stage+1] <=</pre> pl_accum[stage] + (pl_plier[stage] * pl_cand[stage][m-1:0] << stage*m);</pre> pl_cand[stage+1] <= pl_cand[stage] >> m; pl_plier[stage+1] <= pl_plier[stage];</pre> /// SOLUTION -- Problem 1a pl occ[stage+1] <= pl occ[stage];</pre> // Pass the in_valid signal through the pipeline. end end endmodule /// SOLUTION -- Problem 1b (and also 1a) 11 // The fast multiplier is supposed to provide a shortcut connection // from each stage to the multiplier output, prod. Stage x can use the
// shortcut connection if the multiplication that the stage is // carrying is complete and if no higher-numbered stages are occupied. // A multiplication (meaning the result of multiplying a plier and // cand) must appear at the output exactly once, and the arriving // multiplications must appear at the outputs in the same order in // which they arrived. /// The Plan 11 - Find the highest-numbered occupied stage. Call it oldest_idx. // Connect the result at that stage, pl_accum[oldest_idx], to prod.
 Set out_avail to true if stage oldest_idx is finished. // // - Set pl_occ[oldest_idx] to zero if out_avail is true, to avoid duplicates. 11 11 // For the discussion below refer to module mult_fast_1b and to the // timing diagram below. The timing diagram is for a module // instantiated with w=12, m=4, and for which the multiplier is always // 2. The arriving values in the timing diagram below are the same as // the diagram appearing in the solution to Problem 1a. /// Computing oldest_idx 11 // Combinational logic will be added that computes oldest_idx, the // highest-numbered occupied stage. (Stage x is occupied if pl_occ[x] // is true.) If none of the stages are occupied oldest_idx is set to // zero. // See the always_comb block in mult_fast_1b below.

/// Connect Stage's Result to Prod
11 // Output prod is set to pl_accum[oldest_idx], see the assign in // mult fast 1b. The connection is made whether or not stage // oldest_idx is finished or contains a valid value.

// In the timing diagram notice that at cycles 2 and 3 prod holds // incomplete multiplications. That's fine because out avail is zero. // Setting prod to something like zero at cycles like 2 and 3 would // require extra hardware and provide no benefit (based on the problem

// statement in the homework handout).

/// Set out_avail

// // Output out_avail is set to 1 if stage oldest_idx is occupied and if // the multiplicand at that stage is zero, meaning that the // multiplication is complete. Whether it is occupied can be // determined by examining pl occ[oldest idx], whether it is finished // can be determined by examining pl_cand[oldest_idx]. See the "assign
// out_avail" in mult_fast_1b.

/// Set pl_occ[oldest_idx] When Done

11 // Since the result of a multiplication cannot appear at the output
// more than once pl_occ[x] must be set to zero at the end of cycle c
// if x was chosen in cycle c. (If this were not done the same // multiplication would appear at the outputs again in the next clock // cycle [c+1], when it is in stage x+1.) For example, stage 2 is
// chosen in cycle 5, its product 'h8 appears at the output. In cycle
// 6 the calculation is in stage 3, but now its value of pl_occ is

// zero and so it won't be chosen a second time.

₽	<i>cycle</i> clk in_valid		0	1	2	3	4	5	6	7	8
	pl_occ[0]										
	pl_cand[0]			('h 123	Χ	('h4	('h56	χ			
	pl_accum[0]	'h0									
	pl_occ[1]						Í	A			
	pl_cand[1]				('h 12	Χ	('h 0	('h5	Χ		
	pl_accum[1]				(ˈh6	Χ	('h 8	('hc	Χ		
	pl_occ[2]							A	X		
	pl_cand[2]					(h1	χ	('h 0	('h 0	χ	
	pl_accum[2]					(⁻ h46	χ	('h 8	('hac	Χ	
	pl_occ[3]										
	pl_cand[3]						(ⁱ h0	X	('h 0	(h0	X
	pl_accum[3]						(['] h246	Χ	('h 8	(hac	X
	oldest_idx	0			XXX1	XXX2	<u>Х</u> ХЗ	<u> </u>	<u> </u>	XXV0	
	out_avail							¥	¥		
// - E	prod				₩ ⁱ h6	₩h46	(X) h246	(XX'h8	(Whac	Χ	

module mult fast 1b

```
#(int w = 16,
    int m = 4)
  ( output uwire [2*w-1:0] prod,
    output uwire out_avail,
input uwire clk, in_valid,
input uwire [w-1:0] plier, cand );
```

localparam int nstages = (w + m - 1) / m;

logic [2*w-1:0] pl accum[0:nstages]; logic [w-1:0] pl_plier[0:nstages], pl_cand[0:nstages]; logic pl_occ[0:nstages];

/// SOLUTION -- Problem 1b 11

Determine the idx of the last (highest-numbered) occupied 11

stage, in which resides the oldest multiplication in the 11

```
// pipeline.
   11
   logic [<u>$clog2(nstages):0] oldest_idx;</u>
   always_comb begin
      oldest_idx = 0;
       for ( int i=1; i<=nstages; i++ ) if ( pl_occ[i] ) oldest_idx = i;</pre>
   end
   /// SOLUTION -- Problem 1b
   11
   11
       Connect the last occupied stage to the output ..
   //
   assign prod = pl_accum[oldest_idx];
   11
       .. and set out_avail to true if that stage is occupied and finished.
   11
   11
   assign out_avail = pl_occ[oldest_idx] && pl_cand[oldest_idx] == 0;
   always_ff @( posedge clk ) begin
      pl occ[0] = in valid;
       pl_accum[0] = 0;
       pl_plier[0] = plier;
       pl cand[0] = cand;
       for ( int stage=0; stage<nstages; stage++ ) begin</pre>
          pl_accum[stage+1] <=</pre>
            pl_accum[stage] +
               ( pl_plier[stage] * pl_cand[stage][m-1:0] << stage*m );</pre>
          pl_cand[stage+1] <= pl_cand[stage][w-1:m];
pl_plier[stage+1] <= pl_plier[stage];</pre>
          /// SOLUTION -- Problem 1b
          11
              Pass 0 to next stage if this stage is providing the result, otherwise pass this stage's value of occupied to
          11
          11
          11
             the next stage.
          11
          pl occ[stage+1] <=</pre>
            oldest_idx == stage && out_avail ? 0 : pl_occ[stage];
       end
   end
endmodule
module mult_behav_1
  #(int w = 16)
   (output logic [2*w-1:0] prod, input logic [w-1:0] plier, cand);
   assign prod = plier * cand;
endmodule
/// : Example: Basic Pipelined Multiplier -- mult_pipe
11
     Computes m partial products per stage.
//
11
module mult_pipe #( int w = 16, int m = 4 )
   ( output logic [2*w-1:0] prod,
     input logic [w-1:0] plier,
     input logic [w-1:0] cand,
     input clk);
   localparam int nstages = ( w + m - 1 ) / m;
   // Note: pl is for pipeline latch.
   logic [2*w-1:0] pl_accum[0:nstages];
logic [w-1:0] pl_plier[0:nstages];
logic [w-1:0] pl_cand[0:nstages];
   always_ff @( posedge clk ) begin
       pl_accum[0] = 0;
       pl_plier[0] = plier;
       pl_cand[0] = cand;
       for ( int stage=0; stage<nstages; stage++ ) begin</pre>
```

```
logic [w-1:0] cand_next;
cand_next = pl_cand[stage][w-1:m];
pl_accum[stage+1] <=
    pl_accum[stage] +
       ( pl_plier[stage] * pl_cand[stage][m-1:0] << stage*m );
pl_cand[stage+1] <= cand_next;
pl_plier[stage+1] <= pl_plier[stage];</pre>
```

end

end

assign prod = pl_accum[nstages];

endmodule

// cadence translate_off

```
program reactivate
  (output uwire clk_reactive, output int cycle_reactive,
    input uwire clk, input int cycle);
   assign clk_reactive = clk;
   assign cycle_reactive = cycle;
endprogram
```

module testbench;

```
localparam int w = 16;
localparam int num_tests = 400;
localparam int NUM_MULT = 20;
localparam int err_limit = 7;
bit use_others;
logic [w-1:0] plier, cand;
logic [w-1:0] plierp[NUM_MULT], candp[NUM_MULT];
logic [2*w-1:0] prod[NUM_MULT];
uwire availn[NUM_MULT];
logic avail[NUM_MULT]
logic in_valid[NUM_MULT];
typedef struct { int tidx; int cycle_start; } Test_Vector;
typedef struct { int idx;
                   int err_count = 0;
                   int err_timing = 0;
                    Test Vector tests_active[$];
                   bit all_tests_started = 0;
bit seq = 0; bit pipe = 0;
                   bit bpipe = 0;
                   int deg = 1;
                   int ncompleted = 0;
                   int cyc tot = 0;
                   int latency = 0;
                   } Info;
Info pi[string];
localparam int cycle_limit = num_tests * w * 4;
int cycle;
bit done;
logic clock;
logic clk_reactive;
int cycle_reactive;
reactivate ra(clk_reactive,cycle_reactive,clock,cycle);
initial begin
   clock = 0;
   cycle = 0;
   fork
       forever #10 cycle += clock++;
       wait( done );
       wait( cycle >= cycle limit )
    <u>$write</u>("*** Cycle limit exceeded, ending.\n");
   join_any;
   $finish();
```

 $\leftarrow \rightarrow$ Homework 7 end task pi_seq(input int idx, input string name, input int deg); automatic string m = <u>\$sformatf</u>("%s Deg %0d", name, deg); pi[m].deg = deg; pi[m].idx = idx; pi[m].seq = 1; pi[m].bpipe = 0; endtask task pi_pipe(input int idx, input string name, input int deg); automatic string m = <u>\$sformatf</u>("%s Deg %0d", name, deg); pi[m].deg = deg; pi[m].idx = idx; pi[m].seq = 1; pi[m].pipe = 1; pi[m].bpipe = 0; endtask task pi_bpipe(input int idx, input string name, input int deg); automatic string m = <u>\$sformatf</u>("%s Deg %0d", name, deg); pi[m].deg = deg; pi[m].idx = idx; pi[m].seq = 1; pi[m].pipe = 1; pi[m].bpipe = 1; endtask mult_behav_1 #(w) mb1(prod[0], plierp[0], candp[0]); initial pi["Behavioral"].idx = 0; mult_pipe #(w,4) ms2(prod[2], plierp[2], candp[2], clock); initial pi_pipe(2,"Pipelined",ms2.m); <u>mult_pipe</u> #(w,2) ms3(prod[3], plierp[3], candp[3], clock); initial pi pipe(3, "Pipelined", ms3.m); mult fast 1a initial pi_bpipe(8,"Fast 1a",ms8.m); #(w,4) ms17(prod[17], availn[17], clock, mult fast 1b in_valid[17], plierp[17], candp[17]); initial pi_bpipe(17,"Fast 1b",ms17.m); #(w,1) ms15(prod[15], availn[15], clock, mult_fast_1b in_valid[15], plierp[15], candp[15]); initial pi_bpipe(15,"Fast 1b",ms15.m); always @* foreach (availn[i]) if (availn[i] !== 1'bz) avail[i] = availn[i]; // Array of multiplier/multiplicand values to try out. // After these values are used a random number generator will be used. 11 int tests[\$] = {1,1, 1,2, 1,3, 1,4, 1,5, 1,32, 32, 1}; initial begin automatic int awaiting = pi.size(); logic [w-1:0] pliers[num_tests], cands[num_tests]; done = 0;foreach (pi[mut]) begin automatic int midx = pi[mut].idx;

```
automatic int steps = ( w + pi[mut].deg - 1 ) / pi[mut].deg;
    automatic int latency =
    !pi[mut].seq ? 1 : !pi[mut].pipe ? 2 * steps : steps;
    pi[mut].latency = latency;
if ( pi[mut].bpipe == 0 ) begin
        avail[midx] = 1;
    end
    in_valid[midx] = 0;
end
for ( int i=0; i<num_tests; i++ ) begin</pre>
    automatic int num_bits_c = {<u>$random()</u>}%w + 1;
    automatic logic [w-1:0] mask c = ( (w+1)'(1) << num_bits_c ) - 1;
automatic int num_bits_p = {$random()}%w + 1;
automatic logic [w-1:0] mask_p = ( (w+1)'(1) << num_bits_p ) - 1;</pre>
```

pliers[i] = tests.size() ? tests.pop_front() : {<u>\$random()</u>}&mask_p; cands[i] = tests.size() ? tests.pop_front() : {<u>\$random()</u>}&mask_c; end fork forever @(negedge clk reactive) foreach (pi[mut]) begin automatic int midx = pi[mut].idx; if (!in_valid[midx] && pi[mut].pipe) begin plierp[midx] = cycle; candp[midx] = 1; end end join_none; repeat (2 * w) @(negedge clock); foreach (pi[mutii]) begin automatic string muti = mutii; fork begin automatic string mut = muti; automatic int midx = pi[mut].idx; for (int i=0; i<num_tests; i++) begin</pre> automatic int gap_cyc =
 ({\$random} % (w + 2) : 0;
automatic Test_Vector tv; repeat (gap_cyc) @(negedge clock); plierp[midx] = pliers[i]; candp[midx] = cands[i]; in_valid[midx] = 1; tv.tidx = i; tv.cycle_start = cycle; pi[mut].tests_active.push_back(tv); @(negedge clock); in_valid[midx] = 0; end pi[mut].all_tests_started = 1; end join_none; fork begin automatic string mut = muti; automatic int midx = pi[mut].idx; while (1) begin @(negedge clock); while (pi[mut].tests_active.size() == 0 && !pi[mut].all_tests_started) @(negedge clock); if (pi[mut].tests_active.size() == 0) break; begin automatic Test_Vector tv = pi[mut].tests_active.pop_front(); automatic int \overline{i} = tv.tidx; automatic logic [2*w-1:0] shadow_prod = pliers[i] * cands[i]; automatic int eta = tv.cycle_start + pi[mut].latency; automatic bit timing_err = 0; automatic int delta_t; if (pi[mut].bpipe) begin while (!avail[midx] && cycle < eta) @(negedge clock);</pre> if (!avail[midx] || cycle > eta) begin timing_err = 1; if (pi[mut].err_timing++ < err_limit)</pre> <u>\$write</u>("At cyc_%4d (eta %0d) avail not set for %s (idx %0d) after %0d cycles for 0x%0h*0x%0h.\n", cycle, eta, mut, midx, cycle - tv.cycle_start, pliers[i], cands[i]); end end else begin wait (cycle >= eta); end delta_t = cycle - tv.cycle_start; if (!timing_err) begin pi[mut].ncompleted++; pi[mut].cyc_tot += delta_t; end if (!timing err && shadow prod !== prod[midx]) begin pi[mut].err_count++; if (pi[mut].err_count < err_limit) begin</pre> <u>\$write</u> ("%-15s test %5d cyc %0d+%0d (%0d) wrong: 0x%0h * 0x%0h: 0x%0h != 0x%0h (correct)\n", mut, i, tv.cycle_start, delta_t, pi[mut].latency, pliers[i], cands[i], prod[midx], shadow_prod); end end end end awaiting--: end join_none;

end

endmodule

// cadence translate_on

22 Fall 2016 Solutions

LSU EE 4755 Homework 1 solution Due: 9 September 2016

The questions below can be answered without using EDA software, paper and pencil will suffice. Please turn in the solution on paper. Homework 2 will require the use of Verilog implementations. Nevertheless, runnable SystemVerilog code for this assignment can be found at https://www.ece.lsu.edu/koppel/v/2016/hw01.v (plain Verilog) and

https://www.ece.lsu.edu/koppel/v/2016/hw01.v.html (syntax-highlighted HTML).

Those who are rusty about the correspondence between Verilog code and hardware might want to look at the solution to EE 3755 Fall 2013 Homework 1, at http://www.ece.lsu.edu/ee3755/2013f/hw01_sol.pdf.

Problem 1: Show a Verilog explicit structural description of the module illustrated below. In this assignment it is okay to use primitives (and, not,...), but don't get in the habit of using them.



- Base the names of ports, wires, and instances on labels in the illustration.
- Of course, use only primitives and wires. See Table 28-1 of IEEE Std 1800-2012 for a list of gates.

Solution appears below. In order to be explicitly structural NOT gates were instantiated to provide the inverted inputs for the AND gates. In real life, there would be no disadvantage using !a[2] in place of na2. (That may not be 100% true, because working for a company with super-strict HDL style rules is a real-life situation.)

```
module ezmod( output uwire x, y,
                                   input uwire [3:0] a ); // SOLUTION
          na0, na1, na2, na3;
  uwire
  not n0(na0,a[0]);
  not n1(na1,a[1]);
  not n2(na2,a[2]);
  not n3(na3,a[3]);
          alpha, beta, gamma;
  uwire
  and one(alpha,
                   na3, a[2], na1,
                                     a[0]);
  and two(beta,
                   a[3], a[2], na1,
                                     na0
                                          );
  and three(gamma, na3, na2, na1,
                                     na0 );
  or four(x, alpha, beta );
   xor five(y, beta, gamma );
endmodule
```

Problem 2: Answer the following questions about Verilog primitives as defined in IEEE Std 1800-2012. (See Chapter 28.) Indicate the exact section number where the answer is found.

(a) The standard provides a **not** primitive and a **nor** primitive, among others. One can easily argue that a 1-input **nor** gate is the same as a **not** gate. Does the standard actually allow Verilog code to instantiate a 1-input **nor** gate?

Yes, see Section 28.4.

Grading Note: It is not correct to answer "table 28-1 because it is shown as an *n*-input gate", because the table does not explicitly state that n == 1 is acceptable for a nor gate.

(b) Based on the standard, is there anything that can be done with a **not** primitive that can't be done with a 1-input **nor** primitive? (Don't try to answer this too deeply, just show an instantiation.)

Yes, a not primitive can have more than one output. The outputs all have the same value under unstressed circumstances. Multiple-output not gates will not be used for designs in this class.

Problem 3: Output match of module is_1133, shown below, is 1 iff its input d (digits) is 1133 in BCD (which has the same representation as 1133_16). The module instantiates BCD digit detection modules is_1 and is_3.

```
module is_1( output uwire match, input uwire [3:0] d );
    uwire z321;
    nor o0(z321,d[3],d[2],d[1]);
    and a1(match,z321,d[0]);
endmodule
module is_3( output uwire match, input uwire [3:0] d );
    uwire z32;
    nor o0(z32,d[3],d[2]);
    and a1(match,z32,d[1],d[0]);
endmodule
module is_1133( output uwire match, input uwire [15:0] d );
    uwire m1, m2, m3, m4;
    and a1(match, m1, m2, m3, m4);
```

is_1 i0(m1, d[15:12]); is_1 i1(m2, d[11:8]); is_3 i2(m3, d[7:4]); is_3 i3(m4, d[3:0]); endmodule

(a) Draw a diagram of is_1133 based on the explicit structural description above. Show the insides of the is_1 and is_3 modules. Label the diagram using the same wire and instance names used in the Verilog descriptions.

Solution appears to the right.



(a) Design a module is_1133_is that does the same thing as is_1133, but that uses implicit structural code. The correct solution requires adding only one short line to the shell shown below. Don't forget that the value in d is in BCD. Note: The word short was added after the original assignment.

Solution appears below. The comparison operator checks for the correct value. We need to compare d to the BCD representation of 1133. Verilog does not have literal format just for BCD, as it does for binary, octal, decimal, and hexadecimal. But it doesn't need one because the BCD representation of 1133 is the same as the binary representation of 1133_16, which in Verilog is 16'h1133. That means that the is_1333 module (either version) has an output that's one iff the input is the BCD representation of 1333 or the unsigned binary representation of 4403 (because $4403_10 = 1133_16$).

```
// SOLUTION
module is_1133_is( output uwire match, input uwire [15:0] d );
    assign match = d == 16'h1133;
endmodule
```

Problem 4: When completed the output of module is_1235 is 1 iff the input is 1235 in BCD.
module is_1235(output uwire match, input uwire [15:0] d);

endmodule

(a) Complete the module. The module must be explicitly structural except for the use of the concatenation operator (see Section 11.4.12). The module **must** use is_1 and is_3 to detect the digits. Do not assume or design an is_2 or is_5 and don't put in logic to detect those digits.

Solution appears below. The is_1 module is used to detect a 2 by swapping the two least-significant bits. (The same method can be used to detect a 4 or an 8.) Similarly, the is_3 is used to detect a 5 by swapping the two middle digits. (The same method can be used to detect a 6 or a 9.)

// SOLUTION

```
module is_1235( output uwire match, input uwire [15:0] d );
    uwire m1, m2, m3, m4;
    is_1 i0(m1, d[15:12]);
    is_1 i1(m2, {d[11:10],d[8],d[9]}); // Actually detect 2.
    is_3 i2(m3, d[7:4]);
    is_3 i3(m4, {d[3],d[1],d[2],d[0]}); // Actually detect 5.
    and a1(match, m1, m2, m3, m4);
endmodule
```

(b) Draw a diagram of the completed module, which should be very similar to the diagram from the previous problem.

Solution appears to the right.



```
//
/// LSU EE 4755 Fall 2016 Homework 2 -- SOLUTION
11
 /// Assignment http://www.ece.lsu.edu/koppel/v/2016/hw02.pdf
`default_nettype none
/// Problem 1
11
/// Modify aa_digit_val so that it works for any radix, not just 10.
11
11
       [<] The code must be synthesizable.</pre>
11
       [ Make sure that the testbench does not report errors.
11
       [<] Can use behavioral or implicit structural code.</pre>
module aa_decimal_digit_val
  ( output uwire [3:0] val,
   output uwire is_dig,
    input uwire [7:0] char );
  // Do not edit this module.
               is dig = char >= "0" \&\& char <= "9";
  assign
               val = is_dig ? char - "0" : 0;
  assign
endmodule
module aa_digit_val
  #( int radix = 10 )
   ( output uwire [3:0] val,
    output uwire is_dig,
    input uwire [7:0] char );
  /// SOLUTION
  // Check whether char is in range 0-9 or a-f, regardless of radix.
  11
  uwire is dig 09 = char >= "0" && char <= "9";
  uwire is dig af = char >= "a" && char <= "f";
  // Convert char to binary, assuming that it is hexadecimal.
  11
  uwire [3:0] val raw = is dig 09 ? char - "0" : char - "a" + 10;
  // Determine whether char is a valid digit in radix radix.
  11
  assign
             is dig = ( is dig 09 || is dig af ) && val raw < radix;
  assign
             val = is dig ? val raw : 0;
endmodule
```


[*] Make sure that the testbench does not report errors.
 [*] Can use behavioral or implicit structural code.

11

11

```
\leftarrow \rightarrow Fall 2016 \leftarrow \rightarrow Homework 2
```

```
module aa_full_adder
  #( int radix = 10 )
  ( output uwire [7:0] sum,
    output uwire carry_out,
    output uwire is_dig_out,
    input uwire [7:0] a, b,
    input uwire carry_in,
    input uwire is_dig_in);
```

/// SOLUTION

```
// Instantiate two aa_digit_val modules, connecting one to each
// input digit. These will determine whether each character input
// is a valid digit and if so provide the binary value of the
// digit.
11
uwire [3:0] val_a, val_b;
            is_dig_a, is_dig_b;
uwire
aa_digit_val #(radix) dva(val_a, is_dig_a, a);
aa_digit_val #(radix) dvb(val_b, is_dig_b, b);
// Compute the sum of carry_in and the binary versions of a and
// b. Note that the sum may contain a carry, and so it can not be
// assigned to the module output.
11
uwire [4:0] sum_val = carry_in + val_a + val_b;
// Determine whether there is a carry out.
11
assign
           carry_out = sum_val >= radix;
// Determine the sum, in binary, with the carry removed.
11
uwire [3:0] sum_dig_val = carry_out ? sum_val - radix : sum_val;
// Convert the sum to ASCII or to a blank if we don't have a valid digit.
11
assign sum = !is_dig_out ? " " :
       sum_dig_val < 10 ? "0" + sum_dig_val : "a" + sum_dig_val - 10;</pre>
// If the value of is dig out, below, is true then output sum will
// be set to a digit of the sum. Otherwise sum should be set to a
// blank. The value of is dig out will be false when we are past
// the last digit of both a and b, and we don't have a carry out
// from the previous digit.
11
assign is dig out = is dig in && ( carry in || is dig a || is dig b );
```

endmodule

```
module aa_width2
#( int radix = 10 )
( output uwire [1:0][7:0] sum,
    output uwire c_out,
    output uwire is_dig_out,
    input uwire [1:0][7:0] a, b,
    input uwire c_in,
    input uwire is_dig_in);

    uwire co0, id_0;
    aa_full_adder #(radix) fal(sum[0],co0,id_0,a[0],b[0],c_in,is_dig_in);
    aa_full_adder #(radix) fa2(sum[1],c_out,is_dig_out,a[1],b[1],co0,id_0);
```

endmodule

```
module reference adder
  #( int radix = 10,
    int digits = 2,
     int width = <u>$clog2( radix ** digits ) )</u>
   ( output logic [width-1:0] sum,
    output logic carry_out,
    input uwire [width-1:0] a, b,
    input uwire carry_in );
   always_comb { carry_out, sum } = 0 + carry_in + a + b;
endmodule
/// Testbench Code
11
11
   The code below instantiates some of the modules above,
11
   provides test inputs, and verifies the outputs.
11
11
   The testbench may be modified to facilitate your solution. Of
   course, the removal of tests which your module fails is not a
11
11
   method of fixing a broken module. (One might modify the testbench
   so that the first tests it performs are thoe which make it easier
11
// to determine what the problem is, for example, test inputs that
// are all 0's or all 1's.)
// cadence translate_off
// Convert integer A into a radix RADIX ASCII representation.
function automatic string radtos(int unsigned a, int radix);
      begin
         radtos = "";
        while (1)
          begin
             automatic int dig = a % radix;
             if ( radtos.len() > 0 && a == 0 ) break;
             a = a / radix;
             radtos = { dig < 10 ? "0" + dig : "a" + dig - 10, radtos };
          end
      end
endfunction
module aa test;
   logic start_done[32];
   for ( genvar radix = 2; radix <= 16; radix++ )</pre>
    aa test digit val #(radix) aa(start done[radix],start done[radix-1]);
   for ( genvar radix = 2; radix <= 16; radix++ )</pre>
    aa test width2 #(radix) aa(start_done[15+radix],start_done[15+radix-1]);
   initial begin
      start done[1] = 1;
   end
endmodule
module aa test digit val #( int radix = 10 )
   ( output logic done, input uwire start );
   localparam int err_limit = 10;
```

```
logic [7:0] a;
   uwire [3:0] dval;
   uwire
                is_d;
   aa_digit_val #(radix) dv1(dval,is_d,a);
   int digit vals[256];
   int num errs;
   initial begin
      num_errs = 0;
      wait ( start == 1 );
      digit_vals = { 256 { -1 } };
      for ( int i=0; i<radix; i++ )</pre>
        digit_vals[ i < 10 ? "0" + i : "a" + i - 10 ] = i;
      for ( int i=0; i<256; i++ )</pre>
        begin
           automatic bit is_d_shadow = digit_vals[i] >= 0 ;
           #1;
           a = i;
           #1;
           if ( is_d != is_d_shadow ) begin
              <u>$write</u>
                 ("Error in aa_digit_val for char %c (%Od) radix %Od, is_d %Od != %Od (correct)\n",
                  i, i, radix, is_d, is_d_shadow );
              num_errs++;
              if ( num_errs > err_limit ) <u>$finish(2);</u>
              continue;
           end
           if ( is_d_shadow && dval != digit_vals[i] ) begin
              <u>$write</u>
                 ("Error in aa_digit_val for char %c (%0d) radix %0d: val %0d != %0d (correct)\n",
                  i, i, radix, dval, digit_vals[i]);
              num_errs++;
              if ( num_errs > err_limit ) <u>$finish(2);</u>
              continue;
           end
        end
      done = 1;
   end
endmodule
module aa_test_width2 #( int radix = 10 )
   ( output logic done, input uwire start );
   localparam int err_limit = 10;
   localparam int max_digits = 2;
   localparam int max_dno = max_digits - 1;
   localparam int num_tests = 100;
   uwire [max dno:0][7:0] sum;
   logic [max dno:0][7:0] a, b, shadow sum;
   uwire
                CO;
   logic
                fo, ci, fi;
   aa_width2 #(radix) fal(sum[1:0],co,fo,a[1:0],b[1:0],ci,fi);
   int unsigned aval, bval, ssum_val;
   int num_errs;
```

```
initial begin
   num_errs = 0;
   wait ( start == 1 );
   for ( int i=0; i<num_tests; i++ )</pre>
     begin
        automatic int width = max_digits;
        aval = {<u>$random()</u>} >> 1;
        bval = {<u>$random()</u>} >> 1;
        ssum_val = aval + bval;
        a = radtos(aval,radix);
        b = radtos(bval,radix);
        shadow_sum = radtos(ssum_val,radix);
        ci = 0;
        fi = 1;
        #1;
        if ( sum !== shadow_sum ) begin
           $write("Error %s + %s != %s (%s correct).\n",
                   a,b,sum,shadow_sum);
            num_errs++;
            if ( num_errs > err_limit ) <u>$finish(2);</u>
        end
        #1;
     end
   done = 1;
end
```

endmodule

// cadence translate_on

LSU EE 4755

Homework 3 solution Due: 28 September 2016

Problem 1: Module aa_digit_val, below, is the solution to Homework 2 Problem 1. It has an 8-bit input char and two outputs. Output is_dig is 1 iff char (an ASCII character) is considered a radix-R digit, where $2 \le R \le 16$, is the value of parameter radix. Output val is the value of that digit (in binary), or zero if it's not a digit.

```
module aa_digit_val
```

```
#( int radix = 10 )
( output uwire [3:0] val, output uwire is_dig, input uwire [7:0] char );
uwire is_dig_09 = char >= "0" && char <= "9";
uwire is_dig_af = char >= "a" && char <= "f";
uwire [3:0] val_raw = is_dig_09 ? char - "0" : char - "a" + 10;
assign is_dig = ( is_dig_09 || is_dig_af ) && val_raw < radix;
assign val = is_dig ? val_raw : 0;</pre>
```

endmodule

Provide sketches of what you expect the inferred hardware to look like for aa_digit_val as described below. *Hint: Some problems in the EE 4755 2014 Final Exam dealt with numbers in ASCII representation. The optimizations requested below must go beyond those found in the exam solution.*

(a) Show a sketch of the inferred hardware before any optimization is done. Solution appears below. Items in *italic* are constants.



(b) Show a sketch of the inferred hardware after some optimization has been performed.

- The sketches must show the product of human thought (in particular, the human who's name is on the submission), not a synthesis program.
- When considering the optimizations for the logic generating is_dig (including the logic for is_dig_09 and is_dig_af) recall that in general the cost of logic computing a==b is less than the cost of logic computing a>b.
- When considering the optimizations for the logic generating val think about the subtraction operations and what they actually do when is_dig is true. If necessary, work out examples of the subtraction by hand in hexadecimal.

Solution appears below. The optimization to avoid some magnitude comparison when computing is_dig_09 is based on the fact that the ASCII values of characters "0" to "9" are 0x30 to 0x39 and so one can check whether the most-significant four bits are equal to 0x3 and only do a single magnitude comparison on the lower four bits. Similarly, the optimization of is_dig_af is based on the fact that the ASCII values of "a" to "f" are 0x61 to 0x67, and so one can check whether the five most significant bits are 01100_2 and whether the low three bits are neither 000_2 nor 111_2 .

The logic computing the value of "0" to "9" just takes the low four bits of char, no arithmetic is performed. The logic computing the value of "a" to "f" adds 1 to the low three bits of char and puts a 1 in the MSB position to make a four-bit quantity.



There is another problem on the next page!

Problem 2: Module aa_full_adder from Homework 2, Problem 2 adds together two digits of a radix-R number represented in ASCII plus a carry in. The module description from the solution appears below.

```
module aa_full_adder
  #( int radix = 10 )
   ( output uwire [7:0] sum, output uwire carry_out, output uwire is_dig_out,
     input uwire [7:0] a, b, input uwire carry_in, input uwire is_dig_in);
  uwire [3:0] val_a, val_b;
               is_dig_a, is_dig_b;
  uwire
  aa_digit_val #(radix) dva(val_a, is_dig_a, a);
  aa_digit_val #(radix) dvb(val_b, is_dig_b, b);
  assign is_dig_out = is_dig_in && ( carry_in || is_dig_a || is_dig_b );
  uwire [4:0] sum_val = carry_in + val_a + val_b;
              carry_out = sum_val >= radix;
  assign
  uwire [3:0] sum_dig_val = carry_out ? sum_val - radix : sum_val;
  assign sum = !is_dig_out ? " " :
          sum_dig_val < 10 ? "0" + sum_dig_val : "a" + sum_dig_val - 10;</pre>
```

endmodule

An obvious objection to an ASCII-coded radix-R adder is that it uses 8 bits to represent a digit that can be represented using only $\lceil \lg R \rceil$ bits.

(a) Show the hardware that might be synthesized for the module **aa_full_adder** based on the description above. This should be the inferred hardware with some optimizations applied. Take care to show the number of bits at the inputs and output of units like adders and comparison logic.

Solution appears below. Several optimizations were applied. The logic computing sum_val >= radix was eliminated, instead the logic computing sum_val - radix was widened to five bits, if the difference is positive then sum_val >= radix is true. If the radix is a power of two this logic would not be needed at all, an overflow can be detected by examining one bit position and sum_val - radix would simply be the least significant $\lg R$ bits, where R is the radix.

To save multiplexor cost, the 4 LSB of sum were computed separately from the 4 MSB. Note that the four possible values for the 4 MSB, 0x2 (for a space), 0x3 (for digits 0-9), and 0x6 (for digits a-f), can be easily be constructed from is_dig_out and sum_dig_val<10.

Note that only one adder is needed to compute the sum of the two digit values and the carry in, that's because the module's carry in value can go in to the adder's carry in input. It would be very wasteful to show a second adder just to add the carry in.



(b) Compare the cost of a *d*-digit ASCII-coded radix-16 adder to a 4*d*-bit ripple adder. (Note that both adders can add numbers in the range of 0 to $2^{4d} - 1$.) Do so by estimating the cost in terms of the number of gates, and state any assumptions, such as the number of gates needed for an *x*-bit comparison unit.

The following cost model will be used. All x-input AND and OR gates have a cost of x - 1. Inverted inputs and outputs (those little circles) are free! Inverters are also free. A 2-input XOR cost 3 units and a 3-input XOR cost 5 units.

Based on those costs, a binary full adder cost 10 units and a n-bit ripple adder cost 10n units. A comparison unit can be made from a ripple adder by eliminating the sum bits, and would cost 5n units. An equality unit made from an XOR and an AND costs 4n for n bits. (The difference in cost between equality and magnitude is larger for lower-delay designs.) A w-bit, 2-input multiplexor cost 3w units.

In many of the adder, equality, and comparison units one of the inputs is constant. That has a big impact on cost. The cost of an n-bit ripple adder drops to 4n units (the BFA has a 2-input XOR and a 2-input AND gate to propagate the carry). With one input constant n-bit magnitude comparison and equality drop in cost to just n units.

When radix is 16, the aa_digit_val module will be simplified further. The val_raw<radix comparison is no longer necessary. Based on that the cost is (+ 4 4 1 3 5 1 1 0 16 12 0 4); = 51 units. The aa_full_adder module instantiates two of these and has plenty of logic of its own. The cost including the instantiated modules is (+ 51 51 2 1 40 4 12 12 4 1 4); = 182 units. (Figuring out the LISP syntax and attaching the costs to parts is left as an exercise to the reader.)

Based on this, the cost of a d-digit ASCII adder is 182d units. The equivalent ripple adder costs just 40d units. Sure, we expected the ASCII adder to cost more, but over $4 \times$ more? Notice that a big part of the ASCII adder's cost are the two aa_digit_val modules, 112d units.

LSU EE 4755

Homework 4 solution Due: 12 October 2016

Problem 0: First, follow the instructions for account setup and homework workflow on the course procedures page, https://www.ece.lsu.edu/koppel/v/proc.html.

Look through the code in hw04.v. Module lookup_behav in file hw04.v has a w-bit input char and an *n*-element array of w-bit quantities named chars. (Parameter nelts is *n* and parameter charsz is w.) The module also has a 1-bit output found which is logic 1 iff any element of chars is equal to char. Finally, the module has a $\lceil \lg n \rceil$ -bit output index which is set to the element number of chars that matches char, or 0 if found is 0. Assume that no two elements of chars are identical.

For example, suppose input char is set to 102 and that chars is $\{63, 124, 102, 92\}$. Then output found will be 1 and index will be 2. If char were 7 index would be 0 and found would be 0, if char were 63 index would be 0 and found would be 1, etc. The alert student will have recognized that n = 4 and that w > 7 in these examples.

Module lookup is coded in synthesizable behavioral form that describes combinational logic. The hw04.v file contains two other modules which are to do the same thing, lookup_linear and lookup_tree, but those modules are not yet finished.

The testbench tests all of these modules. It tests them for sizes (n) of 4, 5, 10, 15, 16, 30, 40, and 64. To change which sizes are tested (or the order in which they are tested) edit the **testbench** module.

To have the testbench test only some of these modules (say, skip the lookup_tree tests until after lookup_linear is working) look for the for loop with mut=0 and modify it appropriately. (It should be easy to figure out the numbers.)

A synthesis script is provided that will synthesize all three modules at different sizes and both with and very lax timing constraint and a very strict timing constraint. The script can be run using the command rc -files syn.tcl. Initially it will stop with an error. To see it run to completion before starting the assignment have it only synthesize lookup_behav (see below). Pre-set synthesis options (in file .synth_init) were chosen to reject any design that is not combinational.

If there is an error when using the synthesis script then follow the manual synthesis steps on the procedures page and look for error messages.

To change which modules are synthesized edit the set modules line (near the bottom) in file syn.tcl. The values for nelts and other items can also be changed by editing the file.

Note: There are no points for this problem.

Problem 1: Complete lookup_linear so that it does the same thing as lookup_behavioral but by using as many copies of lookup_elt as it needs. That is, lookup_linear should use generate statements to instantiate lookup_elt and it should include whatever other code is needed to use these instances to compute the correct outputs.

- Behavioral or structural code can be used.
- The module must be synthesizable.
- Assume that all elements of chars are different.

(The complete solution Verilog code is in the assignment directory and at

https://www.ece.lsu.edu/koppel/v/2016/hw04-sol.v.html.) There are two approaches to solving this problem. In the easy approach, which is sufficient to get full credit, generate statements are used to instantiate the lookup_elt modules but behavioral code is used to compute index.

In the alternative solution (lookup_linear_alt), generate statements are used both to instantiate the modules and compute index. To compute index an array of wires, [idx_sz-1:0]idx_i[nelts-1:-1] is declared. Element idx_i[i] is the value of index taking into account elements 0 to i.

```
module lookup_linear
  #( int charsz = 8,
    int nelts = 15, // Pronounced en-elts.
    int idx_sz = $clog2(nelts) )
   ( output logic found,
     output logic [idx_sz-1:0] index,
     input uwire [charsz-1:0] char,
     input uwire [charsz-1:0] chars[nelts-1:0] );
   /// SOLUTION – Easy
   11
   // Instantiate nelts modules, but use use behavioral code to examine
   // their found (match) outputs.
   // Declare wires to connect to the found outputs of the instantiated modules.
   11
   uwire
            [nelts-1:0] match;
   for ( genvar i=0; i<nelts; i++ )</pre>
     lookup_elt #(charsz) le(match[i],char,chars[i]);
   always_comb begin
      found = 0;
      index = 0;
      for ( int i=0; i<nelts; i++ )</pre>
        if ( match[i] ) begin index = i; found = 1; end
   end
```

endmodule

```
module lookup linear alt
  #( int charsz = 8,
     int nelts = 15, // Pronounced en-elts.
     int idx_sz = $clog2(nelts) )
   ( output logic found,
     output logic [idx_sz-1:0] index,
     input uwire [charsz-1:0] char,
     input uwire [charsz-1:0] chars[nelts-1:0] );
   /// SOLUTION – Alternative
   11
   // Use generate statements to instantiate the modules and to
   // generate logic to find the index.
   // Instantiate nelts lookup_elt modules and compute found.
   11
   uwire
            [nelts-1:0] match;
   for ( genvar i=0; i<nelts; i++ )</pre>
     lookup_elt #(charsz) le(match[i],char,chars[i]);
   assign found = | match;
   // Instantiate logic to find the index of the last matching character.
   11
   uwire [idx_sz-1:0] idx_i[nelts-1:-1];
   assign idx_i[-1] = 0;
   for ( genvar i=0; i<nelts; i++ )</pre>
    // If no match pass along previous idx_i, otherwise replace it with i.
     assign idx_i[i] = match[i] ? i : idx_i[i-1];
            index = idx_i[nelts-1];
   assign
```

endmodule

Problem 2: Complete module lookup_tree so that it performs the lookup using recursive instantiations of itself. Take care so that index is computed efficiently. *Hint: think about how to compute index efficiently when n* (nelts) *is a power of 2, then get the same efficiency for any n.*

If completed correctly, the cost and especially the performance at larger sizes should be better than lookup_behavioral and (unless you did an unexpectedly good job) better than lookup_linear.

- Behavioral or structural code can be used.
- The module must be synthesizable.
- Assume that all elements of **chars** are different.

(The complete solution Verilog code is in the assignment directory and at

https://www.ece.lsu.edu/koppel/v/2016/hw04-sol.v.html.) First, we need to use generate statements to split elaboration into two cases: n = 1, and n > 1. For n = 1 index will always be zero (there's only one element in the array and its index is zero), and found can directly be assigned the expression char == chars[0].

Two solutions will be described. In lookup_tree_simple work is split evenly between the two instantiated modules but this results in a more costly computation of index than is necessary. In lookup_tree, the size (value of nelts) of one instantiated module is forced to be a power of 2, reducing cost.

For n > 1 we need to split the input array, chars, between two instantiated lookup_tree modules and combine their found and index outputs. In lookup_tree_simple the array is split in half, the approach used in the pop_n module presented in class. Objects lo_sz and hi_sz are the sizes of the instantiated modules, note that these are used to compute the number of bits in the index outputs.

Logic is also needed to take the found and index outputs of the two instantiated modules, named lo_f, hi_f, lo_idx, and hi_idx, and compute the found and index outputs of the module. A mistake that many students make when trying to solve this problem is to try to take into account what is happening in all instantiated modules at every level when designing this logic. Instead, just assume that lo_f, hi_f, lo_idx, and hi_idx are correct, and use them to compute found and index. If such logic can be found, then the module will work at any size.

The output found is simply the OR of lo_f and hi_f. If lo_f is 1, then index is lo_idx, but if hi_f is 1 then index is lo_sz + hi_idx. We don't need to worry about both lo_f and hi_f being one (the problem statement said it couldn't happen). If hi_f and lo_f are both O then lo_idx and hi_idx will both be O and index should be set to zero. Therefore, index can be set to hi_f ? lo_sz + hi_idx : lo_idx. That's it for the simple solution.

The problem though was to find a solution that computed index efficiently. Consider the sum $lo_sz + hi_idx$. If lo_sz were chosen to be a power of 2, and $lo_sz \ge hi_sz$ then instead of adding we would just be putting a 1 in bit position lo_bits : {1'b1, hi_idx }. We can re-write this as { hi_f, hi_idx } since this is the case where hi_f is 1. And since hi_f is 1 we know lo_idx is all zeros, so we can use the expression { $hi_f, lo_idx | hi_idx$ }. As the alert student may have realized, that expression also is correct for the case where lo_f is 1 and the case where both are 0. The OR gates are much less expensive than an adder and a multiplexor, even an adder with a constant input.

The code for the two modules appears below, along with the inferred hardware for the second module (that computes index efficiently.)

module lookup_tree_simple

11

```
#( int charsz = 8,
    int nelts = 15,
    int idx_sz = $clog2(nelts) )
( output uwire found,
    output uwire [idx_sz-1:0] index,
    input uwire [charsz-1:0] char,
    input uwire [charsz-1:0] chars[nelts] );
/// SOLUTION - Unoptimized
if ( nelts == 1 ) begin
    assign found = char == chars[0];
    assign index = 0;
end else begin
    // Split the character array between recursive instantiations.
```

```
localparam int lo_sz = nelts / 2;
localparam int lo_bits = $clog2(lo_sz);
localparam int hi_sz = nelts - lo_sz;
localparam int hi_bits = $clog2(hi_sz);
11
// Note that we need to compute lo_bits and hi_bits correctly so
/\!/ that we can declare index connections, lo_idx and hi_idx, of
// the correct size.
uwire
            lo_f, hi_f;
uwire [lo_bits-1:0] lo_idx;
uwire [hi_bits-1:0] hi_idx;
lookup_tree #(charsz,lo_sz) lo( lo_f, lo_idx, char, chars[ 0:lo_sz-1 ] );
lookup_tree #(charsz,hi_sz) hi( hi_f, hi_idx, char, chars[lo_sz:nelts-1]);
           found = lo_f || hi_f;
assign
           index = hi_f ? lo_sz + hi_idx : lo_idx;
assign
```

end

endmodule



```
module lookup_tree
```

```
/// SOLUTION – Preferred
```

```
if ( nelts == 1 ) begin
   assign found = char == chars[0];
   assign index = 0; // Actually, we are assigning a zero-bit vector.
end else begin
   // Make the size of the first lookup_tree (lo) a power of two.
   localparam int lo_bits = idx_sz - 1;
   localparam int lo_sz = 1 << lo_bits;</pre>
   // Compute the size of the second lookup_tree (hi).
   localparam int hi_sz = nelts - lo_sz;
   localparam int hi_bits = $clog2(hi_sz);
   uwire
               lo_f, hi_f;
   uwire [lo_bits-1:0] lo_idx;
   uwire [hi_bits-1:0] hi_idx;
   lookup_tree #(charsz,lo_sz) lo( lo_f, lo_idx, char, chars[ 0:lo_sz-1 ] );
   lookup_tree #(charsz,hi_sz) hi( hi_f, hi_idx, char, chars[lo_sz:nelts-1]);
              found = lo_f || hi_f;
   assign
   if ( lo_bits == 0 ) assign index = hi_f;
                       assign index = { hi_f, hi_idx | lo_idx };
   else
end
```

endmodule

Problem 3: Run the synthesis script and characterize the strengths and weaknesses of each module. (For example, module X has lowest cost for low-speed designs.)

In a follow-on homework assignment additional questions will be asked about these modules.

The cost of the tree solution is almost always lower than the other designs, the performance is usually but not always better. For the low-cost (large delay) configurations behavioral design is usually most expensive, but is less expensive than the linear designs for the high-performance designs.

Note: linear_tree below is linear_tree_simple above,

and linear_tree_opt below is]	linear_tree ab	ove.	
Module Name	Area	Delay	Delay
		Actual	Target
lookup_behav_charsz8_nelts4	9152	927	10000
lookup_linear_charsz8_nelts4	9012	990	10000
lookup_tree_charsz8_nelts4	8916	1026	10000
<pre>lookup_tree_opt_charsz8_nelts4</pre>	8988	952	10000
lookup_behav_charsz8_nelts15	35444	2348	10000
lookup_linear_charsz8_nelts15	34996	2338	10000
lookup_tree_charsz8_nelts15	34280	2606	10000
<pre>lookup_tree_opt_charsz8_nelts15</pre>	33532	2238	10000
lookup_behav_charsz8_nelts32	74648	3691	10000
lookup_linear_charsz8_nelts32	74212	3257	10000
lookup_tree_charsz8_nelts32	70932	2480	10000
<pre>lookup_tree_opt_charsz8_nelts32</pre>	71084	2443	10000
lookup_behav_charsz8_nelts40	94028	3862	10000
lookup_linear_charsz8_nelts40	94288	2585	10000
lookup_tree_charsz8_nelts40	95996	3501	10000
<pre>lookup_tree_opt_charsz8_nelts40</pre>	89292	2778	10000
lookup_behav_charsz8_nelts60	143268	5913	10000
lookup_linear_charsz8_nelts60	141792	5638	10000
lookup_tree_charsz8_nelts60	142828	3963	10000
<pre>lookup_tree_opt_charsz8_nelts60</pre>	138288	3501	10000
lookup_behav_charsz8_nelts4	12304	621	100
lookup_linear_charsz8_nelts4	13344	594	100
lookup_tree_charsz8_nelts4	13280	598	100
lookup_tree_opt_charsz8_nelts4	10888	640	100
lookup_behav_charsz8_nelts15	46896	1136	100
lookup_linear_charsz8_nelts15	47528	1120	100
lookup_tree_charsz8_nelts15	45268	1151	100
<pre>lookup_tree_opt_charsz8_nelts15</pre>	41696	1003	100
lookup_behav_charsz8_nelts32	105032	1247	100
lookup_linear_charsz8_nelts32	108688	1288	100
lookup_tree_charsz8_nelts32	96980	1093	100
<pre>lookup_tree_opt_charsz8_nelts32</pre>	96408	1056	100
lookup_behav_charsz8_nelts40	120132	1523	100
lookup_linear_charsz8_nelts40	131344	1114	100
lookup_tree_charsz8_nelts40	134444	1260	100
<pre>lookup_tree_opt_charsz8_nelts40</pre>	116320	1144	100
lookup_behav_charsz8_nelts60	184892	1726	100
lookup_linear_charsz8_nelts60	210512	1461	100

lookup_tree_charsz8_nelts60	185628	1890	100
lookup_tree_opt_charsz8_nelts60	176544	1500	100

```
//
/// LSU EE 4755 Fall 2016 Homework 4 --- SOLUTION
11
/// Assignment http://www.ece.lsu.edu/koppel/v/2016/hw04.pdf
/// Solution: http://www.ece.lsu.edu/koppel/v/2016/hw04_sol.pdf
`default_nettype none
/// Problem 0
11
// Look over but don't modify this module.
module lookup behav
  #( int charsz = 8,
     int nelts = 15,
     int idx_sz = <u>$clog2</u>(nelts) )
   ( output logic found,
   output logic [idx_sz-1:0] index,
     input uwire [charsz-1:0] char,
     input uwire [charsz-1:0] chars[nelts] );
   always comb begin
      found = 0;
      index = 0;
      for ( int i=0; i<nelts; i++ )</pre>
        if ( chars[i] == char ) begin
          index = i;
           found = 1;
        end
   end
endmodule
/// Problem 1
11
/// Complete lookup_linear so that it does the lookup using instantiated lookup_elt.
11
11
       [<] The code must be synthesizable.</pre>
       [r] The code must synthesize to combinational logic. (No latches.)
//
       [<] Make sure that the testbench does not report errors.</pre>
11
       [...] Can use behavioral or implicit structural code.
11
11
       [~] Do not rename modules or change ports.
module lookup_elt
  #( int charsz = 4 )
   ( output logic match,
    input uwire [charsz-1:0] char_lookup,
     input uwire [charsz-1:0] char elt);
   /// Don't modify this module.
   always_comb match = char_lookup == char_elt;
endmodule
module lookup_linear
  #( int charsz = 8,
     int nelts = 15, // Pronounced en-elts.
   int idx_sz = <u>$clog2</u>(nelts) )
( output logic found,
     output logic [idx_sz-1:0] index,
     input uwire [charsz-1:0] char,
     input uwire [charsz-1:0] chars[nelts-1:0] );
   /// SOLUTION -- Easy
   11
   11
      Instantiate nelts modules, but use use behavioral code to examine
      their found (match) outputs.
   //
   // Declare wires to connect to the found outputs of the instantiated modules.
   11
   uwire
            [nelts-1:0] match;
   for ( genvar i=0; i<nelts; i++ )</pre>
    lookup_elt #(charsz) le(match[i],char,chars[i]);
```

```
always_comb begin
      found = 0;
      index = 0;
      for ( int i=0; i<nelts; i++ )</pre>
        if ( match[i] ) begin index = i; found = 1; end
   end
endmodule
module lookup_linear_alt
 #( int charsz = 8,
     int nelts = 15,
     int idx_sz = <u>$clog2(nelts)</u>)
   ( output logic found,
   output logic [idx_sz-1:0] index,
     input uwire [charsz-1:0] char,
     input uwire [charsz-1:0] chars[nelts-1:0] );
   /// SOLUTION -- Alternative
  //
// Use generate statements to instantiate the modules and to
   // generate logic to find the index.
   // Instantiate nelts lookup elt modules and compute found.
   11
   uwire
            [nelts-1:0] match;
   for ( genvar i=0; i<nelts; i++ )</pre>
    lookup_elt #(charsz) le(match[i],char,chars[i]);
   assign found = | match;
   // Instantiate logic to find the index of the last matching character.
   11
  uwire [idx_sz-1:0]
                       idx_i[nelts-1:-1];
   assign idx_i[-1] = 0;
   for ( genvar i=0; i<nelts; i++ )</pre>
    // If no match pass along previous idx_i, otherwise replace it with i.
assign idx_i[i] = match[i] ? i : idx_i[i-1];
   assign
           index = idx i[nelts-1];
endmodule
/// Problem 2
//
/// Complete lookup_tree so that it does the lookup using recursive
/// instantiations of itself.
```

```
//
// [*] The code must be synthesizable.
// [*] The code must synthesize to combinational logic. (No latches.)
// [*] Make sure that the testbench does not report errors.
// [*] Can use behavioral or implicit structural code.
// [*] Do not rename modules or change ports.
```

module lookup_tree_simple

#(int charsz = 8, int nelts = 15, int idx_sz = <u>\$clog2</u>(nelts)) (output uwire found, output uwire [idx_sz-1:0] index, input uwire [charsz-1:0] char, input uwire [charsz-1:0] chars[nelts]);

/// SOLUTION -- Unoptimized

if (nelts == 1) begin

```
assign found = char == chars[0];
assign index = 0;
```

```
// Split the character array between recursive instantiations.
   //
   localparam int lo_sz = nelts / 2;
localparam int lo_bits = <u>$clog2</u>(lo_sz);
   localparam int hi_sz = nelts - lo_sz;
   localparam int hi_bits = <u>$clog2(hi_sz);</u>
   //
   // Note that we need to compute lo bits and hi bits correctly so
   // that we can declare index connections, lo_idx and hi_idx, of
   // the correct size.
   uwire lo_f, hi_f;
uwire [lo_bits-1:0] lo_idx;
   uwire [hi_bits-1:0] hi_idx;
   lookup_tree #(charsz,lo_sz) lo( lo_f, lo_idx, char, chars[ 0:lo_sz-1 ] );
lookup_tree #(charsz,hi_sz) hi( hi_f, hi_idx, char, chars[lo_sz:nelts-1]);
   assign
                  found = lo_f || hi_f;
                  index = hi_f ? lo_sz + hi_idx : lo_idx;
   assign
   11
   /// Notes:
   // It's okay to use lo_idx if hi_f is false, because if
// lo_f is false too then lo_idy must b
   11
   // This solution is less efficient because an adder is required
   // to compute lo_sz + hi_idx. In the preferred solution lo_sz
// is chosen so that it is always a power of 2, avoiding the
   // need for an addition.
end
```

```
endmodule
```

```
module lookup_tree
#( int charsz = 8,
    int nelts = 15,
    int idx_sz = <u>$clog2</u>(nelts) )
( output uwire found,
    output uwire [idx_sz-1:0] index,
    input uwire [charsz-1:0] char,
    input uwire [charsz-1:0] chars[nelts] );
/// SOLUTION -- Preferred
if ( nelts == 1 ) begin
```

assign found = char == chars[0]; assign index = 0;

```
end else begin
```

```
// Make the size of the first lookup_tree, lo, a power of two.
11
localparam int lo_bits = idx_sz - 1;
localparam int lo_sz = 1 << lo_bits;</pre>
// Compute the size of the second lookup_tree, hi.
11
localparam int hi_sz = nelts - lo_sz;
localparam int hi_bits = <u>$clog2(hi_sz);</u>
uwire lo_f, hi_f;
uwire [lo_bits-1:0] lo_idx;
uwire [hi_bits-1:0] hi_idx;
lookup_tree #(charsz,lo_sz) lo( lo_f, lo_idx, char, chars[ 0:lo_sz-1 ] );
lookup_tree #(charsz,hi_sz) hi( hi_f, hi_idx, char, chars[lo_sz:nelts-1]);
             found = lo_f || hi_f;
assign
if ( lo_bits == 0 ) assign index = hi_f;
                       assign index = { hi_f, hi_idx | lo_idx };
else
11
/// Notes:
11
// Because char can be found in at most one location and because
    index is zero if the char is not found, we can compute
11
```

```
index as:
11
11
//
         index = ( hi_f ? lo_sz : 0 ) + lo_idx + hi_idx;
11
     or even better:
11
//
||
||
||
         index = ( hi_f ? lo_sz : 0 ) + ( lo_idx | hi_idx );
     Because lo_sz is a power of two, and because lo_sz > hi_idx,
//
     lo_sz > lo_idx, and lo_sz >= hi_sz we can use concatenation
//
...
11
11
     to avoid the add:
         index = ( hi_f << lo_bits ) + ( lo_idx | hi_idx );
index = { hi_f, lo_idx | hi_idx };
11
||
||
/// Example:
//
     nelts = 14, lo_sz = 8, lo_bits = 3, hi_sz = 6, hi_bits = 3;
chars = { 100, 101, ..., 113 }
//
11
//
     Suppose: char = 106. We want index = 6.
11
||
||
||
      lo_f = 1, lo_idx = 6 = 3'b110
hi_f = 0, hi_idx = 0.
idx = { 1'b0, 3'b110 + 3'b0 } = { 1'b0, 3'b110 } = 4'b0110 = 6
11
11
     Suppose: char = 112. We want index = 12.
lo_f = 0, lo_idx = 0.
hi_f = 1, hi_idx = 4 = 3'b100
//
11
//
      idx = { 1'b1, 3'b000 + 3'b100 } = { 1'b1, 3'b100 } = 4'b1100 = 12
11
11
```

/// Synthesized Hardware:



end

endmodule

` <i>ifdef xxx</i>			
Module Name	Area	Delay	Delay
		<u>Actual</u>	Target
lookup_behav_charsz8_nelts4	9152	927	10000
lookup_linear_charsz8_nelts4	9012	990	10000
lookup_tree_charsz8_nelts4	8916	1026	10000
lookup_tree_opt_charsz8_nelts4	8988	952	10000
lookup_behav_charsz8_nelts15	35444	2348	10000
lookup_linear_charsz8_nelts15	34996	2338	10000
lookup_tree_charsz8_nelts15	34280	2606	10000
<pre>lookup_tree_opt_charsz8_nelts15</pre>	33532	2238	10000
lookup behav charsz8 nelts32	74648	3691	10000
lookup linear charsz8 nelts32	74212	3257	10000
lookup_tree_charsz8_nelts32	70932	2480	10000
lookup tree opt charsz8 nelts32	71084	2443	10000
lookup behav charsz8 nelts40	94028	3862	10000
lookup linear charsz8 nelts40	94288	2585	10000
lookup tree charsz8 nelts40	95996	3501	10000
lookup tree opt charsz8 nelts40	89292	2778	10000
lookup behav charsz8 nelts60	143268	5913	10000

<pre>lookup_linear_charsz8_nelts60 lookup_tree_opt_charsz8_nelts60 lookup_behav_charsz8_nelts4 lookup_linear_charsz8_nelts4 lookup_tree_opt_charsz8_nelts4 lookup_tree_opt_charsz8_nelts1 lookup_linear_charsz8_nelts15 lookup_tree_opt_charsz8_nelts15 lookup_tree_opt_charsz8_nelts15 lookup_tree_opt_charsz8_nelts15 lookup_linear_charsz8_nelts32 lookup_linear_charsz8_nelts32 lookup_tree_opt_charsz8_nelts32 lookup_tree_opt_charsz8_nelts32 lookup_tree_opt_charsz8_nelts32 lookup_tree_opt_charsz8_nelts32 lookup_linear_charsz8_nelts40 lookup_linear_charsz8_nelts40 lookup_tree_opt_charsz8_nelts40 lookup_tree_opt_charsz8_nelts40 lookup_tree_opt_charsz8_nelts40 lookup_tree_opt_charsz8_nelts40 lookup_tree_opt_charsz8_nelts40</pre>	141792 142828 138288 12304 13344 13280 10888 46896 47528 45268 41696 105032 108688 96980 96408 120132 131344 134444 116320 184892	5638 3963 3501 621 594 598 640 1136 1120 1151 1003 1247 1288 1093 1056 1523 1114 1260 1144 1726	10000 10000 1000 1000 100 100 100 100 1
<pre>lookup_tree_charsz8_nelts40 lookup_tree_opt_charsz8_nelts40 lookup_behav_charsz8_nelts60 lookup_linear_charsz8_nelts60 lookup_tree_charsz8_nelts60</pre>	134444 116320 184892 210512 185628	1260 1144 1726 1461 1890	100 100 100 100 100
cookup_cree_opt_cnarszo_nettsoo	1/0344	100	100

```
`endif
```

/// Testbench Code

// 11 The code below instantiates some of the modules above, // provides test inputs, and verifies the outputs.

//

11 The testbench may be modified to facilitate your solution. Of 11 course, the removal of tests which your module fails is not a

method of fixing a broken module. (One might modify the testbench 11

11

so that the first tests it performs are thoe which make it easier to determine what the problem is, for example, test inputs that //

// are all 0's or all 1's.)

// cadence translate_off

```
function automatic int min( int a, int b );
         min = a \le b ? a : b;
endfunction
```

module testbench();

```
localparam int nelts[] = { 4, 5, 10, 15, 16, 30, 40, 64 };
localparam int nnelts = 8;
logic
           start_done[-1:nnelts];
for ( genvar i = 0; i < nnelts; i++ )</pre>
 testbench_sz #(nelts[i]) aa(start_done[i],start_done[i-1]);
```

initial begin

```
if ( nnelts != nelts.size() ) begin
    <u>$write</u>("Value of nnelts, %0d, different than number of elts in nelts, %0d. (See module testbench.\n",
           nnelts, nelts.size());
    $fatal(1);
end
```

```
start_done[-1] = 1;
```

end

```
endmodule
```

```
module testbench sz
  #( int nelts = 100 )
   ( output logic done, input uwire start );
   localparam int telts = nelts * 2;
   localparam int idx_sz = $clog2(nelts);
   localparam int charsz = 8;
   localparam int charmk = ( 1 << charsz ) - 1;</pre>
   localparam int num_tests = min(nelts,500);
```

 $\leftarrow \rightarrow$ Fall 2016

 $\leftarrow \rightarrow$ Homework 4

```
localparam int stride = nelts/num_tests;
   localparam int nmuts = 3;
   logic [charsz-1:0] char, chars[telts-1:0];
   uwire
                          found[nmuts];
   uwire [idx_sz-1:0] idx[nmuts];
   logic
                         shadow_found;
   logic [idx_sz-1:0] shadow_idx;
   lookup_behav #(charsz,nelts) l00(found[0],idx[0],char,chars[nelts-1:0]);
lookup_linear #(charsz,nelts) l01(found[1],idx[1],char,chars[nelts-1:0]);
   lookup_tree #(charsz,nelts) l02(found[2],idx[2],char,chars[nelts-1:0]);
   string mutnames[] = { "lookup_behav", "lookup_linear", "lookup_tree" };
   int err[nmuts];
   initial begin
      automatic int tot_errors = 0;
      localparam int gap = charmk / telts;
      chars[0] = {<u>$random</u>} % gap;
      for ( int i=1; i<telts; i++ )</pre>
         chars[i] = chars[i-1] + 1 + {<u>$random</u>} % gap;
      for ( int i=0; i<telts; i++ ) begin</pre>
          automatic int idx = {$random} % telts;
{chars[i],chars[idx]} = {chars[idx],chars[i]};
      end
      wait ( start == 1 );
      for ( int i=0; i<num tests; i++ ) begin</pre>
          automatic int idx_try = {<u>$random</u>} % telts;
          char = chars[idx_try];
          shadow_found = idx_try < nelts;</pre>
          shadow_idx = idx_try;
          #1:
          for ( int mut=0; mut<3; mut++ ) begin</pre>
              automatic int cr_fnd = shadow_found === found[mut];
             automatic int cr_idx = shadow_idx === idx[mut];
              if ( cr fnd && ( shadow found == 0 || cr idx ) ) continue;
             if ( err[mut] > 100 ) break;
             $write("Mod %s nelts %0d test %3d char %h: wrong %s. Found %h%s%h (correct) idx %4d %s %4d (correct)\n",
    mutnames[mut], nelts, i, char,
                      cr_idx ? "found" : "index",
                     found[mut],
                     cr_fnd ? "==" : "!=",
                     shadow found,
                     idx[mut], cr fnd ? "!=" : "??", shadow idx);
             err[mut]++;
          end
      end
      for ( int i=0; i<num tests; i++ ) tot errors += err[i];</pre>
      $write("For nelts %0d performed %0d tests, %0d errors found.\n",
              nelts, num_tests, tot_errors);
      done = 1:
   end
endmodule
// cadence translate_on
```
LSU EE 4755

Homework 5 solution Due: 7 November 2016

Problem 0: This first problem provides background on the module used in this assignment. Please read the background and then solve the problems further below. The Verilog source can be found in directory hw05, however for this assignment there is no need to do anything with it.

Module ortho has one input, v, a three-element vector of signed integers, and one output, u, also a three-element vector of signed integers. The output is computed so that u is orthogonal to v in the geometric sense. For those who are rusty on linear algebra, non-zero vectors u and v are orthogonal if $u \cdot v = 0$ or $u_x v_x + u_y v_y + u_z v_z = 0$. Using Verilog notation, u is computed so that u[0]*v[0]+u[1]*v[1]+u[2]*v[2]=0 and at least one element of u is not zero. It does so by finding the smallest element of v, setting the corresponding element in u to zero, swapping the to remaining two elements, and negating one of the two. For example, if v = (4, 7, 55) then the module would set u = (0, 55, -7).

```
module ortho #( int alternative = 1, int w = 32 )
   ( output logic signed [w-1:0] u [3], input wire signed [w-1:0] v [3] );
  logic [1:0] idx_min, idx_a, idx_b;
  always_comb begin
      idx_min = 0;
      for ( int i=1; i<3; i++ ) if ( $abs(v[i]) < $abs(v[idx_min]) ) idx_min = i;</pre>
      idx_a = (idx_min + 1) \% 3;
      idx_b = (idx_min + 2) \% 3;
      if ( alternative == 1 ) begin
         // The loop below is a hint to synthesis program Cadence Encounter 14.28.
         for ( int i=0; i<3; i++ ) u[i] = 0;
         u[idx_min] = 0;
         u[idx_a] = v[idx_b];
         u[idx_b] = -v[idx_a];
      end else if ( alternative == 2 ) begin
         for ( int i=0; i<3; i++ )
           u[i] = idx_min == i ? 0 : idx_a == i ? v[idx_b] : -v[idx_a];
      end else $fatal(1);
   end
```

Important: For all problems below in which hardware is shown:

- Clearly show inputs and outputs of ortho.
- Try to draw diagrams showing all hardware for **ortho** and refer to parts of the diagram in your answers below.

Complete solution appears below. See the problems for detail.



Problem 1: Consider the following part of the module:

```
idx_min = 0;
for ( int i=1; i<3; i++ )
    if ( $abs(v[i]) < $abs(v[idx_min]) ) idx_min = i;</pre>
```

(a) Show the hardware that will be synthesized for this fragment. (Please refer to the entire module when determining what will be synthesized.) Make reasonable optimizations. (See the next subproblem.) In this subpart show abs as a box.

Un-optimized and optimized solution appears below. In the un-optimized solution absolute value units appear at the output of the index operation multiplexors (the multiplexors implementing $v[idx_min]$), whereas in the optimized

solution the absolute value is computed earlier. In the optimized version one index operation mux is removed entirely, in the other an input is eliminated. (See the midterm exam solution.) As shown in Problem 3, the absolute value hardware is shared with the hardware used for negation.







See the solution to the part above.

Problem 2: Consider the part of the module below: Show the hardware that will be synthesized for this code, taking into consideration that idx_min is two bits. *Hint: This is easy. Just consider all possible values of* idx_min.

idx_a = (idx_min + 1) % 3; idx_b = (idx_min + 2) % 3;

Solution appears below. The most important point is that there is no hardware to compute the remainder (modulo), which would be costly, nor are there adders. Drawing a truth table will show that only a single gate is needed.



Problem 3: Show the hardware that will be synthesized for the alternative 2 code, below, after optimization. As with the other problems, take into account the rest of the module. Look for opportunities to optimize $-v[idx_a]$ taking advantage of hardware for abs.

```
for ( int i=0; i<3; i++ )
```

u[i] = idx_min == i ? 0 : idx_a == i ? v[idx_b] : -v[idx_a];

Solution appears below. Since this part needs negation (computing -x) and the hardware computing idx_min needs absolute value, which uses negation, this part computes the absolute value. Negation itself of a 2's complement value is computed by negating the bits and adding one. If the negated value were only needed for an adder, or adder-like hardware, then the adder could be eliminated.



Problem 4: As directed below, estimate the critical path in ortho for a *w*-bit instantiation. Do so using ripple-adder like implementations for absolute value, comparison, and negation. Use the performance model in which *n*-input AND and OR gates have delay $\lceil \lg n \rceil$ units.

(a) Find the critical path using the assumption that in hardware for an expression like a + b < c the delay through the adder must be added to the delay through the comparison unit. The answer should be a function of w.

Solution appears in the diagram below in the upper timing number. See the last part for details.

(b) Find the critical path accounting for the fact that in ripple-like hardware for an expression like a + b < c the low bits of the comparison can start as soon as the low bits of the sum are available. The answer should be a function of w.

Solution appears in the diagram below in the lower timing number. See the last part for details.

(c) Show a sketch of the hardware with an arrow tracing the critical path through the hardware, from input to output. Annotating that arrow with intermediate delays will help in assigning partial credit.

The critical path appears in red in the figure below, the critical path (but not its length) is the same with both timing assumptions. The paired purple boxed numbers give the absolute time that the signal arrives at the labeled wire. The upper of the pair is under the assumption that one piece of ripple-like hardware must completely finish before a subsequent piece of ripple-like hardware can start. The lower number is computed under the correct assumption, that computation starts when data arrives. In the diagram this only affects the first comparison unit.

The delay of each component is shown as an unboxed purple number. The delay of the neg unit is based on a ripple adder constructed with binary half adders. The carry chain consists only of AND gates.

Purple arrows point to wires carrying the critical path, green arrows point to non-critical wires.



```
11
/// LSU EE 4755 Fall 2016 Homework 6
/// PRELIMINARY SOLUTION
11
/// Assignment http://www.ece.lsu.edu/koppel/v/2016/hw06.pdf
 /// Additional Resources
 11
 // Instructions for Account Setup, Verilog, Synthesis, Chipware, Emacs.
         http://www.ece.lsu.edu/koppel/v/proc.html
 11
 11
 11
 // Verilog Documentation
       The Verilog Standard
 11
 11
          http://standards.ieee.org/getieee/1800/download/1800-2012.pdf
        Introductory Treatment (Warning: Does not include SystemVerilog)
  11
  11
         Brown & Vranesic, Fundamentals of Digital Logic with Verilog, 3rd Ed.
  //
  // ChipWare Component Library Documentation
        Documentation for the FP modules (and other) such as CW fp add.
 11
       Look for the link to ChipWare on: <u>http://www.ece.lsu.edu/v/ref.html</u>
 11
 11
// Load Verilog for ChipWare floating-point multiply and add modules.
//
include "/apps/linux/cadence/RC142/share/synth/lib/chipware/sim/verilog/CW/CW fp mult.v"
`include "/apps/linux/cadence/RC142/share/synth/lib/chipware/sim/verilog/CW/CW fp add.v"
`default_nettype none
/// Problem 0
11
// Look over but don't modify these modules.
// cadence translate_off
 /// Non-Synthesizable Mag Module --- Complete, Don't Edit
11
module mag functional
  ( output shortreal mag,
   input shortreal v [3] );
  always comb begin
      shortreal sos;
      sos = 0;
      for ( int i=0; i<3; i++ ) sos += v[i] * v[i];</pre>
      mag = sos;
  end
endmodule
// cadence translate_on
/// Combinational Module --- Complete, Don't Edit
11
module mag_comb
  ( output uwire [31:0] mag,
   input uwire [31:0] v [3] );
   uwire [31:0]
                 vsq[3];
  uwire [7:0]
                 status[5]:
   uwire [31:0]
                  sum01;
                logic [2:0] rnd = 0; // 0 is round toward even.
   localparam
   for ( genvar i=0; i<3; i++ )</pre>
    <u>CW fp mult m1( v[i], v[i], rnd, status[i], vsq[i]); // Product is last!</u>
   <u>CW_fp_add</u> al( vsq[0], vsq[1], rnd, sum01, status[3] );
   CW fp add a2( sum01, vsq[2], rnd, mag, status[4] );
```

```
/// Problem 1
11
/// Complete mag_seq so that it computes mag sequentially, using one
/// fp add and one fp multiply module.
11
11
       [x] Learn to use SimVision *before* wasting hours on simple problems.
       [x] The code must be synthesizable.
11
11
       [x] Make sure that the testbench does not report errors.
       [x] Can use behavioral or implicit structural code.
11
       [x] Do not rename modules or change ports.
11
       [x] Must use exactly one CW_fp_add and one CW_fp_mult.
11
       [x] Assume that data arrives at module inputs late in the clock cycle.
11
// cadence translate_off
class Debug;
   int cycle;
   int test_cyc; // Number of cycles since test began.
   int test_num;
   shortreal vr[3];
   logic [31:0] v[3];
   shortreal magr; // Correct result.
   logic [31:0] mag; // Correct result.
endclass
// cadence translate_on
module mag seq
  ( output uwire [31:0] mag,
    output uwire ready,
    input uwire [31:0] v [3],
    input uwire start,
    input uwire clk );
   // cadence translate_off
   <u>Debug</u> db;
   // cadence translate_on
   localparam logic [2:0] rnd = 0; // 1 is round towards zero.
   uwire [7:0] sm, sa;
   logic [31:0] accum[2];
   uwire [31:0] prod, sum;
   logic [2:0] step;
   /// SOLUTION -- Assign multiplier input.
   11
   uwire [31:0] ma = v[ step ];
                                <u>.b</u>(ma),
   <u>CW_fp_mult</u> m1( .a(ma),
                                            .rnd(rnd), .z(prod), .status(sm));
   <u>CW_fp_add</u> al( .a(accum[0]), .b(accum[1]), .rnd(rnd), .z(sum), .status(sa));
   localparam int last step = 4;
   assign
             ready = step == last_step;
   always_ff @( posedge clk )
     if ( start ) step <= 0;</pre>
     else if ( step < last step ) step <= step + 1;</pre>
   always ff @( posedge clk )
     begin
         case ( step )
           0: accum[0] <= prod; // Save v[0] * v[0].
           /// SOLUTION below.
           1: accum[1] <= prod; // Save v[1] * v[1].
           2: begin
```

```
/// Problem 2
//
/// Complete mag_pipe so that it computes mag in pipelined fashion and
/// has at most one fp operation delay per cycle.
11
       [x] Learn to use SimVision *before* wasting hours on simple problems.
11
11
       [x] The code must be synthesizable.
       [x] Make sure that the testbench does not report errors.
11
       [x] Can use behavioral or implicit structural code.
//
       [x] Do not rename modules or change ports.
11
11
       [x] Choose number of stages to maximize throughput (minimize delay).
       [x] Use as many CW_fp_add and CW_fp_mult modules as needed, but no more.
11
       [x] Assume that data arrives at module inputs late in the clock cycle.
11
module mag pipe
  ( output uwire [31:0] mag,
    input uwire [31:0] v [3],
    input uwire clk );
   // cadence translate off
   Debug db;
   // cadence translate_on
   /// Do not rename nstages. The testbench examines its value and it must be set
   /// correctly.
   // For a vector arriving at cycle t, magnitude will be available at
   // cycle t + nstages.
   localparam int nstages = 4;
   localparam logic [2:0] rnd = 0; // 1 is round towards zero.
   logic [31:0] pl_vsq[1:2][3];
   logic [31:0] pl_sos[2:3];
   uwire [31:0] vsq[3], sum01, sum012;
   uwire [7:0]
                 s[5];
   // Pipeline latches between inputs and stage 0.
   //
   logic [31:0] pl_v[3];
   ///
   /// Logic Within Stages
   111
   // Stage 0: Three Multipliers.
   11
   // Instantiate 3 multipliers. All of these are in stage 0.
   //
   for ( genvar i=0; i<3; i++ )</pre>
     <u>CW_fp_mult</u> m1(.a(pl_v[i]), .b(pl_v[i]),
                   .rnd(rnd), .z(vsq[i]), .status(s[i]));
   // Stage 1: An adder.
   //
   <u>CW_fp_add</u> a1( pl_vsq[1][0], pl_vsq[1][1], rnd, sum01, s[3] );
   // Stage 2: Another adder.
```

```
\leftarrow \rightarrow Fall 2016 \leftarrow \rightarrow Homework 6
```

```
//
<u>CW_fp_add</u> a2( pl_sos[2], pl_vsq[2][2], rnd, sum012, s[4] );
111
/// Pipeline Latches (Registers Separating Stages)
111
always ff @( posedge clk ) begin
   // Module input -> Stage 0
   pl_v <= v;
   // Stage 0 -> 1
   11
   // Result of multiplications done in stage 0.
   11
   pl_vsq[1] <= vsq; // Note: vsq is a 3-element array of 32-bit vals.</pre>
   // Stage 1 -> 2
   //
   // Pass along multiplications done in stage 1.
   pl_vsq[2][2] <= pl_vsq[1][2];</pre>
   //
   // Sum performed in stage 1.
   11
   pl sos[2] <= sum01;</pre>
   // Stage 2 -> 3
   11
       Sum performed in stage 2.
   11
   11
   pl_sos[3] <= sum012;</pre>
end
assign mag = pl sos[3];
```



```
\leftarrow \rightarrow Fall 2016 \leftarrow \rightarrow Homework 6
```

```
11
11
   The code below instantiates some of the modules above,
    provides test inputs, and verifies the outputs.
11
11
// The testbench may be modified to facilitate your solution. Of
// course, the removal of tests which your module fails is not a
// method of fixing a broken module. (One might modify the testbench
// so that the first tests it performs are thoe which make it easier
// to determine what the problem is, for example, test inputs that
// are all 0's or all 1's.)
// cadence translate_off
function automatic real rand_real(real minv, real maxv);
      rand real = minv + ( maxv - minv ) * ( real'({<u>$random</u>}) ) / 2.0**32;
endfunction
function automatic shortreal fabs(shortreal val);
      fabs = val < 0 ? -val : val;</pre>
endfunction
program reactivate
   (output uwire clk_reactive, output int cycle_reactive,
    input uwire clk, input var int cycle);
   assign clk reactive = clk;
   assign cycle_reactive = cycle;
endprogram
module testbench();
   typedef enum { MT_comb, MT_seq, MT_pipe } Module_Type;
   localparam int wid = 32;
   localparam int max_latency = 10;
   localparam int num_tests = 16;
   localparam int nmuts = 10;
   int err[nmuts];
   uwire [31:0] mag[nmuts];
   uwire
                 ready[nmuts];
   shortreal
               magr;
   shortreal vr[3];
   logic [31:0] v[3];
   logic [31:0] vp[3];
   logic
                start;
   typedef struct
     {
      int idx;
      int err_count = 0;
      int ncyc = 0;
      Module Type mt = MT_comb;
      logic [wid-1:0] sout = 'h111;
      int cyc_tot = 0;
      int latency = 0;
      } Info;
   Info pi[string];
   localparam int cycle limit = num tests * max latency * 4;
   int cycle, cyc_start;
   bit done;
   logic clock;
   bit use others;
   logic
              clk_reactive;
   int cycle reactive;
   reactivate ra(clk_reactive,cycle_reactive,clock,cycle);
   task pi seq(input int idx, input string name);
      automatic string m = <u>$sformatf("%s", name</u>);
```

```
pi[m].idx = idx; pi[m].mt = MT_seq;
endtask
task pi_pipe(input int idx, input string name, input int ncyc);
   automatic string m = <u>$sformatf("%s", name);</u>
   pi[m].idx = idx; pi[m].mt = MT_pipe;
   pi[m].ncyc = ncyc;
endtask
Debug db;
initial db = new;
initial begin
   clock = 0;
   cycle = 0;
   fork
       forever #10 begin
          cycle += clock++;
          db.cycle = cycle;
          db.test_cyc = cycle - cyc_start;
      end
      wait( done );
      wait( cycle >= cycle_limit )
         $write("*** Cycle limit exceeded, ending.\n");
   join_any;
   $finish();
end
mag_functional mf( magr, vr );
mag_comb m1( mag[0], v );
initial pi["Comb."].idx = 0;
mag_seq m2( mag[1], ready[1], v, start, clock );
initial begin pi_seq(1,"Seq."); m2.db = db; end
mag_pipe m4( mag[3], vp, clock );
initial begin pi_pipe(3,"Pipe",m4.nstages); m4.db = db; end
initial begin
   while ( !done ) @( posedge clk reactive ) #2
      if ( use_others ) begin
          vp = v;
          use_others = 0;
          start = 1;
      end else begin
          vp[0] = <u>$shortrealtobits(shortreal'(cycle-cyc_start));</u>
          vp[1] = cycle - cyc_start;
          vp[2] = 0;
          start = 0;
      end
end
initial begin
   automatic int tot_errors = 0;
   done = 0;
   use_others = 0;
   start = 0;
   @( posedge clk_reactive );
   for ( int i=0; i<num_tests; i++ ) begin</pre>
      automatic int awaiting = pi.num();
      db.test_num = i;
```

```
\leftarrow \rightarrow Fall 2016
                                                   Homework Sol Code
                    \leftarrow \rightarrow Homework 6
             cyc_start = cycle;
             db.test_cyc = 0;
             if (i < 8) begin
                 // In first eight test vector components are zero or one.
                 11
                 for ( int j=0; j<3; j++ ) vr[j] = i & 1 << j ? 1.0 : 0.0;</pre>
             end else begin
                 // In other tests vector components are randomly chosen.
                 11
                 for ( int j=0; j<3; j++ ) vr[j] = rand real(-10,+10);</pre>
             end
             for ( int j=0; j<3; j++ ) v[j] = <u>$shortrealtobits(vr[j]);</u>
             db.vr = vr;
             db.v = v;
             fork
                 #0 begin
                    db.magr = magr;
                    db.mag = <u>$shortrealtobits</u>(magr);
                 end
             join_none
             vp = v;
             use_others = 1;
             /// Collect Result (mag) From Each Module Under Test (mut)
             11
             foreach ( pi[muti] ) begin
                 automatic string mut = muti; // Informal name of module.
                 automatic Info p = pi[mut];
                 // Create a child thread to get response from current mut.
                 // The parent thread, without delay, proceeds to join_none.
                 11
                 fork begin
                    automatic int steps = pi[mut].ncyc;
                    automatic int latency =
                     pi[mut].mt == MT_comb ? 1 :
                     pi[mut].mt == MT_seq ? 2 : steps;
                    // Compute time at which result should be ready or
                    // when to start examining a READY output.
                    11
                    automatic int eta = 1 + cyc_start + latency;
                    pi[mut].latency = latency;
                    // Wait (just this thread waits) until result should be ready.
                    11
                    wait ( cycle reactive == eta );
                    // If this module has a READY output, wait for it.
                    11
                    if ( pi[mut].mt == MT_seq ) wait( ready[pi[mut].idx] );
                    // Decrement count of the number of modules we are waiting for.
                    11
                    awaiting--;
                    // Store the module MAG output, it will be checked later
                    // for correctness.
                    11
                    pi[mut].sout = mag[pi[mut].idx];
                    pi[mut].cyc_tot += cycle - cyc_start;
                    // This thread ends execution here.
```

```
end join_none;
         end
         // Wait until data collected from all modules under test.
         11
         wait ( awaiting == 0 );
         // Check the output of each Module Under Test.
         11
         foreach ( pi[ mut ] ) begin
            // Assign module output to a shortreal.
            11
            automatic shortreal mmagr = <u>$bitstoshortreal(pi[mut].sout);</u>
            //
            // Note: pi[mut].sout is type logic which is assumed to be
            // an unsigned integer. However, the contents is really an
            // IEEE 754 single-precision float (shortreal in
            // SystemVerilog) and so $bitstoshortreal is used so that
            // pi[mut].sout is copied bit-for-bit unchanged to mmagr.
            // Compute difference between module output and expected
            // output. With FP small differences can be okay, they might
            // occur, for example, due to differences in the order of
            // operations.
            11
            automatic shortreal err mag = fabs( mmagr - magr );
            automatic bit okay = err mag < 1e-4;
            if ( !okay ) begin
              pi[mut].err_count++;
if ( pi[mut].err_count < 5 )</pre>
                $write("%s test #%0d vec (%.1f,%.1f,%.1f) error: h'%8h %7.4f != %7.4f (correct)\n",
                   mut, i, vr[2], vr[1], vr[0],
                       pi[mut].sout, mmagr, magr);
           end
         end
         while ( {$random} & 1 == 1 ) @( posedge clk_reactive );
         11
         // Note: By waiting for reactive clock we can be sure that
         // modules under test have completed all work due to the
         // positive edge of the regular clk. Wait a random amount of
         // time in case any modules are only correct at some stride.
      end
      foreach ( pi[ mut ] )
        <u>$write</u>("Ran %4d tests for %-25s, %4d errors found. Avg cyc %.1f\n",
               num tests, mut, pi[mut].err count,
               pi[mut].mt == MT comb ? 1 : real'(pi[mut].cyc tot) / num tests);
      done = 1;
      $finish(2);
   end
endmodule
// cadence translate on
```

23 Fall 2015 Solutions

LSU EE 4755 Homework 1 solution Due: 9 September 2015

The questions below can be answered without using EDA software, paper and pencil will suffice. Please turn in the solution on paper. Homework 2 will require the use of Verilog implementations.

Those who are rusty about the correspondence between Verilog code and hardware might want to look at the solution to EE 3755 Fall 2013 Homework 1, at http://www.ece.lsu.edu/ee3755/2013f/hw01_sol.pdf.

Problem 1: The routine shift_right_fixed_amt uses the >> operator to perform the right shift. Perhaps you are wondering if the operation is an arithmetic right shift or a logical right shift. (In a logical right shift the vacated bit positions are always set to zero, in an arithmetic shift they are set to the MSB of the input.) Look up the operation performed by this operator in the SystemVerilog 2012 documentation.

```
module shift_right_fixed_amt
#( int fsamt = 4 ) // Fixed shift amount.
( output wire [15:0] shifted,
    input wire [15:0] unshifted,
    input wire shift );
// If shift is true shift by fsamt, otherwise don't shift.
//
assign shifted = shift ? unshifted >> fsamt : unshifted;
```

endmodule

(a) Indicate the section and page in which this information can be found. Section 11.4.10, on page 233.

(b) Show how the module can be modified to perform the other kind of shift (if it's currently arithmetic, make it logical, if it's currently logical make it arithmetic).

Two changes need to be made: The type of the value to be shifted must be changed to signed, and the operator must be changed from >> to >>>. The changed code appears below.

```
module shift_right_fixed_amt_sol
#( int fsamt = 4 ) // Fixed shift amount.
  ( output wire [15:0] shifted,
    input wire signed [15:0] unshifted, // SOLUTION, change to signed.
    input wire shift );
  // SOLUTION, change ">>" operator to ">>>".
  //
  assign shifted = shift ? unshifted >>> fsamt : unshifted;
```

Problem 2: Appearing below are two variations on a min_4 module that finds the minimum of four unsigned integers. Both of these modules instantiate the following min_2 module.

```
module min_2
#( int elt_bits = 4 )
  ( output [elt_bits-1:0] elt_min,
      input [elt_bits-1:0] elt_0,
      input [elt_bits-1:0] elt_1 );
      assign elt_min = elt_0 < elt_1 ? elt_0 : elt_1;
endmodule</pre>
```

(a) Draw a diagram of the hardware that will be synthesized for the min_4_t module below. Your diagram should include two-input multiplexors and a comparison module. To get an idea of what to draw, see the EE 3755 Homework solution mentioned at the top of this assignment.

```
module min_4_t
#( int elt_bits = 4 )
  ( output [elt_bits-1:0] elt_min,
      input [elt_bits-1:0] elts [4] );
wire [elt_bits-1:0] im1, im2;
min_2 #(elt_bits) m1( im1, elts[0], elts[1] );
min_2 #(elt_bits) m2( im2, elts[2], elts[3] );
min_2 #(elt_bits) m3( elt_min, im1, im2 );
endmodule
      Solution appears below.
```

min 4 t m1 m3 min 2 elt min min 2 elt_0 elts[0] elt 0 im1 FF | min elts[1] min elt elt 1 elt 1 < Ð m2 min_2 elt 0 elts[2] im2 ⊕ min elts[3] elt elt 1

(b) Draw a diagram of the hardware that will be synthesized for the min_4_1 module below. Your diagram should include two-input multiplexors and a comparison module.

```
module min_4_1
#( int elt_bits = 4 )
( output [elt_bits-1:0] elt_min,
    input [elt_bits-1:0] elts [4] );
wire [elt_bits-1:0] im1, im2;
min_2 #(elt_bits) m1( im1, elts[0], elts[1] );
min_2 #(elt_bits) m2( im2, im1, elts[2] );
min_2 #(elt_bits) m3( elt_min, im2, elts[3] );
```

endmodule

Solution appears below.



(c) Which of the two modules above would you expect to have lower cost? Which would you expect to be faster? Briefly explain.

The cost of the two modules should be the same. Module min_4_t should be faster because the longest path through the module is through two min_2 modules, whereas in min_4_1 the longest paths is through three min_2 modules.

Problem 3: The module min_4_err below is correct Verilog, but it won't do what we want.

```
module min_4_err
#( int elt_bits = 4 )
  ( output [elt_bits-1:0] elt_min,
      input [elt_bits-1:0] elts [4] );
wire [elt_bits-1:0] im;
min_2 #(elt_bits) m1( im, elts[0], elts[1] );
min_2 #(elt_bits) m2( im, im, elts[2] );
min_2 #(elt_bits) m3( elt_min, im, elts[3] );
```

endmodule

(a) Explain why it's correct Verilog yet provides the incorrect result.

The problem is that the output of m1 and m2 are both connected to the same net, im. This may lead to conflicts, for example, when m1 wants to set bit im[O] to 1 but m2 wants to set it to 0. The simulator will assign an x for such cases. Worse, in m2 an output and an input are connected to the same loop.

(b) Look up uwire in the SystemVerilog standard and explain how that might help catching such errors.

Unlike a net of type wire, a net of type uwire can only be driven by one source. See IEEE Std 1800-2012 Section 6.6.2. A net connected in the same way as im, above, would result in a Verilog compiler error.

Problem 4: Appearing below is yet another variation on min_4, this one attempting to take advantage of a special case by using generate statements. The module is correctly using generate statements to handle a special case. Do you think the synthesized hardware will be less expensive for the special case beyond the reduction in cost for using fewer bits. Hint: Think about what the comparison unit and mux would look like with 1-bit inputs and how such logic can be optimized.

Note: In the original assignment this problem had a typo, which made the Verilog illegal. Further, the phrase above starting "beyond the reduction" was not in the original question, making it difficult to see what was really being asked. The answer below is for the corrected question.

```
module min_4_special1
#( int elt_bits = 4 )
( output [elt_bits-1:0] elt_min,
    input [elt_bits-1:0] elts [4] );
if ( elt_bits == 1 ) begin
    assign elt_min = elts[0] && elts[1] && elts[2] && elts[3];
end else begin
    wire [elt_bits-1:0] im1, im2;
    min_2 #(elt_bits) m1( im1, elts[0], elts[1] );
    min_2 #(elt_bits) m2( im2, im1, elts[2] );
    min_2 #(elt_bits) m3( elt_min, im2, elts[3] );
```

end

endmodule

The special case is, of course, and AND gate and we expect that the synthesis program can easily handle those. When elt_bits is greater than one the synthesis program sees a linear connection of min_2 modules **Problem 5:** The module below handles another special case, in this case the case where the first element is zero.

```
module min_4_special2
#( int elt_bits = 4 )
( output [elt_bits-1:0] elt_min,
    input [elt_bits-1:0] elts [4] );
wire [elt_bits-1:0] im1, im2;
if ( elts[0] == 0 )
    assign elt_min = 0;
else begin
    min_2 #(elt_bits) m1( im1, elts[0], elts[1] );
    min_2 #(elt_bits) m2( im2, im1, elts[2] );
    min_2 #(elt_bits) m3( elt_min, im2, elts[3] );
end
```

endmodule

(a) Explain why the module is illegal Verilog.

The if statement, testing elts[0], is not in procedural code (for example, in an initial or always), and so it will be interpreted as a generate statement. Generate statements can only access elaborate-time constants, such as parameters and variables declared genvar. A module input port, such as elts, is definitely not such a constant and so there is an error.

(b) Explain why what it's trying to do would be unlikely to help within a larger design. *Hint: Think about critical path.*

Suppose that the delay through min_4_special2 when elts [0] ==0 is 1 ns and is 3 ns in other cases. Suppose that the output of min_4_special2 is connected to logic that has another 5 ns of delay. Setting a clock period to 1 + 5 = 6 ns would result in errors when the special case was not present and setting it to 3 + 5 = 8 ns would make the special-case hardware unnecessary.

It's not impossible to take advantage of the special case. To do so external logic would need to detect it (an output indicating the special case could be added to min_4_special2) and there would have to be some advantage for the special case. One possibility is that for the special case results from the external logic would be captured in one cycle, otherwise it would take two cycles.

LSU EE 4755

Homework 2 solution Due: 16 September 2015

The Verilog part of the solution to this assignment can be found in

/home/faculty/koppel/pub/ee4755/hw/2015f/hw02/hw02/hw02-sol.v and a syntax-highlighted version can be found at http://www.ece.lsu.edu/koppel/v/2015/hw02-sol.v.html.

Problem 0: Follow the instructions for account setup and homework workflow on the course procedures page, http://www.ece.lsu.edu/koppel/v/proc.html. Run the testbench on the unmodified file. There should be errors on all but the min_4 (Four-element) module. Try modifying min_4 so that it simulates but produces the wrong answer. Re-run the simulator and verify that it's broken. Then fix it.

Note: There are no points for this problem.

Problem 1: Module min_n has an elt_bits-bit output elt_min and an elt_count-element array of elt_bits-bit elements, elts. Complete min_n so that elt_min is set to the minimum of the elements in elts, interpreting the elements as unsigned integers. Do so using a linear connection of min_2 modules instantiated with a genvar loop. (A linear connection means that the output of instance i is connected to the input of instance i + 1.)

Verify correct functioning using the testbench. Solution appears below.

```
module min_n
#( int elt_bits = 4,
    int elt_count = 8 )
    ( output uwire [elt_bits-1:0] elt_min,
        input uwire [elt_bits-1:0] elts [ elt_count ] );
```

/// SOLUTION

```
// Declare wires to interconnect the instances of min_2 instantiated
// in the genvar loop.
11
uwire [elt_bits-1:0] im[elt_count:0]; // im: Inter-Module
                     im[0] = elts[0];
assign
// Instantiate elt_count-1 min_2 modules. The inputs of the first
// module (i=1) connect to elt[0] and elt[1]. Subsequent modules
// connect to an elt and the module instantiated in the previous
// iteration.
11
for ( genvar i = 1; i < elt_count; i++ )</pre>
 min_2 #(elt_bits) m( im[i], elts[i], im[i-1] );
// Connect the output of the last instance to the module output.
11
assign elt_min = im[elt_count-1];
```

Problem 2: Module min_t is to have the same functionality as min_n. Complete min_t so that it recursively instantiates itself down to some minimum size. The actual comparison should be done by a min_2 module.

Verify correct functioning using the testbench.

Solution appears below. In this solution recursion ends when elt_count is 1, in which case the module output, elts_min is connected directly to the module input, elts[0]. Otherwise two smaller min_t modules are instantiated.

```
module min t
```

```
#( int elt_bits = 4,
  int elt_count = 8 )
 ( output uwire [elt_bits-1:0] elt_min,
   input uwire [elt_bits-1:0] elts [ elt_count-1:0 ] );
/// SOLUTION
if ( elt_count == 1 ) begin
   /\!/ Recursion ends here with one elt. Of course, it is the
   // minimum. (And the maximum, and the average, and the median.)
   11
   assign elt_min = elts[0];
 end else begin
   // If there are at least two elements instantiate two smaller
   // modules.
   // Compute the number of elements to be handled by each
   // module. (Note that elt_count can be odd, which is why we need
   // a separate elt_hi and elt_lo.)
   11
   localparam int elt_hi = elt_count / 2;
   localparam int elt_lo = elt_count - elt_hi;
   // Wires for interconnection of modules.
   uwire [elt_bits-1:0] minl, minh;
   // Recursively declare two modules.
   11
   min_t #(elt_bits,elt_hi) mhi(minl,elts[elt_count-1:elt_lo]);
   min_t #(elt_bits,elt_lo) mlo(minh,elts[elt_lo-1:0]);
   // Combine the output of the two modules above.
   11
   min_2 #(elt_bits) m2(elt_min,minl,minh);
```

end

endmodule

Problem 3: By default the synthesis script will synthesize each module for two array sizes, four

elements and eight elements.

(a) Run the synthesis script unmodified. Use the command rc -files syn.tcl. Explain the differences in performance between the different modules.

The output of the synthesis script appears below.

We should expect the cost and performance of min_n and min_b to be about the since they should synthesize to the same hardware. That can be seen by comparing the if statement in min_b to the assign in min_2: both will synthesize to a multiplexor. The behavioral for loop in min_b and the generate loop in min_n should interconnect those multiplexors in the same way. From the table below we see that the synthesis program output is consistent with our expectations.

We should expect the cost of min_n and min_t to be about the same since they have the same number of comparison units, they are just connected in a different order. But we should expect min_t to be faster since the critical path is through $\log_2 n \min_2$ modules. The delay numbers match our expectations for the eight-element version, but at four elements the linear versions are faster. One reason for this might be that for some reason, the synthesis program is using a higher-cost comparison unit in the linear versions, adding to their cost and improving their performance. In the four-element versions that added performance puts them ahead of the tree version. But for the eight-input versions the tree version is clearly faster.

Possible Test Question: Estimate the critical path in the tree and linear versions of the min units.

The second table below shows the synthesis of the modules at a much higher delay target so that the synthesis program will be optimizing primarily for area. In this case the both the cost and performance differences between the tree and linear versions meet our expectations.

Module Name	Area	Delay	Delay
		Actual	Target
<pre>min_t_elt_bits4_elt_count4</pre>	8592	1416	100
<pre>min_b_elt_bits4_elt_count4</pre>	14360	1367	100
<pre>min_n_elt_bits4_elt_count4</pre>	14360	1367	100
<pre>min_t_elt_bits4_elt_count8</pre>	25536	1935	100
<pre>min_b_elt_bits4_elt_count8</pre>	29460	3712	100
<pre>min_n_elt_bits4_elt_count8</pre>	29460	3712	100
Module Name	Area	Delay	Delay
		Actual	Target
<pre>min_t_elt_bits4_elt_count4</pre>	5180	2413	50000
<pre>min_b_elt_bits4_elt_count4</pre>	5152	3280	50000
<pre>min_n_elt_bits4_elt_count4</pre>	5152	3280	50000
<pre>min_t_elt_bits4_elt_count8</pre>	11784	3609	50000
<pre>min_b_elt_bits4_elt_count8</pre>	12176	7796	50000
<pre>min_n_elt_bits4_elt_count8</pre>	12176	7796	50000

(b) Modify and re-run the synthesis script so that it synthesizes the modules with elt_bits set to 1.

The synthesis program should do a better job on the behavioral and linear models in comparison to the tree model. Why do you think that is? *Hint: The 1-bit minimum module is equivalent to* another common logic component that the synthesis program can handle well. Note: the phrase about the tree model was not in the original assignment.

In the table below we see that with a 1-bit element size all three modules have identical cost and performance.

With a one-bit element size the circuit acts as an AND gate, and this is something the synthesis program can figure out. Since the synthesis program sees that min_n and min_b are performing AND operations it can apply the same kind of tree reduction technique that we incorporated by hand in min_t, and so all modules are the same.

Note that the key insight here is that in the general case the synthesis program could not figure out that the minimum operation is associative, and so it could not apply a tree reduction. But with the element size set to 1, it converted minimum to AND, which it did recognize as associative.

Area	Delay	Delay
	Actual	Target
288	155	100
288	155	100
288	155	100
912	292	100
912	292	100
912	292	100
	Area 288 288 288 912 912 912	Area Delay Actual 288 155 288 155 288 155 912 292 912 292 912 292 912 292 912 292 912 292

11 /// LSU EE 4755 Fall 2015 Homework 2 -- SOLUTION 11 /// Assignment http://www.ece.lsu.edu/koppel/v/2015/hw02.pdf /// Solution http://www.ece.lsu.edu/koppel/v/2015/hw02_sol.pdf /// Instructions: 11 // (1) Find the undergraduate workstation laboratory, room 126 EE 11 Building. 11 // (2) Locate your account. If you did not get an account please E-mail: koppel@ece.lsu.edu 11 11 // (3) Log in to a Linux workstation. The account should start up with a WIMP interface (windows, icons, 11 mouse, pull-down menus) (:-)) but one or two things need 11 to be done from a command-line shell. If you need to brush up 11 on Unix commands follow http://www.ece.lsu.edu/koppel/v/4ltrwrd/. 11 11 // (4) If you haven't already, follow the account setup instructions here: http://www.ece.lsu.edu/koppel/v/proc.html 11 11 // (5) Copy this assignment, local path name /home/faculty/koppel/pub/ee4755/hw/2015f/hw02 11 to a directory ~/hw02 in your class account. (~ is your home 11 directory.) Use this file for your solution. 11 11 // (6) Find the problems in this file and solve them. 11 11 Your entire solution should be in this file. 11 11 Do not change module names. 11 // (7) Your solution will automatically be copied from your account by the TA-bot. 11 /// Additional Resources 11 // Verilog Documentation The Verilog Standard 11 http://standards.ieee.org/getieee/1800/download/1800-2012.pdf 11 11 Introductory Treatment (Warning: Does not include SystemVerilog) 11 Brown & Vranesic, Fundamentals of Digital Logic with Verilog, 3rd Ed. 11 // Account Setup and Emacs (Text Editor) Instructions 11 http://www.ece.lsu.edu/koppel/v/proc.html To learn Emacs look for Emacs tutorial. 11 11 // Unix Help http://www.ece.lsu.edu/koppel/v/4ltrwrd/ 11

// `default_nettype none

```
\leftarrow \rightarrow Fall 2015
                                                  Homework Solution Sol Code
                   \leftarrow \rightarrow Homework 2
    11
          Look over the code below.
    11
          There is nothing to turn in for this problem.
    11
     /// Behavioral elt count-input Minimum Module
    //
    module min b
      #( int elt_bits = 4,
          int elt_count = 8 )
        ( output logic [elt_bits-1:0] elt_min,
          input uwire [elt_bits-1:0] elts[elt_count] );
       always @* begin
```

elt_min = elts[0];
for (int i=1; i<elt_count; i++)
 if (elts[i] < elt_min) elt_min = elts[i];</pre>

end

endmodule

endmodule

```
/// Explicit Structural 4-Input Minimum Module
//
module min_4
#( int elt_bits = 4 )
  ( output uwire [elt_bits-1:0] elt_min,
        input uwire [elt_bits-1:0] elts [4] );

   uwire [elt_bits-1:0] im1, im2;
   min_2 #(elt_bits) m1( im1, elts[0], elts[1] );
   min_2 #(elt_bits) m2( im2, elts[2], elts[3] );
   min_2 #(elt_bits) m3( elt_min, im1, im2 );
```

```
Problem 1 -- SOLUTION
111
11
/// Linear Generate minimum module.
11
   Complete the module.
11
11
11
     [✓] Use a generate loop.
//
     [<] The code must be synthesizable.</pre>
     [v] Make sure that the testbench does not report errors.
11
module min n
```

```
#( int elt_bits = 4,
```

```
int elt_count = 8 )
( output uwire [elt_bits-1:0] elt_min,
    input uwire [elt bits-1:0] elts [ elt count ] );
```

/// SOLUTION

```
// Declare wires to interconnect the instances of min 2 instantiated
// in the genvar loop.
11
uwire [elt_bits-1:0] im[elt_count:0]; // im: Inter-Module
                    im[0] = elts[0];
assign
// Instantiate elt_count-1 min_2 modules. The inputs of the first
// module (i=1) connect to elt[0] and elt[1]. Subsequent modules
// connect to an elt and the module instantiated in the previous
// iteration.
11
for ( genvar i = 1; i < elt_count; i++ )</pre>
  min_2 #(elt_bits) m(im[i], elts[i], im[i-1] );
// Connect the output of the last instance to the module output.
11
            elt min = im[elt count-1];
assign
```

```
/// Problem 2
11
/// Tree Generate minimum module.
11
11
    Complete the module.
11
      [<] Use recursion: the module should instantiate itself or a min_2.</pre>
11
      [<] The code must be synthesizable.</pre>
//
//
      [~] Make sure that the testbench does not report errors.
module min t
 #( int elt bits = 4,
    int elt count = 8 )
   ( output uwire [elt bits-1:0] elt min,
    input [elt bits-1:0] elts [ elt count-1:0 ] );
  /// SOLUTION
  if ( elt count == 1 ) begin
     // Recursion ends here with one elt. Of course, it is the
     // minimum. (And the maximum, and the average, and the median.)
     11
     assign elt min = elts[0];
  end else begin
     // If there are at least two elements instantiate two smaller
     // modules.
     // Compute the number of elements to be handled by each
     // module. (Note that elt_count can be odd, which is why we need
     // a separate elt_hi and elt_lo.)
     11
     localparam int elt hi = elt count / 2;
```

```
← → Fall 2015 ← → Homework 2 Homework Solution Sol Code
localparam int elt_lo = elt_count - elt_hi;
// Wires for interconnection of modules.
uwire [elt_bits-1:0] minl, minh;
// Recursively declare two modules.
//
```

```
min_t #(elt_bits,elt_hi) mhi(minl,elts[elt_count-1:elt_lo]);
min_t #(elt_bits,elt_lo) mlo(minh,elts[elt_lo-1:0]);
```

```
// Combine the output of the two modules above.
//
```

```
min_2 #(elt_bits) m2(elt_min,minl,minh);
```

end

endmodule

/// Testbench Code 11 11 The code below instantiates some of the modules above, 11 provides test inputs, and verifies the outputs. 11 The testbench may be modified to facilitate your solution. Of 11 11 course, the removal of tests which your module fails is not a 11 method of fixing a broken module. (The idea is to put in tests // which make it easier to determine what the problem is, for // example, test inputs that are all 0's or all 1's.)

```
// cadence translate_off
```

module testbench;

```
testbench_sz #(1,4) t0();
testbench_sz #(4,4) t1();
testbench_sz #(8,32) t2();
testbench_sz #(7,17) t3();
```

```
module testbench_sz
#( int elt_bits = 8,
    int elt_count = 80 );
localparam int mut_cnt_max = 5;
logic [elt_bits-1:0] elts[elt_count];
uwire [elt_bits-1:0] elt_m[mut_cnt_max];
struct { int err_cnt = 0; int idx; } md[string];
min_b #(elt_bits,elt_count) m0(elt_m[0],elts);
min_n #(elt_bits,elt_count) m1(elt_m[1],elts);
if ( elt_count == 4 )
    min_4 #(elt_bits) m2(elt_m[2],elts);
min_t #(elt_bits,elt_count) m3(elt_m[3],elts);
localparam int num_tests = 10000;
initial begin
```

```
Homework Solution Sol Code
\leftarrow \rightarrow Fall 2015
                   \leftarrow \rightarrow Homework 2
           md["Linear Generate"].idx = 1;
           md["Tree Generate"].idx = 3;
           if ( elt count == 4 )
             md["Four-Element"].idx = 2;
           for ( int i=0; i<num_tests; i++ ) begin</pre>
              for ( int j=0; j<elt_count; j++ ) elts[j] = <u>$random();</u>
              #1;
              foreach ( md[mut] ) begin
                  if ( elt_m[0] !== elt_m[md[mut].idx] ) begin
                     md[mut].err_cnt++;
                     if ( md[mut].err_cnt < 5 )</pre>
                       <u>$write("Error test %0d for %s, 0x%x != 0x%x (correct)\n",</u>
                                  i, mut, elt_m[md[mut].idx], elt_m[0] );
                  end
              end
           end
```

hw02-sol.v.html

```
foreach ( md[mut] )
    <u>$write</u>("Tests completed for %s at %0d x %0d, error count %0d\n",
        mut, elt_bits, elt_count, md[mut].err_cnt );
```

end

endmodule

// cadence translate_on

LSU EE 4755

Homework 3 solution Due: 7 October 2015

Problem 1: Solve EE 4755 Fall 2014 Midterm Exam Problem 4 and Problem 5. The solutions are available, but please make an honest effort to solve them on your own. See the posted solutions at http://www.ece.lsu.edu/koppel/v/2014/mt_sol.pdf.

Problem 2: The homework Verilog file, hw04.v contains two versions of the sequential shifter used in class, those modules are also reproduced below. Module shift_lt_seq_d_live, is based on the version written during class and module shift_lt_seq_d is the one prepared in advance. Though both work correctly their timing is not identical.

(a) Show the hardware that might be synthesized for each module using the default parameters. Include reasonable optimizations, the initially inferred hardware can be omitted. This should be a human-to-human diagram, don't show the output of a synthesis program.

Note: In the original assignment the parameters for the shift_lt_seq_d_live module were not set as intended, that has been corrected in this version of the homework assignment. Both solutions appear below, they are referred to as the original and intended module. In the intended assignment (this one) both modules have the same parameters, in the original assignment the live module had just one shifter and could shift more bits. The hardware appears below. In shift_lt_seq_d_live the initially inferred multiplexors at the inputs to the ready and shift registers have been replaced by logic gates. The logic computing the next state of ready includes the old value of ready. The old value of ready isn't really needed, but it's shown because it is probably what the synthesis program would have included.



The intended live module appears below:



The original live module appears below:





- The register-to-register delay within the module.
- How far in advance of the positive edge module inputs must become stable.
- How long after the positive edge module outputs will be available.

As with the previous part, this should be done by hand though synthesis tools can be used to help solve the problem.

An answer might look like this: "For register-to-register delay Module A is slower because its critical path has two multipliers, whereas in module B the two multiplications are split between cycles and so at most one multiplier is on the critical path. In module A inputs connect directly to a divider, and so they must arrive long before the positive edge, whereas in module B inputs can arrive just before the positive edge because \ldots " Of course, this question does not have a module A or B, nor does it really have multipliers and dividers.

The following timing will be assumed when comparing the modules. Multiplexor delay is two gate delays from either the select or data inputs. For a two-bit decrementor the x=0, x>0, and x-1 outputs are all 1 gate delay (draw a truth table). A six-bit decrementor is assumed to take two gate delays to compute x=0 and 6 gate delays to compute x-1. Since it's essentially a multiplexor the shift_fixed modules take two gate delays regardless of the shift amount.

An important difference between the live and prepared module, is that the in the live module the shift input to shift_fixed comes from a register output, and so it will be available at the beginning of a the clock cycle. In the prepared module the shift input is generated by checking if a portion of cnt is zero, the check adds a small delay. Though this may sound like a small advantage for the live module, but it may not be because it doesn't use the shift signal until the next clock cycle and so it takes one clock cycle longer to perform the shift. If wid_lg/num_shifters is large than the extra clock cycle will be a small fraction of the total time and so the live module would be better. If the ratio is small the extra clock cycle will make things slower.

For the assigned problem, in which shift_lt_seq_d_live has 1 shifter, the register-to-register critical path in the live module is 10 gate delays, assuming 6 gate delays for the 6-bit subtract. The prepared module, shift_lt_seq_d, module has a critical path of 7 delays. Thus, the live module can have a higher clock frequency—that's the good news—but it will take $\frac{2^6}{2^{4/2}-1} = 21.33$ times as many cycles to perform the largest shift.

A concise answer to the assigned problem might be: the register-to-register delay in the live module is much longer because it must decrement a much larger number, six versus two bits. This overcomes any benefit of having one shifter, versus two in the prepared module.

In the intended problem the live module has the same parameters as the prepared module, including two shifters. In that case the critical path is 6 gate delays, 1 gate delay faster than the prepared module. But because it takes one cycle longer the benefit in clock frequency would not be large enough to overcome the disadvantage of requiring one more clock cycle, at least not for the default parameters.

The two modules have equivalent input setup times, two gate delays. So for both, the inputs can arrive near the end of the clock cycle.

In the live module the outputs are available at the beginning of the clock cycle. In the prepared module the **ready** signal is generated using an AND gate connected to the decrementors. Based on the analysis above, the prepared module's ready output is not available until two gate delays after the clock edge.

Modules on next page.

```
module shift_lt_seq_d_live
  #( int wid_lg = 4, // In original assignment, 6
     int num_shifters = 2, // In original assignment, 1.
     int wid = 1 << wid_lg )</pre>
   ( output logic [wid-1:0] shifted,
     output logic ready,
     input [wid-1:0] unshifted,
     input [wid_lg-1:0] amt,
     input start,
     input clk );
  localparam int bits_per_seg = wid_lg / num_shifters;
  logic [num_shifters-1:0] shift;
  wire [wid-1:0] shin[num_shifters-1:-1];
  assign shin[-1] = shifted;
  for ( genvar i=0; i<num_shifters; i++ ) begin</pre>
      localparam int fs_amt = 2 ** ( i * bits_per_seg );
      shift_fixed #( wid_lg, fs_amt ) sf( shin[i], shin[i-1], shift[i] );
  end
  logic [num_shifters-1:0][bits_per_seg-1:0] cnt;
  always_ff @( posedge clk ) begin
      if ( start == 1 ) begin
         ready = 0;
         cnt = amt;
         shift = 0;
         shifted = unshifted;
      end else begin
         if ( cnt == 0 ) ready = 1;
         for ( int i=0; i<num_shifters; i++ ) begin</pre>
            shift[i] = cnt[i] > 0;
            if ( cnt[i] != 0 ) cnt[i]--;
         end
         shifted = shin[num_shifters-1];
      end
   end
endmodule
```

Another module on next page.

```
module shift_lt_seq_d
  #( int wid_lg = 4,
     int num_shifters = 2,
     int wid = 1 << wid_lg )</pre>
   ( output logic [wid-1:0] shifted,
     output wire ready,
     input [wid-1:0] unshifted,
     input [wid_lg-1:0] amt,
     input start,
     input clk );
   localparam int cnt_bits = ( wid_lg + num_shifters - 1 ) / num_shifters;
   logic [num_shifters-1:0][cnt_bits-1:0] cnt;
   wire [wid-1:0] inter_sh[num_shifters-1:-1];
   assign inter_sh[-1] = shifted;
   for ( genvar i = 0; i < num_shifters; i++ ) begin</pre>
      localparam int shift_amt = 1 << i * cnt_bits;</pre>
                 shift = cnt[i] != 0;
      wire
      shift_fixed #(wid_lg,shift_amt) sf( inter_sh[i], inter_sh[i-1], shift );
   end
   always_ff @( posedge clk )
      if ( start == 1 ) begin
         shifted = unshifted;
         cnt = amt;
      end else if ( cnt > 0 ) begin
         shifted = inter_sh[num_shifters-1];
         for ( int i=0; i<num_shifters; i++ ) if ( cnt[i] ) cnt[i]--;</pre>
      end
   assign ready = cnt == 0;
endmodule
```
LSU EE 4755

Homework 4 Solution Due: 12 October 2015

Problem 0: Follow the instructions for account setup and homework workflow on the course procedures page, http://www.ece.lsu.edu/koppel/v/proc.html. Run the testbench on the unmodified file. There should be errors on the shift_lt_seq_d_sol module, but the others should run correctly. Run the Note: There are no points for this problem.

Problem 1: The homework Verilog file, hw04.v, contains a module shift_lt_seq_d_sol which is based on shift_lt_seq_d. It contains an always_ff block that assigns the same variables that are assigned in shift_lt_seq_d, however it assigns them from variables of the same name with next_ prefixed:

```
always_ff @( posedge clk ) begin
  ready = next_ready;
  shifted = next_shifted;
  shift = next_shift;
  cnt = next_cnt;
end
```

Add code so that these next_ objects will be assigned values from combinational logic, and so that the resulting module describes the same hardware as shift_lt_seq_d. A hand-drawn diagram of synthesized hardware should be identical, though it's possible that there will be small differences in the actual output of a synthesis program.

The added code can be implicit structural or behavioral, but it must synthesize to combinational logic.

The simplest approach is to start with the always_ff block from module shift_lt_seq_d. Change the always type to always_comb and rename some of the objects that are to synthesize to registers, namely ready, shifted, shift, and cnt.

If an assignment is made to any of these in the always_comb block, the assignment must be changed to write the next_version. For example change cnt=amt; to next_cnt=amt;. The right-hand side of an assignment should only use the next_version of a variable if it was assigned earlier in the block. For example, next_shift in the excerpt from the solution below:

```
next_shift[i] = cnt[i] > 0;
next_cnt[i] = next_shift[i] ? cnt[i] - 1 : cnt[i];
```

The code also has to be modified so that each of the next_ variables is assigned at least once no matter what path is taken through the always_comb block. That is, they must be assigned for every possible outcome of the if statements. That's why there is no if statement in the assignment to next_cnt above. (That is, the following would be wrong: if (next_shift[i])next_cnt[i]=cnt[i]-1). (If a variable is not always assigned then its value will come from the output of a latch, rather than from combinational logic.)

The solution uses both continuous assign statements and an **always_comb** block. The complete solution appears below:

```
module shift_lt_seq_d_sol
```

<pre>#(int wid_lg = 4, int num_shifters = 2,</pre>	<pre>int wid = 1 << wid_lg)</pre>
(output logic [wid-1:0] shifted,	output logic ready,
<pre>input [wid-1:0] unshifted,</pre>	<pre>input [wid_lg-1:0] amt,</pre>
input start,	<pre>input clk);</pre>

```
logic [num_shifters-1:0] shift;
```

```
wire [wid-1:0]
                            shin[num_shifters-1:-1];
  localparam int bits_per_seg = wid_lg / num_shifters;
  for ( genvar i=0; i<num_shifters; i++ ) begin</pre>
      localparam int fs_amt = 2 ** ( i * bits_per_seg );
      shift_fixed #( wid_lg, fs_amt ) sf( shin[i], shin[i-1], shift[i] );
   end
  assign shin[-1] = shifted;
  logic [num_shifters-1:0][bits_per_seg-1:0] cnt;
  logic [wid-1:0] next_shifted;
  logic next_ready;
   logic [num_shifters-1:0] next_shift;
   logic [num_shifters-1:0][bits_per_seg-1:0] next_cnt;
   always_comb begin
      if ( start == 1 ) begin
        next_cnt = amt;
         next_shift = 0;
      end else begin
         for ( int i=0; i<num_shifters; i++ ) begin</pre>
            next_shift[i] = cnt[i] > 0;
            // Note that next_cnt is always assigned, this avoids latches.
            next_cnt[i] = next_shift[i] ? cnt[i] - 1 : cnt[i];
         end
      end
   end
   // Use a continuous assignment for next_ready and next_shifted.
   assign next_ready = start ? 0 : cnt == 0 ? 1 : ready;
   assign next_shifted = start ? unshifted : shin[num_shifters-1];
   always_ff @( posedge clk ) begin
      shifted = next_shifted;
     ready = next_ready;
      shift = next_shift;
      cnt = next_cnt;
   end
endmodule
```

Problem 2: Module shift_lt_seq_d_live takes one more cycle to produce a result than module shift_lt_seq_d. Module shift_lt_seq_d_p2 initially is identical to shift_lt_seq_d_live.
(a) Modify shift_lt_seq_d_p2 so that it uses one less cycle to produce a result without changing the number of shifters per stage. There are two possible ways of doing this, performing some work in the same cycle that the start signal arrives, or doing work in the cycle when ready is set to 1. Either method is fine. The original module, shift_lt_seq_d_live, does not start to shift until the cycle after start is set to 1. In the solution the logic generating the shift signal is moved so that it operates at every cycle. That was done by moving the i loop out of the if/else block, the logic generating the ready signal was also moved.

By doing this we are requiring start and amt to arrive early in the cycle. Before the change they could arrive late in the cycle.

```
module shift_lt_seq_d_p2
  #( int wid_lg = 6, int num_shifters = 1, int wid = 1 << wid_lg )</pre>
                                         output logic ready,
   ( output logic [wid-1:0] shifted,
     input [wid-1:0] unshifted,
                                            input [wid_lg-1:0] amt,
     input start,
                                            input clk );
   localparam int bits_per_seg = wid_lg / num_shifters;
   logic [num_shifters-1:0] shift;
   wire [wid-1:0] shin[num_shifters-1:-1];
   assign shin[-1] = shifted;
   for ( genvar i=0; i<num_shifters; i++ ) begin</pre>
      localparam int fs_amt = 2 ** ( i * bits_per_seg );
      shift_fixed #( wid_lg, fs_amt ) sf( shin[i], shin[i-1], shift[i] );
   end
   logic [num_shifters-1:0][bits_per_seg-1:0] cnt;
   always_ff @( posedge clk ) begin
      if ( start == 1 ) begin
         ready = 0;
         cnt = amt;
         shifted = unshifted;
      end else begin
         shifted = shin[num_shifters-1];
      end
      if ( cnt == 0 ) ready = 1;
      for ( int i=0; i<num_shifters; i++ ) begin</pre>
         shift[i] = cnt[i] > 0;
         if ( cnt[i] != 0 ) cnt[i]--;
      end
```

end

endmodule

(b) Run syn.tcl and compare the cost and performance of your design and shift_lt_seq_d_live. Comment on the differences. An answer might start "The cost was about the same because the same hardware was used...".

A table showing area (cost) and timing as reported by the synthesis program appears below. That's followed by a sketch of our guess of the synthesized hardware for each module, along with a timing analysis. These expectations are compared with the output of the synthesis program.

Module Name

shift_lt_seq_d_live_wid_lg6_num_shifters1
shift_lt_seq_d_p2_wid_lg6_num_shifters1
shift_lt_seq_d_live_wid_lg6_num_shifters2
shift_lt_seq_d_p2_wid_lg6_num_shifters3
shift_lt_seq_d_p2_wid_lg6_num_shifters3
shift_lt_seq_d_live_wid_lg6_num_shifters6
shift_lt_seq_d_p2_wid_lg6_num_shifters6

Area	Delay	Delay
	Actual	Target
68368	1253	100
68428	1229	100
77528	1355	100
78700	1348	100
96648	1527	100
95820	1539	100
143412	2002	100
142380	2007	100



To determine the expected area and timing differences between the two modules examine the sketches of the expected synthesized hardware for the two modules, which appears above. The change that enables us to save a cycle is moving the mux that selects a new value of **amt** from the input of **cnt** to the input of the decrement unit. That lets the shifter get started one cycle earlier.

Notice that by moving the hardware to compute **cnt** and **shift** out of the loop we are simplifying the logic at the input to those registers because they no longer have to check **start**. For this reason we would expect the cost to be slightly lower. The costs reported by the synthesis program are close and show no consistent pattern.

The sketches of the expected hardware include a simple timing analysis. The timing analysis is based on an assumed delay of two units for a mux, $\lceil \lg n \rceil$ units for an *n*-input gate and a delay of 3 for a 3-bit decrementor.

Based on this analysis the changes in the p2 module don't affect the path that ends in the **shifted** register, that's the same 6 units in both cases.

Moving the amt mux from cnt to the decrementer inputs does not change the critical path. The move does delay the shift and ready signals by one or two units, but since they are not critical it doesn't matter. When num_shifters is 1 the path ending at cnt remains critical so moving the mux doesn't change anything. When num_shifters is larger the path ending at shifted is critical so moving the mux has no impact.

Based on this analysis we would not expect a change in the clock period. The output of the synthesis program shows only small changes.

The fact that the clock period is about the same is good news for us since one less clock cycle is needed. If the changes increased the clock period we may not actually get higher performance.

```
11
/// LSU EE 4755 Fall 2015 Homework 4
11
/// SOLUTION
/// Assignment http://www.ece.lsu.edu/koppel/v/2015/hw04.pdf
 /// Solution discussion http://www.ece.lsu.edu/koppel/v/2015/hw04_sol.pdf
 /// Instructions:
 11
 // (1) Find the undergraduate workstation laboratory, room 126 EE
 11
         Building.
 11
  // (2) Locate your account. If you did not get an account please
        E-mail: koppel@ece.lsu.edu
 11
 11
  // (3) Log in to a Linux workstation.
 11
        The account should start up with a WIMP interface (windows, icons,
         mouse, pull-down menus) ( :-) ) but one or two things need
 11
        to be done from a command-line shell. If you need to brush up
 11
         on Unix commands follow <a href="http://www.ece.lsu.edu/koppel/v/4ltrwrd/">http://www.ece.lsu.edu/koppel/v/4ltrwrd/</a>.
 11
 11
 // (4) If you haven't already, follow the account setup instructions here:
 11
        http://www.ece.lsu.edu/koppel/v/proc.html
 11
 // (5) Copy this assignment, local path name
         /home/faculty/koppel/pub/ee4755/hw/2015f/hw04
 11
 11
        to a directory ~/hw04 in your class account. (~ is your home
 11
         directory.) Use this file for your solution.
 11
 // (6) Find the problems in this file and solve them.
 11
 11
         Your entire solution should be in this file.
 11
 11
         Do not change module names.
 11
 // (7) Your solution will automatically be copied from your account by
        the TA-bot.
 11
 /// Additional Resources
 11
 // Verilog Documentation
        The Verilog Standard
 11
 11
          http://standards.ieee.org/getieee/1800/download/1800-2012.pdf
        Introductory Treatment (Warning: Does not include SystemVerilog)
 11
          Brown & Vranesic, Fundamentals of Digital Logic with Verilog, 3rd Ed.
 11
 11
 // Account Setup and Emacs (Text Editor) Instructions
         http://www.ece.lsu.edu/koppel/v/proc.html
 11
 11
         To learn Emacs look for Emacs tutorial.
 //
```

// Unix Help 11 http://www.ece.lsu.edu/koppel/v/4ltrwrd/ /// Problem 0 11 /// Shift Left Modules 11 11 Look over the code below. There is nothing to turn in for this problem. 11 11 `default_nettype none module shift_fixed #(int wid_lg = 4, int amt = 1, int wid = 1 << wid_lg)</pre> (output uwire [wid-1:0] shifted, input uwire [wid-1:0] unshifted, input uwire shift); assign shifted = shift ? unshifted << amt : unshifted;</pre>

endmodule

```
module shift_lt_behav
  #( int wid_lg = 4,
     int wid = 1 << wid_lg )</pre>
   ( output uwire [wid-1:0] shifted,
     input uwire [wid-1:0] unshifted,
     input uwire [wid_lg-1:0] amt );
```

assign shifted = unshifted << amt;</pre>

```
module shift_lt_comb
  #( int wid_lg = 4,
     int wid = 1 << wid lg )</pre>
   ( output uwire [wid-1:0] shifted,
     input uwire [wid-1:0] unshifted,
     input uwire [wid_lg-1:0] amt );
   uwire [wid-1:0]
                          step[wid_lg-1:-1];
   assign step[-1] = unshifted;
   assign shifted = step[wid_lg-1];
   for ( genvar i=0; i<wid_lg; i++ )</pre>
     shift_fixed #(wid_lg,1<<i) sf( step[i], step[i-1], amt[i] );</pre>
```

```
module shift_lt_seq
  #( int wid_lg = 4,
     int wid = 1 << wid_lg )</pre>
   ( output logic [wid-1:0] shifted,
     output uwire ready,
     input uwire [wid-1:0] unshifted,
     input uwire [wid_lg-1:0] amt,
     input uwire start,
     input uwire clk );
   logic [wid_lg-1:0] cnt;
   uwire [wid-1:0] sf_out;
   shift fixed #(wid_lg,1) sf( sf_out, shifted, 1'b1 );
   always_ff @( posedge clk ) begin
      if ( start == 1 ) begin
         shifted = unshifted;
         cnt = amt;
      end else if ( cnt > 0 ) begin
         shifted = sf_out;
         cnt--;
      end
   end
   assign ready = cnt == 0;
endmodule
module shift_lt_seq_d
  #( int wid_lg = 4,
     int num_shifters = 2,
     int wid = 1 << wid_lg )</pre>
   ( output logic [wid-1:0] shifted,
     output uwire ready,
     input uwire [wid-1:0] unshifted,
     input uwire [wid_lg-1:0] amt,
     input uwire start,
     input uwire clk );
   localparam int cnt_bits = ( wid_lg + num_shifters - 1 ) / num_shifters;
   logic [num_shifters-1:0][cnt_bits-1:0] cnt;
   uwire [wid-1:0] inter_sh[num_shifters-1:-1];
```

```
\leftarrow \rightarrow Fall 2015
                   \leftarrow \rightarrow Homework 4
                                                Homework Solution Sol Code
       assign inter_sh[-1] = shifted;
       for ( genvar i = 0; i < num_shifters; i++ ) begin</pre>
          localparam int shift_amt = 1 << i * cnt_bits;</pre>
          uwire
                       shift = cnt[i] != 0;
          shift fixed #(wid_lg,shift_amt) sf( inter_sh[i], inter_sh[i-1], shift );
       end
       always_ff @( posedge clk )
          if ( start == 1 ) begin
              shifted = unshifted;
              cnt = amt;
          end else if ( cnt > 0 ) begin
              shifted = inter_sh[num_shifters-1];
              for ( int i=0; i<num_shifters; i++ ) if ( cnt[i] ) cnt[i]--;</pre>
          end
```

hw04-sol.v.html

```
assign ready = cnt == 0;
```

```
/// Problem 1
11
11
    Modify shift_lt_seq_d_sol so that it synthesizes to the same
    hardware as shift_lt_seq_d_live (further below).
11
11
      [<] Be sure that all code that you add synthesizes to</pre>
11
         combinational logic.
11
11
11
     [ / ] Make sure that the module runs correctly.
11
module shift_lt_seq_d_sol
 #( int wid_lg = 4,
    int num_shifters = 2,
```

```
int wid = 1 << wid_lg )
( output logic [wid-1:0] shifted,
  output logic ready,
  input uwire [wid-1:0] unshifted,
  input uwire [wid_lg-1:0] amt,
  input uwire start,
  input uwire clk );</pre>
```

```
← → Fall 2015 ← → Homework 4 Homework Solution Sol Code
logic [num_shifters-1:0] shift;
uwire [wid-1:0] shin[num_shifters-1:-1];
localparam int bits_per_seg = wid_lg / num_shifters;
for ( genvar i=0; i<num_shifters; i++ ) begin
localparam int fs_amt = 2 ** ( i * bits_per_seg );
shift_fixed #( wid_lg, fs_amt ) sf( shin[i], shin[i-1], shift[i] );
end
assign shin[-1] = shifted;
logic [num_shifters-1:0][bits_per_seg-1:0] cnt;
```

```
logic [wid-1:0] next_shifted;
logic next_ready;
logic [num_shifters-1:0] next_shift;
logic [num_shifters-1:0][bits_per_seg-1:0] next_cnt;
```

/// Problem 1: Modify this module, especially around here.

```
/// SOLUTION
11
// Some logic from shift_lt_seq_d has been placed into the
// always comb block and some has been placed in assigns.
// It would be equally correct to put all of the logic in
// an always_comb block (or blocks) or to put all of the logic
// in assign statements. The deciding factor should be on how
// easy it is to read the code.
always_comb begin
   if ( start == 1 ) begin
      next_cnt = amt;
      next shift = 0;
   end else begin
      for ( int i=0; i<num_shifters; i++ ) begin</pre>
         next_shift[i] = cnt[i] > 0;
         // Note that next_cnt is always assigned, this avoids latches.
         next_cnt[i] = next_shift[i] ? cnt[i] - 1 : cnt[i];
      end
```

end

```
\leftarrow \rightarrow Fall 2015
                  \leftarrow \rightarrow Homework 4
                                             Homework Solution Sol Code
       // Use a continuous assignment for next_ready and next_shifted.
       assign next_ready = start ? 0 : cnt == 0 ? 1 : ready;
       assign next_shifted = start ? unshifted : shin[num_shifters-1];
       always_ff @( posedge clk ) begin
          shifted = next_shifted;
          ready = next_ready;
          shift = next_shift;
          cnt = next_cnt;
       end
   endmodule
   module shift_lt_seq_d_live
     #( int wid_lg = 6,
         int num_shifters = 1,
         int wid = 1 << wid_lg )</pre>
       ( output logic [wid-1:0] shifted,
         output logic ready,
         input uwire [wid-1:0] unshifted,
         input uwire [wid_lg-1:0] amt,
         input uwire start,
         input uwire clk );
       /// DO NOT modify this module.
       localparam int bits_per_seg = wid_lg / num_shifters;
       logic [num_shifters-1:0] shift;
       uwire [wid-1:0] shin[num_shifters-1:-1];
       assign shin[-1] = shifted;
       for ( genvar i=0; i<num_shifters; i++ ) begin</pre>
          localparam int fs_amt = 2 ** ( i * bits_per_seg );
          shift fixed #( wid_lg, fs_amt ) sf( shin[i], shin[i-1], shift[i] );
       end
       logic [num_shifters-1:0][bits_per_seg-1:0] cnt;
       always_ff @( posedge clk ) begin
          if ( start == 1 ) begin
             ready = 0;
             cnt = amt;
             shift = 0;
             shifted = unshifted;
          end else begin
```

```
if ( cnt == 0 ) ready = 1;
for ( int i=0; i<num_shifters; i++ ) begin
    shift[i] = cnt[i] > 0;
    if ( cnt[i] != 0 ) cnt[i]--;
end
shifted = shin[num_shifters-1];
end
```

end

endmodule

```
/// Problem 2
11
11
    Modify shift_lt_seq_d_p2 so that it uses one less cycle.
11
11
      [ Make sure that the module runs correctly.
      [.] Don't change the number of shifters per stage.
11
module shift_lt_seq_d_p2
 #( int wid_lg = 6,
    int num shifters = 1,
    int wid = 1 << wid_lg )</pre>
   ( output logic [wid-1:0] shifted,
    output logic ready,
    input uwire [wid-1:0] unshifted,
    input uwire [wid_lg-1:0] amt,
    input uwire start,
    input uwire clk );
  localparam int bits_per_seg = wid_lg / num_shifters;
  logic [num_shifters-1:0] shift;
   uwire [wid-1:0] shin[num_shifters-1:-1];
  assign shin[-1] = shifted;
  for ( genvar i=0; i<num_shifters; i++ ) begin</pre>
     localparam int fs_amt = 2 ** ( i * bits_per_seg );
     shift_fixed #( wid_lg, fs_amt ) sf( shin[i], shin[i-1], shift[i] );
  end
  logic [num_shifters-1:0][bits_per_seg-1:0] cnt;
```

always_ff @(posedge clk) begin

```
if ( start == 1 ) begin
   ready = 0;
   cnt = amt;
   shifted = unshifted;
end else begin
   shifted = shin[num_shifters-1];
end
/// SOLUTION
11
// Set shift and update cnt whether or not start==1.
11
if ( cnt == 0 ) ready = 1;
for ( int i=0; i<num_shifters; i++ ) begin</pre>
   shift[i] = cnt[i] > 0;
   if ( cnt[i] != 0 ) cnt[i]--;
end
```

end

endmodule

endprogram

```
/// Testbench Code
//
// Testbench Code
//
// The code below instantiates some of the modules above,
// provides test inputs, and verifies the outputs.
//
// The testbench may be modified to facilitate your solution. Of
// course, the removal of tests which your module fails is not a
// method of fixing a broken module. (The idea is to put in tests
// which make it easier to determine what the problem is, for
// example, test inputs that are all 0's or all 1's.)
// cadence translate_off
program reactivate(output uwire clk_reactive, input uwire clk);
    assign clk_reactive = clk;
```

```
\leftarrow \ \rightarrow \ {\rm Fall} \ 2015 \qquad \ \leftarrow \ \rightarrow \ {\rm Homework} \ 4
```

```
module testbench;
   localparam int wid lg = 6;
   localparam int wid = 1 << wid_lg;</pre>
   localparam int max_units = 20;
   logic
            clk;
   bit
              done;
   int cycle;
   uwire [wid-1:0] sout[max_units];
   uwire ready[max_units];
   logic [wid-1:0] sin;
   logic [wid_lg-1:0] amt;
   logic
                      start;
   typedef struct { int idx; int err_count = 0; bit seq = 0;
                    logic [wid-1:0] sout = 'h111; int cyc_tot = 0; } Info;
   <u>Info</u> pi[string];
   shift lt seq_d #(wid_lg,1) my_sld4(sout[4], ready[4], sin, amt, start, clk);
   initial begin
      automatic string m = "Degree 1";
      pi[m].idx = 4; pi[m].seq = 1;
   end
   shift lt seq_d #(wid_lg,3) my_sld5(sout[5], ready[5], sin, amt, start, clk);
   initial begin
      automatic string m = "Degree 3";
      pi[m].idx = 5; pi[m].seq = 1;
   end
   shift lt seq_d live #(wid_lg,1) my_sld9(sout[9], ready[9], sin, amt, start, clk);
   initial begin
      automatic string m = "Degree 1 live";
      pi[m].idx = 9; pi[m].seq = 1;
   end
   shift lt seq_d live #(wid_lg,3) my_sld2(sout[2], ready[2], sin, amt, start, clk);
   initial begin
      automatic string m = "Degree 3 live";
      pi[m].idx = 2; pi[m].seq = 1;
   end
   shift lt seq_d sol #(wid_lg,1) my_sld1(sout[1], ready[1], sin, amt, start, clk);
   initial begin
      automatic string m = "Degree 1 sol";
      pi[m].idx = 1; pi[m].seq = 1;
   end
   shift lt seq_d sol #(wid_lg,3) my_sld10(sout[10], ready[10], sin, amt, start, clk);
   initial begin
      automatic string m = "Degree 3 sol";
```

```
\leftarrow \rightarrow \text{ Fall 2015} \qquad \leftarrow \rightarrow \text{ Homework 4}
```

```
pi[m].idx = 10; pi[m].seq = 1;
end
shift lt seq_d p2 #(wid_lg,1) my_sld3(sout[3], ready[3], sin, amt, start, clk);
initial begin
   automatic string m = "Degree 1 P2";
   pi[m].idx = 3; pi[m].seq = 1;
end
shift lt seq_d p2 #(wid_lg,3) my_sld6(sout[6], ready[6], sin, amt, start, clk);
initial begin
   automatic string m = "Degree 3 P2";
   pi[m].idx = 6; pi[m].seq = 1;
end
localparam int tests_per_sa = 50;
localparam int num_tests = wid * tests_per_sa;
localparam int cycle_limit = num_tests * wid * 2;
uwire clk_reactive;
reactivate ra(clk_reactive,clk);
initial begin
   clk = 0;
   cycle = 0;
   fork
      forever #10 cycle += clk++;
      wait( done );
      wait( cycle >= cycle_limit )
        $write("*** Cycle limit exceeded, ending.\n");
   join_any;
   $finish();
end
initial begin
   // Number of test inputs (stimuli).
   11
   automatic int test_count = 0;
   done = 0;
   start = 1;
   @( posedge clk_reactive ); @( posedge clk_reactive );
   // Provide one test pattern per shift amount.
   11
   for ( int i=0; i<num_tests; i++ ) begin</pre>
      automatic int cyc_start = cycle;
      automatic int cyc_timeout = cycle + wid * 2;
```

```
\leftarrow \rightarrow Fall 2015 \leftarrow \rightarrow Homework 4
```

```
logic [wid-1:0] shadow_sout;
   int awaiting;
   automatic logic [wid_lg-1:0] amt_1 = i / tests_per_sa;
   amt = { amt_1[1:0], amt_1[wid_lg-1:2] };
   test_count++;
   for ( int p=0; p<wid; p+=32 ) sin[p+:32] = <u>$random;</u>
   shadow_sout = sin << amt;</pre>
   start = 1;
   @( posedge clk_reactive );
   start = 0;
   // Collect output as ready signals go to 1, or immediately
   // for non-sequential modules.
   11
   awaiting = pi.num();
   foreach ( pi[muti] ) begin
      automatic string mut = muti; // Bug workaround?
      fork begin
         while ( pi[mut].seq
                 && ready[pi[mut].idx] !== 1
                 && cycle < cyc_timeout )
           @( posedge clk_reactive );
         awaiting--;
         pi[mut].sout = sout[pi[mut].idx];
         pi[mut].cyc_tot += cycle - cyc_start;
      end join_none;
   end
   wait ( awaiting == 0 );
   // Check the output of each Module Under Test.
   11
   foreach ( pi[ mut ] )
     if ( shadow_sout !== pi[mut].sout ) begin
        pi[mut].err_count++;
        if ( pi[mut].err_count < 5 )</pre>
          <u>$write</u>
            ("%-20s wrong result for 0x%0h << %0d: 0x%0h != 0x%0h (correct)\n",
             mut, sin, amt, pi[mut].sout, shadow_sout);
     end
end
done = 1;
foreach ( pi[ mut ] )
   <u>$write</u>("Ran %4d tests for %-15s, %4d errors found. Avg cyc %.1f\n",
            test_count, mut, pi[mut].err_count,
          pi[mut].seq ? real'(pi[mut].cyc_tot) / test_count : 1
```

);

end

endmodule

// cadence translate_on

LSU EE 4755 Homework 5 solution Due: 23 Oct 2015 17:00

Problem 1: The homework Verilog file, hw05.v, contains something similar to the streamlined multiplier presented in class, mult_seq_stream, and even more streamlined versions of the multiplier, mult_seq_stream_2, and mult_seq_stream_3. These modules are reproduced at the end of this assignment. For an HTML version visit

http://www.ece.lsu.edu/koppel/v/2015/hw05.v.html. See the 2014 midterm exam for similar problems.

(a) Show the hardware that will be synthesized for each module for the default parameters. Show the module after optimization.

The synthesized hardware for each module appears below, and they also appear next to the respective Verilog descriptions at the end of this assignment. The red numbers show signal arrival times based on the assumptions given in the sub-problem below. The red wires show the critical path based on this analysis.

A decr unit has been used compute both pos-1 and pos==0, under the assumption that it might be possible to share some hardware. An enable signal is used on the prod register.







(b) Estimate the clock frequency of each module based on the following latencies:

Latch delay: 10 units. Multiplexor latency: 2 units. Latency of an *n*-bit adder: $5\lceil \lg n \rceil$ units. Latency of an *n*-input gate: $\lceil \lg n \rceil$ units. Let a unit be equal to 10 ps. Note: The duration of a unit was not given in the original assignment.

The timing analysis is shown in red on the three modules and the wires carrying the critical path are shown in red. This timing analysis strictly follows the guidelines above, using a $5\lceil \lg 17 \rceil = 25$ unit delay for the big adder. Realistically, that would be a 16-bit adder with a carry out. Solutions that used 20 rather than 25 units for the adder are correct.

For mult_seq_stream the critical path ends at accum with a period of 41 units or $410 \,\mathrm{ps}$. That would give a clock frequency of $\frac{1}{41}$ cycles per unit or 2.44 GHz.

For mult_seq_stream_2 and mult_seq_stream_3 the critical path is 2 units shorter, at 39 units. This is because the big adder uses the accum signal right out of the register outputs, in contrast to mult_seq_stream in which the particular accum to use must be routed through a mux based on a pos==0 select, adding delay. The clock frequency for these two modules would be 2.56 GHz.

(c) Why would module mult_seq_stream_3 provide a result in less time than the other two, even assuming that the clock frequency for all the modules was the same?

The product is available one cycle earlier because it is written to **prod** from the output of the big adder rather than from **accum**.







LSU EE 4755 Homework 6 solution Due: 2 December 2015

The solution code has been placed in /home/faculty/koppel/pub/ee4755/hw/2015f/hw06/hw06.v and an htmlized version is at http://www.ece.lsu.edu/koppel/v/2015/hw06sol.v.html, the original code in htmlized form can be found at http://www.ece.lsu.edu/koppel/v/2015/hw06.v.html.

Problem 0: The homework Verilog file, hw06.v, contains something similar to the integer compression modules presented in class. (Follow the homework workflow instructions on the course procedures page to get a copy of the assignment package.) These modules compress an ASCII character stream by substituting a binary-encoded integer for a string of ASCII digits. These modules were based on 2014 Homework 4. Feel free to look at that assignment an solution for help.

Module icomp_none is a version of the module that does no compression at all. It does though implement the handshaking protocol so that characters can be passed from input to output. This module can be studied to help understand how the others work.

Module icomp_2cyc is one of the compression modules covered in class. It computes the encoded value in stage 0, and checks for overflow in stage 1. Don't modify this module, save if for reference. Module icomp_sol is initially identical to icomp_2cyc, but it should be modified as part of this assignment.

The testbench is set to simulate icomp_sol on a sample test string. At the end it will report the amount of compression and whether there was any errors. The testbench also prints out a trace showing some module inputs and outputs and the status of internal signals. Examine the testbench code to see how this is done and feel free to modify it to add signals of your own. A more detailed trace of execution can be obtained using the SimVision gui. To start that use the command irun hw06.v -gui. See http://www.ece.lsu.edu/koppel/v/v/s/SimVisionIntro.pdf for documentation. (On campus access only without password.)

The synthesis script will synthesize the modules icomp_2cyc and icomp_sol. Use the synthesis script to make sure that your designs are synthesizable and to determine their cost and performance.

(There is nothing to turn in for this assignment.)

Problem 1: In module icomp_sol there is a declaration of a variable named val_encode_size_1, but no uses of that variable. Add code to that module so that val_encode_size_1 is set to the number of bytes that are needed for the number currently in the register val_encode_1. For example, if val_encode_1 has a 0, then val_encode_size_1 should be 0. If val_encode_1 has a 123 then val_encode_size_1 should be 1 (one byte), if val_encode_1 has a 300 then val_encode_size_1 should be 2 (for 2 bytes), etc.

To help with your solution add code to the testbench to show the value of this variable.

The solution appears below. The idea is to check each byte of val_encode_1, from least significant to most significant. If the byte is non-zero tentatively set val_encode_size_1 to the byte position (starting at one for the least-significant byte). Note that val_encode_1 is declared as a two-dimensional packed array, and so the expression val_encode_1[i] evaluates to the value of byte number i (with 0 being least significant, see the declaration).

```
logic [max_chars:0][7:0] val_encode_1;
logic [mc_bits:0] val_encode_size_1;
always_comb begin
  val_encode_size_1 = 0;
  for ( int i=0; i<max_chars; i++ )
      if ( val_encode_1[i] ) val_encode_size_1 = i + 1;
end
```

Problem 2: Modify module icomp_sol so that a group of ASCII digits is compressed into the smallest number of bytes needed, up to max_chars. For example, if max_chars is 4 then just use one byte to compress 200, two bytes for 4000, and for 1234567890123 use a four-byte integer (for 1234567890) followed by a one byte integer (for 123).

Precede the compressed integer by the character 128 plus the number of bytes in the compressed number. For example, if the compressed value takes two bytes then where the first character of the uncompressed value would go emit a 130, then the next two characters should be the compressed number. (See how char_out is assigned in the unmodified code.)

To solve this problem you'll need to understand how the existing code works, how to interpret the trace output provided by the simulator, and how to use the SimVision waveform viewer. Random guesses based on a vague understanding will get you nowhere.

- The module should be written for arbitrary values of max_chars.
- Make sure that the testbench is not reporting errors.
- Make sure that your module is compressing the string.

In the original module integers were encoded into max_chars bytes. So that the module can now encode integers into sizes from 1 up to max_chars bytes the following must be changed:

Encoding Acceptance: The hardware that decides whether to accept an encoded integer must now compare the ASCII length (ascii_int_len) to the actual encoded size (val_encode_size_1), not to max_chars. See Changed Line below.

```
wire use_encoding = end_encoding
    && ( ascii_int_len > 2 ) /// Changed Line
    && ( !val_wait_full || end_draining );
```

Tail Changes: The position for writing incoming characters into storage is tail. Ordinarily tail is incremented each time a character is read. But because an encoded integer takes less space than the ASCII version tail must be adjusted after the last character of an encoded integer is encountered. In the original code the adjusted tail value is found by adding the starting point of the ASCII string (tail_at_enc_start_1) to max_chars plus a possible overflow adjustment. In the solution max_chars is replaced by val_encode_size_1. (The overflow adjustment adds an extra one to the tail because the tail is being updated one cycle late.)

```
wire [size_lg:1] tail_adj =
    tail_at_enc_start_1 + val_encode_size_1 + overflow_1;
```

Head/Char Out Changes: Module output char_out can connect to either storage (where the ASCII characters are stored), the escape character (a constant value in the original module), or val_wait (the encoded integer). In the original code control logic would connect char_out to val_wait until max_chars characters were read. In the modified module it connects char_out to val_wait until val_encode_size_1 characters were read.

In the original code each element of array esc_here was one bit, indicating that the corresponding ASCII character in storage was the start of an ASCII string that should be replaced by an encoded integer. In the solution each element of esc_here indicates how many bytes are in the encoded integer (a 0 means that an encoded integer does not start here). The solution excerpt below shows the new declaration for esc_here and how esc_here gets written:

/// SOLUTION HIGHLIGHTS -- SURROUNDING CODE REMOVED

```
/// SOLUTION -- Problem 2
```

- // Increase the size of the "escape here" marker from 1 bit to
- // mc_bits. Its value now indicates the size of the encoded

```
// integer in bytes.
logic [mc_bits-1:0] esc_here [size];
    /// SOLUTION -- Problem 2
    //
    // Write the size of the encoded integer into the esc_here array.
    // (Previously we just wrote a 1, to indicate that an encoded
    // integer starts at this position.)
    //
    always_ff @( posedge clk )
    if ( use_encoding ) esc_here[tail_at_enc_start_1] <= val_encode_size_1;</pre>
```

Head/Char Out Changes continued: The variable drain_idx indicates the byte position in val_wait that should be sent to char_out. In the original code it was initialized to max_chars-1, an elaboration-time constant. In the solution it is set to esc_here [head]-1, see the first excerpt below. The final change is to change the escape character. In earlier classroom examples the escape character was a constant, Char_escape. In this assignment the escape character should be set to the sum of Char_escape and the size of the encoded integer. In the original code, that's still a constant because both Char_escape and max_chars are elaboration-time constants. But in the solution the encoded size can vary, so we must add the actual encoded size, esc_here [head] to Char_escape, that appears in the second excerpt below.

```
/// SOLUTION -- Problem 2
   11
   // Initialize drain_idx with one minus the size of
   // the encoded integer, rather than max_chars - 1.
   11
   drain_idx <= start_draining ? esc_here[head] - 1 :</pre>
                drain_idx > 0 ? drain_idx - 1 :
                                   0;
/// SOLUTION -- Problem 2
11
// When we reach an encoded integer output the escape character
// plus the size of the encoded integer.
11
assign char_out =
       start_draining ? Char_escape + esc_here[head] :
                      ? val_wait[drain_idx] :
       draining
                          storage[head];
```

24 Fall 2014 Solutions

```
// LSU EE 4755 Fall 2014 Homework 1 -- SOLUTION
// Assignment http://www.ece.lsu.edu/koppel/v/2014/hw01.pdf
```

`*default_nettype* none

```
/// Problem 1
11
/// Logical Right Shift Module 1
11
    The module below performs a logical right shift of a 16-bit
11
11
    quantity.
17
         Fix the module, the testbench should not report errors.
     [X]
11
     [x] Don't substantially change the way the code works.
11
     [x] Don't try to make the code synthesizable.
11
     [x] Don't use shift (<<) or concatenation operators ({}) ...</pre>
11
         .. assign shifted bit-by-bit as the code already does.
11
// cadence translate_off
module shift_right1
   ( output logic [15:0] shifted,
    input wire [15:0] unshifted,
    input wire [3:0] amt );
  /// Problem 1 solution goes in this module.
  localparam int width = 16;
  always @* begin
     automatic int limit = width - amt;
     for ( int i=0; i<limit; i++ ) shifted[i] = unshifted[i+amt];</pre>
     /// SOLUTION
     // Just zero the "vacated" bits.
     11
     for ( int i=limit; i<width; i++ ) shifted[i] = 0;</pre>
  end
```

endmodule

// cadence translate_on


```
// The module below performs a logical right shift of a 16-bit
// quantity.
//
```

```
\leftarrow \rightarrow Fall 2014
                  \leftarrow \rightarrow Homework 1
                                               Homework Sol Code
   11
         [x] Complete module shift right2, the testbench should not report errors.
    // Perform Two Possible Shifts: by 0 bits or by fsamt bits.
   11
   module shift right fixed
       ( output wire [15:0] shifted,
         input wire [15:0] unshifted,
         input wire shift );
       // Problem 2: DON'T modify this module.
       // (Fixed) Shift Amount
       11
       parameter int fsamt = 3;
       // If shift is true shift by fsamt, otherwise don't shift.
       11
```

hw01-sol.v.html

assign shifted = shift ? unshifted >> fsamt : unshifted;

endmodule

```
// Declare wires to interconnect the modules.
//
uwire [15:0] s8, s4, s2;
shift_right_fixed #(8) sm8
  ( .shifted(s8), .unshifted(unshifted), .shift(amt[3]) );
/// SOLUTION
//
// Instantiate three more modules and connect them.
// Note: You don't have to use named ports.
shift_right_fixed #(4) sm4 (s4, s8, amt[2]);
shift_right_fixed #(2) sm2 (s2, s4, amt[1]);
```

shift right fixed #(1) sml (shifted, s2, amt[0]);

endmodule


```
11
   The code below instantiates shift right1 and shift right2,
//
11
   provides test inputs and verifies the outputs.
11
11
   The testbench may be modified to facilitate your solution. Of
11
   course, the removal of tests which your module fails is not
   considered a correct solution. (The idea is to put in tests which
11
   make it easier to determine what the problem is, for example, test
11
    inputs that are all 0's or all 1's.)
11
```

```
module testbench();
   uwire logic [15:0] sout1, sout2;
   logic [15:0] sin;
   logic [3:0] amt;
   shift_right1 my_srl(sout1, sin, amt);
   shift_right2 my_sr2(sout2, sin, amt);
   // Width of shifters' input and output.
   // The parameter is used only by this testbench.
   11
  localparam int width = 16;
   //
   // To keep things simple the shifter modules themselves are written
  // with a hardcoded width of 16 bits. That's bad style since
   // changing the width would be tedious and error prone. The
   // hardcoded widths are used in this first homework assignment only
   // to keep things simple. (The shifter modules could have used a
   // parameter to specify the width or a user-defined type.)
   // Provide names for the modules for use in error messages.
   localparam string name[2] = '{"Prob 1", "Prob 2"};
   initial begin
      // Count of errors for each module.
      11
      automatic int err_count[2] = '{0,0};
      //
      // Note: The automatic qualifier is needed so that the initialization
      // could appear on the same line as the declaration.
      // Number of test inputs (stimuli).
      11
      automatic int test count = 0;
      // Provide one test pattern per shift amount.
      //
      for ( int i=0; i<width; i++ ) begin</pre>
         int shadow sout;
         test count++;
         sin = $random;
         amt = i;
         shadow sout = sin >> amt;
         #1;
         // Check the output of each Module Under Test.
         //
         foreach ( name[ mut ] ) begin
            automatic logic [15:0] sout = mut == 0 ? sout1 : sout2;
            if ( shadow sout !== sout ) begin
               err_count[mut]++;
               if ( err_count[mut] < 5 )</pre>
                 <u>$display</u>
                   ("MUT %s wrong result for %h >> %d: %h != %h (correct)\n",
```

name[mut], sin, amt, sout, shadow_sout);

end

end

end

\$display("Ran %d tests, %d, %d errors found.\n",
 test_count, err_count[0], err_count[1]);

 $\operatorname{\mathsf{end}}$

endmodule

// cadence translate_on

```
11
/// LSU EE 4755 Fall 2014 Homework 2
11
/// Assignment http://www.ece.lsu.edu/koppel/v/2014f/hw02.pdf
/// Instructions:
 11
  // (1) Find the undergraduate workstation laboratory, room 126 EE
         Building.
  11
  11
  // (2) Locate your account. If you did not get an account please
         E-mail: koppel@ece.lsu.edu
  11
  11
  // (3) Log in to a Linux workstation.
         The account should start up with a WIMP interface (windows, icons,
  11
  11
         mouse, pull-down menus) (:-) ) but one or two things need
         to be done from a command-line shell. If you need to brush up on Unix commands follow <a href="http://www.ece.lsu.edu/koppel/v/4ltrwrd/">http://www.ece.lsu.edu/koppel/v/4ltrwrd/</a>.
  11
  11
  11
  // (4) If you haven't already, follow the account setup instructions here:
  11
         http://www.ece.lsu.edu/koppel/v/proc.html
  11
  // (5) Copy this assignment, local path name
         /home/faculty/koppel/pub/ee4755/hw/2014f/hw02
  11
  11
         to a directory ~/hw02 in your class account. (~ is your home
         directory.) Use this file for your solution.
  11
  11
  // (6) Find the problems in this file and solve them.
  11
  11
         Your entire solution should be in this file.
  11
  11
         Do not change module names.
  11
  // (7) Your solution will automatically be copied from your account by
         the TA-bot.
  11
 /// Additional Resources
  11
  // Verilog Documentation
        The Verilog Standard
  11
          http://standards.ieee.org/getieee/1800/download/1800-2012.pdf
  11
        Introductory Treatment (Warning: Does not include SystemVerilog)
  11
  11
          Brown & Vranesic, Fundamentals of Digital Logic with Verilog, 3rd Ed.
  11
  // Account Setup and Emacs (Text Editor) Instructions
          http://www.ece.lsu.edu/koppel/v/proc.html
  11
  11
          To learn Emacs look for Emacs tutorial.
  11
  // Unix Help
  11
          http://www.ece.lsu.edu/koppel/v/4ltrwrd/
```



```
module mult_behav_1
  #(int wid = 16)
  (output logic[2*wid-1:0] prod, input logic[wid-1:0] plier, cand);
  assign prod = plier * cand;
```

```
module mult_behav_2
#(int wid = 16)
(output logic[2*wid-1:0] prod, input logic[wid-1:0] plier, cand);
always @* begin
prod = 0;
for ( int i=0; i<wid; i++ ) if ( plier[i] ) prod = prod + ( cand << i );
end</pre>
```

endmodule


```
/// Simple Adder, Don't Modify
module good_adder#(int w=16)(output [w:1] s, input [w:1] a,b);
    assign s = a + b;
endmodule
```

module mult linear

```
#(int wid = 16)
(output logic[2*wid-1:0] prod, input logic[wid-1:0] plier, cand);
/// Problem 2 Solution Goes Here.
// This module should be a structural version of mult_behav_2,
// using generate statements to instantiate good_adder.
```

```
/// SOLUTION BELOW
```

```
logic [2*wid-1:0] rsum [wid-1:-1];
logic [2*wid-1:0] pp [wid-1:0];
assign rsum[-1] = 0;
for ( genvar i=0; i<wid; i++ ) begin
    assign pp[i] = plier[i] ? cand << i : 0;
    good_adder #(2*wid) adder(rsum[i], rsum[i-1], pp[i] );
end
```

```
assign prod = rsum[wid-1];
```

endmodule

/// Problem 3 Solutions

```
//
// Several solutions appear below to Problem 3. The easy to
// understand solution is mult_tree_simple. Module mult_tree is
// compact (does not require alot of Verilog code). Module
// mult_tree_rec shows a recursive implementation. Module
// mult_tree_better uses a cost saving technique.
```

11 /// mult tree // This one is the shortest. The tree is constructed using // a single loop. 11 /// mult_tree_rec // A recursive version. The cost and performance will // not be very good unless synthesized with option "-effort high" because without that option the synthesis program synthesizes 11 11 modules without taking into account how they are instantiated. 11 Among other things, that means the synthesis program can't eliminate // unused wires. 11 /// mult_tree_simple // Maybe the easiest to understand. The tree is constructed using // two nested loops, the outer loop iterates over tree levels and the inner loop iterates over adders within a level. 11 11 /// mult_tree_better // This is like mult_tree_simple, but instead of shifting the 11 multiplicand, the intermediate sums are shifted. module mult tree #(int wid = 16)(output logic[2*wid-1:0] prod, input logic[wid-1:0] plier, cand); localparam int widp2 = 1 << <u>\$clog2(wid);</u> /// SOLUTION BELOW to Problem 3 11 // This is one of several solutions to Problem 3. logic [2*wid-1:0] rsum [2*wid-1:0]; localparam int mask = 2*wid-1; // Compute partial products. 11 for (genvar i=0; i<wid; i++)</pre> assign rsum[i] = plier[i] ? cand << i : 0;</pre> // Add partial products together. // for (genvar i=wid; i<2*wid-1; i++)</pre> good adder #(2*wid) adder (rsum[i],], // Left child. rsum[mask & (i<<1) rsum[mask & ((i<<1) + 1)] // Right child.); prod = rsum[2*wid-2]; assign endmodule module mult tree rec #(int wid plier = 16, int wid cand = wid plier) (output logic [2*wid_plier-1:0] prod, input logic [wid_plier-1:0] plier, input logic [wid_cand-1:0] cand); localparam int wid cr h = wid cand / 2;localparam int wid_cr_l = wid_cand - wid_cr_h;

generate

```
if ( wid_cand == 1 ) begin
    assign prod = cand[0] ? plier : 0;
end else begin
    wire    logic [2*wid_plier-1:0] prod_h, prod_l;
    <u>mult_tree_rec</u> #(wid_plier, wid_cr_h) m_h
    (prod_h, plier, cand[wid_cand-1:wid_cr_l] );
    <u>mult_tree_rec</u> #(wid_plier, wid_cr_l) m_l
    (prod_l, plier, cand[wid_cr_l-1:0] );
    <u>good_adder</u> #(2*wid_plier) adder
    (prod, prod_h << wid_cr_l, prod_l);
    end
endgenerate
endmodule
```

```
module mult_tree_simple
  #(int wid = 16)
   (output logic[2*wid-1:0] prod, input logic[wid-1:0] plier, cand);
   localparam int levels = <u>$clog2(wid);</u>
   logic [2*wid-1:0] rsum [2*wid-1:0][levels:0];
   for ( genvar lev=0; lev<levels; lev++ ) begin</pre>
      localparam int siblings = 1 << lev;</pre>
      for ( genvar i=0; i<siblings; i++ )</pre>
         good adder #(2*wid) adder
                       ( rsum[i][lev],
                         rsum[i*2][lev+1],
                         rsum[i*2+1][lev+1] );
   end
   for ( genvar i=0; i<wid; i++ )</pre>
     assign rsum[i][levels] = plier[i] ? cand << i : 0;</pre>
           prod = rsum[0][0];
   assign
endmodule
module mult tree better
  #(int wid = 16)
```

(output logic[2*wid-1:0] prod, input logic[wid-1:0] plier, cand);

localparam int levels = <u>\$clog2(wid);</u>

logic [2*wid-1:0] rsum [2*wid-1:0][levels:0];

for (genvar lev=0; lev<levels; lev++) begin</pre>

```
for ( genvar i=0; i<wid; i++ )
   assign rsum[i][levels] = plier[i] ? cand : 0;</pre>
```

```
assign prod = rsum[0][0];
```


// cadence translate_off

module testbench;

```
localparam int wid = 64;
localparam int num_tests = 1000;
localparam int NUM MULT = 7;
localparam int err_limit = 4;
logic [wid-1:0] plier, cand;
logic [2*wid-1:0] prod[NUM MULT];
mult_behav_1 #(wid) mb1(prod[0], plier, cand);
mult_behav_2 #(wid) mb2(prod[1], plier, cand);
mult_linear #(wid) ms1(prod[2], plier, cand);
            #(wid) ms2(prod[3], plier, cand);
<u>mult_tree</u>
mult tree rec #(wid) ms3(prod[4], plier, cand);
mult_tree_simple #(wid) ms4(prod[5], plier, cand);
mult tree better #(wid) ms5(prod[6], plier, cand);
int err cnt[NUM MULT];
int tests[$] = {1,1, 1,2, 1,32, 32, 1};
initial begin
  for ( int i=0; i<num tests; i++ ) begin</pre>
      plier = tests.size() ? tests.pop front() : <u>$random();</u>
      cand = tests.size() ? tests.pop front() : <u>$random();</u>
      #1:
      for ( int mut=1; mut<NUM MULT; mut++ ) begin</pre>
        if ( prod[0] !== prod[mut] ) begin
           err cnt[mut]++;
```
```
\leftarrow \rightarrow Fall 2014 \leftarrow \rightarrow Homework 2
```

end

endmodule

// cadence translate_on

LSU EE 4755

Homework 3 Solution Updated 7 November 2014, 13:49:47 CST

Due: 24 October 2014

The Homework 3 code package contains a simple behavioral multiplier and several sequential multipliers. It also contains a synthesis script in file syn.cmd.

Problem 0: Copy the code package from /home/faculty/koppel/pub/ee4755/hw/2014f/hw03. Verify that everything is working by running the simulation on the unmodified file. It should report a 0% error rate for all modules.

Problem 1: The module mult_seq_csa is a sequential multiplier that instantiates an adder, however unlike mult_seq_ga shown in class, mult_seq_csa instantiates a carry-save adder from the Chipware library, CW_csa. The carry save adder computes the sum of three integers, a, b, and c (those are the port names). It produces two sums, which we'll call sum_a and sum_b (the port names for these are carry and sum). All of these ports are w bits wide, where w is a parameter. The actual sum of a, b, and c is obtained by adding together outputs sum_a and sum_b using a conventional adder. Carry save adders are used when there many integers to be added. Some arrangement (linear, tree) of many carry-save adders will produce a sum_a and sum_b, which will be added by a single conventional (called carry-propagate) adder.

The advantage of a carry save adder is that it can compute a sum of w-bit numbers in O(1) time (the amount of time is not affected by w), which of course is much better than the O(w) time for a ripple adder or the $O(\log w)$ time for much more expensive carry look-ahead adders. The performance advantage of a CSA is lost for mult_seq_csa because the module only computes one partial product at a time.

(a) Sketch the hardware that will be synthesized for mult_seq_csa. Show the carry-save adder and other major units as boxes, but be sure to show registers, multiplexors, and other such components. Do not show the actual output produced by an actual synthesis program. (It's okay if you look at a synthesis program's output.)

The hardware appears below. In the diagram the critical path is shown in red. Notice that the critical path goes through *both* the CSA and conventional adders.



(b) Based on this sketch of synthesized hardware, explain why the benefit of using a CSA is lost. Also explain how the module can be made a little faster (with a small change), but is still not a good way to use a CSA.

The clock frequency is based on the (longest) critical path. For the module the critical path is the sum of the delay through the CSA and carry-propagate (regular) adder. If a carry-propagate adder were used

Problem 2: Module mult_seq_csa_m initially contains the *m*-partial-products-per-cycle module that we did in class. In this problem modify it to use CSA's, and avoid the issue identified in the previous problem.

(a) Modify mult_seq_csa_m so that it uses the carry-save adder to compute m partial products per cycle. Use generate statements to instantiate the CSA's, and of course, connect them appropriately. (In class we used generate statements for the pipelined adder to instantiate stages, that code is in mult_pipe_ia in the same file as the assignment.)

Solution appears below.

```
module mult_seq_csa_m #( int wid = 16, int pp_per_cycle = 2 )
   ( output logic [2*wid-1:0] prod,
     input logic [wid-1:0] plier, input logic [wid-1:0] cand,
                                                                     input clk);
   localparam int iterations = ( wid + pp_per_cycle - 1 ) / pp_per_cycle;
   localparam int iter_lg = $clog2(iterations);
   localparam int wid_lg = $clog2(wid);
   logic [iter_lg:0] iter;
   wire [2*wid-1:0] accum_sum_a[0:pp_per_cycle], accum_sum_b[0:pp_per_cycle];
   logic [2*wid-1:0] accum_sum_a_reg, accum_sum_b_reg;
   initial iter = 0;
                    accum_sum_a[0] = accum_sum_a_reg;
   assign
                    accum_sum_b[0] = accum_sum_b_reg;
   assign
   for ( genvar i=0; i<pp_per_cycle; i++ ) begin</pre>
      wire [wid_lg:1] pos = iter * pp_per_cycle + i;
                      co; // Unconnected.
      wire
      // The "pos < wid" below is needed in case wid is not an integer multiple of pp_per_cycle.
      wire [2*wid-1:0] pp = pos < wid && cand[pos] ? plier << pos : 0;</pre>
      CW_csa #(2*wid) csa
        ( .sum(accum_sum_a[i+1]), .carry(accum_sum_b[i+1]), .co(co),
          .a(accum_sum_a[i]), .b(accum_sum_b[i]), .c(pp), .ci(1'b0) );
   end
   always @( posedge clk ) if ( iter == iterations ) begin
         prod <= accum_sum_a_reg + accum_sum_b_reg;</pre>
         accum_sum_a_reg <= 0;</pre>
         accum_sum_b_reg <= 0;</pre>
         iter \leq 0:
      end else begin
         accum_sum_a_reg <= accum_sum_a[pp_per_cycle];</pre>
         accum_sum_b_reg <= accum_sum_b[pp_per_cycle];</pre>
         iter <= iter + 1;</pre>
      end
endmodule
```

(b) Sketch the hardware that you expect to be synthesized for an m = 2 version. Make sure that your design does not do something foolish with the conventional adder.

The hardware appears below. Coloring has been used to emphasize the hardware corresponding to each iteration of the generate loop (blue and green) and hardware corresponding to Verilog outside of the generate loop (black). Pay close attention to accum_sum_a[i] and accum_sum_b[i]. They are declared outside the generate loop but are used to interconnect items in different generate loop iterations.

The diagram shows the inferred hardware, before any optimization. Note that the conventional adder (the big box with the plus) receives its inputs from the outputs of register accum_sum_a_reg and accum_sum_b_reg, rather than the CSA outputs. This gives the adder the entire clock period to produce its sum.





Problem 3: Run the synthesis program to compare the cost and performance of mult_seq_csa_m to mult_seq_m. The synthesis script syn.cmd can be used to synthesize these modules at different sizes. To run it use the command rc -files syn.cmd. Feel free to modify the script. (It is written in TCL, it should be easy to find information on this language.)

(a) Show the cost and performance versus m for these modules.

The cost and performance appear below. The first table shows the results using the unmodified synthesis script, in which area was minimized. The second table shows the results using a synthesis script in which the synthesis program was set to minimize delay.

Area Optimization				
Module Name	Area	Clock	Total	Init.
		Period	Delay	Interv
<pre>mult_seq_csa_m_wid16_pp_per_cycle1</pre>	110308	14170	226720	226720
<pre>mult_seq_csa_m_wid16_pp_per_cycle2</pre>	135192	13692	109536	109536
<pre>mult_seq_csa_m_wid16_pp_per_cycle4</pre>	157668	12828	51312	51312
<pre>mult_seq_csa_m_wid16_pp_per_cycle8</pre>	195212	11110	22220	22220
<pre>mult_seq_m_wid16_pp_per_cycle1</pre>	74092	16444	263104	263104
<pre>mult_seq_m_wid16_pp_per_cycle2</pre>	99884	17470	139760	139760
<pre>mult_seq_m_wid16_pp_per_cycle4</pre>	112664	16508	66032	66032
<pre>mult_seq_m_wid16_pp_per_cycle8</pre>	154744	16463	32926	32926
Delay Optimization				
Module Name	Area	Clock	Total	Init.
		Period	Delay	Interv
<pre>mult_seq_csa_m_wid16_pp_per_cycle1</pre>	164940	2054	32864	32864
<pre>mult_seq_csa_m_wid16_pp_per_cycle2</pre>	195408	2255	18040	18040
<pre>mult_seq_csa_m_wid16_pp_per_cycle4</pre>	239340	2756	11024	11024
<pre>mult_seq_csa_m_wid16_pp_per_cycle8</pre>	316748	4043	8086	8086
<pre>mult_seq_m_wid16_pp_per_cycle1</pre>	125408	3062	48992	48992
<pre>mult_seq_m_wid16_pp_per_cycle2</pre>	166488	3368	26944	26944
<pre>mult_seq_m_wid16_pp_per_cycle4</pre>	202096	3777	15108	15108
mult_seq_m_wid16_pp_per_cycle8	263772	4285	8570	8570

(b) If you solved the previous problem correctly the total delay shown for mult_seq_csa_m should be wrong. Explain why, and (optional) if you like try modifying syn.cmd to fix it.

The TCL script computes the total delay by multiplying the clock period by w/m. (In the TCL script w/m is computed by the routine get_stages. In that routine variable bits is used for w and deg for m.) The values of m and w used by the script are chosen so that m always divides w, so the problem has nothing to do with integer truncation errors.

The module designed for the solution to Problem 2 uses an extra cycle to compute the sum, so it takes m/w + 1 cycles, and the TCL script does not take this into account. (Of course, that would be easy enough to fix.)

(c) Explain how you might expect the total delay (time needed to compute a product) of $mult_seq_csa_m$ to change with increasing m? Explain your expectation and whether the synthesis results bear that out.

The clock period is determined by either the delay of one carry-propagate (conventional) adder or the delay of m carry-save adders, whichever is larger. For small values of m the carry-propagate adder would have the larger delay. So, one might expect that the clock period for the modules with m = 1 and m = 2 would be the same. However, the time needed to compute a product, T(m), would go from $T(1) = (w/1 + 1) t_{clk} \approx w t_{clk}$ to $T(2) = (w/2 + 1) t_{clk} \approx \frac{w}{2} t_{clk}$ which is nearly half the time. For these small values of m the clock period $t_{clk} = t_{latch} + t_{adder}$, where t_{latch} is the setup time needed for the registers and t_{adder} is the time needed for the carry-propagate adder. When m is increased further the clock period time will be more like $t_{clk} = t_{latch} + m t_{csa}$ where t_{csa} is the delay for one carry-save adder. At that point, further increases in m will not improve total performance by as much:

$$T(m) = (w/m+1) \left(t_{\text{latch}} + mt_{\text{csa}} \right)$$
$$= (w+1)t_{\text{csa}} + \left(\frac{w}{m} + 1\right) t_{\text{latch}}$$

When the synthesis program is optimizing delay, results are consistent with this analysis: Performance improvement with increasing m is much better when m is small than when m is large.

///// // ///	LSU	J EE 4755 Fall 2014 Homework 3					
///	SOL	UTION					
/// ///	<pre>/ Assignment <u>http://www.ece.lsu.edu/koppel/v/2014/hw03.pdf</u> / Solution <u>http://www.ece.lsu.edu/koppel/v/2014/hw03_sol.pdf</u></pre>						
///	Instr	ructions:					
	(1)	Find the undergraduate workstation laboratory, room 126 EE Building.					
	(2)	Locate your account. If you did not get an account please E-mail: koppel@ece.lsu.edu					
 	(3)	Log in to a Linux workstation. The account should start up with a WIMP interface (windows, icons, mouse, pull-down menus) (:-)) but one or two things need to be done from a command-line shell. If you need to brush up on Unix commands follow <u>http://www.ece.lsu.edu/koppel/v/4ltrwrd/</u> .					
	(4)	<pre>If you haven't already, follow the account setup instructions here: http://www.ece.lsu.edu/koppel/v/proc.html</pre>					
 	(5)	Copy this assignment, local path name /home/faculty/koppel/pub/ee4755/hw/2014f/hw03 to a directory ~/hw02 in your class account. (~ is your home directory.) Use this file for your solution.					
	(6)	Find the problems in this file and solve them.					
		Your entire solution should be in this file.					
		Do not change module names.					
 	(7)	Your solution will automatically be copied from your account by the TA-bot.					
///	Add	itional Resources					
// // // //	Ver	ilog Documentation The Verilog Standard <u>http://standards.ieee.org/getieee/1800/download/1800-2012.pdf</u> Introductory Treatment (Warning: Does not include SystemVerilog) Brown & Vranesic, Fundamentals of Digital Logic with Verilog, 3rd Ed.					
 	Acco	ount Setup and Emacs (Text Editor) Instructions <u>http://www.ece.lsu.edu/koppel/v/proc.html</u> To learn Emacs look for Emacs tutorial.					
 	Uni>	<pre>k Help http://www.ece.lsu.edu/koppel/v/4ltrwrd/</pre>					

```
module mult_behav_1
  #(int wid = 16)
   (output logic[2*wid-1:0] prod, input logic[wid-1:0] plier, cand);
  assign prod = plier * cand;
endmodule
```



```
module mult_seq_m #( int wid = 16, int pp_per_cycle = 2 )
   ( output logic [2*wid-1:0] prod,
     input logic [wid-1:0] plier,
     input logic [wid-1:0] cand,
     input clk);
   localparam int iterations = ( wid + pp_per_cycle - 1 ) / pp_per_cycle;
   localparam int iter_lg = <u>$clog2(iterations);</u>
   logic [iter lg:1] iter;
   logic [2*wid-1:0] accum;
   // cadence translate off
   initial iter = 0;
   // cadence translate_on
   always @( posedge clk ) begin
      if ( iter == iter lg'(iterations) ) begin
         prod = accum;
         accum = 0;
         iter = 0;
      end
      for ( int i=0; i<pp per cycle; i++ )</pre>
        begin
           int pos; pos = iter * pp per cycle + i;
           if ( cand[pos] ) accum += plier << pos;</pre>
        end
      iter++;
   end
```

```
endmodule
```

```
// Examine this module for Problem 1.
// Don't modify the module.
```

`include "/apps/linux/cadence/RC141/share/synth/lib/chipware/sim/verilog/CW/CW_csa.v"

```
\leftarrow \rightarrow Fall 2014
                  \leftarrow \rightarrow Homework 3
                                              Homework Solution Sol Code
   module mult seq csa #( int wid = 16 )
       ( output logic [2*wid-1:0] prod,
         input logic [wid-1:0] plier,
         input logic [wid-1:0] cand,
         input clk);
       localparam int wlog = <u>$clog2(wid);</u>
       logic [wlog-1:0] pos;
       logic [2*wid-1:0] accum_sum_a_reg, accum_sum_b_reg;
       wire
                         CO;
       // cadence translate off
       initial begin pos = 0; accum sum a reg = 0; accum sum b reg = 0; end
       // cadence translate on
      wire [2*wid-1:0] accum sum a, accum sum b;
      wire [2*wid-1:0] pp = cand[pos] ? plier << pos : 0;</pre>
       CW csa #(2*wid) csa
         (.carry(accum_sum_a), .sum(accum_sum_b), .co(co),
           .a(accum_sum_a_reg), .b(accum_sum_b_reg), .c(pp), .ci(1'b0) );
       always @( posedge clk ) pos <= pos + 1;
       always @( posedge clk ) begin
          if ( pos == wid-1 ) begin
             prod = accum sum a + accum sum b;
             accum sum a reg = 0;
             accum sum b reg = 0;
          end else begin
             accum sum a reg = accum sum a;
             accum sum b reg = accum sum b;
          end
```

end

endmodule

```
/// Problem 2: Modify this module.
```

```
module mult_seq_CSa_m #( int wid = 16, int pp_per_cycle = 2 )
  ( output logic [2*wid-1:0] prod,
    input logic [wid-1:0] plier,
    input logic [wid-1:0] cand,
    input clk);
  /// SOLUTION
  localparam int iterations = ( wid + pp_per_cycle - 1 ) / pp_per_cycle;
  localparam int iter_lg = $clog2(iterations);
  localparam int wid_lg = $clog2(wid);
```

```
logic [iter lg:0] iter;
   // cadence translate off
   initial iter = 0;
   // cadence translate on
   wire [2*wid-1:0] accum sum a[0:pp per cycle], accum sum b[0:pp per cycle];
   logic [2*wid-1:0] accum_sum_a_reg, accum_sum_b_reg;
   assign
                    accum_sum_a[0] = accum_sum_a_reg;
                    accum_sum_b[0] = accum_sum_b_reg;
   assign
   for ( genvar i=0; i<pp_per_cycle; i++ ) begin</pre>
     wire [wid_lg:1] pos = iter * pp_per_cycle + i;
     wire
                      co; // Unconnected.
     wire [2*wid-1:0] pp = pos < wid && cand[pos] ? plier << pos : 0;</pre>
     <u>CW csa</u> #(2*wid) csa
        ( .sum(accum_sum_a[i+1]), .carry(accum_sum_b[i+1]), .co(co),
          .a(accum_sum_a[i]), .b(accum_sum_b[i]), .c(pp), .ci(1'b0) );
   end
   always @( posedge clk ) begin
      if ( iter == iterations ) begin
         // The commented-out line below shows the wrong way of
         // designing this module.
         11
         // prod = accum sum a[pp per cycle] + accum sum b[pp per cycle];
         // Note that the product is computed by using the register
         // outputs, rather than the output of the last CSA.
         11
         prod <= accum_sum_a_reg + accum_sum_b_reg;</pre>
         accum sum a reg <= 0;
         accum sum b reg <= 0;
         iter \leq 0;
      end else begin
         accum sum a reg <= accum sum a[pp per cycle];</pre>
         accum sum b reg <= accum sum b[pp per cycle];
         iter <= iter + 1;
      end
   end
endmodule
```


module mult_pipe #(int wid = 16, int pp_per_stage = 2)
 (output logic [2*wid-1:0] prod,

```
\leftarrow \rightarrow Fall 2014
                   \leftarrow \rightarrow Homework 3
                                                Homework Solution Sol Code
         input logic [wid-1:0] plier,
         input logic [wid-1:0] cand,
         input clk);
       localparam int stages = ( wid + pp per stage - 1 ) / pp per stage;
       logic [2*wid-1:0] pl accum[0:stages];
       logic [wid-1:0] pl_plier[0:stages];
       logic [wid-1:0] pl_cand[0:stages];
       always @( posedge clk ) begin
          pl_accum[0] = 0;
          pl_plier[0] = plier;
          pl_cand[0] = cand;
          for ( int stage=0; stage<stages; stage++ ) begin</pre>
              logic [2*wid-1:0] accum; accum = pl_accum[stage];
              for ( int j=0; j<pp_per_stage; j++ ) begin</pre>
```

```
int pos; pos = stage * pp_per_stage + j;
```

```
if ( pos < wid && pl_cand[stage][pos] )
    accum += pl_plier[stage] << pos;</pre>
```

end

```
pl_accum[stage+1] <= accum;
pl_cand[stage+1] <= pl_cand[stage];
pl plier[stage+1] <= pl plier[stage];</pre>
```

end

end

```
assign prod = pl_accum[stages];
```

endmodule


```
module mult_pipe_stage #( int wid = 16, int pp_per_stage = 2, int stage = 0 )
  ( output logic [2*wid-1:0] accum_out,
    input [2*wid-1:0] plier,
    input [wid-1:0] cand);
  always @* begin
    logic [2*wid-1:0] accum; accum = accum_in;
    for ( int j=0; j<pp_per_stage; j++ ) begin
        int pos; pos = stage * pp_per_stage + j;
        if ( pos < wid && cand[pos] ) accum += plier << pos;
    }
}
```

accum out = accum;

end

endmodule

```
module mult_pipe_ia #( int wid = 16, int pp_per_stage = 2 )
   ( output logic [2*wid-1:0] prod,
     input logic [wid-1:0] plier,
     input logic [wid-1:0] cand,
     input clk);
   localparam int stages = ( wid + pp_per_stage - 1 ) / pp_per_stage;
   logic [2*wid-1:0] pl_accum[0:stages];
   logic [wid-1:0] pl_plier[0:stages];
   logic [wid-1:0] pl_cand[0:stages];
   always @* begin
      pl accum[0] = 0;
      pl_plier[0] = plier;
      pl_cand[0] = cand;
   end
   for ( genvar stage = 0; stage < stages; stage++ ) begin</pre>
      wire logic [2*wid-1:0] accum;
      mult_pipe stage x #(wid, pp_per_stage, stage) this_stage
        ( accum, pl accum[stage], pl plier[stage], pl cand[stage]);
      always @( posedge clk ) begin
         pl accum[stage+1] <= accum;</pre>
         pl plier[stage+1] <= pl plier[stage];</pre>
         pl cand[stage+1] <= pl cand[stage];</pre>
      end
   end
   assign prod = pl accum[stages];
```

endmodule

// cadence translate_off

module testbench;

```
localparam int wid = 16;
localparam int num_tests = 1000;
localparam int NUM_MULT = 10;
localparam int err_limit = 7;
localparam bit pipeline_test_exact = 1;
logic clock;
always #1 clock <= !clock;
logic [wid-1:0] plier, cand;
```

```
\leftarrow \rightarrow Fall 2014
                  \leftarrow \rightarrow Homework 3
                                               Homework Solution Sol Code
       logic [wid-1:0] plierp, candp;
       logic [2*wid-1:0] prod[NUM MULT];
       logic [2*wid-1:0] prodp[NUM MULT];
       mult behav 1 #(wid) mb1(prod[0], plier, cand);
                     #(wid,8) ms44(prod[1], plier, cand, clock);
       mult seq m
                     #(wid,3) ms43(prod[2], plier, cand, clock);
       <u>mult seq m</u>
       mult seq csa
                       #(wid) mc(prod[3], plier, cand, clock);
       <u>mult_seq_csa_m</u>
                         #(wid,4) mc4(prod[4], plier, cand, clock);
                         #(wid,1) mcl(prod[5], plier, cand, clock);
       <u>mult seq csa m</u>
       localparam int ppps_2 = 1;
                     #(wid,4) mp4(prodp[6], plierp, candp, clock);
       <u>mult_pipe</u>
                     #(wid,ppps_2) mp3(prodp[7], plierp, candp, clock);
       <u>mult_pipe</u>
       mult_pipe_ia #(wid,4) mpi4(prodp[8], plierp, candp, clock);
       mult pipe ia #(wid,ppps_2) mpi3(prodp[9], plierp, candp, clock);
       string names[] = '{"Behav_1",
                           "Seq m\overline{4}",
                           "Seq m3"
                           "Seq CSA",
                           "Seq CSA m4",
                           "Seg CSA m1",
                           "Pipelined m4"
                           "Pipelined m1",
                           "Pipelined IA m4"
                           "Pipelined IA m1"
                           };
       int err cnt[NUM MULT];
       // Array of multiplier/multiplicand values to try out.
       // After these values are used a random number generator will be used.
       11
       int tests[$] = {1,1, 1,2, 2,1, 'h10, 'h20, 1,32, 32, 1};
       initial begin
          clock = 0;
          for ( int i=0; i<num tests; i++ ) begin</pre>
             // Change input to pipelined units.
             11
             for ( int t=0; t<=wid; t++ ) begin</pre>
                plierp = t;
                candp = 256;
                 #2;
             end
             // Set multiplier and multiplicand values for non-piped units.
             11
             plier = tests.size() ? tests.pop front() : <u>$random();</u>
             cand = tests.size() ? tests.pop front() : <u>$random();</u>
             // Set multiplier and multiplicand values for piped units.
             11
             plierp = plier;
             candp = cand;
             // For pipelined units, copy output at the time it should be ready.
             11
             fork
```

hw03-sol.v.html

```
\leftarrow \ \rightarrow \ \text{Fall} \ 2014
                   \leftarrow \ \rightarrow \ \text{Homework} \ 3
                                                Homework Solution Sol Code
                 #(2 * wid/4) prod[6] = prodp[8];
                 #(2 * wid/4) prod[8] = prodp[8];
                 #(2 * ((wid+ppps_2-1)/ppps_2)) prod[7] = prodp[7];
                 #(2 * ((wid+ppps 2-1)/ppps 2)) prod[9] = prodp[9];
              join none
              if ( pipeline test exact ) begin
                 // Modify the inputs to the pipelined units in subsequent cycles.
                 11
                 for ( int t=0; t<=wid; t++ ) begin</pre>
                    #2
                    plierp = t;
                    candp = 1;
                 end
                 plierp = 0;
                 candp = 0;
              end
              #1000;
              // Make sure each module's output is correct.
              11
              for ( int mut=1; mut<NUM MULT; mut++ ) begin</pre>
                 if ( prod[0] !== prod[mut] ) begin
                    err_cnt[mut]++;
                    if ( err_cnt[mut] < err_limit )</pre>
                       $display("Error in %s test %4d: %x != %x (correct)\n",
                                 names[mut], i, prod[mut], prod[0]);
                 end
              end
          end
          // Tests completed, report error count for each device.
          //
          for ( int mut=1; mut<NUM MULT; mut++ ) begin</pre>
              $display("Mut %s, %d errors (%.1f%% of tests)\n",
                        names[mut], err cnt[mut],
                        100.0 * err cnt[mut]/real'(num tests) );
          end
```

hw03-sol.v.html

```
$finish(2);
```

end

```
endmodule
```

// cadence translate_on

LSU EE 4755

Homework 4 solution Due: 24 November 2014

Problem 0: Copy the code package from /home/faculty/koppel/pub/ee4755/hw/2014f/hw04. Verify that everything is working by running the simulation on the unmodified file. It should report that there is correct output but no compression:

Correct output, strings match. But no compression! In size 117 bytes, out size 117 bytes.

Problem 1: Module asc_to_bin is to filter a stream of ASCII characters so that ASCII decimal numbers are replaced by binary numbers preceded by an escape character. The idea is to reduce the size of data streams that contain lots of large numbers. For example, consider the sentence, "There are 31536000 seconds in a year." The module asc_to_bin should replace that sequence of eight ASCII characters 31536000 with an escape character and an integer encoding of the number.

The module has an 8-bit input and output for the character, char_in and char_out. There is a 1-bit input can_insert which is true when the module can read a character from char_in. If input insert_req is asserted when can_insert is true then the character on char_in will be read.

There is a 1-bit output can_remove which is true when the character on char_out is valid. (It would not be valid if the module does not contain any characters and for other reasons.) If input remove_req is set to 1 and can_remove is true then the character at char_out will change to the next character or, if that's the last available character, can_remove will go to zero.

There is also a 1-bit input reset. If reset is high at the positive edge of the clock then the module should reset itself.

Initially in the homework package, module asc_to_bin passes through characters unchanged. Modify it so that it converts ASCII decimal numbers to binary as described above.

At the end of the simulation the testbench will indicate whether the output string is correct, and the original and compressed sizes. For example, the output using the unmodified code package will be:

```
Correct output, strings match. But no compression!
```

In size 117 bytes, out size 117 bytes.

The testbench also provides a trace showing some information each time a character is removed. For the unmodified code,

```
ncsim> run
c 79 = 0
            tail
                  1 head
                           0
c 110 = n
            tail
                  3 head
                           1
            tail
                           2
c 101 = e
                  4 head
  32 =
                  7 head
                           3
с
            tail
  49 = 1
            tail
                  8 head
                          4
```

The character removed is shown as a decimal number and as a character, for example 110 and "n" for the second line. Also shown are the values of two objects in the asc_to_int module, tail and head. Feel free to add your own variables to the list. Search for "Trace execution" to find the code that prints this trace.

The parameter max_chars indicates the maximum size of the integer that should be created. Currently the testbench expects all integers to be of this size.

Keep the following in mind:

- Do not convert a number to binary if it would take more space than the original.
- The module must be synthesizable.
- The synthesized hardware must be reasonably efficient.

For extra credit, modify both the asc_to_bin module and the testbench so that asc_to_bin can compress a string of ASCII digits to the smallest integer (in multiple of bytes) that can hold the integer. (The current behavior is to use one size integer, determined by parameter max_chars.)

The complete solution can be found at /home/faculty/koppel/pub/ee4755/hw/2014f/hw04/hw04-sol.v and on the Web at http://www.ece.lsu.edu/koppel/v/2014/hw04-sol.v.html.

Encoding the incoming ASCII characters as an integer is straightforward. The tricky part is sending the encoded integer and escape character to the module outputs at the correct time. Remember that characters are removed from the module only when the external device requests them (asserts remove_req) so one can't assume that something that has just been read can immediately be sent to the output.

The following approach is used in the solution. Two registers hold the encoded binary values. The design encodes incoming digits as they arrive into register val_encode, a second register val_wait, holds completed integers that are worth using (the ASCII version is not too short).

Let's suppose the value of tail was 7 when the first ASCII digit of a suitable string of digits arrived. Normally, the first ASCII character of this string would be sent to the module output when head reaches 7. What we want instead is that the escape character be sent to the output, followed by the bytes of the binary number in subsequent cycles. The solution uses a new array, esc_here, to indicate that an encoded integer starts here. If esc_here[head] is 1 the module will output an escape character and will switch to using val_wait as the source of module outputs for the next max_chars characters. It then returns to using storage as the source of characters.

Array esc_here[tail] is set to zero each time a character is read. When the start of a string of digits is detected (see start_encoding) the tail location is saved in tail_at_enc_start. When encoding is to end (either due to a non-digit character or overflow, see end_encoding) if the encoded number can be used (ASCII number not too short, and val_wait is not being used, see use_encoding) then we set esc_here[tail_at_enc_start]=1.

The updating of the head pointer has not been modified: it's incremented at each remove_req. However tail is adjusted whenever an encoded value is to be used. If the encoding reduces the number of characters by x then x is subtracted from tail.

An alternative to using val_wait would be to write the escape character and encoded integer into storage. This would simplify the design by removing the multiplexor at the character output and the associated "drain" logic (see the solution code), but it would require a second write port for storage.

Problem 2: Synthesize your module.

(a) Indicate the cost and performance with and without timing optimization. (With timing optimization means using define_clock.)

See the table below. The column headed "Timing Constr" indicates the kind of timing optimization. None means that no timing constraints were specified and so there was no timing optimization. Reg -¿ Reg means that the Encounter define_clock command was used, and so timing was optimized from register outputs to register inputs. However the timing of paths starting at module inputs or leading to module outputs was ignored. For the column headed In, Reg -¿ Reg, Out the define_clock command was used and external_delay was also used to indicate the assumption that module inputs are available at the beginning of the clock cycle and that module outputs are expected to be available at the end of the clock cycle.

Without timing optimization the module is 20% cheaper but five times slower. The optimizations were performed with effort set to medium.

Module Name		Area	Clock	Timing
			Period	Constr
asc_to_bin_sol	4 4	206728	20084	None
asc_to_bin_sol	4 4	255460	3844	Reg -> Reg
asc_to_bin_sol	4 4	251736	3687	In, Reg -> Reg, Out

(b) Even if define_clock is used, the synthesis program won't optimize all paths, only those with both ends affected by the clock. Show how to use the Encounter external_delay command to get the proper timing optimization.

The first command below tells Encounter that all inputs are assumed to be available at the beginning of the clock period for my_clk (which needs to have been defined with define_clock). The second tells encounter that all outputs are expected to be stable at the end of the clock period. The stuff in the square brackets returns the list of ports, the port names could also have been typed by hand.

```
external_delay -clock my_clk -output 0 [find /designs/*/ports_out/ -port *]
external_delay -clock my_clk -input 0 [find /designs/*/ports_in/ -port *]
```

logic val_wait_full;

```
11
/// LSU EE 4755 Fall 2014 Homework 4
11
 /// SOLUTION
 // Assignment <u>http://www.ece.lsu.edu/koppel/v/2014f/hw04.pdf</u>
 /// The solution is in module asc to bin sol.
typedef enum { Char escape = 1, Char 0 = 48, Char 9 = 57 } Chars Special;
module asc to bin
  int size = 1 << size_lg )</pre>
  ( output [7:0] char_out,
output can_insert, can_remove,
input [7:0] char_in,
input insert_req, remove_req,
input reset, clk);
   logic [7:0] storage [size];
   logic [size_lg:1] head, tail;
   uwire is_digit = char_in >= Char_0 && char_in <= Char_9;</pre>
    uwire
              empty = head == tail;
             full = tail + 1 == head;
   uwire
   assign can_insert = !full;
   assign can_remove = !empty;
   assign char_out = storage[head];
    // cadence translate_off
    initial for ( int i=0; i<size; i++ ) storage[i] = 255;</pre>
    // cadence translate_on
   always @( posedge clk ) if ( reset ) begin
        tail <= 0;
   end else begin
       if ( insert_req ) begin
            storage[tail] = char_in;
            tail <= tail + 1;</pre>
       end
   end
    always @( posedge clk ) if ( reset ) begin
       head \leq 0:
   end else if ( remove_req ) begin
       head <= head + 1;</pre>
   end
endmodule
module asc_to_bin_sol
  #( int size_lg = 4,
    int max_chars = 4,
      int size = 1 << size_lg )</pre>
  ( output [7:0] char_out,
output can insert, can_remove,
input [7:0] char_in,
input insert_req, remove_req,
input reset, clk);
    // Storage for characters
   logic [7:0] storage [size];
    // Location at which encoded number should start. That is,
   // if esc_here[x] is 1, then storage[x] is the first character of
// an ASCII string that should be replaced with an escape character
    // and a binary encoded value;
    logic esc_here [size];
   // Register used for preparing encoded integer.
logic [max_chars-1:0][7:0] val_encode;
// Register for holding encoded integer until all characters removed.
logic [max_chars-1:0][7:0] val_wait;
    // True if val_wait holds a value that has not yet been read.
```

// Pointers into storage. // Pointers into storage.
logic [size_lg:1] head; // Location being read (sent to module output).
uwire [size_lg:1] write_idx; // Next location to write.
logic [size_lg:1] tail; // Possible next location to write.
logic [size_lg:1] tail_at_enc_start; // Note: encoding refers to the process of converting a string of // ASCII characters to an integer. uwire now_encoding, end_encoding; logic was_encoding; logic [7:0] ascii_int_len; // Note: draining refers to sending the bytes in val_wait to the // module outputs. logic draining; logic [<u>\$clog2</u>(max_chars)-1:0] drain_idx; uwire start_draining, end_draining; uwire empty, full; // cadence translate_off
initial for (int i=0; i<size; i++) storage[i] = 255;
// cadence translate_on</pre> /// Hardware For Encoding ASCII Digits into Binary 111 // Check whether a digit is present. 11 uwire is_digit = char_in >= Char_0 && char_in <= Char_9;</pre> uwire is_nz_digit = char_in > Char_0 && char_in <= Char_9; // Non-Zero</pre> // Convert ASCII digit to an integer. uwire [3:0] char_bin = char_in - Char_0; // Combine digit at char_in with current value of val_encode. 11 uwire [max_chars:0] [7:0] next_val_encode = val_encode * 10 + char_bin; uwire overflow = next_val_encode[max_chars] != 0; /// Hardware to Detect the Start, End, and Suitability of a String of Digits 11 logic was_digit; always @(posedge clk) if (reset) was digit <= 0;</pre> else if (insert_req) was_digit <= is_digit;</pre> // True if we should start encoding a string of digits. uwire start_encoding =
 insert_req && is_nz_digit && (!was_digit || overflow); assign now_encoding = start_encoding || was_encoding && !end_encoding; always @(posedge clk) was_encoding <= 0;</pre> if (reset) else if (insert_req) was_encoding <= now_encoding;</pre> // True if encoding should end, whether or not the encoding will be used. assign end_encoding insert_req && was_encoding && (!is_digit || overflow); // True if encoded integer should be used. // We don't want to do this if the ASCII string is too short, // or if val_wait is still occupied. uwire use_encoding = end_encoding && (ascii_int_len > max_chars) && (!val_wait_full || end_draining); // Update registers holding encoded integer, and those keeping // track of locations. always @(posedge clk) if (insert_req) begin if (start_encoding) begin // Initialize val encode with first character. val_encode <= char_bin;</pre> // Remember where ASCII digits started. tail_at_enc_start <= write_idx;</pre> // Keep track of how many digits there are. ascii_int_len <= 1;</pre> end else begin // Update registers assuming that we are continuing to
// encode. (It doesn't hurt if we are not currently encoding.)
val_encode <= next_val_encode;
ascii_int_len <= ascii_int_len + 1;</pre>

```
\leftarrow \ \rightarrow \ \text{Homework} \ 4
\leftarrow \rightarrow Fall 2014
                                                                                    Homework Solution Sol Code
              end
              // Move val_encode to a second register so that the next string of
// ASCII digits can be encoded without having to wait for this
// value to be removed.
              if ( use encoding ) val wait <= val encode;</pre>
          end
          ///
          /// Hardware for Writing Characters into Storage
          111
          // If the encoded integer is used we need to move the tail back by
         // the number of characters saved. That's easier to compute using
// the location at which the encoded number started.
uwire [size_lg:1] tail_adj = tail_at_enc_start + max_chars + 1;
          // Location at which to write current character.
          assign write_idx = use_encoding ? tail_adj : tail;
          /// Write the Storage and the Tail Pointer
          always @( posedge clk ) if ( reset ) begin
              tail <= 0;
          end else if ( insert_req ) begin
              // We've decided to use an encoded number. Remember where.
              // When head reaches tail_at_enc_start we will start sending
// the encoded number to the output.
              if ( use_encoding ) esc_here[tail_at_enc_start] <= 1;</pre>
              storage[write_idx] <= char_in;
esc_here[write_idx] <= 0;</pre>
              tail <= write_idx + 1;</pre>
          end
               Hardware For Removing Characters From Storage
          ///
          111
          /// Character Out Mux
          //
//
               The char_out port can be connected to three things:
          11
          11
                    A memory holding stored characters: storage[].
          //
                  - The escape character (a constant, Char_escape).
          11
                  - A register holding a number encoded in binary, val_wait.
          11
          assign char out =
                   start_draining ? Char_escape :
draining ? val_wait[drain_idx]
                                       : storage[head];
         assign start_draining = !empty && esc_here[head];
assign end_draining = remove_req && draining && drain_idx == 0;
          // Update the register that indicates whether val_wait is holding
          // something.
          always @( posedge clk )
            if ( reset ) val_wait_full <= 0;
else if ( use_encoding ) val_wait_full <= 1;
else if ( end_draining ) val_wait_full <= 0;</pre>
          always @( posedge clk ) if ( reset ) begin
              draining <= 0;
             drain_idx <= 0;
head <= 0;</pre>
          end else if ( remove_req ) begin
              draining <= start_draining ? 1 : drain_idx == 0 ? 0 : draining;</pre>
              head <= head + 1;</pre>
          end
          /// Hardware Related to Storage Full and Empty Status
          111
          assign empty = head == tail;
assign full = tail + 1 == head;
```

```
assign can_remove = !empty && ( !now_encoding || head != tail_at_enc_start );
assign can_insert = !full;
```

endmodule

```
// cadence translate_off
module testbench();

    localparam int elts_lg = 4;
    localparam int elts = 1 << elts_lg;
    localparam int int_chars = 2;

    uwire [7:0] char_out;
    uwire can_insert, can_remove;
    logic [7:0] char_in;
    logic insert_req, remove_req, reset, clk;
    asc_to_bin_sol #(elts_lg,int_chars) b1
        (char_out, can_insert, can_remove, char_in, insert_req, remove_req, reset, clk);</pre>
```

int cycle_num;

```
initial begin
    clk = 0;
    cycle_num = 0;
    fork
        forever #1 clk = !clk;
        forever @( posedge clk ) cycle_num++;
    join
end
```

string in_str = "One 1 two 12 three 317 four 1029 six 123456 ten 1234567890. There are 60 seconds in a minute and 31536000 in a year."
string out_str = "";

initial begin

```
automatic int insert_finished_cyc = 0;
automatic int out size = 0;
automatic bit tb_insert_done = 0;
automatic bit tb_remove_done = 0;
/// Reset the module.
11
reset = 0;
insert_req = 0;
remove_req = 0;
@( negedge clk ) reset = 1;
@( negedge clk ) reset = 0;
@( negedge clk );
/// Check for one possible error.
if ( can_insert !== 1 ) begin
    $display("Module did not reset, can_insert: %h\n", can_insert);
    $fatal(1);
end
/// Start Main Testing Loops
11
fork
    /// Watchdog -- Stop simulation if it's taking too long.
   fork begin
       automatic int cyc_limit = in_str.len() * 100;
       fork
           wait ( cycle_num == cyc_limit );
wait ( tb_insert_done && tb_remove_done );
       join any
        if ( cycle_num >= cyc_limit ) begin
           $display("Exceeded cycle limit, exiting.\n");
           $fatal(1);
       end
    end ioin none
    /// Trace Execution -- Print Signal Values After Interesting Changes
    while ( !tb_insert_done || !tb_remove_done ) begin
       @( insert_req or remove_req or can_insert or can_remove
        or bl.tail or bl.head or tb_insert_done or tb_remove_done );
       @( negedge clk );
       /// Trace execution by showing removed character and
       /// related information.
        11
       $display( "c In %c Out %d = %c tail %d head %d b2 %d",
                    char_in, char_out, char_out, b1.tail, b1.head, b1.val_wait);
```

/// Insert Characters begin automatic int in_pos = 0; while (in_pos < in_str.len()) begin</pre> @(negedge clk); // Flip a coin, and if it comes up tails send a character
// in if module is ready for one. 11 if ({\$random} & 'h1 && can_insert) begin char_in = in_str[in_pos++]; insert_req = 1; end else begin insert_req = 0; end end @(negedge clk); insert_req = 0; insert_finished_cyc = cycle_num; \$display("Done feeding inputs.");
tb_insert_done = 1; end /// Remove Characters // begin int buffer; automatic int bytes_remaining = 0; @(negedge clk); if ({<u>\$random</u>} & 1 && can_remove) begin remove_req = 1; out_size++; if (bytes_remaining > 0) begin buffer = (buffer << 8) + char_out;</pre> bytes_remaining--; if (bytes_remaining == 0) begin // Convert binary number back to ASCII. string iasc; iasc.itoa(buffer); out_str = {out_str,iasc}; end end else if (char_out == Char_escape) begin bytes_remaining = int_chars; buffer = 0;end else begin out_str = {out_str,char_out}; end end else begin remove_req = 0;end end \$display("Done gathering outputs.\n");
tb_remove_done = 1; end join if (in_str != out_str)
 <u>\$display(</u>"** Error - strings don't match.\n"); else

<u>\$finish(2);</u>

end

endmodule

// cadence translate_on

25 Spring 2001 Solutions

/// Solution to LSU EE 4702-1 Spring 2001 Homework 1

```
module priority_encoder_1_b(grant,found out,request,found in);
   output grant, found out;
   input request, found in;
          request, found_in;
   wire
          grant, found out;
   reg
   always @( request or found in ) begin
      found out = found in | request;
      grant = !found in & request;
   end
endmodule
module priority_encoder_1_es(grant, found out, request, found in);
   output grant, found out;
   input request, found in;
          grant, found out;
   wire
   wire
        request, found in;
   or ol(found_out, found_in, request);
   and al(grant, not_found_in, request);
   not n1(not found in, found in);
endmodule
module priority_encoder_1_is(grant, found out, request, found in);
   input request, found in;
   output grant, found_out;
          found_out = found in | request;
  wire
   wire
          grant
                  = !found in & request;
endmodule
module test_pe(done, okay_b, okay_is, okay_es);
   output done, okay b, okay is, okay es;
          done, okay b, okay is, okay es;
   reg
         request, found in;
   reg
   wire grant b, found out b;
   wire grant_is, found_out_is;
   wire grant es, found out es;
   priority_encoder_1_b peb(grant_b,found_out_b,request,found_in);
   priority_encoder_1_es pees(grant_es,found_out_es,request,found_in);
   priority encoder 1 is peis(grant is,found out is,request,found in);
   reg [1:0] answers [0:3];
   integer
             i;
   initial begin
      done
             = 0;
      okay_b = 1; okay_es = 1; okay_is = 1;
      answers[2'b00] = 2'b00;
      answers[2'b01] = 2'b01;
      answers[2'b10] = 2'b11;
```

```
answers[2'b11] = 2'b01;
   for(i=0; i<4; i=i+1) begin</pre>
       {request, found_in } = i;
       #1;
       if( {grant_b,found_out_b} !== answers[i] ) okay_b = 0;
       if( {grant_is,found_out_is} !== answers[i] ) okay_is = 0;
if( {grant_es,found_out_es} !== answers[i] ) okay_es = 0;
    end // for (i=0; i<4; i=i+1)</pre>
   done = 1;
end // initial begin
```

endmodule // test_pe

/// Solution to LSU EE 4702-1 Spring 2001 Homework 3

// Includes a testbench (which was not graded).

`timescale lus/lus

```
module microwave_oven_controller(beep,dmt,dmu,dst,dsu,mag_on,key_code,clk);
   input key code;
                                     // Key begin pressed (see parameters).
   input clk; // A 64 Hz clock.
output mag_on; // When 1, magnetron is on (oven is heating).
output beep; // When 1, emit tone.
output dmt; // Tens digit of minute display.
output dmu; // Units digit of minute display.
output dst, dsu; // Tens and units digits of seconds display.
   wire clk;
   wire [5:0] key_code;
   reg [3:0] dmt, dmu, dst, dsu;
   reg
                mag_on;
   parameter key_none = 6'd0; // No key pressed.
   parameter key_never = 6'd1; // This code will never be returned.
   parameter key_start = 6'd10;
   parameter key_reset = 6'd11;
parameter key_power = 6'd12;
   parameter key_0 = 6'd20;
   parameter key 1 = 6'd21;
   parameter key_2 = 6'd22;
   parameter key_3 = 6'd23;
   parameter key_4 = 6'd24;
parameter key_5 = 6'd25;
parameter key_6 = 6'd26;
   parameter key_7 = 6'd27;
   parameter key_8 = 6'd28;
   parameter key_9 = 6'd29;
   /// States
   11
   parameter st reset = 0;
   parameter st_entry_1 = 1; // One digit entered.
   parameter st_entry_1p = 2; // One digit and power.
   parameter st_entry_n = 3;
parameter st_heating = 4;
                                     // At least 2 digits (including power level).
   parameter st_paused = 5;
   reg [3:0] state, next state;
   reg [2:0] digit count; // Number of digits entered.
   reg [3:0]
                power;
                                      // Power level set by user.
   reg [5:0] key_type;
                                      // Type of key. (unless digit, key_code)
   parameter kty_digit = 6'd30;
   // Number of tics before beep stops. Zero if not beeping.
   11
   reg [7:0] beep timer;
                 beep = | beep timer;
   assign
   always @( posedge clk ) if( beep timer ) beep timer = beep timer - 1;
```

```
// Add Digit to Display
11
task add_digit;
   begin
      dmt = dmu;
      dmu = dst;
      dst = dsu;
      dsu = key_code - key_0;
      digit_count = digit_count + 1;
   end
endtask // add_digit
// Actions when switching to st_reset, including setting next_state.
11
task do_reset;
   begin
      dmt = 0;
      dmu = 0;
      dst = 0;
      dsu = 0;
      digit_count = 0;
      beep_timer = 0;
      next_state = st_reset;
      mag_on = 0;
   end
endtask // do_reset
initial begin do_reset; state = st_reset; end
/// State Transitions
11
always @( key_code ) if( key_code != key_none ) begin
   key_type = key_code >= key_0 && key_code <= key_9</pre>
              ? kty_digit : key_code;
   casez( {state, key type} )
     {st_reset,kty_digit}:
       begin
          add digit;
          power = 10;
          next state = st entry 1;
       end
     {st_entry_lp,kty_digit}:
       begin
          dsu = 0;
          add digit;
          next state = st entry n;
       end
     {st_entry_n,kty_digit}:
       begin
          if( digit_count == 4 )
            beep_timer = 16;
          else
            add digit;
          next_state = state;
       end
     {st_entry_1,kty_digit}:
       begin
```

```
add digit;
          next state = st entry n;
       end
     {st_entry_1,key_power}:
       begin
          power = dsu;
          next_state = st_entry_1p;
       end
     {st_entry_n,key_start}, {st_entry_1,key_start}:
       begin
          if(dst > 5)
            begin
               beep_timer = 16;
               next_state = state;
            end else
              next_state = st_heating;
       end
     {st_heating,key_reset}:
       begin
          disable HEAT LOOP;
          next state = st paused;
       end
     {st_paused,key_start}:
       begin
          next_state = st_heating;
       end
     {4'b????,key reset}: do reset;
     default: beep timer = 16;
   endcase // casez( {state, key_type} )
   state = next state;
end // if ( key code != key none )
// Clock Divider
11
// Divides 64 Hz clock by 64 so that sec timer == 0 once per second.
11
reg [5:0] sec timer;
initial sec timer = 0;
always @( posedge clk ) sec timer = sec timer + 1;
always wait( state == st heating ) begin
   fork:HEAT LOOP
     reg [7:0] on_timer, off_timer;
     // Turn magnetron on and off.
     11
     forever begin
        on_timer = power * 64 * 2.5 / 10;
        off_timer = 64 * 2.5 - on_timer;
        mag_on
                 = 1;
        while ( on_timer ) @( posedge clk ) on_timer = on_timer - 1;
        if( off timer ) begin
           mag on = 0;
```

```
hw03 sol.html
```

```
while ( off timer ) @( posedge clk ) off_timer = off_timer - 1;
           end
        end
         // Update display during heating.
         11
         forever @( posedge | sec timer ) begin:T
            if( {dmt,dmu,dst,dsu} == 0 ) begin
               beep_timer = 128;
               state = st_reset;
               mag on \leq 0;
               disable HEAT_LOOP;
            end
            if( dsu ) begin dsu = dsu - 1; disable T; end
            dsu = 9;
            if( dst ) begin dst = dst - 1; disable T; end
            dst = 5;
            if( dmu ) begin dmu = dmu - 1; disable T; end
            dmu = 9;
            if (dmt) dmt = dmt - 1;
         end // block: T
      join
      mag on = 0;
   end // always wait
endmodule // microwave_oven_controller
module test oven();
   reg clk;
```

```
wire [3:0] dmt, dmu, dst, dsu;
          mag_on;
wire
reg [5:0] key mod;
reg
           reset;
// Set this to 1 to have each change in the oven display appear
// on the console.
          monitor_display;
reg
// Set this to one to have each key press appear on the console.
          monitor_keys;
reg
// Set this to one to get long test.
reg
           patient;
microwave oven controller oven(beep,dmt,dmu,dst,dsu,mag on,key mod,clk);
time
           tics;
initial tics = 0;
always begin clk = 0; #5625; tics = tics + 1; #0; clk=1; #10000; end
parameter
           ss_reset = 3'd0;
           ss_digit1 = 3'd1; // Single digit, power not entered.
parameter
           ss_digit2 = 3'd2; // Power entered or > 1 digit.
parameter
           ss_cook = 3'd3;
parameter
           ss_pause = 3'd4;
parameter
            kty_digit = 6'd30;
parameter
reg [15:0] shadow_display, alt_display;
reg [2:0] shadow_state;
```

```
\leftarrow \rightarrow Homework 3
                                              Homework Sol Code
\leftarrow \rightarrow Spring 2001
       integer
                 shadow secs, mod secs, delta;
                 shadow tics, pause tics, start tics;
       integer
                 shadow power, shadow digits;
       integer
                expected beep done, expecting done beep;
       integer
       integer
                 watch display;
                 error display, error mag, error beep, error total;
       integer
    `include "oven keys.v"
       function integer abs;
          input a;
          integer a;
          abs = a < 0 ? -a : a;
       endfunction // abs
    `define check_digit(d,l)
       if((d) > (l) || (d) < 0) begin
          error_display = error_display + 1;
          secs = -1;
          disable tosecs;
                           end
       // Convert time on display to seconds.
       11
       task tosecs;
          output secs;
          integer secs;
          begin
              check digit(dmt,9)
             `check digit(dmu,9)
             `check_digit(dst,5)
             `check digit(dsu,9)
             secs = dmt * 600 + dmu * 60 + dst * 10 + dsu;
          end
       endtask // tosecs
       /// Listen Beep
       11
       always @( beep )
         if( beep ) begin
            if( expecting done beep )
              begin
                 expected beep_done = 128;
                 expecting_done_beep = 0;
              end
            if( expected beep done == 0 ) begin
               $display("Should not be beeping.");
               error_beep = error_beep + 1;
            end
         end else begin:B // if ( beep )
            integer delta;
            delta = abs( tics - expected_beep_done );
            if( shadow state != ss reset
                && expected beep done && delta > 5 ) begin
               $display("Beep wrong time. %d",delta);
               error_beep = error_beep + 1;
            end
            expected_beep_done = 0;
         end
```

hw03 sol.html

/

/

١

١

```
/// Watch Magnetron
//
integer mag on start, mag on total;
always @( mag on )
  if( mag_on ) begin
     if( shadow_state != ss_cook )
       begin
          $display("Mag on when cooking off.");
          error_mag = error_mag + 1;
       end
     if( mag on start != 0 ) begin:A
        integer cycle this;
        cycle_this = tics - mag_on_start;
        if (shadow power > 0 && shadow power < 10
            && abs( cycle_this - 160 ) > 10 )
          begin
             $display("Mag cycle error.");
             error mag = error mag + 1;
          end
     end
     mag_on_start = tics;
  end else begin // if ( mag_on )
    mag_on_total = mag_on_total + tics - mag_on_start;
 end // else: !if( mag_on )
// Verify correct magnetron-on time.
11
task verify_cooking;
   begin:A
      integer correct mag tics;
      integer delta;
      correct mag tics = shadow tics * shadow power / 10;
      delta = abs(correct mag tics - mag on total);
      if( delta > 128 ) begin
         $display("Wrong power level. %d %d ",
                  correct_mag_tics, mag_on_total);
         error_mag = error_mag + 1;
      end
   end // block: A
endtask // verify cooking
/// Watch display, etc.
11
always @( dmt or dmu or dst or dsu or shadow display ) #1 begin
   if( monitor display ) $display("Display: %d%d:%d%d",dmt,dmu,dst,dsu);
   if( shadow_state == ss_cook ) begin
      shadow secs = shadow secs - 1;
      shadow_tics = shadow_tics + 64;
      tosecs(mod secs);
      if( mod_secs !== shadow_secs )
        begin
           $display("Wrong count. (cooking)");
           error_display = error_display + 1;
        end
```

```
delta = shadow tics - ( tics - start tics );
      if(abs(delta) > 96)
        begin
           $display("More than 96 tics off: %d",delta);
           error display = error display + 1;
        end
      if ( shadow secs == 0 ) begin
         expecting_done_beep = 1;
         delay(1.5);
         verify_cooking;
         if( expecting_done_beep ) begin
            $display("End of cooking beep missing.");
            error_beep = error_beep + 1;
         end
         shadow_state = ss_reset;
         shadow_digits = 0;
      end // if ( shadow_secs == 0 )
   end else if ( shadow_state == ss_pause ) begin
      tosecs(mod secs);
      if( mod secs !== shadow secs ) begin
         $display("Wrong count. (paused)");
         error_display = error_display + 1;
      end
   end else if ( watch_display ) begin
      if( {dmt,dmu,dst,dsu} !== shadow display
          && {dmt,dmu,dst,dsu} !== alt display ) begin
        $display("Wrong display, should be %h", shadow display);
         error display = error display + 1;
      end
   end
end
   Reset shadow state and expected outputs maintained by
//
//
   testbench.
//
task to reset;
   begin
      shadow digits = 0;
      shadow_state = ss_reset;
      alt_display = shadow_display;
      shadow_display = 0;
      shadow power = 10;
      watch_display = 1;
   end
endtask // to_reset
// Send keys to module, update correct state and expected output information.
11
task command;
   input [799:0] cmd;
```

```
integer initialized;
integer c;
integer consec_reset;
reg [5:0] to_key [0:255];
reg [5:0] key;
```

```
begin
   if( initialized === 'bx ) begin
      for( c = 0; c < 256; c = c + 1 ) to_key[c] = key_never;</pre>
      for( c = 0; c < 10; c = c + 1) to key[ "0" + c] = key 0 + c;
      to key["s"] = key start;
      to_key["r"] = key_reset;
      to_key["p"] = key_power;
      to_key[" "] = key_none;
      to_key[0] = key_none;
      initialized = 1;
      consec_reset = 0;
  end // if ( initialized === 'bx )
  while( cmd ) begin:COMMAND LOOP
      reg [7:0] c;
      reg [5:0] key_type;
      c = cmd[799:792];
      key_mod = to_key[ c ];
      key = key mod;
      key_type = ( c >= "0" && c <= "9" ) ? kty_digit : key_mod;</pre>
      if( key == key_never ) begin
         $display("Testbench error: illegal key in command, %s (%d)",c,c);
         $stop;
      end
      casez( {shadow state,key type} )
        {3'b???,key_none}:;
        {ss_reset,key_reset}:
          begin
             to_reset;
          end
        {ss reset,kty digit}:
          begin
             shadow digits = 1;
             shadow state = ss digit1;
             alt display = shadow display;
             shadow display = key-key 0;
          end
        {ss_pause,key_reset},
        {ss_digit1,key_reset},
        {ss digit2,key reset}:
          begin
             to_reset;
          end
        {ss_digit1,kty_digit}:
          begin
             shadow_digits = 2;
             shadow_state = ss_digit2;
             alt_display = shadow_display;
             shadow_display = (shadow_display << 4) | key-key_0;</pre>
          end
```

```
\leftarrow \ \rightarrow \ {\rm Spring} \ 2001 \quad \leftarrow \ \rightarrow \ {\rm Homework} \ 3 \qquad \qquad {\rm Homework} \ {\rm Sol} \ {\rm Code}
```

```
{ss digit1,key power}:
    begin
       shadow state = ss digit2;
       shadow digits = 0;
       alt_display = shadow_display; // Power level.
       shadow power = shadow display;
       shadow display = 0;
    end
  {ss_digit1,key_start},{ss_digit2,key_start}:
    begin
       if (shadow display [7:4] > 5)
         begin
            expected_beep_done = tics + 16;
         end else begin
            tosecs(shadow secs);
            start_tics = tics;
            shadow_tics = 0;
            mag_on_total = 0;
            mag_on_start = 0;
            shadow_state = ss_cook;
         end
    end
  {ss_digit2,kty_digit}:
    if( shadow digits == 4 )
      expected_beep_done = tics + 16;
    else
      begin
         shadow_digits = shadow_digits + 1;
         // If shadow display zero then power was pressed.
         if( shadow display ) alt display = shadow display;
         shadow display = (shadow display << 4) | key-key 0;</pre>
      end
  {ss_cook,key_reset}:
    begin
       shadow state = ss pause;
       pause_tics = tics;
    end
  {ss pause,key start}:
    begin
       verify_cooking;
       mag on start = 0;
       shadow tics = 0;
       mag on total = 0;
       start tics = tics;
       shadow state = ss cook;
    end
  default:
    begin
       if( expected beep done && expected beep done < tics )
         begin
            $display("Missed a beep. (overlap)");
            error_beep = error_beep + 1;
         end
       expected_beep_done = tics + 16;
    end
endcase // casez( {shadow_state,key_type} )
@( posedge clk ) @( negedge clk );
repeat ( <u>$random()</u> & 15 + 3 ) @( negedge clk );
```

```
\leftarrow \rightarrow Spring 2001
                 \leftarrow \rightarrow Homework 3
                                              Homework Sol Code
                key mod = key none;
                @( posedge clk ) @( negedge clk );
                @( posedge clk ) @( negedge clk );
                if( key != key none )
                  consec reset = key == key reset ? consec reset + 1 : 0;
                if( monitor keys && key != key none && consec reset < 2 )
                  $display("Key %s State %d, Display: %d%d:%d%d B %d",
                            c,shadow_state, dmt,dmu,dst,dsu,beep);
                cmd = cmd \ll 8;
             end // block: COMMAND_LOOP
          end
       endtask // command
       // Reset oven module either using reset line or
       // reset button.
       11
       task reset_oven;
          input hard;
          begin
             if( 0 && hard ) begin
                reset = 1;
                fork:F
                  begin repeat ( 256 ) @( clk ); disable F; end
                   wait( !beep );
                   wait( !mag_on );
                join
                reset = 0;
             end else begin
                command("rrrrrr");
                fork
                   wait( !beep );
                   wait( !mag on );
                join
                command("rrrrr");
             end // else: !if( 0 && hard )
             if( beep || mag on )
               begin
                  $display("Could not reset oven.");
               end
          end
       endtask // reset_oven
       // Actions to be done at the end of a test.
       11
       task endtest;
          input [159:0] name;
          begin
             if( expected_beep_done )
               begin
                  if( expected_beep_done >= tics )
                    sdisplay("Testbench not waiting long enough for beep.");
                  $display("Missed a beep.");
                  error_beep = error_beep + 1;
                  expected_beep_done = 0;
               end
             if( {dmt,dmu,dst,dsu}!==0 )
```

```
begin
           $display("Expected to be finished.");
           error display = error display + 1;
        end
      watch display = 0;
      $display("Test %s completed. (dsp,beep,mag) (%d,%d,%d)",
               name,
               error_display, error_beep, error_mag);
      error_total = error_total + error_display + error_beep + error_mag;
      reset_oven(0);
      error display = 0;
      error_beep = 0;
      error_mag = 0;
   end
endtask // endtest
task delay;
   input [63:0] secs;
   #( secs * 1000000 );
endtask // delay
initial begin
   monitor_display = 0;
   monitor_keys = 0;
   patient = 0;
   expected beep done = 0;
   expecting done beep = 0;
   error display = 0;
   error beep = 0;
   error mag = 0;
   error total = 0;
   #1;
   to reset;
   reset oven(1);
   command("50prr");
   delay(40);
   endtest("Power Too High");
   command("12s"); delay(16);
   endtest("Basic");
   if( patient ) begin
      sdisplay("Starting test Long, be patient or modify testbench.");
      command("100s"); delay(90*60+5);
      endtest("Long");
   end
   command("30s"); delay(14);
   command("1"); delay(2); command("p");
   delay(20);
   endtest("Basic Disturbed");
   command("5p30s");
   delay(40);
   endtest("Half Power");
```

```
command("9p3p0s");
      delay(40);
      endtest("Power Twice");
      command("3ppp19s");
      delay(40);
      endtest("Power Thrice");
      command("20s");
      delay(10);
      command("r");
      delay(5);
      command("s");
      delay(10);
      endtest("Reset Start");
      command("20s");
      delay(10);
      command("r");
      delay(5);
      command("r");
      delay(1);
      endtest("Reset Reset");
      command("s");
      delay(5);
      endtest("Null Start");
      command("ps");
      delay(5);
      endtest("Null Power Start");
      command("7p30s"); delay(10);
      command("1"); delay(2); command("s"); delay(3);
      command("12344321");
      delay(40);
      endtest("Power Disturbed");
      command("12r5s"); delay(10);
      endtest("Twelve no 5");
      command("90s"); delay(1); command("rr");
      endtest("Ninety Seconds");
      command("12345rr");
      endtest("Display Overflow");
      $display("All tests completed, %d total errors.",error total);
      $stop;
   end // initial begin
endmodule // test oven
```
/// Solution to LSU EE 4702-1 Spring 2001 Homework 4

/// ///

// Includes a testbench (which was not graded).

`timescale lus/lus

module microwave_oven_controller(beep,dmt,dmu,dst,dsu,mag_on,

```
key code,reset,clk);
                                          // Key begin pressed (see parameters).
input key code;
                                          // Can be tested on the positive edge of clk.
input reset;
input reset;
input clk;
output mag_on;
output beep;
output dmt;
output dmt;
output dmu;
output dst, dsu;
// Can be tested on the positive edge of ctk.
// Reset signal. Can be tested on posedge clk.
// A 64 Hz clock. (Did Edison consider it?)
o/ When 1, magnetron is on (oven is heating).
// When 1, emit tone.
// Tens digit of minute display.
// Units digit of minute display.
// Tens and units digits of seconds display.
wire clk;
wire [5:0] key_code;
reg [3:0] dmt, dmu, dst, dsu;
reg
                mag_on;
                beep;
reg
parameter key_none = 6'd0; // No key pressed.
parameter key_never = 6'd1; // This code will never be returned.
parameter key_start = 6'd10;
parameter key reset = 6'd11;
parameter key_power = 6'd12;
parameter key_0 = 6'd20;
parameter key_1 = 6'd21;
parameter key_2 = 6'd22;
parameter key_3 = 6'd23;
parameter key_4 = 6'd24;
parameter key 5 = 6'd25;
parameter key_6 = 6'd26;
parameter key 7 = 6'd27;
parameter key_8 = 6'd28;
parameter key_9 = 6'd29;
parameter kty_digit = 6'd30;
parameter st_reset
                                 = 0;
parameter st_entry
                              = 1;
parameter st_entry_p1 = 2;
parameter st_entry_p2 = 5;
parameter st_heating = 3;
parameter st_paused = 4;
reg [2:0]
                digit count;
reg [3:0]
                power;
               key_type, last_key;
reg [5:0]
reg [3:0] state, next state;
reg [7:0] beep_timer;
task add_digit;
     begin
         if( digit count == 4 )
```

```
beep timer = 16;
      else begin
         dmt = dmu;
         dmu = dst;
         dst = dsu;
         dsu = key_code - key_0;
         digit_count = digit_count + 1;
      end
   end
endtask // add_digit
task do_reset;
   begin
      dmt = 0;
      dmu = 0;
      dst = 0;
      dsu = 0;
      digit_count = 0;
      beep_timer = 0;
      next state = st reset;
      mag_on = 0;
   end
endtask // do_reset
reg [7:0] on_timer, off_timer;
reg [5:0] sec_timer;
always @( posedge clk )
  if( reset ) begin
     do_reset;
     state
             = st_reset;
     sec timer = 0;
     on timer = 0;
     off timer = 0;
     last key = key none;
              = 0;
     beep
  end else begin // if ( reset )
     if ( key code != key none && last key == key none ) begin
        if( key_code >= key_0 && key_code <= key_9 )</pre>
          key_type = kty_digit;
        else
          key_type = key_code;
        casez( {state, key_type} )
          {st_reset,kty_digit}:
            begin
               add_digit;
               power = 10;
               next state = st entry;
            end
          {st_entry_p1,kty_digit}:
            begin
               dsu = 0;
               add digit;
               next_state = st_entry_p2;
            end
          {st_entry_p2,kty_digit}:
            begin
```

 $\leftarrow \rightarrow$ Spring 2001

 $\leftarrow \rightarrow$ Homework 4

```
add digit;
          next state = state;
       end
     {st entry,kty digit}:
       begin
          add digit;
          next_state = state;
       end
     {st_entry,key_power}:
       begin
          if( digit_count == 1 )
            power = dsu;
          else
            beep timer = 16;
          next_state = st_entry_p1;
       end
     {st_entry_p2,key_start}, {st_entry,key_start}:
       begin
          next_state = st_heating;
       end
     {st_paused,key_start}:
       begin
          next_state = st_heating;
       end
     // Leonardo incorrectly infers parallel case, so need
     // to test state.
     {4'b????,key_reset}:
       if( state == st heating )
         next state = st paused;
       else
         do_reset;
     default:
       begin
          next state = state; beep timer = 16;
       end
   endcase // casez( {state, key type} )
end // if ( key code != key none && last key == key none )
// next state may be reassigned below.
sec timer = sec timer + 1;
beep = | beep timer;
if( beep timer ) beep timer = beep timer - 1;
if( state == st_heating ) begin
   if( {dmt,dmu,dst,dsu} == 0 ) begin
      beep_timer = 128;
      mag_on = 0;
      next_state = st_reset;
   end else begin
      if( !sec_timer ) begin:T
         if( dsu ) begin dsu = dsu - 1; disable T; end
         dsu = 9;
         if( dst ) begin dst = dst - 1; disable T; end
```

```
\leftarrow \rightarrow Homework 4
                                               Homework Sol Code
\leftarrow \rightarrow Spring 2001
                      dst = 5;
                      if( dmu ) begin dmu = dmu - 1; disable T; end
                      dmu = 9;
                      if (dmt) dmt = dmt - 1;
                   end
                   if( on timer )
                                          on timer = on timer - 1;
                   else if( off timer ) off timer = off timer - 1;
                   mag_on = |on_timer | ~|off_timer;
                   if( !on_timer && !off_timer ) begin
                      on_timer = power * 16;
                      off_timer = 160 - on_timer;
                   end
                end // else: !if( {dmt,dmu,dst,dsu} == 0 )
            end else begin // if ( state == st_heating )
                on_timer = 0;
                off_timer = 0;
                mag_on = 0;
            end // else: !if( state == st heating )
```

```
endmodule // microwave_oven_controller
```

last_key = key_code; state = next_state;

end // else: !if(reset)

```
module test oven();
```

// exemplar translate off

```
reg clk;
wire [3:0] dmt, dmu, dst, dsu;
wire
          mag on;
reg [5:0] key mod;
          reset;
reg
// Set this to 1 to have each change in the oven display appear
// on the console.
reg
          monitor display;
// Set this to one to have each key press appear on the console.
          monitor keys;
reg
          monitor beep;
reg
          monitor mag;
reg
// Set this to one to get long test.
          patient;
reg
microwave oven controller oven(beep,dmt,dmu,dst,dsu,mag on,key mod,reset,clk);
time
          tics;
wire [15:0] mod_digits = {dmt,dmu,dst,dsu};
initial tics = 0;
always begin clk = 0; #5625; tics = tics + 1; #0; clk=1; #10000; end
parameter ss reset = 3'd0;
parameter ss_digit1 = 3'd1; // Single digit, power not entered.
parameter ss_digit2 = 3'd2; // Power entered or > 1 digit.
          ss_cook = 3'd3;
parameter
           ss_pause = 3'd4;
parameter
```

/

\ \

١

```
parameter kty_digit = 6'd30;
  reg [15:0] shadow display, alt display;
  integer
              alt disp stale;
  reg [2:0] shadow state;
  integer shadow secs, mod secs, delta;
            shadow tics, pause tics, start tics;
  integer
            shadow power, shadow digits;
  integer
  integer expected_beep_done, expecting_done_beep;
  integer
            watch display;
  reg [7:0] error_display, error_mag, error_beep;
  integer error_total;
  reg [7:0] error_beep_total, error_mag_total, error_display_total;
  parameter key_none = 6'd0; // No key pressed.
  parameter key_never = 6'd1; // This code will never be returned.
  parameter key_start = 6'd10;
  parameter key_reset = 6'd11;
  parameter key_power = 6'd12;
  parameter key 0 = 6'd20;
  parameter key_1 = 6'd21;
  parameter key 2 = 6'd22;
  parameter key_3 = 6'd23;
  parameter key_4 = 6'd24;
  parameter key_5 = 6'd25;
  parameter key_6 = 6'd26;
  parameter key 7 = 6'd27;
  parameter key_8 = 6'd28;
  parameter key_9 = 6'd29;
  parameter show_key = 0;
  function integer abs;
     input a;
     integer a;
     abs = a < 0 ? -a : a;
  endfunction // abs
`define check_digit(d,l)
  if((d) > (l) || (d) < 0) begin
     error display = error display | 1;
     secs = -1;
     disable tosecs;
  end
  // Convert time on display to seconds.
  11
  task tosecs;
     output secs;
     integer secs;
     begin
         check_digit(dmt,9)
         `check_digit(dmu,9)
         `check_digit(dst,5)`
         `check_digit(dsu,9)
        secs = dmt * 600 + dmu * 60 + dst * 10 + dsu;
     end
```

```
/// Listen Beep
11
always @( beep )
  if( beep ) begin
     if( monitor beep ) <u>$display("Beep starting.");</u>
     if( expecting_done_beep )
       begin
          expected beep done = 128;
          expecting_done_beep = 0;
       end
     if( expected_beep_done == 0 ) begin
        $display("Should not be beeping.");
        error beep = error beep | 1;
     end
  end else begin:B // if ( beep )
     integer delta;
     if( monitor_beep ) <u>$display("Beep ending.");</u>
     delta = abs( tics - expected beep done );
     if( shadow state != ss reset
         && expected beep done && delta > 5 ) begin
        $display("Beep wrong time. %d",delta);
        error_beep = error_beep | 2;
     end
     expected_beep_done = 0;
 end
/// Watch Magnetron
integer mag on start, mag on total;
always @( mag on )
  if( mag on ) begin
     if( monitor mag ) $display("Mag on.");
     if( shadow state != ss cook )
       begin
          $display("Mag on when cooking off.");
          error mag = error mag | 1;
       end
     if( mag on start != 0 ) begin:A
        integer cycle_this;
        cycle this = tics - mag on start;
        if (shadow power > 0 && shadow power < 10
            && abs( cycle_this - 160 ) > 10 )
          begin
             $display("Mag cycle error.");
             error mag = error mag | 2;
          end
     end
     mag on start = tics;
  end else begin // if ( mag_on )
     if( monitor_mag ) <u>$display("Mag off.");</u>
     mag on total = mag on total + tics - mag on start;
 end // else: !if( mag on )
/// Verify correct magnetron-on time.
11
task verify_cooking;
   begin:A
      integer correct_mag_tics;
      integer delta;
      correct_mag_tics = shadow_tics * shadow_power / 10;
```

```
\leftarrow \rightarrow Spring 2001 \leftarrow \rightarrow Homework 4 Homework Sol Code
```

```
hw04 sol.html
```

```
delta = abs(correct mag tics - mag on total);
      if( mag on ) begin
         $display("Mag should be off.");
         error mag = error mag | 'h10;
      end
      if (delta > 128) begin
         $display("Wrong power level. %d %d ",
                  correct_mag_tics, mag_on_total);
         error_mag = error_mag | 4;
      end
   end // block: A
endtask // verify_cooking
/// Watch display, etc.
11
always @( dmt or dmu or dst or dsu or shadow display ) #1 begin
   if( monitor display )
     $display("Display: %h
                             sh: %h alt: %h
                                                secs %d, state %d",
              mod_digits, shadow_display,alt_display,
              shadow_secs, shadow_state);
   if( shadow_state == ss_cook ) begin
      shadow_secs = shadow_secs - 1;
      shadow tics = shadow tics + 64;
      tosecs(mod_secs);
      if( mod secs !== shadow secs )
        begin
           $display("Wrong count. (cooking)");
           error display = error display | 4;
        end
      delta = shadow tics - ( tics - start tics );
      if(abs(delta) > 96)
        beain
           $display("More than 96 tics off: %d",delta);
           error display = error display | 2;
        end
      if( mod digits == 0 ) begin
         expecting done beep = 1;
         delay(1.5);
         verify_cooking;
         if( expecting_done_beep ) begin
            $display("End of cooking beep missing.");
            error_beep = error_beep | 4;
         end
         shadow_state = ss_reset;
         shadow display = 0;
      end else if ( shadow secs == 0 )
        begin
           $display("Count problem.");
        end
   end else if ( shadow_state == ss_pause ) begin
      tosecs(mod secs);
      if( mod_secs !== shadow_secs ) begin
         $display("Wrong count. (paused)");
         error display = error display | 8;
```

```
end
   end else if ( watch display ) begin
      if ( mod digits !== shadow display
         && ( alt disp stale <= tics || mod digits !== alt display ) )
       begin
         shadow_display,alt_display,mod_digits);
        error_display = error_display | 'h10;
     end
   end
end
   Reset shadow state and expected outputs maintained by
//
// testbench.
//
task to_reset;
   begin
      shadow_digits = 0;
      alt_display = shadow_display;
     alt disp stale = tics + 2;
      shadow_state = ss_reset;
      shadow_display = 0;
      shadow_power = 10;
     watch display = 1;
   end
endtask // to_reset
// Send keys to module, update correct state and expected output information.
11
task command;
   input [799:0] cmd;
   integer initialized;
   integer c;
   integer consec reset;
   reg [5:0] to_key [0:255];
   reg [5:0] key;
   begin
      if( initialized === 'bx ) begin
         for( c = 0; c < 256; c = c + 1 ) to key[c] = key never;
         for( c = 0; c < 10; c = c + 1) to key[ "0" + c] = key 0 + c;
         to key["s"] = key start;
        to_key["r"] = key_reset;
        to_key["p"] = key_power;
to_key[""] = key_none;
         to key[0] = key none;
         initialized = 1;
         consec reset = 0;
     end // if ( initialized === 'bx )
     while( cmd ) begin:COMMAND LOOP
         reg [7:0] c;
         reg [5:0] key_type;
```

```
Homework Sol Code
\leftarrow \rightarrow Spring 2001
                \leftarrow \rightarrow Homework 4
                c = cmd[799:792];
                 cmd = cmd \ll 8;
                 if( c == 0 || c == " " ) disable COMMAND LOOP;
                 key mod = to key[ c ];
                 key = key mod;
                 key type = ( c >= "0" && c <= "9" ) ? kty digit : key mod;
                 if( key == key_never ) begin
                    sdisplay("Testbench error: illegal key in command, %s (%d)",c,c);
                    $stop;
                 end
                 if( key != key_none )
                   consec_reset = key == key_reset ? consec_reset + 1 : 0;
                 if( monitor_keys && key != key_none && consec_reset < 3 )</pre>
                   $display("Key %s ", c);
                 casez( {shadow_state,key_type} )
                   {3'b???,key none}:;
                   {ss_reset,key_reset}:
                     begin
                        to reset;
                     end
                   {ss_reset,kty_digit}:
                     begin
                        shadow_digits = 1;
                        shadow state = ss digit1;
                        alt display = shadow display;
                        alt disp stale = tics + 2;
                        shadow_display = key-key_0;
                     end
                   {ss_pause,key_reset},
                   {ss digit1,key reset},
                   {ss digit2,key reset}:
                     begin
                        to reset;
                     end
                   {ss digit1,kty digit}:
                     begin
                        shadow digits = 2;
                        shadow state = ss digit2;
                        alt display = shadow display;
                        alt disp stale = tics + 2;
                        shadow_display = (shadow_display << 4) | key-key_0;</pre>
                     end
                   {ss_digit1,key_power}:
                     begin
                        shadow_state = ss_digit2;
                        shadow_digits = 0;
                        alt_display = shadow_display; // Power level.
                        alt_disp_stale = 'h7fffffff;
                        shadow_power = shadow_display;
                        shadow_display = 0;
                     end
```

{ss_digit1,key_start},{ss_digit2,key_start}:

hw04 sol.html

```
begin
                tosecs(shadow secs);
                start tics = tics;
                shadow tics = 0;
                mag on total = 0;
                mag_on_start = 0;
                shadow state = ss cook;
             end
           {ss_digit2,kty_digit}:
             if( shadow_digits == 4 )
               expected_beep_done = tics + 16;
             else
               begin
                  shadow_digits = shadow_digits + 1;
                  // If shadow display zero then power was pressed.
                  alt_disp_stale = tics + 2;
                  alt_display = mod_digits;
                  shadow_display = (shadow_display << 4) | key-key_0;</pre>
               end
           {ss_cook,key_reset}:
             begin
                shadow state = ss pause;
                shadow_display = mod_digits;
                pause_tics = tics;
             end
           {ss_pause,key_start}:
             begin
                verify cooking;
                mag on start = 0;
                shadow tics = 0;
                mag on total = 0;
                start_tics = tics;
                shadow_state = ss_cook;
             end
           default:
             begin
                if( expected beep done && expected beep done < tics )
                  begin
                      $display("Missed a beep. (overlap)");
                     error beep = error beep | 8;
                  end
                expected beep done = tics + 16;
             end
         endcase // casez( {shadow state,key type} )
         @( posedge clk ) @( negedge clk );
         repeat ( <u>$random() & 15 + 3 ) @( negedge clk );</u>
         key mod = key none;
         @( posedge clk ) @( negedge clk );
         @( posedge clk ) @( negedge clk );
      end // block: COMMAND_LOOP
endtask // command
```

```
// Reset oven module either using reset line or
// reset button.
11
```

end

```
task reset_oven;
   input hard;
   begin
      if( hard ) begin
         reset = 1;
         fork:F
           begin repeat ( 5 * 60 * 64 ) @( posedge clk ); disable F; end
            wait( !beep );
            wait( !mag on );
         join
         reset = 0;
      end else begin
         command("rrrrr");
         fork:T
            wait( !beep );
            wait( !mag on );
            begin repeat ( 5 * 60 * 64 ) @( posedge clk ); disable T; end
         join
         command("rrrrr");
      end // else: !if( 0 && hard )
      if( beep || mag_on )
        begin
           $display("Could not reset oven.");
           if( beep ) error beep = error beep | 'h20;
           if( mag_on ) error_mag = error_mag | 8;
        end
   end
endtask // reset_oven
// Actions to be done at the end of a test.
11
task endtest;
   input [159:0] name;
   integer error count;
   begin
      if( expected beep done )
        begin
           if( expected beep done >= tics )
             $display("Testbench not waiting long enough for beep.");
           $display("Missed a beep.");
           error beep = error beep | 'h10;
           expected_beep_done = 0;
        end
      if( mod digits!==0 )
        begin
           $display("Display should be zero.");
           error display = error display + 'h20;
        end
      verify cooking;
      watch display = 0;
      error_count = ( error_display ? 1 : 0 )
      + ( error beep ? 1 : 0 ) + ( error mag ? 1 : 0 );
      error_total = error_total + error_count;
      error_beep_total = error_beep_total | error_beep;
      error mag total = error mag total | error mag;
      error_display_total = error_display_total | error_display;
      sdisplay("OUTCOME: %s on test %s. (dsp,beep,mag) (%2h,%2h,%2h)",
```

```
\leftarrow \rightarrow Spring 2001
                  \leftarrow \rightarrow Homework 4
                                                Homework Sol Code
                       error count ? "FAIL" : "PASS",
                       name,
                       error display, error beep, error mag);
              reset oven(0);
             error display = 0;
             error beep = 0;
             error_mag = 0;
             mag_on_total = 0;
              shadow_tics = 0;
          end
       endtask // endtest
       task delay;
          input [63:0] secs;
          #( secs * 1000000 );
       endtask // delay
       initial begin
          monitor_display = 1;
monitor_keys = 1;
          monitor_beep = 1;
          monitor_mag = 1;
          patient = 1;
          expected_beep_done = 0;
          expecting_done_beep = 0;
          error_display = 0;
          error_display_total = 0;
          error_beep = \overline{0};
          error beep total = 0;
          error mag = 0;
          error mag total = 0;
          error total = 0;
          mag on total = 0;
          #1:
          to reset;
          reset oven(1);
          error display = 0;
          error display total = 0;
          error beep = 0;
          error_beep_total = 0;
          error_mag = 0;
          error_mag_total = 0;
          error total = 0;
          mag_on_total = 0;
          command("50prr");
          delay(54);
          endtest("Power Too High");
          command("32s"); delay(36);
          endtest("Basic");
          if( patient ) begin:PATIENT
              integer old mon, old mag;
             old_mon = monitor_display;
             old_mag = monitor_mag;
             monitor_display = 0;
              sdisplay("Starting test Long, be patient or modify testbench.");
```

```
command("30s"); delay(14);
command("1"); delay(2); command("p");
delay(20);
endtest("Basic Disturbed");
command("5p30s");
delay(40);
endtest("Half Power");
command("9p3p0s");
delay(40);
endtest("Power Twice");
command("3ppp19s");
delay(40);
endtest("Power Thrice");
command("20s");
delay(10);
command("r");
delay(5);
command("s");
delay(16);
endtest("Reset Start");
command("20s");
delay(10);
command("r");
delay(5);
command("r");
delay(16);
endtest("Reset Reset");
command("s");
delay(5);
endtest("Null Start");
command("ps");
delay(5);
endtest("Null Power Start");
command("7p30s"); delay(10);
command("1"); delay(2); command("s"); delay(3);
command("12344321");
delay(40);
endtest("Power Disturbed");
command("12r5s"); delay(135);
endtest("Twelve no 5");
```

```
command("12345rr"); delay(5);
endtest("Display Overflow");
```

```
if( show_key ) begin
```

```
$display("\n ** Error Codes **
Display (Codes in hexadecimal. Error codes or'ed together.)
1 Digit out of range. (Check digit.)
2 Display digit change more than 96 tics off.
```

```
\leftarrow \rightarrow Spring 2001
                \leftarrow \rightarrow Homework 4
                                               Homework Sol Code
        4 Wrong count. (cooking)
        8 Wrong count. (paused)
       10 Wrong count displayed. (Not cooking nor paused.)
       20 Display should be zero.
      Beep:
        1 Should not be beeping.
        2 Beep duration wrong.
        4 End of cooking beep missing.
        8 Missed a beep. (overlap)
       10 Missed a beep. (endtest)
       20 Wouldn't stop beeping!
      Mag
        1 Mag on when cooking off.
        2 Mag cycle error.
        4 Wrong power level.
        8 Would not turn off.
       10 Should be off (when cooking verified).
    ");
          $display("\n ** Testbench Monitoring ** ");
                         Display %s", monitor_display ? "on" : "off");
          <u>$display("</u>
          <u>$display(</u>"
                         Keys %s", monitor_keys ? "on" : "off");
                         Beep %s", monitor_beep ? "on" : "off");
Mag %s", monitor_mag ? "on" : "off");
          <u>$display(</u>"
          <u>$display(</u>"
          <u>$display("</u>
                         To turn monitoring on and off edit monitor FOO variables.");
          <u>$display("</u>
                         at last \"initial begin\" in testbench.\n\n");
          end
          $display("%s, mag tests (code: %h).",
error_mag_total ? "FAIL" : "PASS", error_mag_total);
          $display("%s, display tests (code: %h)."
                    error display total ? "FAIL" : "PASS", error display total);
          sdisplay("All tests completed, %d total errors.",error total);
          <u>$stop;</u>
       end // initial begin
```

endmodule // test_oven

// exemplar translate_on

/// Solution to LSU EE 4702-1 Spring 2001 Homework 5

// Assignment: <u>http://www.ee.lsu.edu/v/2001/hw05.pdf</u>

```
// The log 2 of the number of numbers stored by the bsearch module.
// Keep this small to limit synthesis time.
define SIZELG 4
`define SIZE (1<<`SIZELG)</pre>
                              // The number of numbers stored by bsearch.
`define SIZERANGE `SIZELG-1:0
`define ELEMBITS 8
                               // The number of bits in each number stored.
`define ELEMRANGE `ELEMBITS-1:0
`define MAXELEM (1<<`ELEMBITS)</pre>
11
// Original bsearch module.
11
// Not part of the solution, here for comparison to the other modules.
// This module is synthesizable (despite misleading macro names).
// synthesized hardware does the entire lookup in one cycle, which
// requires alot of hardware.
// Number of gates :
                                      5365
// clk
                        : 50.7 MHz
// Critical path: num 2 -> result[1], 19.18 ns
`define xNOT SYN
`ifdef NOT SYN
module bsearch(result,din,op,reset,clk);
   input din, op, reset, clk;
   output result;
  wire [7:0] din;
   wire [2:0] op;
   reg [2:0] result;
  `include "bsearch names.v"
   reg [7:0] dtable [0:`SIZE-1];
   reg [`SIZELG:0] num;
   reg [`SIZERANGE] current, try, delta;
   reg [`ELEMRANGE] trydata;
                   match;
   reg
   // Bug workaround. Needed to avoid a synthesis bug.
   wire [`ELEMRANGE] bug_workaround = dtable[1];
   always @( posedge clk )
    if( reset ) begin
        num = 0;
        result = re_r_idle;
     end else begin
        case( op )
```

input din, op, reset, clk;

```
op nop:;
         op reset:
           begin
              num = 0;
              result = re r idle;
           end
         op_insert:
           if( num == `SIZE ) begin
              result = re_i_full;
           end else if( num > 0 && dtable[num-1] >= din ) begin
              result = re_i_misordered;
           end else begin
              dtable[num] = din;
              num = num + 1;
              result = re_i_inserted;
           end
         op_find:
           begin
              match = 0;
              current = 0;
              delta = 1 << ( `SIZELG - 1 );</pre>
              begin:BLOOP forever begin
                 try = current | delta;
                 if( try < num ) begin</pre>
                    trydata = dtable[try];
                    match = trydata == din;
                    if( match ) disable BLOOP;
                    if( trydata < din ) current = try;</pre>
                 end
                 if( !delta ) disable BLOOP;
                 delta = delta >> 1;
              end end
              result = match ? re_f_present : re_f_absent;
           end
       endcase
    end
endmodule
`endif
11
// Problem 1: Form 2 bsearch Module
11
// Synthesizable Form 2.
11
11
// Clock Frequency (MHz):
                                      113.5 MHz
// Area (number of gates):
                                      4275
// Worst-case time to find a number: 6 / 113.5 MHz = 52.9 ns
11
`define xFORM2
`ifdef FORM2
module bsearch(result,din,op,reset,clk);
```

```
output result;
 wire [7:0] din;
 wire [2:0] op;
 reg [2:0] result;
`include "bsearch names.v"
             looping;
 reg
  reg [7:0] dtable [0:`SIZE-1];
  reg [`SIZELG:0] num;
 reg [`SIZERANGE] current, try, delta;
 reg [`ELEMRANGE] trydata;
                   match;
 reg
 wire [`ELEMRANGE] bug_workaround = dtable[12];
 always @( posedge clk )
   if( reset ) begin
       looping = 0;
       num
              = 0;
       result = re_r_idle;
    end else if( looping ) begin
       try = current + delta;
       if( try < num ) begin</pre>
          trydata = dtable[try];
          match = trydata == din;
          if (match ) looping = 0;
          if( trydata < din ) current = try;</pre>
       end
       if( !delta ) looping = 0;
       delta = delta >> 1;
       if( !looping ) result = match ? re_f_present : re_f_absent;
   end else begin
       case( op )
         op nop:;
         op reset:
           begin
              num
                     = 0;
              result = re r idle;
           end
         op_insert:
           if( num == `SIZE ) begin
              result = re_i_full;
           end else if( num > 0 && dtable[num-1] >= din ) begin
              result = re_i_misordered;
           end else begin
              dtable[num] = din;
              num = num + 1;
              result = re_i_inserted;
           end
         op_find:
           begin
              match = 0;
              current = 0;
```

```
\leftarrow \rightarrow Spring 2001 \leftarrow \rightarrow Homework 5
```

```
delta
                     = 1 << ( `SIZELG - 1 );
              result = re busy;
              looping = 1;
           end
       endcase
    end
endmodule
`endif
11
// Problem 2: Form 3 bsearch Module
11
// Synthesizable Form 3.
// Module does one dtable lookup per cycle.
11
// Clock Frequency (MHz):
                                        109.1 MHz
// Area (number of gates):
                                       4155
// Worst-case time to find a number: 5 / 109.1 MHz = 45.8 ns
11
// Critical path: reg_delta(1)/XQ to result[1], 8.47 ns
`define xFORM3
`ifdef FORM3
module bsearch(result,din,op,reset,clk);
   input din, op, reset, clk;
   output result;
  wire [7:0] din;
  wire [2:0] op;
   reg [2:0] result;
 `include "<u>bsearch_names.v</u>"
   reg [7:0] dtable [0:`SIZE-1];
   reg [`SIZELG:0] num;
   reg [`SIZERANGE] current, try, delta;
   reg [`ELEMRANGE] trydata;
   reg
                   match;
   always @( posedge clk )
    if( reset ) begin
       num = 0;
       result = re r idle;
    end else begin
       case( op )
         op_nop:;
         op reset:
           begin
              num = 0;
              result = re_r_idle;
           end
         op_insert:
           if( num == `SIZE ) begin
```

```
result = re i full;
           end else if( num > 0 && dtable[num-1] >= din ) begin
              result = re i misordered;
           end else begin
              dtable[num] = din;
              num = num + 1;
              result = re i inserted;
           end
         op_find:
           begin
              match
                     = 0;
              current = 0;
              delta = 1 << ( `SIZELG - 1 );</pre>
              result = re_busy;
              begin:BL00P forever begin
                 @( posedge clk );
                 try = current + delta;
                 if( try < num ) begin</pre>
                    trydata = dtable[try];
                    // This would split the delta -> result path between two
                    // cycles, but it would take nearly twice as long to find
                    // a result.
                    // @( posedge clk );
                    match = trydata == din;
                    if( match ) disable BLOOP;
                    if( trydata < din ) current = try;</pre>
                 end
                 if( !delta ) disable BLOOP;
                 delta = delta >> 1;
              end end
              result = match ? re_f_present : re_f_absent;
           end
       endcase
    end
endmodule
endif
// Problem 3: Form 3 bsearch Module, Speed Enhanced
// Synthesizable, Form 3.
// Module does two dtable lookups per cycle.
// Several solutions within module, area, time, and performance in comments
// next to code.
// Clock Frequency (MHz):
// Area (number of gates):
// Worst-case time to find a number:
```

`define FORM3 FAST `ifdef FORM3 FAST module bsearch(result,din,op,reset,clk);

11

11

11

11

```
input din, op, reset, clk;
  output result;
  wire [7:0] din;
  wire [2:0] op;
  reg [2:0] result;
 `include "<u>bsearch names.v</u>"
  reg [7:0] dtable [0:`SIZE-1];
  reg [`SIZELG:0] num;
  reg [`SIZERANGE] current, try, delta;
  reg [`SIZERANGE] try0, try1, delta2;
  reg [`ELEMRANGE] trydata, trydata0, trydata1;
                   match, match0, match1, m;
  reg
  always @( posedge clk )
    if( reset ) begin
        num = 0;
        result = re_r_idle;
    end else begin
       case( op )
         op_nop:;
         op_reset:
            begin
               num = 0;
               result = re_r_idle;
            end
         op insert:
            if( num == `SIZE ) begin
               result = re_i_full;
            end else if( num > 0 && dtable[num-1] >= din ) begin
               result = re_i_misordered;
            end else begin
               dtable[num] = din;
               num = num + 1;
               result = re i inserted;
            end
         op find:
            begin
               current = 0;
               delta = 1 << ( `SIZELG - 1 );</pre>
               result = re busy;
`define ALWAYS
 ifdef ALWAYS
               // Two iterations per clock cycle, dtable lookups done simultaneously.
               // Code below clk
                                                     : 3 / 97.8 MHz = 30.7 ns
                                                           7513
                // Number of gates :
               delta2 = delta >> 1;
               begin:BL00P forever begin
                  @( posedge clk );
                  try = current + delta;
                  try0 = current + delta2;
                  try1 = try + delta2;
                  trydata = dtable[try];
                  trydata0 = dtable[try0];
```

```
Homework Sol Code
\leftarrow \rightarrow Spring 2001
                   \leftarrow \rightarrow Homework 5
                        trydata1 = dtable[try1];
                        match = trydata == din;
                        match0 = trydata0 == din;
                        match1 = trydata1 == din;
                        if( try < num ) begin</pre>
                           if( match ) begin m = 1; disable BLOOP; end
                           if( trydata > din )
                             begin
                                 if( match0 ) begin m = 1; disable BL00P; end
                                 if( trydata0 < din ) current = try0;</pre>
                              end
                           else if( try1 < num )</pre>
                             begin
                                 if( match1 ) begin m = 1; disable BLOOP; end
                                 if( trydata1 < din ) current = try1;</pre>
                                 else current = try;
                             end
                                 else
                                   current = try;
                        end else if( try0 < num ) begin</pre>
                           begin
                               if( match0 ) begin m = 1; disable BL00P; end
                              if( trydata0 < din ) current = try0;</pre>
                           end
                        end
                        if( !delta ) begin m = 0; disable BLOOP; end
                        delta = delta >> 2;
                        delta2 = delta2 >> 2;
                    end end
    `endif
    `ifdef NEVER
                    // Completely unrolled, all five iterations in one cycle.
                    // Code below clk
                                                              : 1/ 55.5 MHz = 18.0 ns
                    // Number of gates :
                                                                  5482
                    match = 0;
repeat ( `SIZELG + 1 ) begin
                        try = current + delta;
                        if( !match && try < num ) begin</pre>
                           trydata = dtable[try];
                           match = trydata == din;
                           if( trydata < din ) current = try;</pre>
                        end
                        delta = delta >> 1;
                    end
                    m = match;
    `endif
    `ifdef NEVER
                    // Original Code
                     // Code below: clk
                                                                : 5/109.1 \text{ MHz} = 46.2 \text{ ns}
                     // Number of gates :
                                                                   4155
                    match = 0;
                    begin:BL00P forever begin
                        @( posedge clk );
                        try = current + delta;
                        if( try < num ) begin</pre>
                           trydata = dtable[try];
                           match = trydata == din;
                           if( match ) disable BLOOP;
                           if( trydata < din ) current = try;</pre>
                        end
                        if( !delta ) disable BLOOP;
                        delta = delta >> 1;
                    end end
                    m = match;
```

```
\leftarrow \rightarrow Spring 2001 \leftarrow \rightarrow Homework 5
```

`endif

`*ifdef* NEVER

```
// Two iterations per cycle.
// Iterations are sequential. (Second dtable lookup after first.)
// clk
                             : 3 / 63.7 MHz = 47.1 ns
// Number of gates :
                                           6465
match = 0;
begin:BL00P forever begin
   @( posedge clk );
   repeat( 2 ) begin
      try = current + delta;
      if( !match && try < num ) begin</pre>
         trydata = dtable[try];
         match = trydata == din;
         if( trydata < din ) current = try;</pre>
      end
      delta2 = delta; delta = delta >> 1;
   end
   if( match ) disable BLOOP;
   if( !delta2 ) disable BLOOP;
end end
m = match;
```

Homework Sol Code

```
`endif
```

result = m ? re_f_present : re_f_absent;

end

endcase

end

endmodule `*endif*

// Testbench module is named testbsearch.

// The testbench can be copied into this file or another one and // modified. The testbench might be updated before the homework // is due though.

`include "/home/classes/ee4702/files/v/hw05tb.v"

26 Spring 2000 Solutions

// Solution to LSU EE 4701 Spring 2000 HW 5.

`ifdef ALU module alu(res,err,a,b,op); input a, b, op; output res, err; parameter op_add = 0, // Addition. op_sub = 1, // Subtraction op_and = 2; // Bitwise and. wire [7:0] a, b; wire [2:0] op; reg [7:0] res; reg err; // exemplar full_case always @(a or b or op) case(op) op_add: {err,res} = a + b; op_sub: {err,res} = a - b; op and: begin err = 0; res = a & b; end endcase // case(op) endmodule // alu `endif module latch_thing(w,x,y,z,a,b,c,d,r,clk); input a, b, c, d, r, clk; output w, x, y, z; reg w, x, y, z; wire a, b, c, d, r, clk; always @(negedge clk or posedge r) if(r) w = 0; else w = d; always @(posedge clk or posedge r) if(r) y = 0; else y = a; always @(clk or c or r or d or b) if(r) z = 0; else if(clk & d == b) z = c; wire deqb = d == a && clk; always @(posedge clk or posedge r or posedge deqb) if(r)x = 0;else if(deqb) x = 1;else if(a) x = b; endmodule // latch_thing

```
11
// LSU EE 4702-1 Spring 2000 Homework 6 Solution
11
module width_change(out,full,complete,empty,outclk,in,inclk,reset);
   input outclk, in, inclk, reset;
   output out, full, complete, empty;
   parameter storage = 32;
   wire [7:0] out;
   wire [3:0] in;
              inclk, outclk, full, empty, complete;
   wire
   reg [storage-1:0] sto;
   reg [1:0] head_word;
   reg [2:0] tail_nibble;
              empty in, empty out, full in, full out;
   reg
   assign out
                   = empty ? 0 : sto >> { head word, 3'b0 };
                   = empty in ^ empty out;
   assign empty
                   = full_in ^ full_out;
   assign full
   assign complete = !empty &&
          ( full || head word != tail nibble[2:1] );
   always @( posedge inclk or posedge reset )
     if( reset ) begin
        sto[7:0] = 0; tail nibble = 0; empty in = 1; full in = 0;
     end else if (!full ) begin
        if( empty ) begin empty in = !empty in; tail nibble = 0; end
        case ( tail nibble )
          0: sto[7:0] = {4'b0,in};
          1: sto[7:4] = in;
          2: sto[15:8] = {4'b0,in};
          3: sto[15:12] = in;
          4: sto[23:16] = {4'b0,in};
          5: sto[23:20] = in;
          6: sto[31:24] = {4'b0,in};
          7: sto[31:28] = in;
        endcase
        tail_nibble = tail_nibble + 1;
        if( tail nibble[0]==0 && tail nibble>>1 == head word )
          full in = !full in;
     end
   always @( posedge outclk or posedge reset )
     if( reset ) begin
        head word = 0; empty out = 0; full out = 0;
     end else
       if( !empty ) begin
          if( full ) begin
             full_out = !full_out;
             head_word = head_word + 1;
          end else if( head_word == ( 3 & (tail_nibble-1)>>1 ) ) begin
             empty_out = !empty_out;
             head word = 0;
          end else begin
             head word = head word + 1;
```

```
end
end
```

endmodule // width_change

```
// exemplar translate_off
```

```
module wc_test();
```

```
// If non-zero, stop simulation when an error is encountered.
// If zero, when an error is encountered simulation will proceed
// and a count of errors will be displayed.
parameter stop_on_err = 1;
wire [7:0] out;
wire
           full, empty, comp;
           outclk, inclk, reset;
reg
reg [3:0] indata;
reg [31:0] shadow;
           shadow full, shadow comp, shadow empty;
reg
reg [7:0]
          shadow head;
           shadow occ;
integer
           check;
reg
integer
           phasecount;
           remove_delay_limit_short, remove_delay_limit_long;
time
           remove_delay_limit;
time
time
           fill_delay_limit;
time
           next_empty;
           allow simultaneous clocks;
integer
           allow overlapping clocks;
integer
           error_out_t, error_out;
integer
           error_empty_t, error_empty;
integer
           error_comp_t, error_comp;
integer
integer
           error_full_t, error_full;
integer
           error test, error test t;
width_change wc(out,full,comp,empty,outclk,indata,inclk,reset);
function [31:0] randi;
   input [31:0] limit;
   randi = ( <u>$random</u> >> 1 ) % limit;
endfunction // randi
initial begin
   indata = 0; outclk = 0; inclk = 0; reset = 0;
   shadow empty = 1; shadow comp = 0; shadow full = 0; shadow head = 0;
   check = 0; shadow = 0; shadow occ = 0; phasecount = 0;
   fill delay limit = 20;
   remove delay limit short = 0.5 * fill delay limit * 2;
   remove delay limit long = 2 * fill delay limit * 2;
   // Start filling.
   remove_delay_limit = remove_delay_limit_long;
   allow_overlapping_clocks = 0;
   allow_simultaneous_clocks = 0;
   error_out = 0; error_out_t = 0;
   error empty = 0; error empty t = 0;
   error comp = 0; error comp t = 0;
   error full = 0; error full t = 0;
```

```
error test = 0; error test t = 0;
reset = 1; \#10 reset = 0; \#10;
fork:TESTL00P
   forever begin: FILL
      integer clk_fall_delay;
      integer clk rise delay;
      clk fall delay = allow_overlapping_clocks ?
                        randi(fill_delay_limit)+1 : 1;
      clk_rise_delay = randi(fill_delay_limit)+1;
      indata <= #(10*randi(clk_rise_delay)) <u>$random;</u>
      #(10*clk_rise_delay);
      // Special case: if FIFO is full or empty and data is
      // simultaneously clocked in and out there's no way to
      // tell if FIFO rejected the data begin clocked in.
      while( next_empty == <u>$time</u> &&
             ( !allow simultaneous clocks ||
               shadow_occ >= 20 || shadow_occ < 12 )) #10;</pre>
      inclk = 1;
      check <= #1 !check;</pre>
      shadow_empty = 0;
      if( !shadow_full ) begin
         shadow occ = shadow occ + 4;
         shadow = { indata, shadow[31:4] };
         if( shadow occ > 28 )
           begin
              shadow full = 1;
              if ( remove delay limit === remove delay limit long ) begin
                  remove_delay_limit = remove_delay_limit_short;
                  phasecount = phasecount + 1;
              end
           end
         if( shadow_occ > 7 ) shadow_comp = 1;
      end
      shadow head = shadow >> ( 32 - shadow occ );
      indata <= #(10*randi(clk_fall_delay)) <u>$random;</u>
      inclk = #(10*clk fall delay) 0;
   end
   forever begin: EMPTY
      integer clk_fall_delay;
      integer clk rise delay;
      clk fall delay = allow overlapping clocks ?
                        randi(remove delay limit)+1 : 1;
      clk_rise_delay = randi(remove_delay_limit)+1;
      next_empty = <u>$time</u> + 10 * clk_rise_delay;
      outclk = #(10*clk_rise_delay) 1;
      check <= #1 !check;</pre>
      shadow_full = 0;
      if( !shadow empty ) begin
         if( shadow occ <= 8 ) begin
```

shadow_occ = 0; shadow_empty = 1;

```
remove delay limit = remove delay limit long;
      end else begin
         shadow occ = shadow occ - 8;
      end
      shadow head = shadow >> ( 32 - shadow occ );
      if ( shadow occ < 8 ) shadow comp = 0;
   end
   outclk = #(10*clk fall delay) 0;
end // block: EMPTY
forever @( out or check ) #1
  if( out !== shadow_head ) begin
     if( stop_on_err ) begin
        $display("Wrong output.");
        #2 <u>$stop;</u>
     end
     error_out = error_out + 1;
  end
forever @( empty or check ) #1
  if( empty !== shadow_empty ) begin
     if ( stop on err ) begin
        $display("Wrong empty.");
        #2 <u>$stop;</u>
     end
     error_empty = error_empty + 1;
  end
forever @( comp or check ) #1
  if( comp !== shadow comp ) begin
     if ( stop on err ) begin
        $display("Wrong complete.");
        #2 <u>$stop;</u>
     end
     error comp = error comp + 1;
  end
forever @( full or check ) #1
  if( full !== shadow_full ) begin
     if( stop_on_err ) begin
        $display("Wrong full.");
        #2 <u>$stop;</u>
     end
     error full = error full + 1;
  end
forever @( phasecount ) begin:P
   reg [84:0] test_name;
   if( phasecount == 200 || phasecount == 400 || phasecount == 600 )
     begin
        error test = error out + error empty + error comp + error full;
        error test t = error test t + error test;
        error out t = error out t + error out;
        error_empty_t = error_empty_t + error_empty;
        error_comp_t = error_comp_t + error_comp;
        error_full_t = error_full_t + error_full;
        case( phasecount )
          200:test_name = "No Overlap";
          400:test name = "Not Simult";
          600:test_name = "Full Test";
        endcase // case( phasecount )
        $display("Test %s. Total Errors %d. Errors by type:",
```

```
\leftarrow \rightarrow Spring 2000 \leftarrow \rightarrow Homework 6
```

Homework Sol Code

```
test name, error test);
                $display("
                                  Output %d, empty %d, compl %d, full %d",
                        error out, error empty, error comp, error full);
                if( phasecount == 200 ) begin
                   allow overlapping clocks = 1;
                   if( error test === 0 )
                     $display("Passed all non-overlapping tests!!");
                end else if ( phasecount == 400 ) begin
                   allow_simultaneous_clocks = 1;
                   if( error_test === 0 )
                     sdisplay("Passed all overlapping-but-not-simultaneous tests!!!!");
                end else if ( phasecount == 600 ) begin
                   if( error_test === 0 )
                     sdisplay("Passed all simultaneous clock tests!!!!!!");
                   if( error_test_t === 0 )
                    else
                     $display("Failed %d tests. :-(",error_test_t);
                   disable TESTLOOP;
                end
                error out = 0; error empty = 0; error comp = 0; error full = 0;
                error test = 0;
             end // if ( phasecount == 200 || phasecount == 400 || phasecount == 600 )
        end
     join
  end // initial begin
endmodule // wc test
// exemplar translate on
```