Simple Cost and Performance Model

Motivation

When designing things need to estimate cost and performance.

When running synthesis need to know if results are good or bad.

Simple Models' Goals

Choose between design alternatives.
Plan A is better than Plan B based on the simple model.

Characterize a particular design approach.
Based on the simple model the cost of a module of size n is $\propto n^2 \log n$.

The simple models will be used throughout the semester.

Simple Model Non-Goals

The simple model . . .
. . . **is not suitable for** approximating post-synthesis cost and performance.

Practice Problems

Problems based on the material in these slides.

2019 Homework 3. (Analysis of a shift/add module and a recursive multiply module.)

2016 Final Exam Problem 2b and Problem 4 (greedy and fcfs fit).

2017 Final Exam Problem 3. (Two variations on a module.)

The Simple Cost Model

Simple Model Base Costs

2-input AND gate: $1\,\mathrm{u_c}$**. (One unit of cost.)**

2-input OR gate: $1\,\mathrm{u_c}$**.**

NOT gate: $0\,\mathrm{u_c}$**. (Zero cost.)**

Simple Model Derived Costs—Basic Gates


Based on equivalent circuit using gates above.

Cost of *n-input OR gate:* $(n-1)\,\mathrm{u_c}$.

Cost of *n-input AND gate:* $(n-1)\,\mathrm{u_c}$.

Cost of a *2-input XOR gate:* $3\,\mathrm{u_c}$.

XOR:

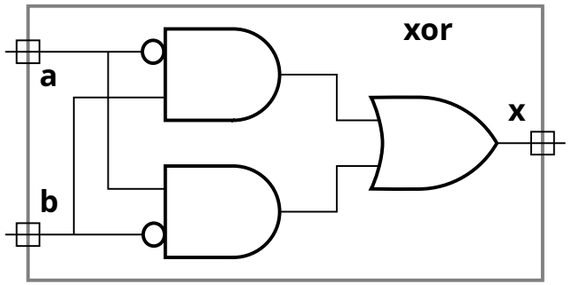


Simple Model Derived Costs—Flip Flops


Cost of an *edge-triggered flip-flop* is $7\,\mathrm{u_c}$.

Cost of an *edge-triggered enable flip-flop* is $10\,\mathrm{u_c}$.

Cost of a *w-bit edge-triggered register* is $7w\,\mathrm{u_c}$.

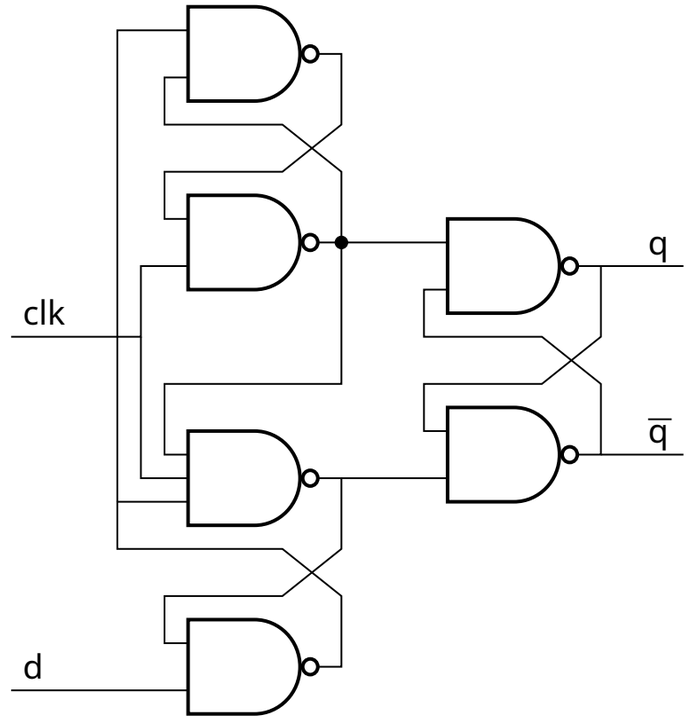Cost of a *w-bit edge-triggered register with enable* is $10w\,\mathrm{u_c}$.



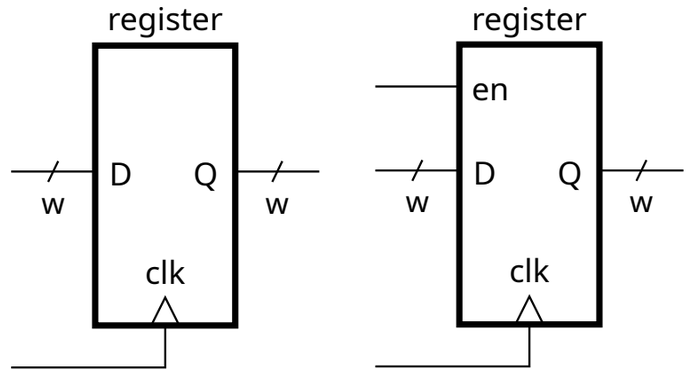

LSU EE 4755 Lecture Transparency. Formatted 14:45, 14 October 2026 from lsli-simple-model-TeXize.


smod-6

Examples


A 2-input AND gate: cost is $1\,\mathrm{u_c}$.

A 10-input OR gate: cost is $9\,\mathrm{u_c}$.

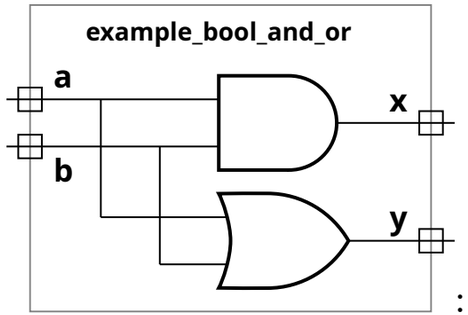A 1-input OR gate: cost is $0\,\mathrm{u_c}$. Yes, it's free!



: cost is $1 + 1 = 2\,\mathrm{u_c}$.

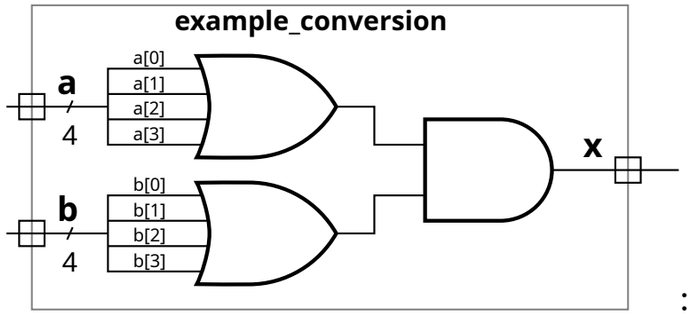

: cost is $3 + 3 + 1 = 7\,\mathrm{u_c}$.

The Simple Performance Model

The Simple Performance Model Base Delays

2-input AND gate: $1\,\mathrm{u_t}$ **(One time unit.)**

2-input OR gate: $1\,\mathrm{u_t}$**.**

NOT gate: $0\,\mathrm{u_t}$**.**

The Simple Performance Model Derived Delays

Based on equivalent circuit using gates above.

Delay of a *2-input XOR gate:* $2\,\mathrm{u_t}$.

Delay of *n-input OR gate:* $\lceil \lg n \rceil\,\mathrm{u_t}$.

Delay of *n-input AND gate:* $\lceil \lg n \rceil\,\mathrm{u_t}$.


Delay of an *edge-triggered flip-flop* is $6\,\mathrm{u_t}$.

Delay and Critical Path

Delay Measurement

Delay is measured between two points or sets of points,. . .
. . . which will be called the *launch point* and *capture point*.

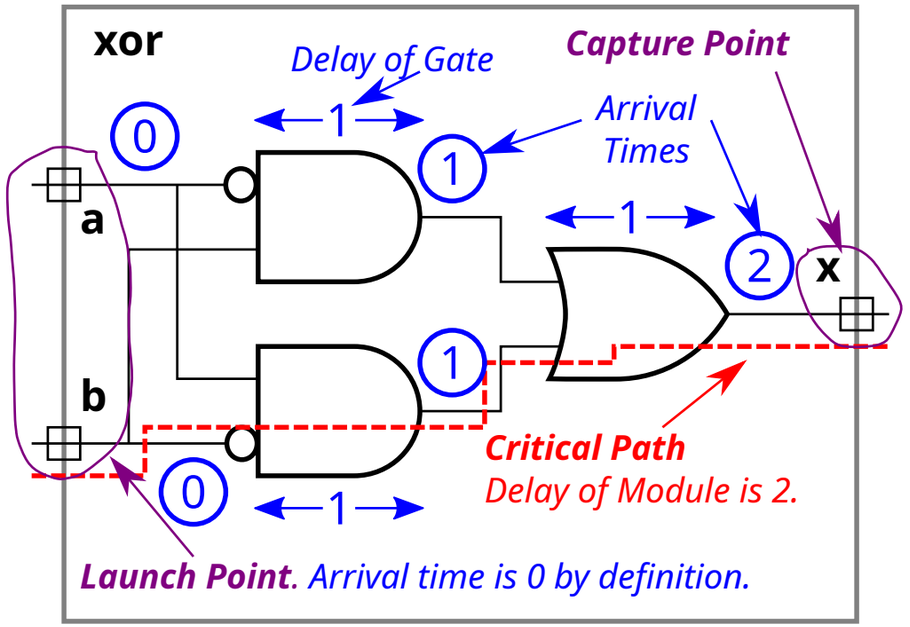Where those two points are depends on the context . . .
. . . for example, for an AND gate the launch point is at the inputs and the capture point is at the outputs.



Definitions

Launch Point:

The starting point defined for measuring delay. For a combinational logic module, the launch points are **often the module inputs**. For sequential logic (covered later) the launch points also include **all register outputs**.

Capture Point:


The end point when measuring delay. For a combinational logic module, the launch points are **often the module outputs**. For sequential logic (covered later) the capture points also include **all register inputs**.


Arrival Time of a Point:

The delay of the longest path from a launch point to the point.

Critical Path:

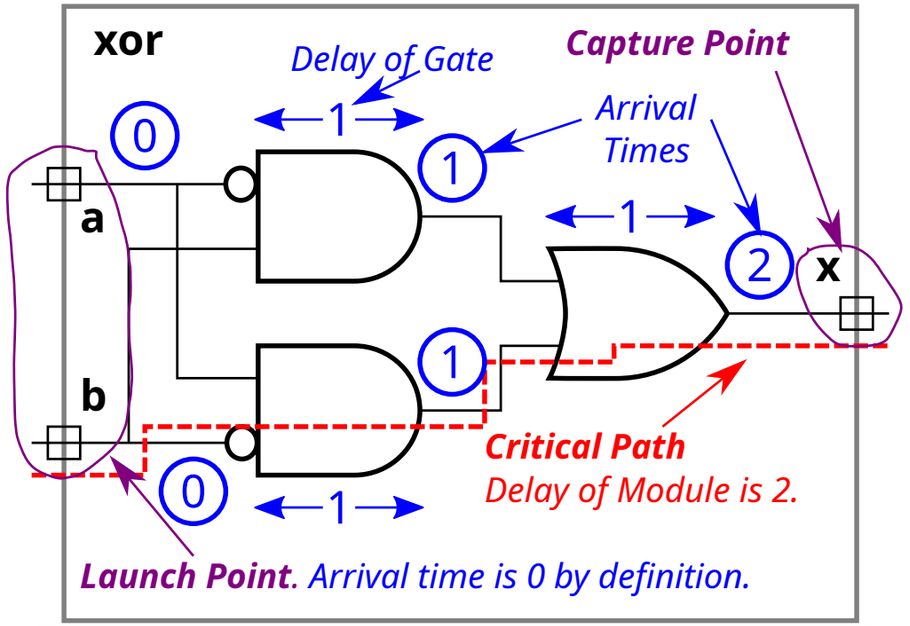A path starting from a launch point, ending at a capture point, and having the longest delay (perhaps tied with others).



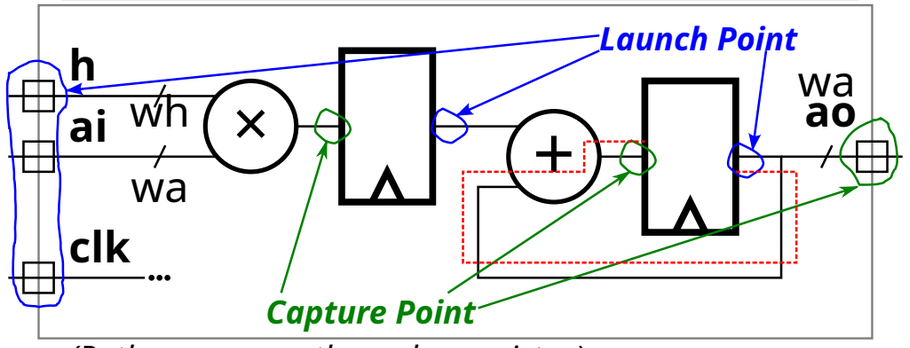


(Path never goes through a register.)

smod-10

Multiplexors

A 2-input, 1-bit mux:

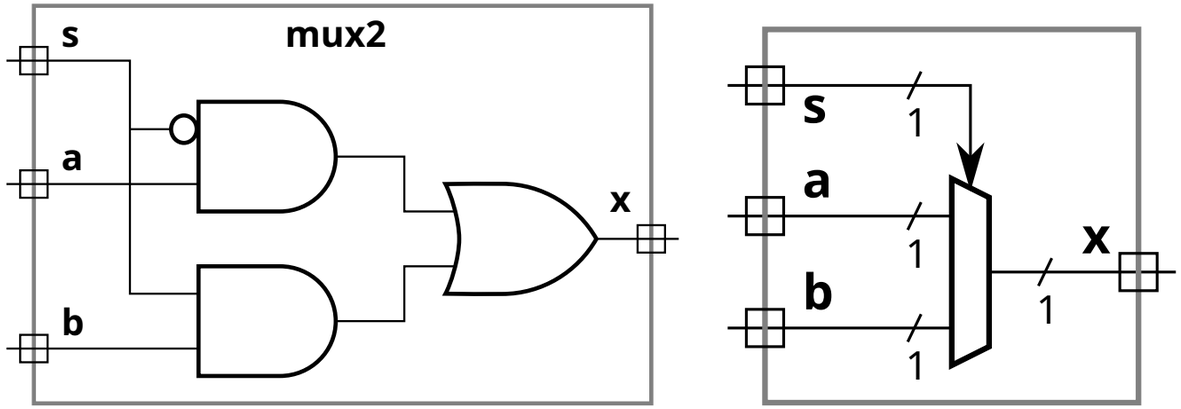

Cost, $3\,\mathrm{u_c}$. Delay, $2\,\mathrm{u_t}$.

A 2-input, w-bit mux:

This is equivalent to w copies of the mux above.

Cost, $3w\,\mathrm{u_c}$. **Delay,** $2\,\mathrm{u_t}$.

An n-input, w-bit mux, tree implementation:

Constructed from 2-input multiplexors.

Illustration is for $n = 8$.


The path from the selected input . . .
. . . is through $\lceil \lg n \rceil$ 2-input muxen . . .
. . . through 3 for illustrated size, $n = 8$.

The number of muxen connected to select bit i. . .
. . . is $n/2^{i+1}$ for $0 \geq i < \lceil \lg n \rceil$. . .
. . . for illustrated size 2 muxen connect to bit 1.

Cost Computation

Total number of 2-input muxen . . .
. . . $\sum_{i=0}^{\lg n-1} n/2^{i+1} = n - 1$ . . .
. . . for illustrated mux, seven 2-input muxen.

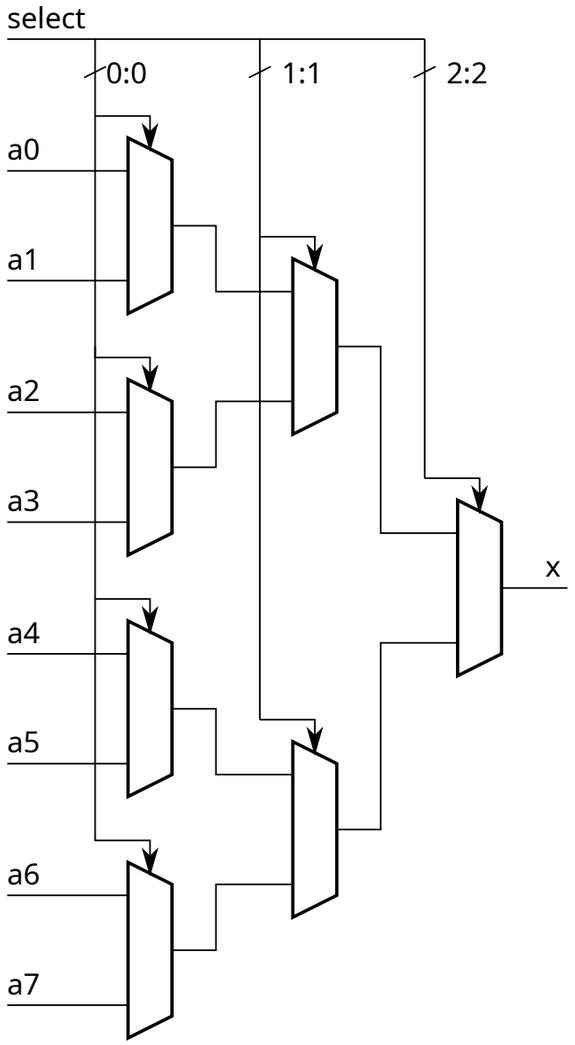Total cost: $3w(n-1)$. Total Delay: $2\lceil \lg n \rceil$.



LSU EE 4755 Lecture Transparency. Formatted 14:45, 14 October 2026 from lsli-simple-model-TeXize.
smod-12

Equality Comparison (`a == b`)

Output is 1 iff w-bit inputs are equal.

Assume w is a power of 2.

Cost Computation

XOR Gates: $3w$.

Reduction tree of AND gates: $\sum_{i=1}^{\lg w} w/2^i = w - 1$.


Total Cost: $4w - 1 \approx 4w$.

Delay Computation

XOR Gates: 2.

Reduction Tree: $\lg w$.

Total Delay: $2 + \lg w \approx \lg w$.

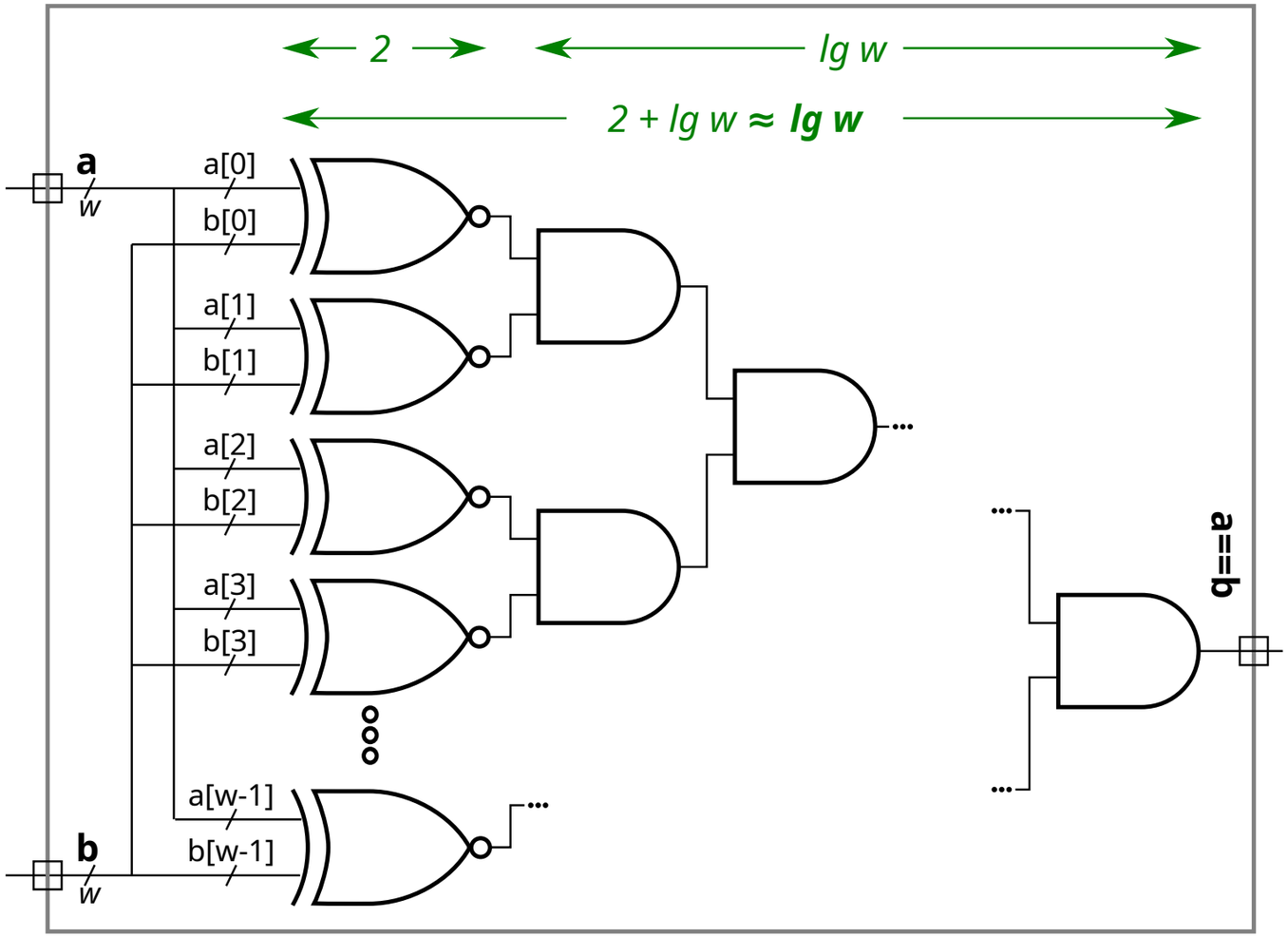

smod-13

Binary Full Adder Constructions

Prerequisite

If necessary, review material on binary half and full adders and ripple adders.

For example, Brown and Vranesic 3rd Edition Section 3.2.

You should either remember the circuits for BFAs and BHAs ...
... or be able to effortlessly derive them using a truth table.

Material in this Section

Binary Full Adder (BFA)

Ripple Adder

Magnitude (Greater Than, Less Than, etc.)

Cascaded Ripple Units


Carry Look Ahead Adder

Binary Full Adder Implementation

Fast BFA

Cost Computation

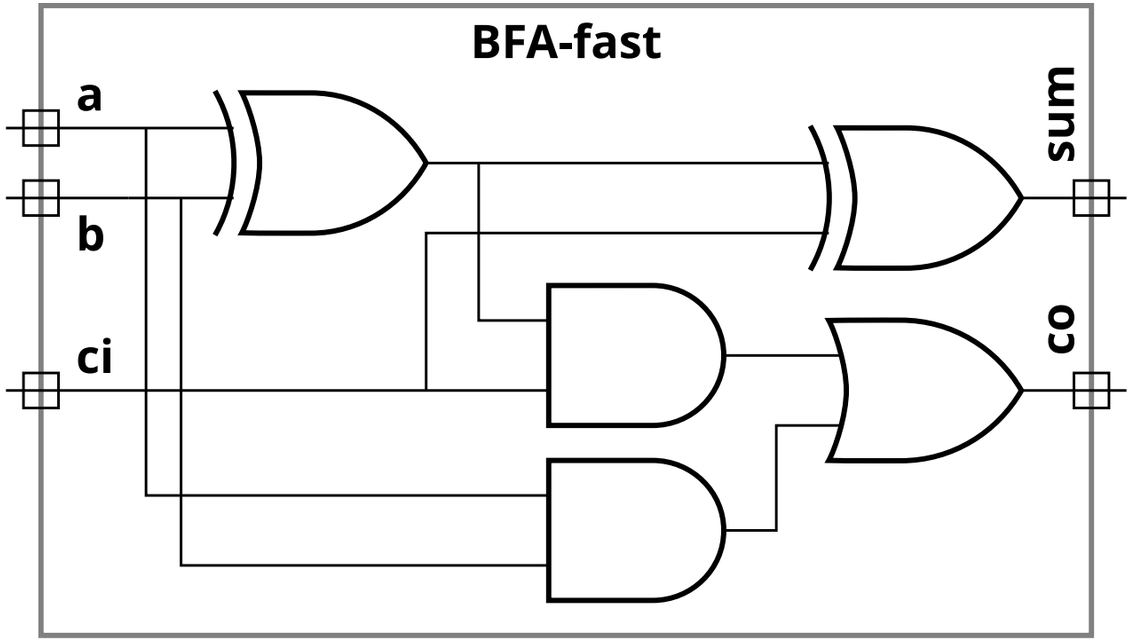Two XOR, 3 AND: $2 \times 3 + 3 = 9\,\mathrm{u_c}$



smod-16

Fast BFA

Delay: Any input to any output.

See Path I and...
... purple labels in diagram.


Delay: $4\,u_t$

Delay: `ci` to `co`.

This delay is useful when `a` and `b` arrive earlier than `ci`.


See Path II and green labels in diagram.

Delay: $2\,u_t$

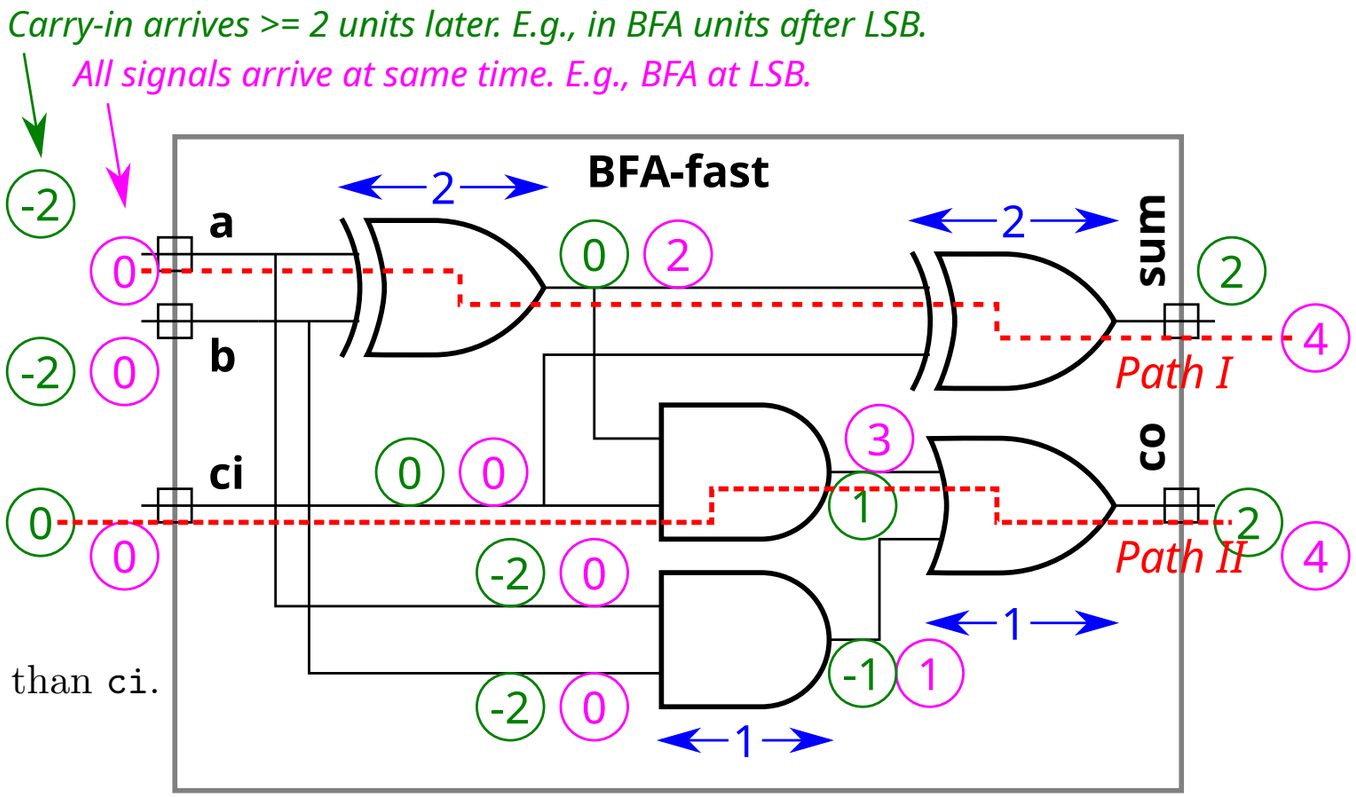

smod-17

w-Bit Ripple Adder

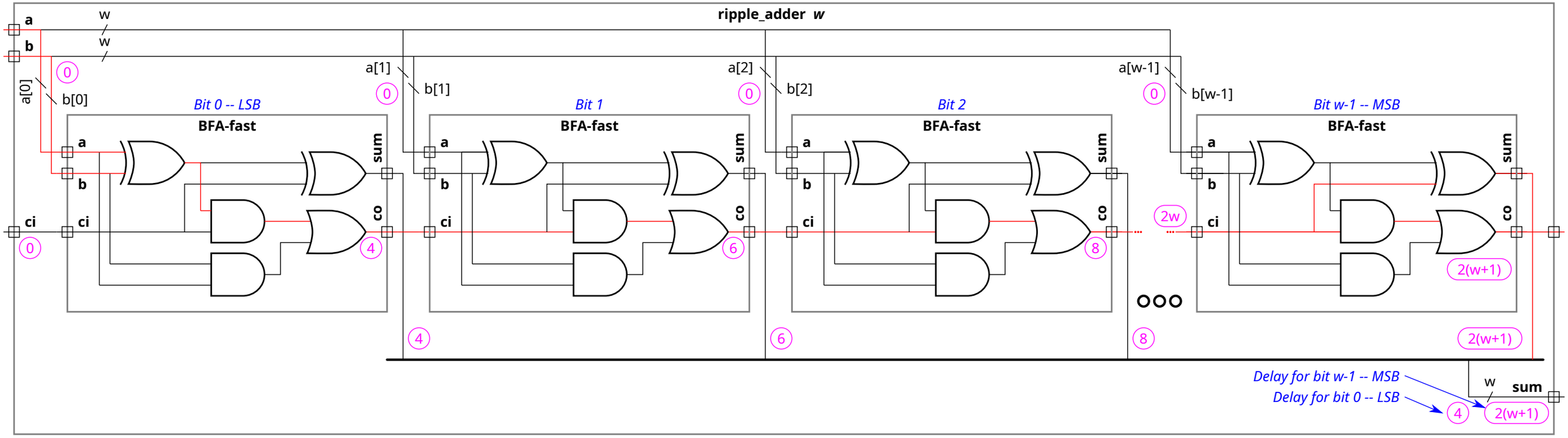

Cost Computation: Cost of w BFAs: $9w\,\mathrm{u_c}$


Delay Computation

See critical path (in red) in diagram.

Delay: $2(w+1) \approx 2w$.

smod-18

w-Bit Ripple Subtractor

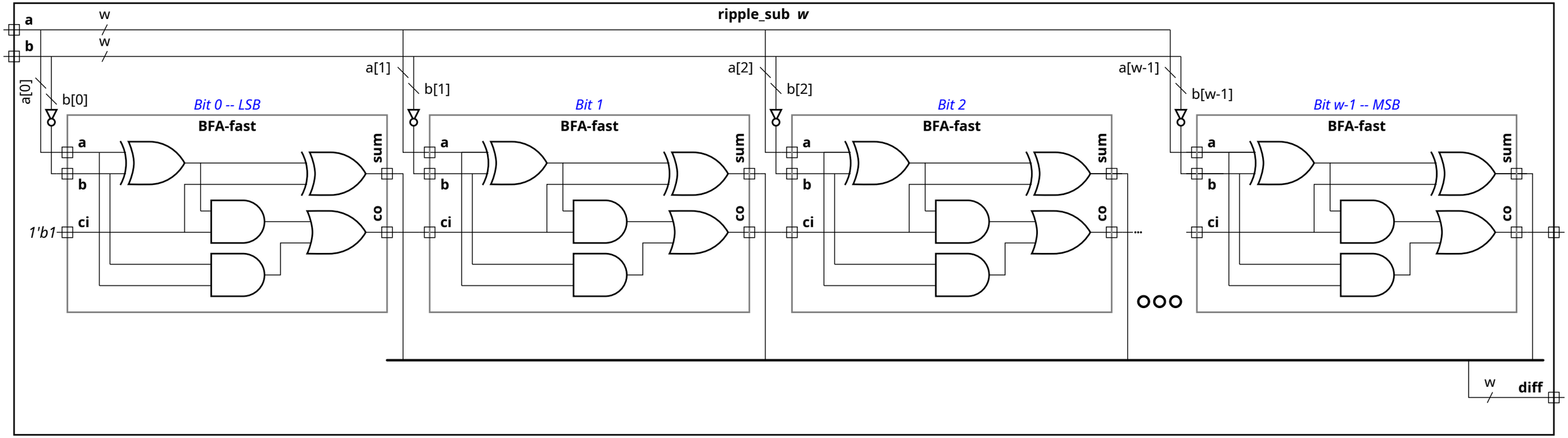

Cost and delay are slightly less due to constant carry in.

smod-19

Integer Magnitude Comparison

For comparisons like $a < b$.

Implementation:


Compute $a - b$ and check whether result negative.

If carry out of MSB is `0` then $a - b < 0$ and so $a < b$ is true.

Omit sum hardware in BFA, and replace remaining XOR with an OR.

See the illustration on the next page.

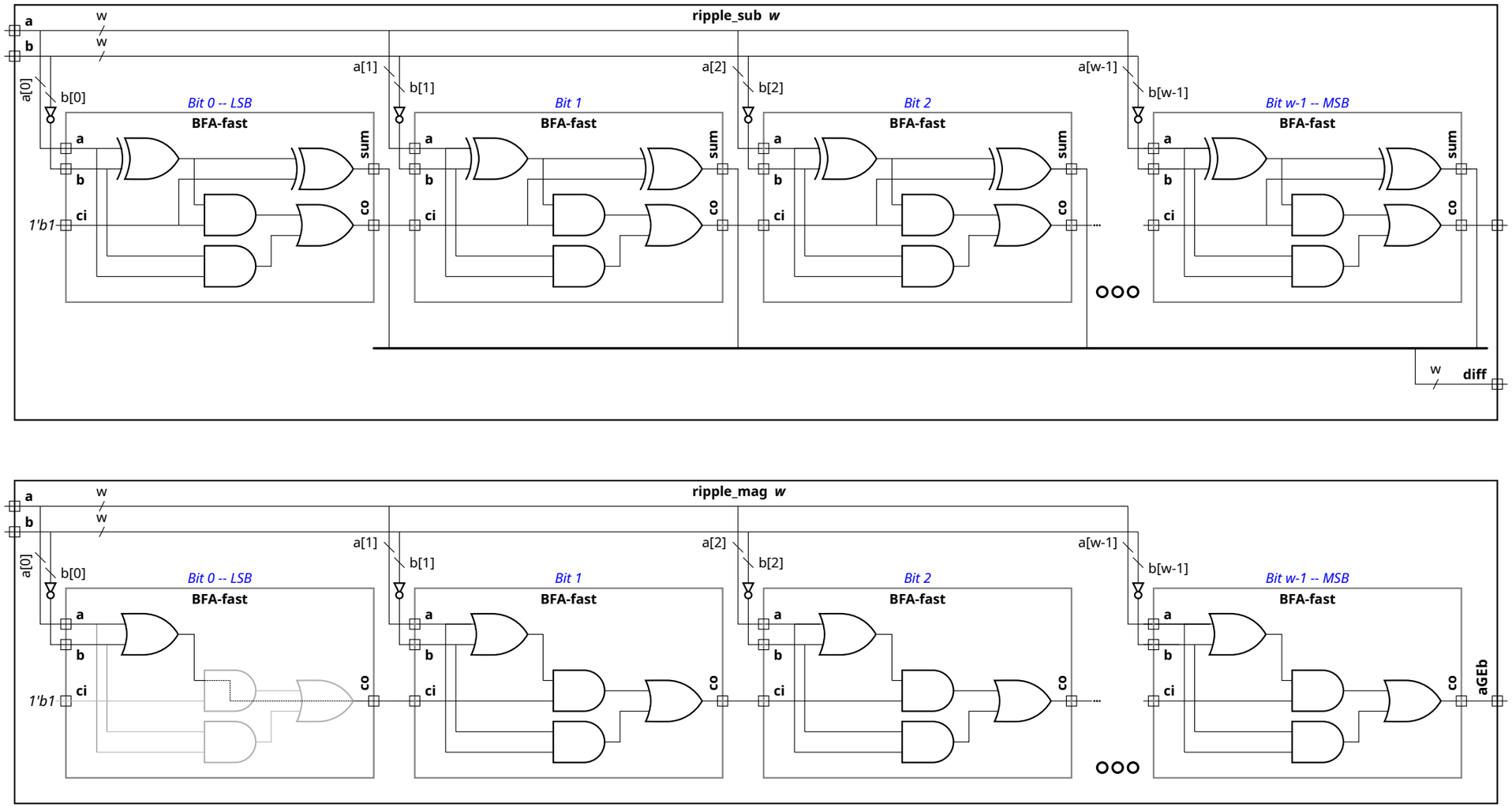Integer Magnitude Comparison Construction



smod-21

Cost and Delay of Integer Magnitude Comparison

Cost Computation

Each modified BFA now costs $4\,\mathrm{u_c}$.

Total cost: $4w\,\mathrm{u_c}$

Delay Computation


Delay is 3 for first bit, 2 for remaining bits.

Total delay: $[2w+1]\,\mathrm{u_t} \approx 2w\,\mathrm{u_t}$.

Cascaded Ripple Units

For computations using ripple units. . .
. . . such as $a + b + e$, and $(a + b) < e$, etc.

Next page shows two cascaded ripple units computing $a + b + e$ . . .
. . . and omitting the usual carry-out signals.

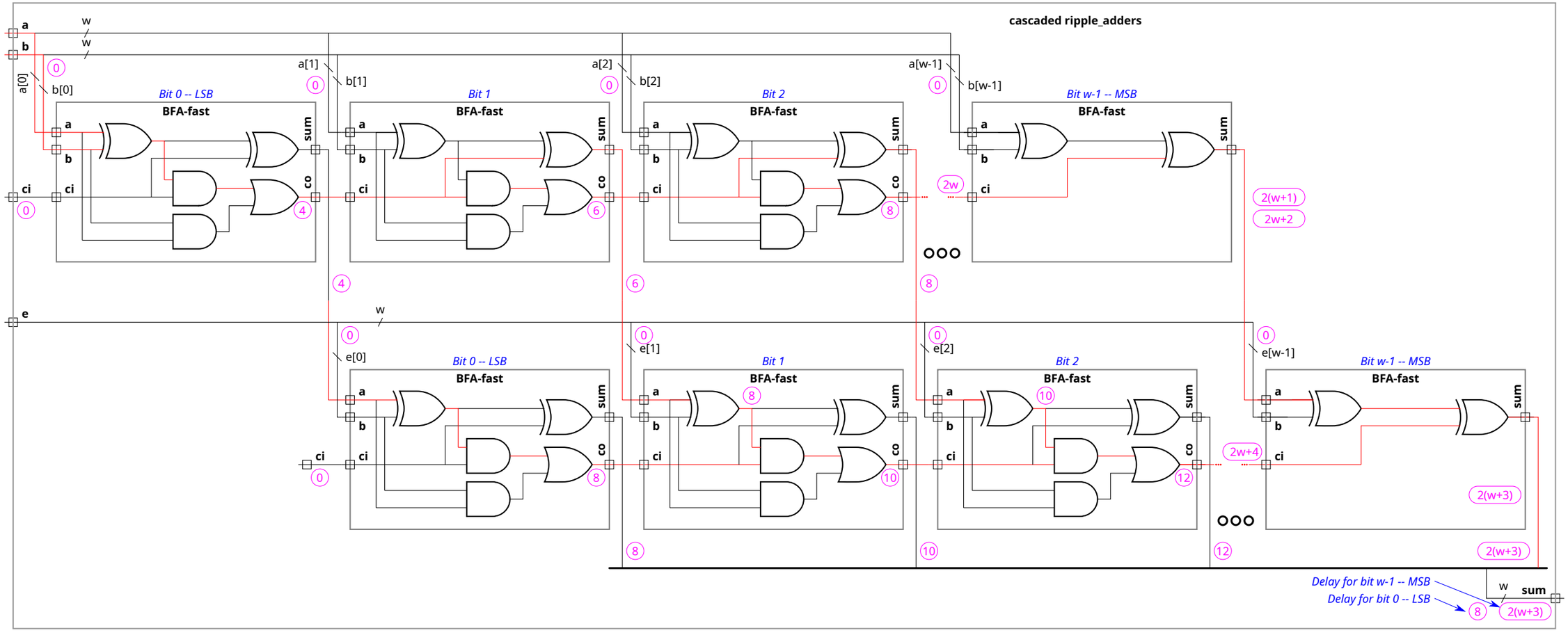
cascaded ripple_adders
a
b
w
w
a[0]
b[0]
a[1]
b[1]
a[2]
b[2]
a[w-1]
b[w-1]
Bit 0 -- LSB
Bit 1
Bit 2
Bit w-1 -- MSB
BFA-fast
a
b
ci
sum
co
2w
2(w+1)
2w+2
e
e[0]
e[1]
e[2]
e[w-1]
2w+4
2(w+3)
Delay for bit w-1 -- MSB
Delay for bit 0 -- LSB

smod-24

Cost Computation

Cost is sum of costs of each ripple unit.

For example, $a + b + c$ is two ripple adders, cost is $18w\,\mathrm{u_c}$ ...
... $(a + b) < e$ is a ripple adder plus a magnitude comparison: $[9w + 4w]\,\mathrm{u_c} = 13w\,\mathrm{u_c}$.

Delay Computation:

Consider $(a + b) + e$.

Naïve analysis: wait for $a + b$ to finish, then start $+e$.

But, LSB of $a + b$ available after only $4\,\mathrm{u_t}$ ...
... bit i is available after $(4 + 2i)\,\mathrm{u_t}$ ...
... so the $+e$ computation can start after $4\,\mathrm{u_t}$.

Delay for two ripple units is $[4 + 2(w + 1)]\,\mathrm{u_t}$.

Delay for bit i at output of n ripple units is $[4(n - 1) + 2(i + 2)]\,\mathrm{u_t}$.

Delay for n ripple units is $[4(n - 1) + 2(w + 1)]\,\mathrm{u_t}$.

Carry Look Ahead Adder (CLA)

Key Idea

Divide adder into b-bit blocks.

Compute the carry-in for block i in terms of ...
... the carry-in for block $i-1$, c_{i-1} ,...
... and *generate*, g_{i-1}, and *propagate*, p_{i-1}, values computed by block $i-1$.

It is possible to compute g and p for a b-bit block in $O(\lg b)\,\mathrm{u_t}$.

CLA Recursive Construction

```
module cla_node #( int w = 16 )
   ( output uwire [w-1:0] sum,     output uwire p, g,
     input uwire cin,              input uwire [w-1:0] a, b );

   if ( w == 1 ) begin


      assign g = a && b;
      assign p = a || b;
      assign sum = ( !g && p ) ^ cin;  // Same as a ^ b ^ cin.

   end else begin

      localparam int wlo = w/2;
      localparam int whi = w - wlo;
      uwire plo, glo, phi, ghi;
      uwire chi = cin && plo || glo;

      cla_node #(wlo) lo(sum[wlo-1:0], plo,glo, cin, a[wlo-1:0],b[wlo-1:0] );
      cla_node #(whi) hi(sum[w-1:wlo], phi,ghi, chi, a[w-1:wlo],b[w-1:wlo] );

      assign p = plo && phi;
      assign g = glo && phi || ghi;
   end
endmodule
```

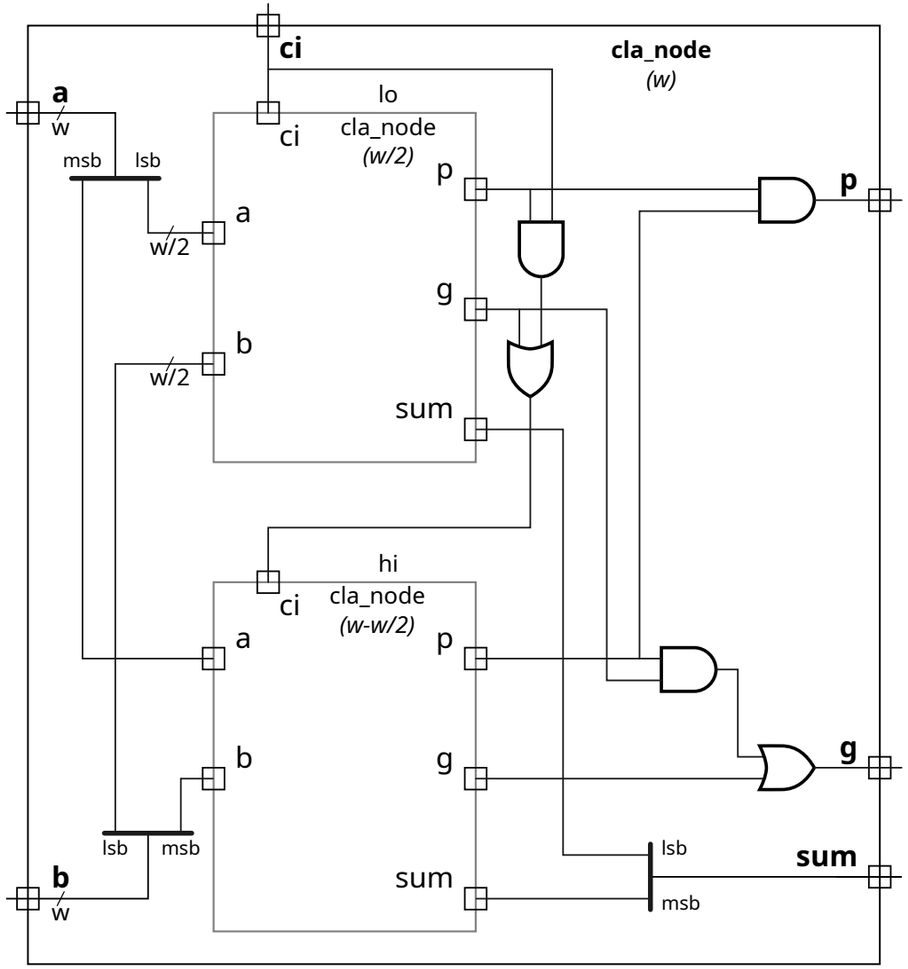

smod-28

Cost and Performance of w-bit CLA

Cost: $[6w + 5(w-1)]\,\mathrm{u_c} = [11w - 5]\,\mathrm{u_c}$.

Delay: $4\lceil \lg w \rceil\,\mathrm{u_t}$.

Comparison with Ripple Adder

Cost: Ripple $\approx 9w\,\mathrm{u_c}$, CLA $\approx 11w\,\mathrm{u_c}$.

Delay: Ripple $\approx 2w\,\mathrm{u_t}$, CLA $\approx 4\lg w\,\mathrm{u_t}$.

The CLA is significantly faster than a ripple adder while costing less than 25% more.

Cost and Performance with Constant Inputs

Constant Inputs

Input values which never change.

Cost and delay are radically different when an input never changes.

In Verilog, this might be an elaboration-time constant . . .
. . . or other expressions that never change.

Multiplexor Constant-Input Optimizations


Sample Mux Optimizations

Costs:

From top to bottom: $1\,u_c$, $1\,u_c$, $0\,u_c$.

Delays:

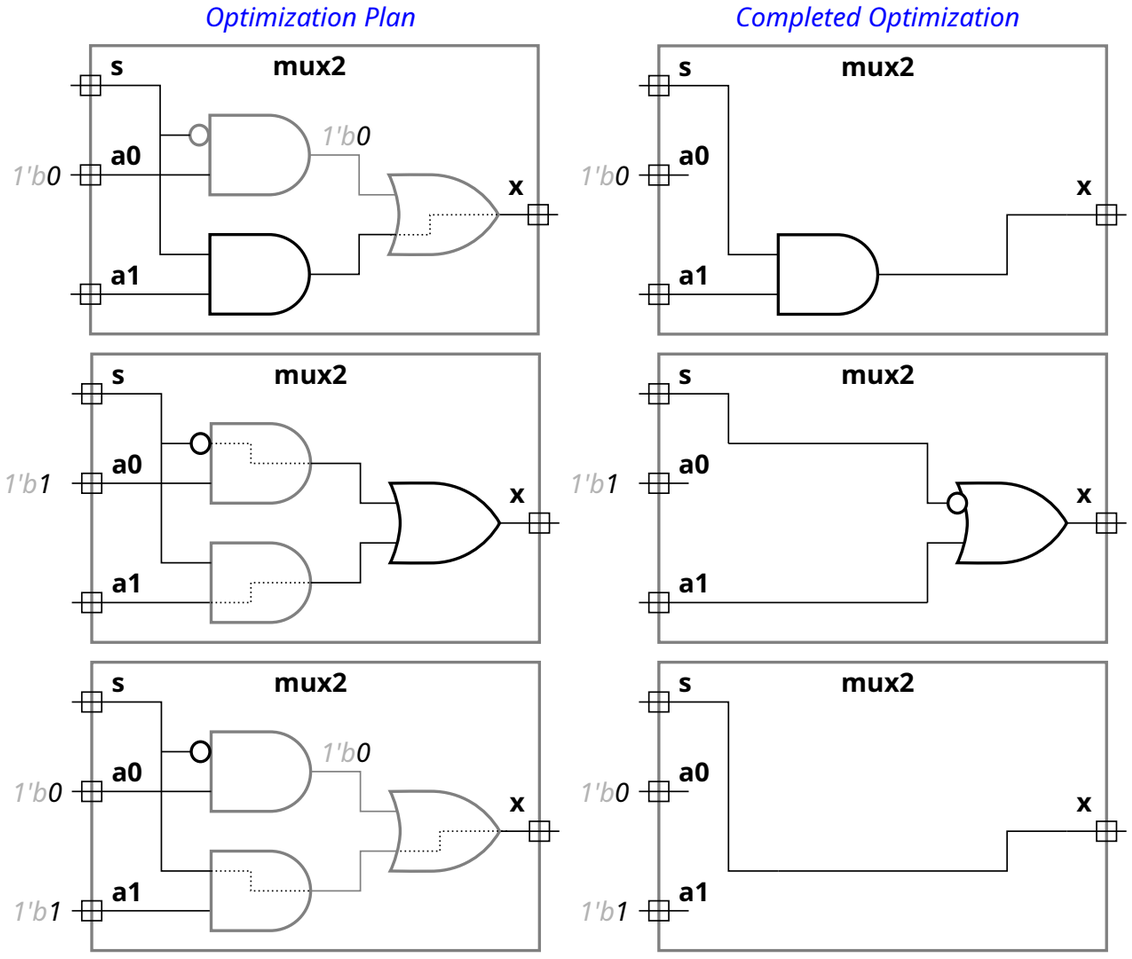From top to bottom: $1\,u_t$, $1\,u_t$, $0\,u_t$.




smod-31

Comparison Unit Constant-Input Optimization

Consider `a == b` where . . .
. . . `a` is an input . . .
. . . and `b` is a constant, `8b'1011001`.

Cost for w-bit comparison to constant: $\lceil w-1 \rceil \, \mathrm{u_c}$.

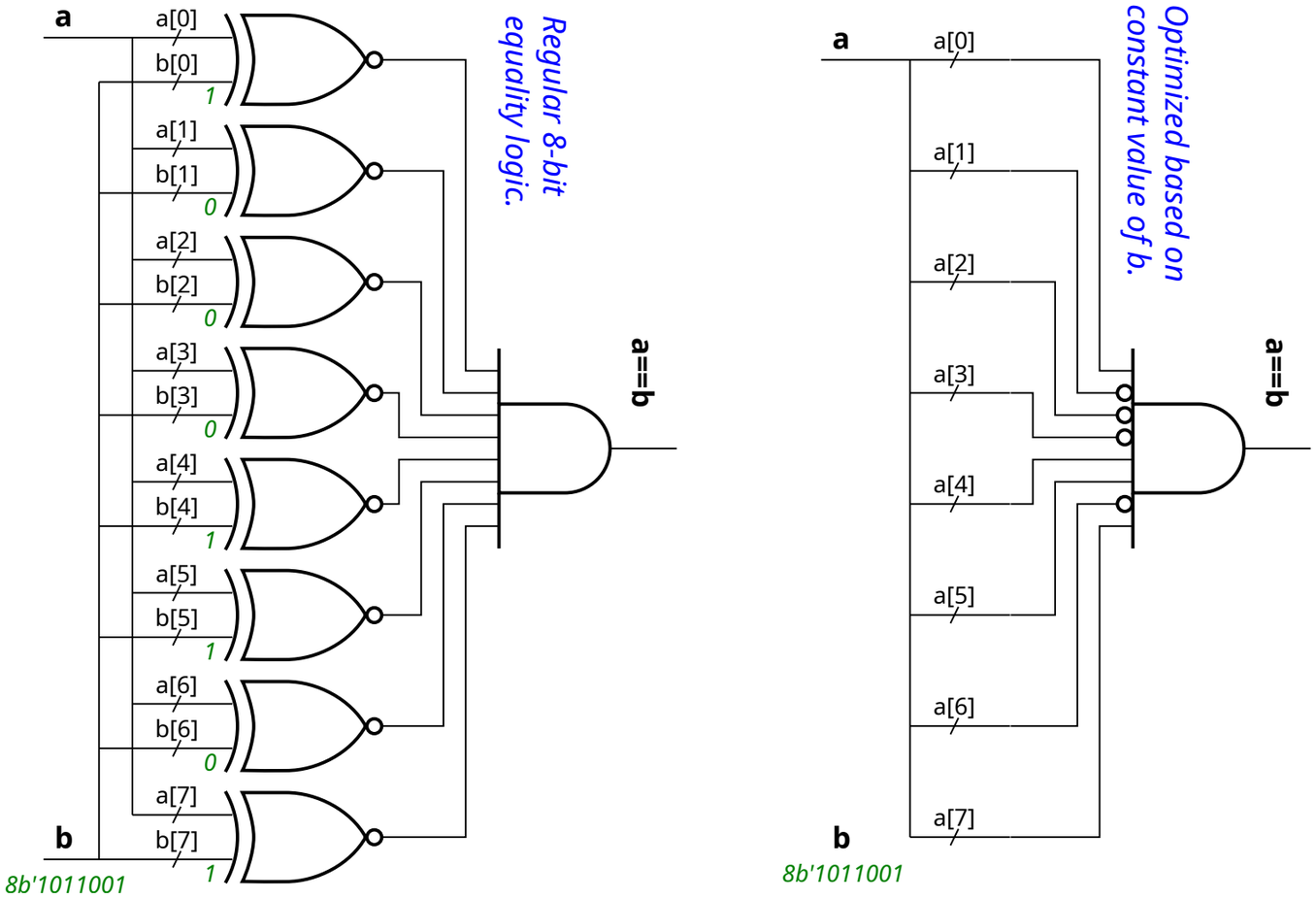Delay for w-bit comparison to constant: $\lceil \lg w \rceil \, \mathrm{u_t}$.



smod-32


Ripple Adder Constant-Input Optimization

Plan:

First, find cost and delay of BFA modules with one constant input ...
... one of which is equivalent to a *binary half adder (BHA)*.


Then, look at cost of ripple adder.

Binary Full Adder (BFA) Optimization

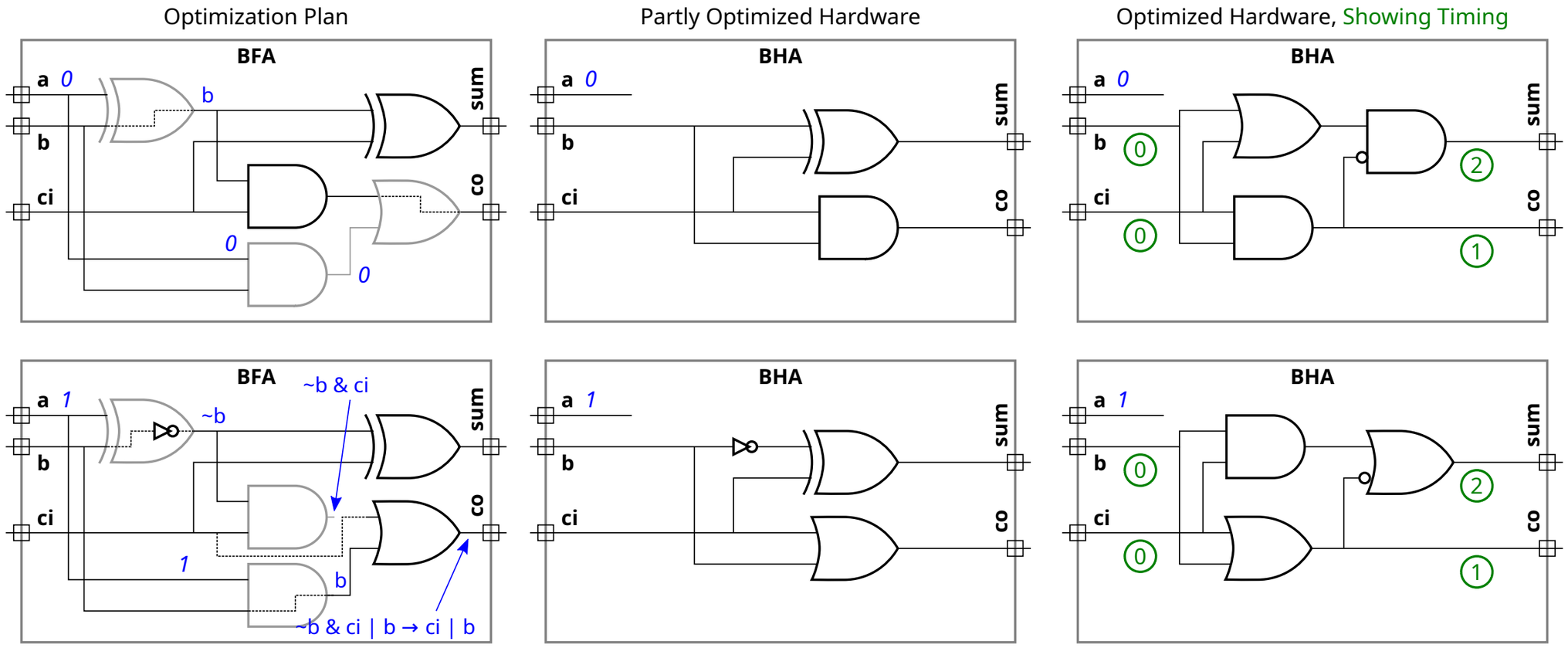

Cost of BHA (optimized BFA): $3\,u_c$. Delay of sum $2\,u_t$. Delay of carry $1\,u_t$.

smod-34

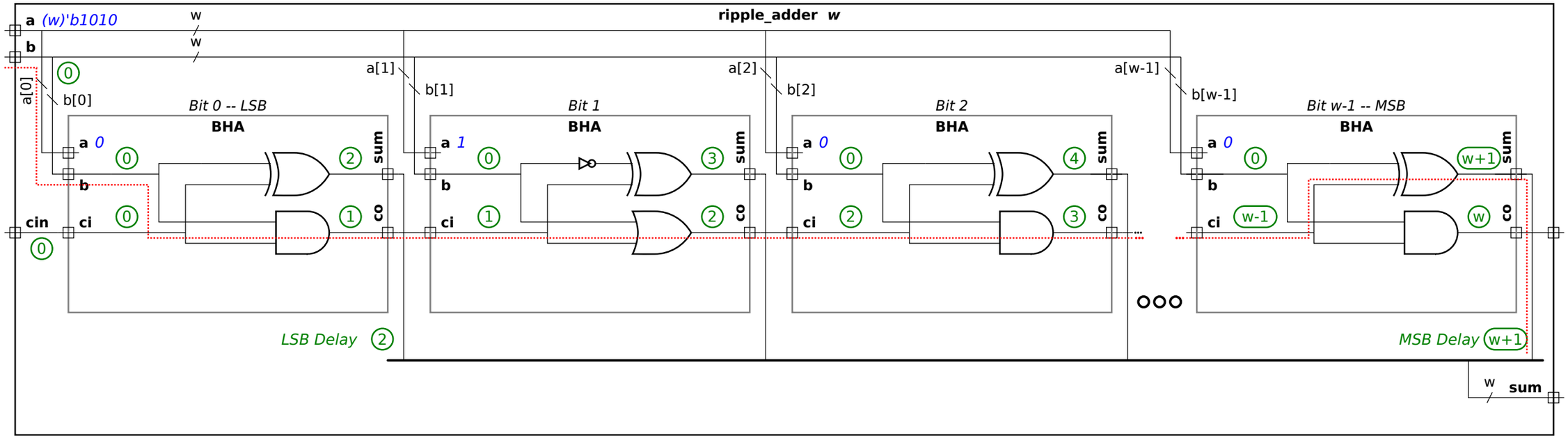
ripple_adder w
a (w)'b1010
b
w
w
a[0]
b[0]
a[1]
b[1]
a[2]
b[2]
a[w-1]
b[w-1]
Bit 0 -- LSB
Bit 1
Bit 2
Bit w-1 -- MSB
BHA
a 0
a 1
b
cin
ci
co
sum
LSB Delay 2
MSB Delay w+1
w
sum

smod-35